

# Calorimeter Upgrade Meeting

Analog Electronics  
COTS design

14/oct/2011



# COTS status

- Integrator Oscillations
- Measurements
  - Input Stage
  - Clipping Stage
  - Integrating Stage
- Conclusions/Ideas

# Integrator Oscillations
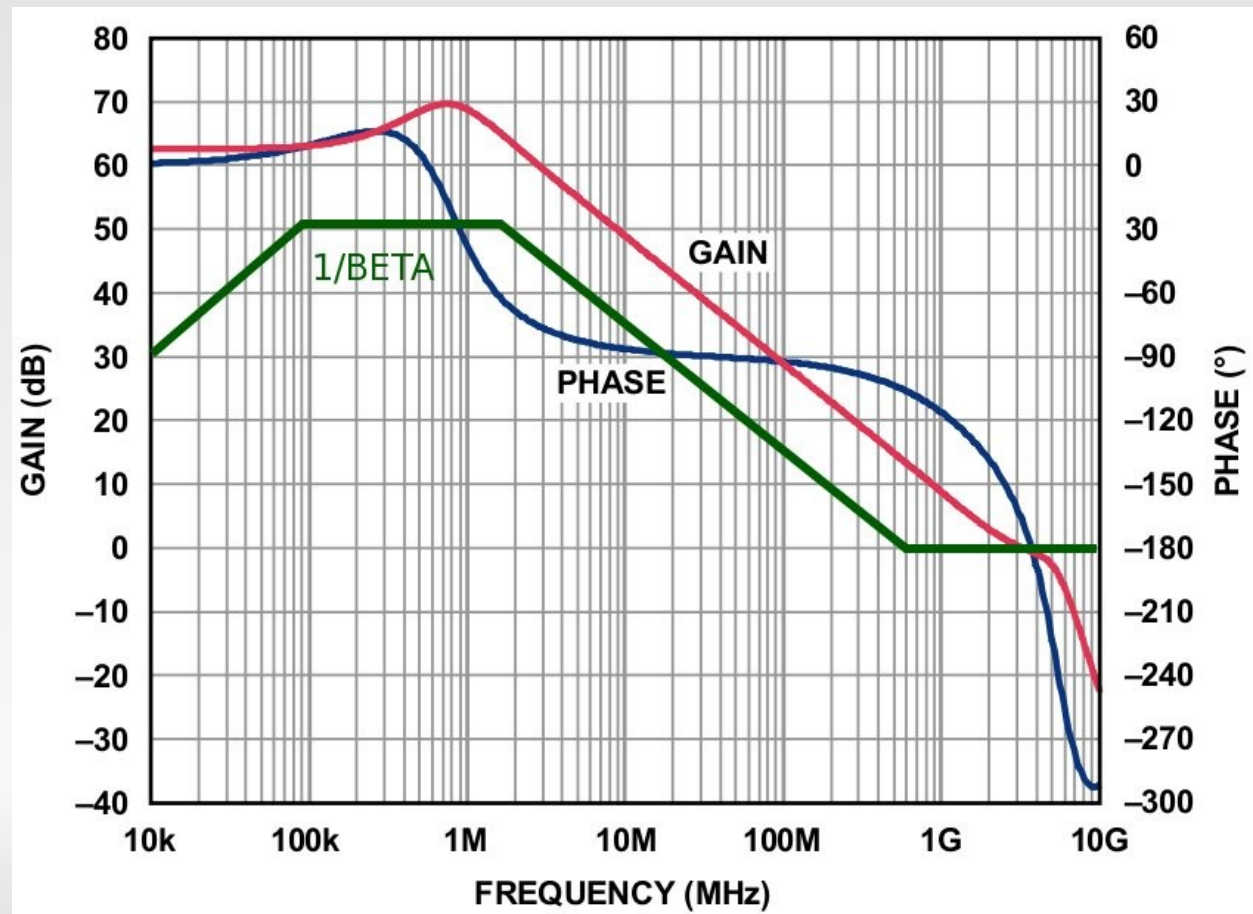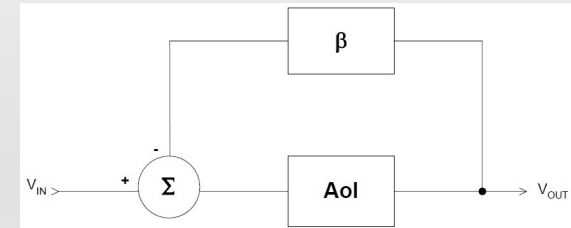
## Integrator Oscillations


- $A_{ol} \cdot \beta \neq -1 \rightarrow A_{ol} \neq -1/\beta$
- ADA4930
- Calculate  $1/\beta$  with all parasitic effects
- Nearly No Phase Margin


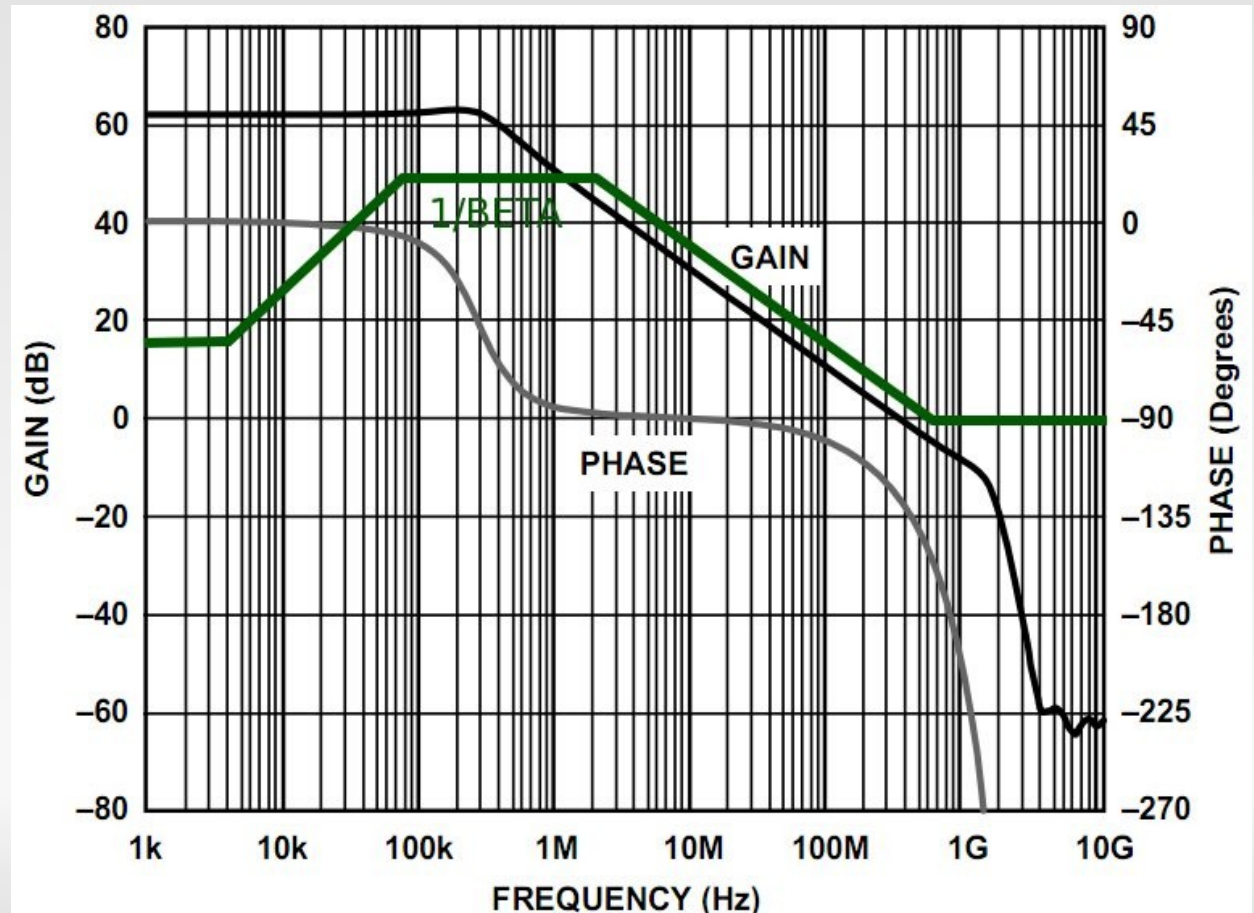
# Integrator Oscillations


Change for other model looking for stability...

- ADA4932
- First Order Calculation OK!!
- Real Life Measure OK too (later shown)
- No more oscillations


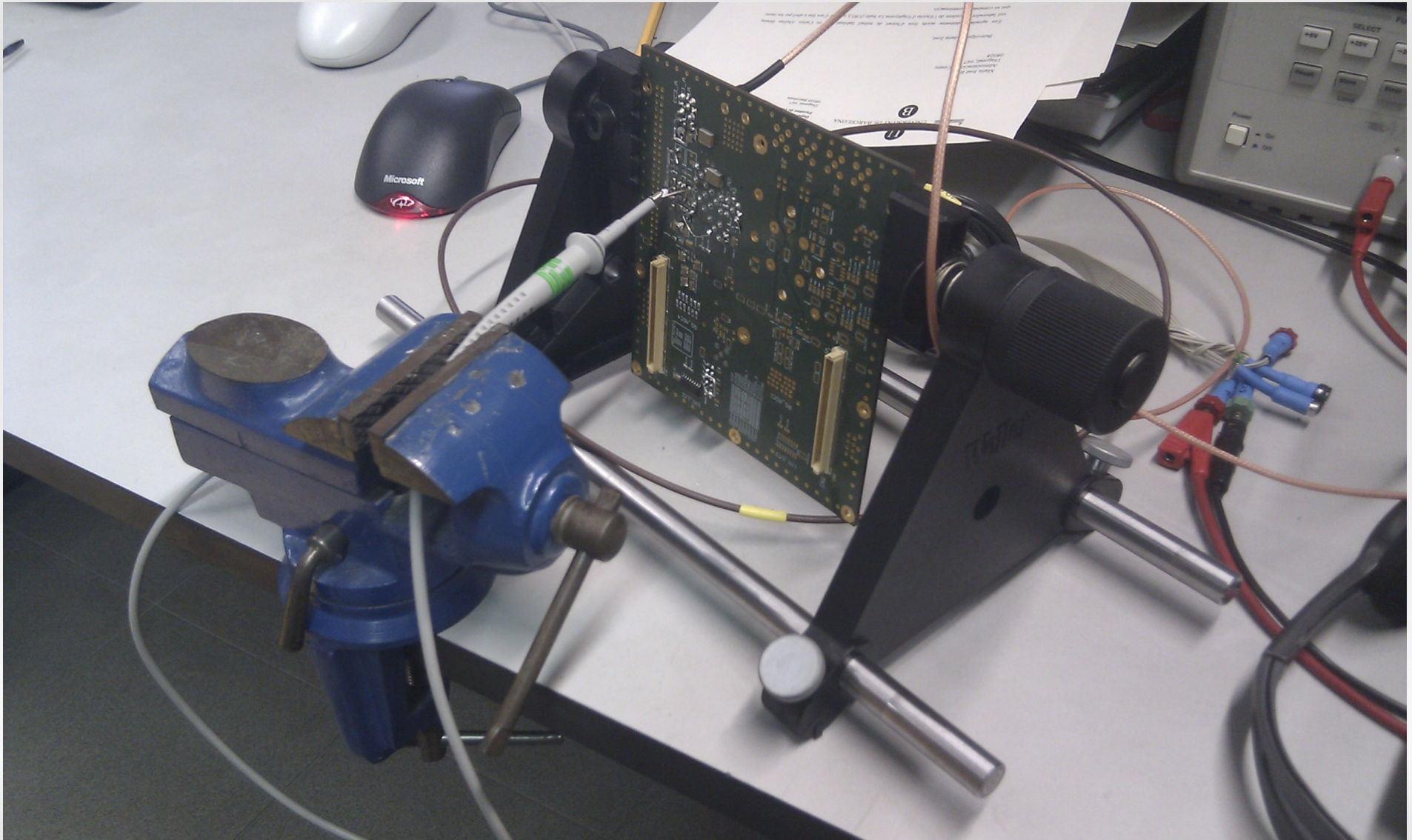
# Measurements

- No oscillations → Continue work → Measurements






# Measurements

# INPUT STAGE


- Input Stage Measurements

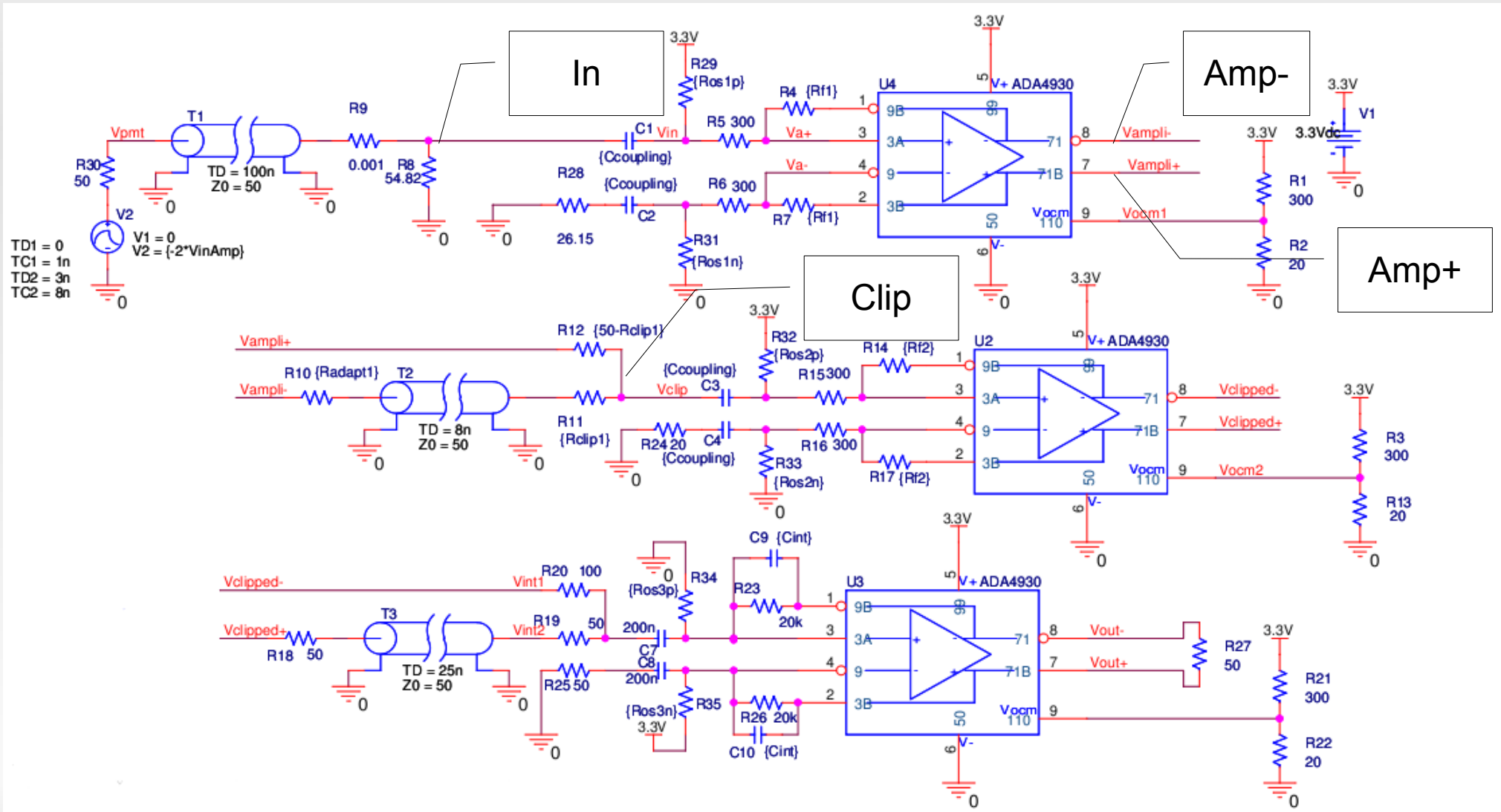

# Measurements

# INPUT STAGE


- Input RAW DATA

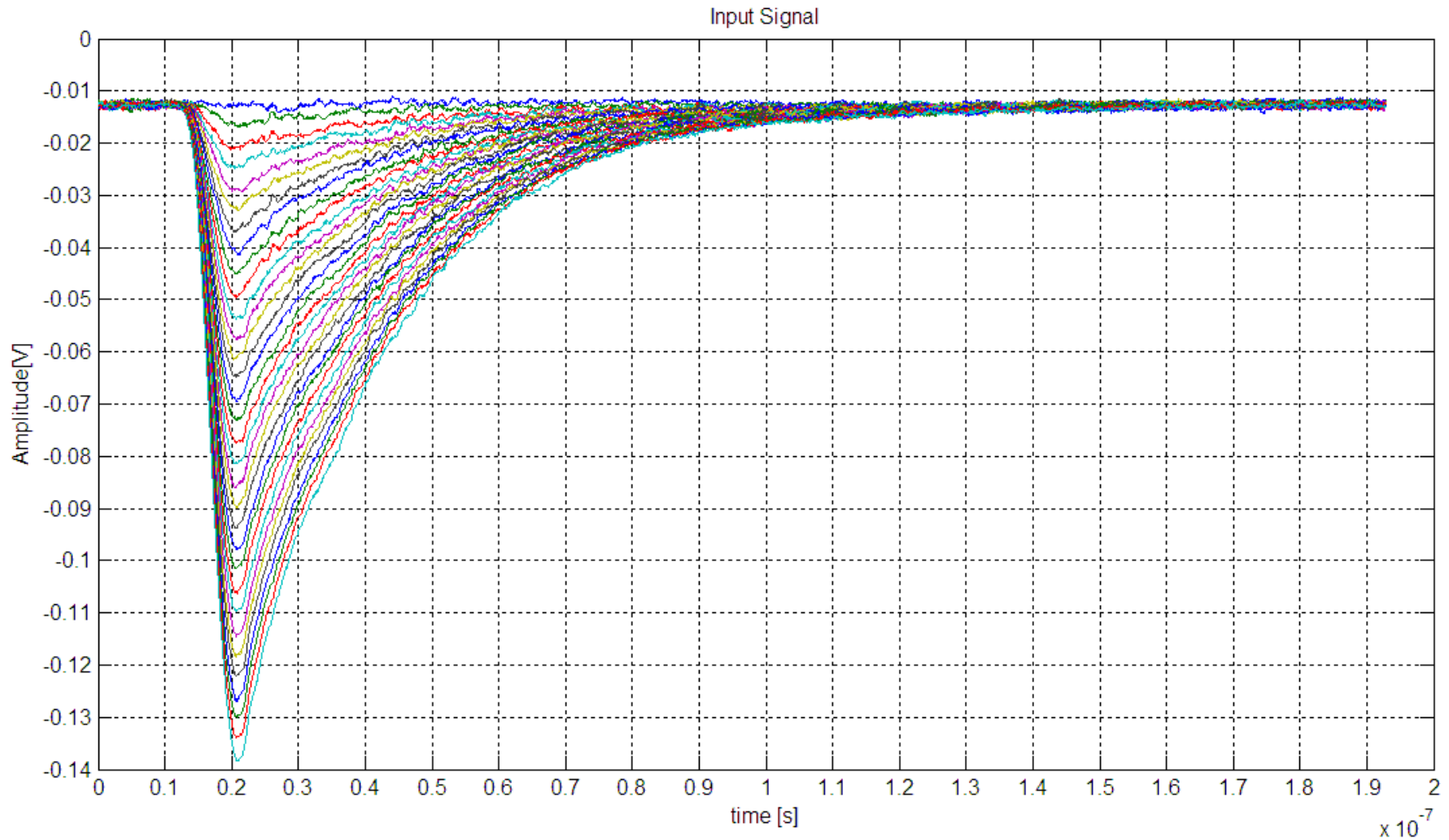

# Measurements

# INPUT STAGE

- Input Normalized (SHAPE)

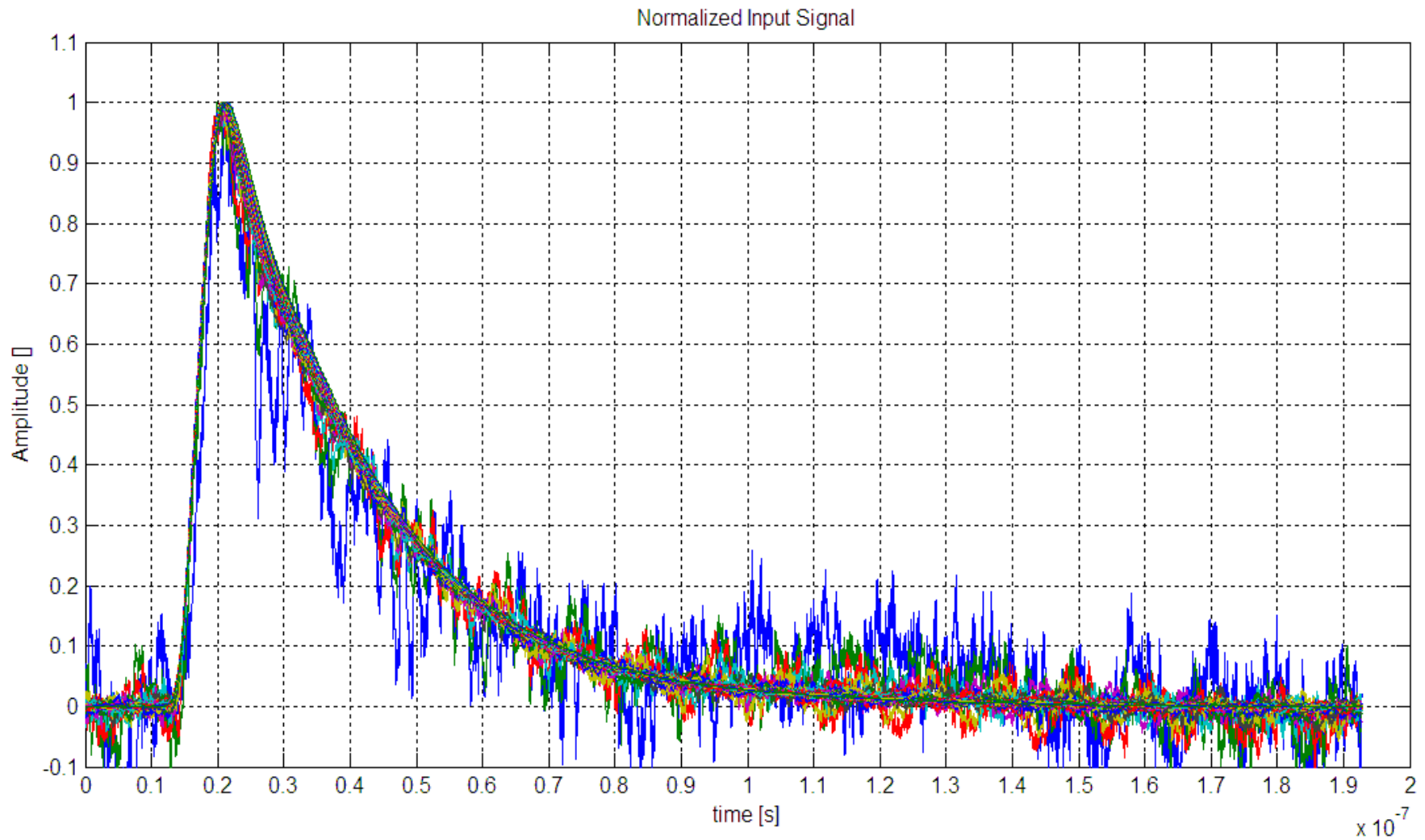




# Measurements

# INPUT STAGE


## Input Linearity

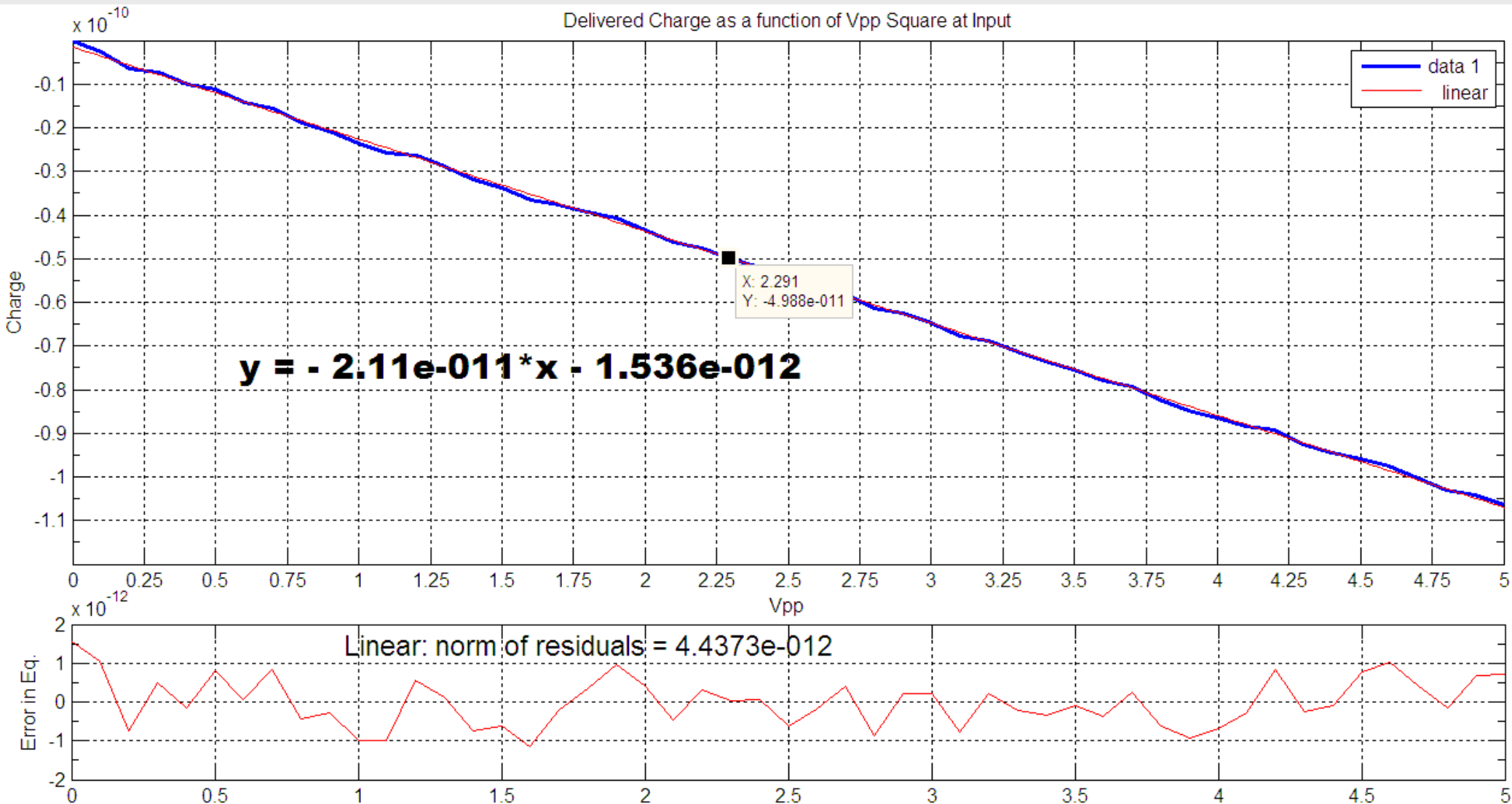

# Measurements

# INPUT STAGE


- AMP- RAW DATA

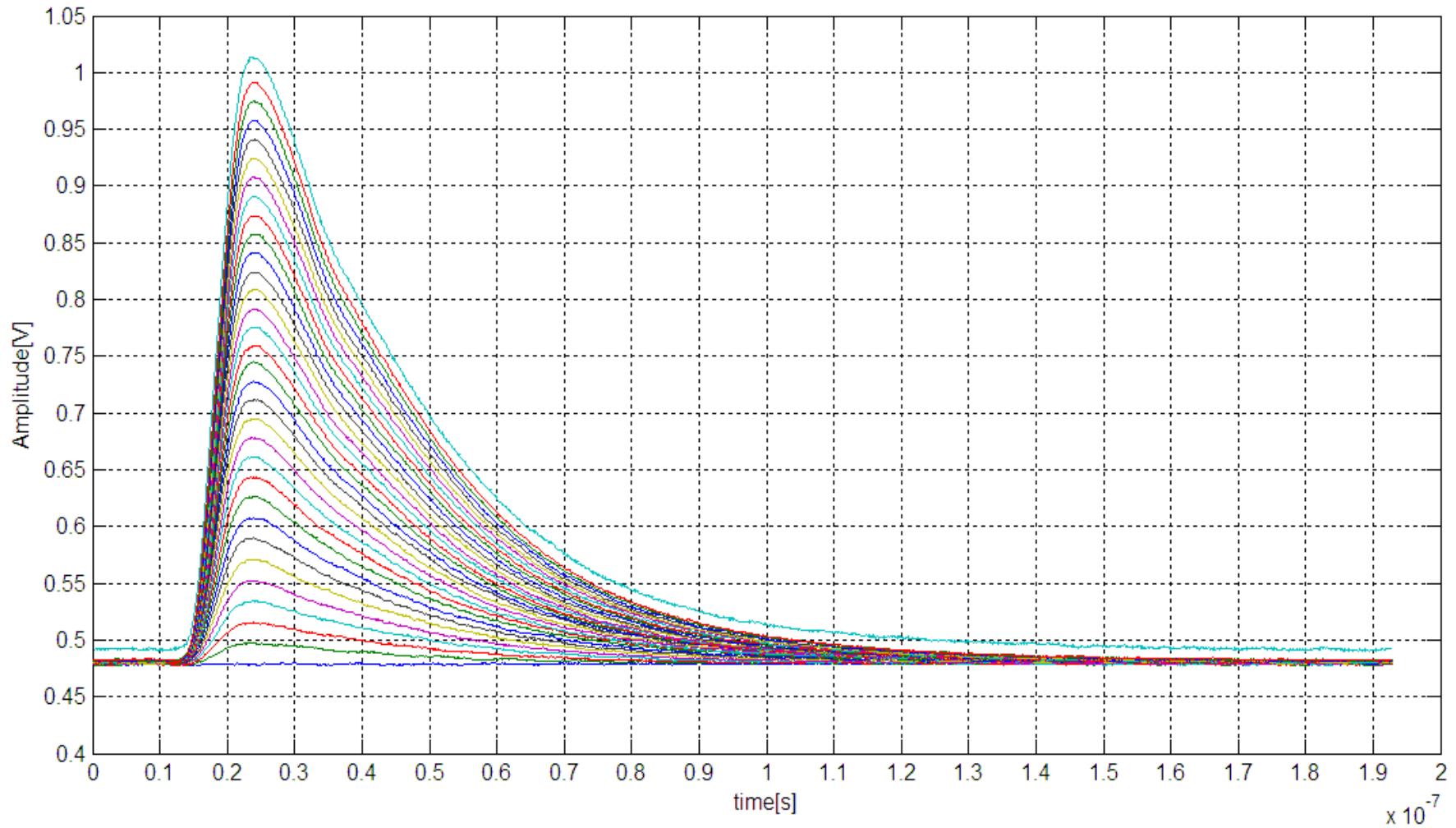

# Measurements

# INPUT STAGE


- AMP+ RAW DATA

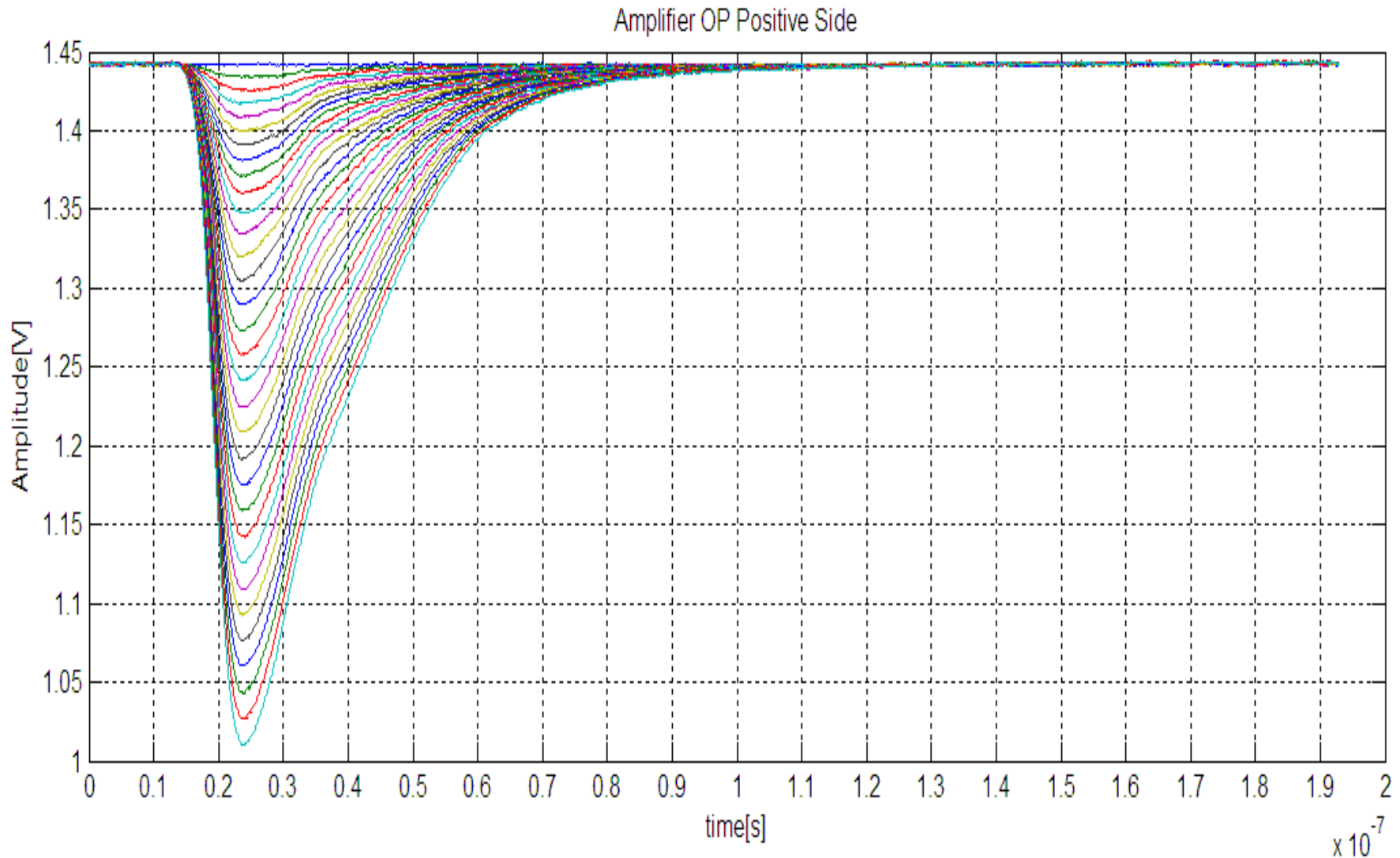

# Measurements

# INPUT STAGE

- CLIP RAW DATA

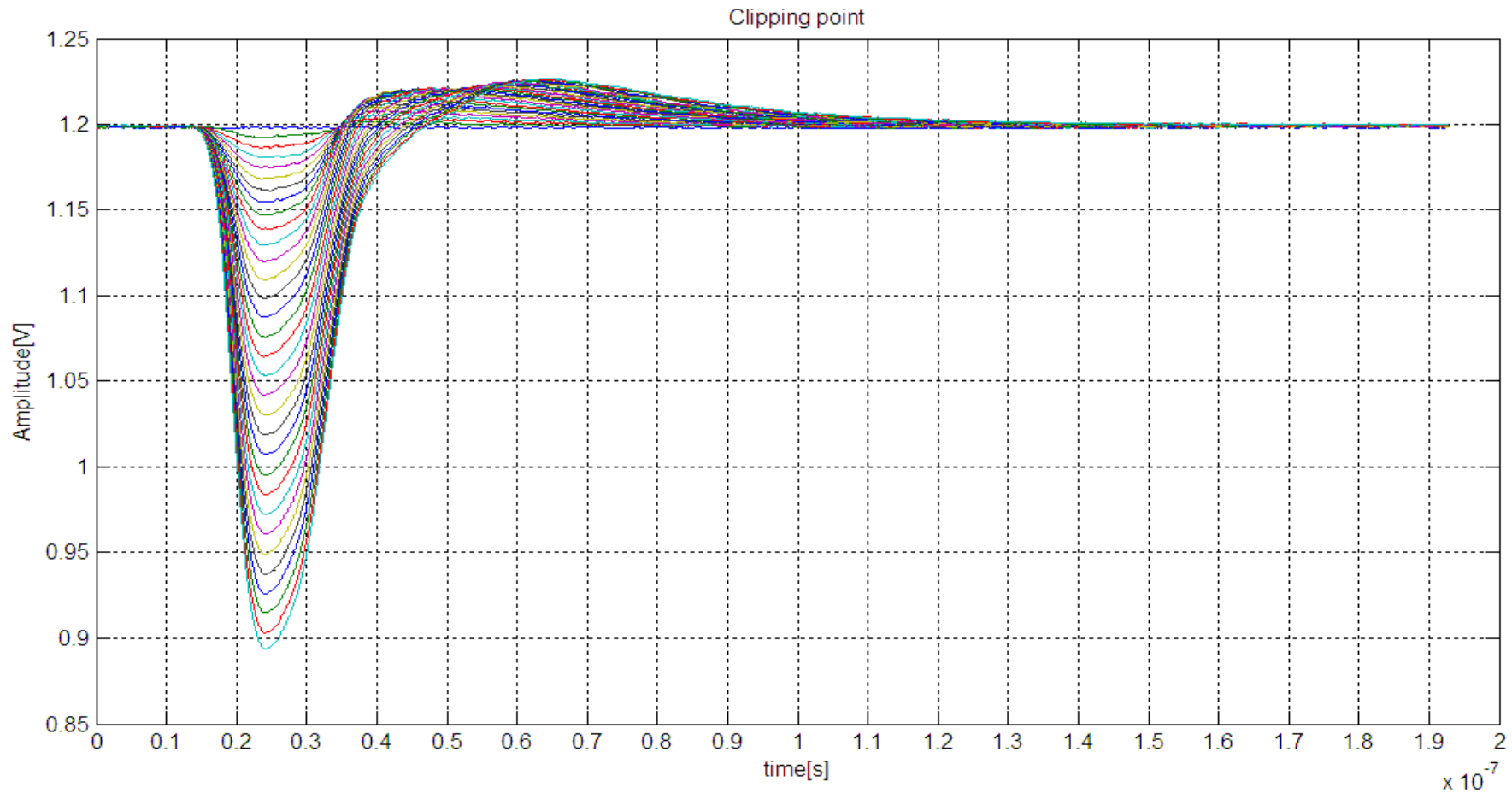


- ¿? Why Undershoot? ( $RC=50 \cdot 200n=1\mu s$ )

# Measurements

# INPUT STAGE

- CLIP Normalized (SHAPE)

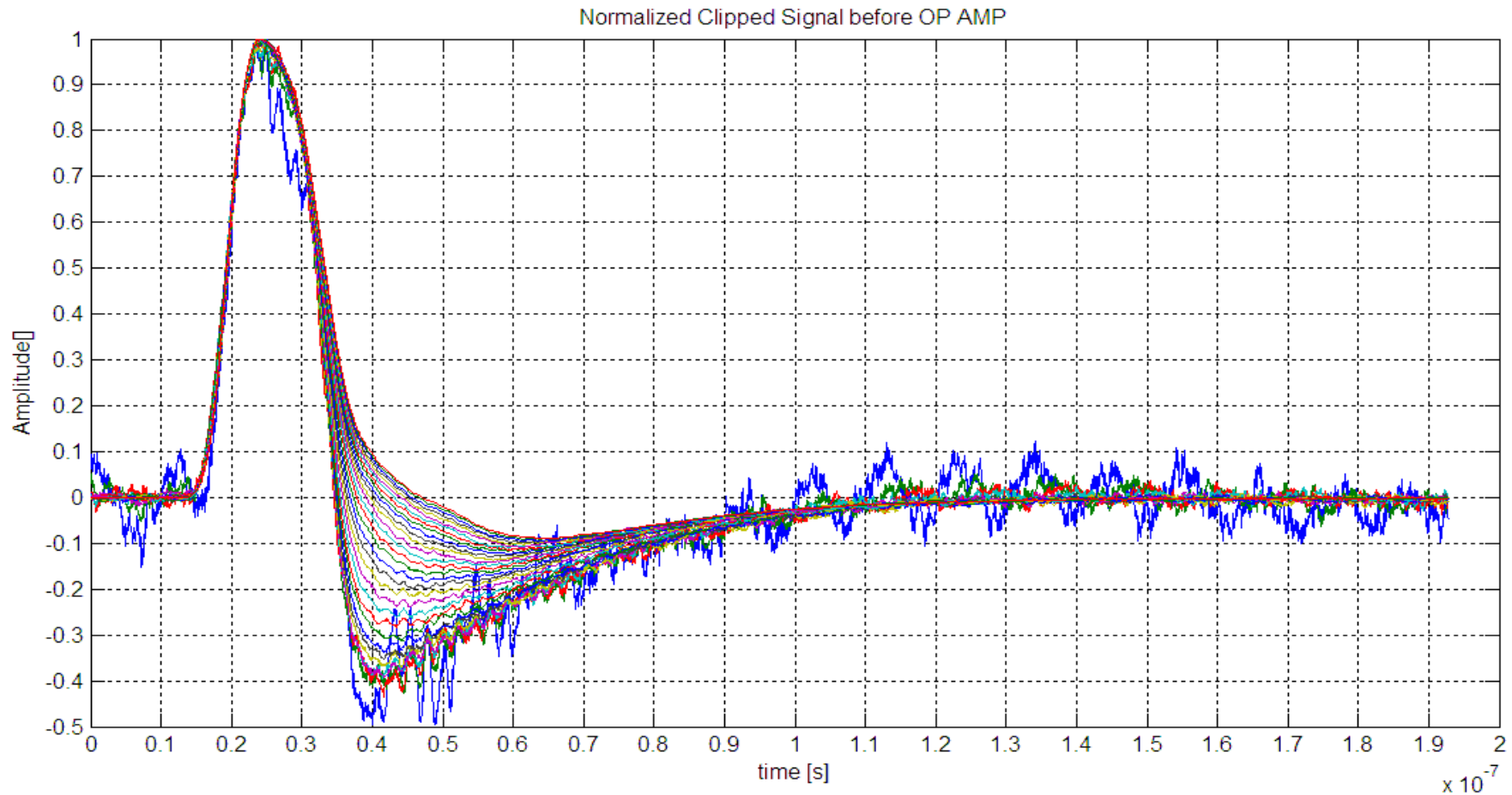


- Undershoot increases when amplitude decreases  $\rightarrow \zeta$ ?
- Let's have a closer look to AMP+ and AMP- at  $0.4E-7s$



# Measurements

# INPUT STAGE

- AMP- Normalized (SHAPE)


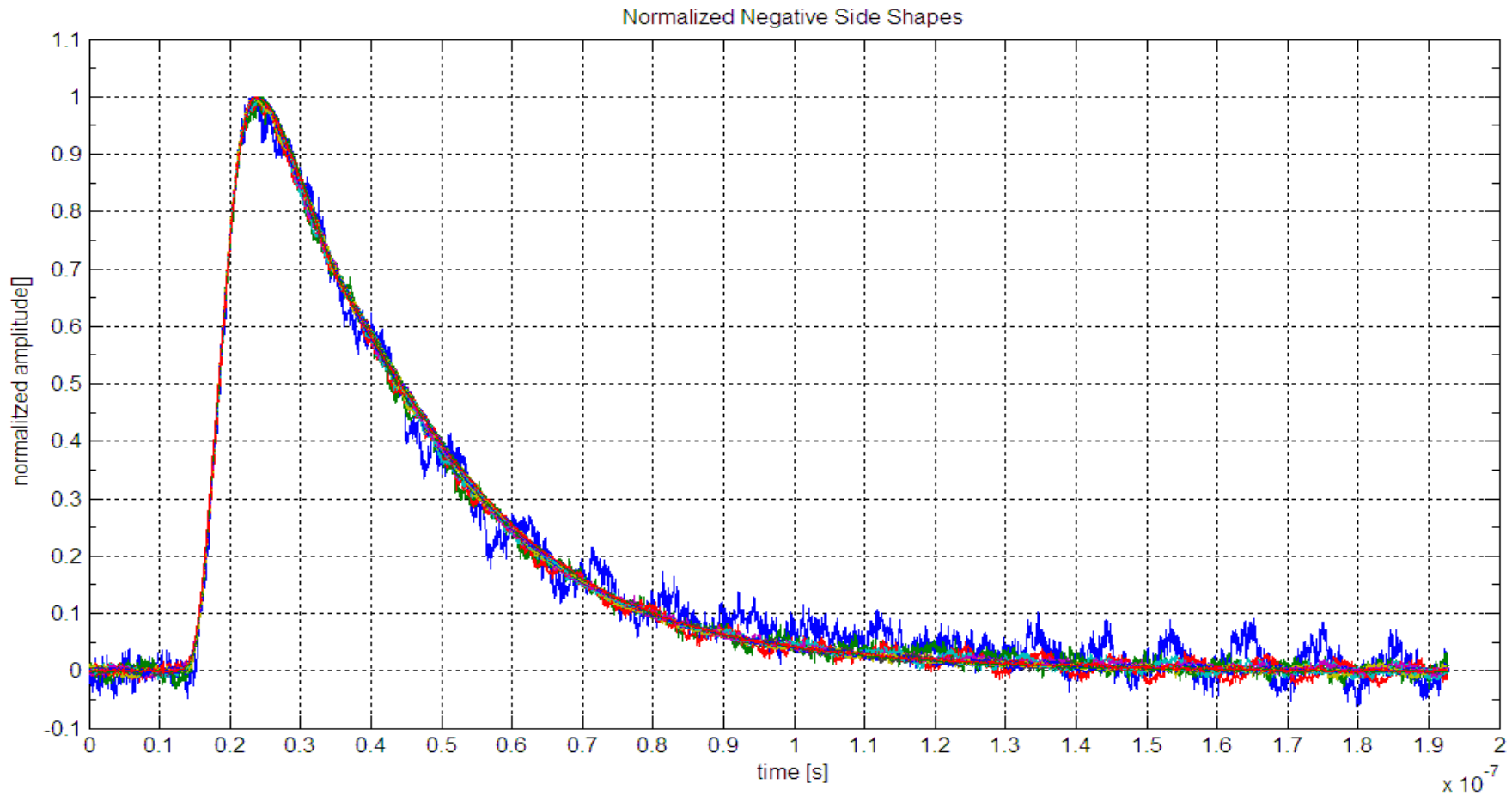


- Looks good

# Measurements

# INPUT STAGE

- AMP+ Normalized (SHAPE)

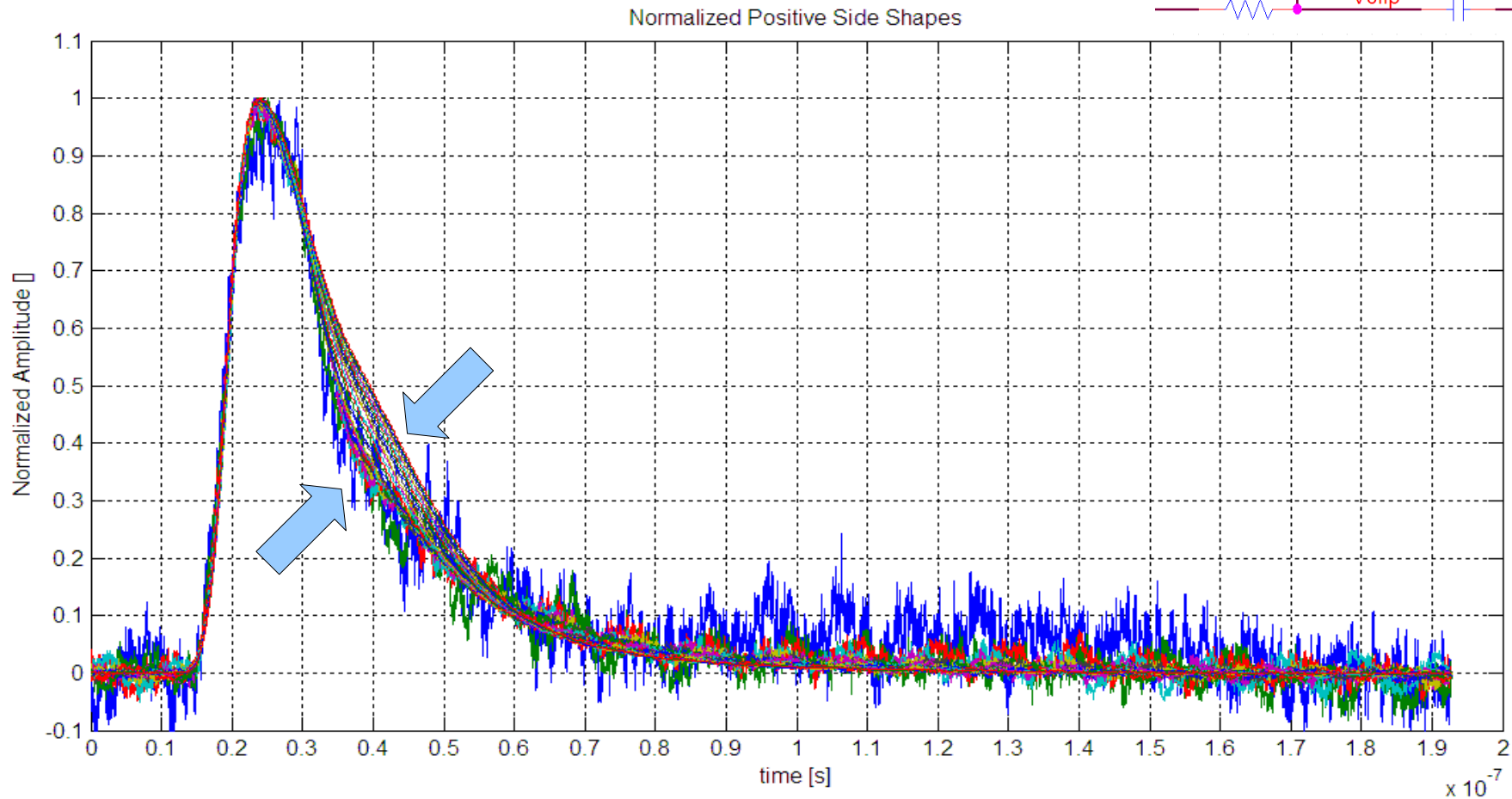
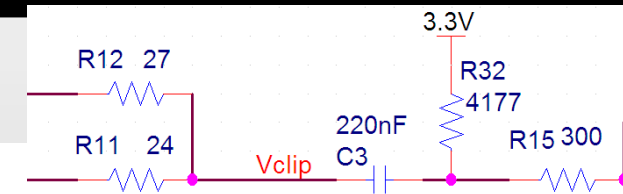


- Variations at  $0.4E-7s$  depending on amplitude
- Maybe because of RC differences?

# Measurements

# INPUT STAGE

- IN, AMP+, AMP- Normalized (SHAPE)

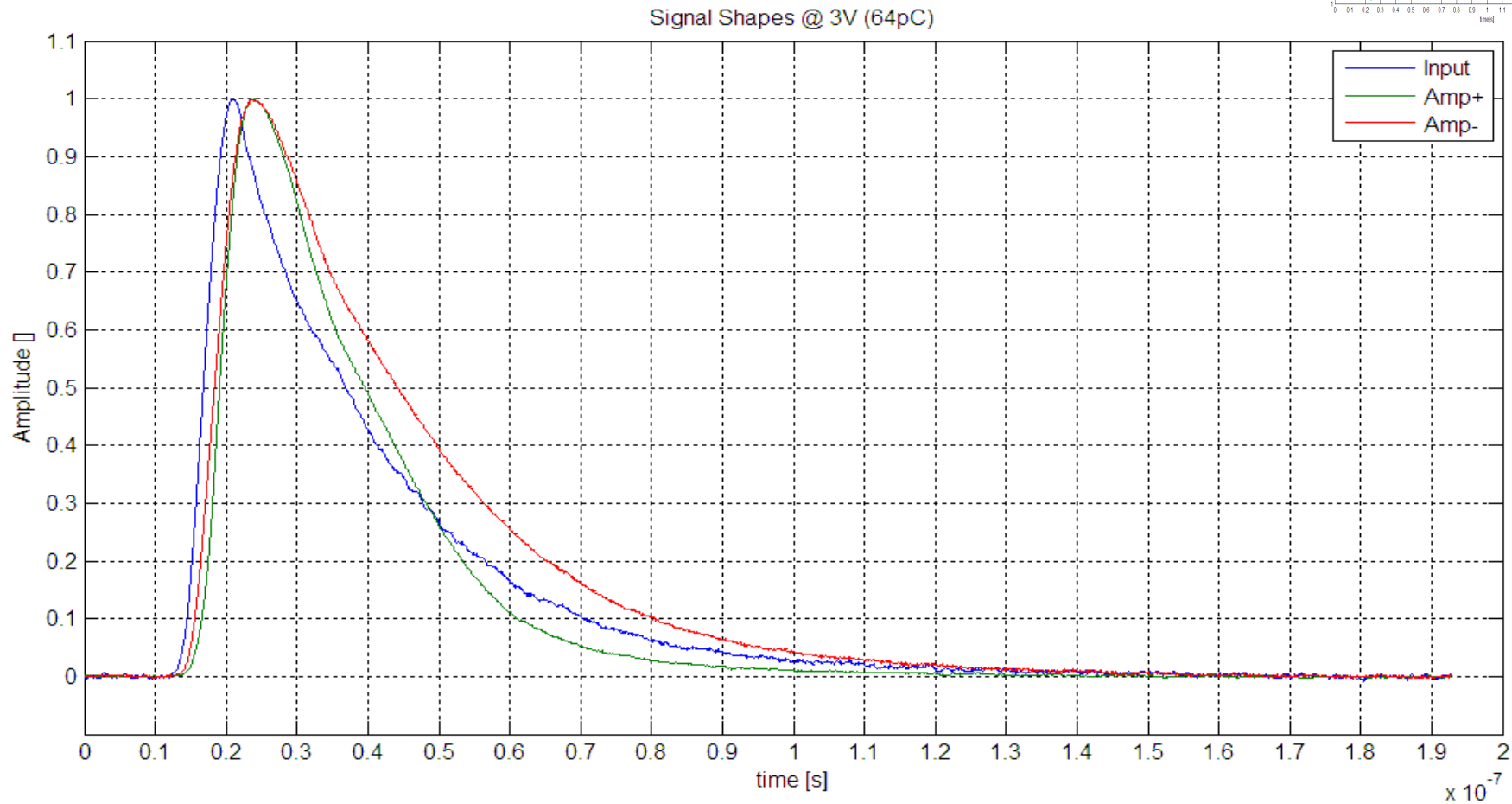
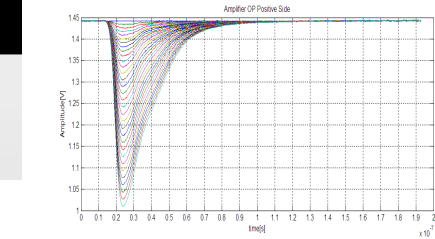


- Different shapes of AMP+ and AMP-
- Ideal (Simulated) clipping with these shapes → measured result

# Measurements
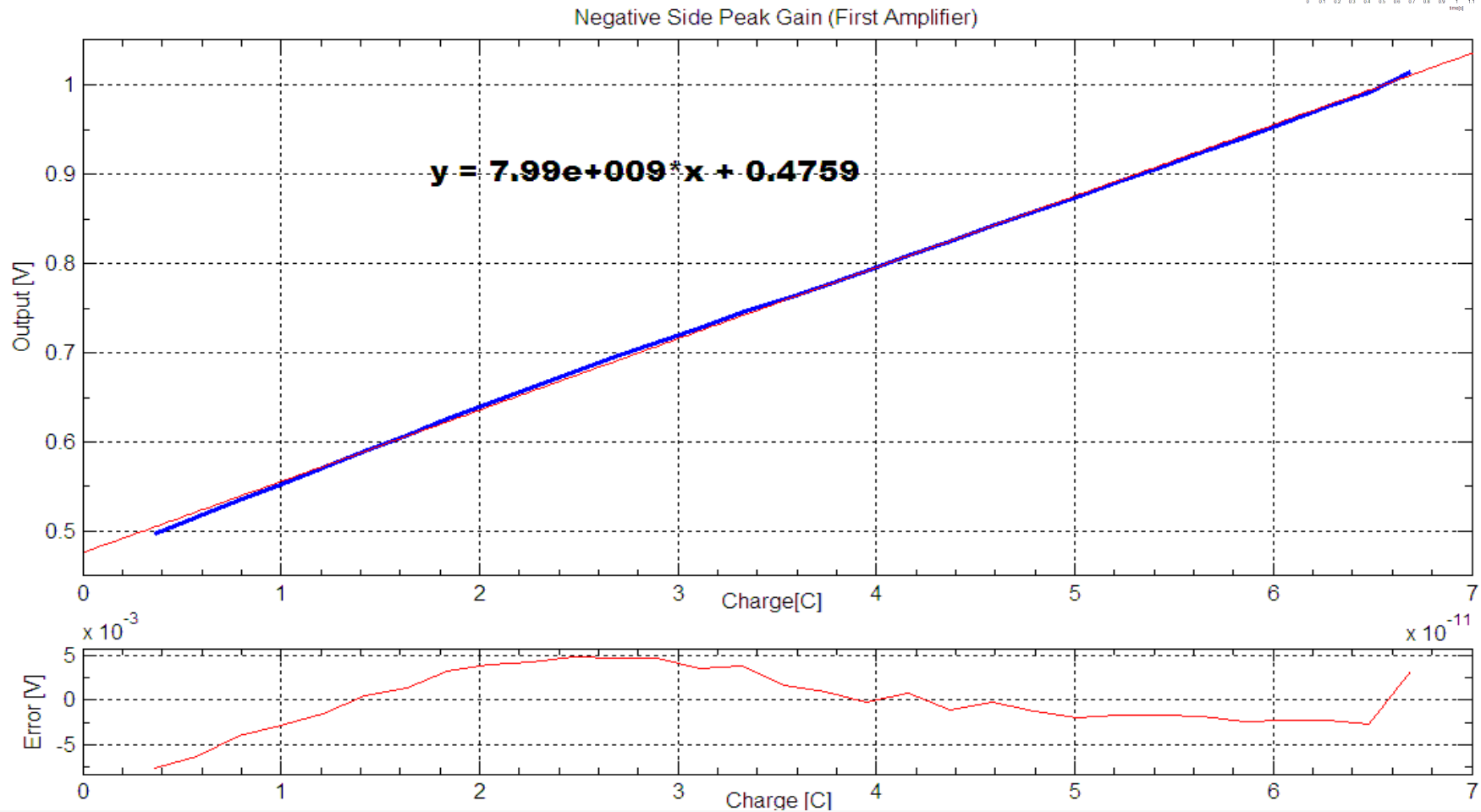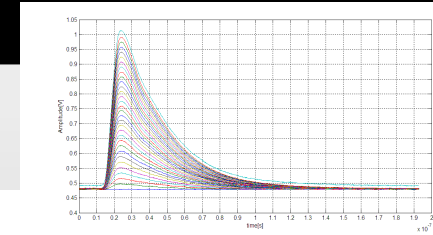
# INPUT STAGE

- AMP- Transfer Function MAX\_Out(Charge\_in)





- Looks good, although 0.4759 is a bit low
- Error about  $5E-3/5E-1 * 100 = 1\%$  (Compatible with IN precision)

# Measurements
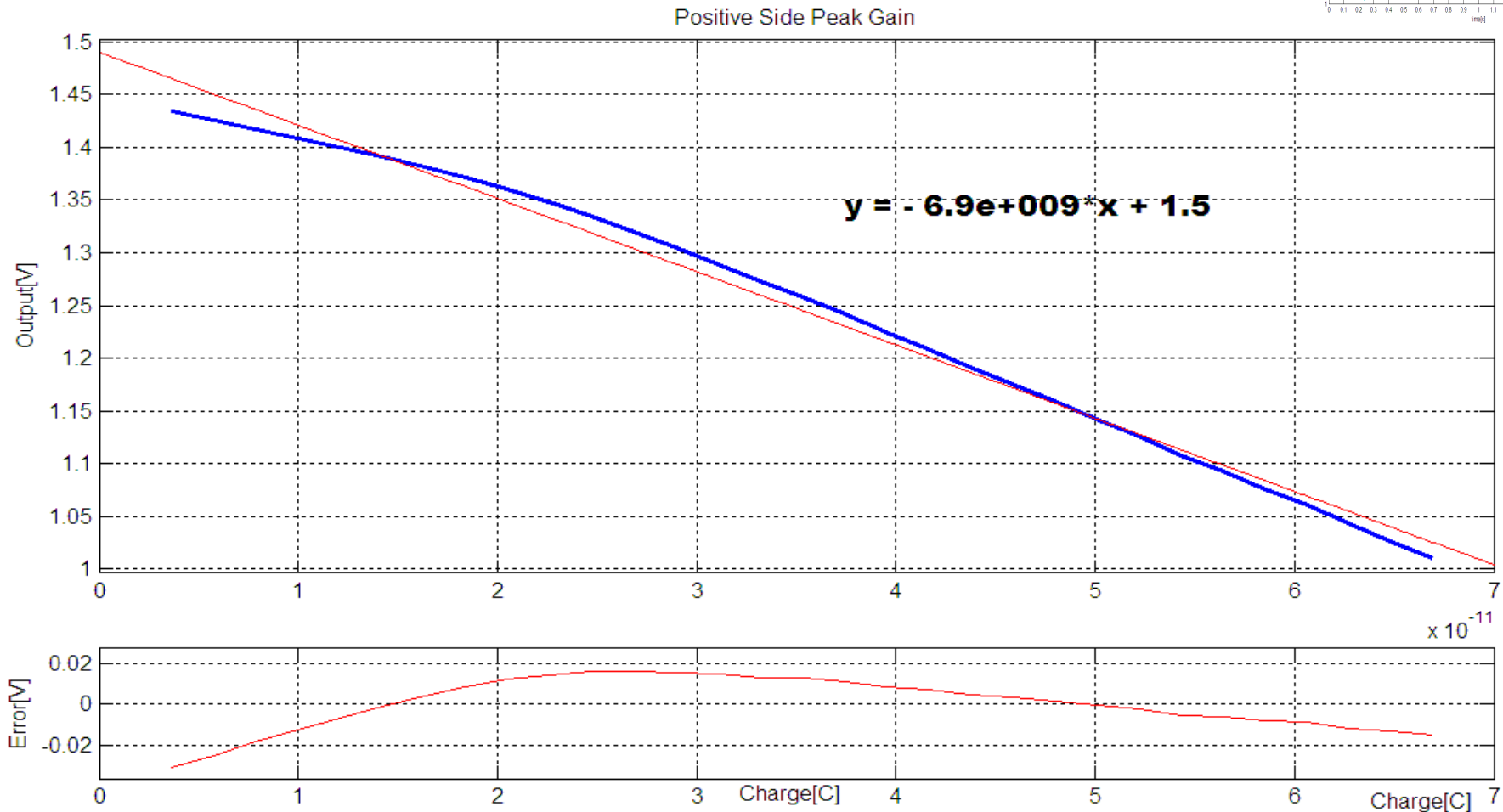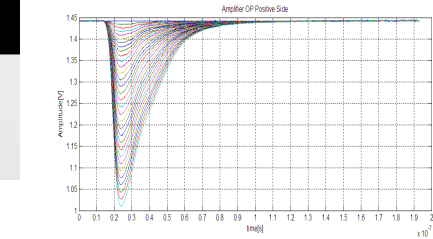
# INPUT STAGE

- AMP+ Transfer Function MAX\_Out(Charge\_in)





- Linearity wrong
- Linear regression useless (need to exclude conflictive zone)



# Measurements
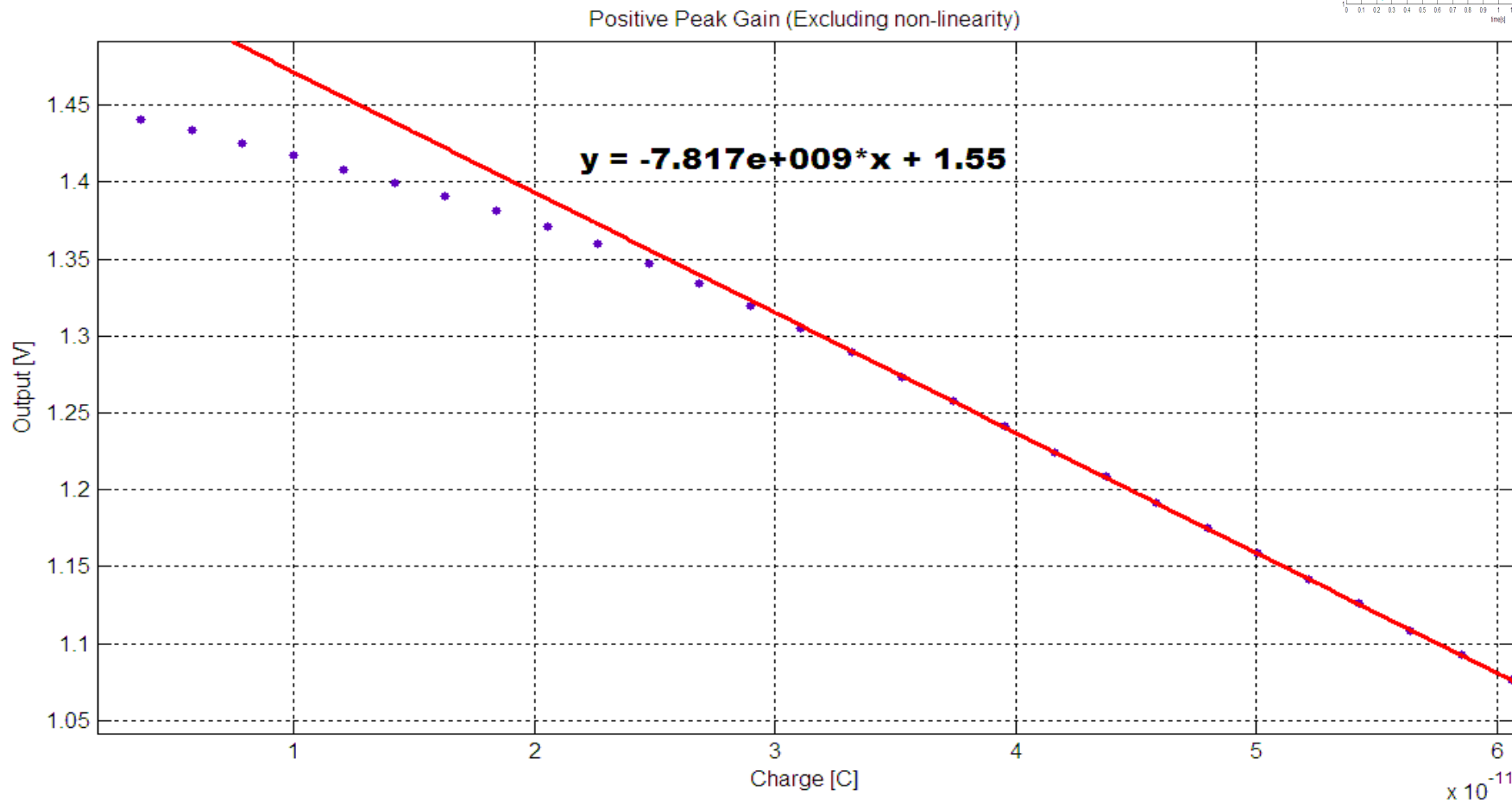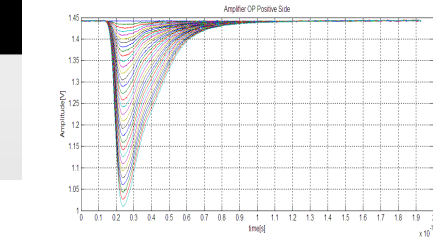
# INPUT STAGE


- AMP+ Transfer Function MAX\_Out(Charge\_in)



- It would like to have a 1.55V at 0 input → too high! (Max=1.45)
- Related to different shapes? Two different errors?


# Measurements CLIPPING STAGE

- Input Stage Measurements

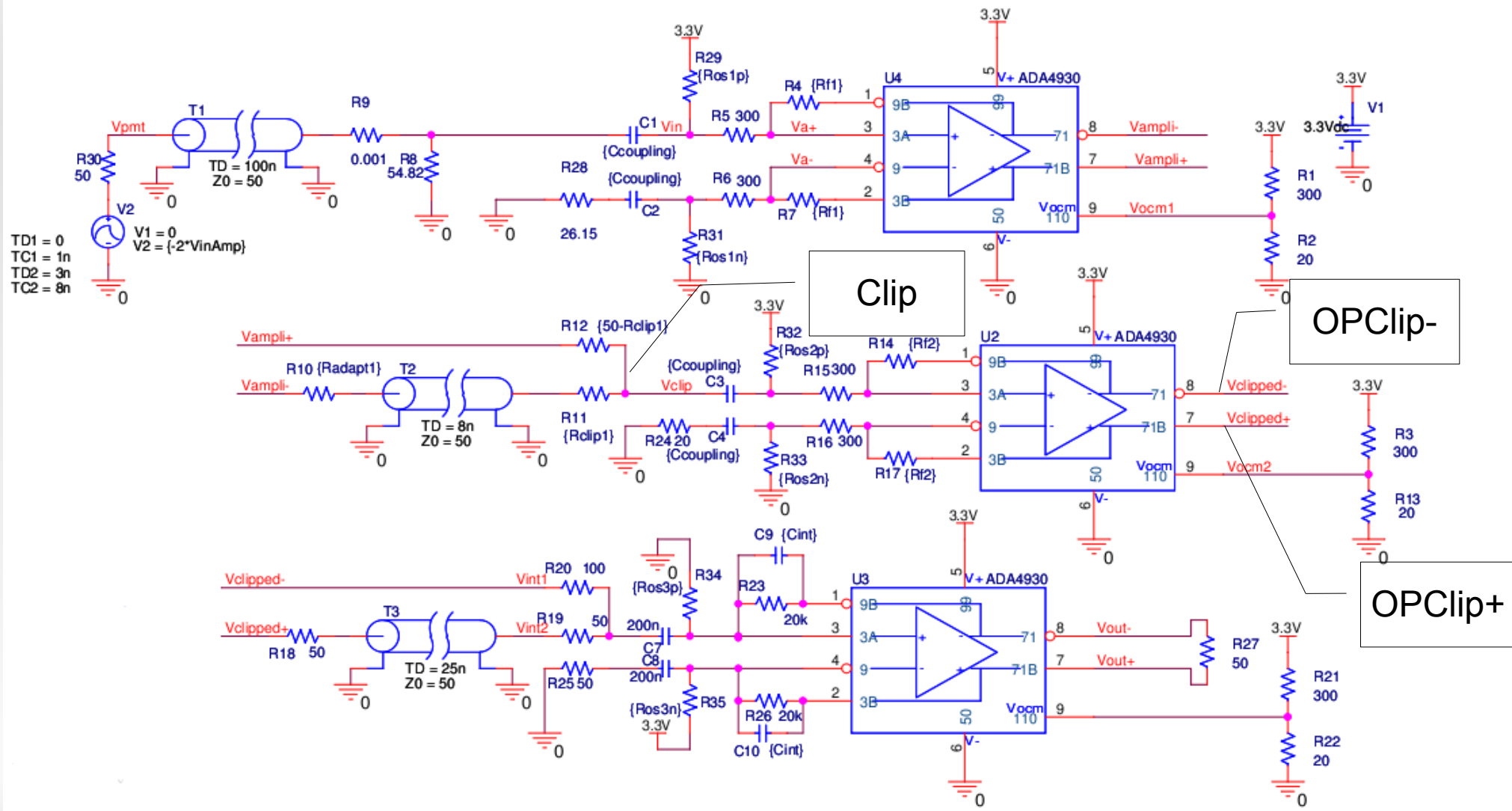

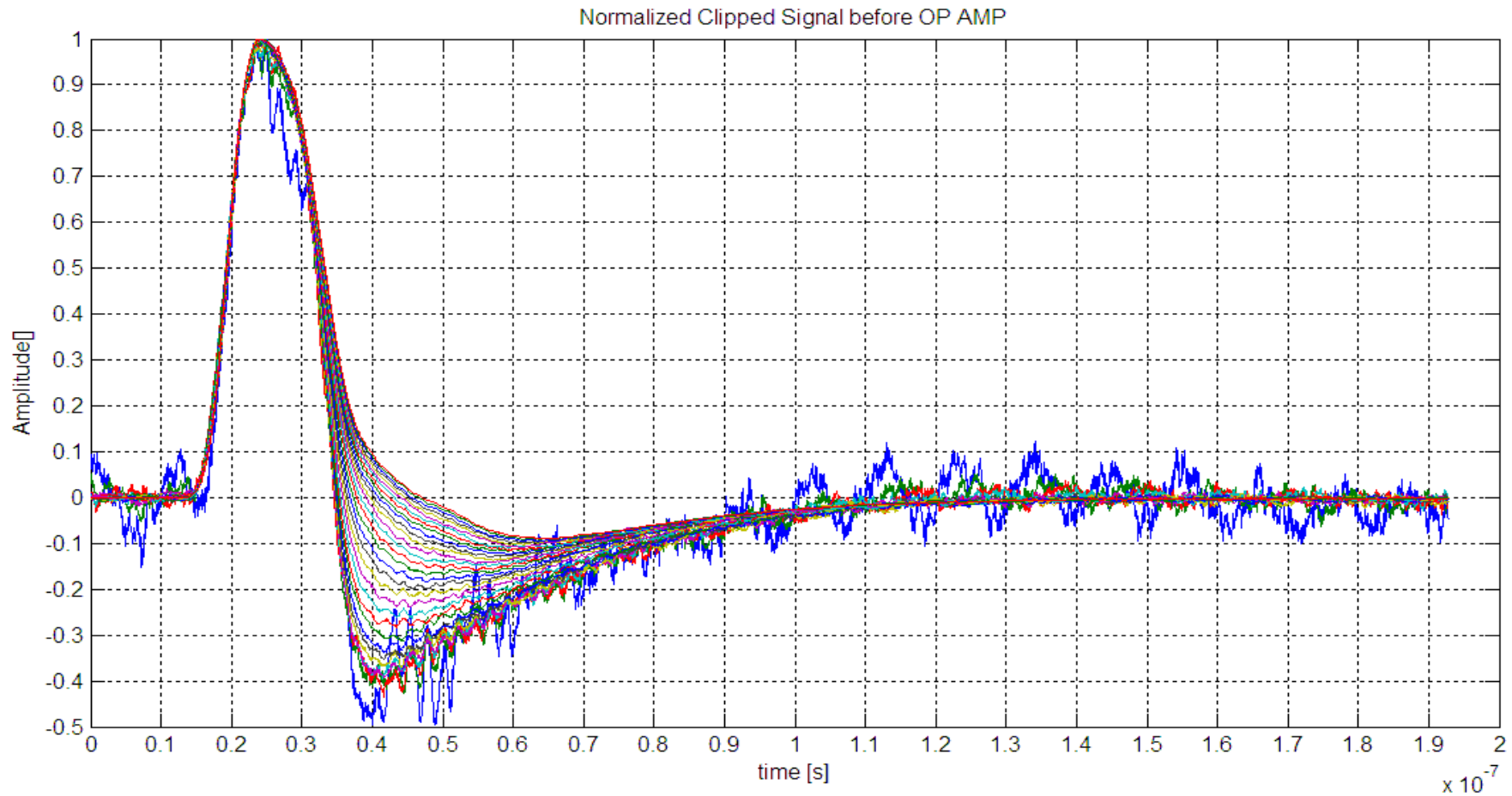
# Measurements CLIPPING STAGE

- Clip Signal Normalized (SHAPE) ← RECALLING



# Measurements CLIPPING STAGE


- OPClip- Normalized (SHAPE)

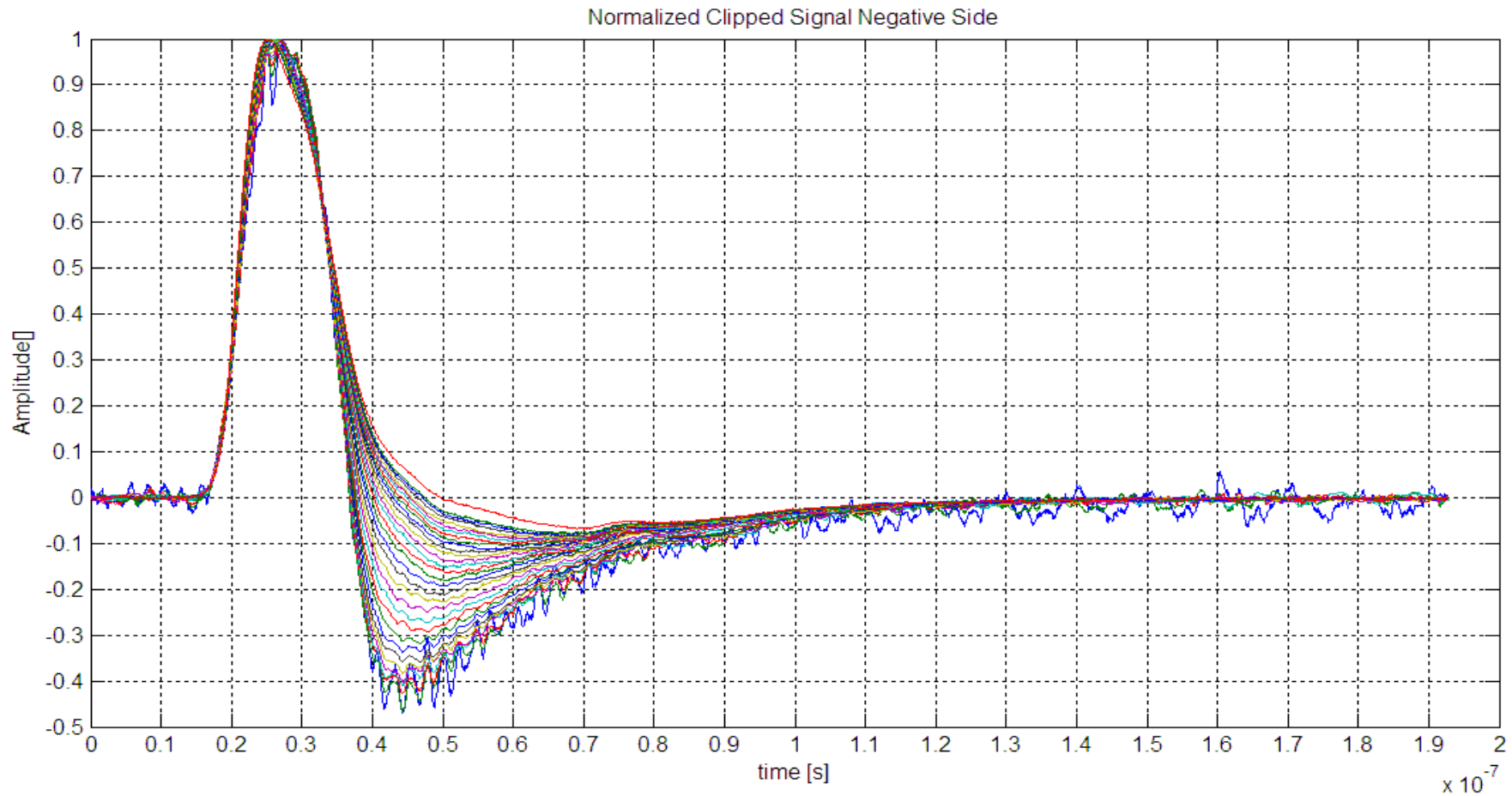

- Same Shape approx
- Linear to the eye

# Measurements CLIPPING STAGE

- OPClip+ Normalized (SHAPE)

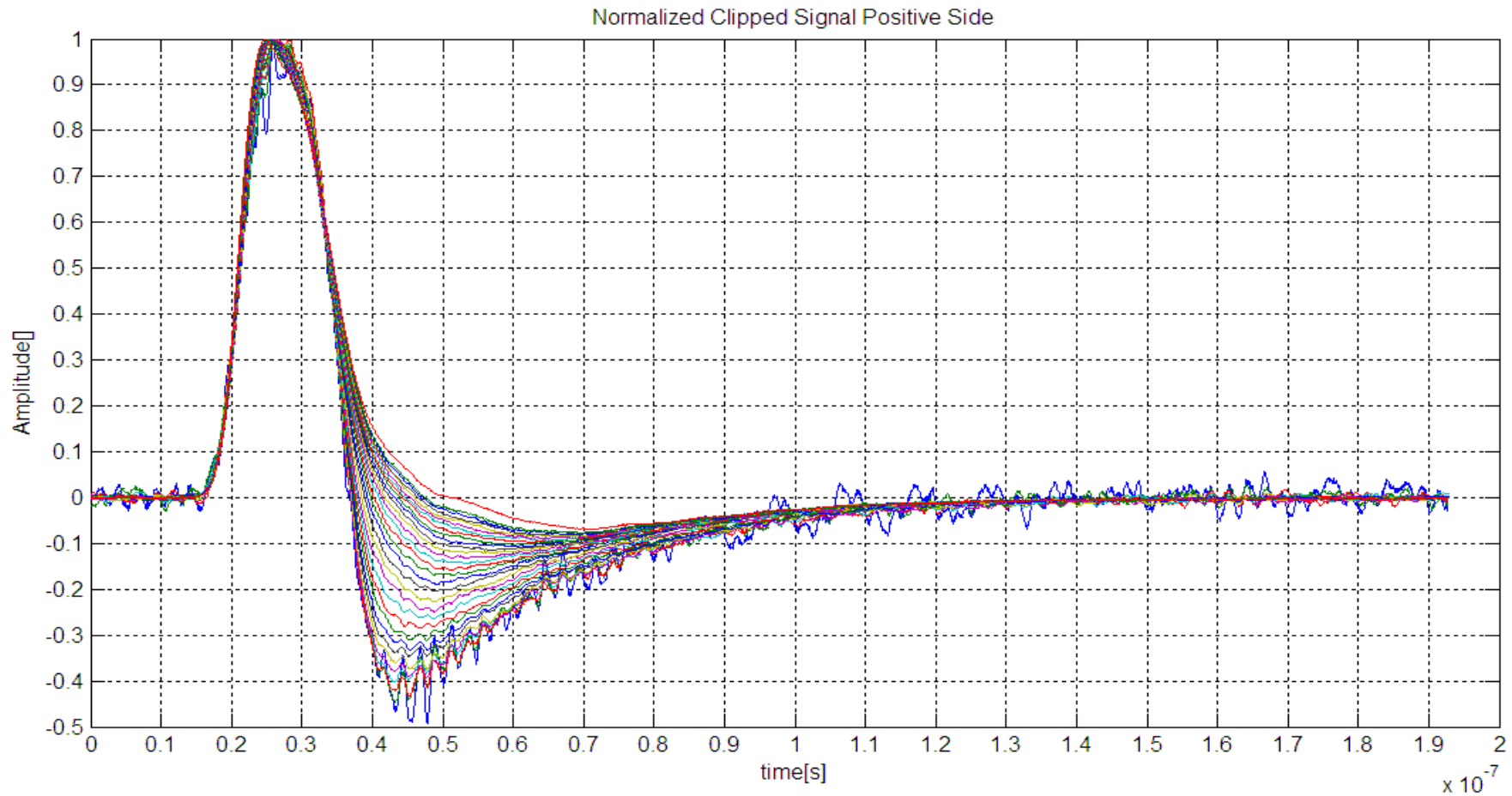


- Same Shape approx
- Linear to the eye NEED A BETTER WAY TO MEASURE



# Measurements CLIPPING STAGE


- OPClip- Gain

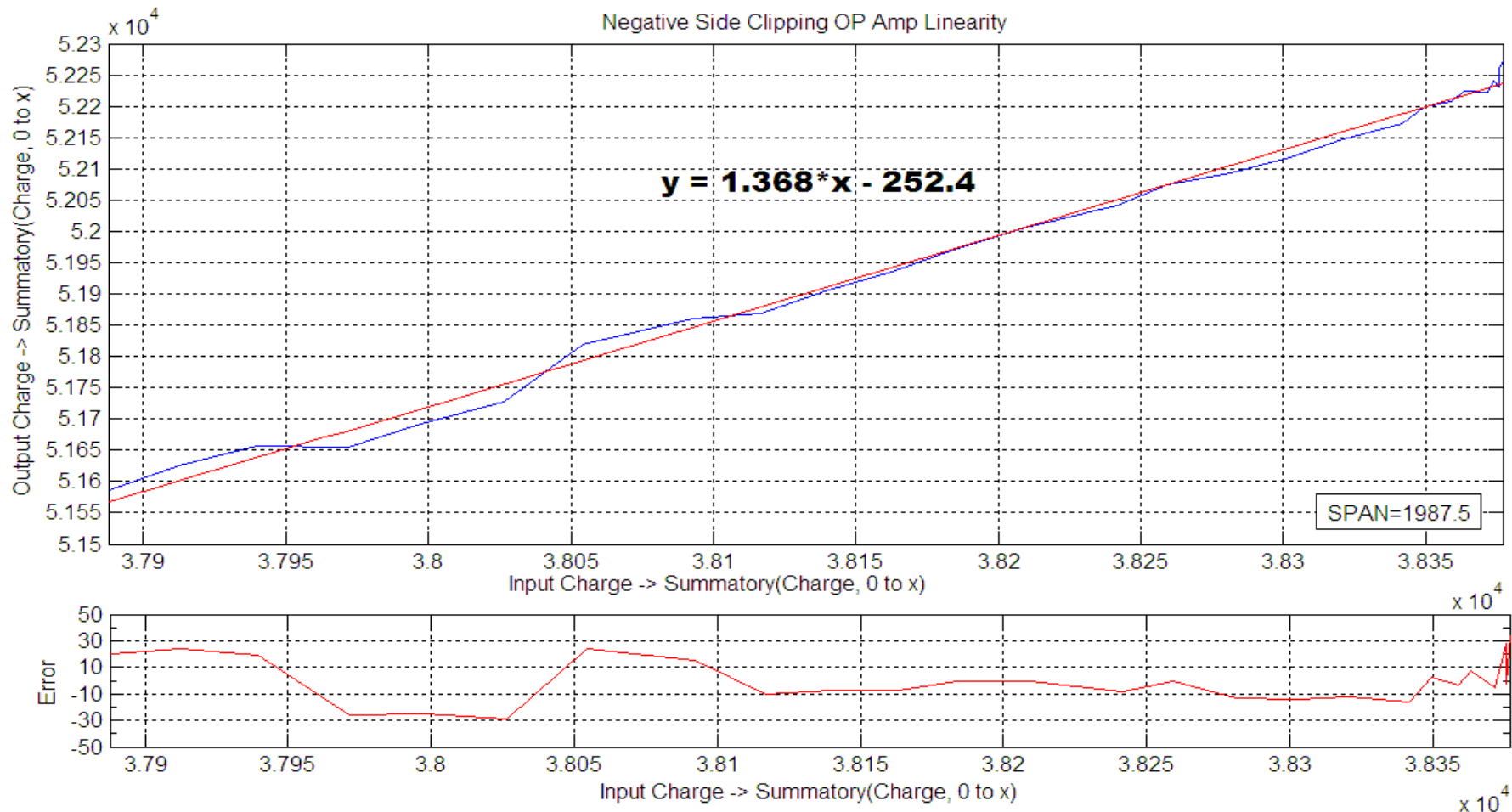

- Reasonable Linearity taking noise into account


# Measurements CLIPPING STAGE

- OPClip+ Gain

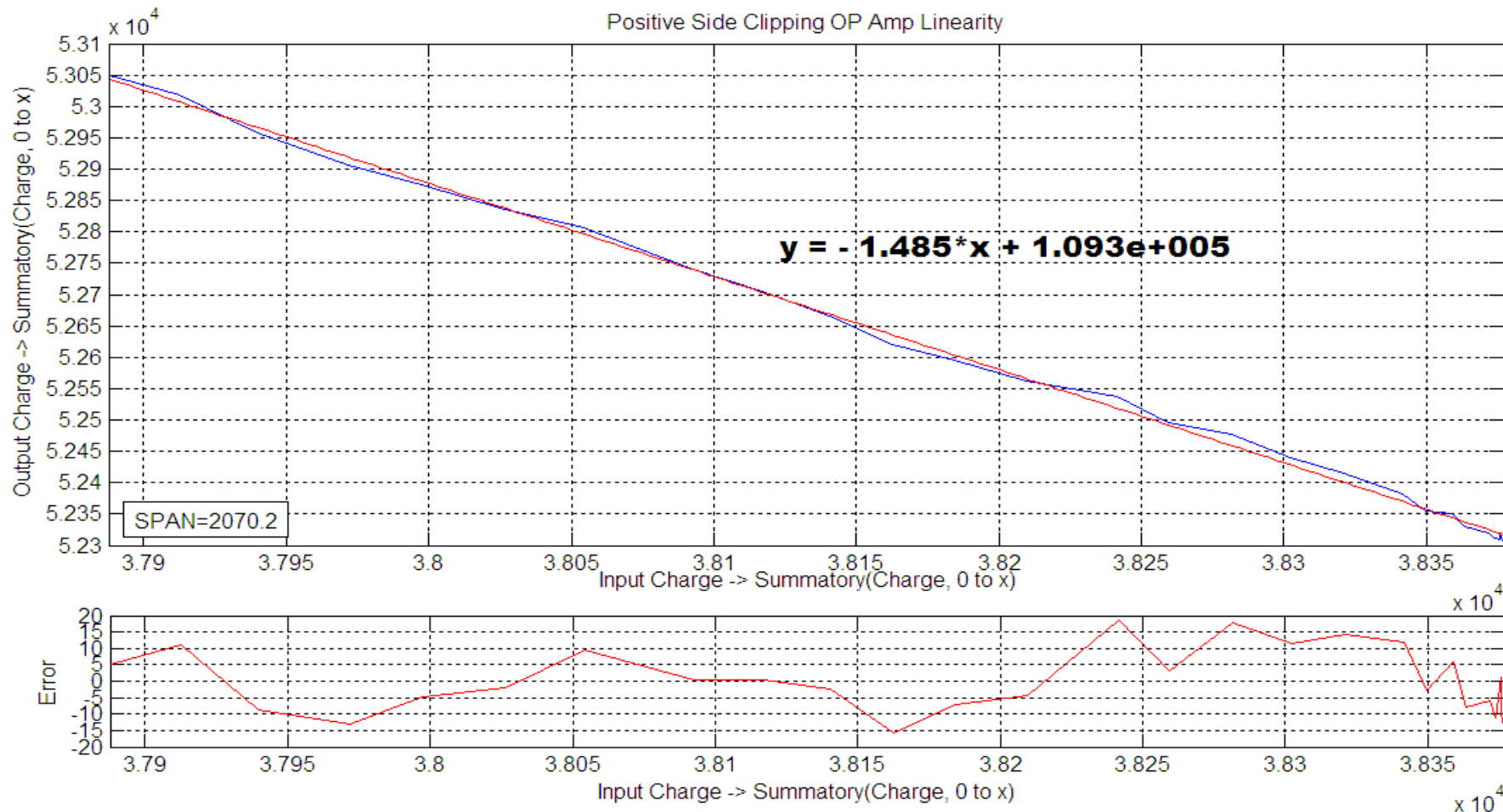

- Reasonable Linearity taking noise into account
- But different gain? 1.368 vs. 1.485?

- Integrator Positive Output

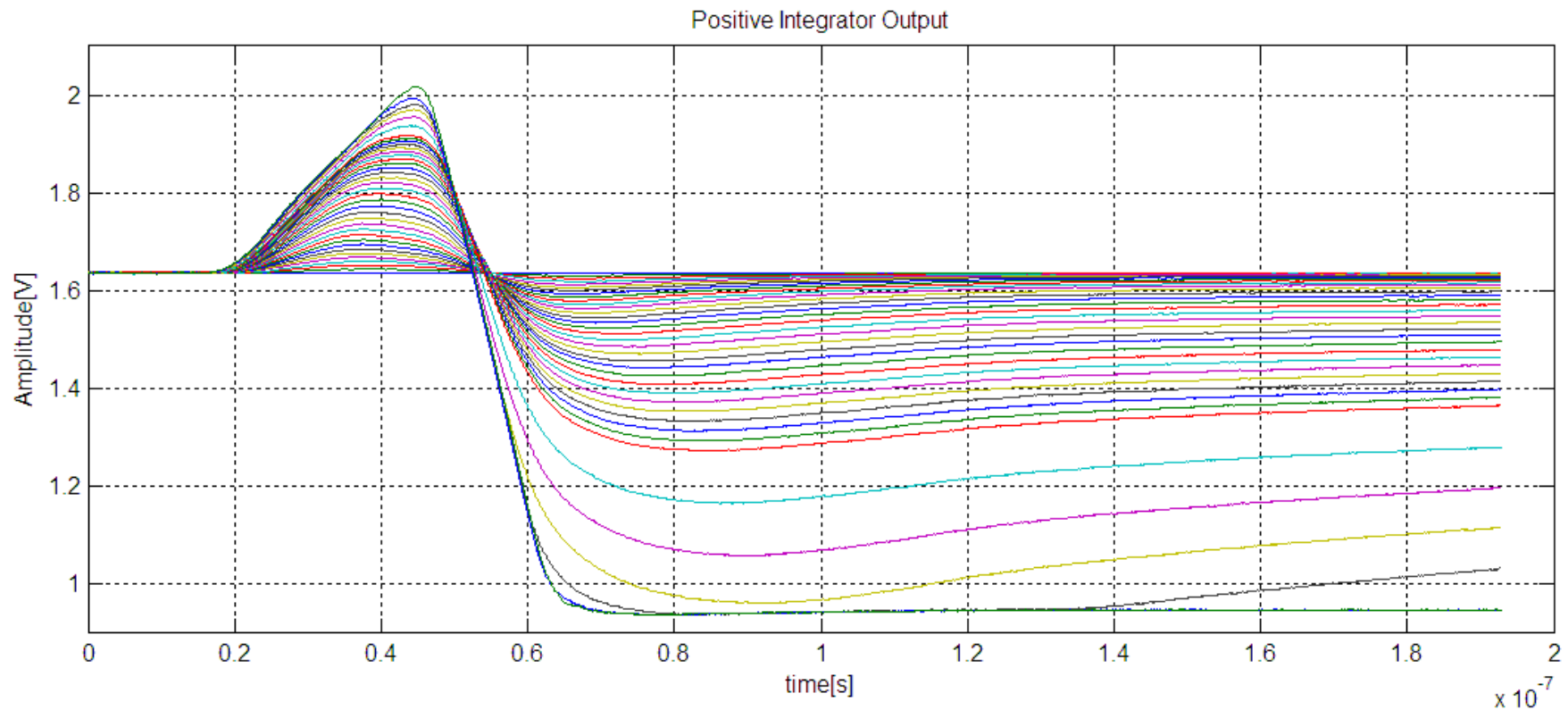


- Need to understand why

# Measurements

# INT. STAGE



- Integrator Negative Output

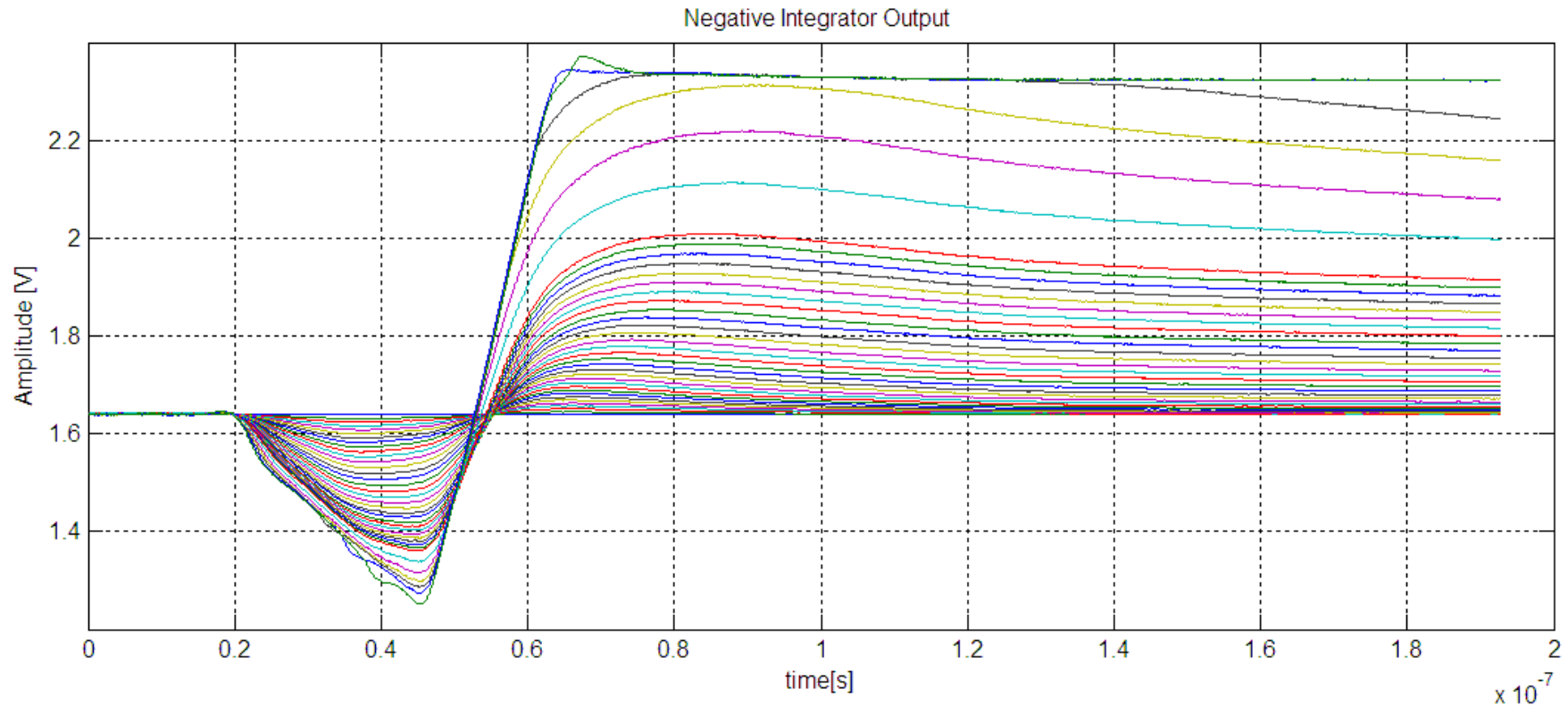

- Need to understand why
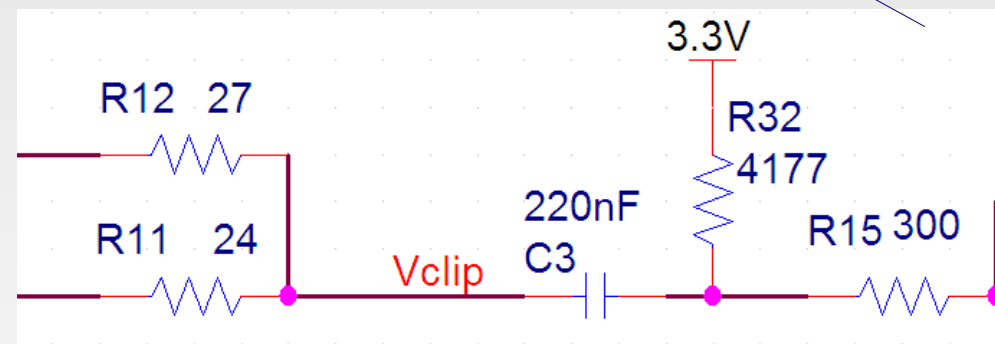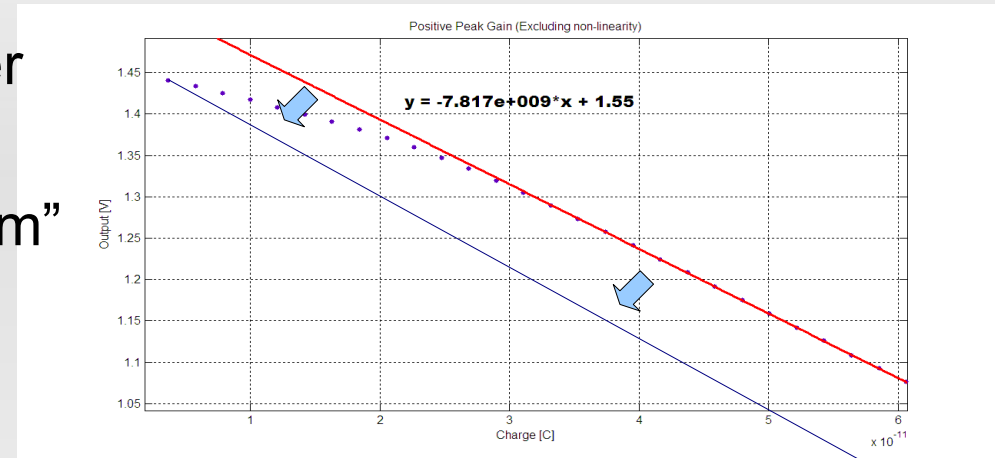
# Conclusions/Ideas

- INPUT STAGE:
  - Need to tune input to have lower offset
  - Need to understand "RC problem"
- Will offset solve it all?
  - Test and see
- If not:
  - Cut DC path between outputs
  - Reduce capacitor
  - Increase next stage impedance



# Conclusions/Ideas

- CLIPPING STAGE:
  - Performs reasonably from linearity point of view
- INTEGRATING STAGE:
  - Oscillation solved
  - Integrator Output not understood
    - Need to simulate with captured data
      - (Numerical Integration)
- GENERAL:
  - Need to use a more precise source
  - Perform noise tests with ADC
  - Possibly change the ADA4930 with ADA4932 → Bipolar supply with no offsets. +3V and -3V → much more dynamic range