



# LHCb Calorimeter Upgrade Electronics: ASIC solution status

E. Picatoste, D. Gascon

**Universitat de Barcelona**  
**Institut de Ciències del Cosmos ICC-UB**

# Outline

---



1. ASIC solution short review
2. Second prototype simulations and preliminary measurements
3. Discussion
4. Plans in short term
5. Plans in mid term

# ASIC solution review

- Integrated circuit for the Upgrade of the LHCb Calorimeter Front End electronics
  - Architecture based on:
    - Current mode preamplifier with cooled termination for reduced input noise
    - 2 fully differential interleaved channels
    - Switched integrator
    - Track-and-Hold
- Measurements of the first prototype of the input stage (preamp+integrator) are about finished
  - Principle is ok
  - Good results with 12 chips statistics
  - Need to study the effect of bias (op. point) variation
- A second prototype was submitted in June and received last week
  - It includes: preamp + integrator + track-and-hold
  - Added a feedback resistor to improve the integrator output stability

# Second prototype

## ICECAL2 chip:



SiGe BiCMOS 0.35um

AMS 2 mm<sup>2</sup>

10 units encapsulated (QFN32)

Submitted: June 6th 2011


Received: October 5<sup>th</sup> 2011

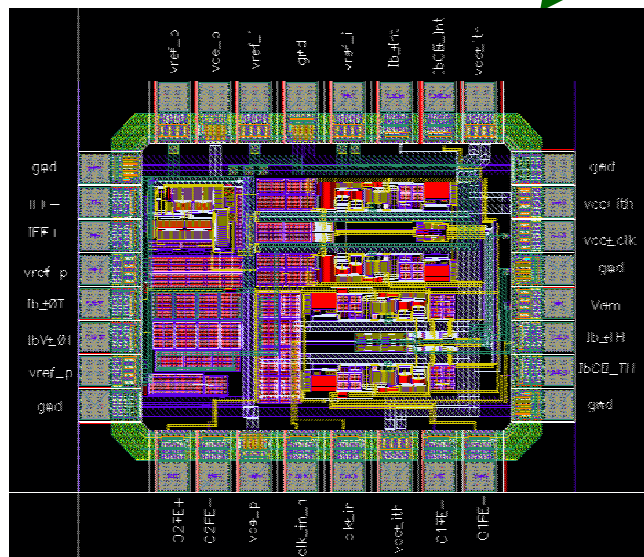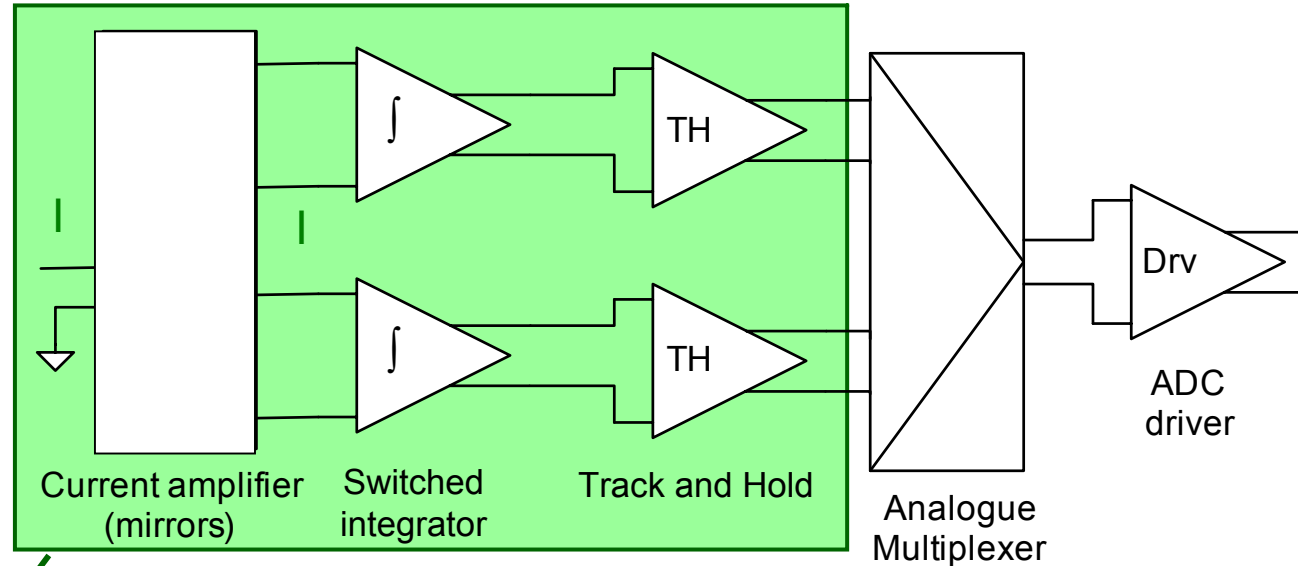



16th December 2011

- Purpose: test key points of the circuit
  - Input impedance control by current feedback
  - Low noise performance
  - Dynamic range: Linearity
- Also, to test critical aspects of a switched solution:
  - Offset between subchannels
  - Noise
  - Plateau of the integrator output
    - Effect of the clock jitter versus signal
    - Integrator Rf effect


# ICECAL2 Simulations

 

# ICECAL2 Preliminary Measurements

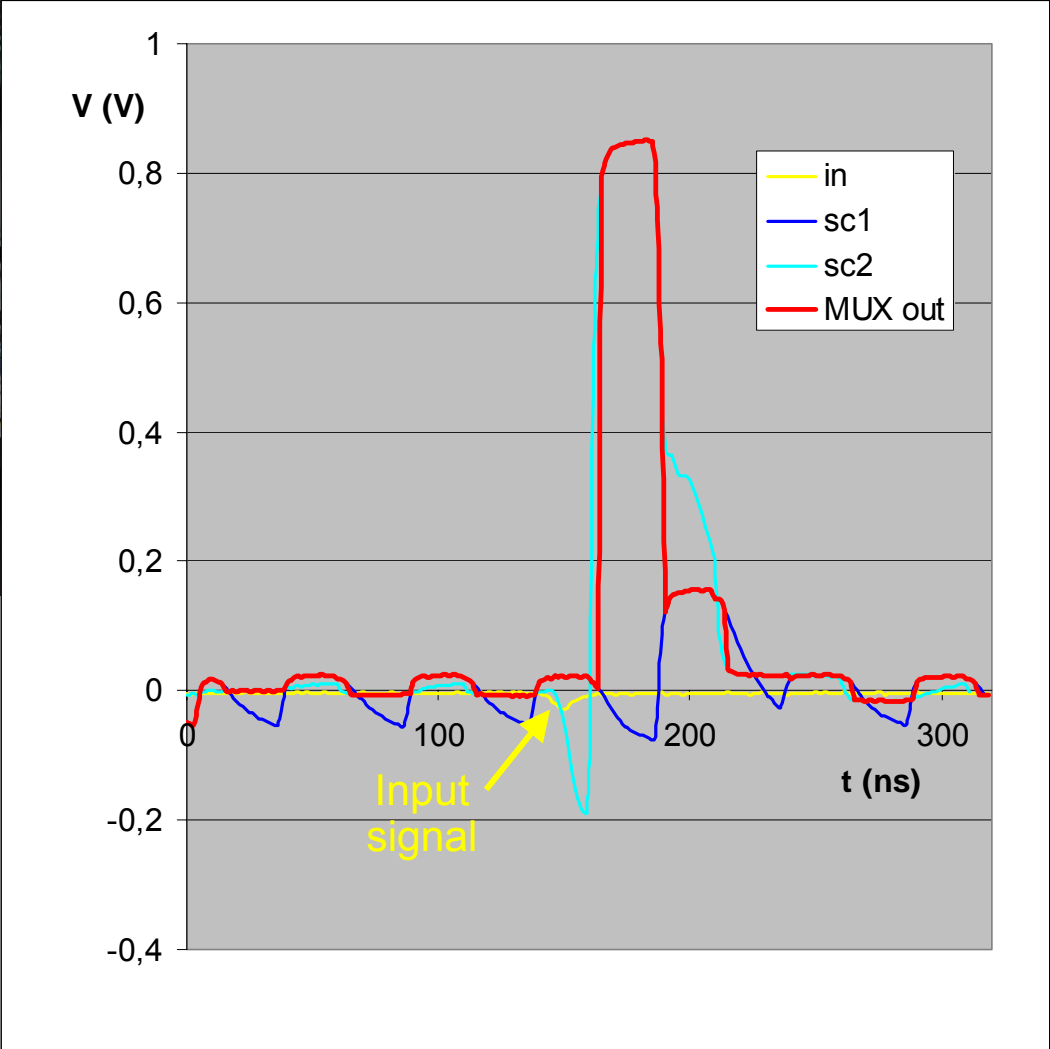 


# ICECAL2 Linearity Simulations

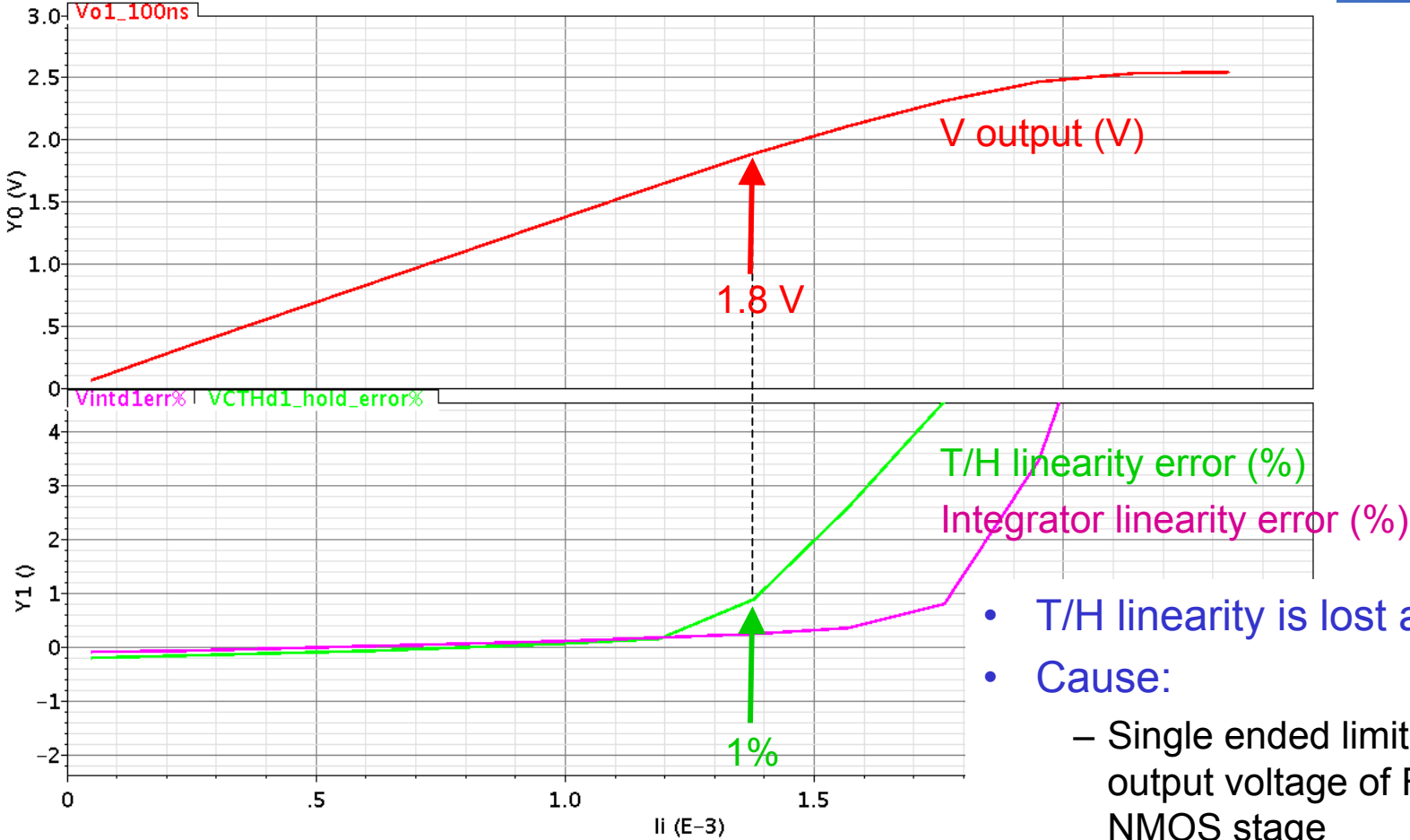

- T/H linearity is lost at  $V_{out} \sim 1.8V$
- Cause:
  - Single ended limit to maximum output voltage of FDOA at the NMOS stage
- Possible solution:
  - Apply different offset to each pos/neg signal to reduce overall signal excursion
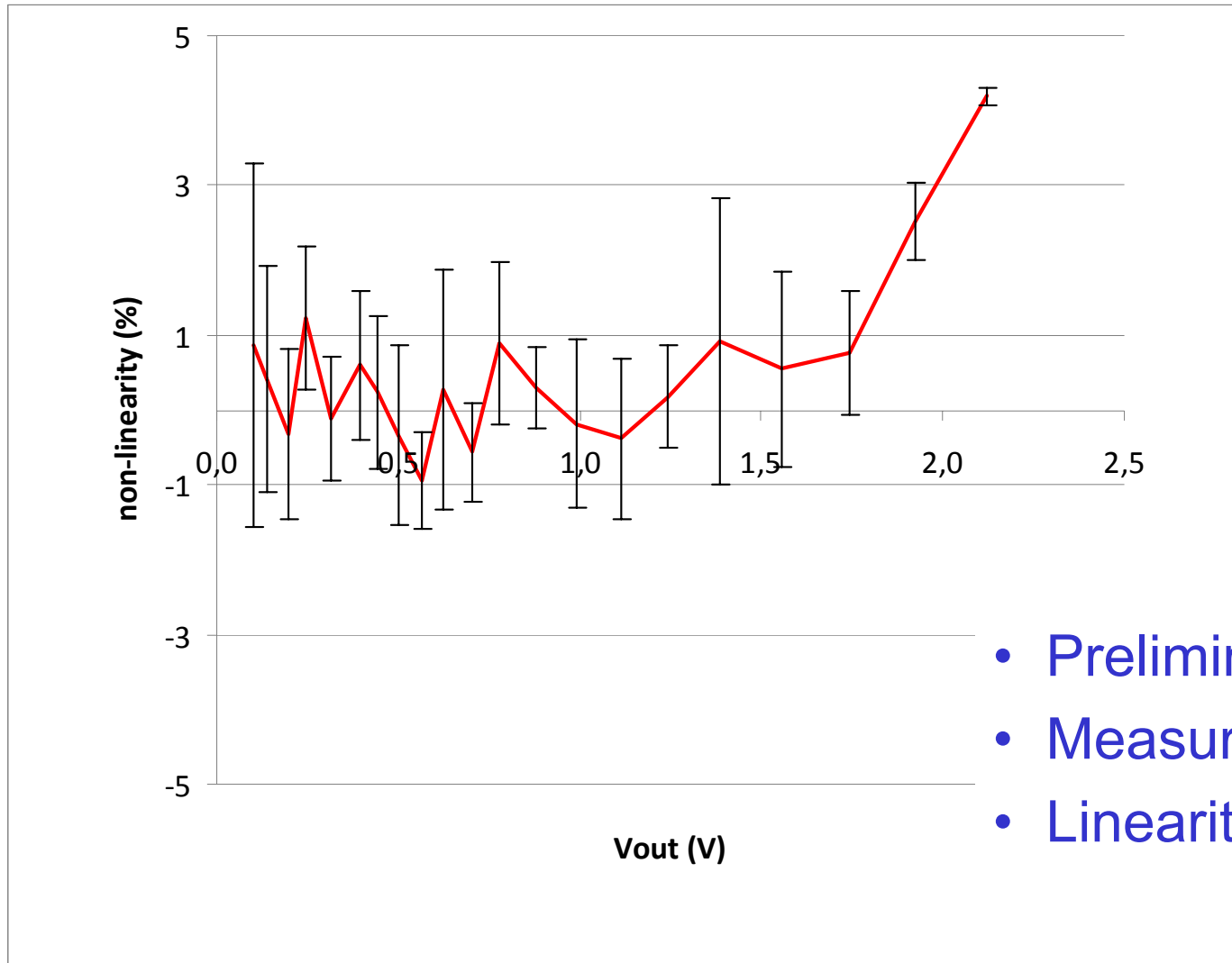
# ICECAL2 Preliminary Linearity Measurement



- Preliminary!
- Measurement of 1 chip
- Linearity seems OK



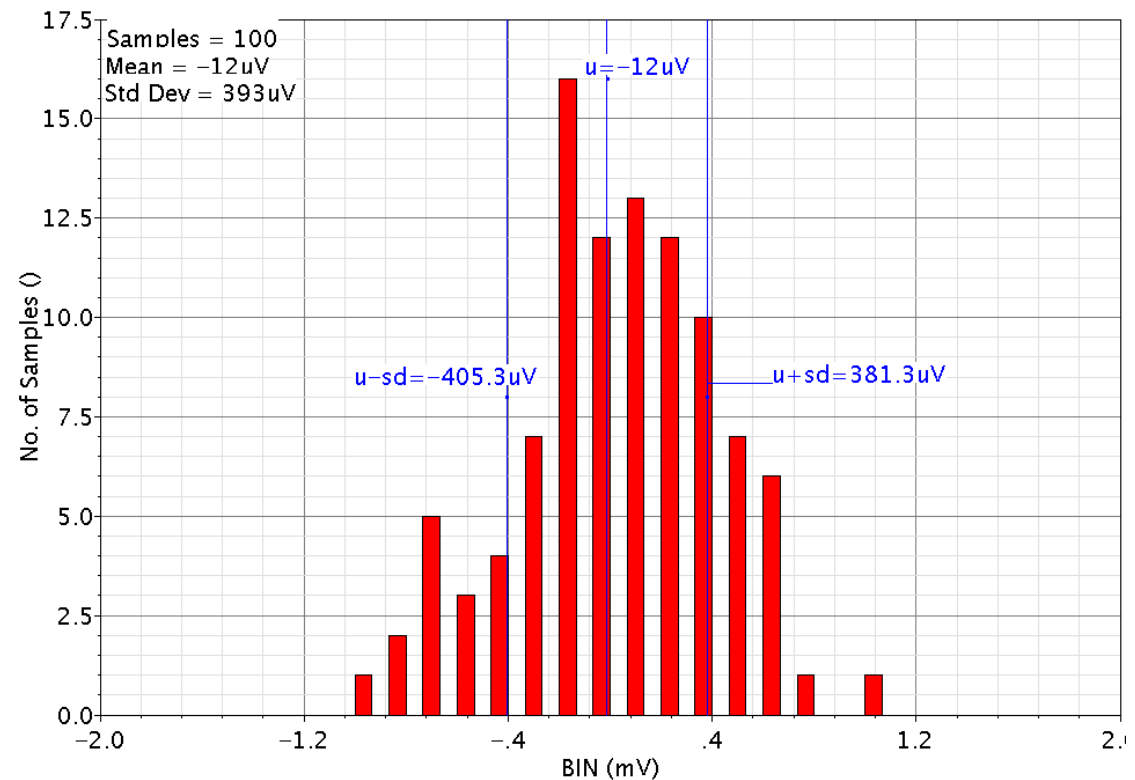
# ICECAL2 Noise Simulations



- The noise:



- Generate a histogram of the voltage value by the end of the cycle (from 100 waveforms).
- Zero input signal
- Gaussian fit => standard deviation
- Noise  $\leq 0.8$  ADC counts
- Cable effect not included



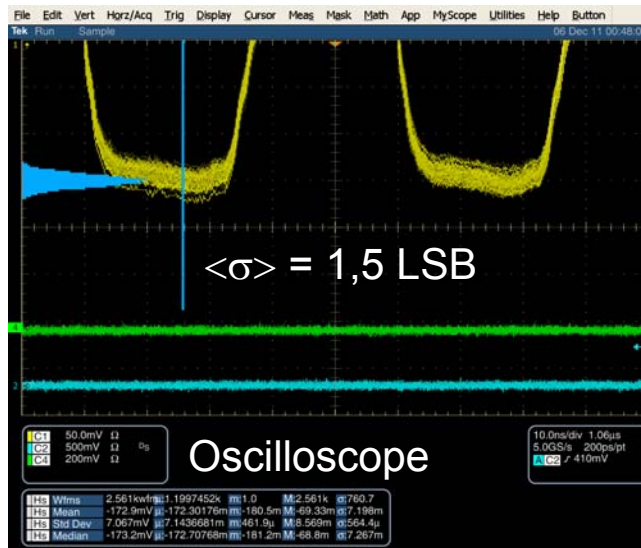 
# ICECAL2 Noise Measurements



- Setup:
  - includes amp x11.2
  - With/without cable+clipping
  - Oscilloscope: sigma for 1 pt
  - WaveCatcher: sigma for 3 points + CDS





If no  
cable+clipping


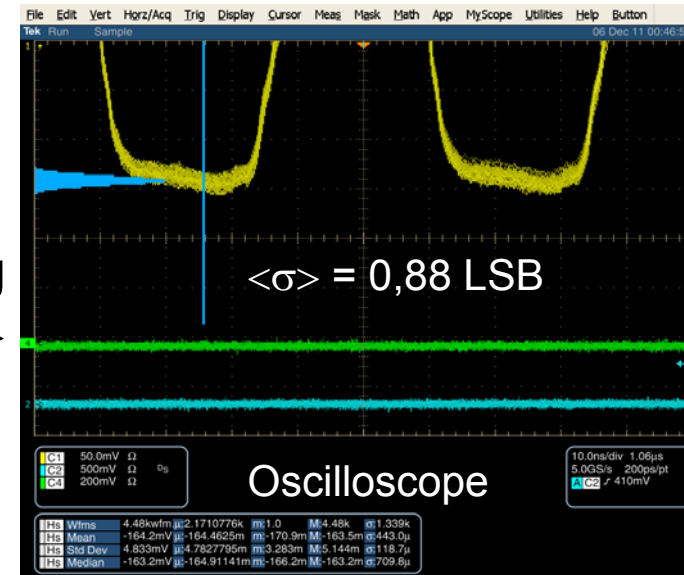


# ICECAL2 Noise Measurements

cable+clipping

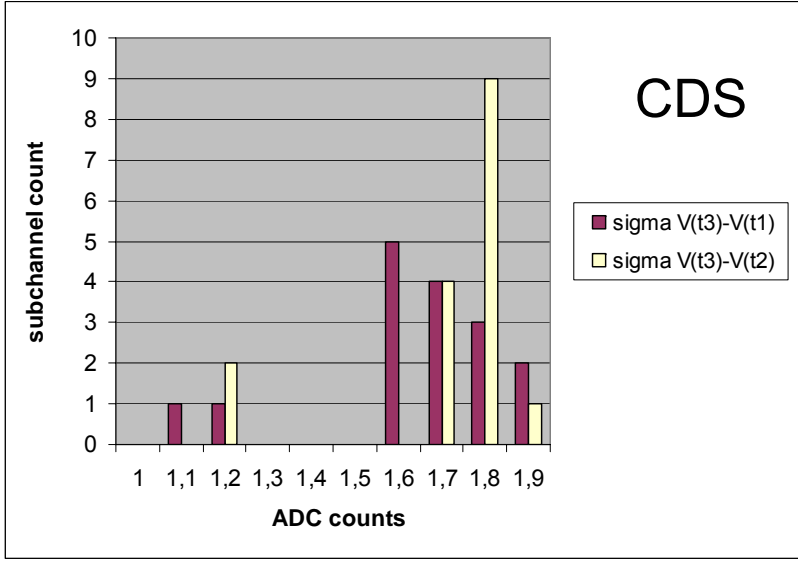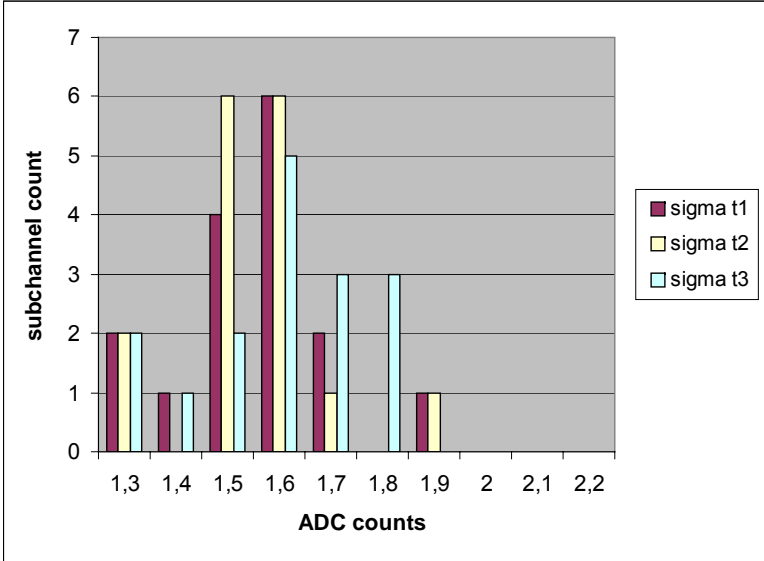

no cable

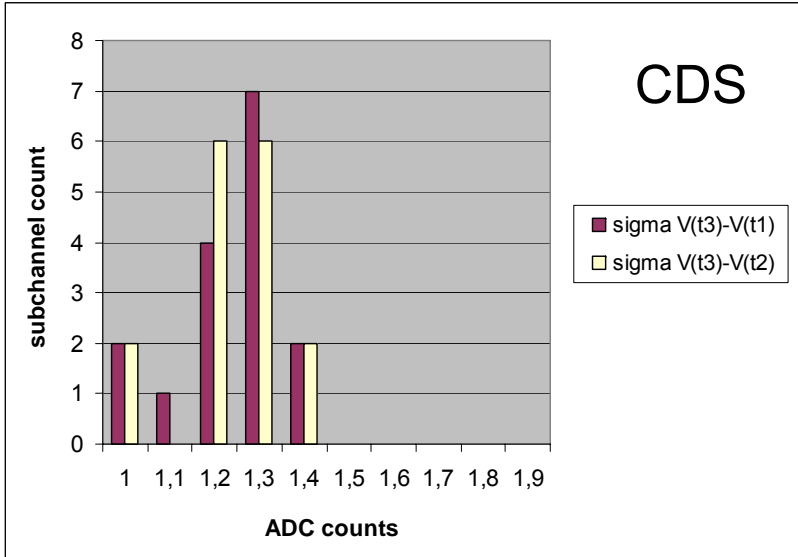 

- Delay chips
  - More than 1 or 2 delay chips per channel
    - 1 for the integrator
    - 1 for the ADC?
  - Only 8 phasers per GBT, maybe some extra phasers can be obtained (extra GBT, CROC...) but anyway it means  $< 2$  per ch!, if more are needed:
    - Re-use existing delay chips
    - Build a new one: no one seems to be planning to do it
    - Integrate 1 phaser/ch in ICECAL
      - Possible if DLL designs done by Dominique's team can be re-used
        - Discuss with Dominique!
        - Any design in AMS 0.35um (either CMOS or BiCMOS) can be reused!
- Slow control interface with GBT-SCA:
  - I2C/JTAG in SCA is 1.5 V CMOS whereas ICECAL I/O is 3.3 V CMOS
    - Design a dedicated pad-level translator
    - Go through FPGA: enough pins? Good I/O bank distribution?

## Outlook & plans: short term

---

- Very short term: finish ICECAL 2 prototype tests before end 2011:
  - Statistic on 10 samples
- Short term: move to common test environment with LAL motherboard **immediately** in 2012
  - New mezzanine for ICECAL V2
  - Develop dedicated CAT software for LAL motherboard:
    - Noise, linearity, time alignment....
  - Test with PMT-base
  - Test with PMT-base + CW base
  - Test with DC-DC converters
    - We have couple of units thanks to G. Blanchot

# Outlook & plans: mid term



- Mid term: produce a final 1 channel chip before end 2012
  - Main changes
    - Add tunability: input impedance, gain, shaping...
      - Need to decide what's to be tuned and range!
    - Add analog multiplexer and driver
    - Differential LVDS input clock and flip-flop with sync reset (L0-like reset)
    - I2C/JTAG ECS interface
    - **Remarkable deisgn effort: shall start ASAP !!!!**
- ASIC with 1 final channel must be ready by 2013:
  - With beam signal: test beam and/or detector tests
  - But even without beam: study LF pick-up noise immunity, grounding, etc... taking profit of long shutdown in the most realistic scenario: the detector