



Field Programmable Gate Arrays

Hannes Sakulin
CERN / PH-CMD

Fourth International School of
Trigger and Data Acquisition
Thessaloniki, Greece, Feb 4th, 2013



What is a **F**ield **P**rogrammable **G**ate **A**rray ?

.. a quick answer for the impatient

- An FPGA is an integrated circuit
 - Mostly digital electronics
- An FPGA is programmable in the in the field (=outside the factory), hence the name “field programmable”
 - Design is specified by schematics or with a hardware description language
 - Tools compute a programming file for the FPGA
 - The FPGA is configured with the design
 - Your electronic circuit is ready to use

With an FPGA you can build electronic circuits ...
... without using a soldering iron
... without plugging together existing modules
... without having a chip produced at a factory




Outline

- Quick look at digital electronics
- Short history of programmable logic devices
- FPGAs and their features
- Programming techniques
- Design flow
- Example Applications in the Trigger and DAQ domain

Digital electronics

The building blocks: logic gates

AND gate

 


Truth table

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

C equivalent

`q = a && b;`

OR gate

 

INPUT		OUTPUT
A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

`q = a || b;`

Exclusive OR gate
XOR gate




INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

`q = a != b;`


⋮

Combinatorial logic (asynchronous)

 

Example: Full adder with carry-in, carry-out


Outputs are determined by Inputs, only

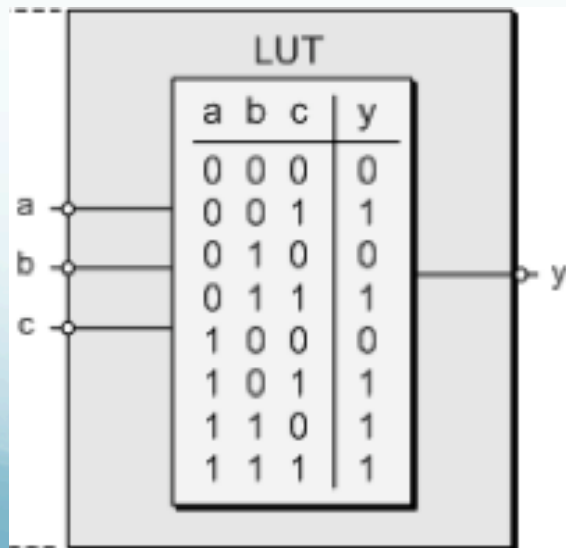

Combinatorial logic may be implemented using Look-Up Tables (LUTs)


LUT = small memory

(Synchronous) sequential logic

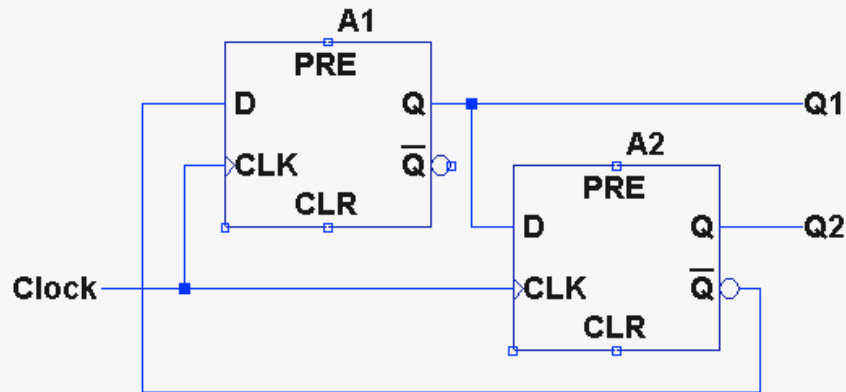

2-bit binary counter

 Outputs are determined by Inputs and their History (Sequence)
The logic has an internal state




D Flip-flop:

samples the data at the rising (or falling) edge of the clock

The output will be equal to the last sampled input until the next rising (or falling) clock edge

D Flip-flop (D=data, delay)

Synchronous sequential logic

 


Using Look-Up-Tables and Flip-Flops
any kind of digital electronics may be implemented

Of course there are some details
to be learnt about electronics design ...


Programmable digital electronics

Long long time ago ...

 

Simple Programmable Logic Devices (sPLDs)

a) Programmable Read Only Memory (PROMs)

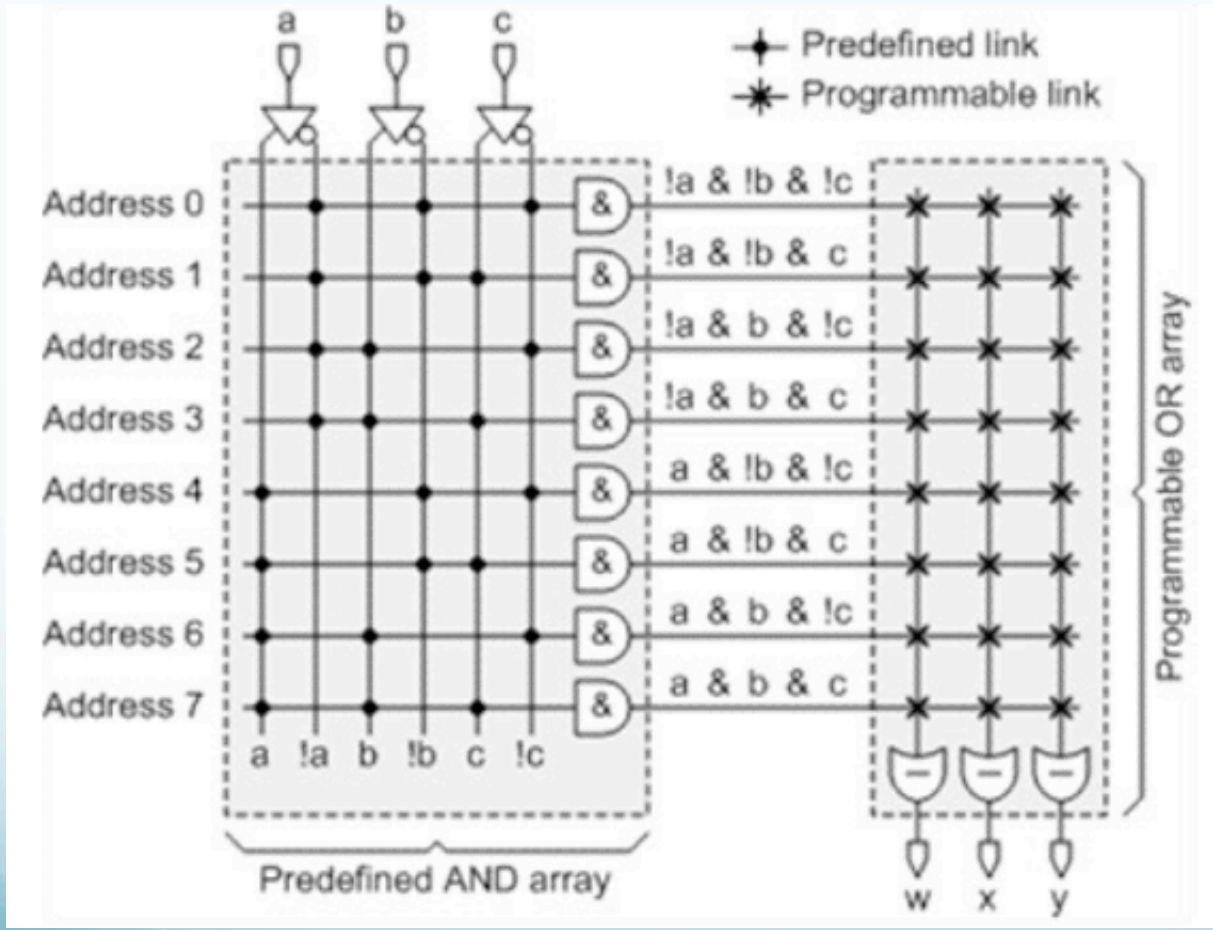


Late 60's

Unprogrammed PROM (Fixed AND Array, Programmable OR Array)

Simple Programmable Logic Devices (sPLDs)

b) Programmable Logic Arrays (PLAs)

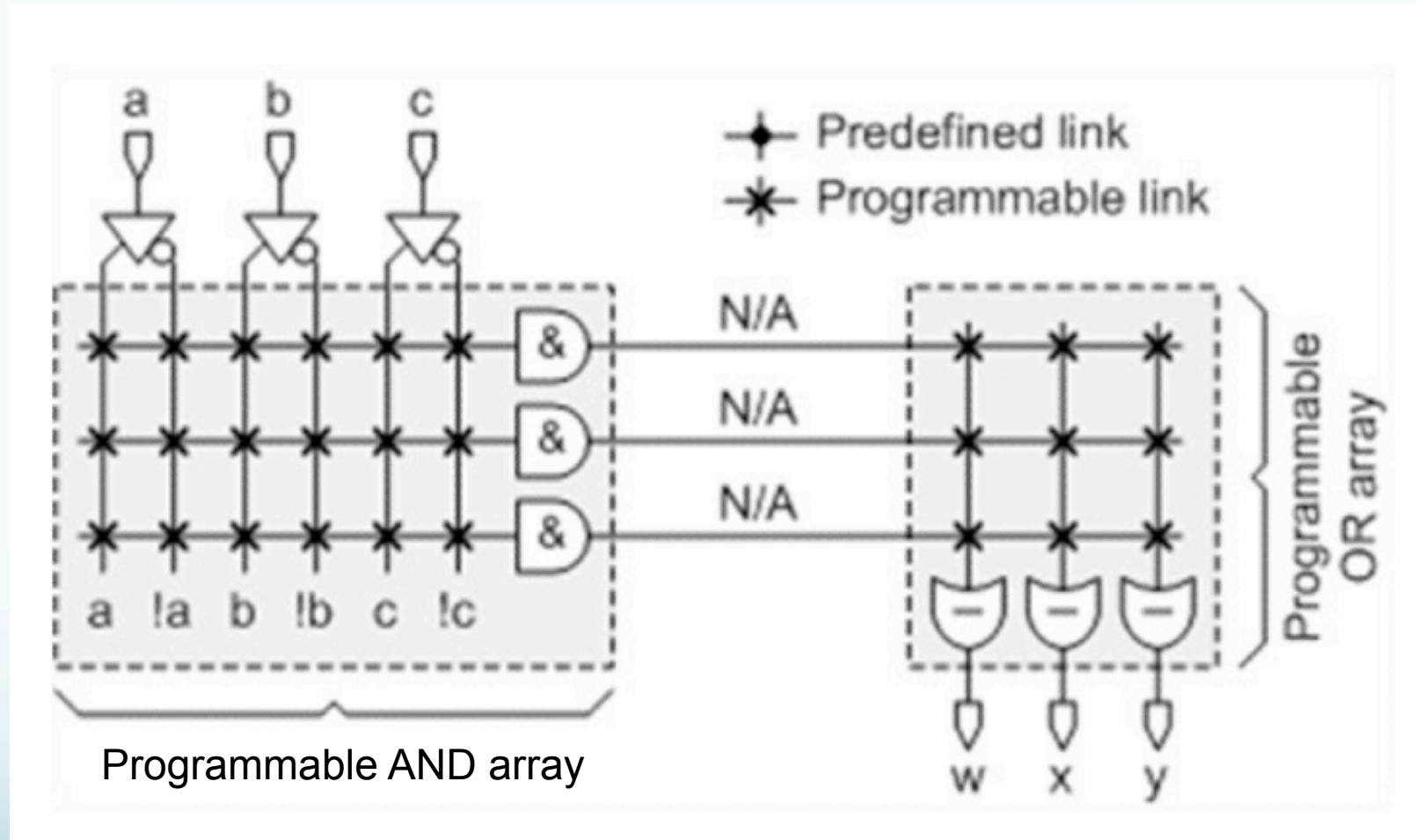



Unprogrammed PLA (Programmable AND and OR Arrays)

Most flexible
but slower

1975


Simple Programmable Logic Devices (sPLDs)

c) Programmable Array Logic (PAL)

 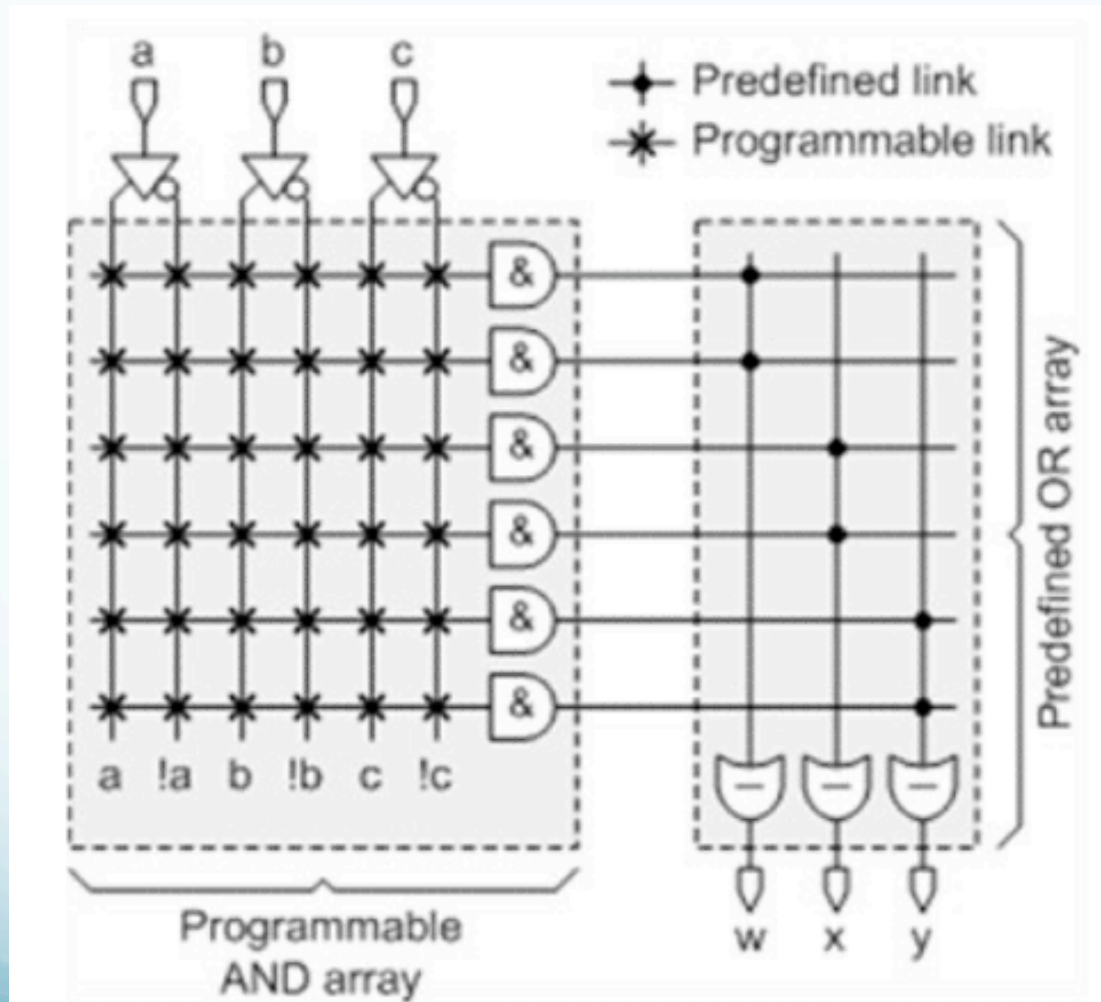

Unprogrammed PAL (Programmable AND Array, Fixed OR Array)

Complex PLDs (CPLDs)

 


Coarse grained
100's of blocks, restrictive structure
(EE)PROM based

FPGAs ...




FPGAs

 


Fine-grained: 100.000's of blocks
today: up to 2 million logic blocks

Programmable Input / Output pins

LUT-based Fabrics

 


Typical LUT-based Logic Cell

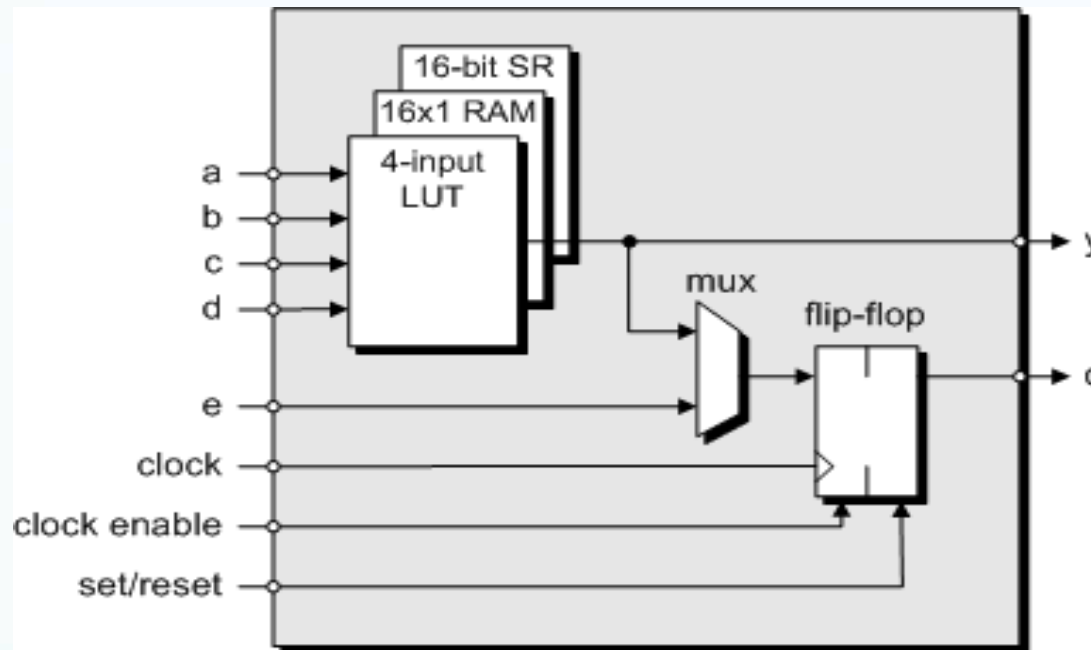

Xilinx: logic cell,
Altera: logic element


- LUT may implement any function of the inputs
- Flip-Flop registers the LUT output
- May use only the LUT or only the Flip-flop
- LUT may alternatively be configured a shift register
- Additional elements (not shown): fast carry logic

Clock Trees

 


Clock trees guarantee that the clock arrives at the same time at all flip-flops

Clock Managers

 


Embedded RAM blocks

 


Today: Up to ~100 Mbit of RAM

Embedded Multipliers & DSPs

 


Soft and Hard Processor Cores

 - Soft core
 - Design implemented with the programmable resources (logic cells) in the chip
- Hard core
 - Processor core that is available in addition to the programmable resources
 - E.g.: Power PC, ARM




General-Purpose Input/Output (GPIO)

 

Today: Up to 1200 user I/O pins
Input and / or output
IO standard (such as LVTTL, LVDS)
programmable
Single signals or differential pairs


High-Speed Serial Interconnect

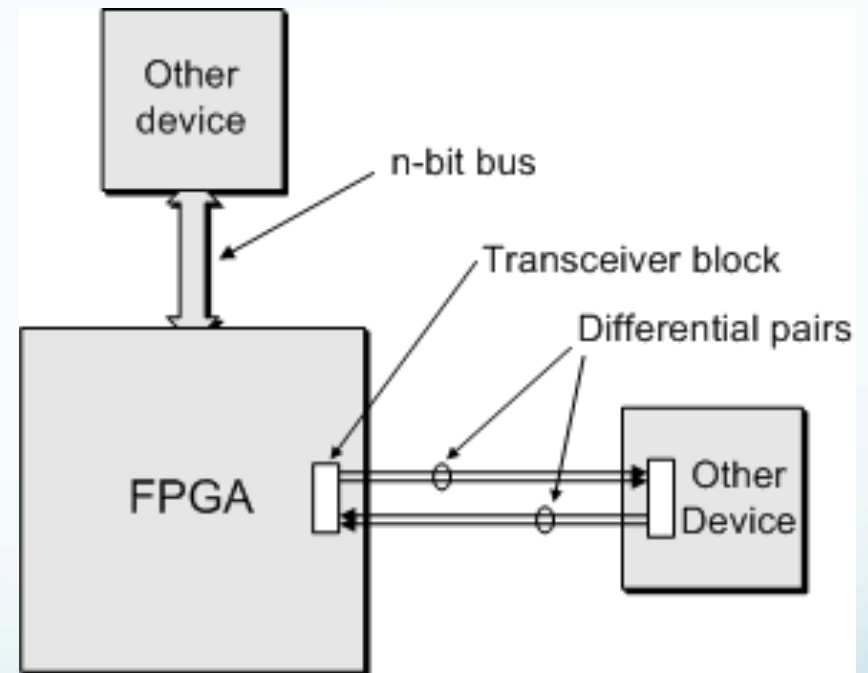- Using differential pairs
- Latest serial transceivers:
10 Gb/s up to 28 Gb/s
- FPGAs with Tbit/s IO
bandwidth
- PCI Express
 - Gen2: 5 Gb/s per lane
 - Gen3: 8 Gb/s per lane
up to 8 lanes / FPGA
 - Hard and soft macros
- 10 Gb/s, 40 Gb/s, 100 Gb/s
Ethernet



Trends

Ever-decreasing feature size

 

- Higher capacity
- Higher speed

130 nm
Xilinx Virtex-2

28 nm
Xilinx Virtex-7 / Altera Stratix V



2 million logic cells

Trends

- Look-up-tables with more inputs (5 or 6)
- Speed of serial links increasing (multiple Gb/s)
- More hard macro cores (Ethernet MAC, Memory interfaces, PCI express ...)
- Sophisticated soft macros
 - CPUs
 - Gb/s MACs
 - Memory interfaces (DDR2/3/4)
 - CPUs
- Processor-centric architectures
 - Multi-core processor + FPGA logic (Xilinx ZYNQ)
- Domain-specific devices
- Ultra-low-power FPGAs
- Mixed-signal FPGAs

FPGA – ASIC comparison


FPGA

- Rapid development cycle (minutes / hours)
- May be reprogrammed in the field (firmware upgrade)
 - New features
 - Bug fixes
- Low development cost
 - You can get started with a \$200 development board and free software




ASIC

 - Higher performance
- Analog designs possible
- Better radiation hardness
- Long development cycle (weeks / months)
- Design cannot be changed once it is produced
- Extremely high development cost
 - ASICs are produced at a semiconductor fabrication facility ("fab") according to your design
- Lower cost per device compared to FPGA, when large quantities are needed





Programming techniques

Fusible Links (not used in FPGAs)

 


Antifuse Technology

  

EPROM Technology


Erasable Programmable Read Only Memory

 

Intel, 1971

EEPROM and FLASH Technology

 
Electrically Erasable Programmable Read Only Memory



EEPROM: erasable word by word



 


FLASH: erasable by block or by device

SRAM-Based Devices




Multi-transistor SRAM cell

Summary of Technologies


Technology	Symbol	Predominantly associated with ...
Fusible-link		SPLDs
Antifuse		FPGAs
EPROM		SPLDs and CPLDs
E ² PROM/ FLASH		SPLDs, CPLDs, and FPGAs
SRAM		FPGAs (some CPLDs)

← Used in most FPGAs

Design Considerations (SRAM Config.)

 


Configuration at power-up

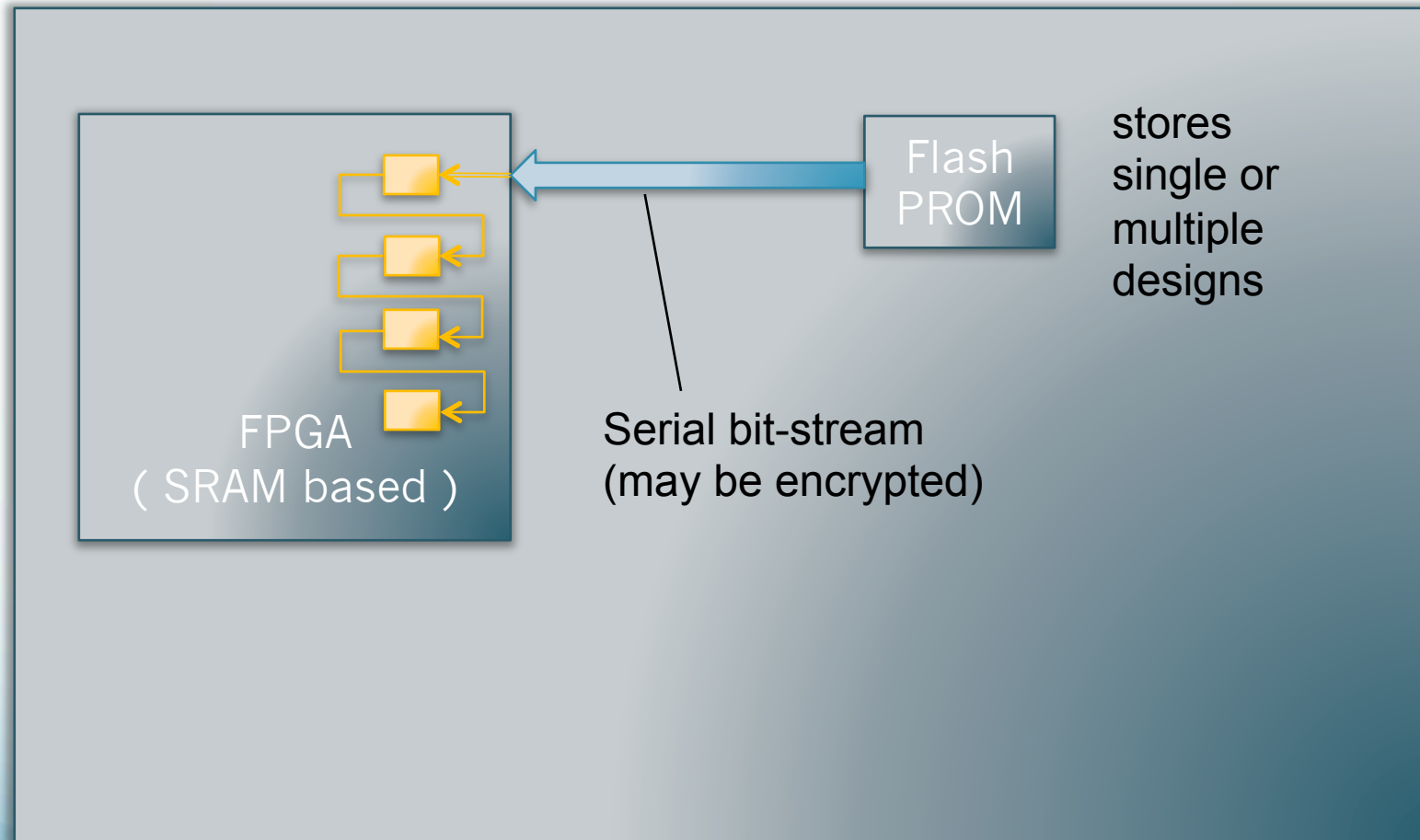

Typical FPGA configuration time: milliseconds

Programming via JTAG


Joint Test Action Group

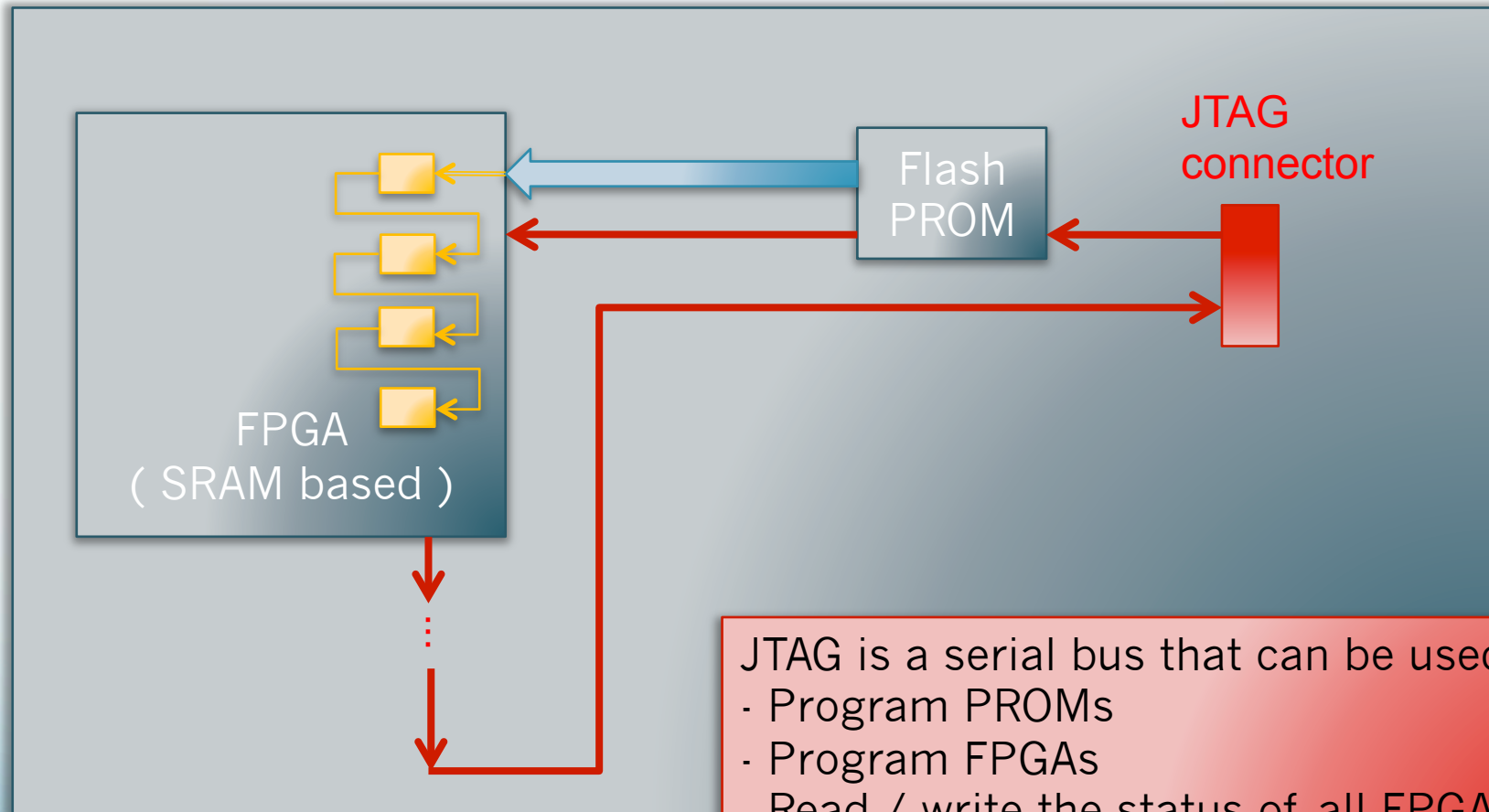

JTAG is a serial bus that can be used to

- Program PROMs
- Program FPGAs
- Read / write the status of all FPGA I/Os
(= Boundary scan)

Programming from a host PC

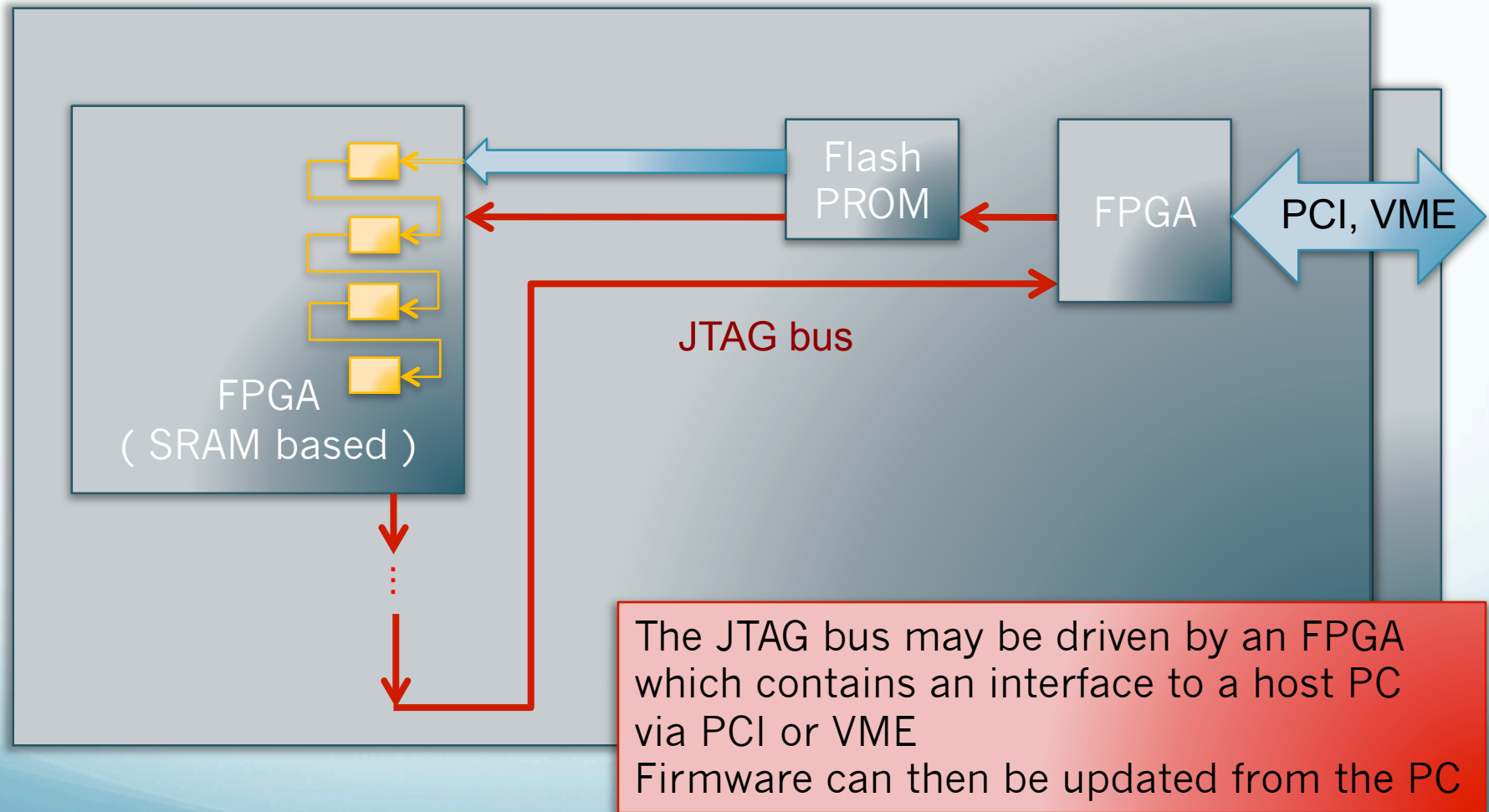

Major Manufacturers


- Xilinx
 - First company to produce FPGAs in 1985
 - About 50% market share, today
 - SRAM based CMOS devices
- Altera
 - About 40% market share
 - SRAM based CMOS devices
- Actel
 - Anti-fuse FPGAs
 - Flash based FPGAs
 - Mixed Signal
- Lattice Semiconductor
 - SRAM based with integrated Flash PROM



FPGA development

Design entry

Schematics

 

- Graphical overview
- Can draw entire design
- Use pre-defined blocks


Hardware description language VHDL, Verilog

```
entity DelayLine is
    generic (
        n_halfcycles : integer := 2);
    port (
        x          : in std_logic_vector;
        x_delayed  : out std_logic_vector;
        clk        : in std_logic);
end entity DelayLine;
```

- Can generate blocks using loops
- Can synthesize algorithms
- Independent of design tool
- May use tools used in SW development (CVS, SVN ...)

Mostly a personal choice depending on previous experience

Schematics

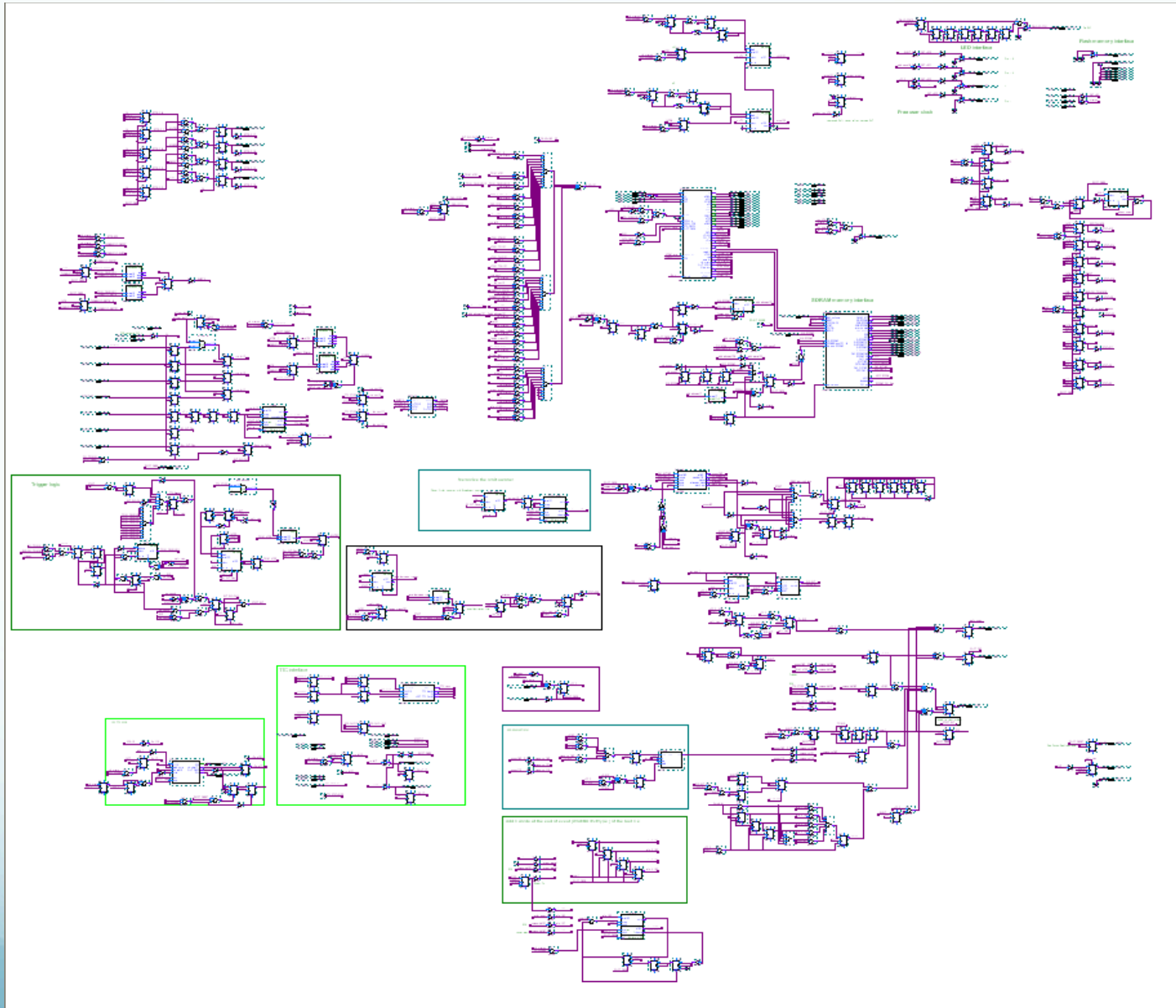

Hardware Description Language

- Similar to a programming language
- Common HDLs
 - VHDL
 - Verilog
 - AHDL (Altera specific)
- Newer trends
 - C-like languages (handle-C)
 - Labview

Example: VHDL

```
architecture behavioral of VMEReg is
```

```
    signal vme_en_i    : std_logic;  
    signal Q : std_logic_vector(15 downto 0);
```

```
begin -- behavioral
```

```
    vme_addr_decode : process (vme_addr, vme_en) is  
        variable my_addr_vec : std_logic_vector(vme_addr'high downto 0);  
        variable selected    : boolean;  
    begin -- process vme_addr_decode  
        my_addr_vec := std_logic_vector( TO_UNSIGNED ( my_vme_base_address, vme_addr'high+1 ) );  
        selected    := my_addr_vec(vme_addr'high downto 1) = vme_addr(vme_addr'high downto 1);  
        vme_en_i <= '0' ;  
        if selected then  
            vme_en_i <= vme_en;  
        end if;  
    end process vme_addr_decode;
```


```
    reg: process (vme_clk, reset) is  
    begin -- process reg  
        if reset = '1' then                -- asynchronous reset  
            Q <= init_val;  
            vme_en_out <= '0';  
        elsif vme_clk'event and vme_clk = '1' then -- rising clock edge  
            vme_en_out <= vme_en_i;  
            if vme_en_i = '1' and vme_wr = '1' then  
                Q <= vme_data;  
            end if;  
        end if;  
    end process reg;
```

```
    data <= Q;  
    vme_data_out <= Q;
```


```
end behavioral;
```

- Looks like a programming language
- All statements executed in parallel, except inside processes


Schematics & HDL combined

 


Design flow

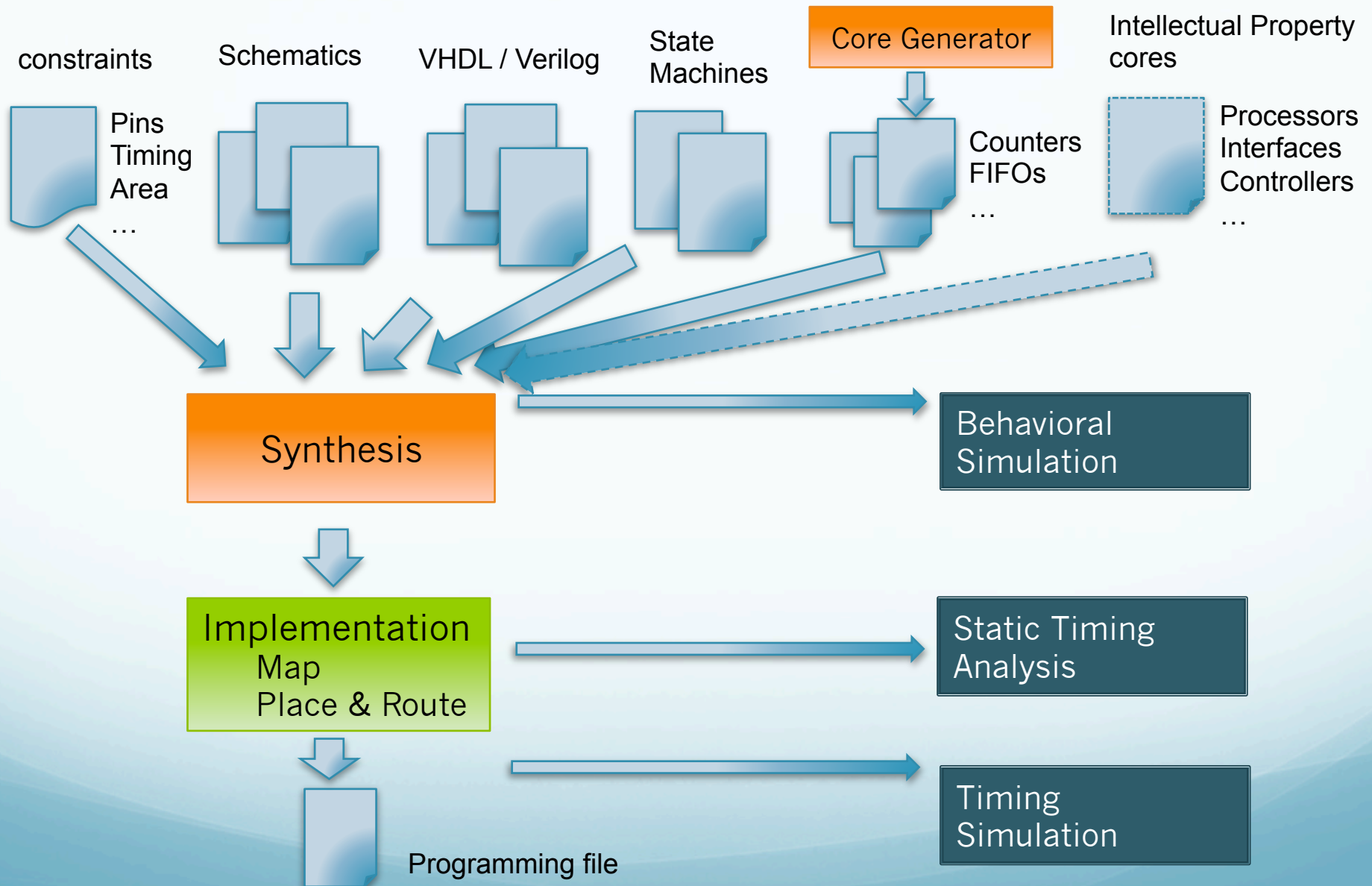


Floorplan (Xilinx Virtex 2)

 


Floorplan (Altera Stratix 4)

 

Simulation

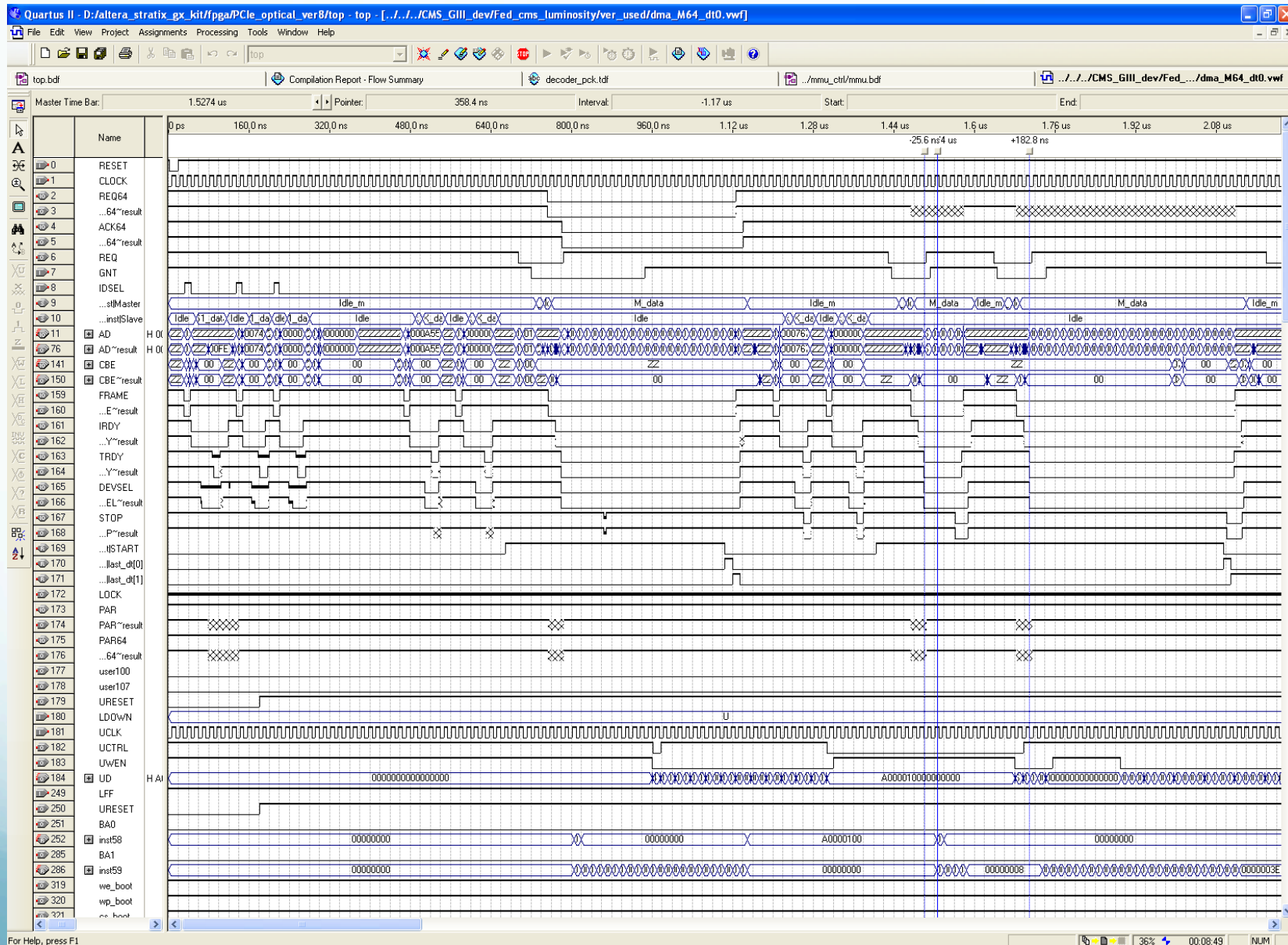

Embedded Logic Analyzers

 

FPGA applications in the Trigger & DAQ domain

First-Level Trigger at Collider



Timing: beam crossings

LHC: 25 ns

detector

Coarse grain data

Full data
(fine grain)

Delay
FIFO

First Level Trigger

Pipelined
Logic

Fixed Latency
(= processing time
of the first
level trigger)


N beam crossings

Trigger decision YES / NO
(for every beam crossing)


De-
randomizer
FIFO

Latency should be short
In order to limit the length
of the delay FIFOs

Pipelined Logic

 

Pipelined Logic – a clock cycle later

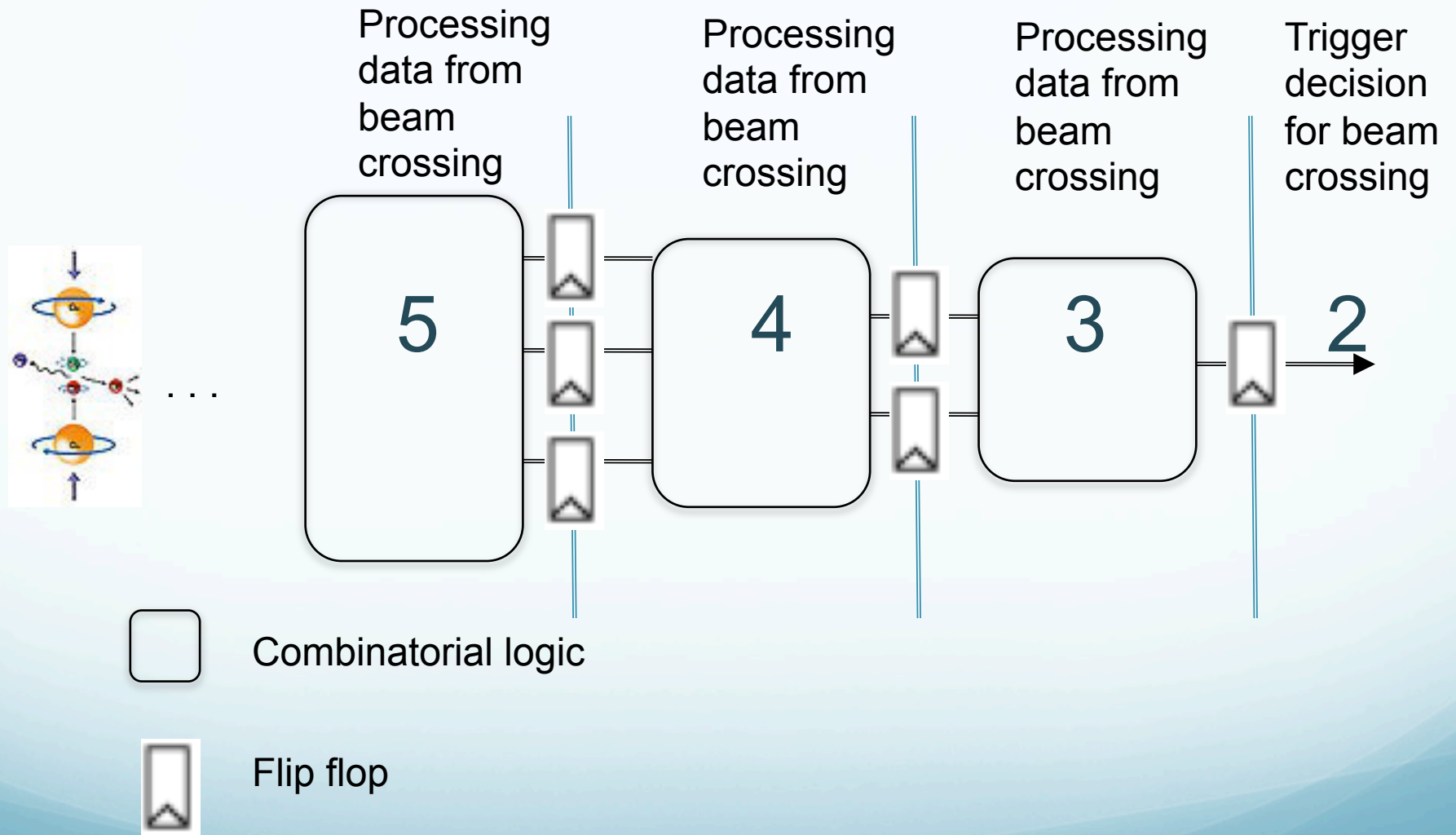

Why are FPGAs ideal for First-Level Triggers ?

- They are fast
 - Much faster than discrete electronics (shorter connections)
- Many inputs
 - Data from many parts of the detector has to be combined
- All operations are performed in parallel
 - Can build pipelined logic
- They can be re-programmed
 - Trigger algorithms can be optimized




Low latency

High performance

Trigger algorithms implemented in FPGAs


- Peak finding
- Pattern Recognition
- Track Finding
- Energy summing
- Sorting
- Topological Algorithms (invariant mass)
- Trigger Control system
- Fast signal merging
- Many more ...

Example: CMS Global Muon Trigger

 


- Input: ~1000 bits @ 40 and 80 MHz
 - Output: ~50 bits @ 80MHz
 - Processing time: 250 ns
 - Pipelined logic one new result every 25 ns
 - 10 Xilinx Virtex-II FPGAs
 - up to 500 user I/Os per chip
 - Up to 25000 LUTs per chip used
 - Up to 96 x 18kbit RAM used
- The CMS Global Muon trigger receives 16 muon candidates from the three muon systems of CMS
 - It merges different measurements for the same muon and finds the best 4 over-all muon candidates

CMS Global Muon Trigger main FPGA

 

Example 2: CMS Fast Merging Modules

 

These modules merge the status of all detector front-ends in CMS in order to throttle the trigger when buffers fill up.

Additionally these modules monitor all status changes of detector frontends.


1 FPGA (Altera) : PCI interface

1 FPGA (Xilinx) :
Merging logic (1 μ s latency)
Monitoring logic
Interface to SRAM

20 inputs


4 outputs

 Example 3: Prototype of future Trigger Board based on Virtex 7 and μ TCA



MP7, Imperial College

 Virtex 7 with 72 x 10 Gb/s transceivers
To be used in the CMS trigger in 2015



FPGAs in Data Acquisition


- Frontend Electronics
 - Pedestal subtraction
 - Zero suppression
 - Compression
 - ...
- Custom data links
 - E.g. SLINK-64
 - Several serial LVDS links in parallel
 - Up to 400 MB/s
- Interface from custom hardware to commercial electronics
 - PCI bus, VME bus, Myrinet, etc.

Example 4: CMS Front-end Readout Link

- SLINK Sender Mezzanine Card: 400 MB / s
 - 1 FPGA (Altera)
 - CRC check
 - Automatic link test

Commercial Myrinet Network Interface Card on internal PCI bus


- Front-end Readout Link Card
 - 1 main FPGA (Altera)
 - 1 FPGA as PCI interface
 - Custom Compact PCI card
 - Receives 1 or 2 SLINK64
 - 2nd CRC check
 - Monitoring, Histogramming
 - Event spy

 

Example 5: CMS Readout Link for Upgrade (2013/14)

10 Gb/s TCP/IP

10 Gb/s TCP/IP

 

Myrinet NIC replaced by custom-built card ("FEROL")

FEROL (FrontEnd Optical Link)
Input from SLINK or from 2x 6Gb/s optical
Output: 2x 10 Gb/s Ethernet optical
TCP/IP sender in FPGA

FPGAs in other domains

- Set-top boxes
- Medical imaging
- Computer vision
- Speech recognition
- Cryptography
- Bioinformatics
- Software-Defined Radio
- Aerospace
- Defense
- Digital Signal Processing
- ASIC Prototyping
- High performance computing
 - Computations performed by FPGA: FFT, Convolution
- Reconfigurable computing

Acknowledgement

- Parts of this lecture are based on material by Clive “Max” Maxwell, author of several books on FPGAs. Many thanks for his kind permission to use his material!



Web lecture: courses.techonline.com

Max@techbites.com , www.TechBites.com

- Many thanks also to Dominique Gigi, who provided material for the lecture and who will be the main tutor for the FPGA exercise

FPGA lab exercise

Lab 6: Programming an FPGA

  

You are going to design the digital electronics inside this FPGA !