



[www.cern.ch](http://www.cern.ch)

# Time Interpolator Mapping from IBM 120nm to TSMC 65nm

Moritz Horstmann  
PH-ESE-ME


# Differences of the Technologies

- CERN uses the TSMC 65nm low power technology, resulting in higher threshold voltages
- Threshold of IBM Low VT MOS is around 200mV;  
of TSMC Low VT MOS around 400mV
- TSMC provides Shallow Trench Isolation (STI) in 65nm, enabling better isolation between different modules

# Mapping


- First approach: Direct mapping by scaling all dimensions to 50%
- Cell runs at more than double the speed
- Higher threshold results in small operation region in which the delay can be controlled
- Matching is worse, especially in the dual- to single-ended buffer

# Maneatis Delay Cell

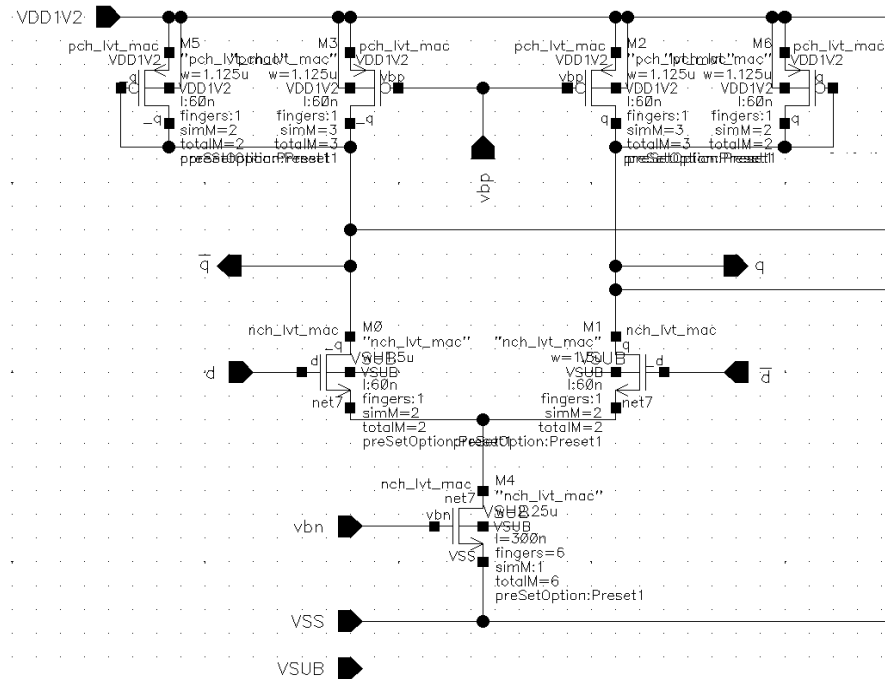


- Length is kept at 50%
- Width of all transistors is scaled to around 75%
- Higher threshold and matching is only partly compensated
- Optimized biasing increases the operating region
- No resistive peaking

# Optimized Biasing

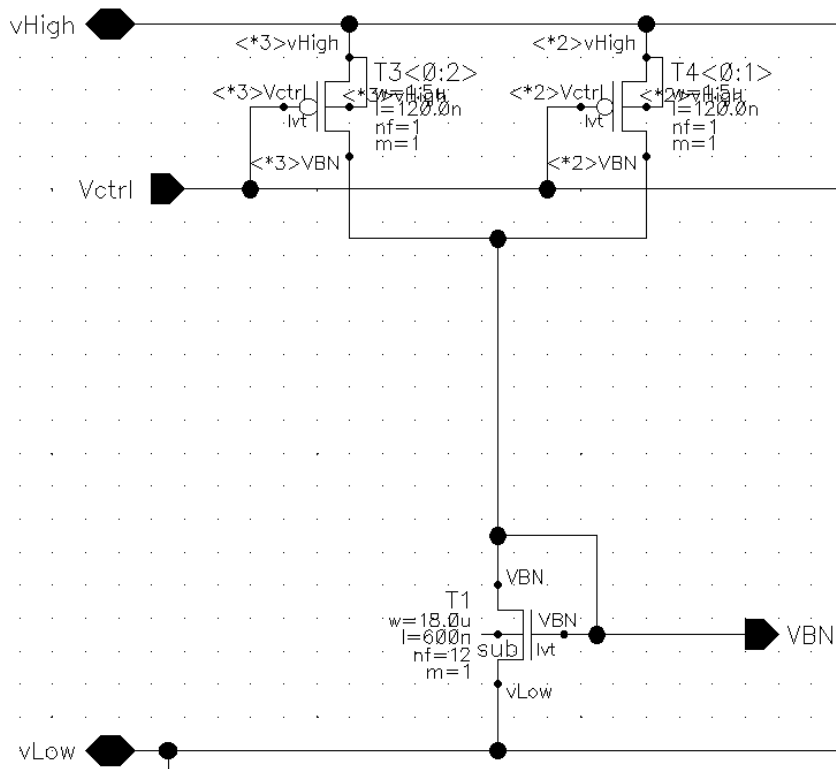


Original Biasing Circuit

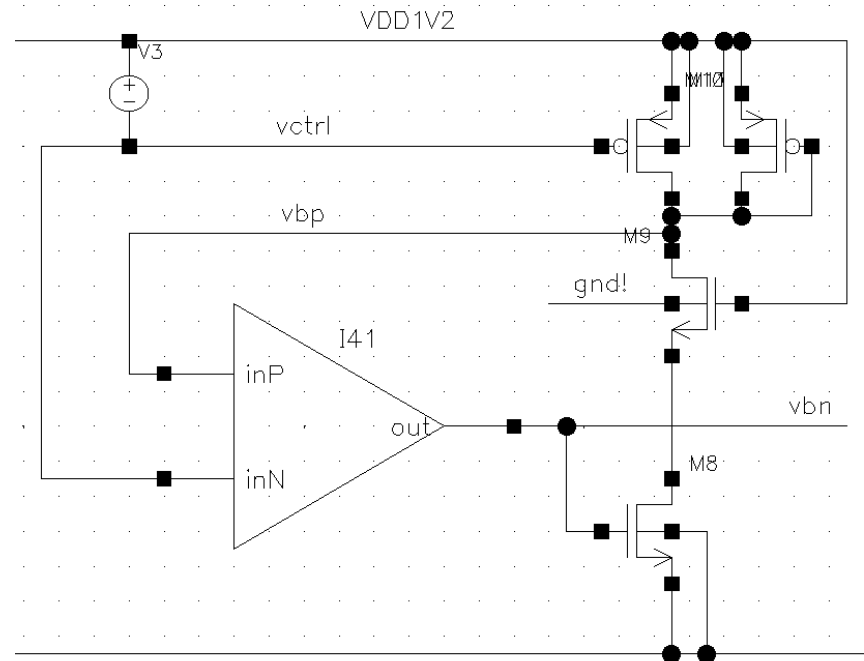


Biassing with Copy of a Branch of the Delay Cell  
 -> vbn can reach VDD1V2


# Operation Region (Post Layout)

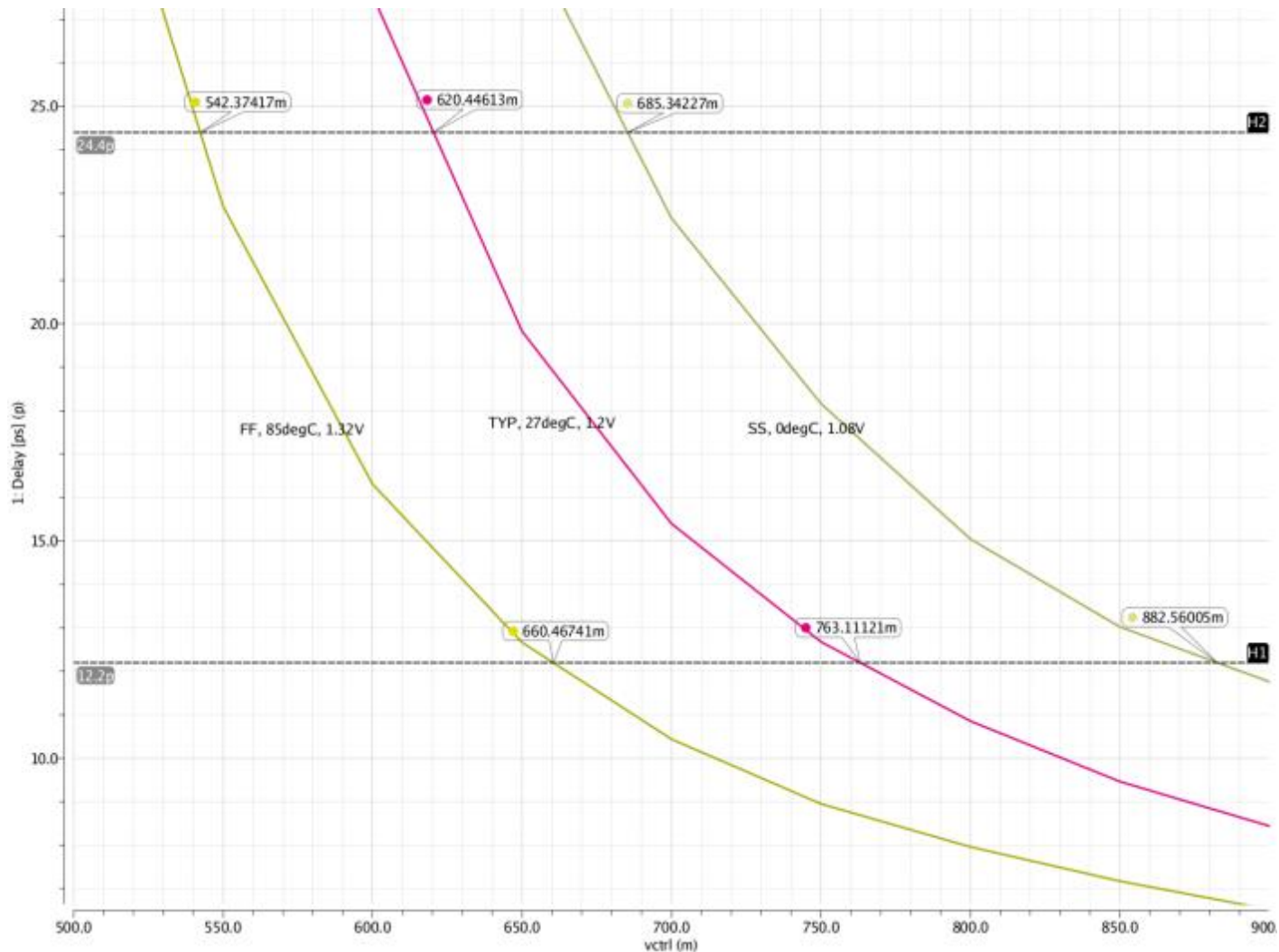

# Faster DE to SE Buffer

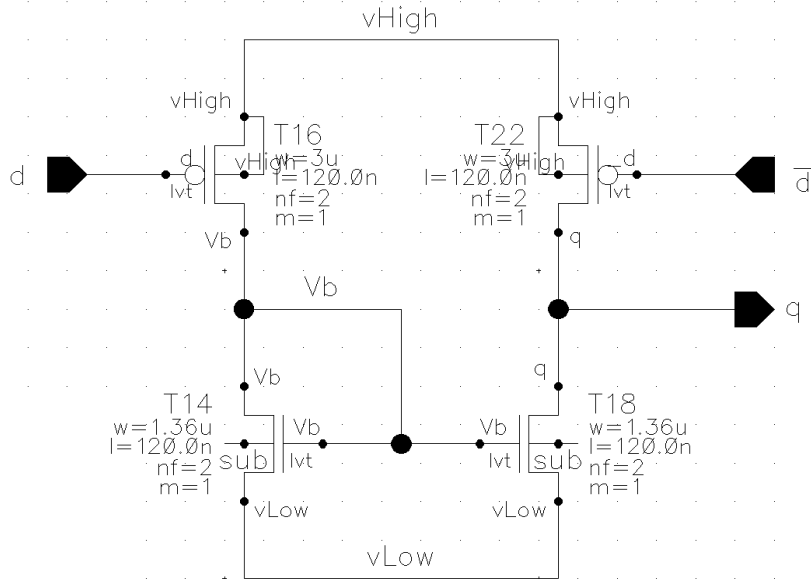

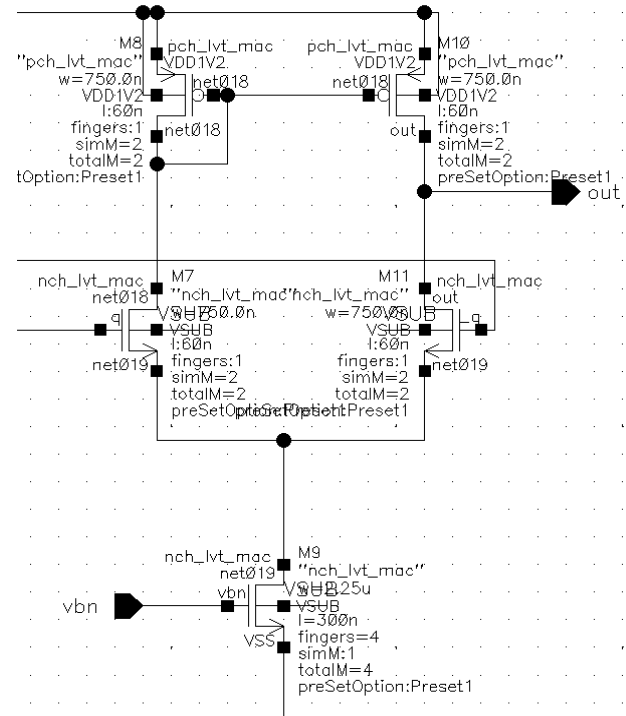
**Original Dual- to Single-Ended Buffer**



**Optimized Design**  
Much faster, resulting in lower mismatch



# Simulation Results

 

# Results Comparison

	TSMC, 12ps	TSMC, 24ps	IBM, 20ps
<b>Absolute Mismatch Delay Element</b>	0.30ps	0.78ps	0.49ps
<b>Relative Mismatch Delay Element</b>	2.4%	3.2%	2.5%
<b>Absolute Mismatch After DE2SE Buffer</b>	0.72ps	1.75ps	2.43ps
<b>Relative Mismatch After DE2SE Buffer</b>	5.9%	7.2%	11.2%
<b>DE2SE Buffer Delay</b>	13ps	17ps	47ps
<b>Power Consumption</b>	38mW	13mW	28mW

Mismatch: 1-sigma variation

Power: 32 delay cells + DE to SE buffers + drivers

TSMC simulations include extracted parasitics, IBM simulations not



[www.cern.ch](http://www.cern.ch)