



PLL

PLL architecture and LC-tank

Content



- PLL architecture
- VCO LC-tank

PLL architecture

- Architecture choice
 - 3rd order PFD charge-pump PLL
 - Reference spur, CP-noise X N, Divider noise
 - Subsample PLL
 - CP-noise not multiplied, No divider
 - Sampled loop-filter
 - Low reference spur
 - Multiplying DLL
 - Only for high bandwidth, low reference jitter
- With low bandwidth, reference spur is less severe.
- More complex = more radiation sensitive

PLL architecture

- 3rd order optimal PLL system

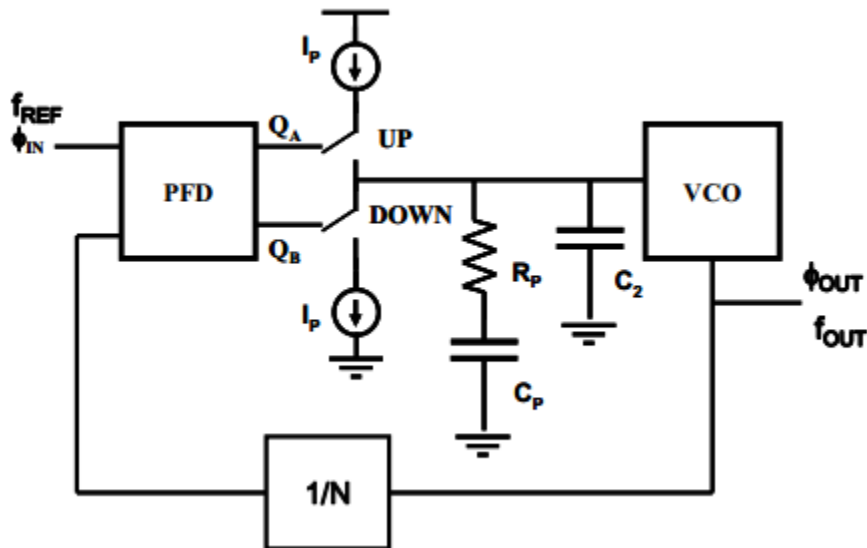 

$$F(s) = \frac{K_{pd} \left(1 + \frac{s}{\omega_z}\right)}{s \left(1 + \frac{s}{\omega_p}\right)}$$

$$\omega_n = \frac{\omega_{-3dB}}{\sqrt{1 + 2\zeta^2 + \sqrt{(1 + 2\zeta^2)^2 + 1}}}$$



$$\omega_z = \frac{\omega_n}{2\zeta}$$

$$\omega_p = \omega_z (2\zeta)^4$$

$$K = \omega_n^2 N$$

PLL architecture

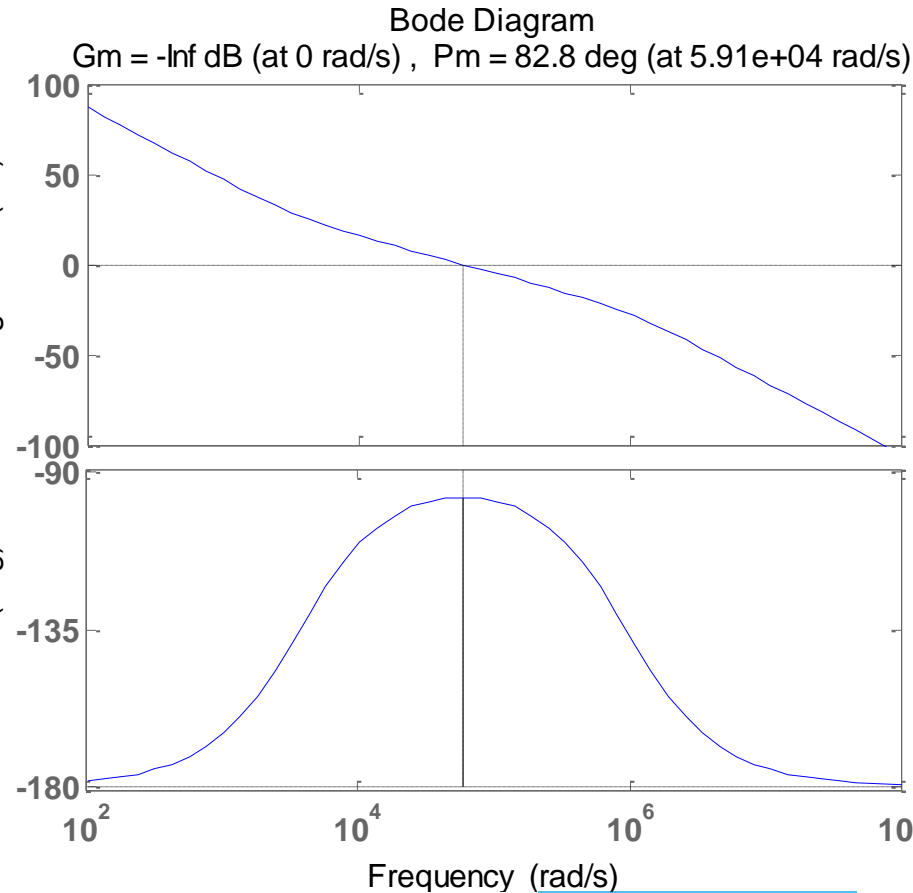 - E.g. 10 kHz (62.8 krad/s) closed loop bandwidth



PLL architecture


- Matlab model is ready
 - Noise calculations
 - System generation
- For low bandwidth PLL, VCO is most important
- Master thesis is working on rad-hard lock detector
- To be determined
 - Frequency range
 - Bandwidth range
 - Type of programming, how to tune BW
 - # of steps , constant damping ...
- Components in AMS kit?

Jitter

$$Jitter = \sqrt{\frac{1}{\omega_0^2} \int_{f_{min}}^{f_{max}} S_{\phi}(f) df}$$

Better VCO = Lower BW allowed!
 
$$\text{where } S_{\phi}(f) = \sum_i \phi_{noise,i}(f) H_i(f)$$



Phase noise

- LC-tank phase noise sources
 - Inductor's R_s
 - Active $-1/g_m$ element (equivalent A. R_s noise)
 - Capacitor less important at this frequency

$$v_n^2(f) = kTR_s(1 + A) \left(\frac{\omega_0}{\Delta\omega}\right)^2$$

- LC-tank amplitude

$$v_{tank}^2 = \frac{4}{\pi} i_{tail} R_p \quad \text{or} \quad v_{sat}$$


- Phase noise depends on noise AND signal power

$$S_\phi(f) = \frac{v_n^2(f)}{v_{tank}^2}$$


Phase noise

- R_s and current determine the phase noise
- What L gives best phase noise?
 - Depends on power consumption and maximum swing
- For given power, take smallest L with best Q that places the VCO near voltage limited region



Q-factor

 

Phase noise

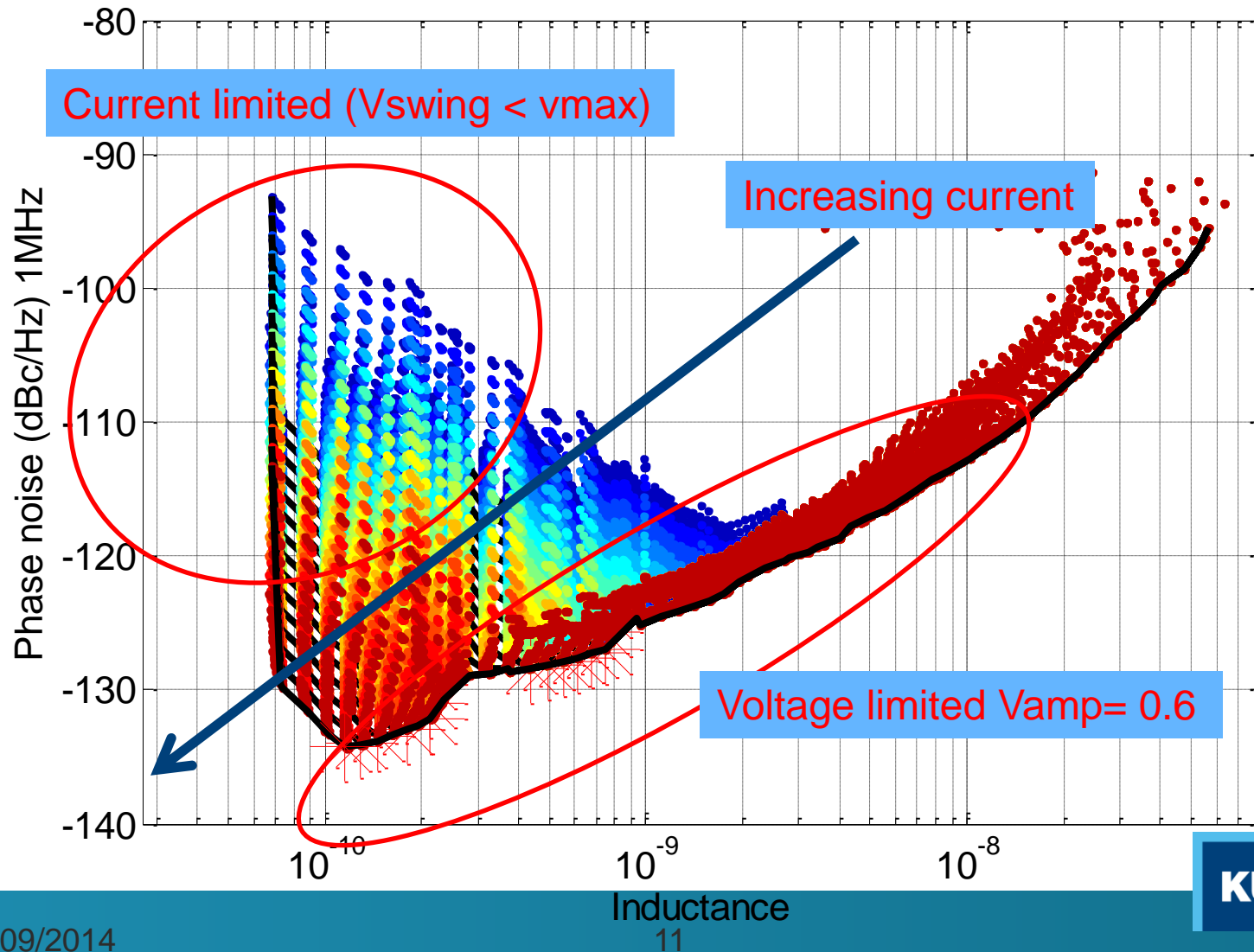

Phase noise

 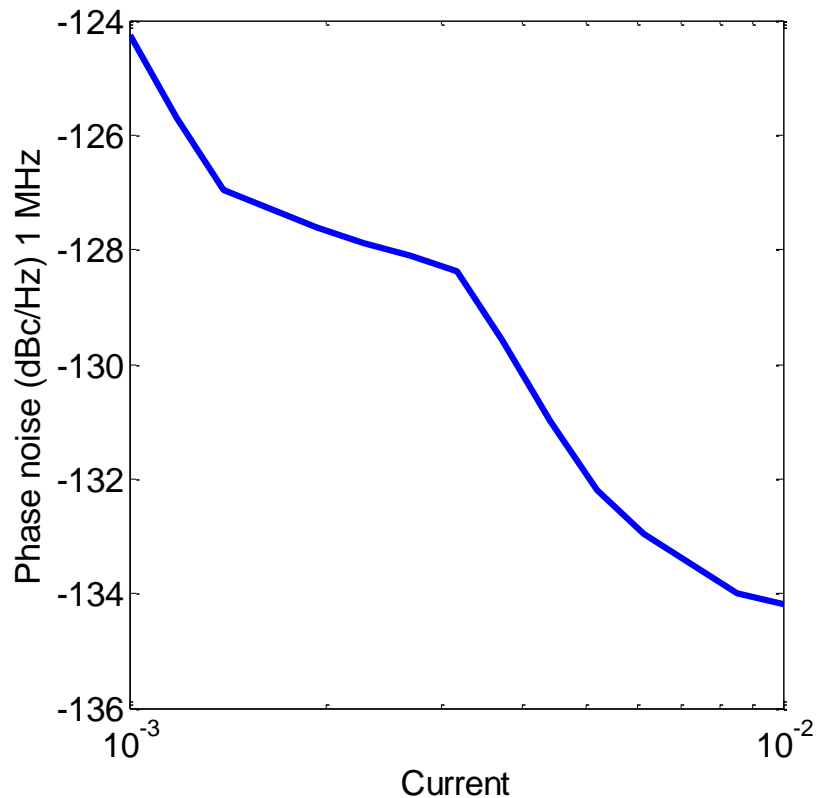

For given power consumption, best phase noise for L that gives largest swing.

-> larger L above voltage limited range = worse PN (more noise at the same signal power)

-> lower L has less noise but also less R_p so lower amplitude and more PN.


-> Optimal L depends on power consumption.

-> Higher power = smaller inductor = less R_s = less voltage noise

Discussion of LC usage

- VCO FOM
 - $20\log(f_0 / P_{df}) - PN(@df)$
 - ± 223 dB
 - This number can compare different VCOs at different frequencies!
 - Indicates the phase noise relative to power consumption

Jitter

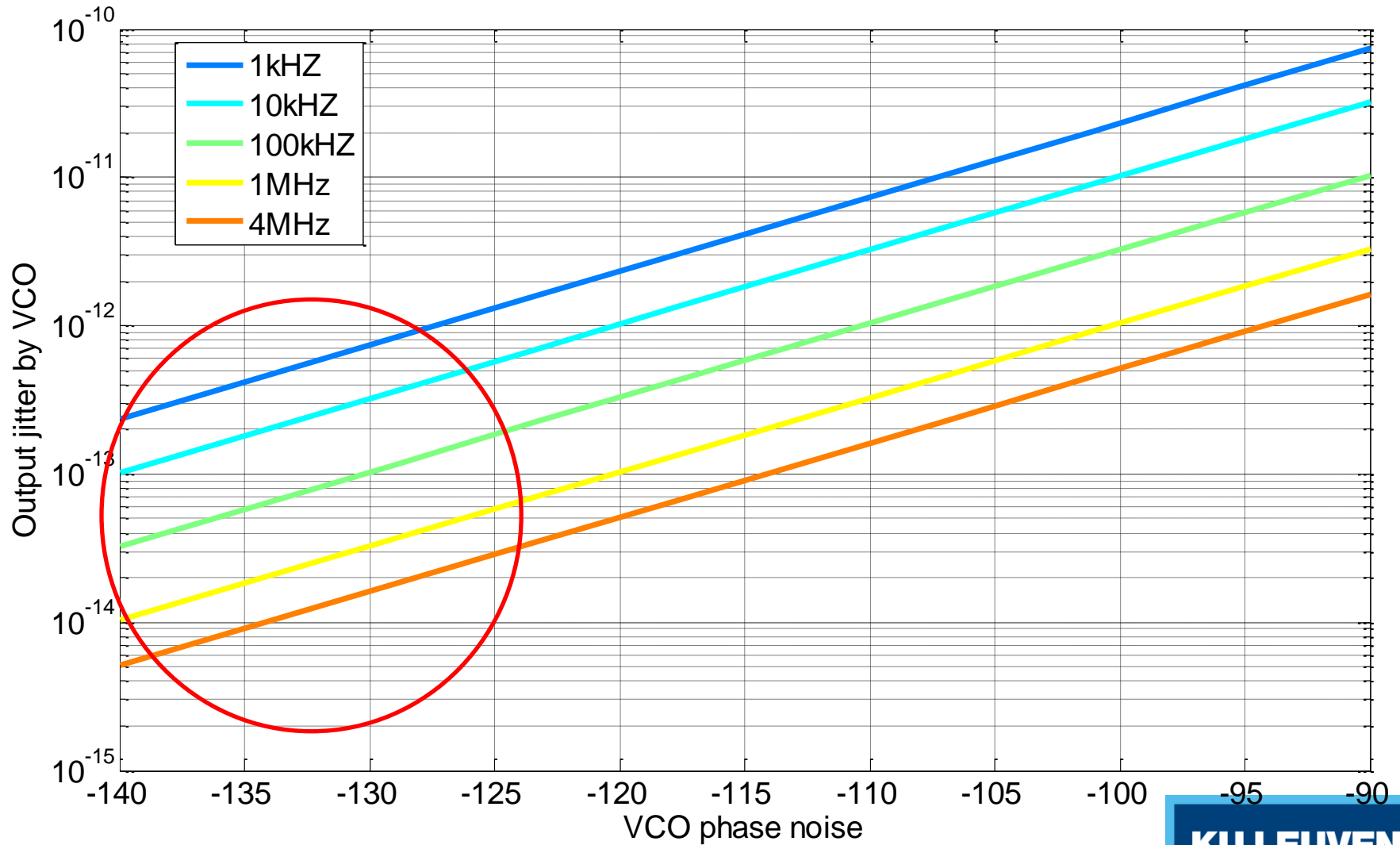

To be discussed

- Bandwidth tuning
- Frequency ranges
- Oscillator type (FOM? Rad-hard?)
- Power consumption