

CERN

European Organization for Nuclear Research


Organisation Européenne pour la Recherche Nucléaire

# ***Power converters***

***Definitions and classifications***  
***Converter topologies***

***Frédéric BORDRY***  
***CERN***

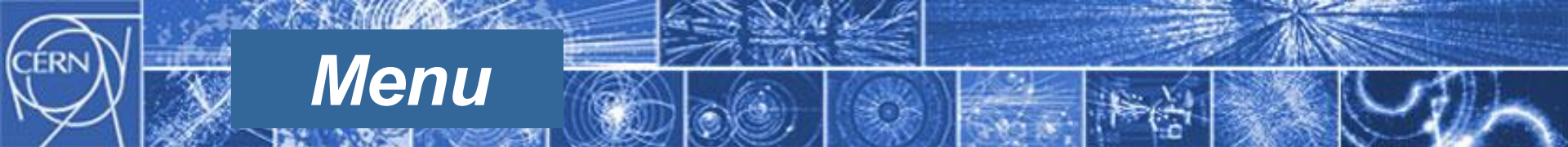**Introduction to Accelerator Physics 2009**  
**Special CAS@CERN**  
**23<sup>rd</sup> – 27<sup>th</sup> February 2009**  
**Divonne**



# Menu

- Power converter definition and classification
- Power converter topologies: *commutation*  
Sources, switches,...semiconductors
- Special case for magnet powering  
(Voltage source - Current source)
- Pulsed power converters
- Control and precision

In 1 hour ????



# ***Power converters : Definitions***

**The source of the beam blow-up when we could not prove it was the RF** (Control room operator)

**A powerful (small) black box able to convert MAD files into currents** (Accelerator Physics group member)

**An equipment with three states, ON, OFF and FAULT** (Another operator)

**Is it the same thing as a power supply?** (Person from another physics lab)

**A big box with wires and pipes everywhere and blinking lamps. Occasionally it goes BANGG!** (Former PO secretary view)



# ***Power converters : Definitions (cont'd)***

**That which feeds the magnets (a visitor)**

**A stupid installation taking a non-sinusoidal current at poor power factor (Power distribution engineer)**

**A standard piece of equipment available from industry off-the-shelf (a higher management person, not in in this room !)**

# Energy source




# Applications


## Power converter

The task of a power converter is to process and control the flow of electric energy by supplying voltages and currents in a form that is optimally suited for user loads.

Control

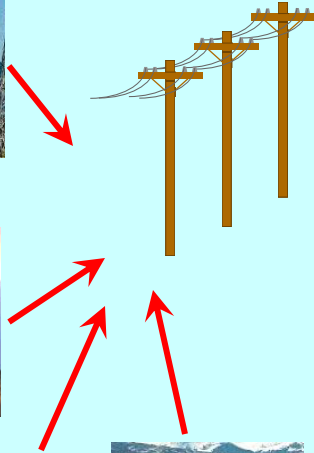

50 or 60 Hz ; AC

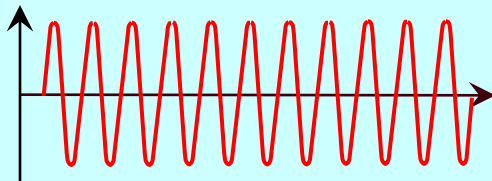


Traction and auxiliary



Domestic Appliance




Medical applications

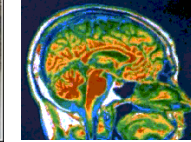


Industrial applications, Welding, Induction Heating, ....



DC current


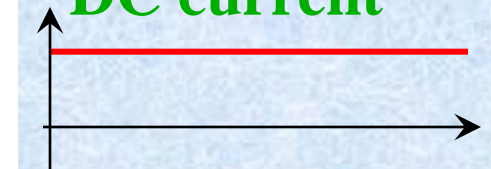




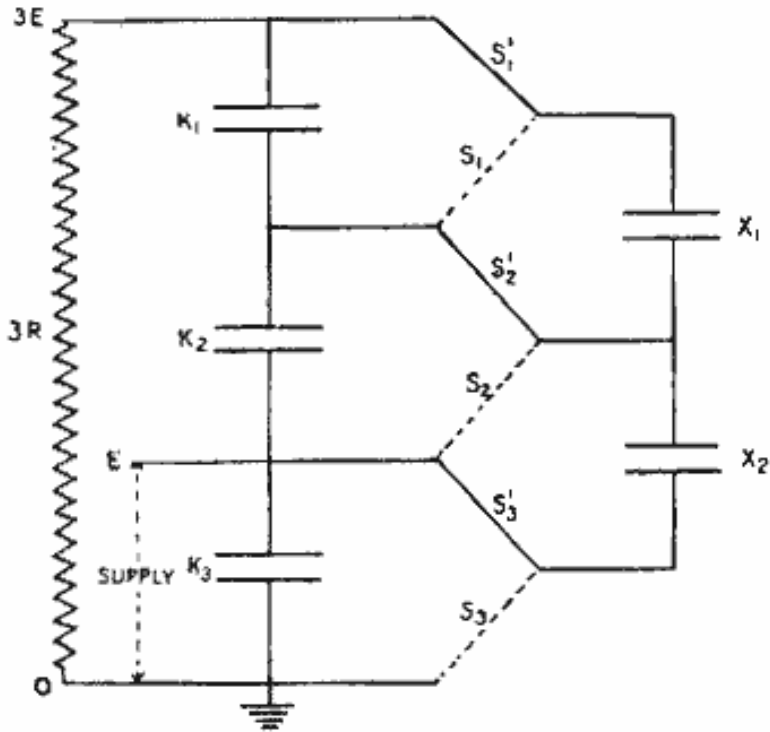

**Schematic of Cockcroft and Walton's voltage multiplier. Opening and closing the switches  $S$  transfers charge from capacitor  $K_3$  through the capacitors  $X$  up to  $K_1$ .**

**Voltage multiplier : switches...**

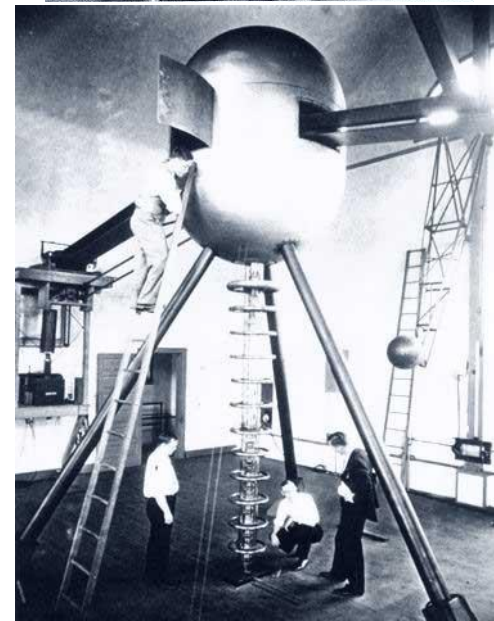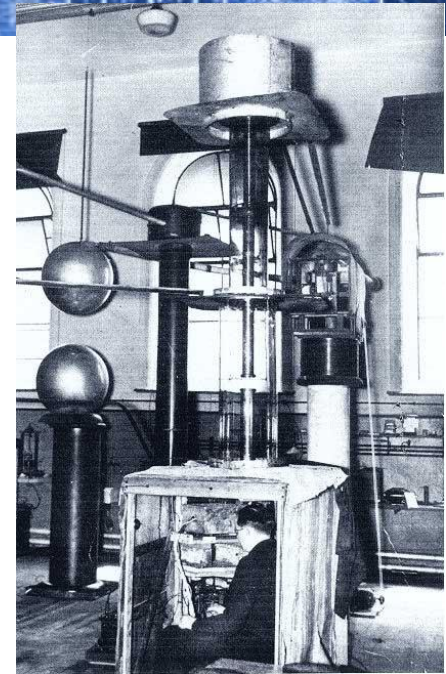

“On a new principle for the production of higher voltages.”


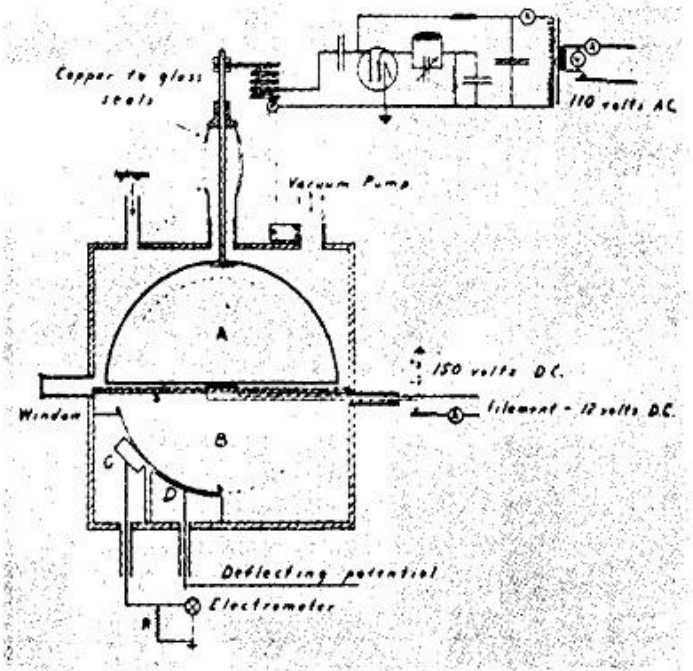


Diagram of the first successful cyclotron constructed by Lawrence and M. S. Livingston. The single dee is five inches in diameter.

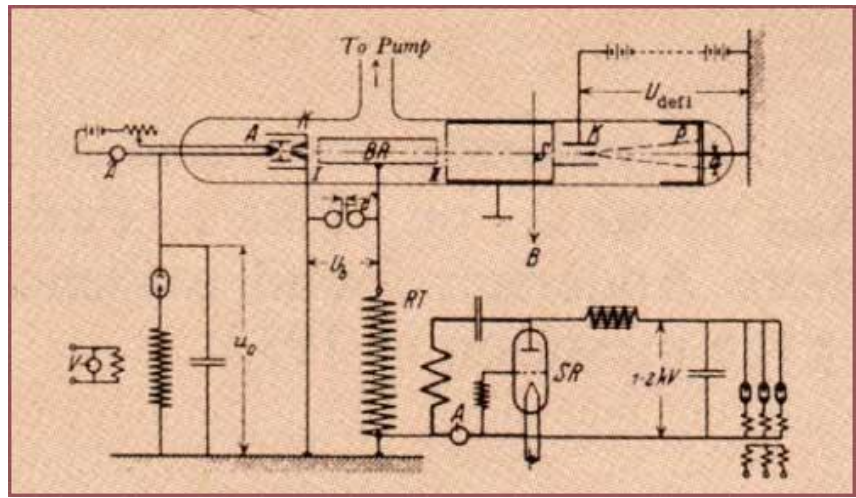

The difficulties of maintaining high voltages led several physicists to propose accelerating particles by using a lower voltage more than once. Lawrence learned of one such scheme in the spring of 1929, while browsing through an issue of *Archiv für Elektrotechnik*, a German journal for electrical engineers. Lawrence read German only with great difficulty, but he was rewarded for his diligence: he found an article by a Norwegian engineer, Rolf Wideröe, the title of which he could translate as “On a new principle for the production of higher voltages.” The diagrams explained the principle and Lawrence skipped the text.




# Once upon a time... not so far

Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009



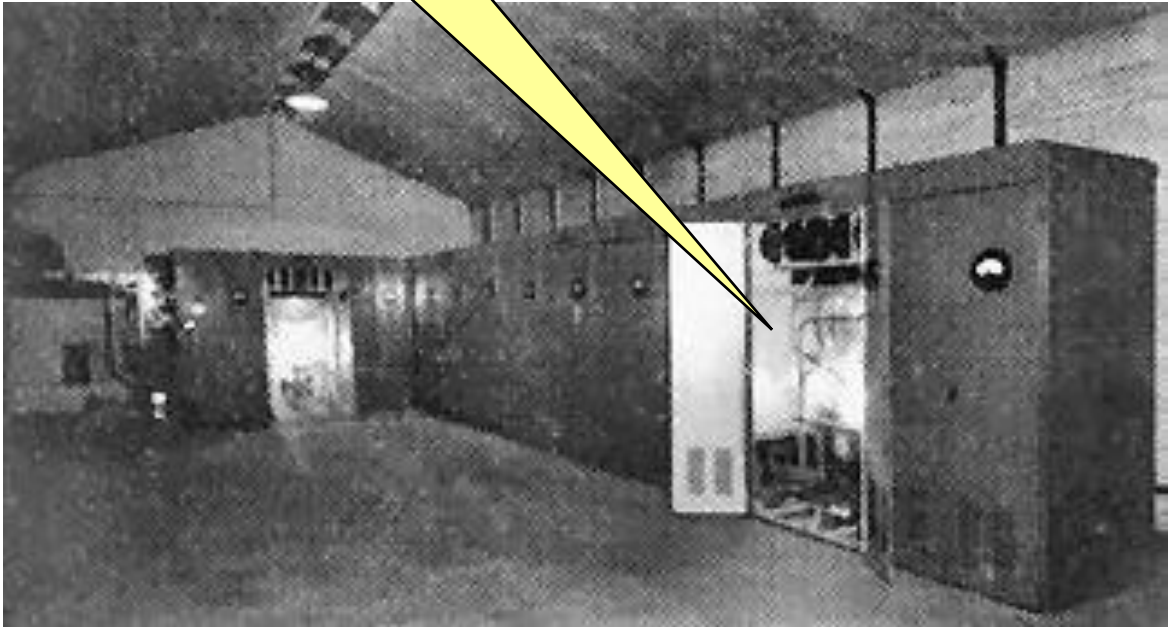
**This is a 6-phase device, 150A rating with grid control. It measures 600mm high by 530mm diameter.**







# In the beginning... for high power

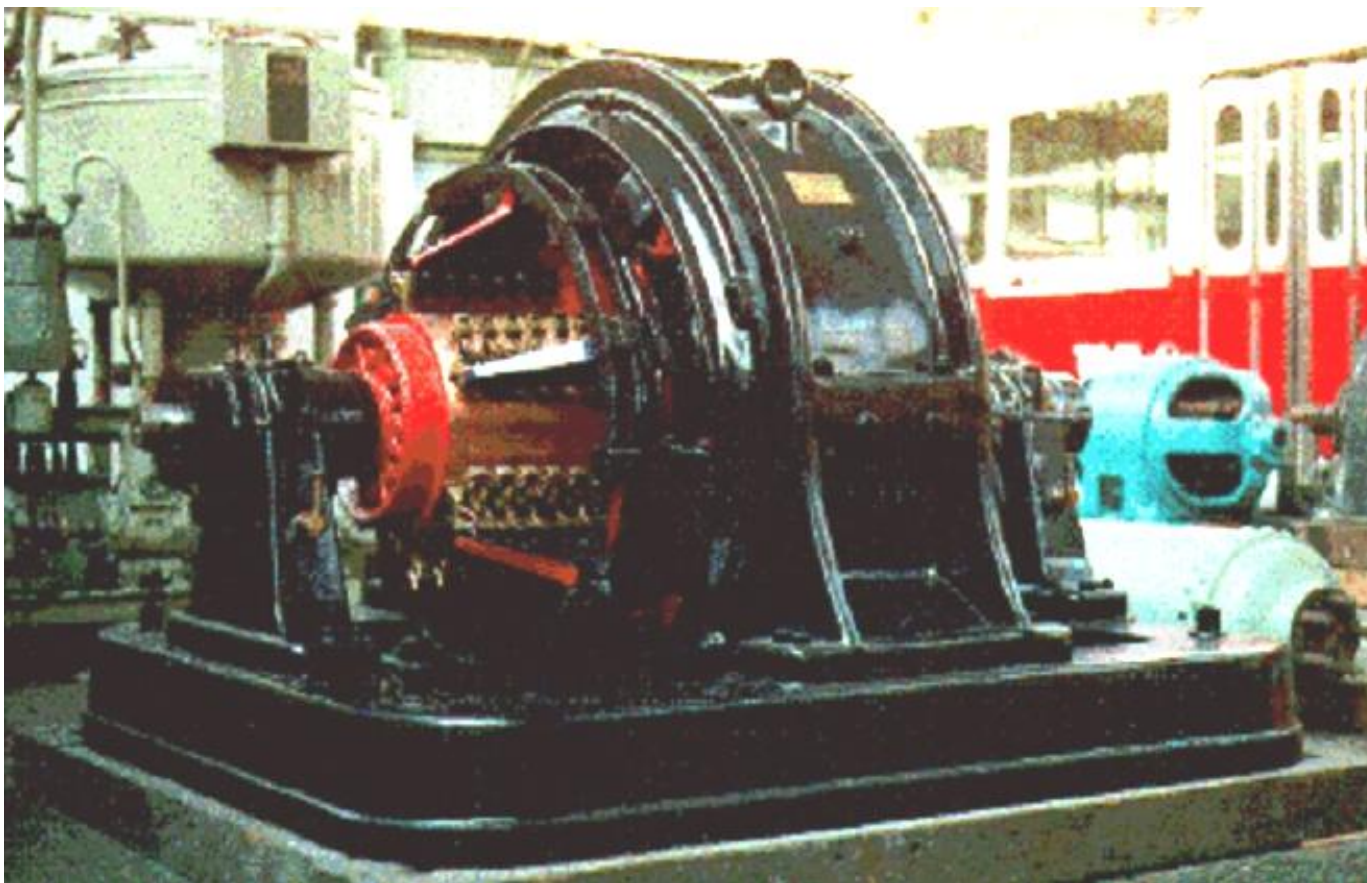

**une commutatrice des tramways de Saint-Etienne, datant de 1907 et ayant fonctionné jusqu'en avril 1991**

Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009


# and still now in “old” accelerators...

## Brookhaven National Laboratory - AGS



By courtesy: I. Marneris

## CERN - PS

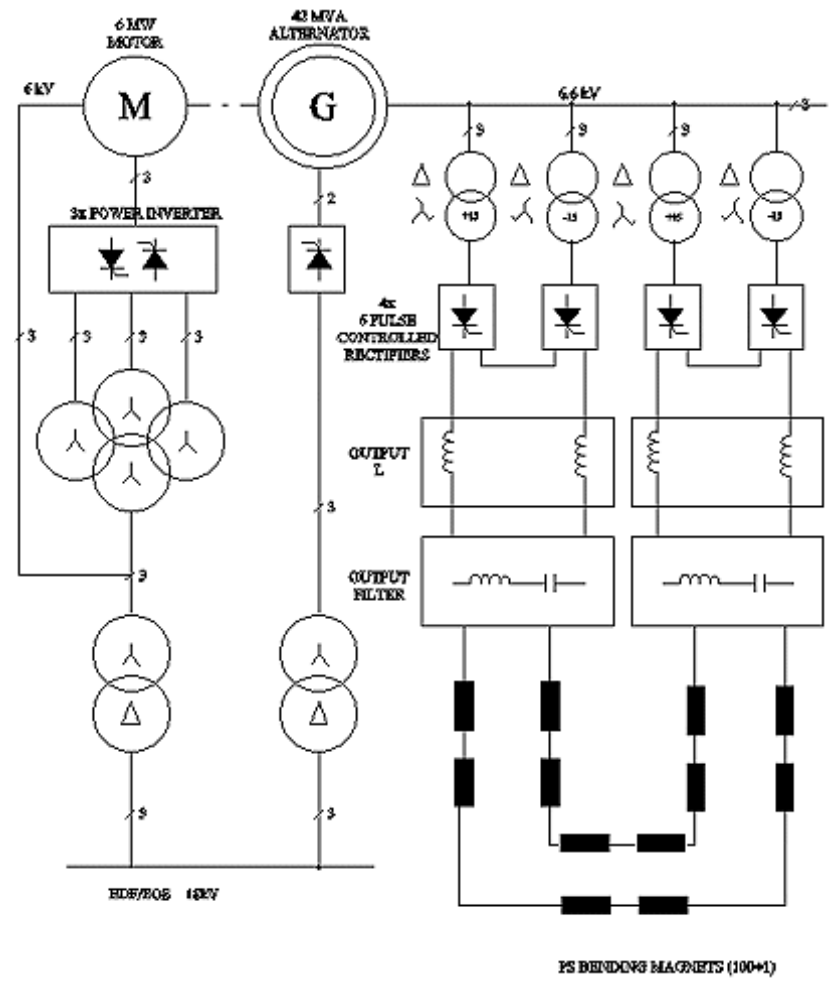



# Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 200 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)

In general, accelerator designers are not power converter experts and vice versa.



Interface is the list of **power converter specifications.**

**The apparent belief on one side that anything is possible and the impression on the other side that the specification have been chosen at random, sometimes leads to rather cynical feelings**

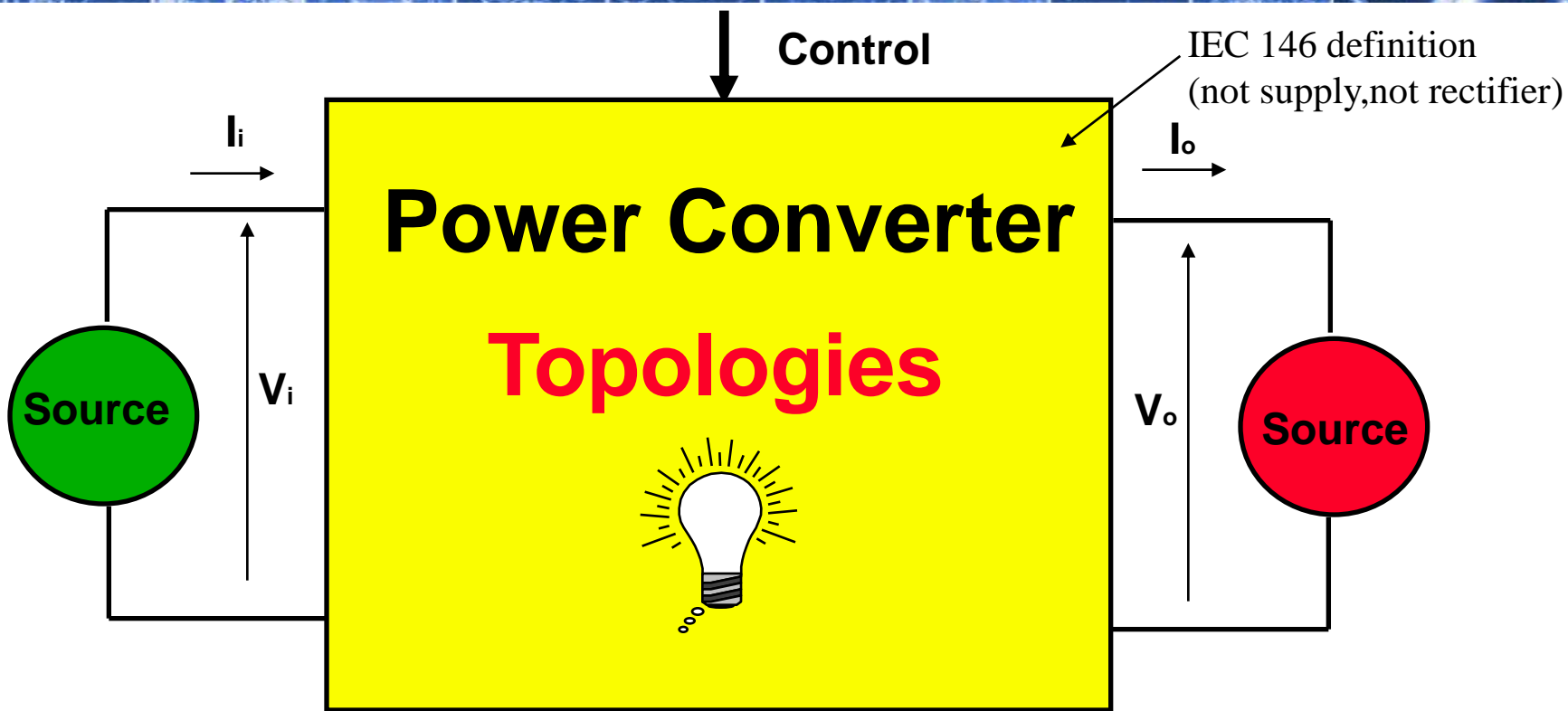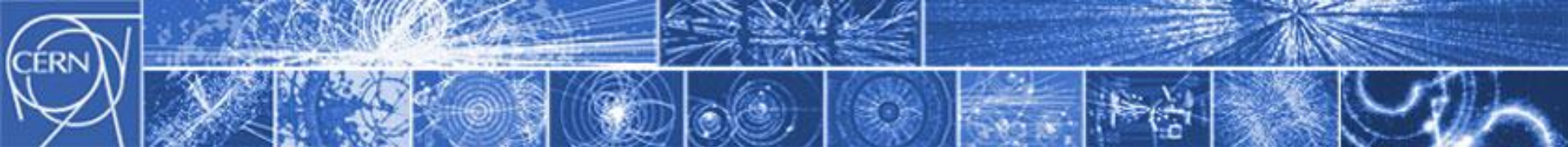**such as:**

- if in doubt, ask an extra order of magnitude, there is never a problem or whatever it is, or**
- however it is calculated, 1 in  $10^3$  will be good enough in the end and they'll never note the ripple and the zero crossing !!!**






Electrical energy transfer

**Power Converter Design**

- performance
- efficiency
- reliability (MTBF), reparability (MTTR),
- effect on environment (RFI, noise,...)
- low cost

# Converter classification

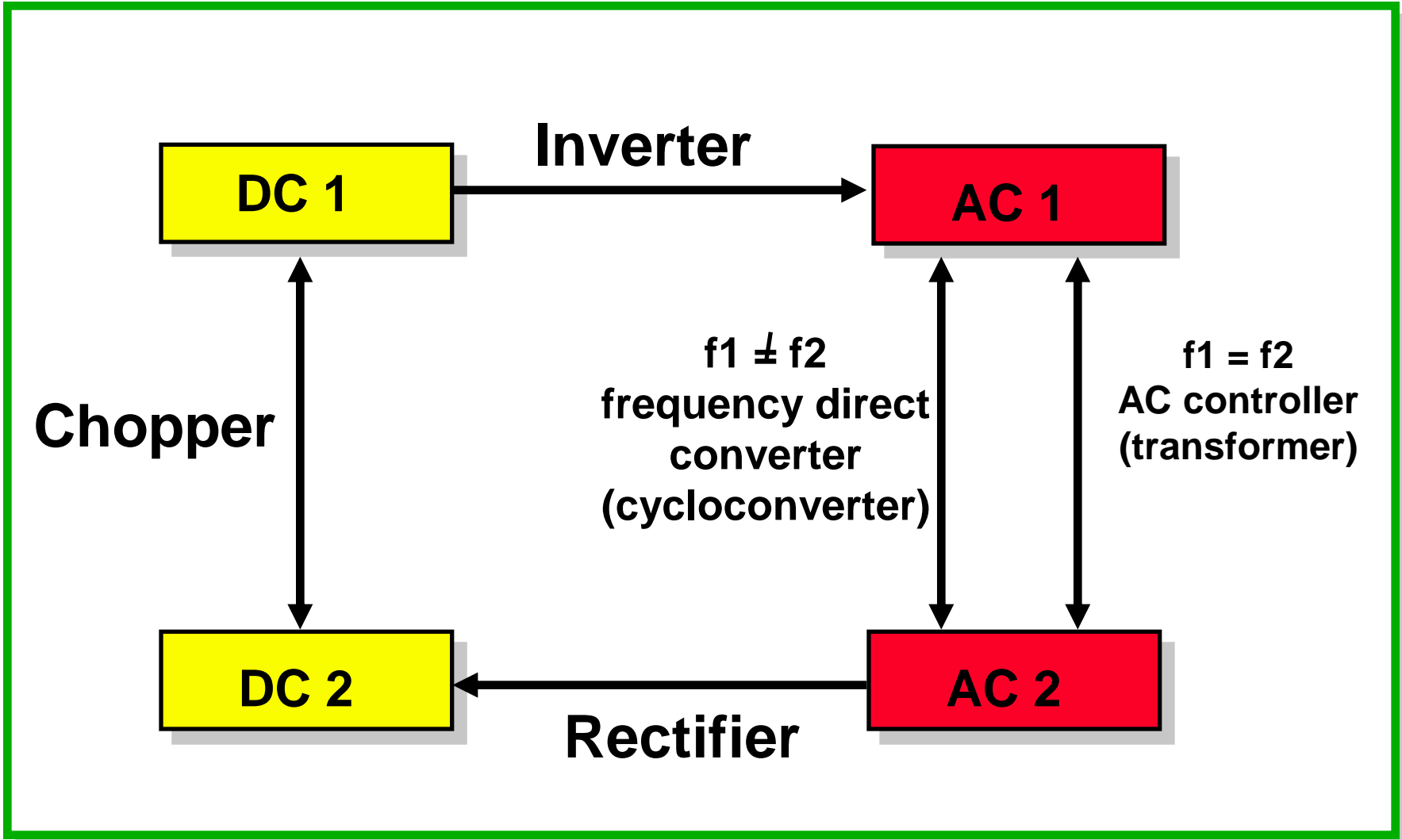



# Source definition

**Source definition:** any element able to impose a voltage or a current, independently of, respectively, the current flowing through, or the voltage imposed at its terminals.

**A source could be a generator or a receptor.**

Two types of sources:



## Voltage source

which imposes a voltage independently of the current flowing through it. This implies that the series impedance of the source is zero (or negligible in comparison with the load impedance)
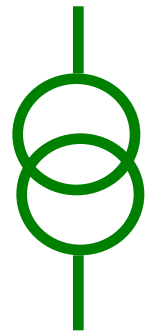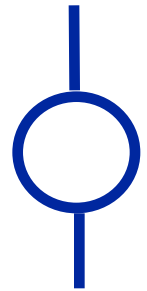
## Current source


which imposes a current independently of the voltage at its terminals.

This implies that the series impedance of the source is infinite (or very large in comparison with the load impedance)







**L**




$E_L = \frac{1}{2}LI^2$

**I state variable**

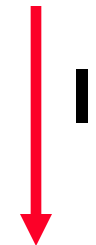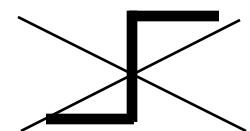
$di/dt \neq \infty$

**→**



 
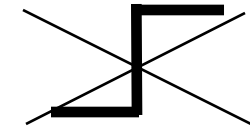
**“ Current source “**

**C**




$E_c = \frac{1}{2}CV^2$

**V state variable**


$dV/dt \neq \infty$

**→**



**“ Voltage source “**



# Eight types of sources (reversibility)

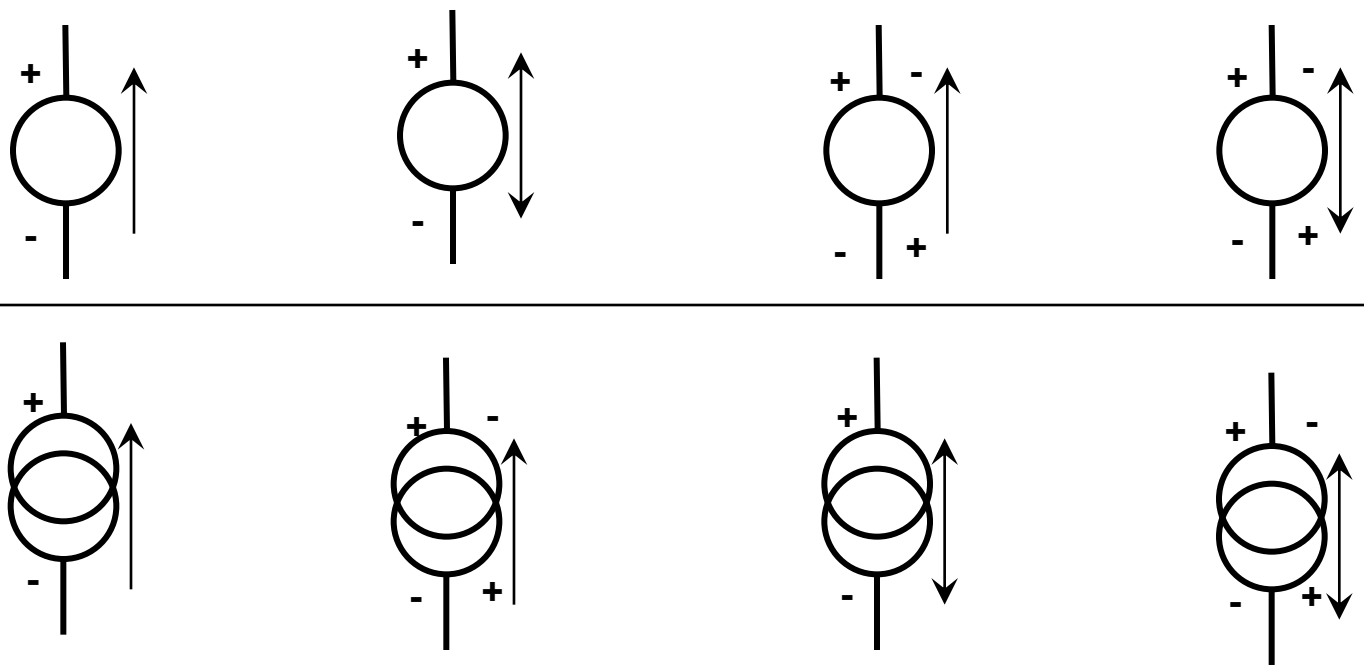

**Unidirectional source**  
 voltage : if the voltage, across its terminal, can't change sign  
 current : if the current, flowing through it, can't reverse

**Bidirectional (reversible) source :**  
 voltage : if the voltage, across its terminal, can change sign  
 current : if the current, flowing through it, can reverse

## Introductory example

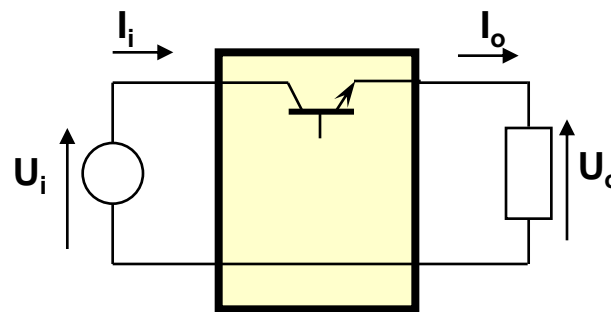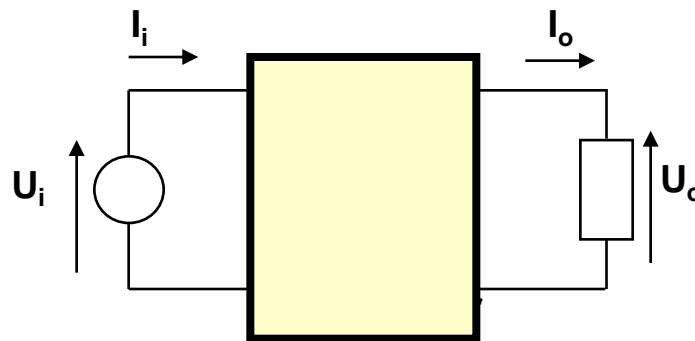

Linear solution

Transfer of energy between


- DC voltage source  $U_i$
- DC source (nature is not defined) :  $U_o, I_o$




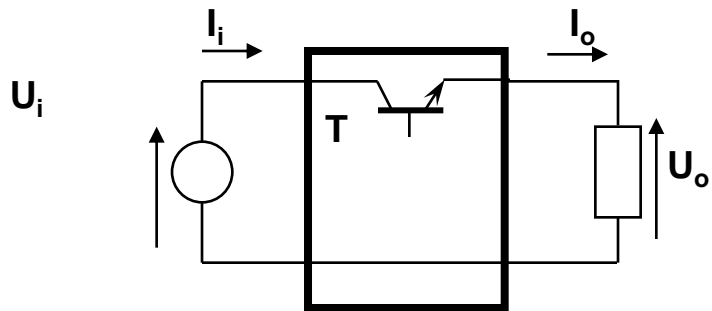
# Linear solution

$$U_i = 24V ; U_o = 10 V \text{ and } I_o = 600A$$



$$P_o = U_o \cdot I_o = 10 \cdot 600 = 6'000 \text{ W}$$

$$P_T \text{ (power dissipated by the switch)} = U_T \cdot I_T = (U_i - U_o) \cdot I_o = (24 - 10) \cdot 600 = 8'400 \text{ W}$$

$$\text{Converter efficiency} = P_o / (P_T + P_o) = 42 \% \text{ !!!!!}$$


Furthermore, it'll be difficult to find a **component (semiconductor) able to dissipate 8'400 W** .

**Then impossible for medium and high power conversion**

## Commutation

$$\left. \begin{array}{l} - U_T = 0 \text{ if } I_T \neq 0 \\ - I_T = 0 \text{ if } U_T \neq 0 \end{array} \right\} P_T = 0$$


~~Linear mode~~

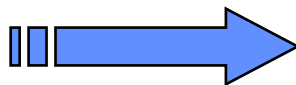


**switch mode  
(saturated-blocked)**

# Commutation

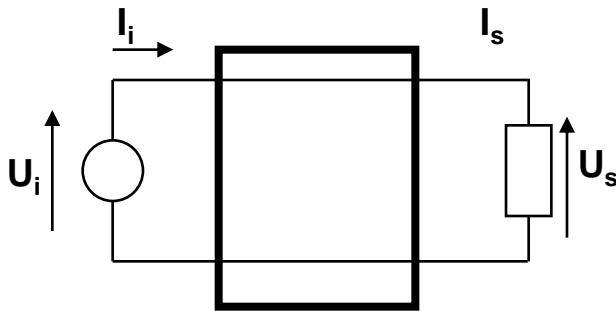
**Active components used as switches to create a succession of link and no link between sources to assure an energy transfer between these sources with high efficiency.**



Direct Link

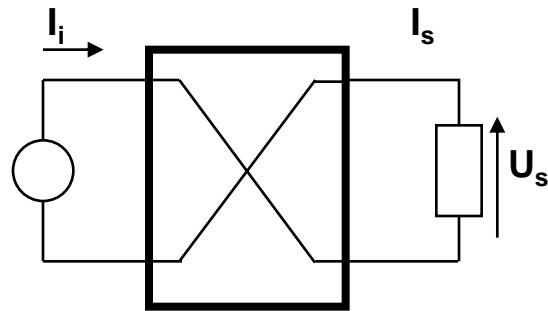


Inverse Link

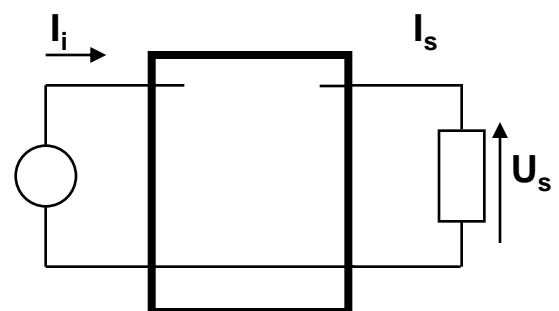


Open Link
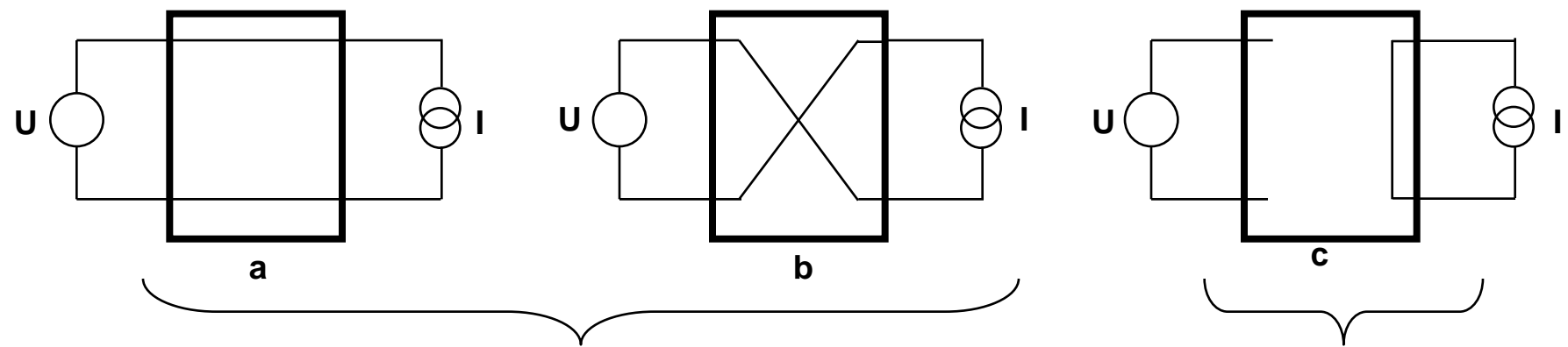
# Direct link configuration : Direct voltage-current converters



**Connexion**  
(energy flow between sources)

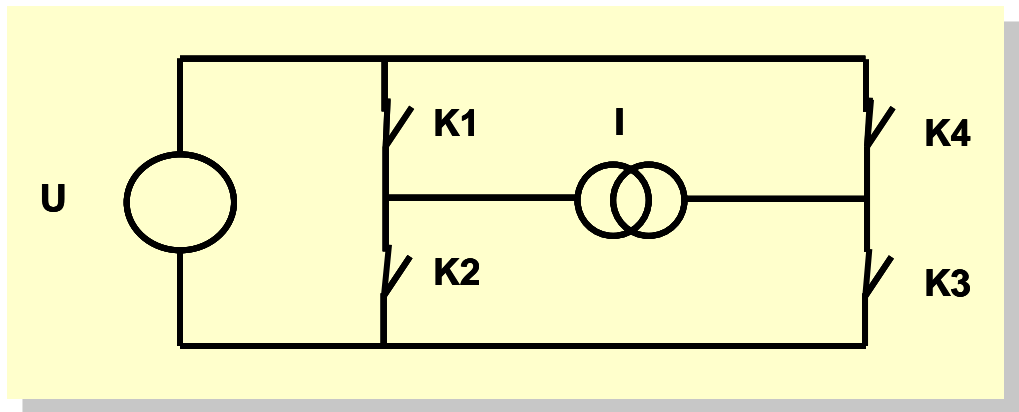
**Disconnexion**  
(current source short-circuited,  
voltage source open circuited)



- K1 and K3 closed => a
- K2 and K4 closed => b
- K1 and K4 (or K2 and K3) closed => c




# Special case for linear application

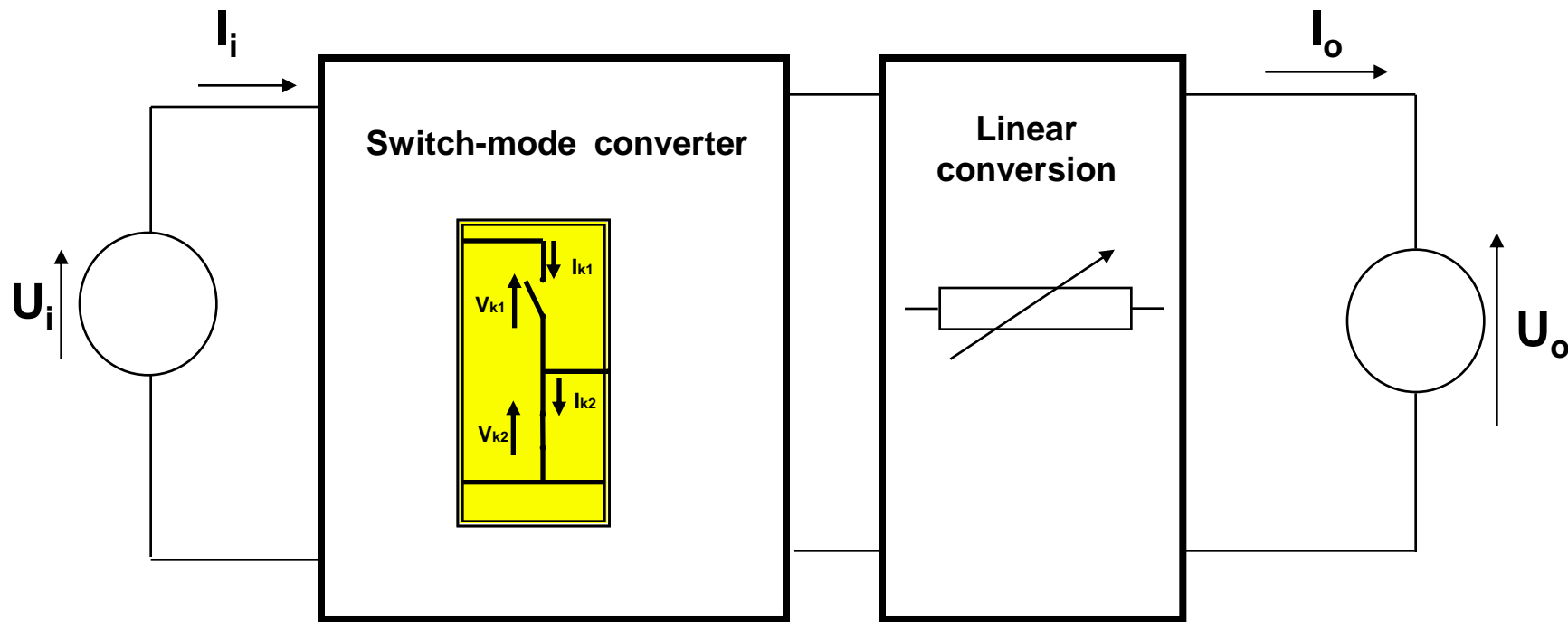



- Active filter
- 4-quadrant converters
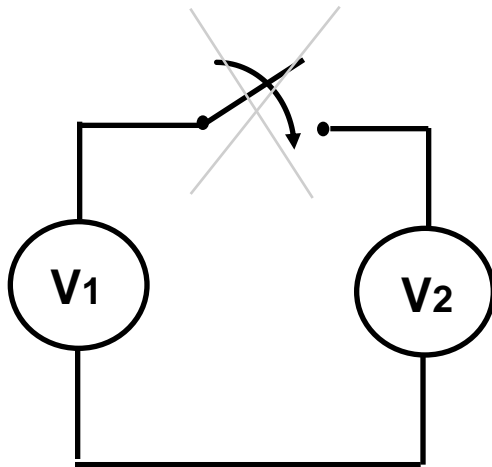
# Commutation rules

- *electronic switches modify the interconnection of impeding circuits*
- *any commutation leading instantaneous variations of a state variable is prohibited*



Turn On impossible

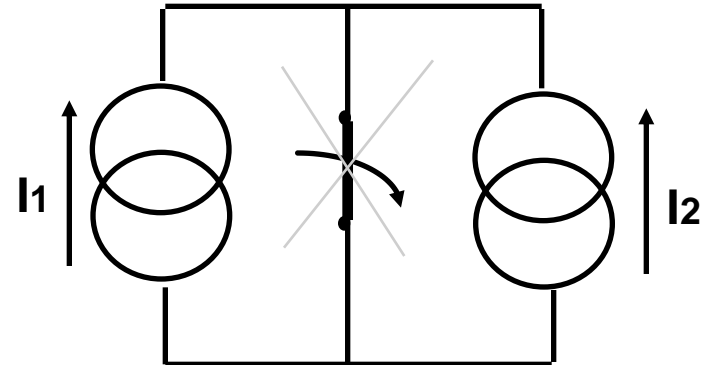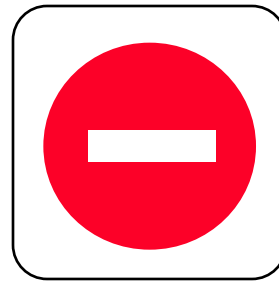


Turn Off impossible

Interconnection between two impeding networks can be modified only if :



- **the two networks are sources of different natures (voltage and current)**
- **the commutation is achieved by TWO switches. The states of the two switches must be different.**
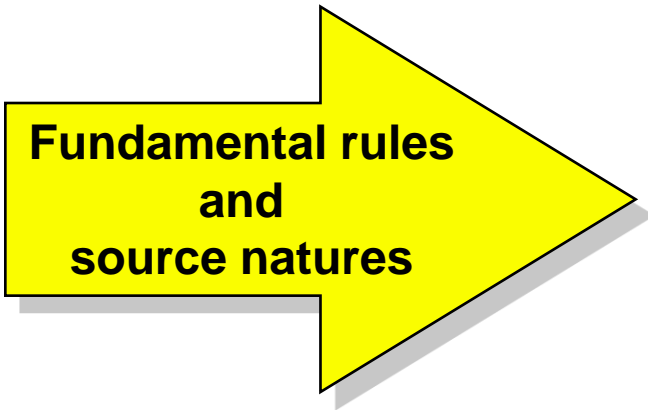
# Power Converter topology design: the problem

the interconnection of sources by switches



switch characteristics

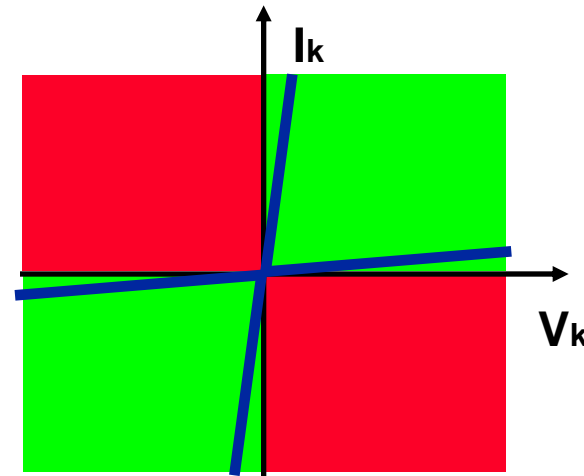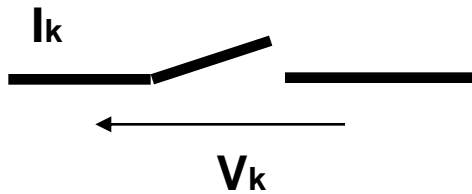


# Switch characteristics

**Switch** : *semiconductor device functioning in commutation*

*The losses in the switch has to be minimized*


*Zon very low*

*Zoff very high*

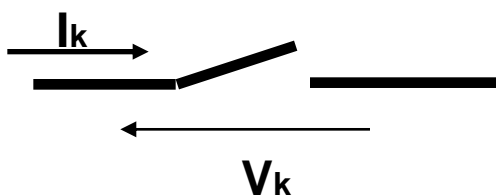


**Switch** : at least two orthogonal segments

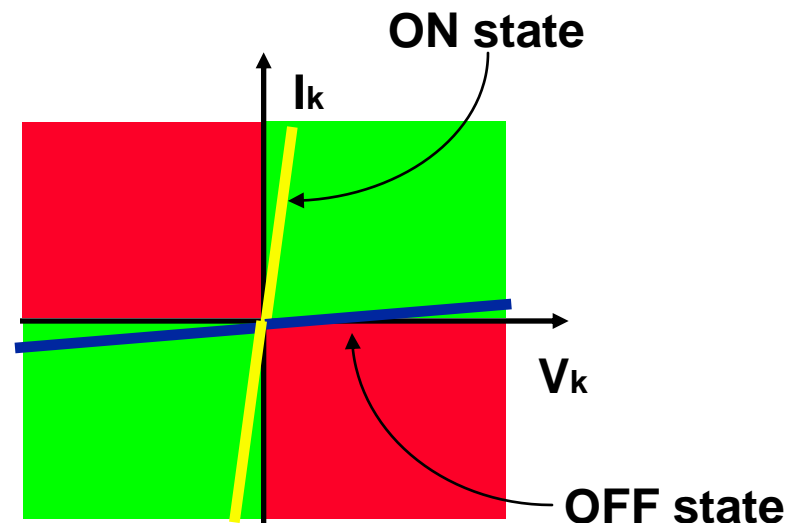(short and open circuit are not switches)







# Switches : *Dynamic characteristics*

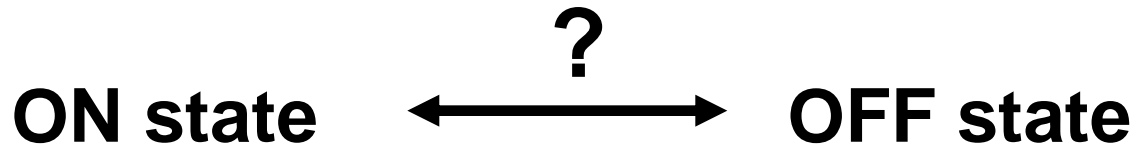

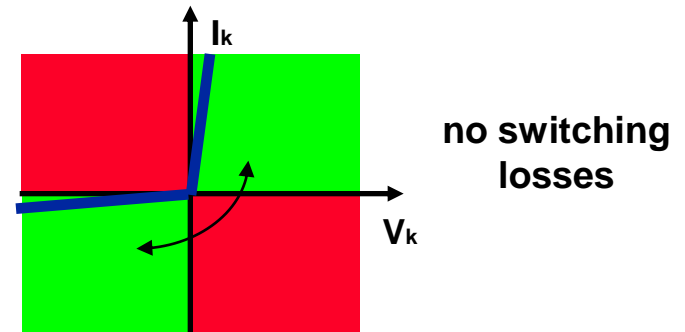- **spontaneous commutation**  
 change of quadrant  
*(auto turn-on ; auto turn-off)*






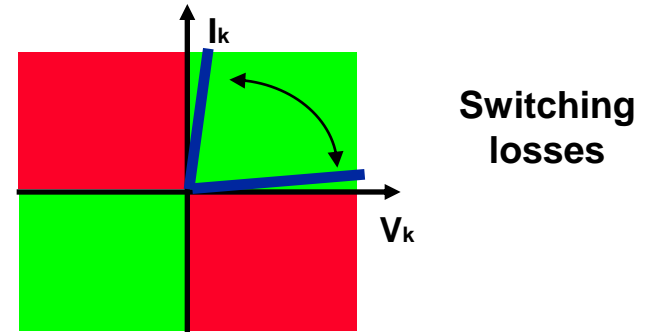- **controlled commutation**  
 no change of quadrant  
*(controlled turn-on ; controlled turn-off)*



↓  
**gate**

# Power Semiconductors

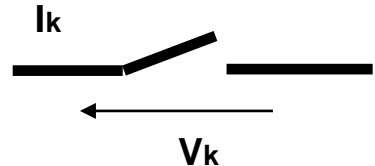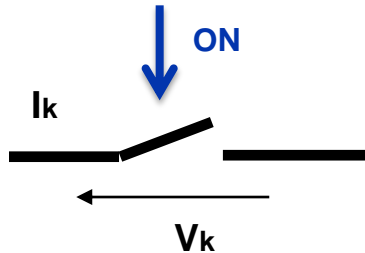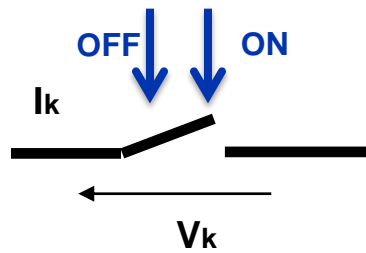

## Power Semiconductors

### Turn-off Devices

### Thyristors

### Diodes




#### Transistors

#### Thyristors


- Fast
- Line commutated
- Avalanche

- MOSFETs
- Darlingtons
- IGBTs

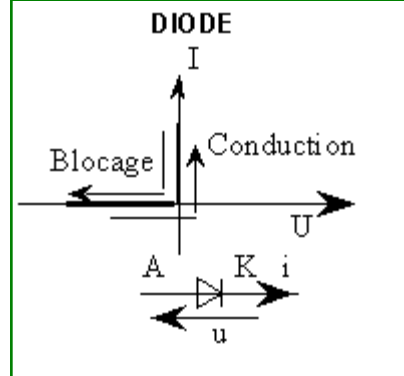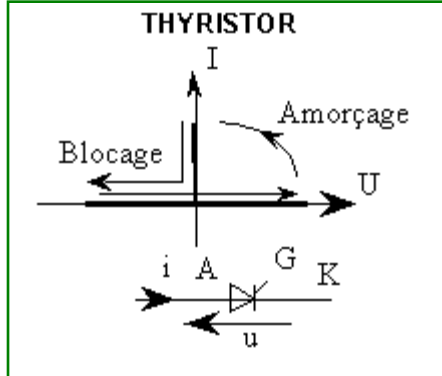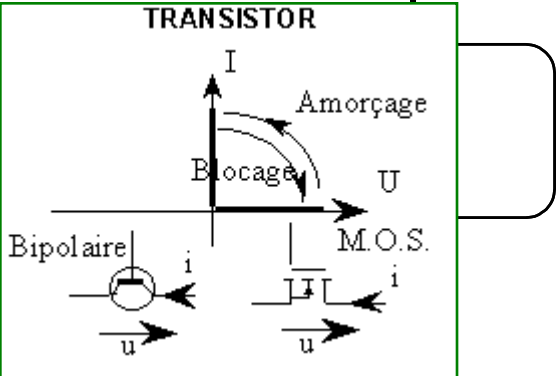- Line commutated
- Fast
- Bi-directional
- Pulse



# Evolution of Power semiconductors

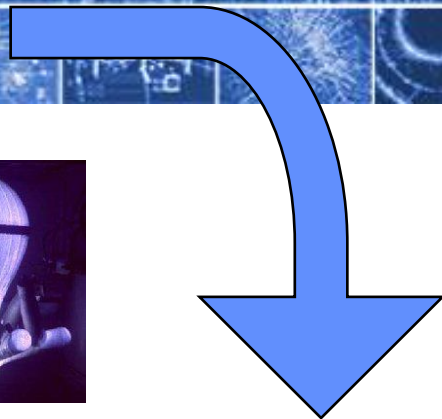

**From mercury arc rectifier, grid-controlled vacuum-tube rectifier, inignitron ,....**



## Power Electronics

**From 1960**


**Power Diode and Thyristor  
or SCR (Silicon-Controlled Rectifier )**



**Link to frequency of the  
electrical network  
50 Hz (60 Hz)**

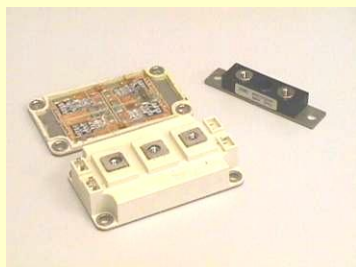**From 1985**



**High frequency power semiconductors :  
MosFet, IGBTs , GTOs, MCTs,....**



**High frequency => high  
performances (ripple,  
bandwidth, perturbation  
rejection,...)  
small magnetic  
(volume, weight)**



# Power Converter for magnets

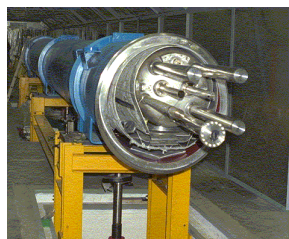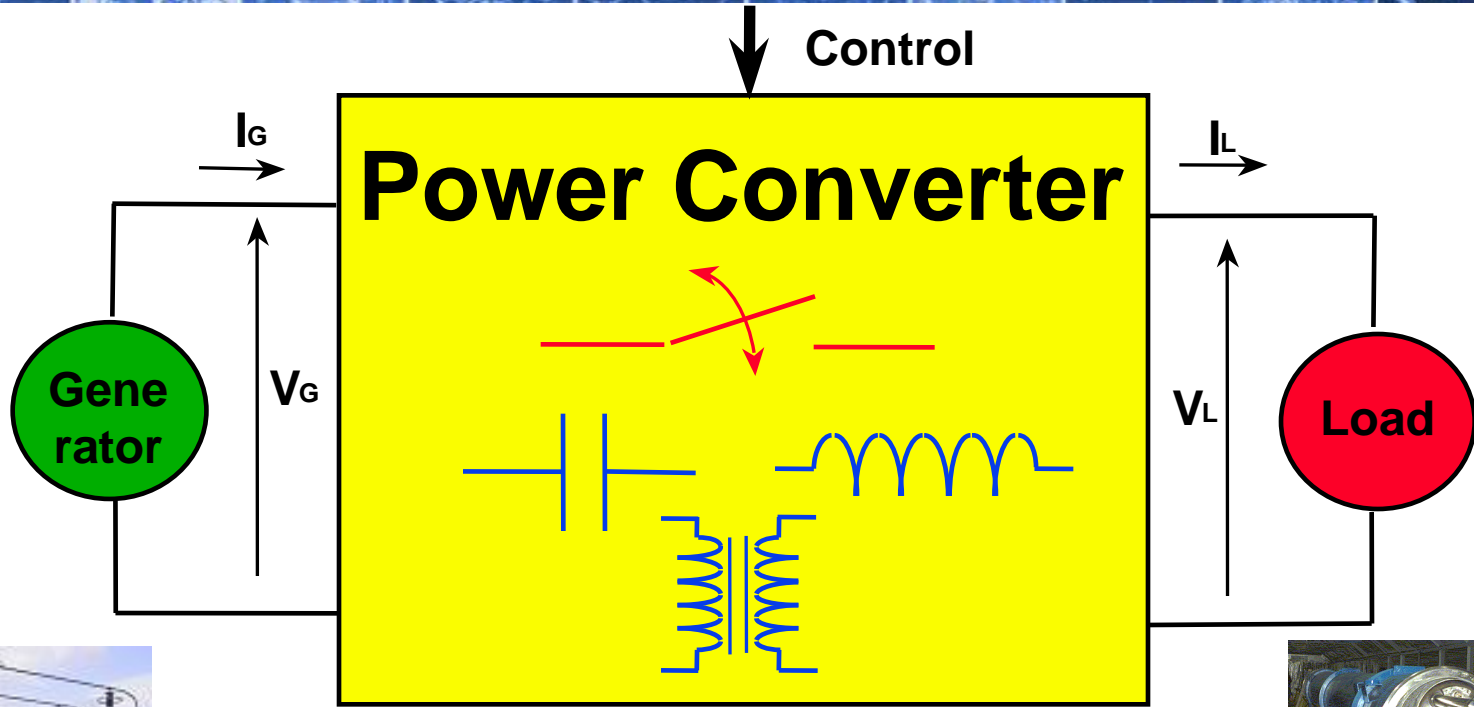

Electrical energy transfer

- low mains harmonic distortion
- power factor (closest to 1)


- low ripple (current)
- reproducibility (short and long term)
- rejection of mains disturbance
- dynamic response

Achieving high performance : **COMPROMISE**












~~Substrate~~

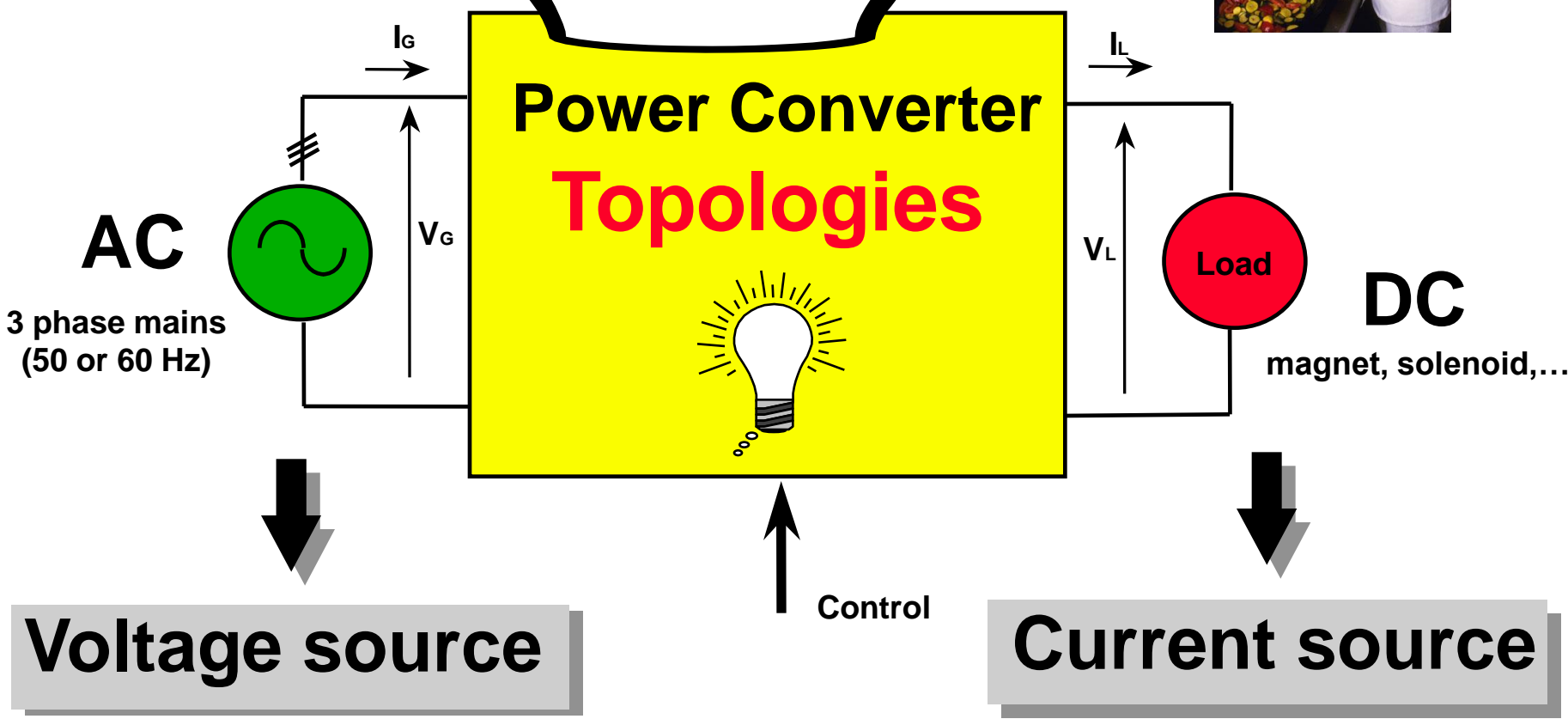


# Operating Modes

**Output Source**

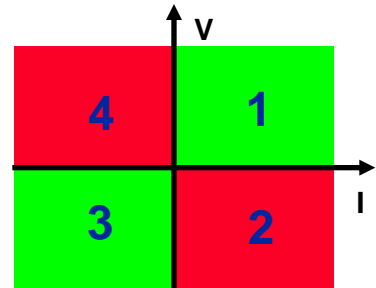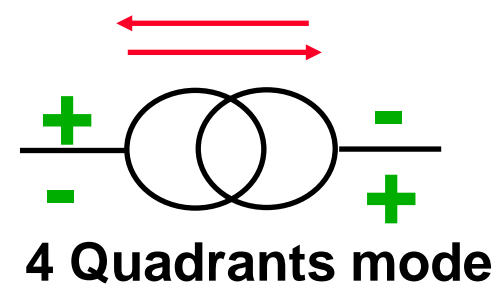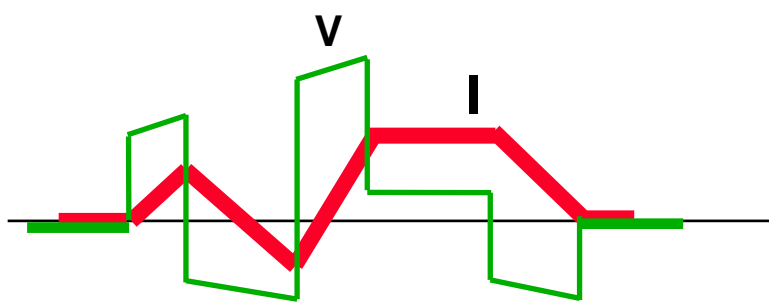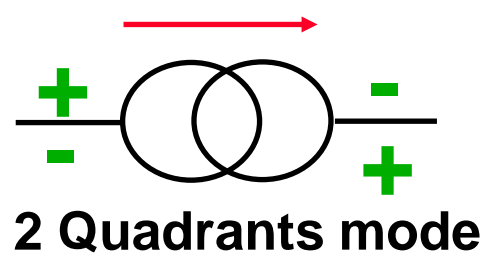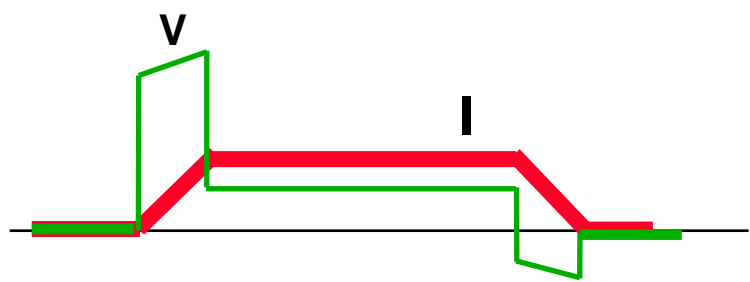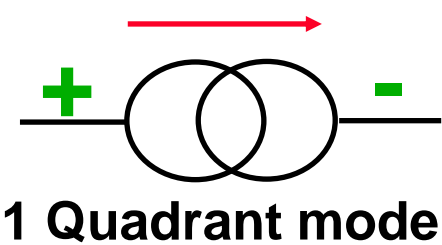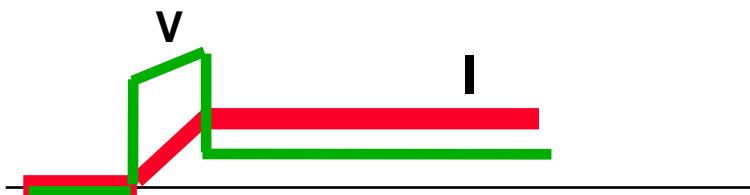





# General power converter topologies

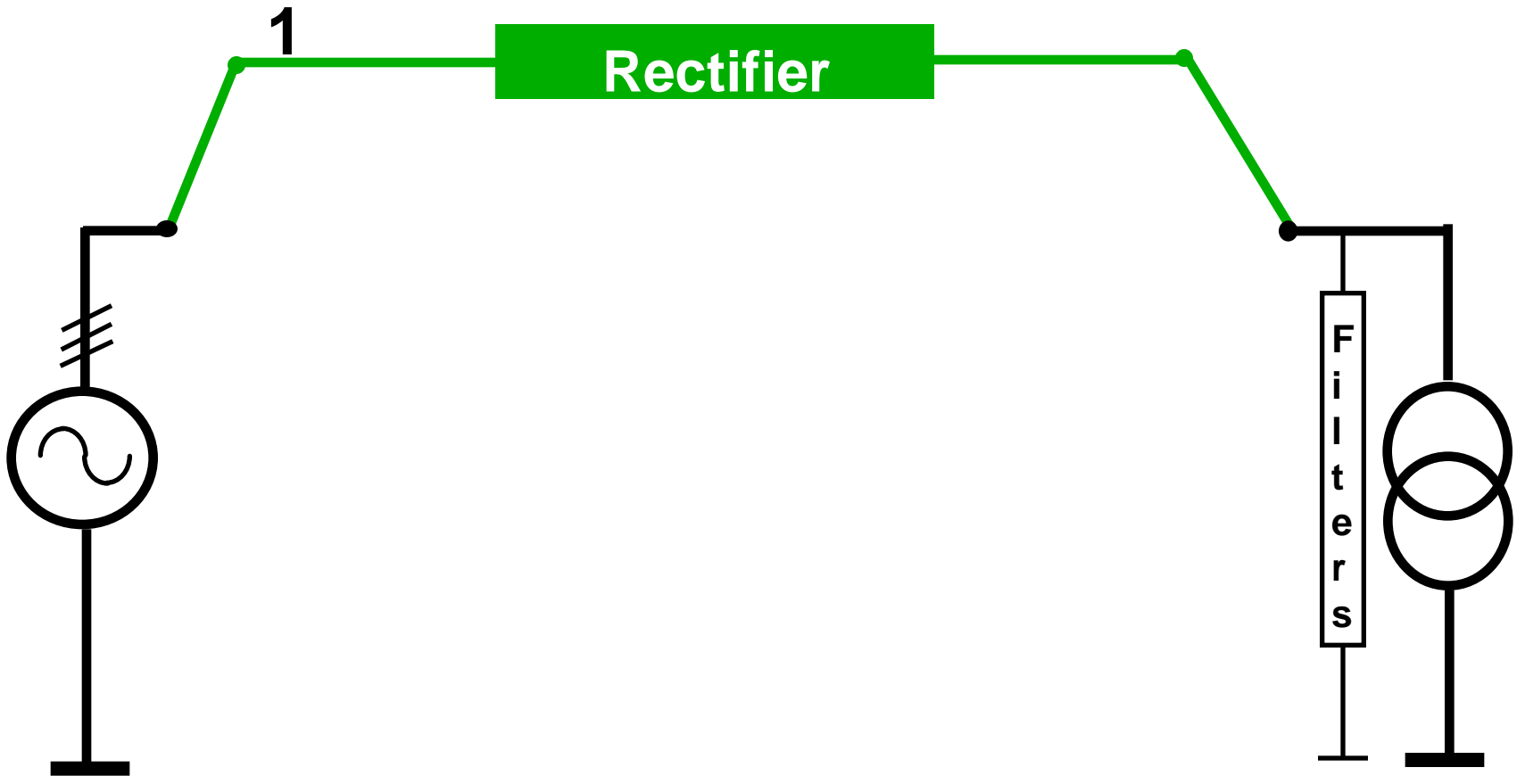



# Direct Converters : Rectifiers




volume 27 February 2009

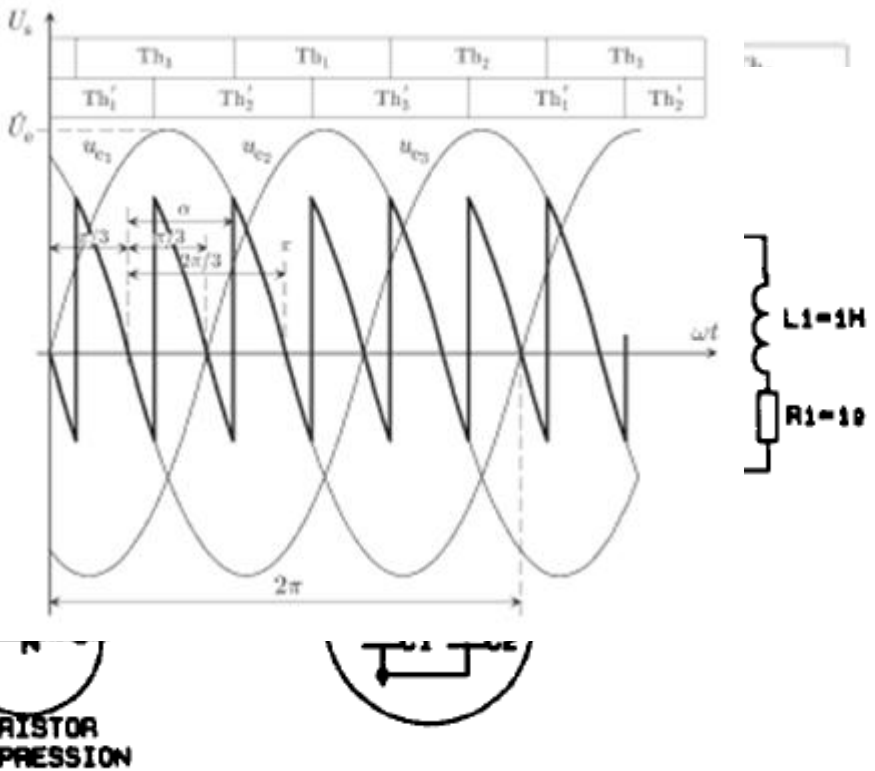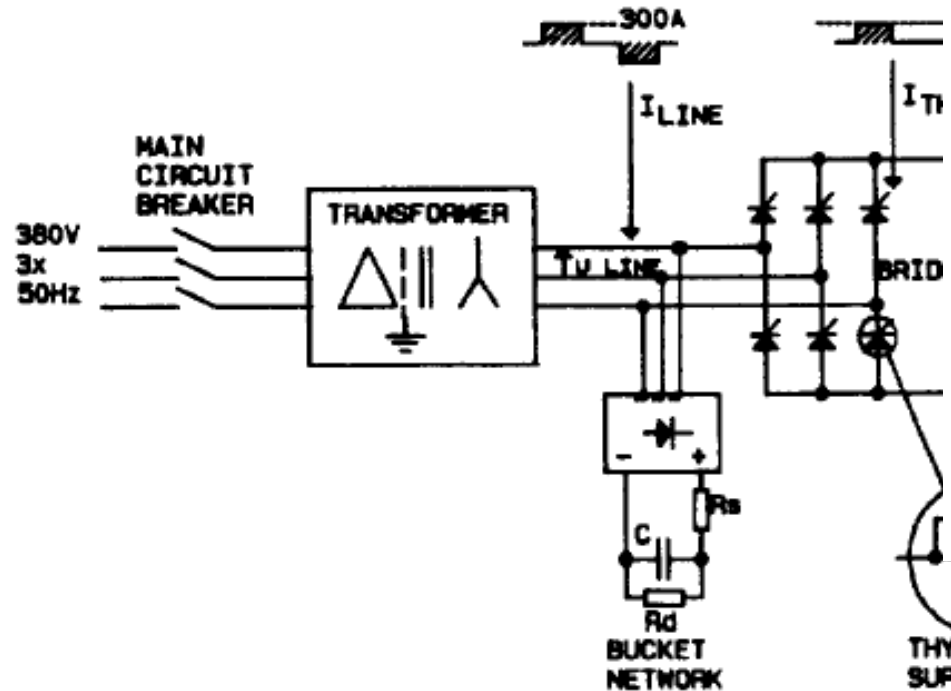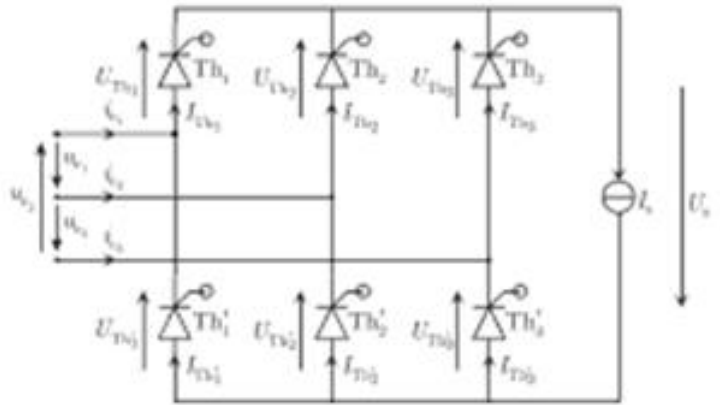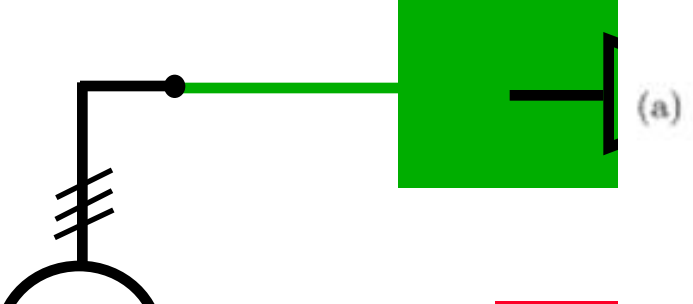


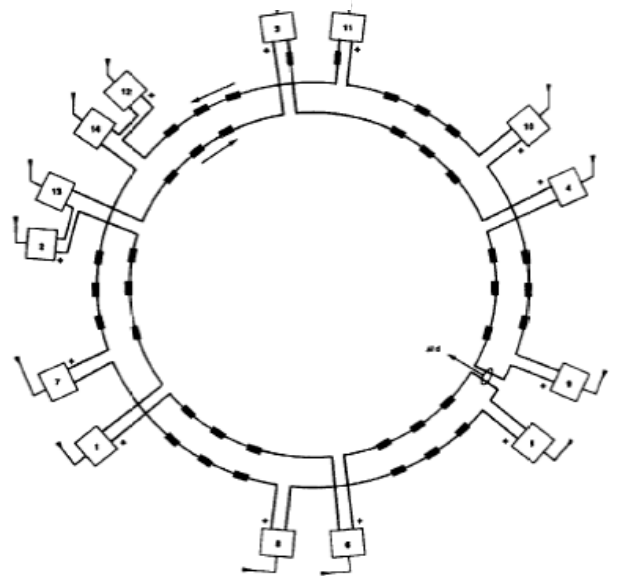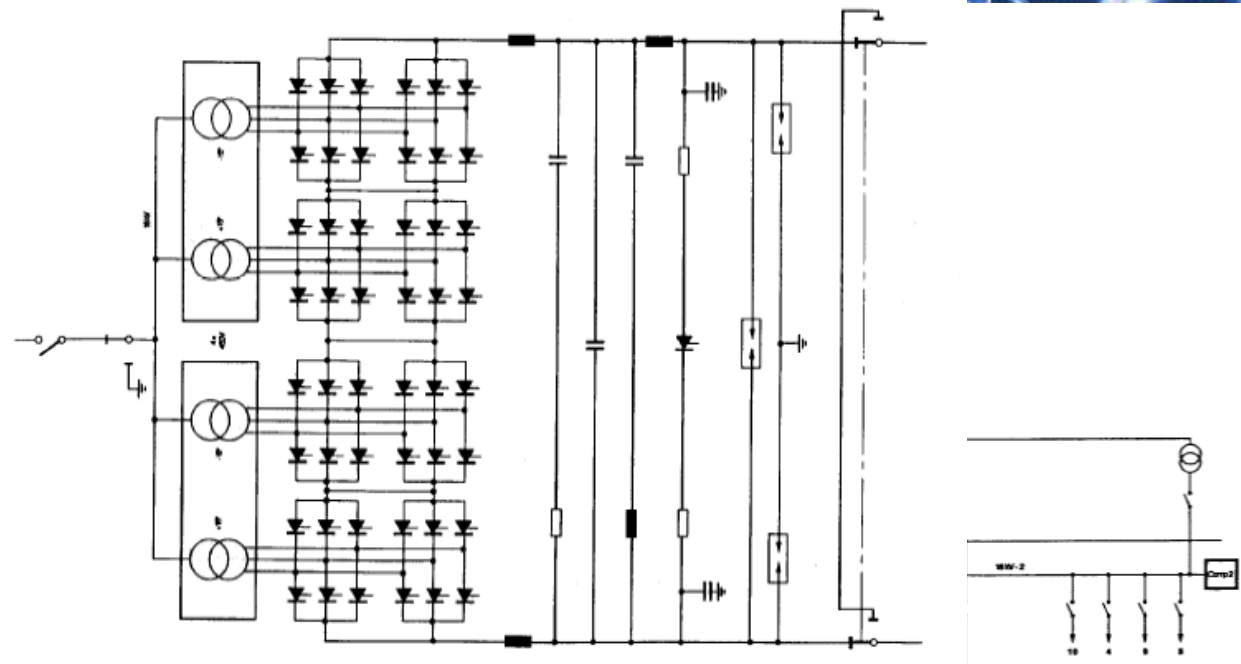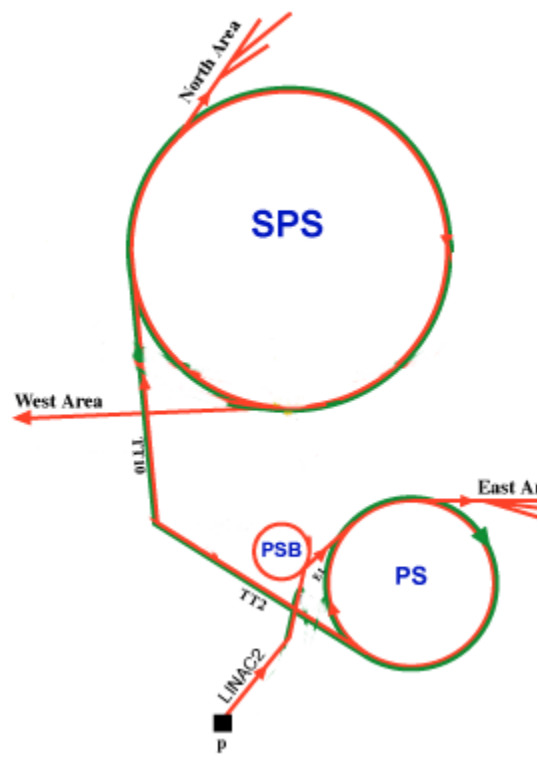
# SPS Main power converters


Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009




**Main power converters  
12 x [6kA, 2 kV]**



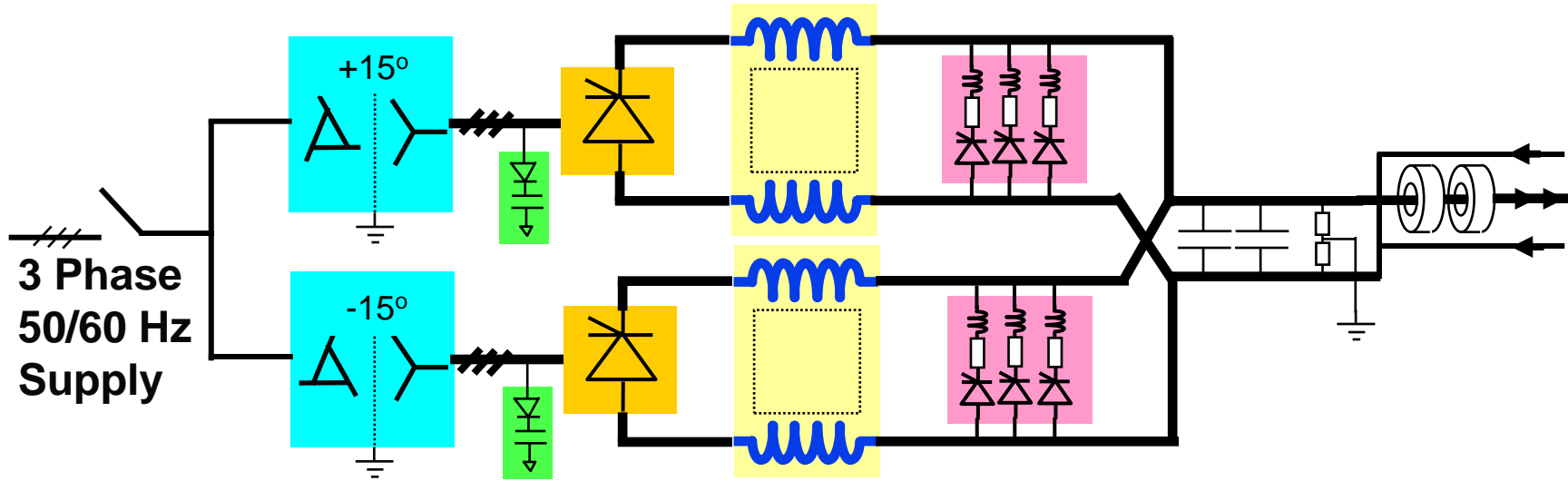
# Two Quadrant Phase Controlled Rectifiers for high current SC magnets



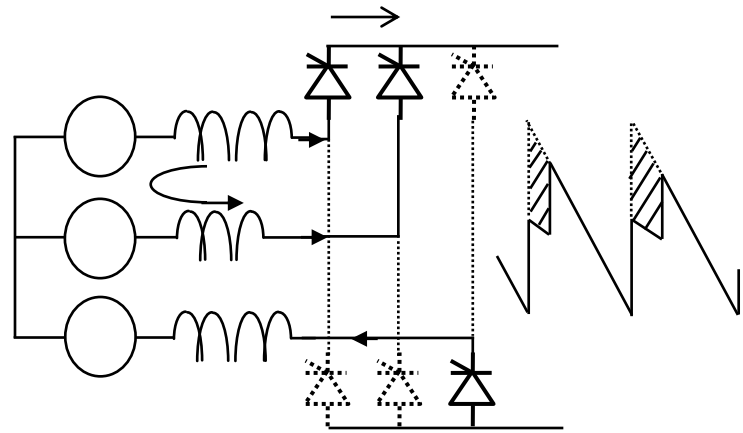
Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009





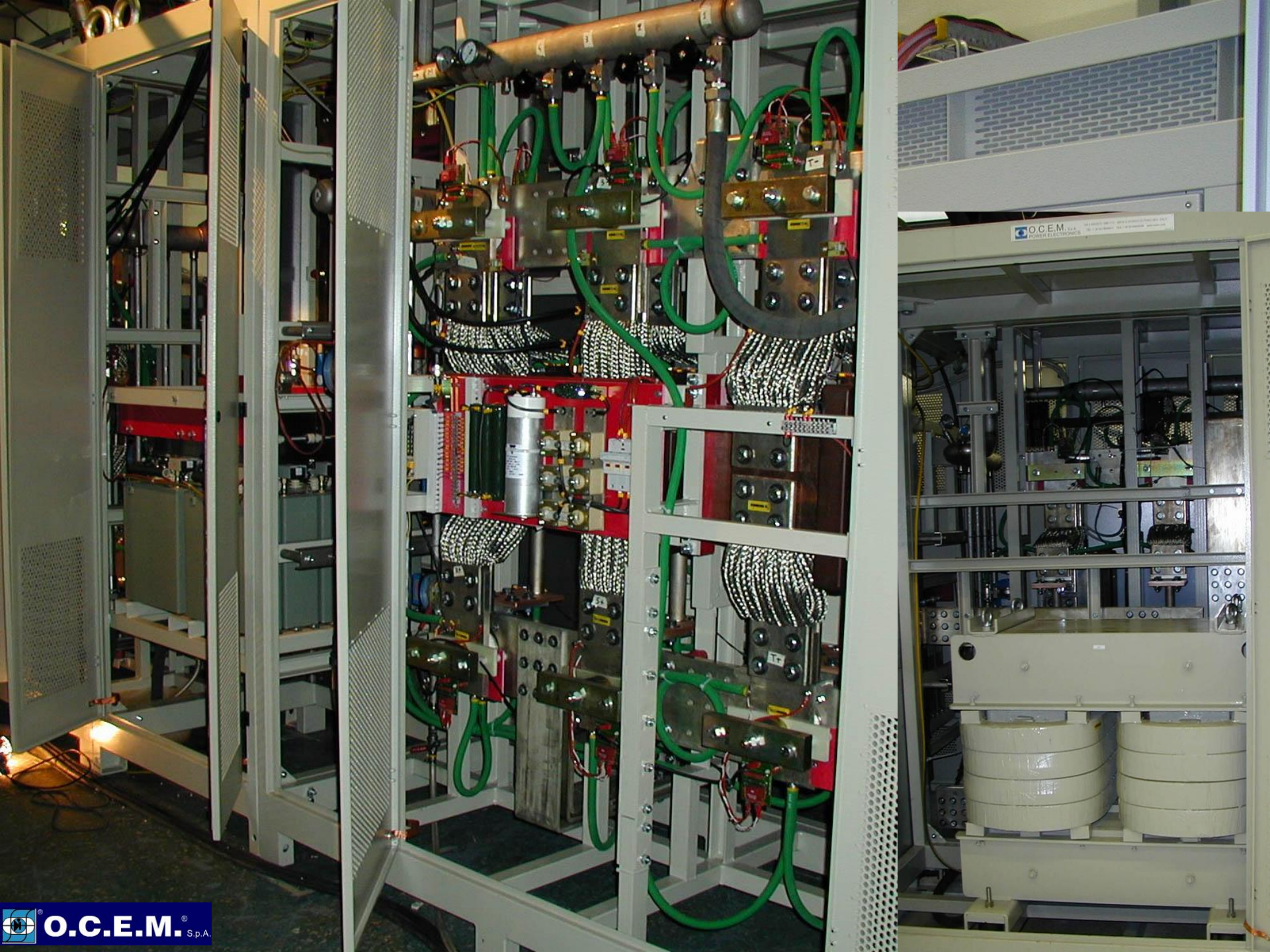

O.C.E.M. S.p.A.  
POWER ELECTRONICS

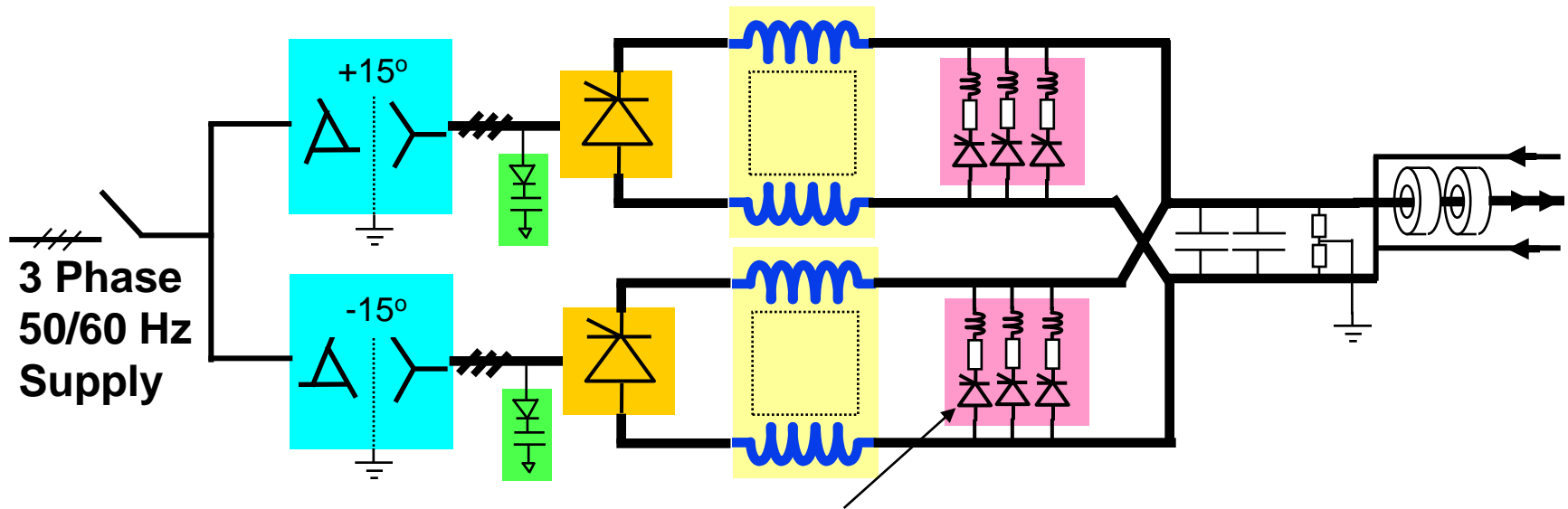


**Free-wheeling path**

- Vital component to assure discharge of magnet.
- In the case of thyristors (two quadrant operation), must have reliable firing with avalanche back-up. (Good idea to have same on main bridge thyristors)
- Need correct sharing devices, static and dynamic.
- Must survive mains failure and no cooling water.





# Direct Converters : Rectifiers

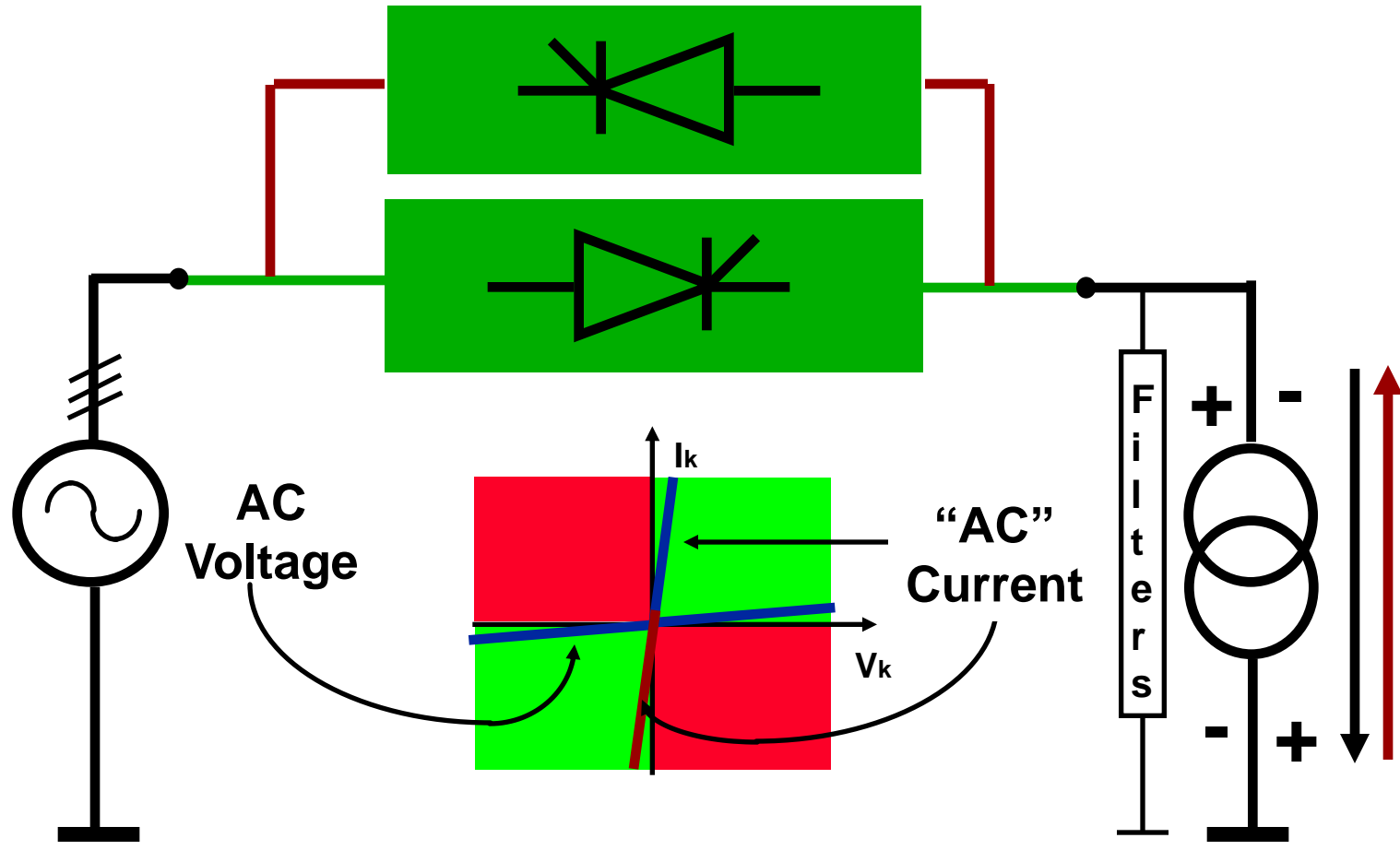

# Direct Converters : Phase Controlled Rectifiers


- ☺ **very high power capability**
- ☺ **moderate prices and competitive market**
- ☺ **simple structure, well understood (but care needed with high currents)**
- ☹ **three phase transformer operates at low frequency (50 or 60 Hz)**
- ☹ **variable power factor from 0 to 0.8**
- ☹ **harmonic content on input current**
- ☹ **response time is large (ms)**
- ☹ **current ripple is large (passive or active filters)**



**passive (active) filters operating at low frequency**


**Increase** of pulse number (3,6,12,24,48) but  
**complexity** (cost, control,...)

# General power converter topologies

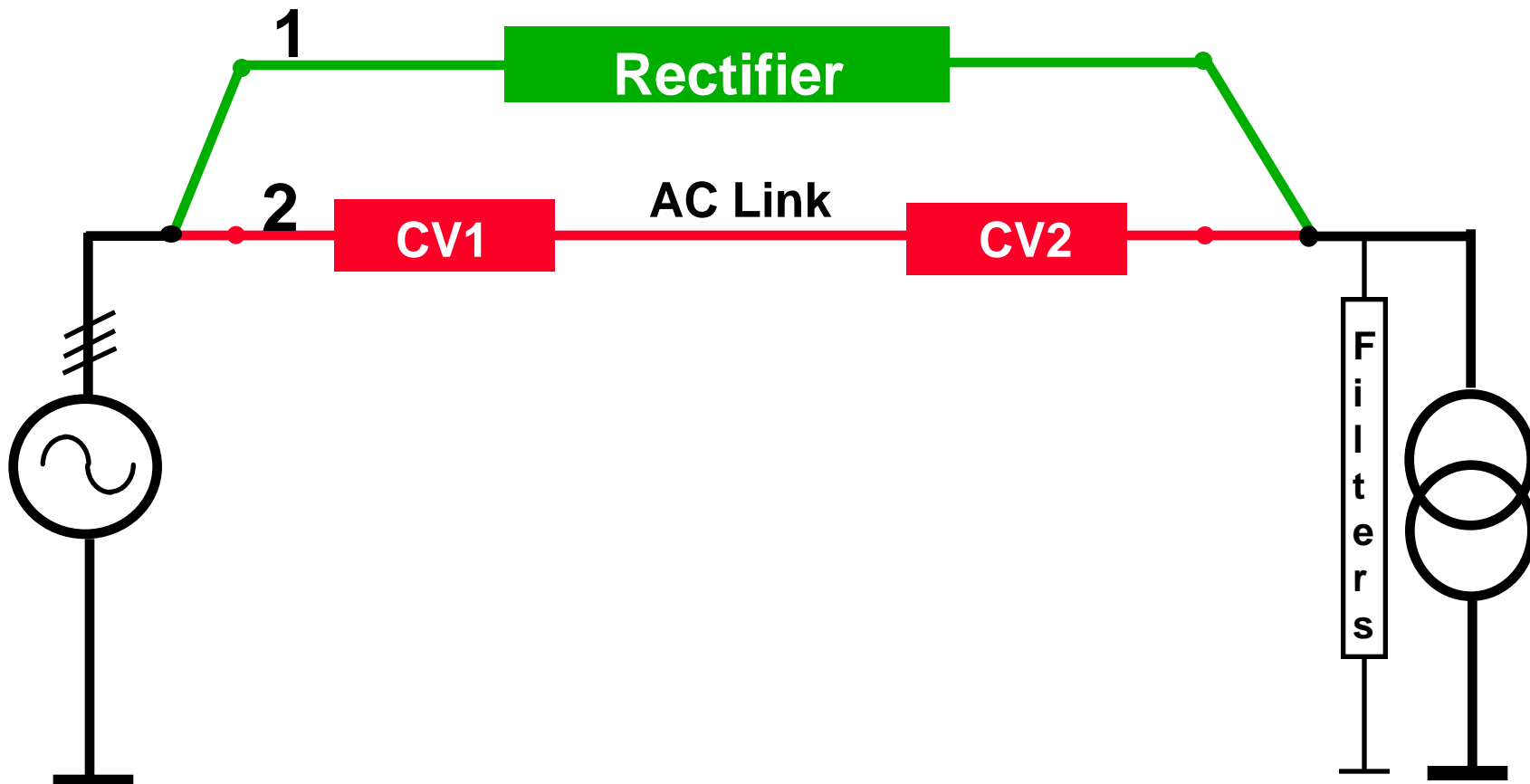

**Application :- very high currents with low voltages  
- (very high voltages with low currents)**

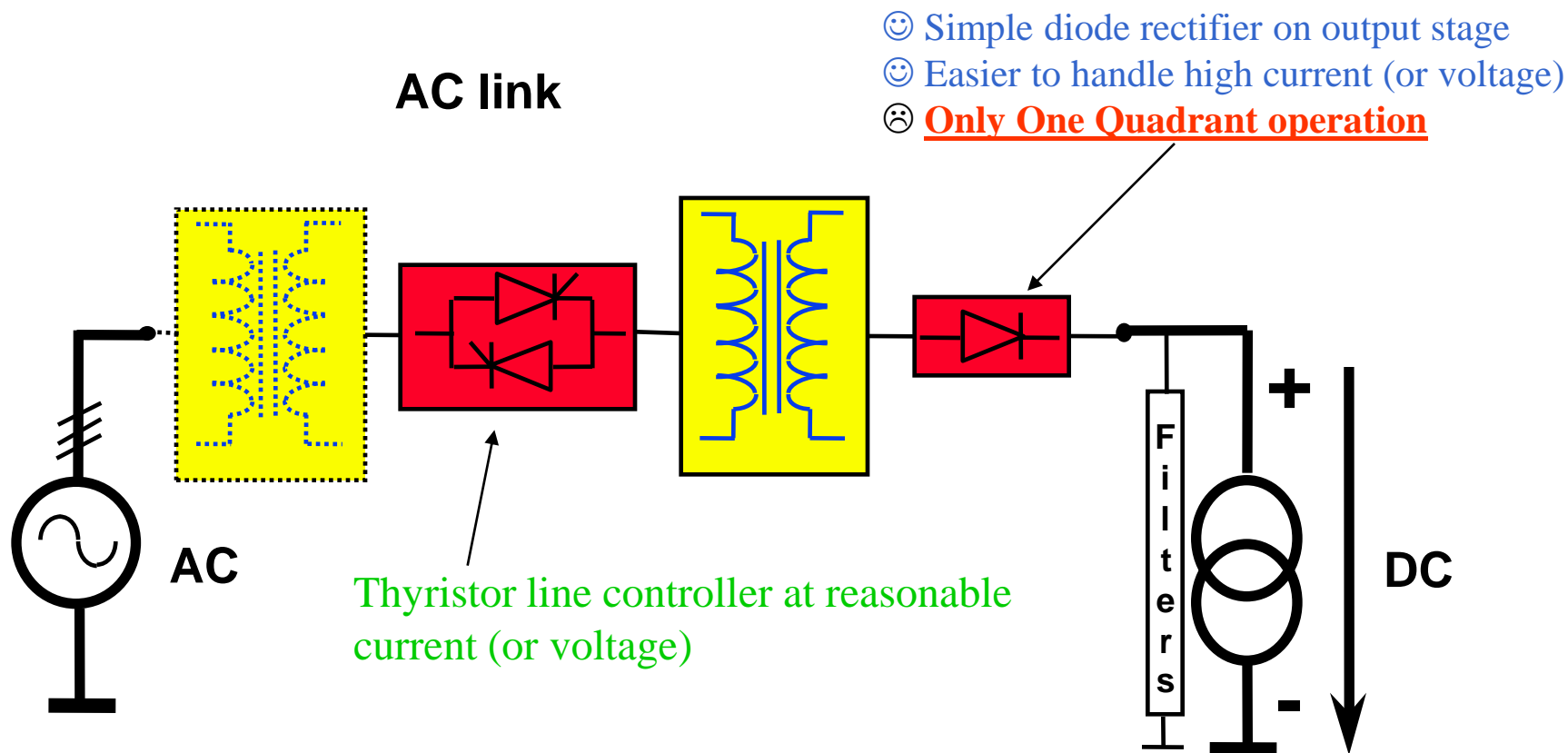
# Direct Converters : AC link (AC line controller)






# [100 kV, 40A] klystron power converter


ne 27 February 2009

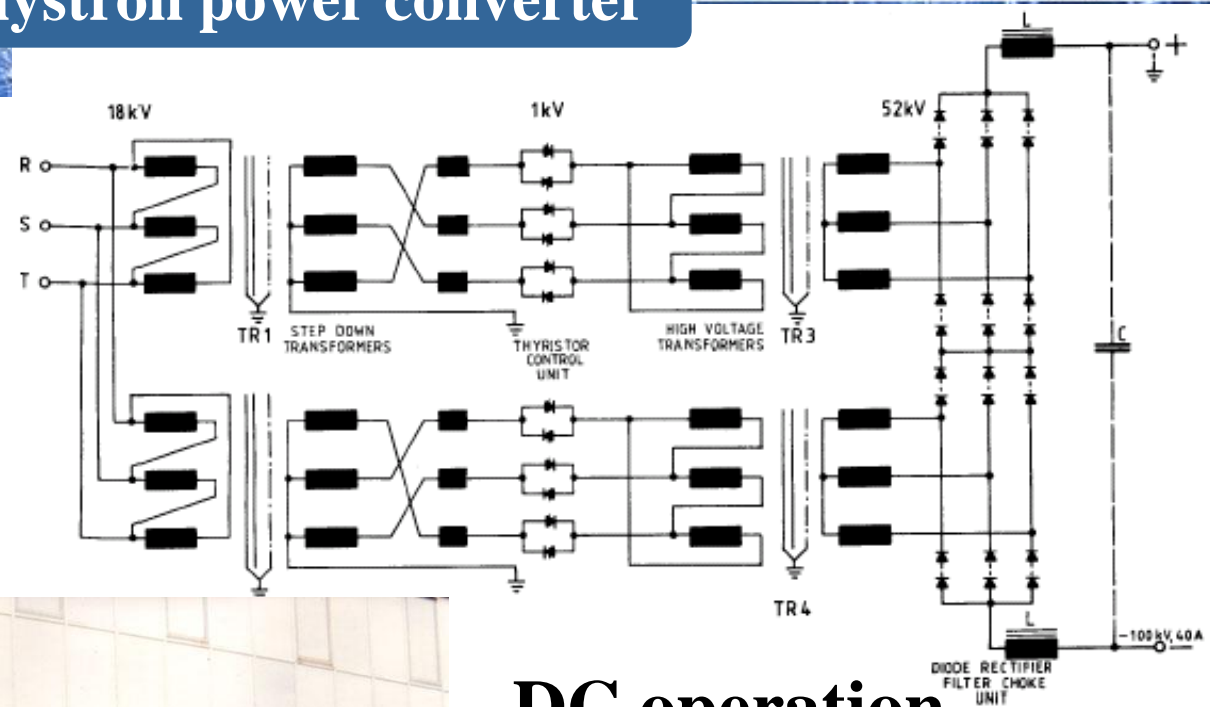


## DC operation

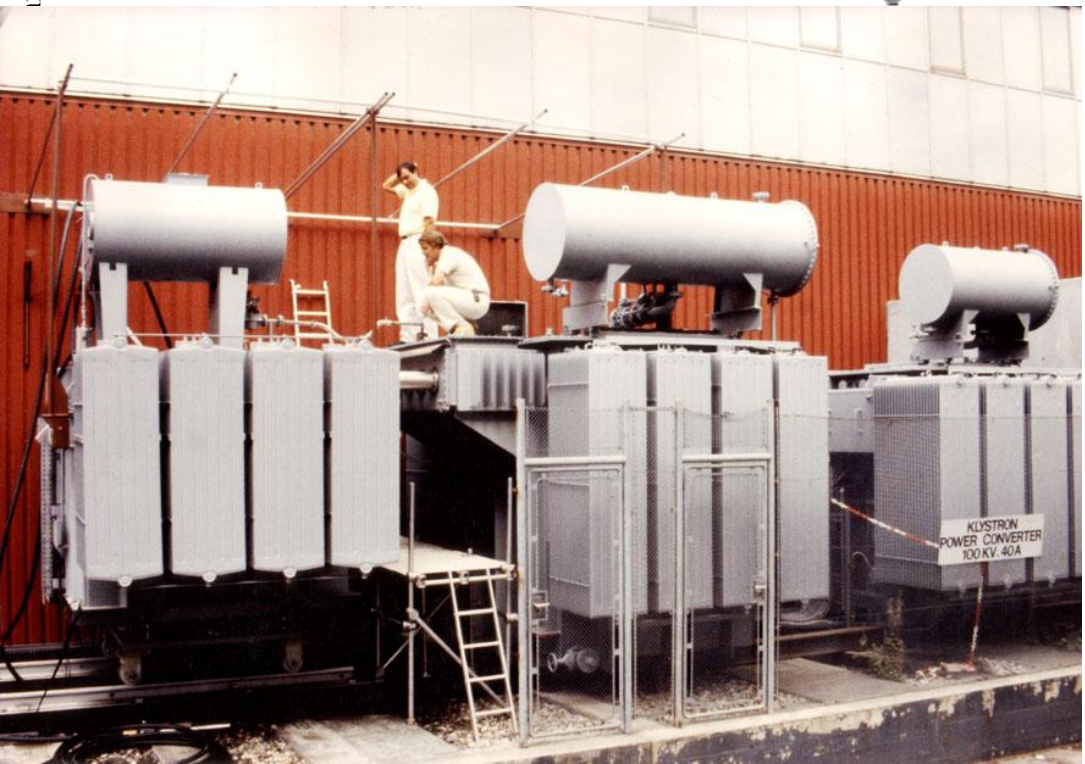


# General power converter topologies

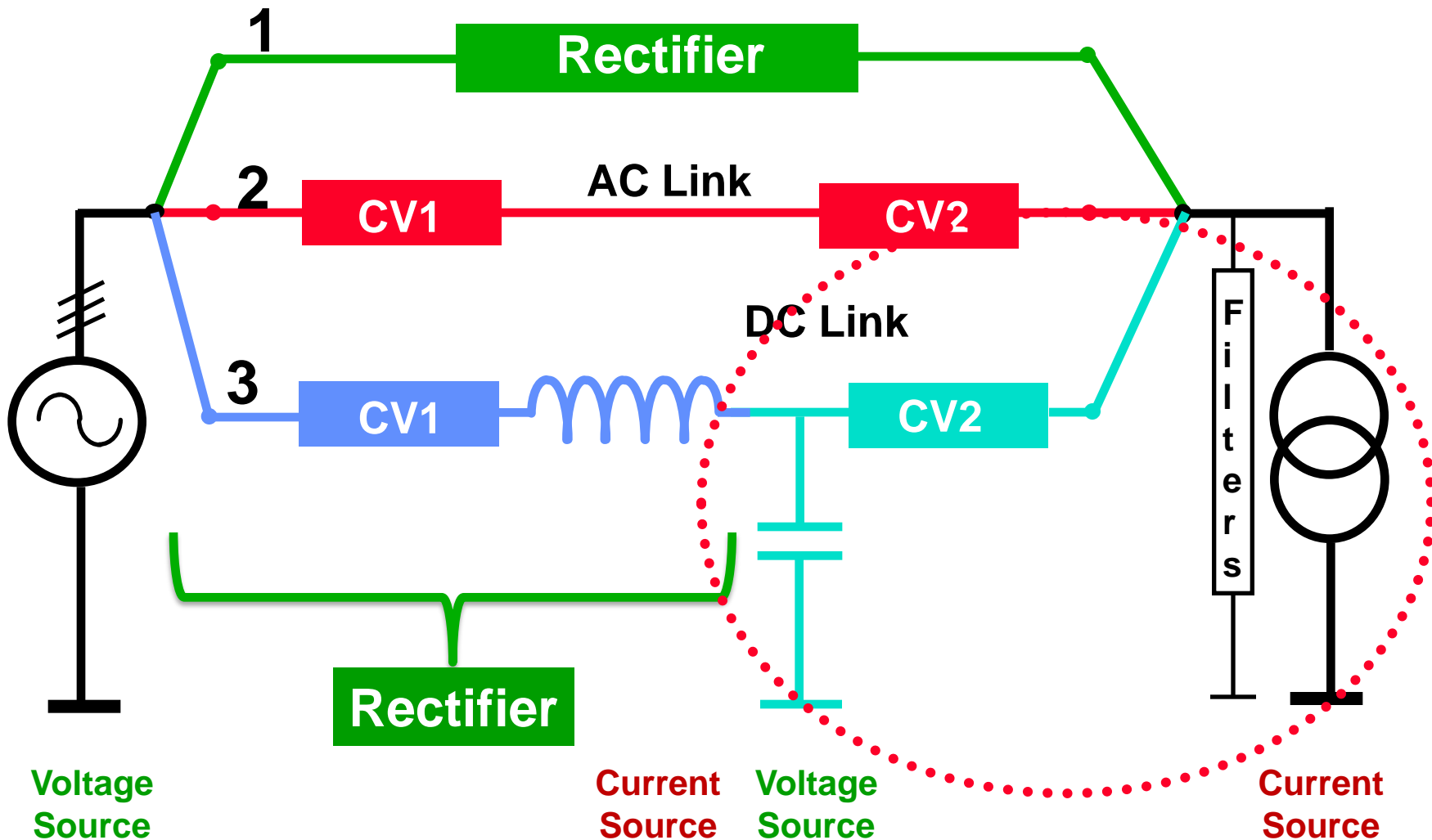

# Power converter topologies : DC - DC

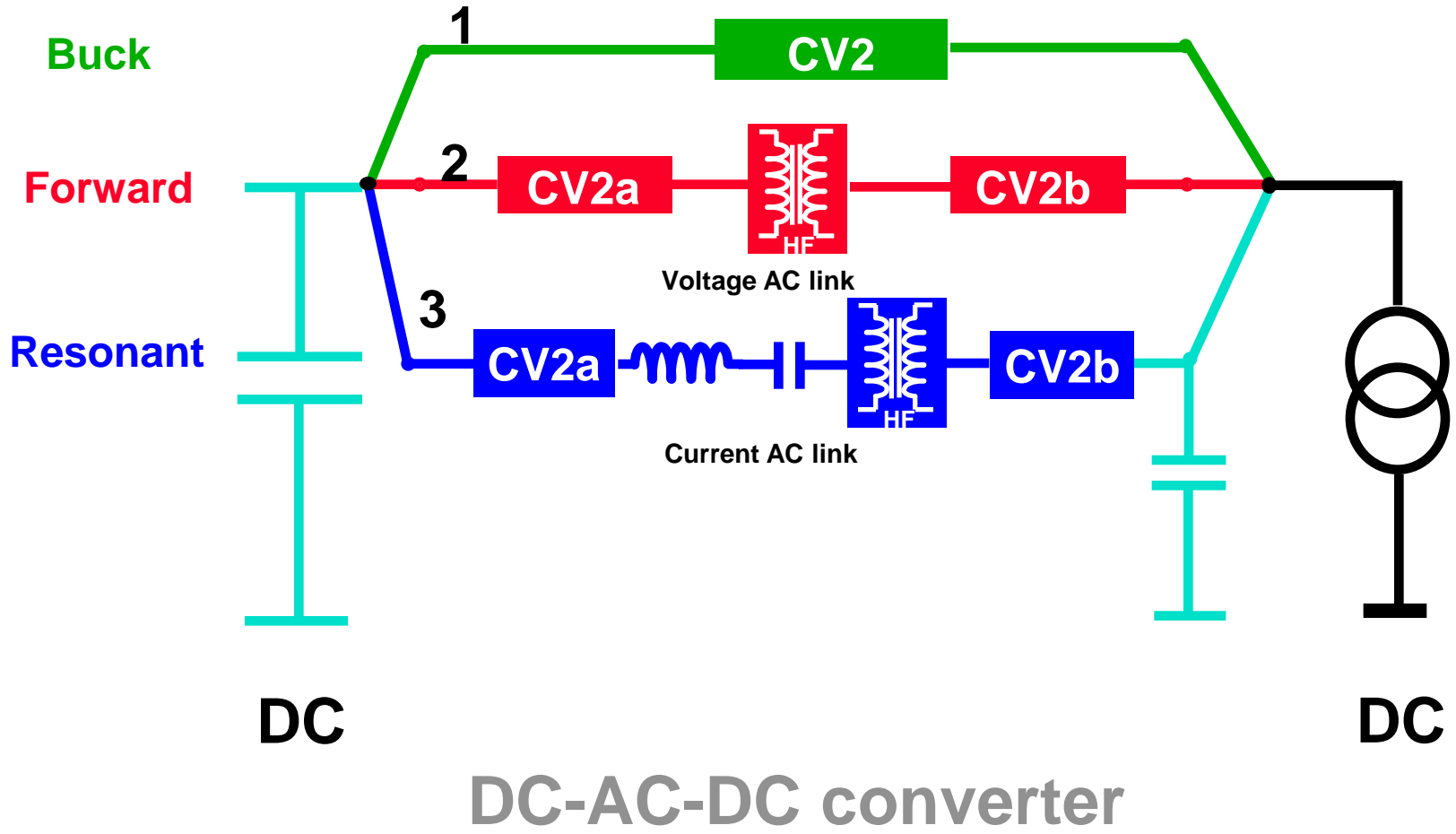
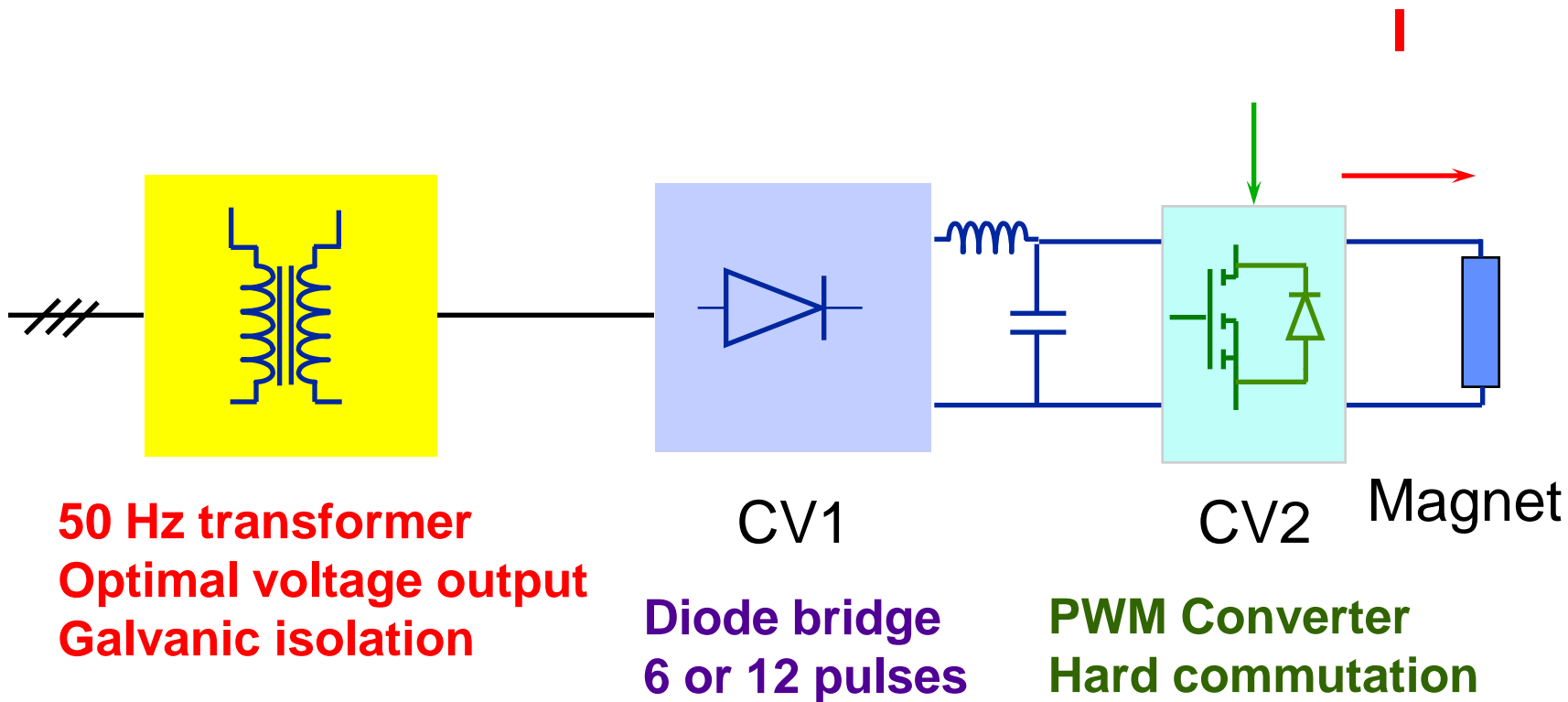
# Galvanic isolation at AC input source (50Hz transformer)








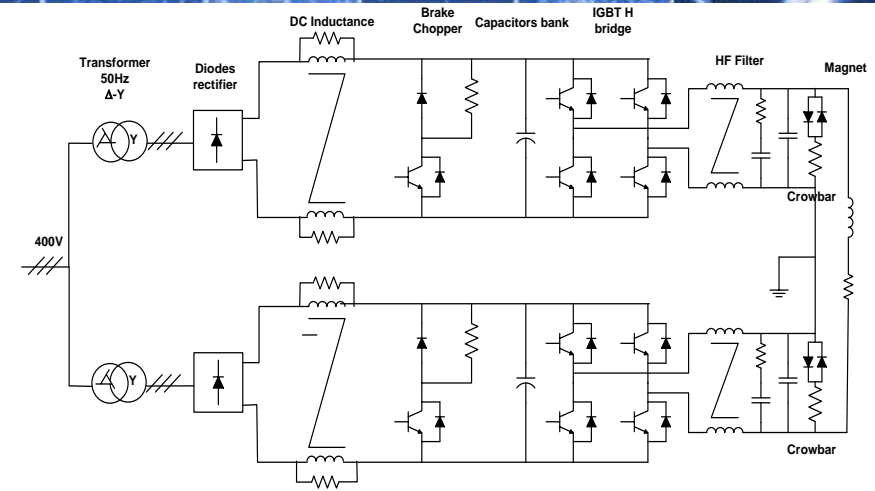
# New PS Auxiliary Power Converters

**Peak Power:** 405 kW  
**Voltage:** ± 900V  
**Max Current:** ± 450A

Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009



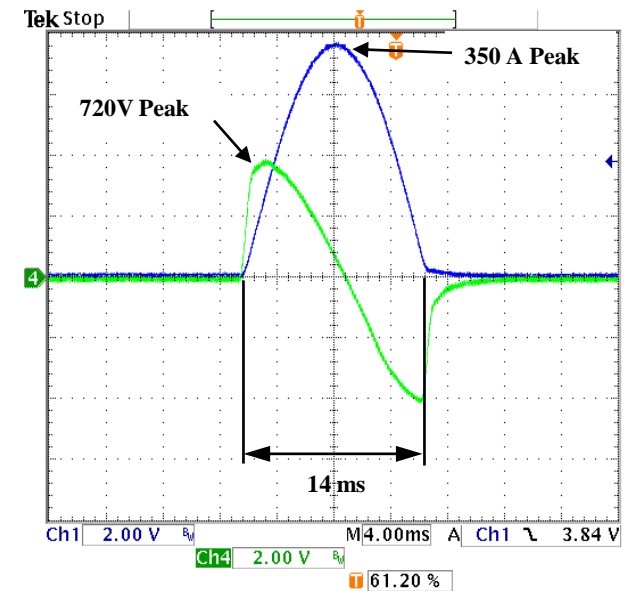**Multi-Turn Extraction: Current/Voltage waveforms**



27 Jun 2008  
 10:29:37

Current Loop Bandwidth ≈ 1kHz





# Indirect AC-DC-AC-DC converter


Three cascade power conversion stages:

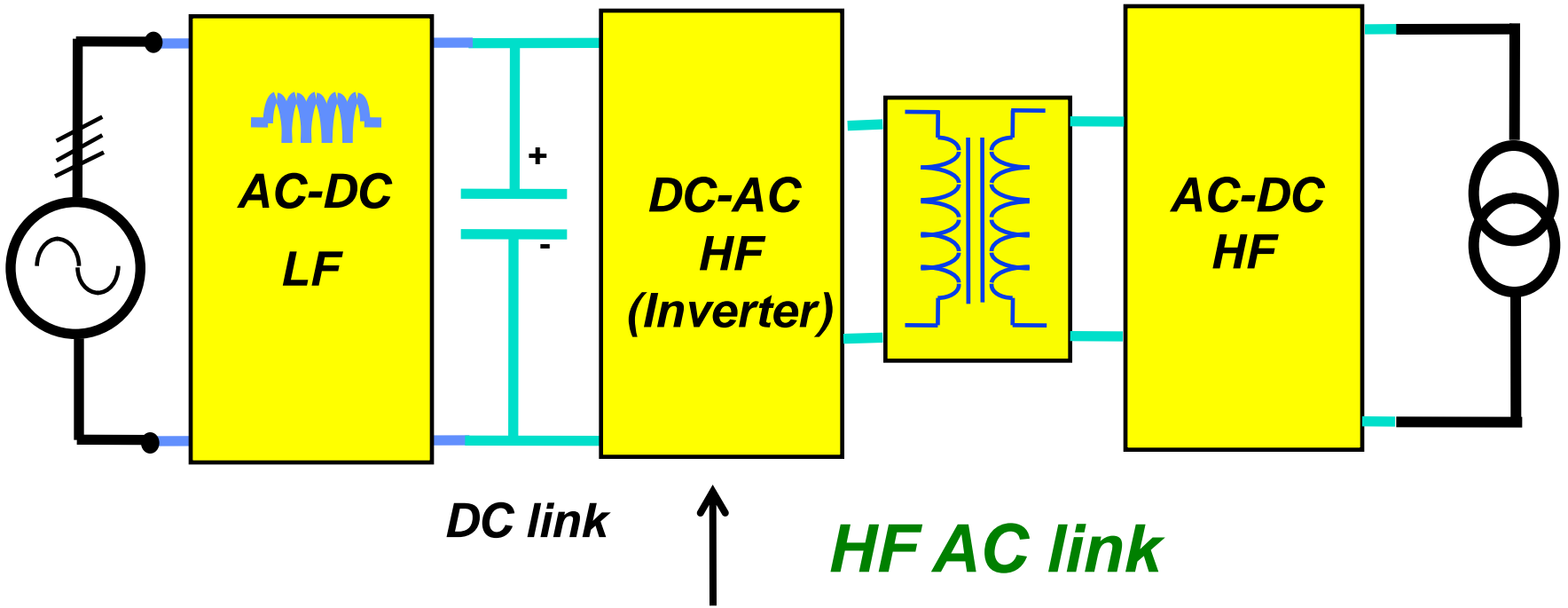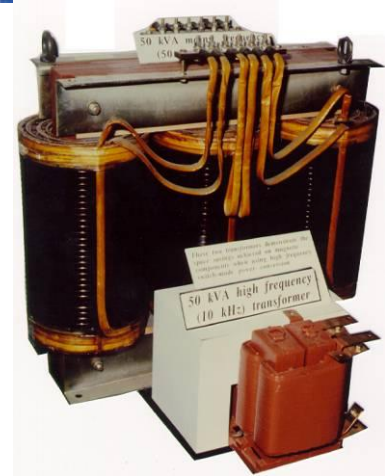- 1) Simple DC source (Diode (thyristor) rectifiers)
- 2) HF DC-AC converter (Inverter)
- 3) HF AC-DC converter (Rectifier) (often diode rectifier)

HF transformer to provide the galvanic isolation



# LHC Switch-Mode Power Converters

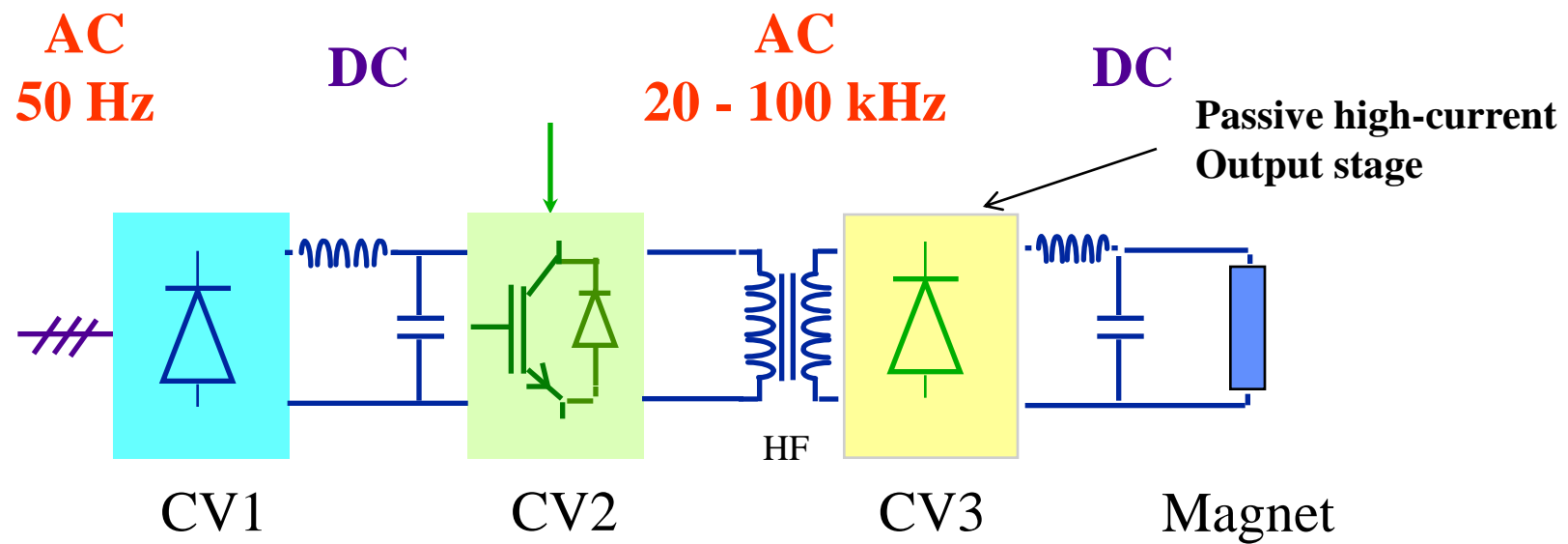

Voltage loop:  
bandwidth few kHz

- Fast power semiconductors (IGBT)
- Semiconductor losses :  
soft commutation
- HF transformer and output filter : ferrite

- light weight, reduced volume (HF transformers and filters)
- good power factor (0.95)
- high bandwidth and good response time
- Soft commutation gives low losses and low electrical noise
- small residual current ripple at output
- More complex structure, less well understood, limited number of manufacturers



# LHC: 1-quadrant converter: modular approach



## 1-quadrant converters:

- [13kA, 18V] : 5\*[3.25kA, 18V]
- [8kA, 8V] : 5\*[2kA, 8V]
- [6kA, 8V] : 4\*[2kA, 8V]
- [4kA, 8V] : 3\*[2kA, 8V]




MTBF and MTTR optimization

# 20.5kA power converter for the ATLAS toroid
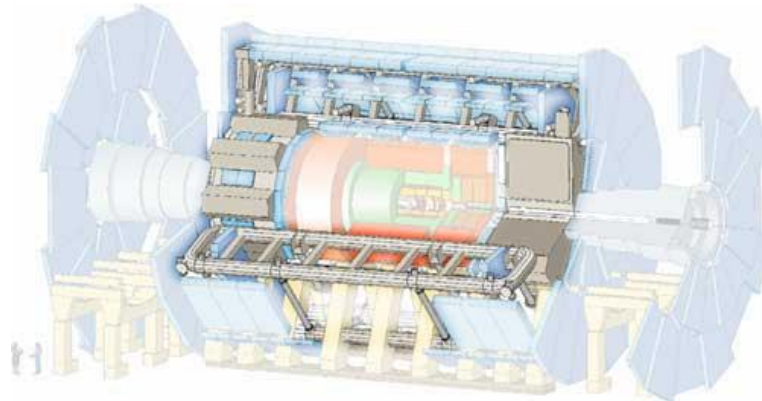
## The load

- Superconducting magnet:  $L = 7.5 \text{ H}$
- Nominal current: 20.5 kA
- Stored energy: 1.6 GJ
- Time constant: 37'500 s



**The power converter :** [20.5 kA, 18V] ; (7+1) x [3.25kA, 18V]






# 20kA power converter for the CMS solenoid
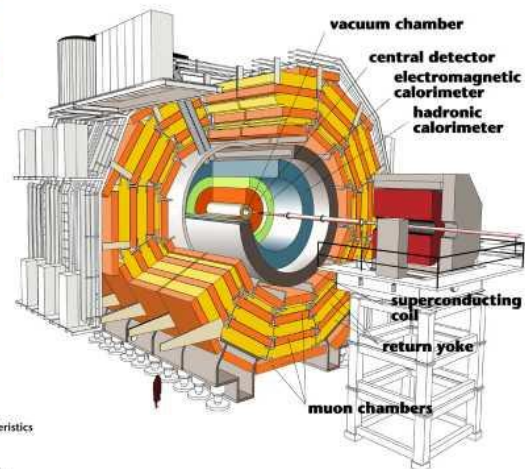
## The load


- Superconducting magnet:  $L = 14\text{H}$
- Nominal current: 20 kA
- Stored energy: 2.8 GJ
- Time constant: 39 hours
- Time for current ramping up: 3h15m
- Energy extraction system (resistor bank, not shown)



Detector characteristics  
Width: 22m  
Diameter: 15m  
Weight: 14'500t

## The power converter

ome 27 February 2009



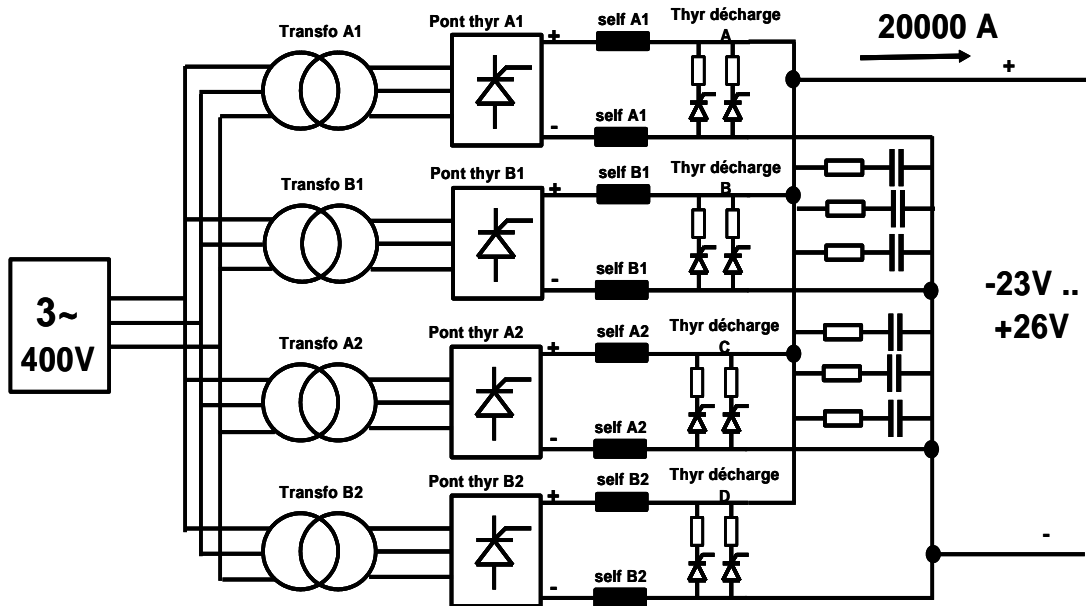


Fk. Bor




CERN

# LHC:4-quadrant converter topology

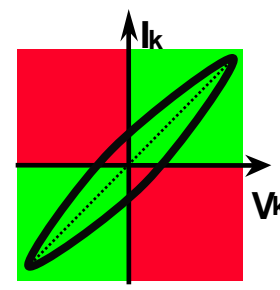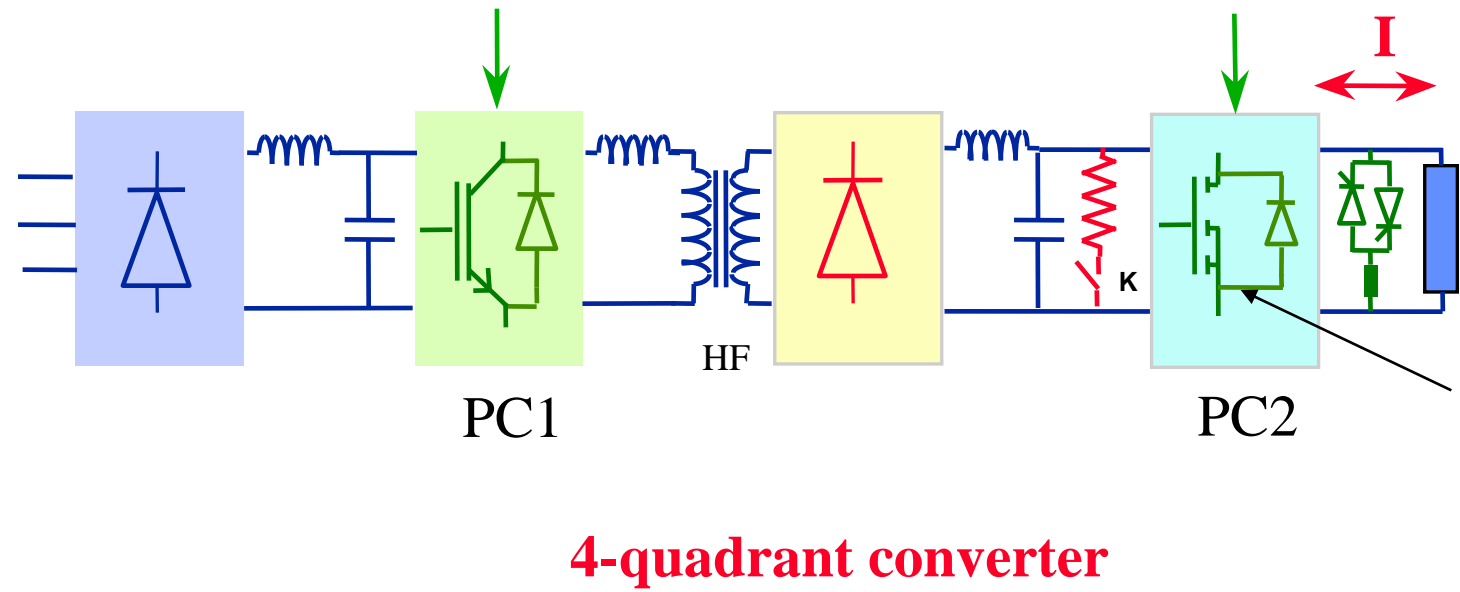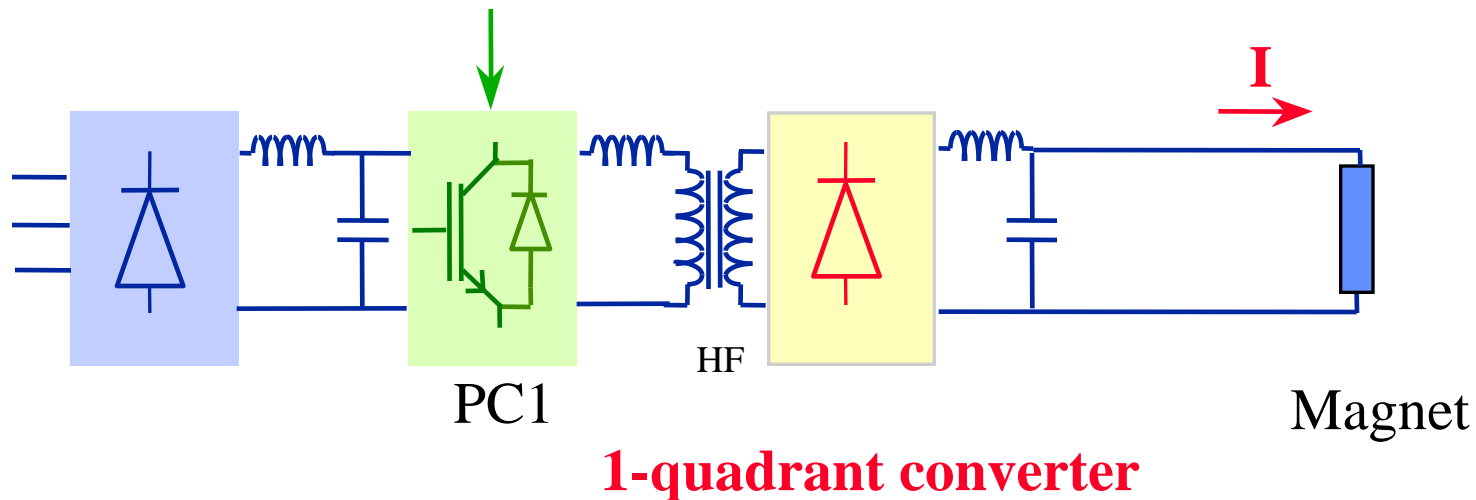

Difficult to find suitable switch

# LHC:4-quadrant converters

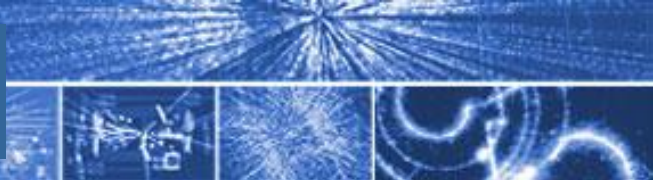

Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009



[ 600A,  $\pm 10V$ ]  
2 converters per rack




[ 600A,  $\pm 40V$ ]  
1 converter per rack



[ 120A,  $8\pm V$ ]  
Up to 4 converters per rack

# DC and slow pulsed converters

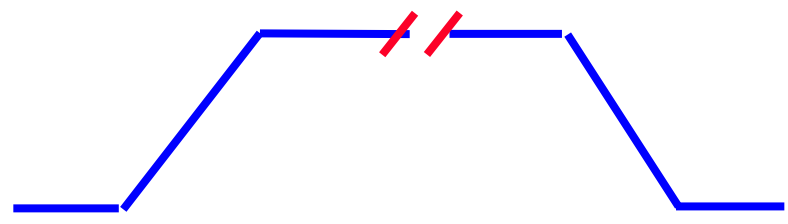

Rise and fall time < few ms

Control of the ramps

## High and medium power

### Phase Controlled Rectifiers

- Diodes and thyristors rectifiers
- 50Hz transformers and magnetic component (filters)
- 1-quadrant and 2-quadrants (but unipolar in current) : energy back to the mains
- 4-quadrant: back-to-back converters


## Low and Medium power

### Switch-mode power converters

- Mosfets , IGBTs, IGCTs,... turn-off semiconductors
- HF transformers and passive filters
- excellent for 1-quadrant converter
- 4-quadrant converters but with energy dissipation (very complex structure if energy back to mains)


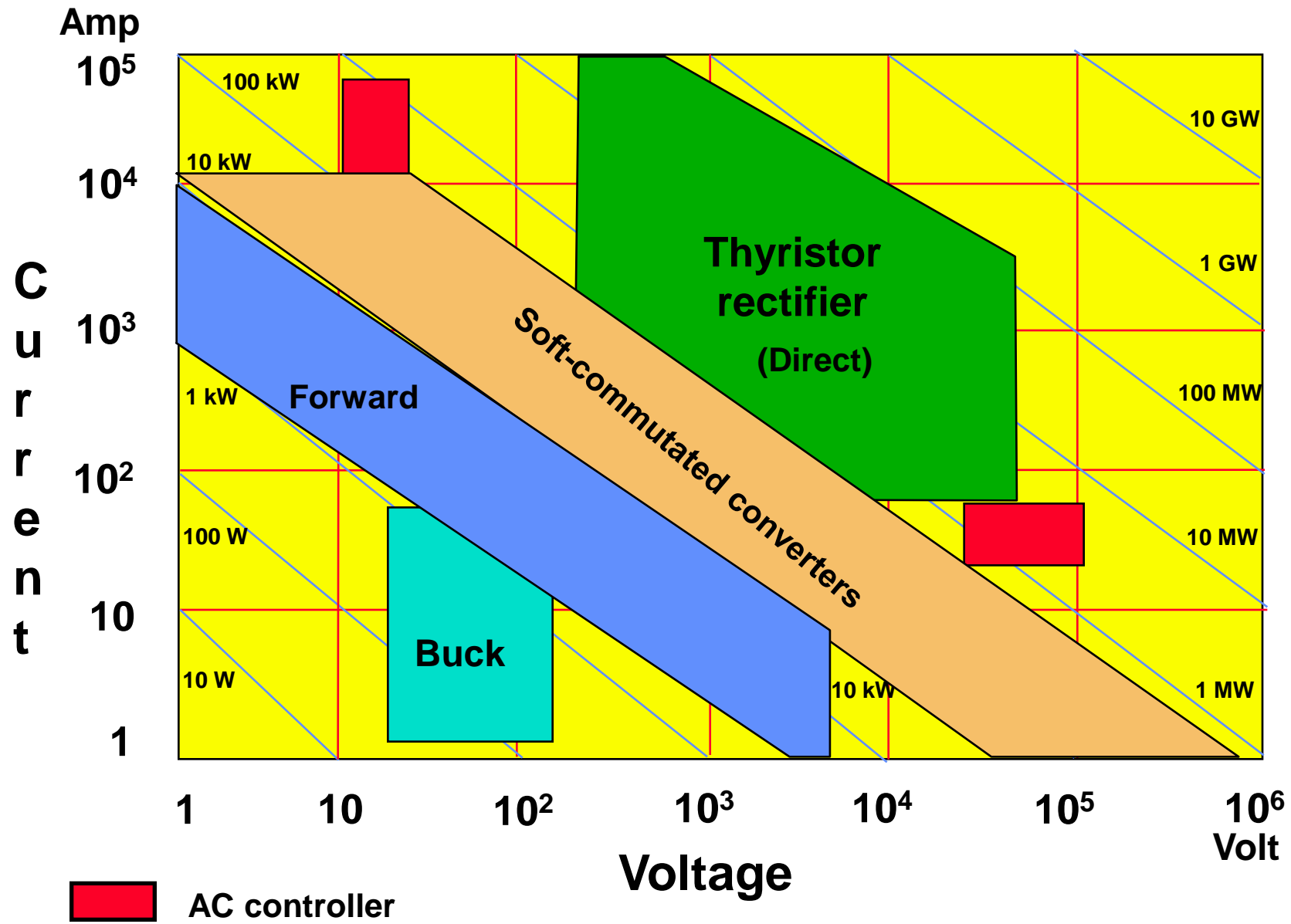
# Power converter : Operational domains for accelerators



Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009







# New Power converter for PS (60 MW)

New PS power system (POPS)  
Fully static power converter  
Exchange of energy between capacitor banks and the magnets




CERN Divonne 27 February 2009

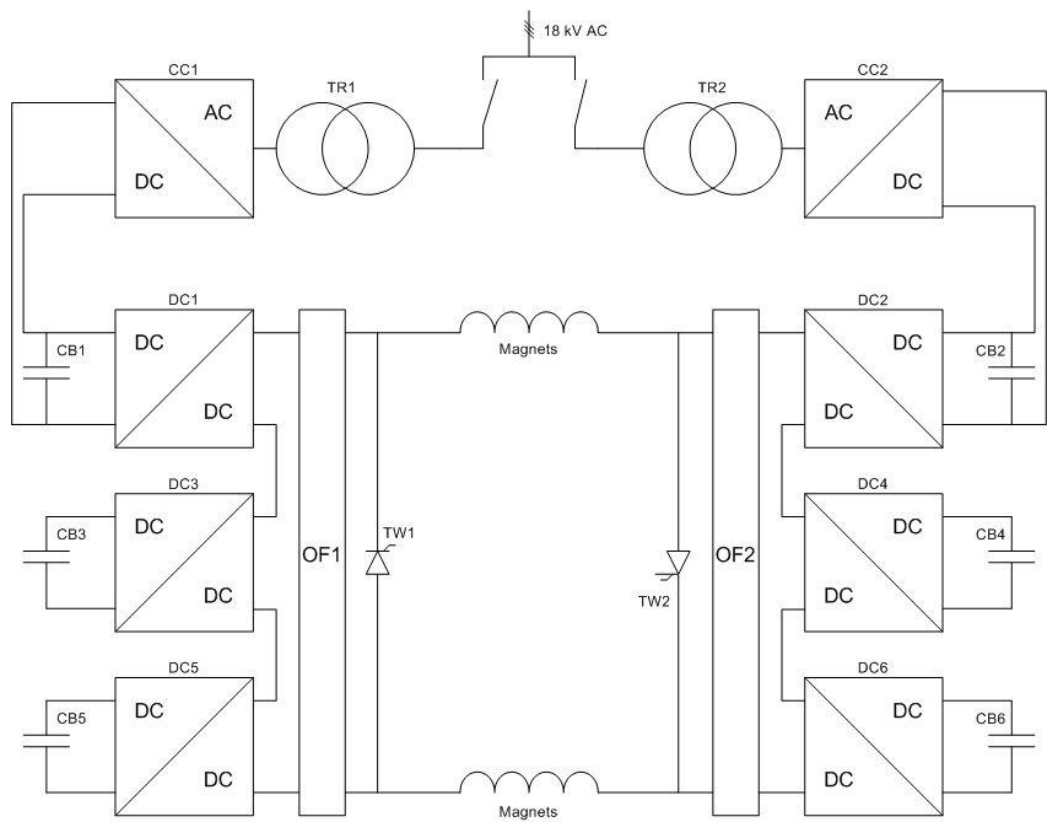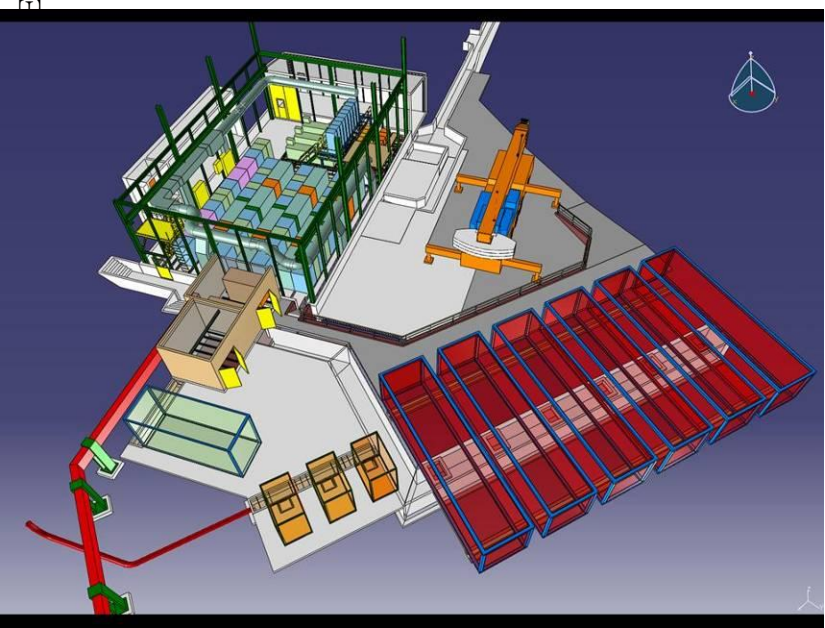

# Pulsed converters

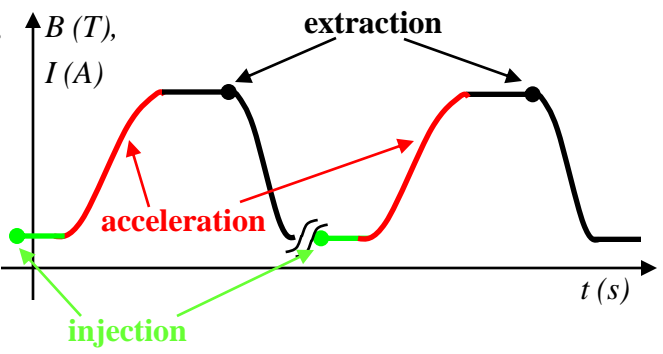
## Synchrotrons

- Beam is injected, accelerated and extracted in several turns;


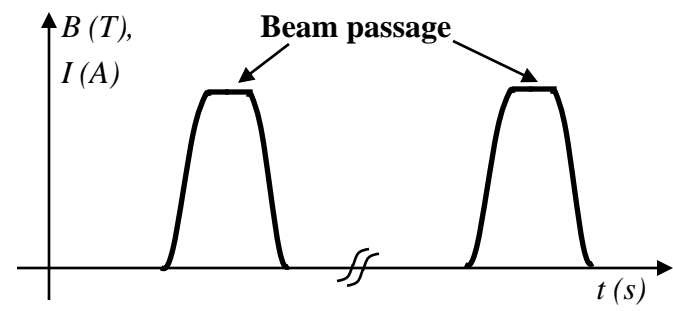
## Linac's and transfer lines

- Beam is passing through in one shot, with a given time period;




Rise and fall time < few ms


Direct Energy transfer  
from mains is not possible:  
**Intermediate storage of energy**


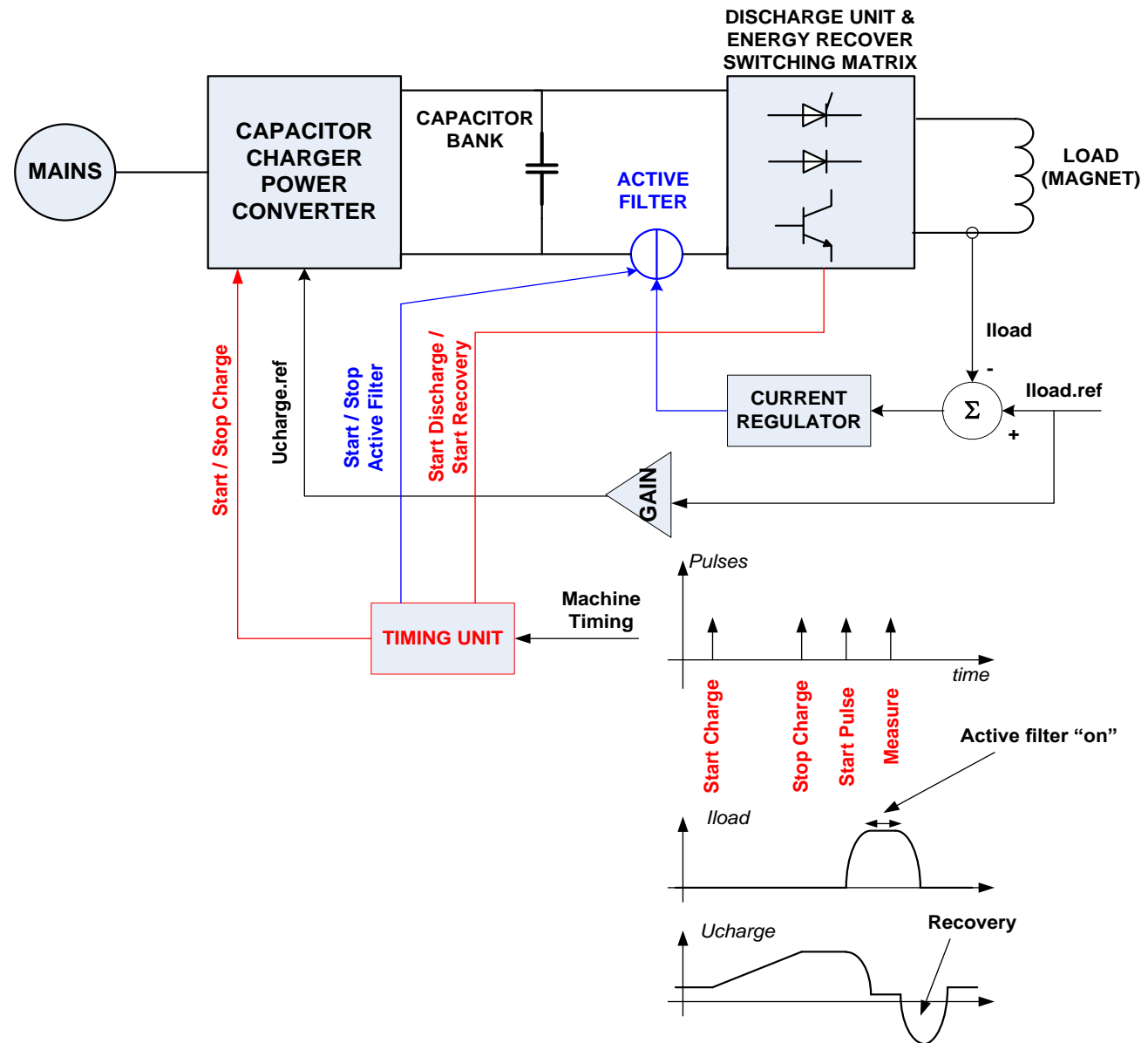
# Block schematic of a fast pulsed converter



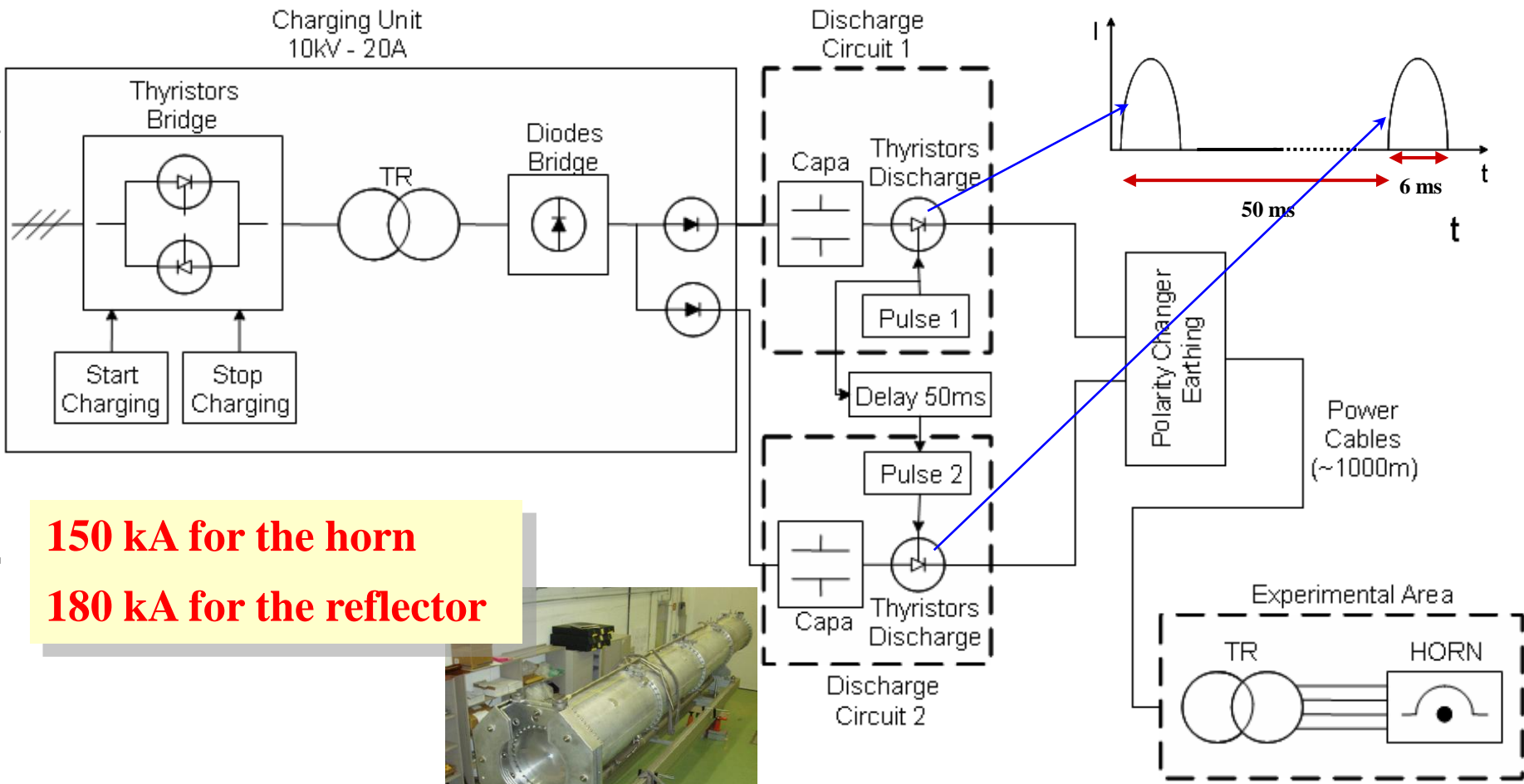Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009



**150 kA for the horn**  
**180 kA for the reflector**









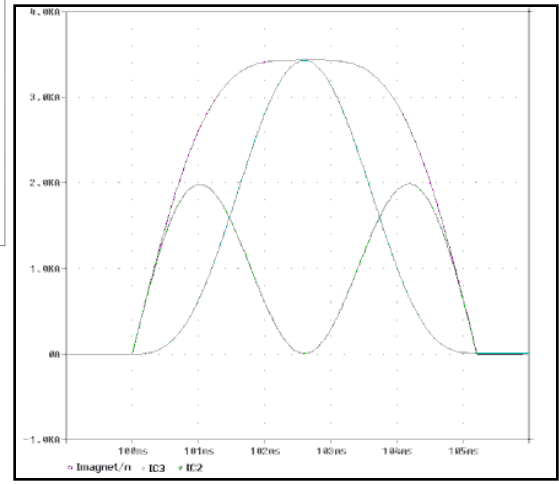
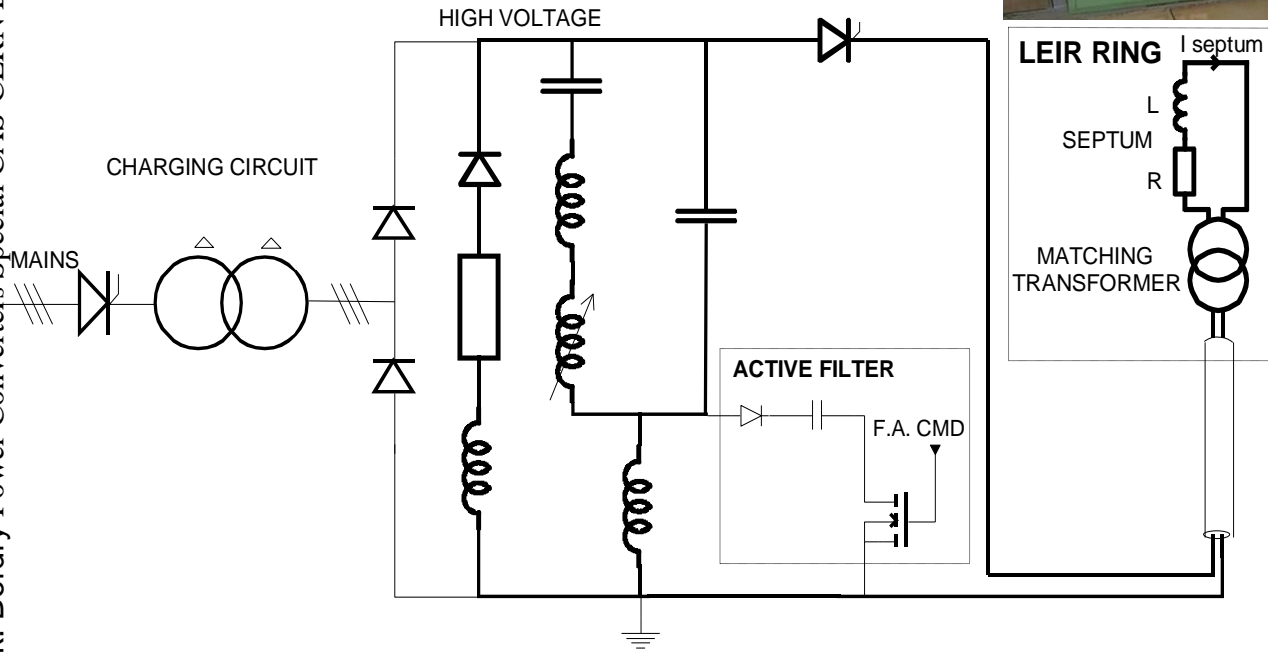
# Power Converters for injection/extraction Septa magnets

- Characteristics :
  - output current : 33.7 kA
  - flat top stability  $< 3 \cdot 10^{-4}$
  - charging voltage : 2.1 kV
  - 1 Hz repetition rate




Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009

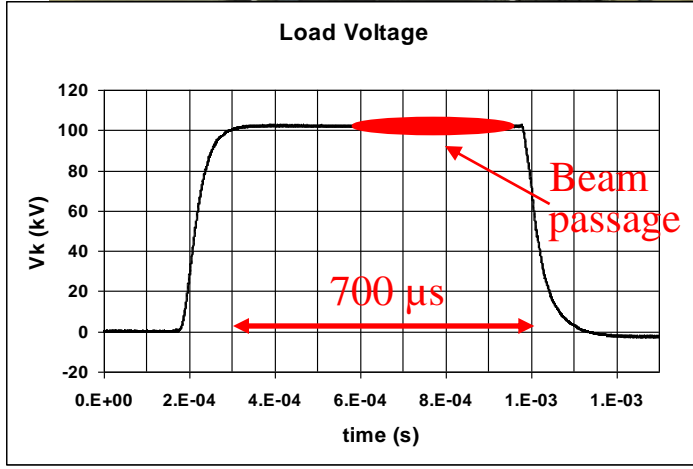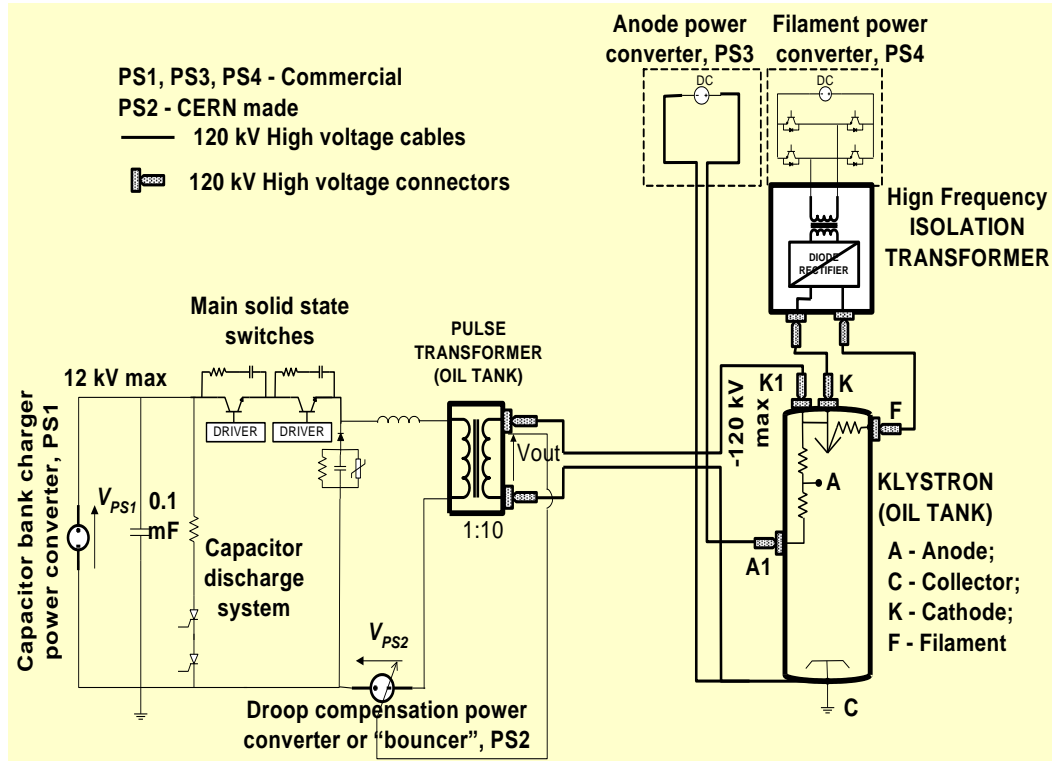- Characteristics :
  - output voltage : 100 kV
  - output current : 20 A
  - pulse length : 700  $\mu$ s
  - flat top stability : better than 1%
  - 2 Hz repetition rate



# Power Converter % Load


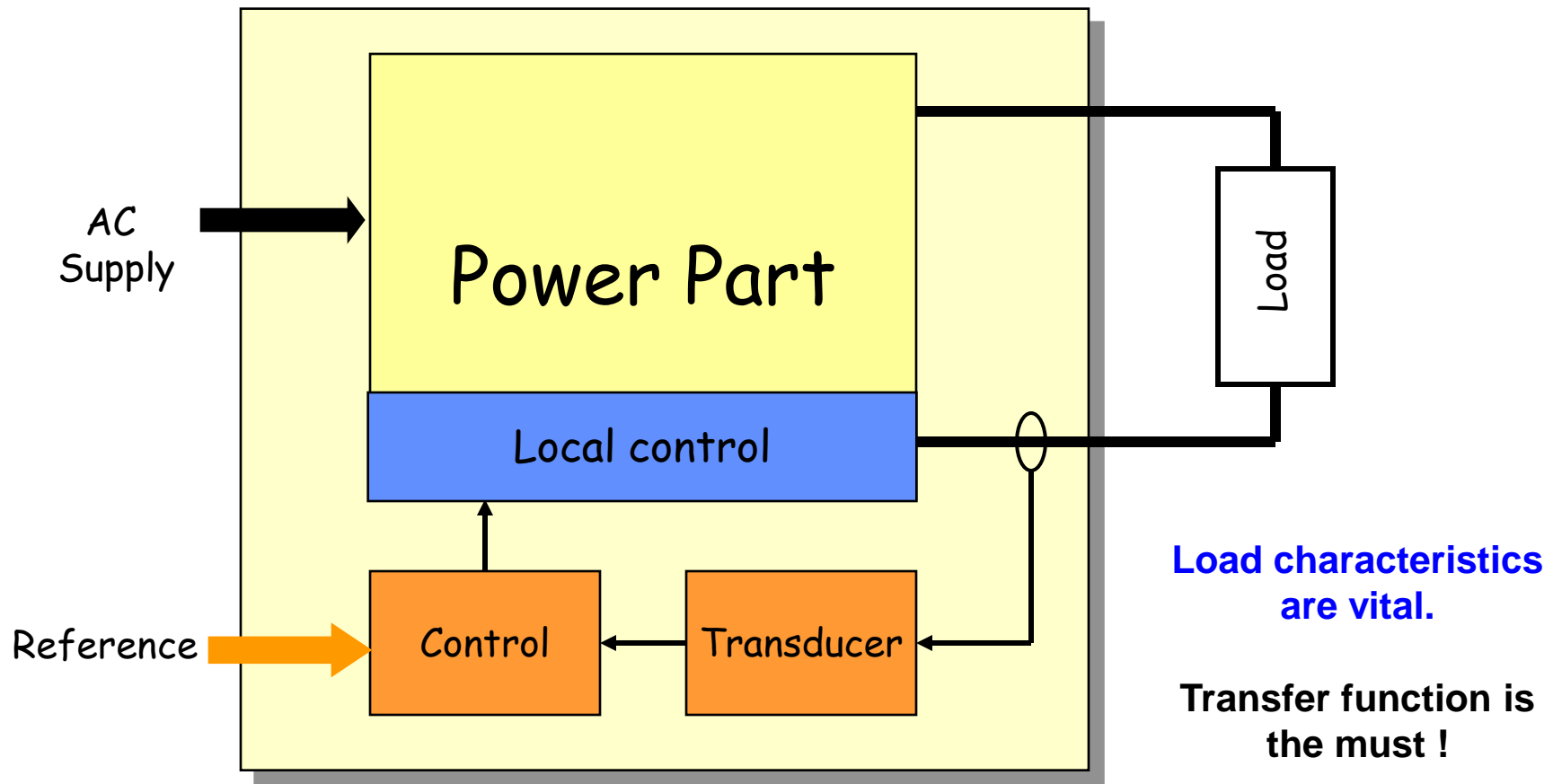


**Load characteristics are vital.**

**Transfer function is the must !**


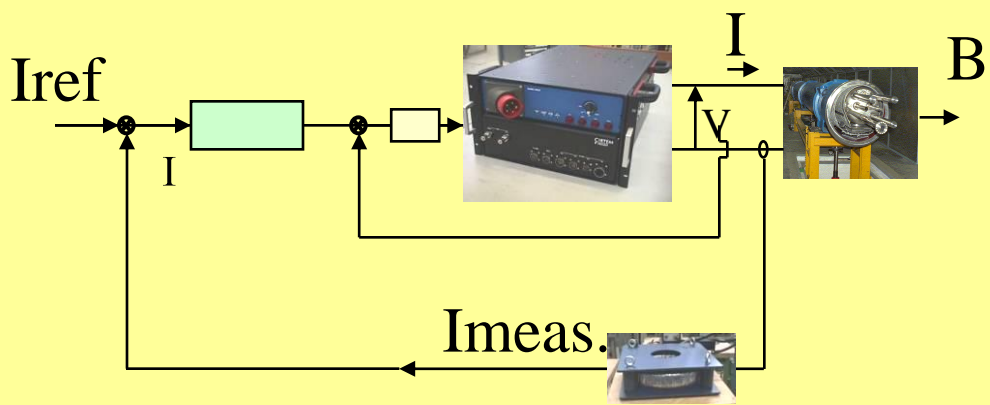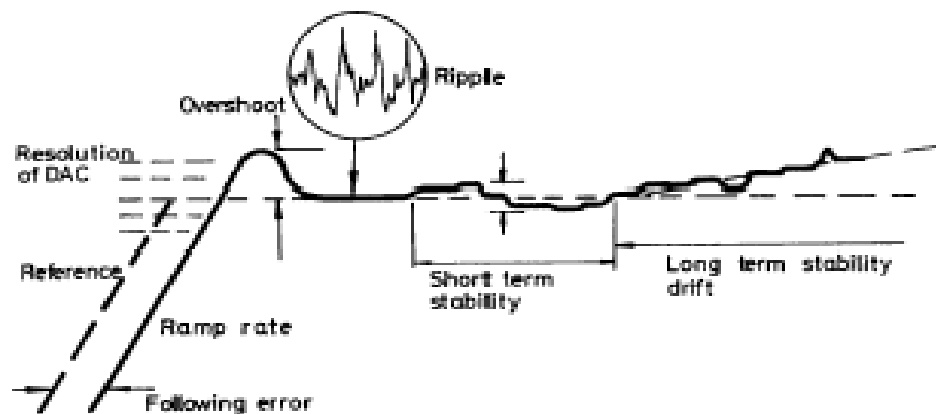
# Power converter : Performance requirements



**Accuracy**   **Reproducibility**   **Stability**

**Resolution**

**Overshoot**

**Bandwidth**





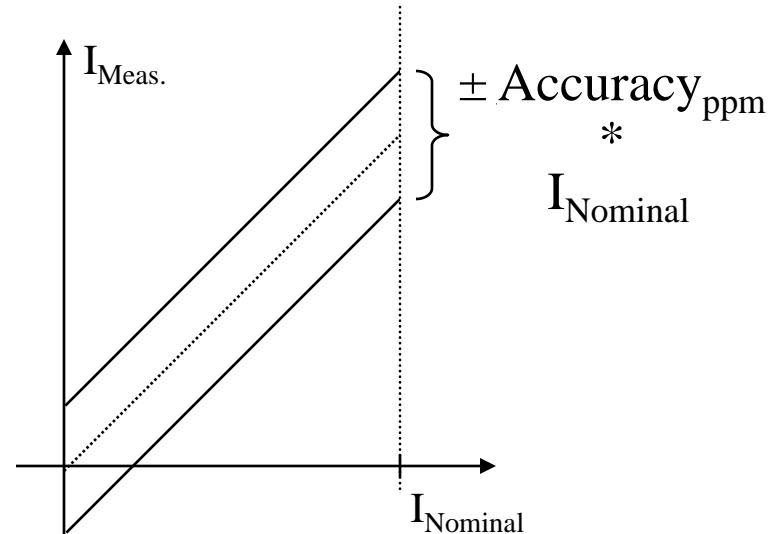
# Accuracy

Long term setting or measuring uncertainty taking into consideration the full range of permissible changes\* of operating and environmental conditions.

\*requires definition :  
(e.g. Electrical distribution system perturbation, temperature variation,...)



The accuracy is defined by default for a defined period ( $T_a$ )  
(e.g. **one year**)


The accuracy is expressed in ppm of  $I_{Nominal}$  •

If the defined period ( $T_a$ ) is too large, a calibration process should be executed more often (e.g every month)
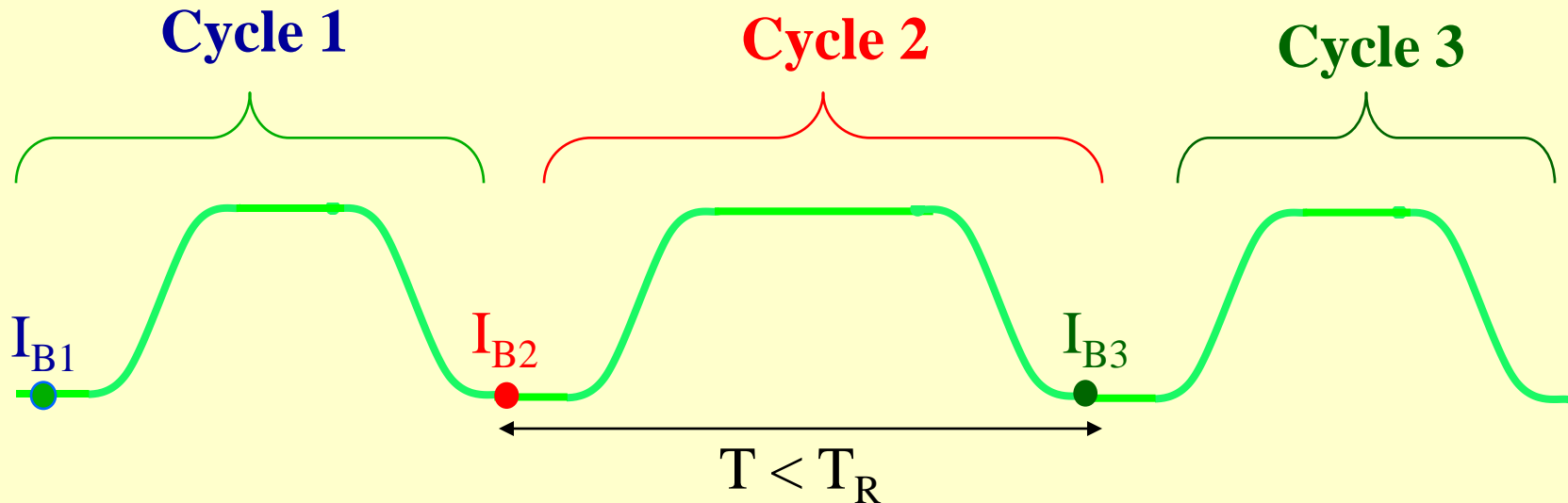
# Reproducibility

Uncertainty in returning to a set of previous working values from cycle to cycle of the machine.

The reproducibility is defined by default for a period of time  $T_R$  without any intervention affecting the calibrated parts (e.g. DCCT, ADC)  
The reproducibility is expressed in ppm of  $I_{\text{Nominal}}$ .



$$I_{B2} = I_{B1} \pm (\text{Reproducibility}_{\text{pmm}} \cdot I_{\text{nominal}})$$




$$I_{B3} = I_{B2} \pm (\text{Reproducibility}_{\text{pmm}} \cdot I_{\text{nominal}})$$



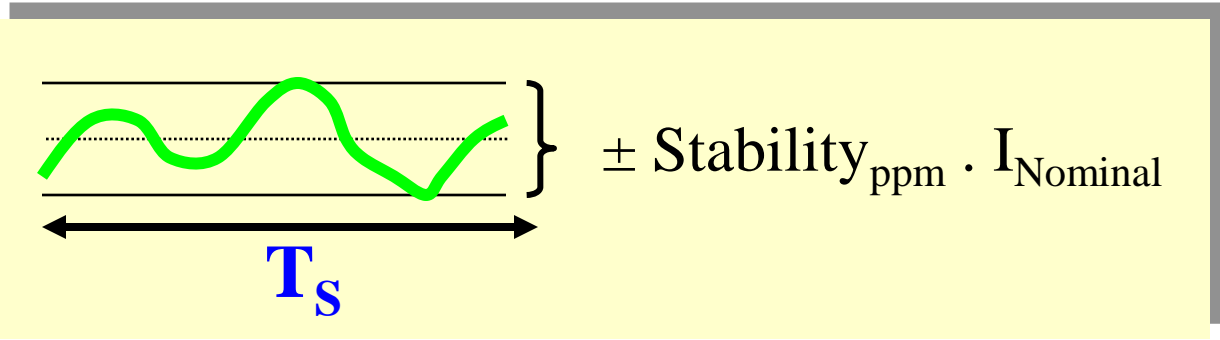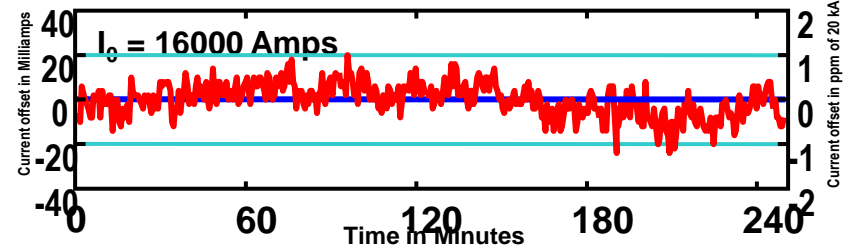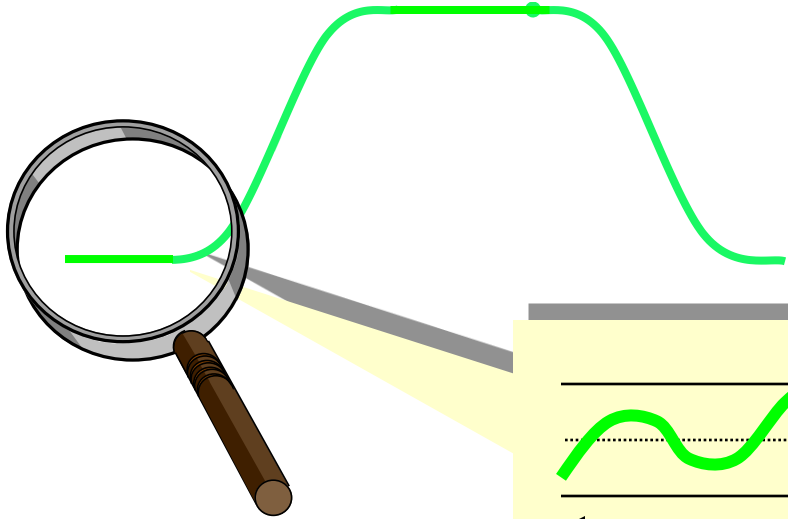
# Stability

Maximum deviation over a period with no changes in operating conditions.

The stability is defined by default for a period of time  $T_S$  (typically 1/2 hour)  
The stability is expressed in ppm of  $I_{Nominal}$  .



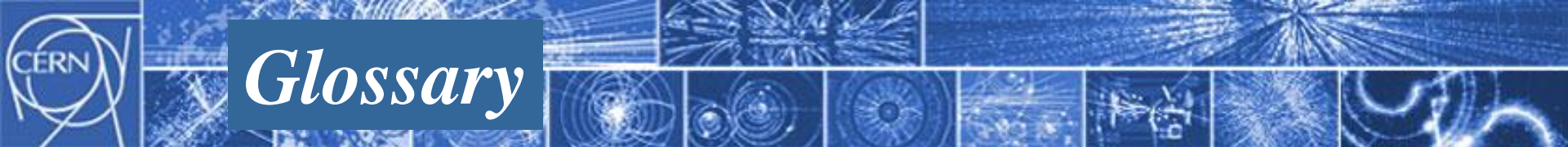

# Glossary


Fk. Bordry Power Converters Special CAS-CERN Divonne 27 February 2009

## Precision

### - Accuracy


Long term setting or measuring uncertainty taking into consideration the full range of permissible changes\* of operating and environmental conditions.

\* requires definition

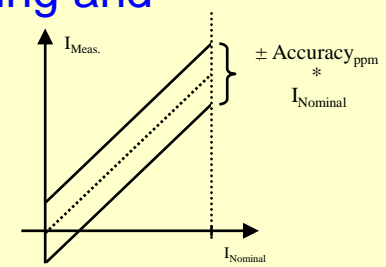

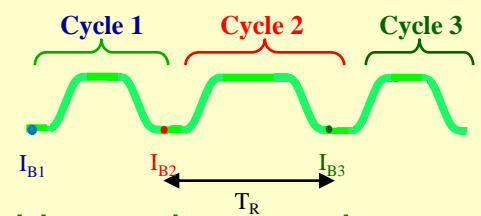
### - Reproducibility

Uncertainty in returning to a set of previous working values from cycle to cycle of the machine.


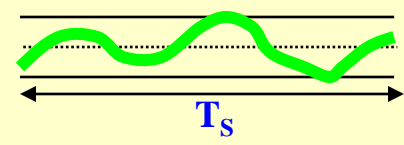
### - Stability

Maximum deviation over a period with no changes in operating conditions.



Accuracy, reproducibility and stability are defined for a given period


**Precision is qualitative . Accuracy is quantitative.**


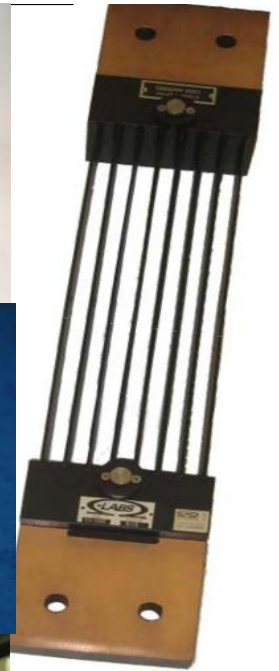
# Current measurement for power converter applications

The most common current measurement technologies used in power converter applications and the electrical principles behind them are summarised below:

- **Resistive shunts, current sense resistors:** Current to voltage conversion (Ohm's law)
- **Hall effect current transducers:** Based on the conductor in the presence of an external magnetic field
- **DCCTs:** A zero flux detector (of the second harmonic) to generate a compensation current which is a measured. This current is converted to a voltage
- **Current Transformers (CTs):** Based on magnetic induction



CTs can also be used on similar applications. They are very useful in high current applications where direct measurement can be a problem.

Like **Optical CTs** are not so common. They use the Faraday effect (polarization rotation of light) to measure current.



## Accuracy Class: $10^{-2}$ to $10^{-3}$ (1% to 1000 ppm)

For this accuracy class, any of the technologies mentioned previously could be chosen. However DCCTs are relatively expensive and "over qualified" for this class so they are not listed below:

### Shunts

- High Currents (tens to hundreds of kA) -> might require forced cooling for  $10^{-2}$  accuracy
- Medium Currents (up to the kA) -> might require forced cooling for  $10^{-3}$  accuracy
- In DC applications performance is limited by power and temperature coefficients
- Low bandwidth. The AC performance is limited by parasitic components and by skin effect
- No isolation from primary current circuit. Common mode might be a problem !

### Hall effect transducers

- Available for a wide range of currents (from hundreds of mA to tens of kA) and accuracies
- Medium bandwidth (tens of kHz)
- Provide isolation from the primary current circuit

### CTs

- Available for medium to high Currents (up to tens of kA) with accuracies of 0.5%
- High bandwidth (up to the MHz) but no DC response
- Provide isolation from the primary current circuit
- Low maintenance (passive device)

### Rogowsky coils

- Available for very high currents (up to hundreds of kA) with  $10^{-3}$  accuracy. No saturation
- Very high bandwidth (up to tens of MHz) but no DC response
- Provide isolation from the primary current circuit



# Current measurement for power converter applications

**Accuracy Class:  $10^{-3}$  to  $10^{-4}$  (1000 ppm to 100 ppm)**

## Shunts

- Available for medium Currents (10A..1kA) at DC and 50/60Hz with accuracies to 500ppm
- On the 1 to 100A range, a new generation of laboratory coaxial shunts has pushed the accuracy to  $10^{-4}$  at frequencies up to 100kHz. Not viable for industrial applications.
- Small currents (<10A) up to a few kHz can be measured close to  $10^{-4}$  using current sensing resistors (metal foil resistors are the most used)

## DCCTs

- Available for the medium to high current ranges (up to tens of kA) to  $10^{-4}$
- Most suited for DC applications with tight accuracy requirements
- AC response up to a few tens of kHz
- Provide isolation from primary circuit

**Accuracy Class:  $10^{-4}$  to  $10^{-5}$  (100 ppm to 10 ppm)**

## Current sense resistors

- Can be used for small currents (<10A) at DC and AC (few kHz). Metal foil current sensing resistors are suited for this range of accuracy. Particularly Zeranin foil resistors offer very low Temperature and Power Coefficients and have a very low inductance.

## DCCTs

- Available for the medium to high current ranges (up to tens of kA) to  $10^{-5}$
- Need good current sensing resistors to convert the compensation current into a measurable voltage
- Factors like magnetic head design, output stage drift, thermal management, output noise become very important at this level



**Accuracy Class:  $10^{-5}$  to  $10^{-6}$  (10 ppm to 1 ppm)**

Current sense resistors

- Small currents (<10A) at DC and AC (some kHz). Special designs can achieve accuracies of a few ppm but factors such as humidity, temperature, power dissipation, ageing and EMI mean that it is very difficult to assure this performance outside a controlled environment.

DCCTs

- Available for the medium to high current ranges (up to >kA) to better than  $10^{-5}$ .
- High quality current sensing resistors are essential. ppm level performance is only possible to achieve in a controlled environment.
- Factors like head centering, head error, magnetic remanence become very important

Picture: Temperature controlled EMC Racks housing 6 electronic chassis for the 13kA High Precision DCCTs for the LHC main power converters








# Resolution


**Smallest increment that can be induced or discerned.**

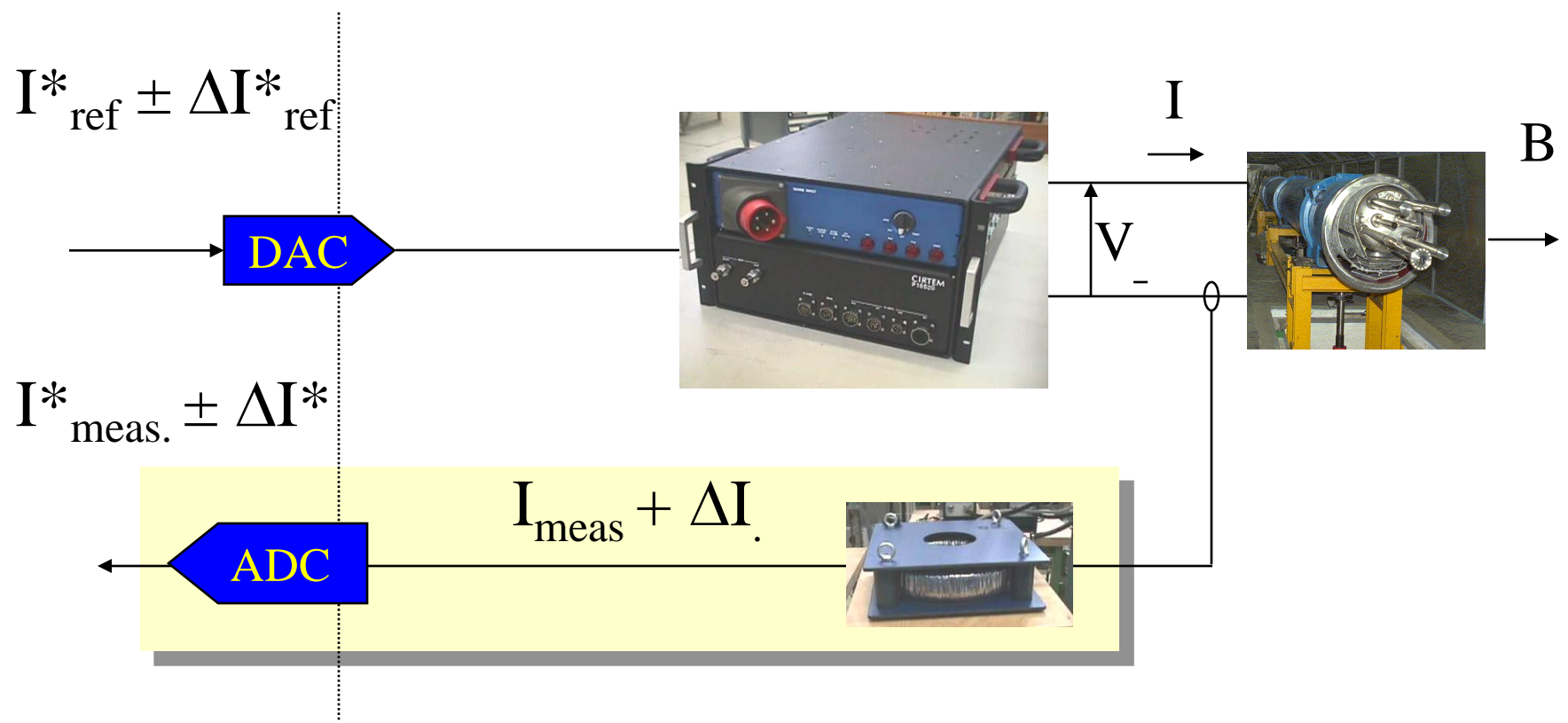
**The resolution is expressed in ppm of  $I_{Nominal}$  • Resolution is directly linked to A/D system**




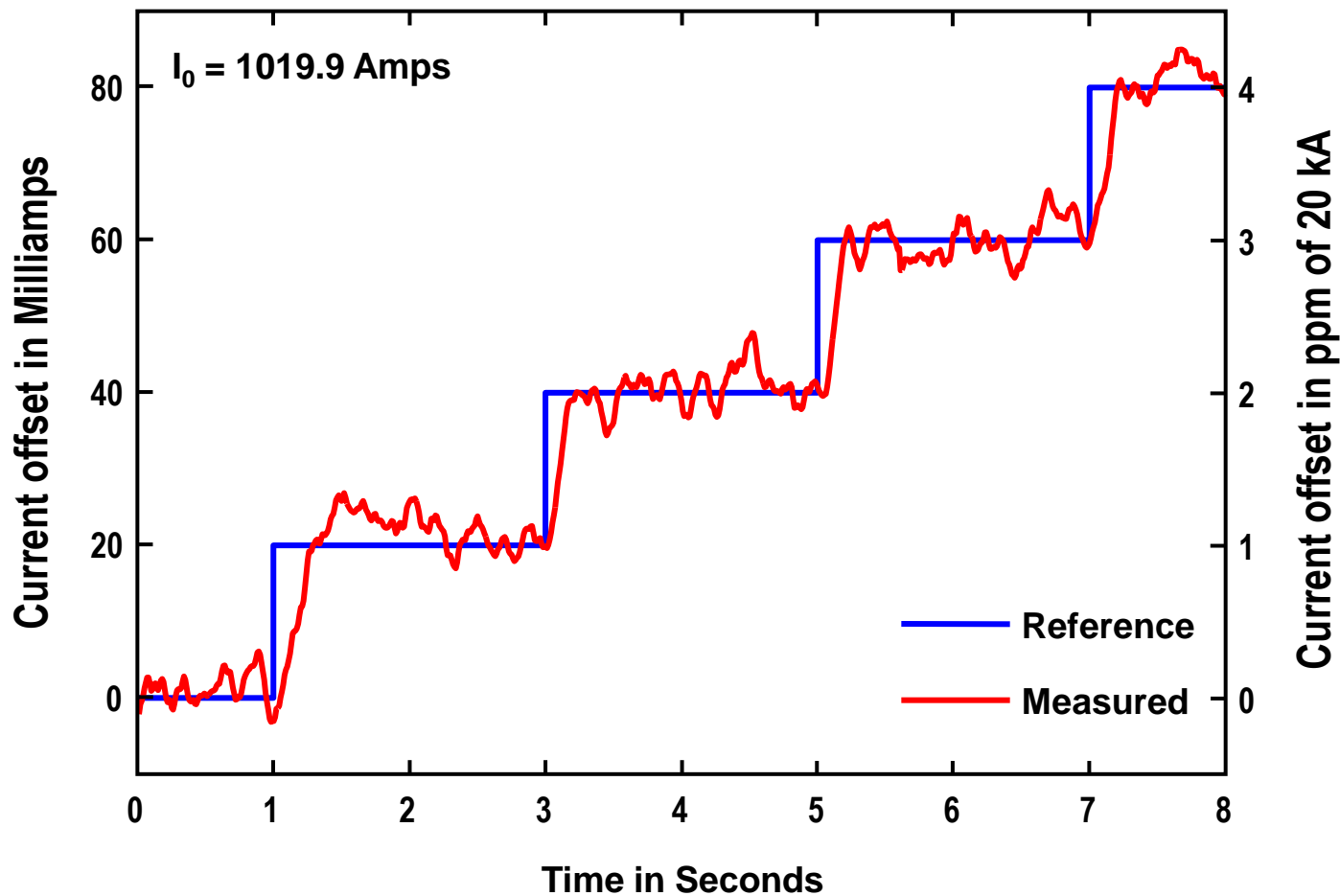
# Results of Resolution Test with the LHC Prototype Digital Controller



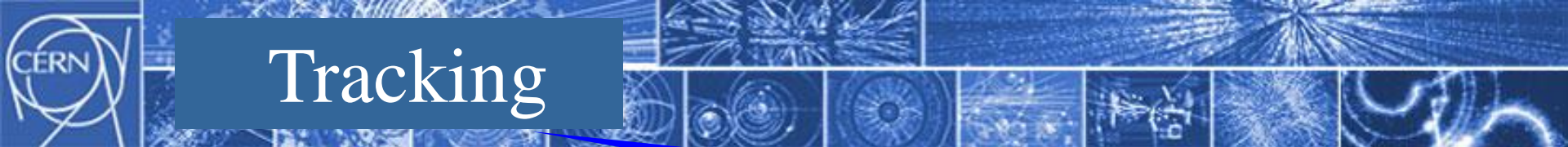


# Tracking


Ability of the converter  $S$  to follow the reference function (static, dynamics)

Static part is covered by the static definition : accuracy, reproducibility


Tracking error between I1 and I2

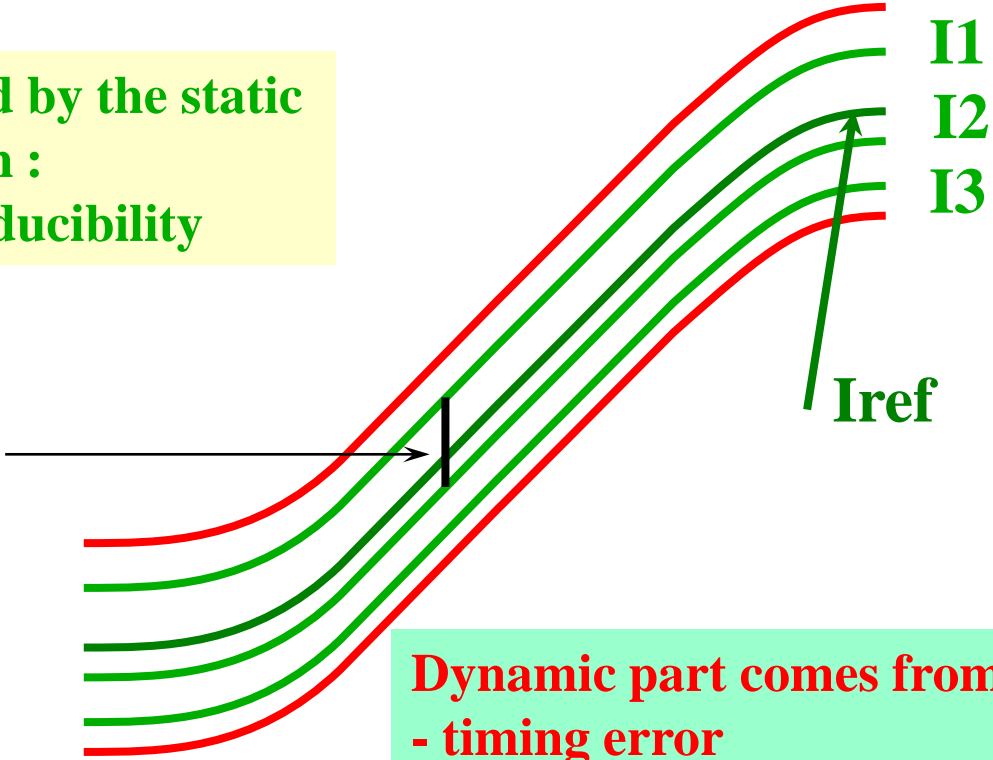

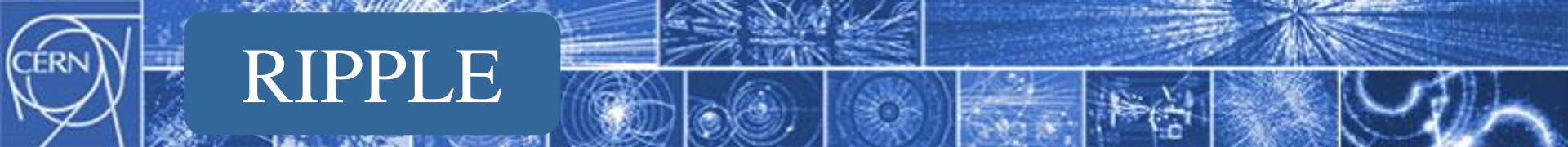Dynamic part comes from :  
- timing error  
- lagging error in the regulation



# RIPPLE

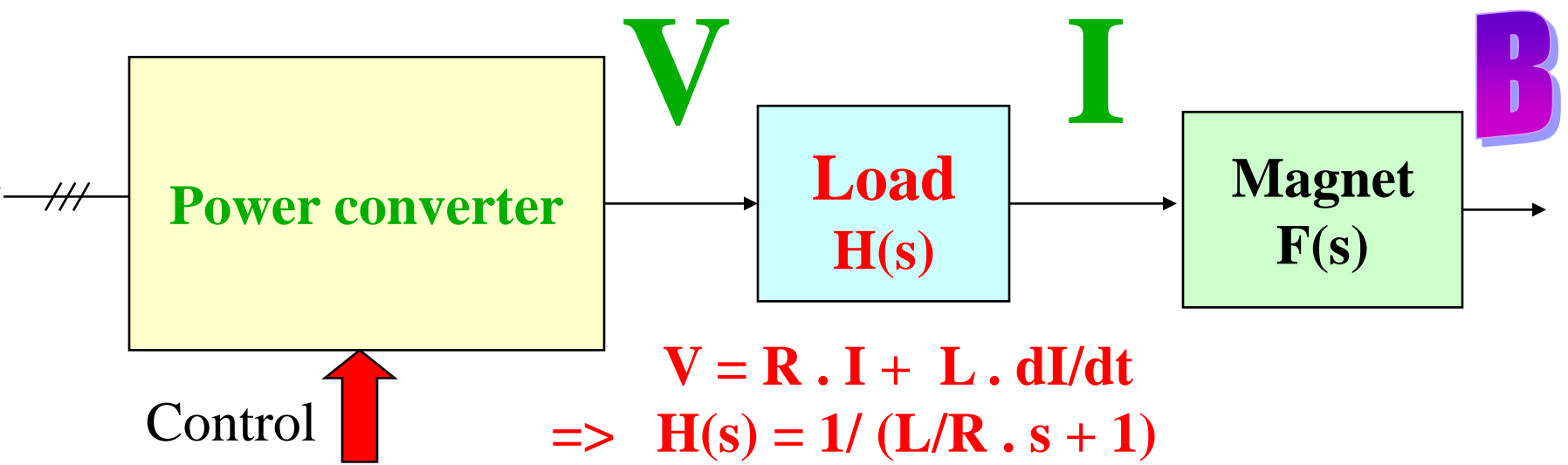

**Voltage ripple is defined by the power converter**

**Current ripple : load transfer function**

**(cables, magnet inductance,...)**

**(good identification is required if the load is a long string of magnets )**

**Field ripple : magnet transfer function (vacuum chamber,...)**



# EMC : ELECTROMAGNETIC COMPATIBILITY

## COMPATIBILITY : Emission - Immunity

IEC 61204-3

Norms for the power converters :

### Emission :

IEC 61204-3 ( replaced IEC-60478-3)  
(CISPR 11 ; EN 55011)


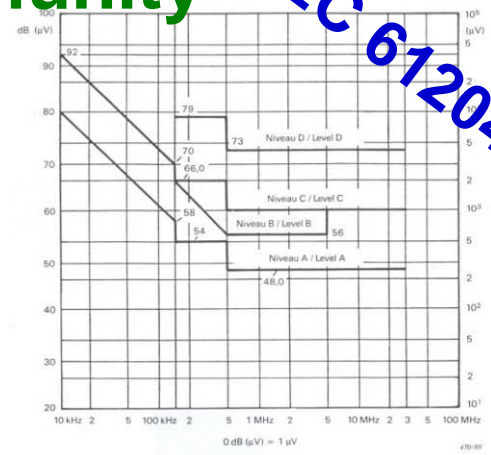


Figure 3 - Valeurs limites pour PEM par conduction  
Limit values for conducted EMI


### Immunity :

IEC 61000 - 4 :  
Burst 61000 - 4 - 4  
Surge 61000- 4 - 5

IEC 61000-4-4

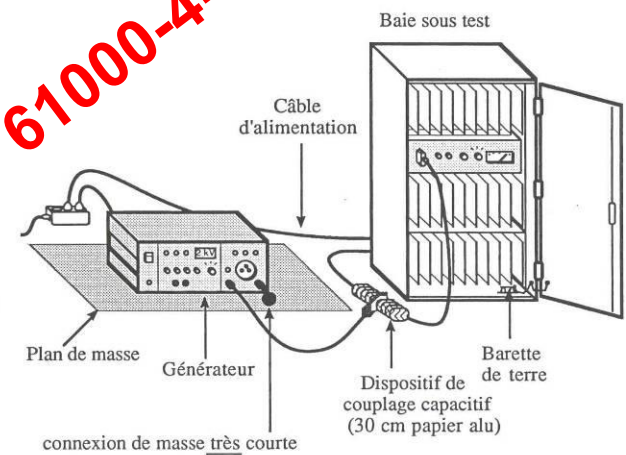
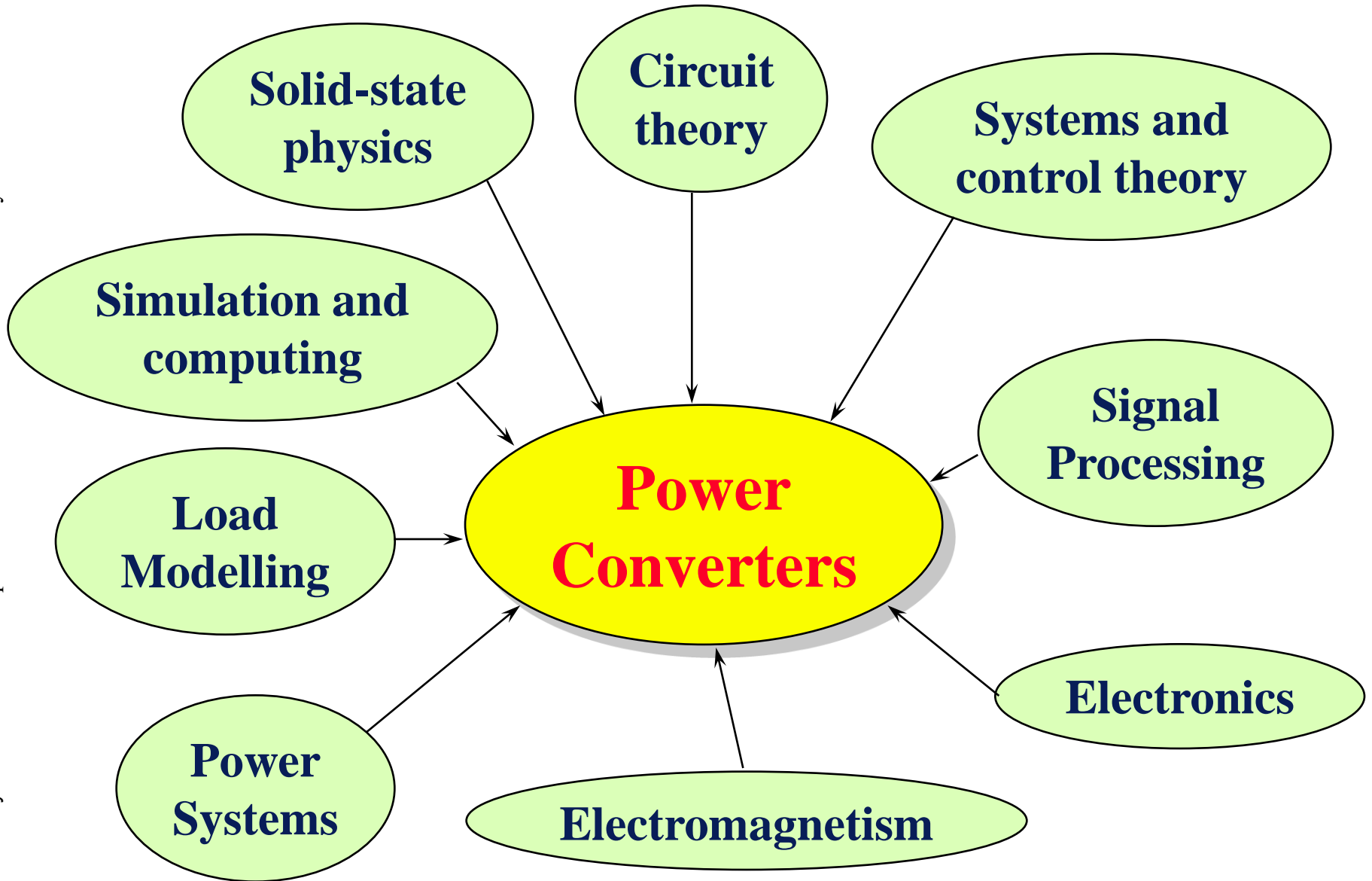
# Interdisciplinary nature of power converters





# Power converters specifications

**"Do you have one or two power converters for the test of magnet prototype? 200 A will be enough ? Precision is not important for time being. Don't worry it's not urgent. Next month is OK "**  
**(Email received 05.12.08)**

**Load characteristics :** I and V reversibility ( 1 , 2 or 4-quadrants ? ) ;  
Transfer function (at least R, L, C) => will define V and the power

**Range :** I<sub>max</sub> (and I<sub>min</sub>)

**Rise and fall time (di/dt max; voltage constraint on the load);** is the precision an issue during the ramps (beam or no beam) => Pulsed converters with intermediate storage ?  
=> bandwidth (topology and control strategy)


**Precision:** accuracy, reproducibility, stability

**Ripple:**  $\Delta V(f)$  => passive (or active) filters ; control strategy (SMPC)

**Is the volume a constraint ? Is water cooling possible ?**

**Environment:** temperature and humidity; EMI conditions, radiation,...

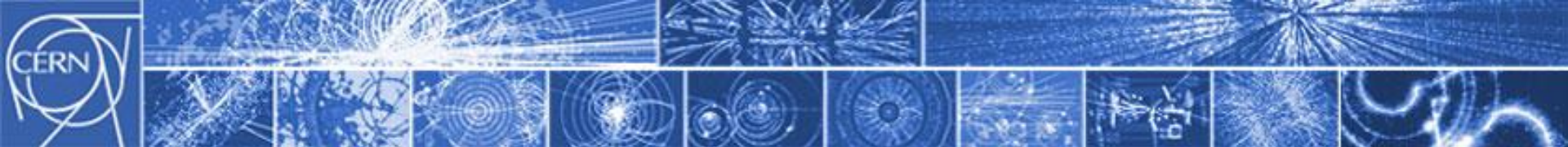**Hardware design and production take time.....**



# The end

**CAS - CERN Accelerator School :**  
**Power converters for particle accelerators**  
**26 - 30 Mar 1990, Switzerland**

**CERN Accelerator School and CLRC Daresbury Laboratory :**  
**Specialised CAS Course on**  
**Power Converters for particle accelerators**  
**12 - 18 May 2004 - Warrington, UK**