

*STUDY OF THE DISCRETE
COMPONENT OPTION FOR THE
ANALOGIC PART OF THE
ENHANCED FRONT END BOARD*

LIFAELS, EALS, Universitat Ramon Llull


Carlos Abellan Beteta

8 th April de 2009


The Chosen Amplifier

- ◎ Main characteristics for the AD8009AR
 - Size 3x3mm
 - Bandwidth 1GHz $G=+1$
 - Slew Rate 5,5V/ns
 - Input Equivalent Noise 1.9nV/sqrt(Hz)
 - Offset Error 5mV


Testing the amplifier

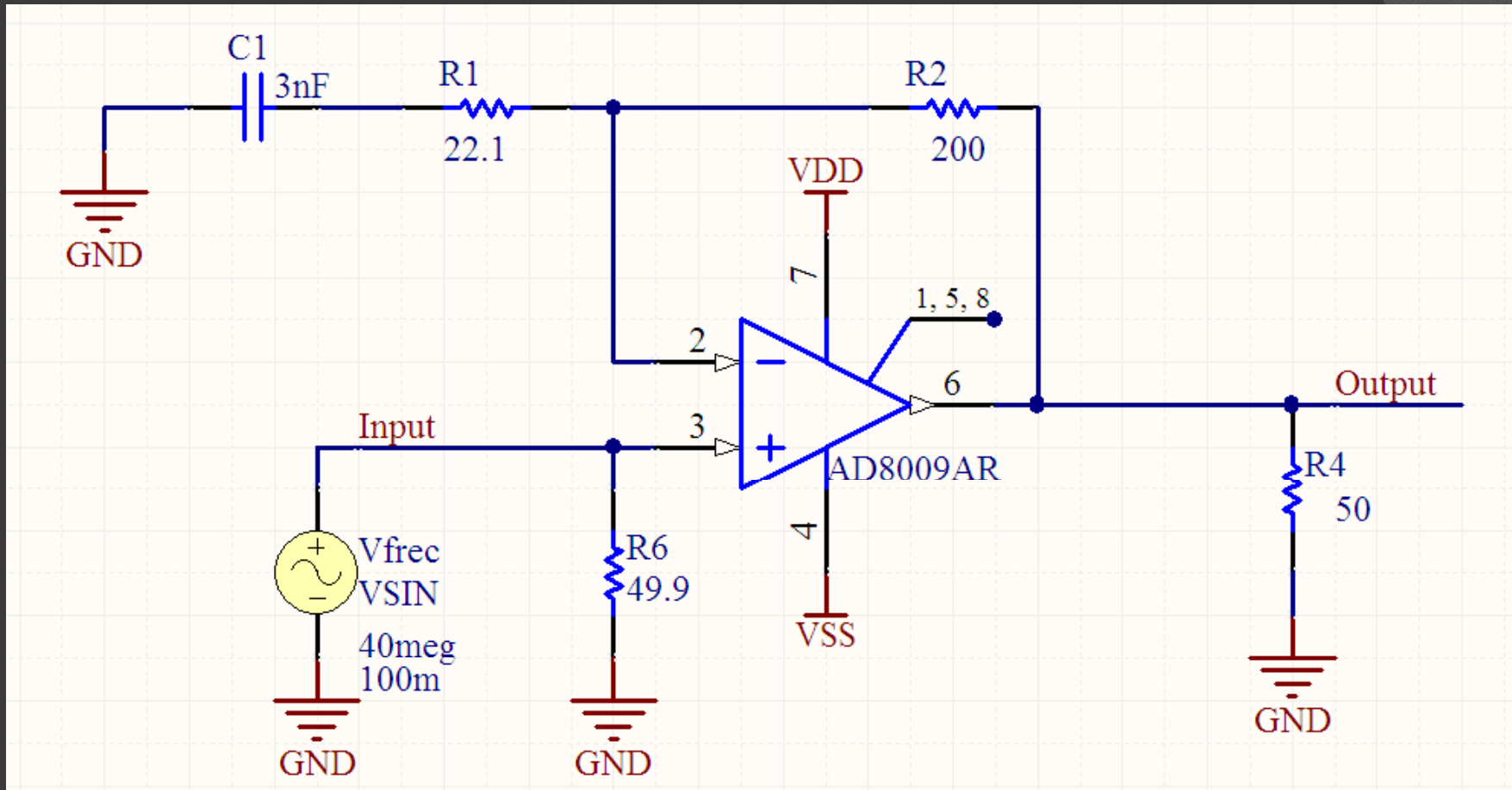

Testing the amplifier (no BW limit)

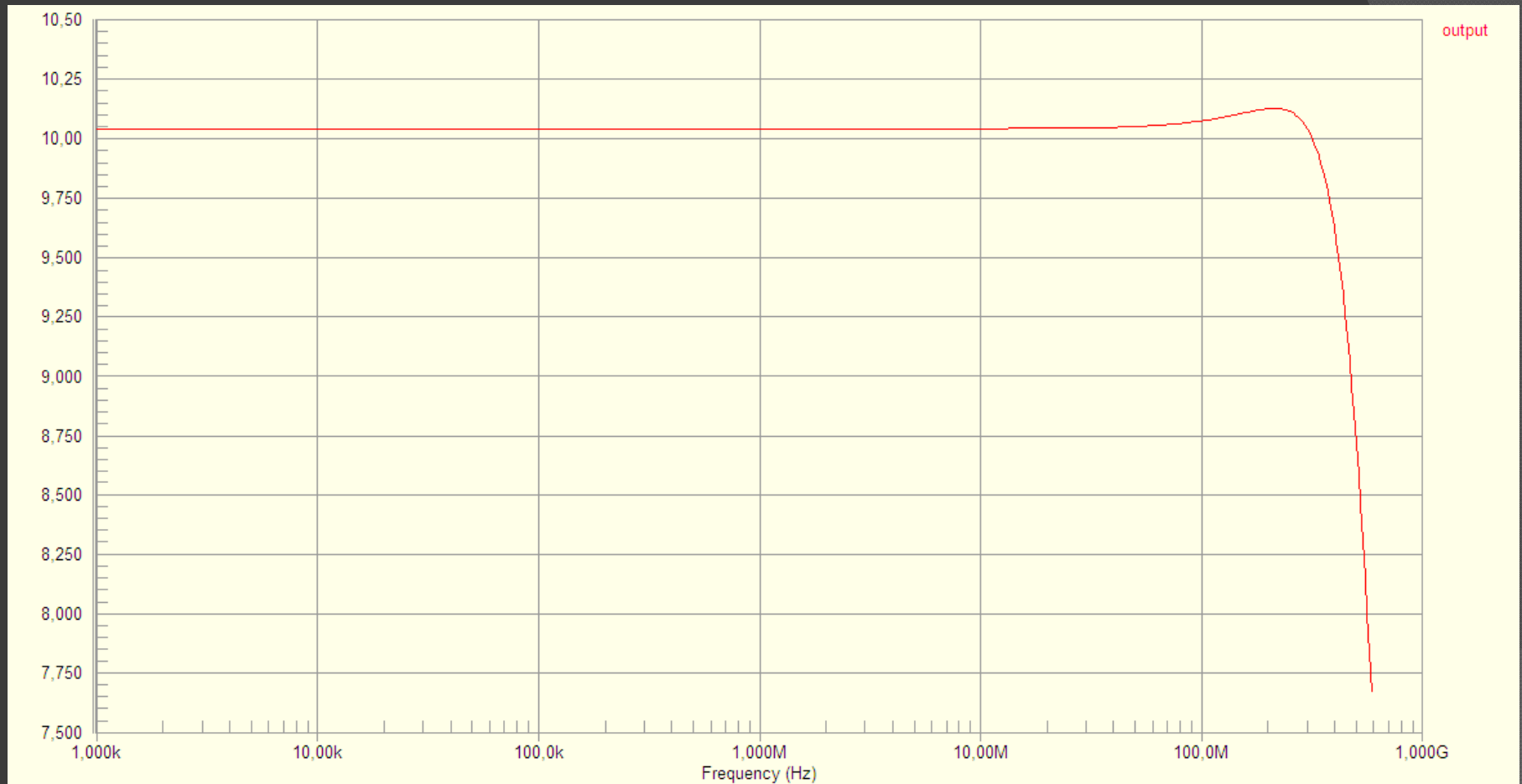


Testing the amplifier (3nF BW limit)

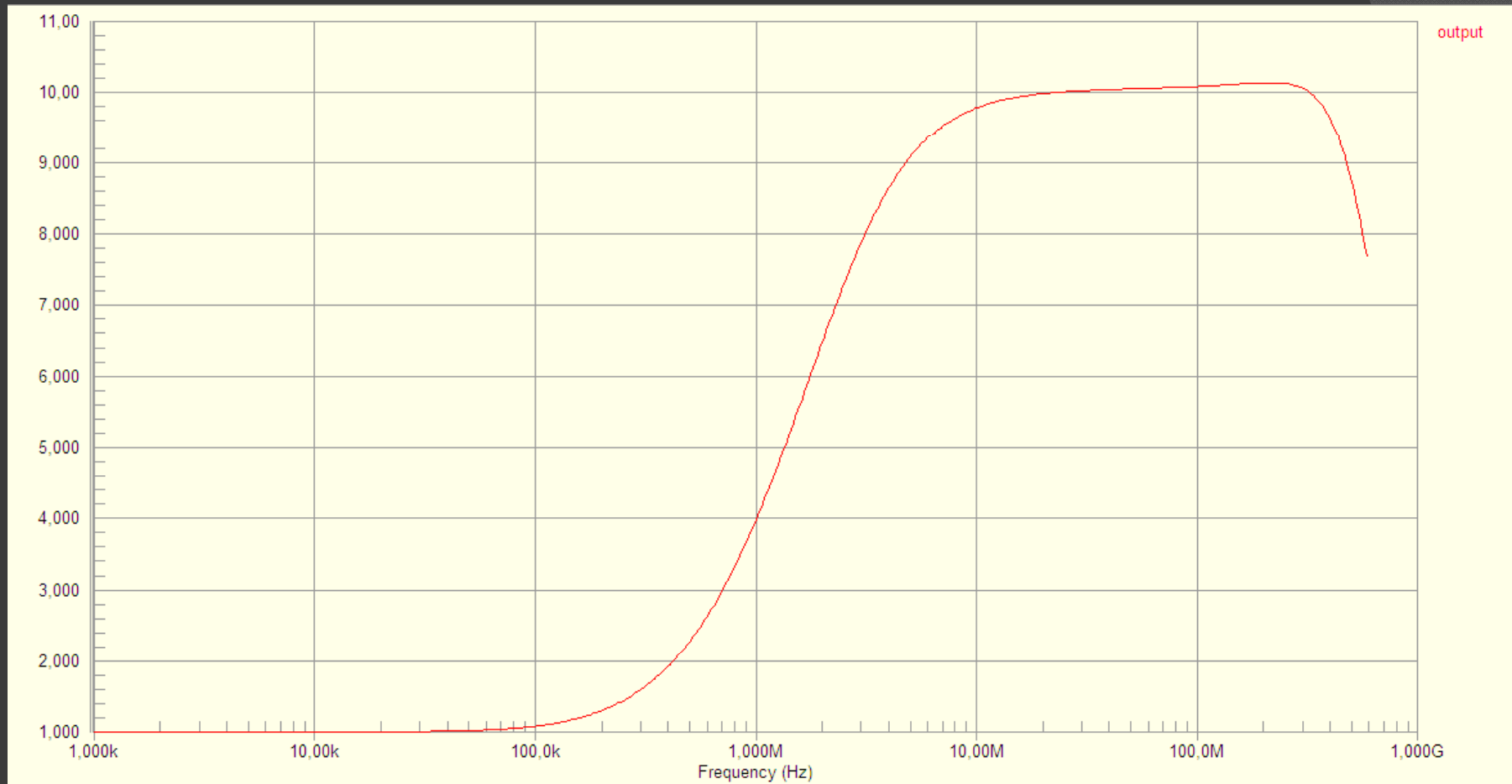


⦿ Reducing Bandwidth to decrease noise

First Approximation to the circuit(I)

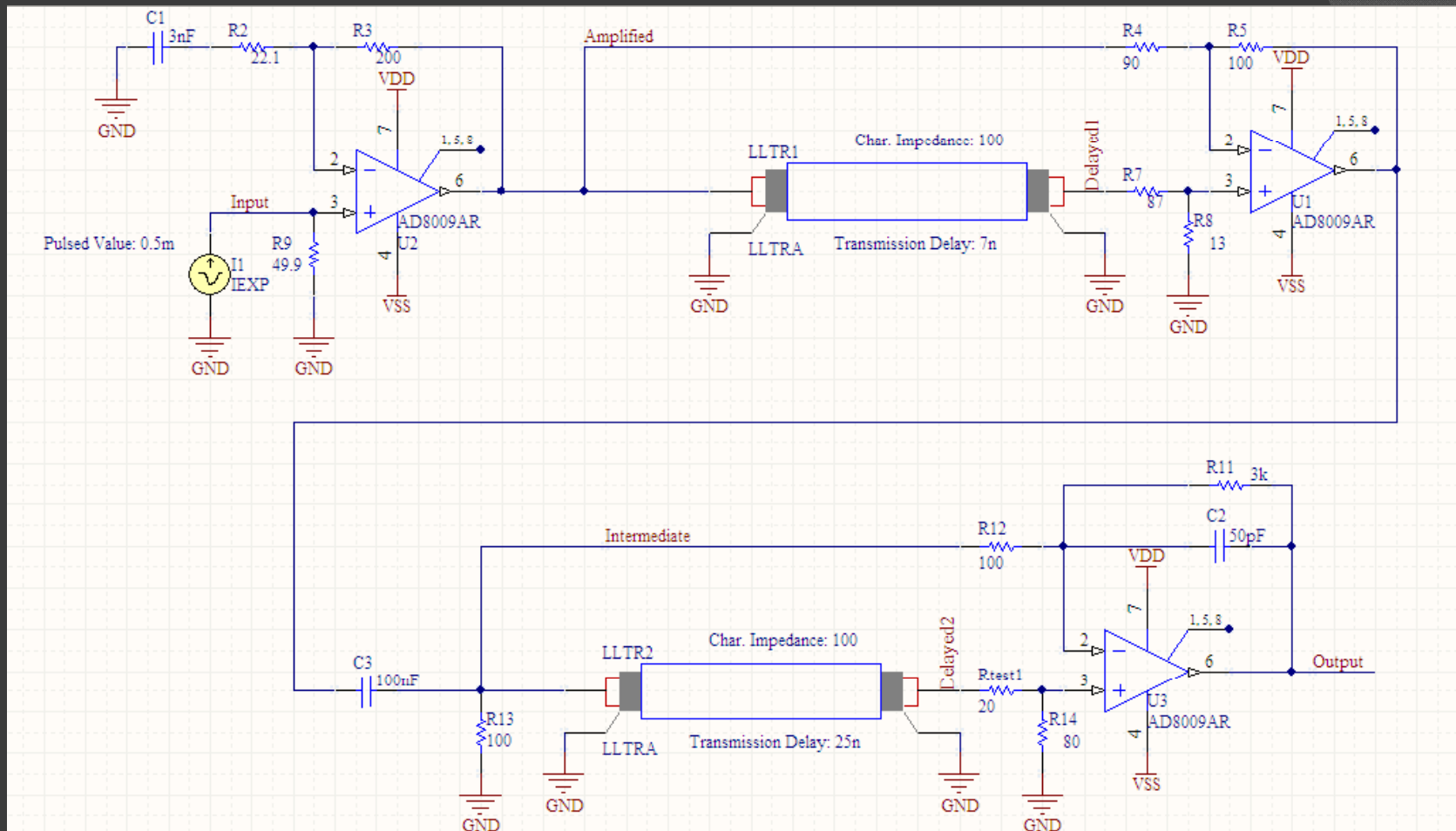


● Only 3 Ops.

First Approximation to the circuit(II)

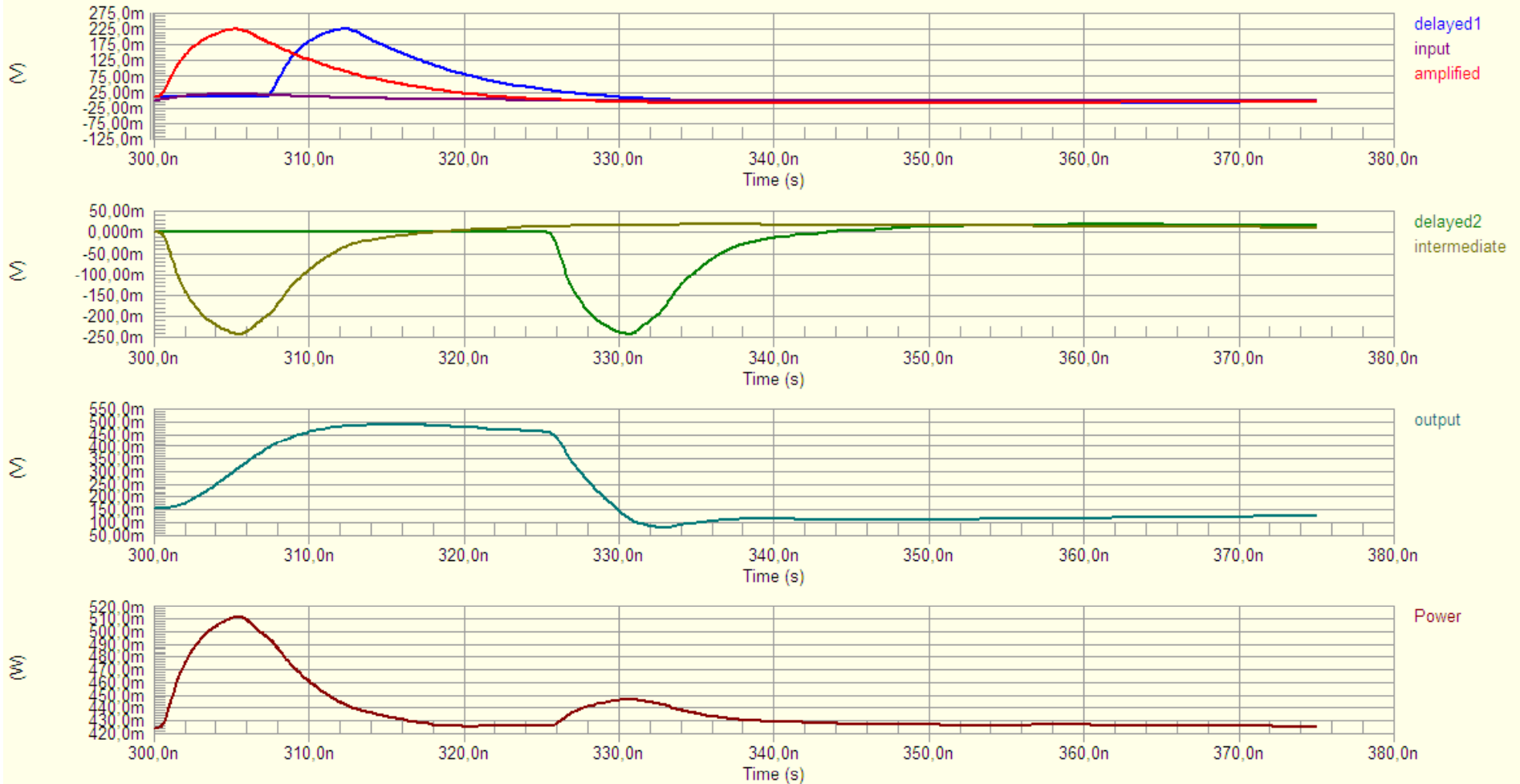


First Approximation to the circuit (III)

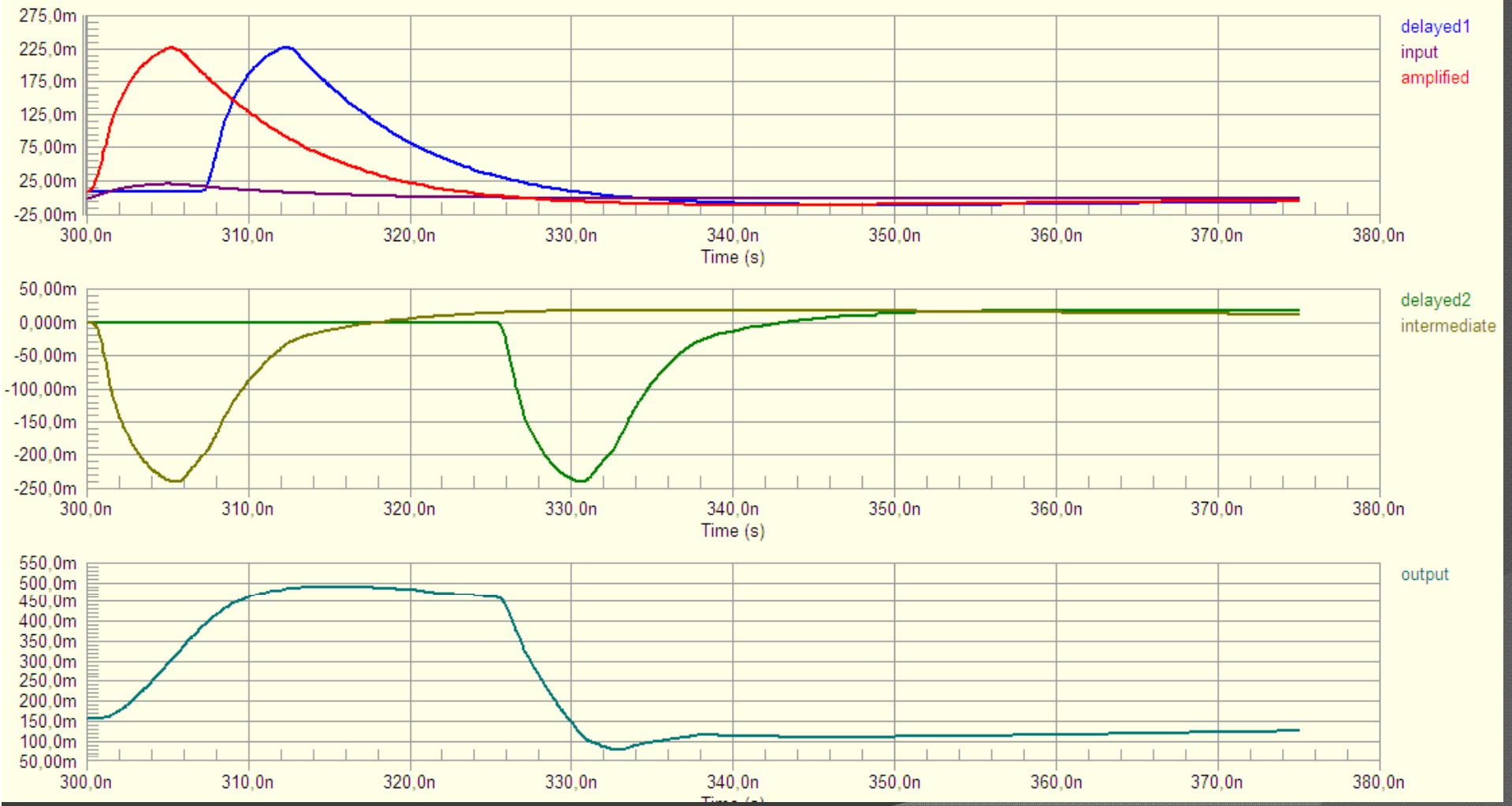

Other Studied Ideas

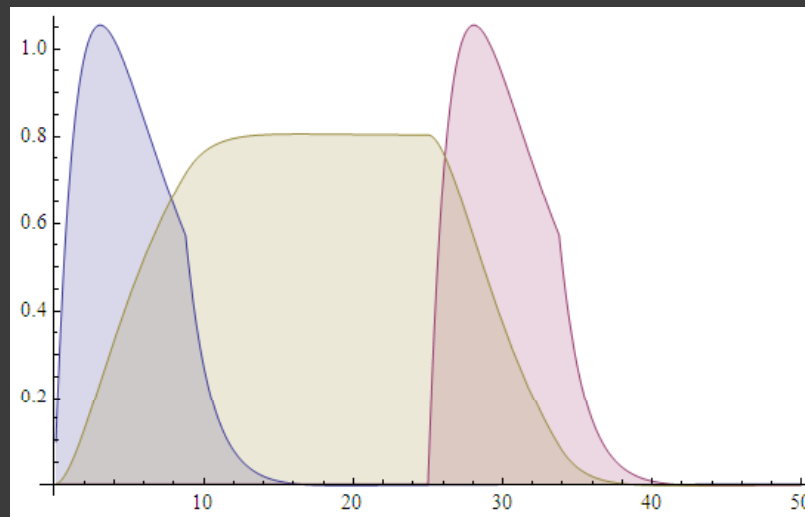- Is it possible to change the clipping system?
 - We could gain stability if we make the pulses go narrower. This way we may have a wide plateau and sample without problems.
 - Could it be useful to use multiplexed ADCs?



Other Studied Ideas

- Do we have to forget about using a discrete component solution for the low noise amplifier?
 - Already done in LAr calo.
 - I have a PCB design that is 1.5X3mm 2 ch.

