

Study of Frequency Divider PLL

Shruti Shrestha
KSU

September 18, 2009



Outlines:

Working principle of PLL

Importance of PLL in ROC


Behavior of PLL at room and low temperature

Simulation Results of ADC




Working Principle of PLL

Circuit for PLL

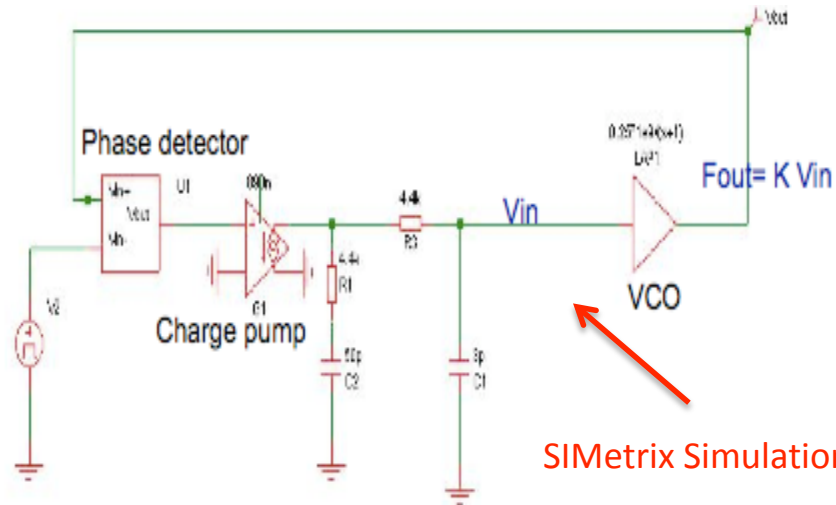


SIMatrix Simulation

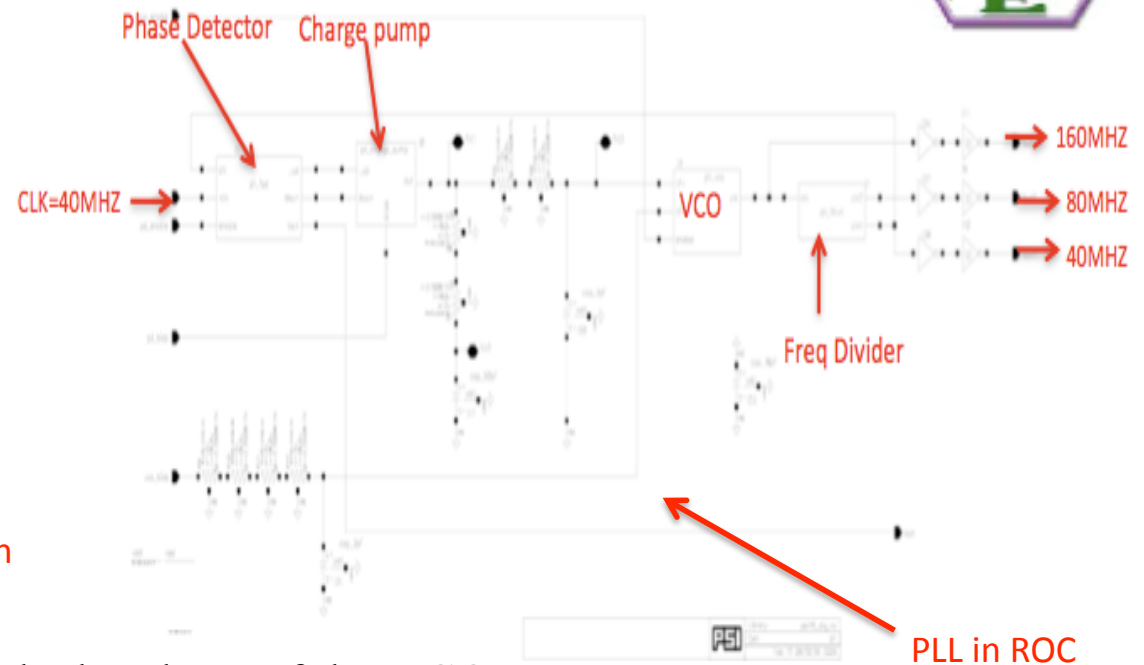

- Feed back Control system that controls the phase of the VCO.
- Input signal applied one input of P.D, the other input is connected to the output of a divide by N counter.
- The Output of the P.D is phase difference between the two inputs.
- This signal is applied to the loop filter with the help of charge pump. The filter signal controls the VCO . (if $f_{vco} > f_{clk}$, the capacitor to discharges to decrease input voltage to the VCO since $f_{out} = K V_{in}$)




Components of PLL

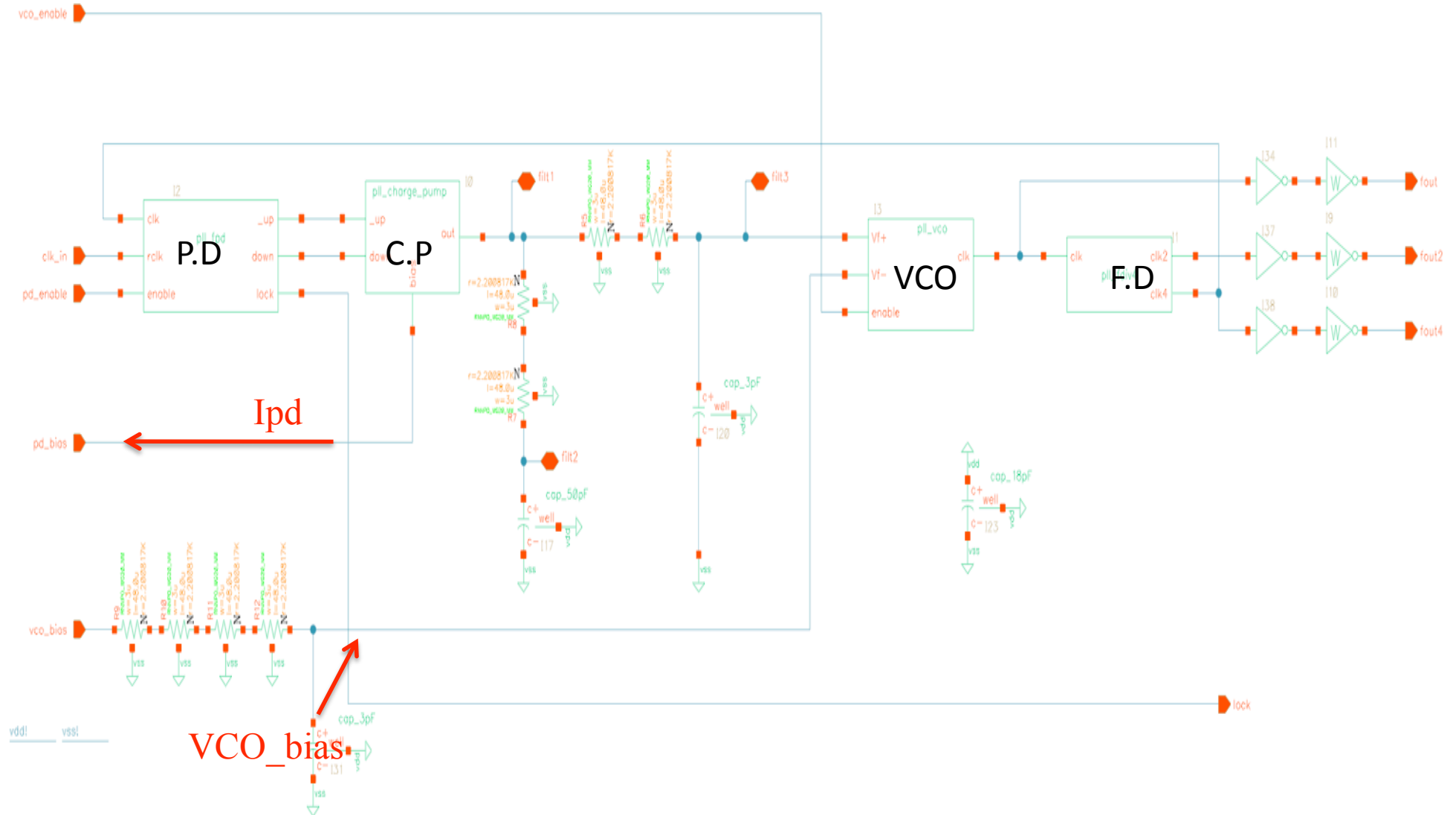



Use of PLL in ROC


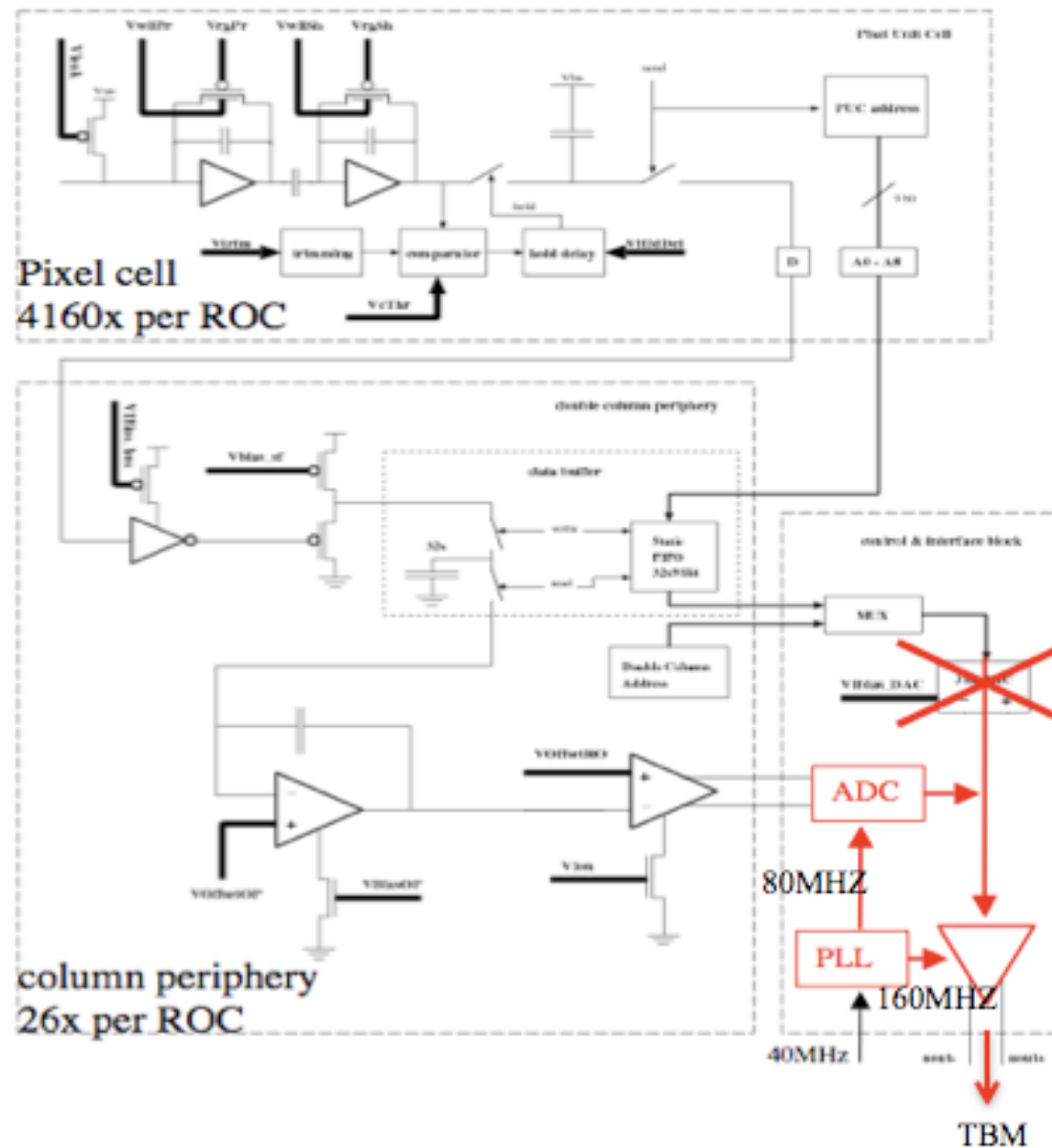


Layout of PLL



Circuit for
Input and Outputs to be taken

Test Setup for periphery Board

 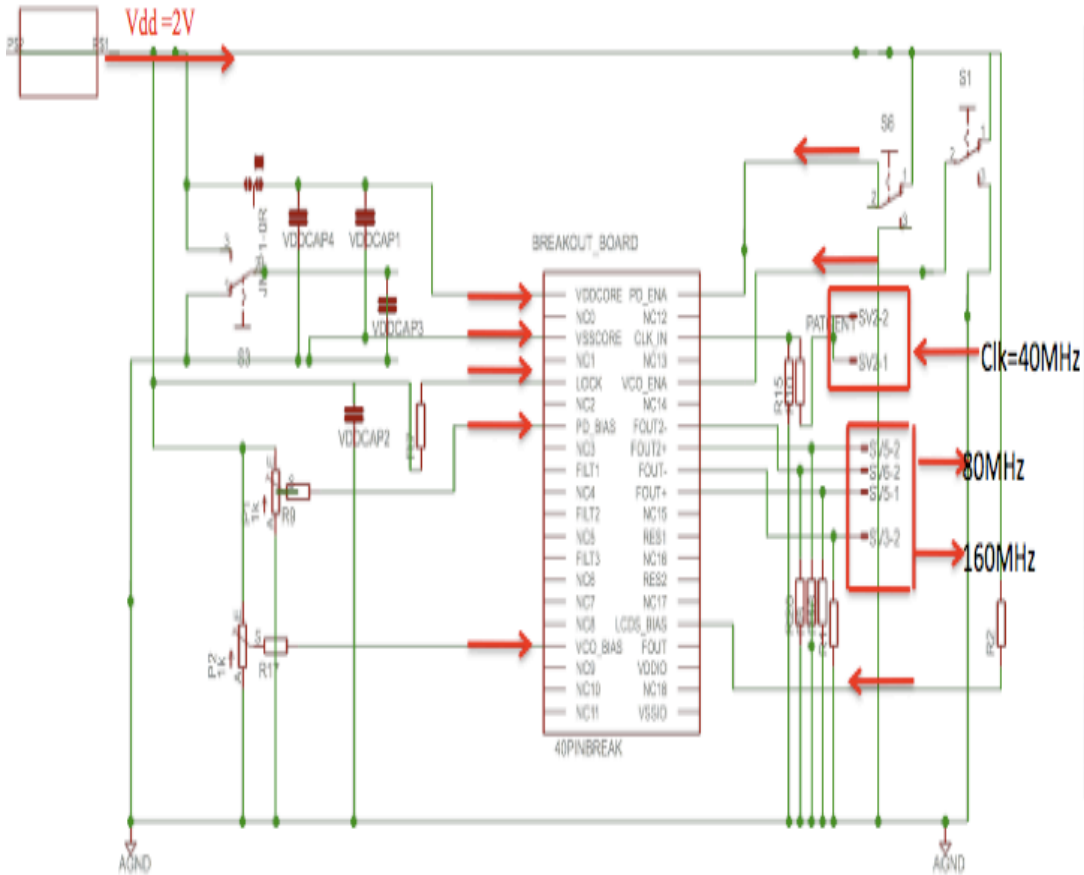




Results from PLL

Power Consumption



Ref Frequency(40MHZ)	I(mA)	Power Consumption (mW)
Without 50Ω resistances	0.773	1.546
Without 50Ω and 8.2KΩ	0.728	1.456
With all 50Ω and 8.2KΩ	4.783	9.566

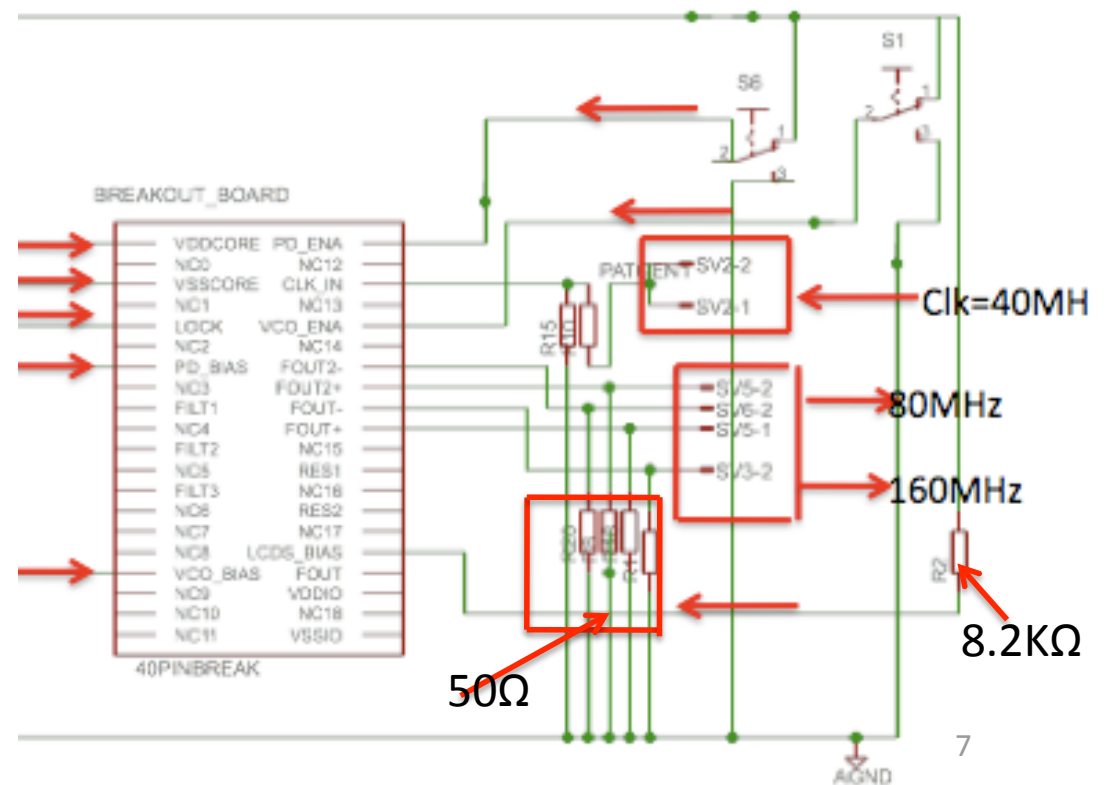

Calculation of Locking time PLL



Locking time:

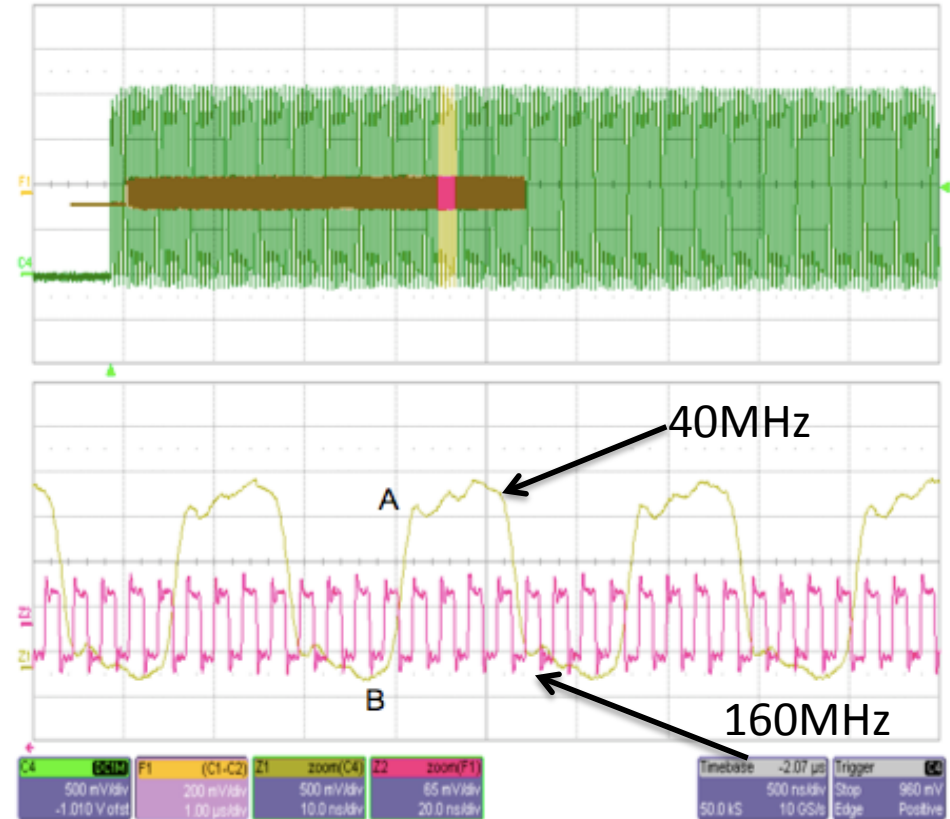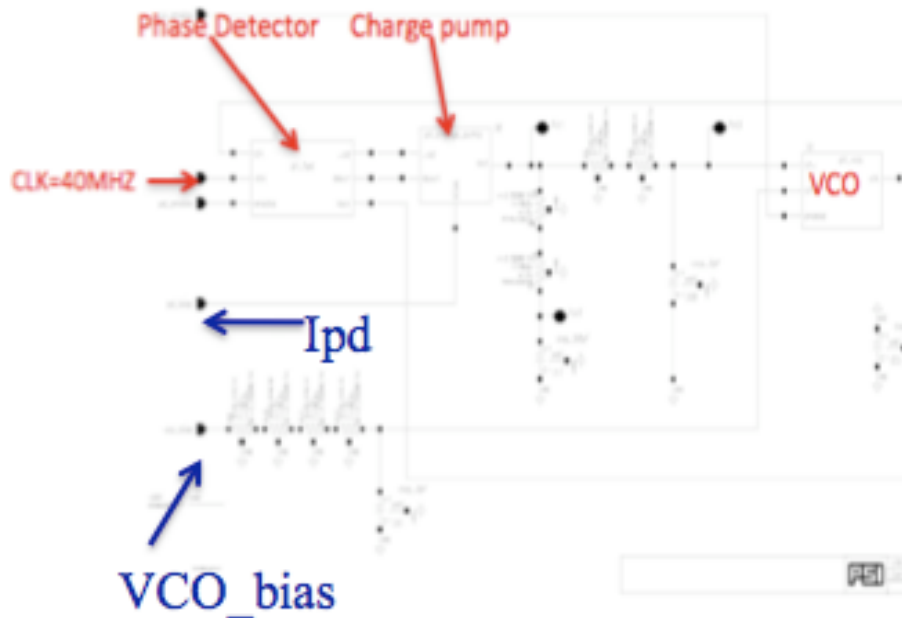


Variation parameters taken for calculating locking time are Ipd and VCO_bias

Results from PLL




Locking time

 Study of Range of Frequency that can be locked based upon VCO bias voltage for I_{pd} bias



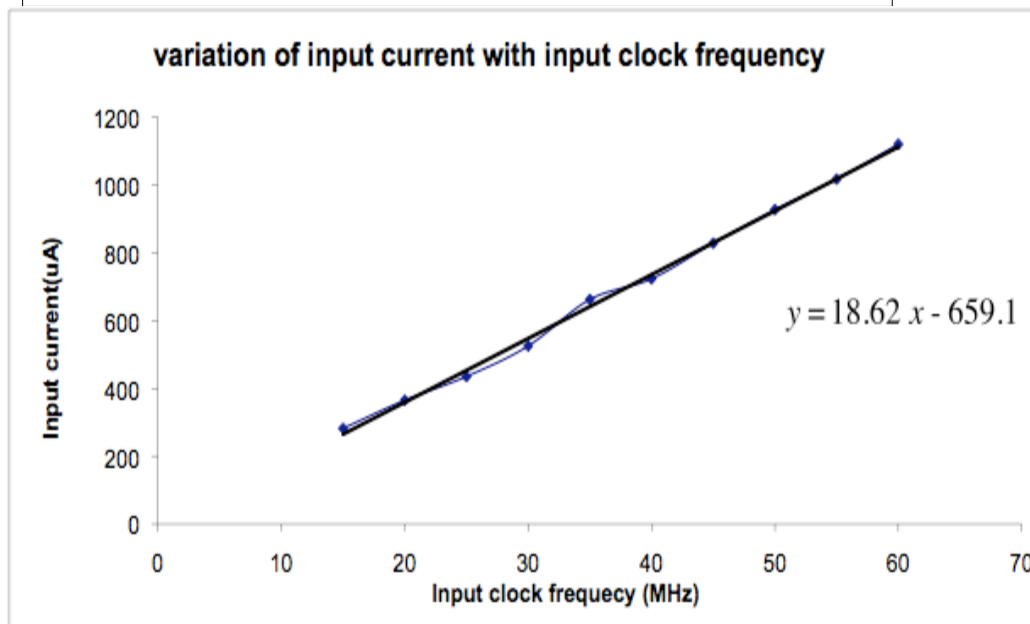From 80MHz output, PLL locks from 10MHz - 75MHz Reference Input frequency.



When F_{ref} = 0 , I = -659uA
Observed when F_{ref} = 0, I = 134uA


Results from PLL




Locking time:

Standard Fref = 40MHz and VCO = 0.8V

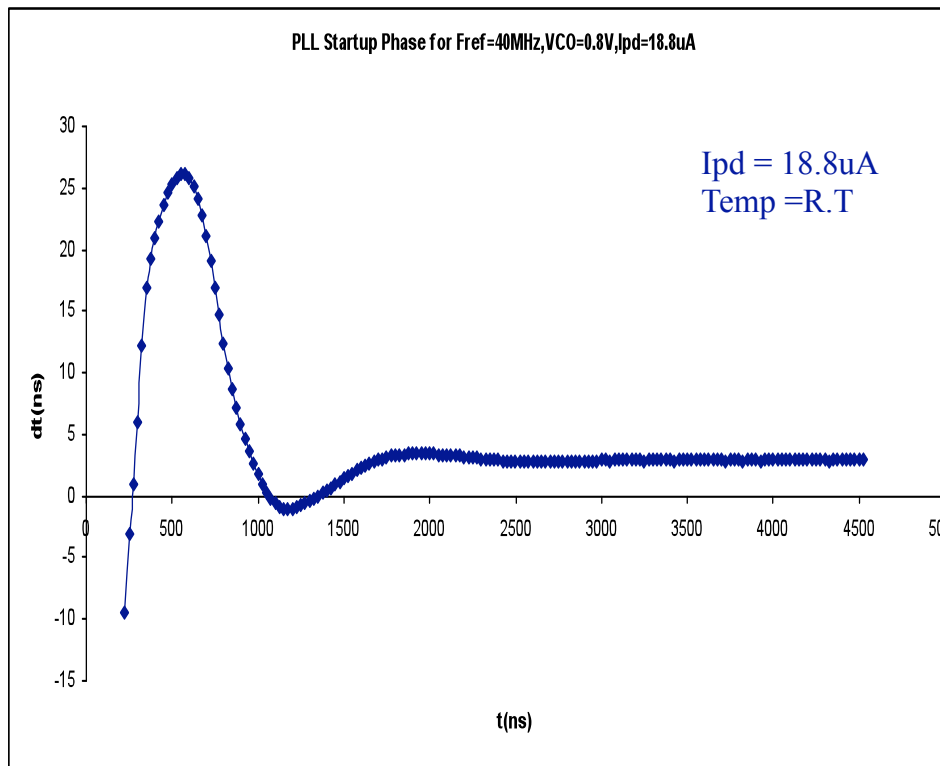Comparison Plots for temperature for different Ipd



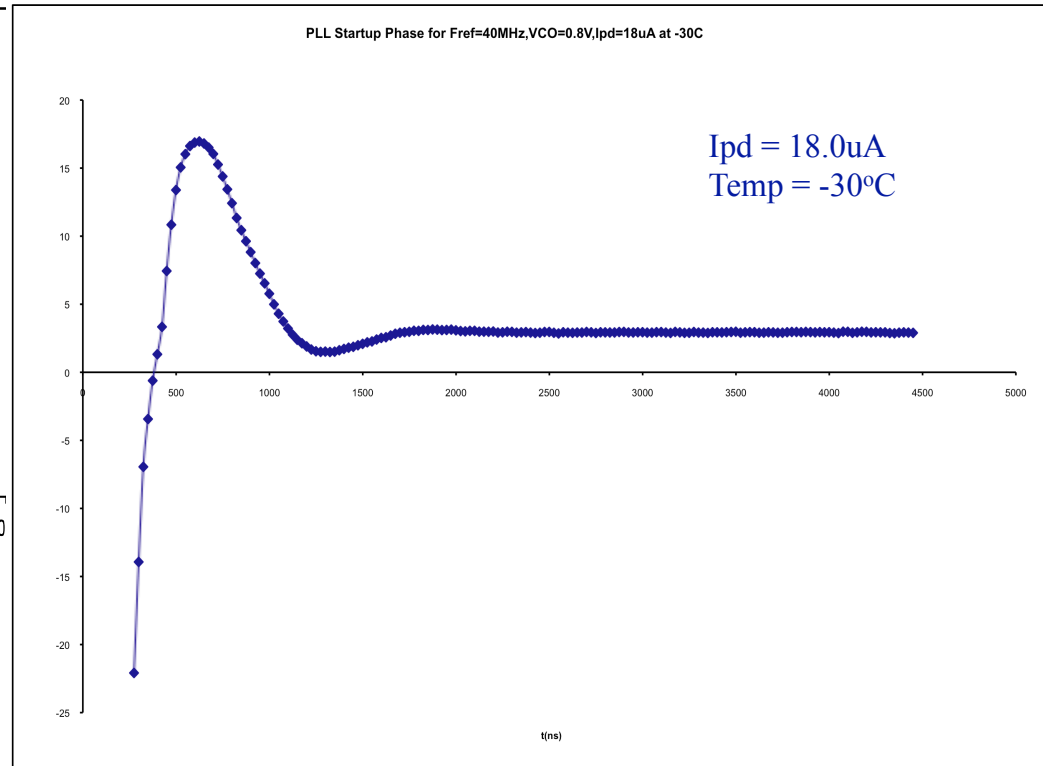1st overshoot 23ns at 600ns
1st undershoot -3.9ns at 1100ns
2nd overshoot 0.6ns at 1900ns
Damping = 38
Locking time ~3.5us



1st overshoot 14ns at 625ns
1st undershoot -1.4ns at 250ns
2nd overshoot 0.1ns at 1800ns
Damping = 140
Locking time ~2.5us


Results from PLL



Locking time:

Standard Fref = 40MHz and VCO = 0.8V

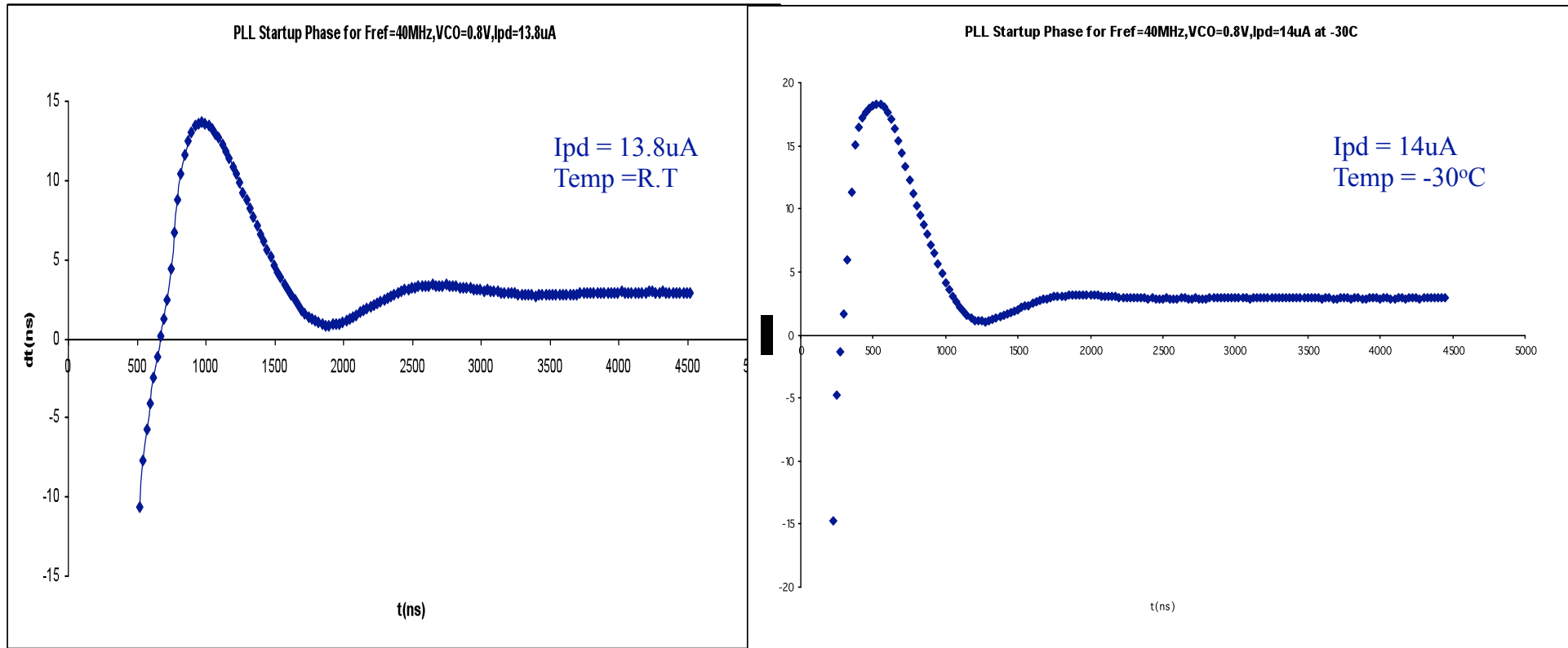Comparison Plots for temperature for different Ipd



1st overshoot 10ns at 945ns
1st undershoot -2.0ns at 1845ns
2nd overshoot 0.4ns at 2600ns
Damping = 25
Locking time ~3.7us

1st overshoot 15.5ns at 542ns
1st undershoot -1.8ns at 1200ns
2nd overshoot 0.2ns at 1800ns
Damping = 77.5
Locking time ~ 3.0us


Results from PLL




Locking time:

Standard $f_{ref} = 40\text{MHz}$ and $V_{CO} = 0.8\text{V}$

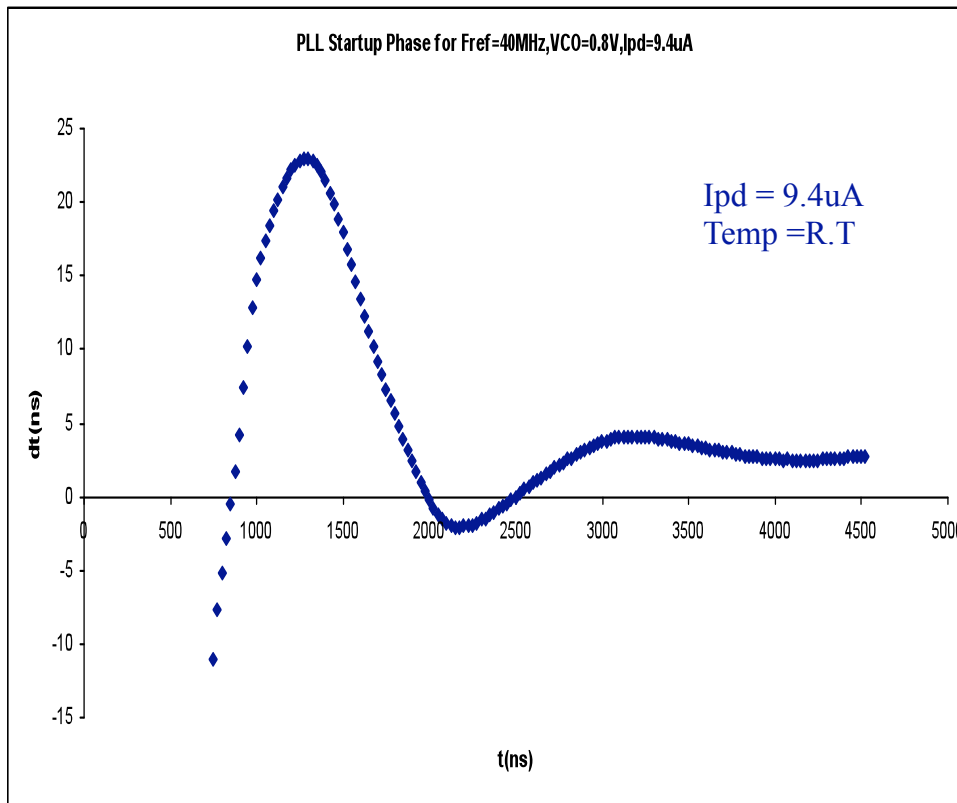Comparison Plots for temperature for different I_{pd}



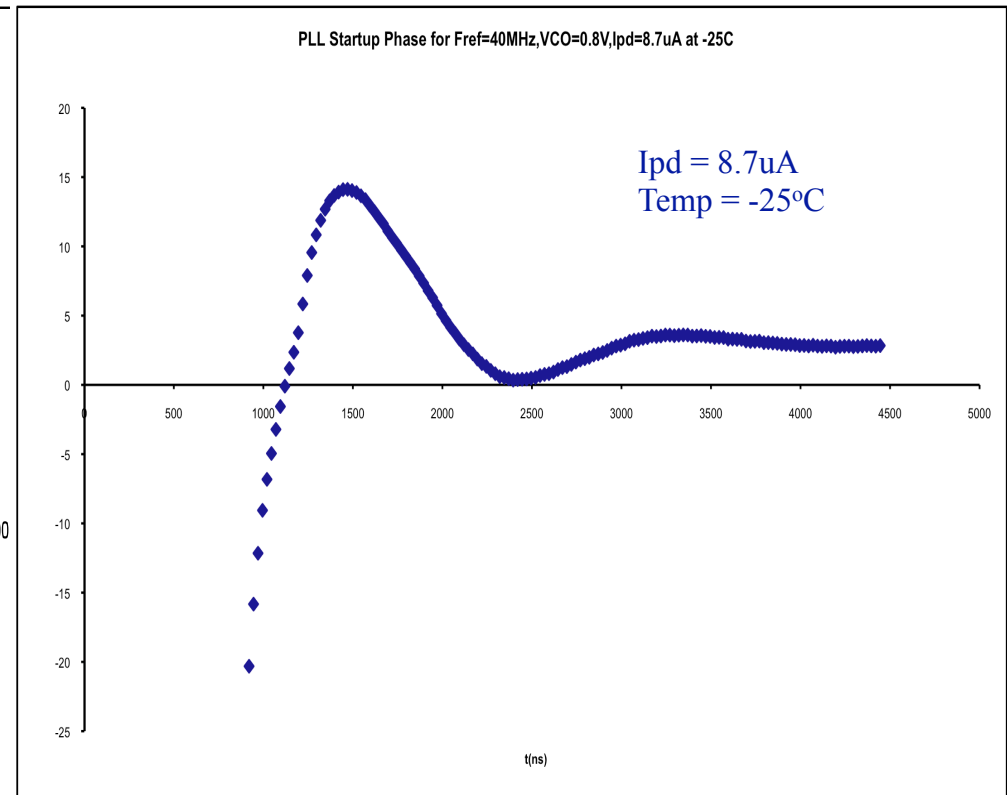1st overshoot 20ns at 1273ns
1st undershoot -4.4ns at 2200ns
2nd overshoot 1.6ns at 3200ns
2nd undershoot 0.1ns at 4200ns
Damping = 12.8
Locking time >4.5us



1st overshoot 11.3ns at 1445ns
1st undershoot -2.4ns at 2420ns
2nd overshoot 0.7ns at 3220ns
Damping = 16
Locking time >4.5us

Results from SIMetrix Simulation



For the study of K parameter for VCO using relation $V_{out} = K \cdot V_{in}$ for the test

Using the Simetrix simulation



$I_{ref} = f(\text{phase difference between two input signals})$

$K_{pd} = 0.89 \text{ uA/rad}$ for $I_{pd} = 5.6 \text{ uA}$

$K_{pd} = 1.5 \text{ uA/rad}$ for $I_{pd} = 9.4 \text{ uA}$

$K_{pd} = 2.2 \text{ uA/rad}$ for $I_{pd} = 13.8 \text{ uA}$

 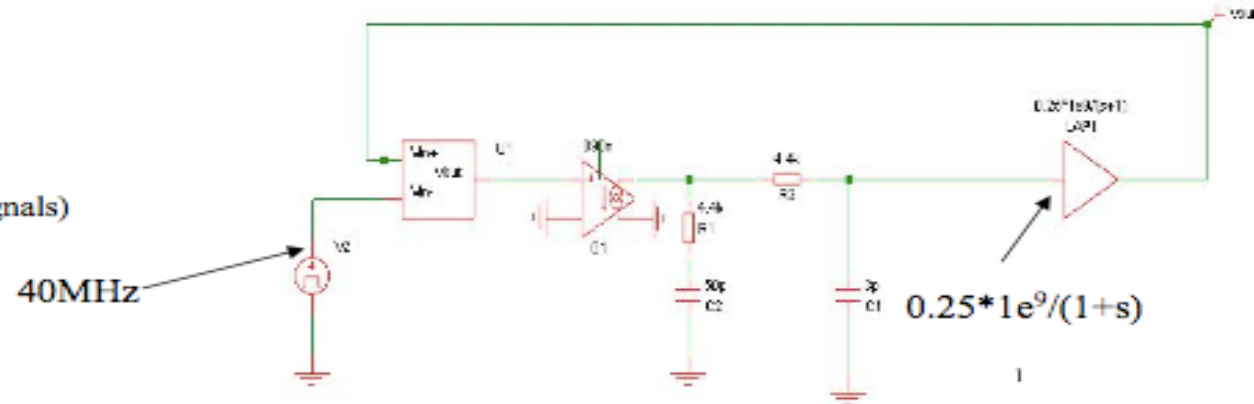$K_{pd} = 3 \text{ uA/rad}$ for $I_{pd} = 18.8 \text{ uA}$



Study of ADC



In Upgrade ROC




Working Principle : Successive approximation

SAR initialized so that MSB =1 → DAC which supplies the analog \sim of this digital code ($V_{ref}/2$).

Comparator to compare with V_{in} .

If analog voltage $> V_{in}$, the comparator leads SAR to reset this bit and set the next bit to a digital 1.

 
This binary search continues until every bit in SAR is tested. The resulting code is the digital approximation of V_{in} and is finally output by the DAC at EOC.



Study of ADC





4 bit ADC

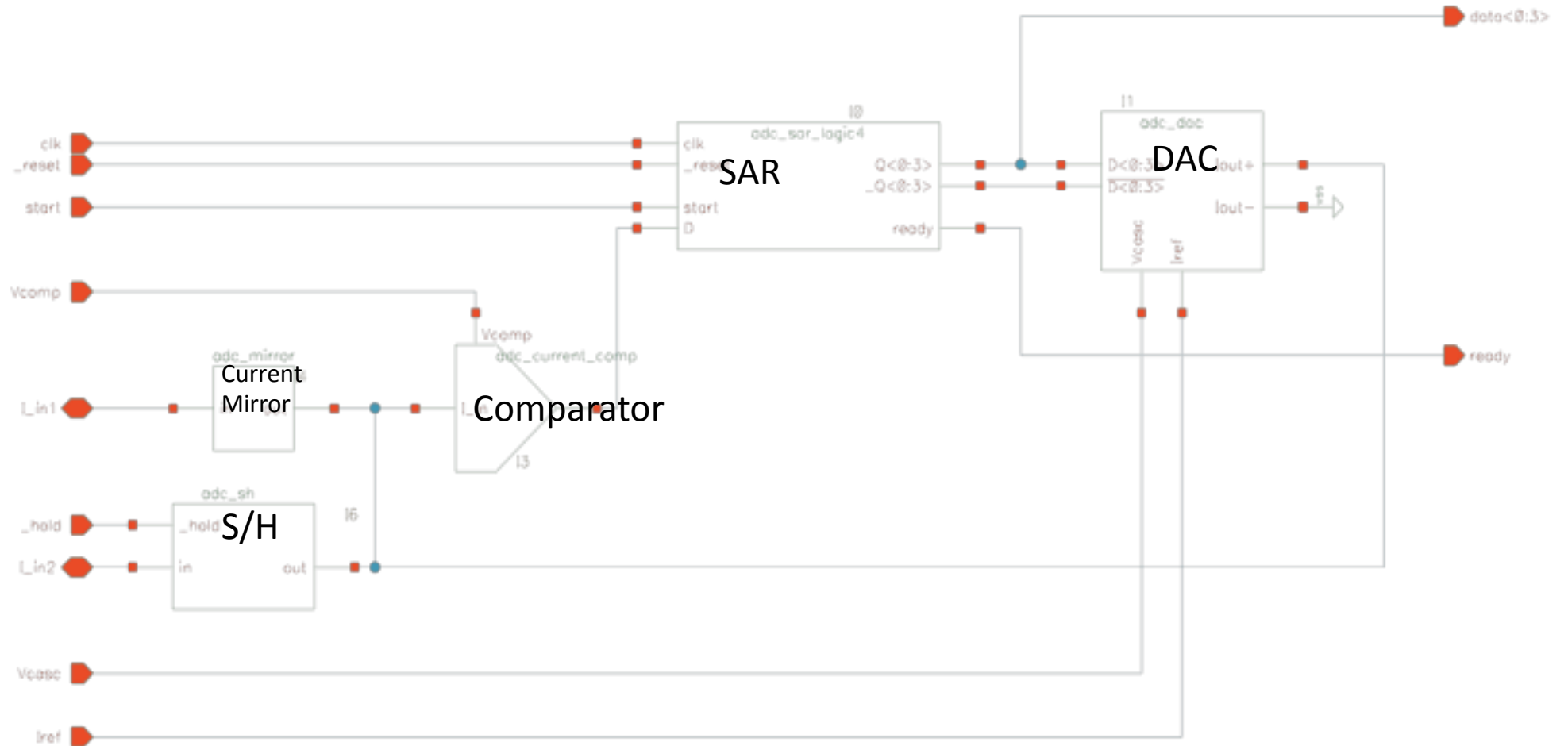




Study of ADC



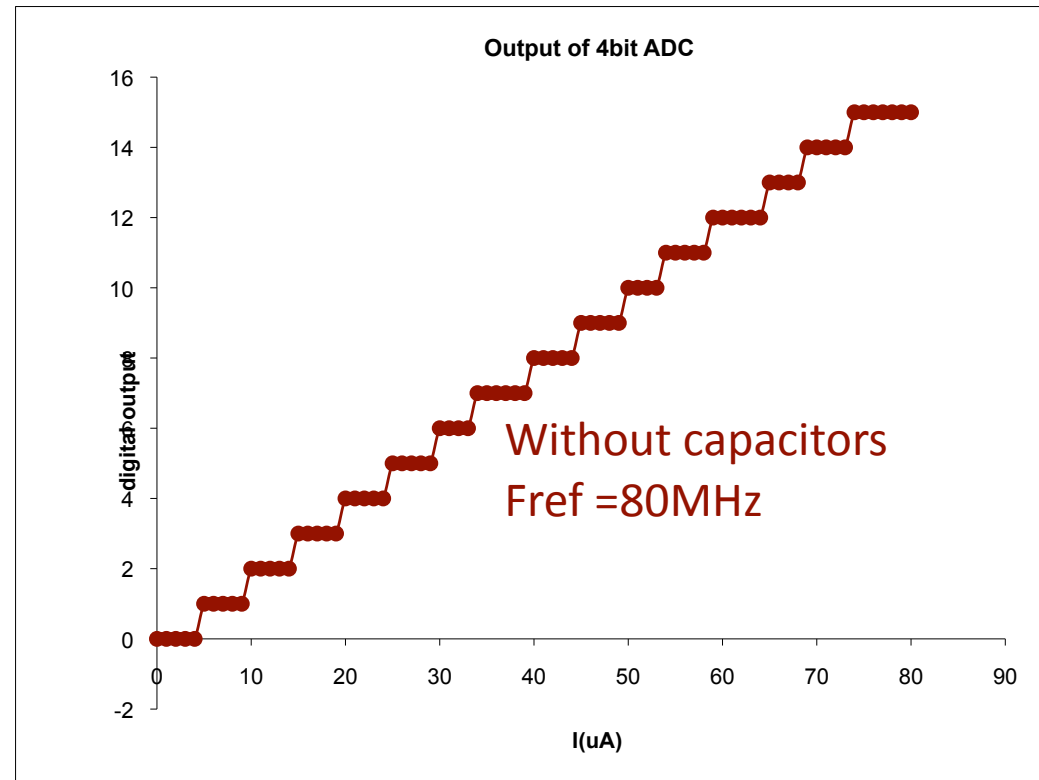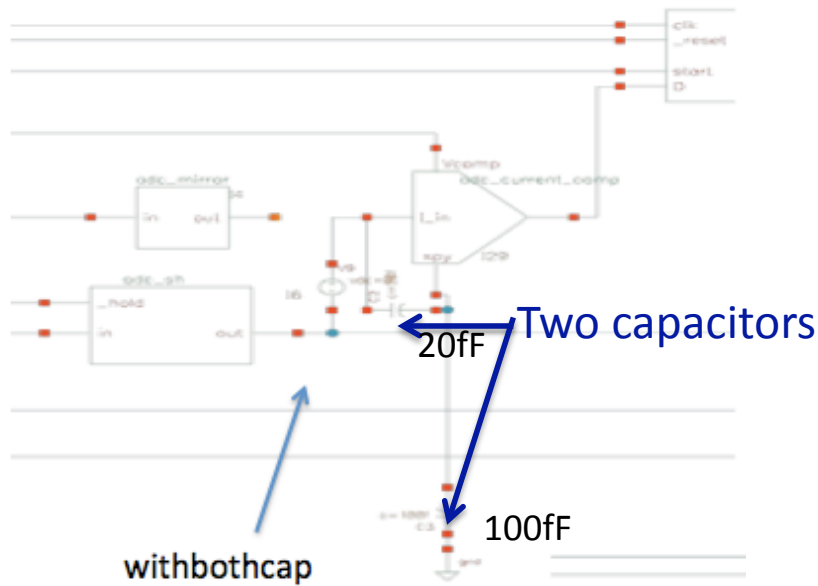Study of unequal step with testing the 4 bit ADC with the help of Simulation



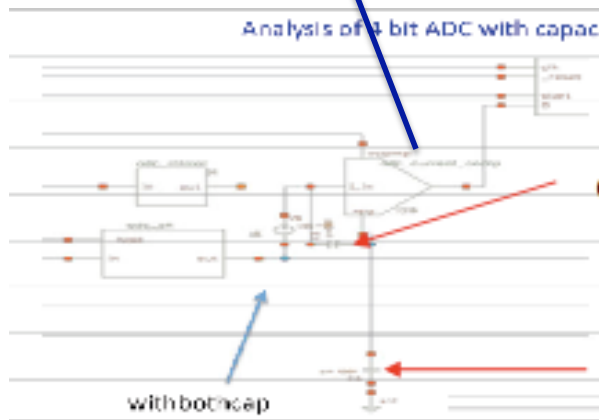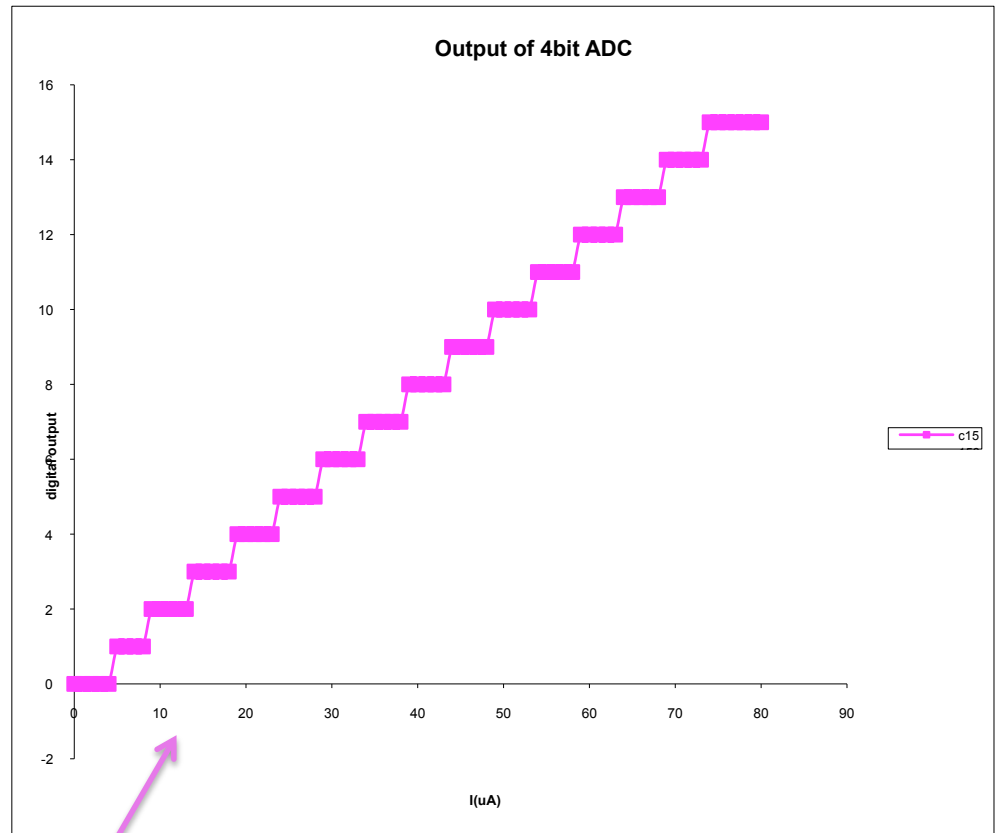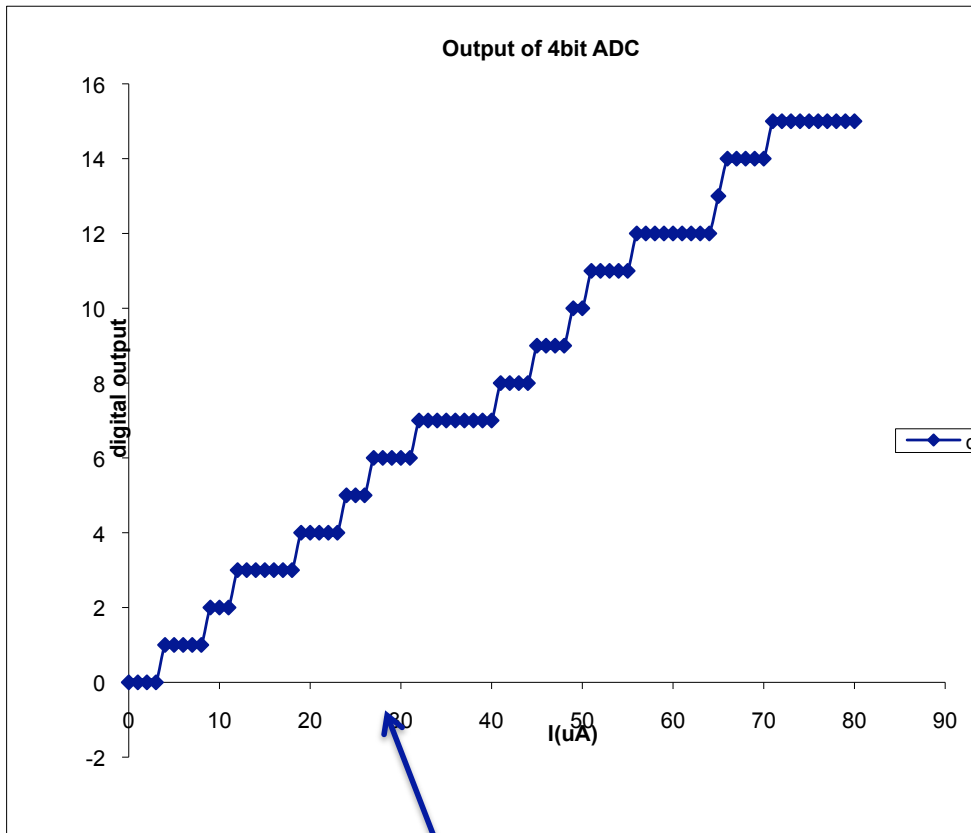Analysis of 4bit ADC with capacitor across the comparator



C1=15fF , 15fF



C2=50fF, 150fF

Study of Sample and Hold Circuit



Study of sample and Hold circuit

Sample and Hold circuit

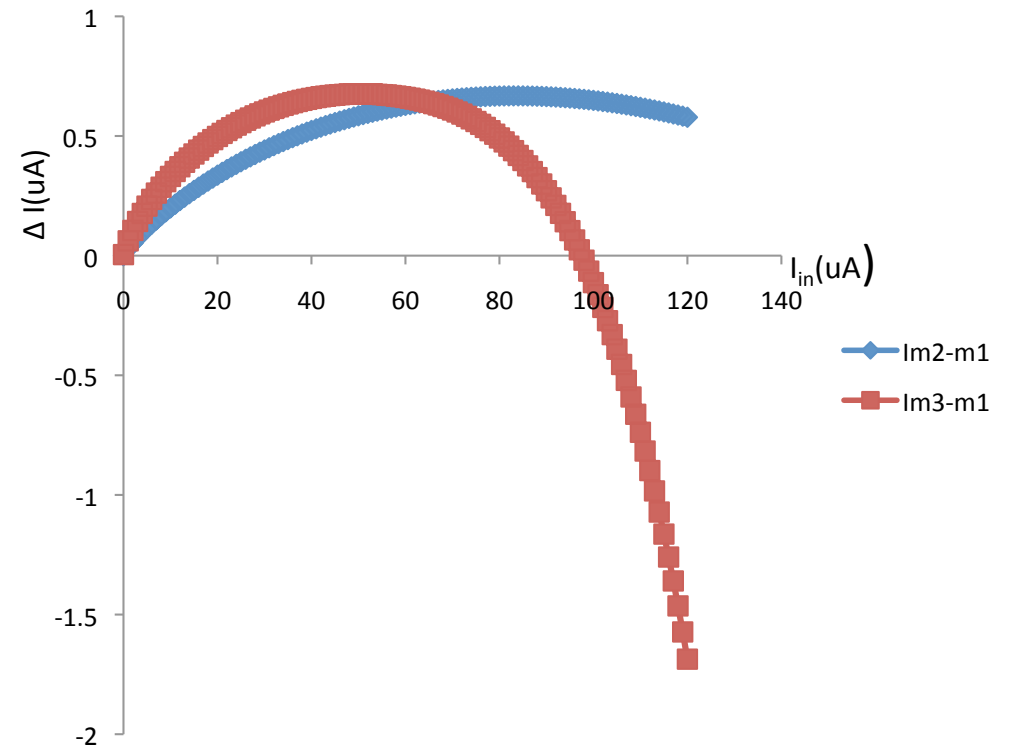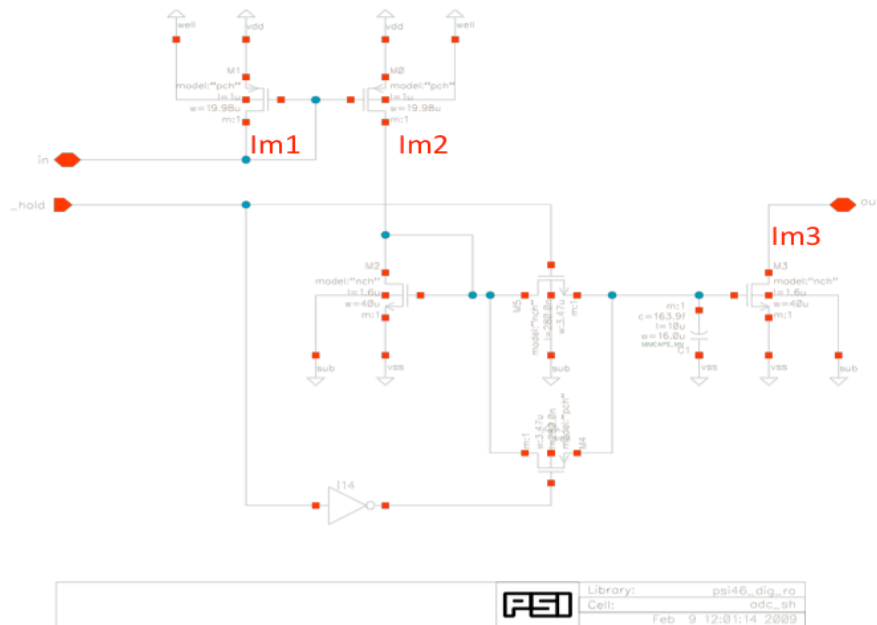

Next Step




For ADC, need to take some more measurements by connecting microprobe to the spy pad to understand the unequal step.

For PLL, calculate locking time using irradiated chip.

Back up Slide



 Test Set up for calculation of Locking time at low temperature.



1,1,1,2-Tetrafluoroethane