

# Study of Frequency Divider PLL

Shruti Shrestha  
KSU

September 18, 2009



## Outlines:

Working principle of PLL

Importance of PLL in ROC


Behavior of PLL at room and low temperature

Simulation Results of ADC




# Working Principle of PLL

## Circuit for PLL

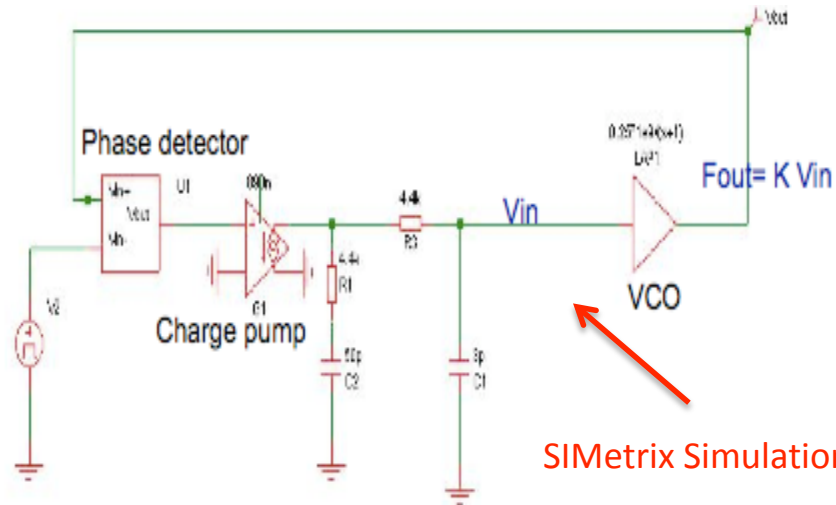


SIMatrix Simulation

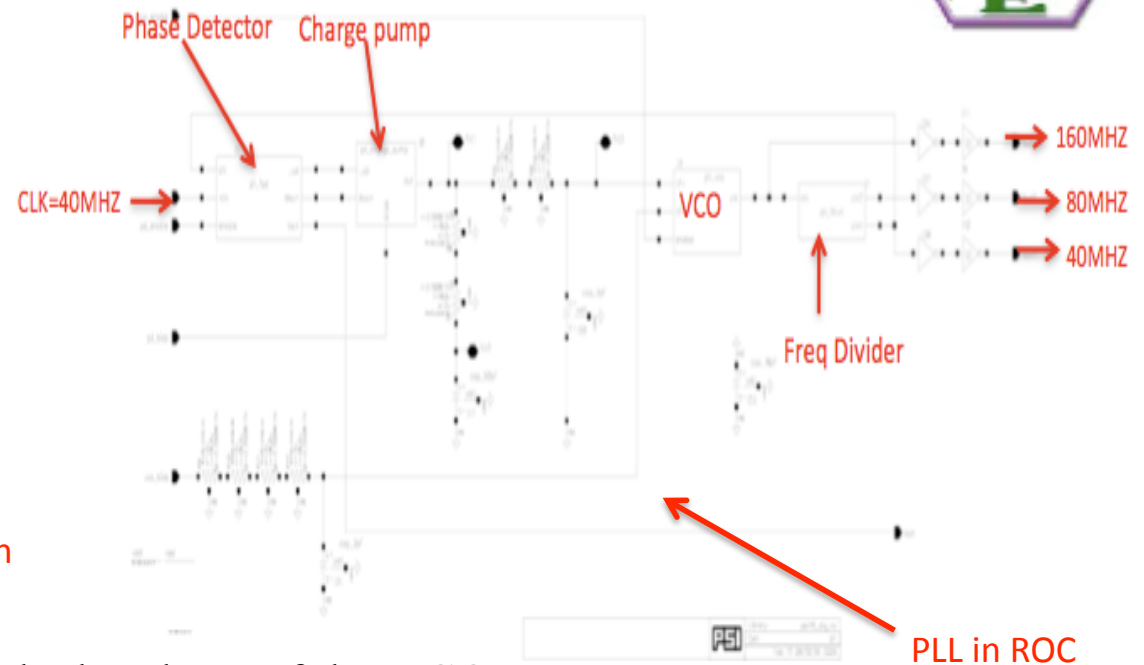

- Feed back Control system that controls the phase of the VCO.
- Input signal applied one input of P.D, the other input is connected to the output of a divide by N counter.
- The Output of the P.D is phase difference between the two inputs.
- This signal is applied to the loop filter with the help of charge pump. The filter signal controls the VCO . (if  $f_{vco} > f_{clk}$ , the capacitor to discharges to decrease input voltage to the VCO since  $f_{out} = K V_{in}$ )




# Components of PLL

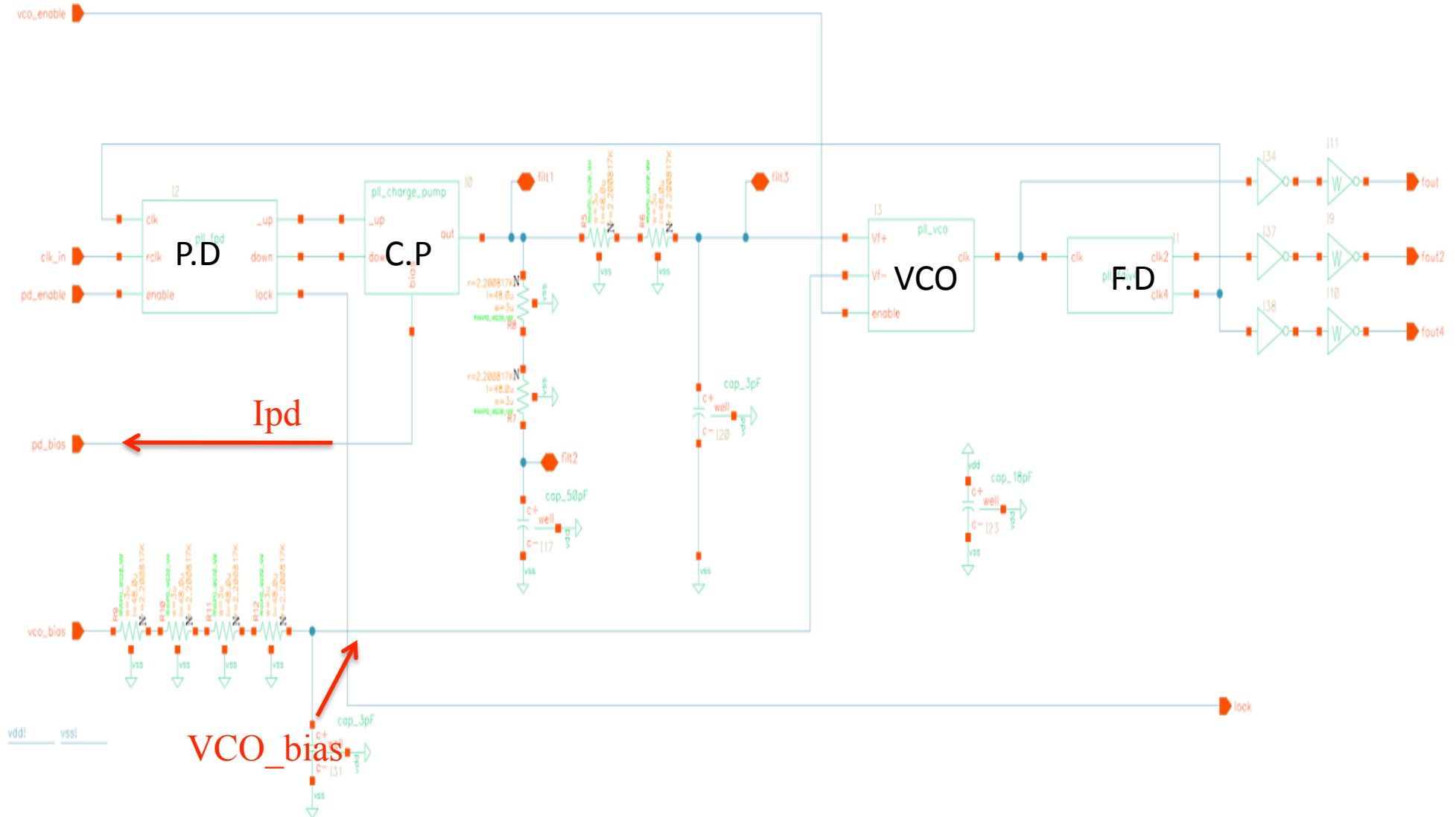



# Use of PLL in ROC


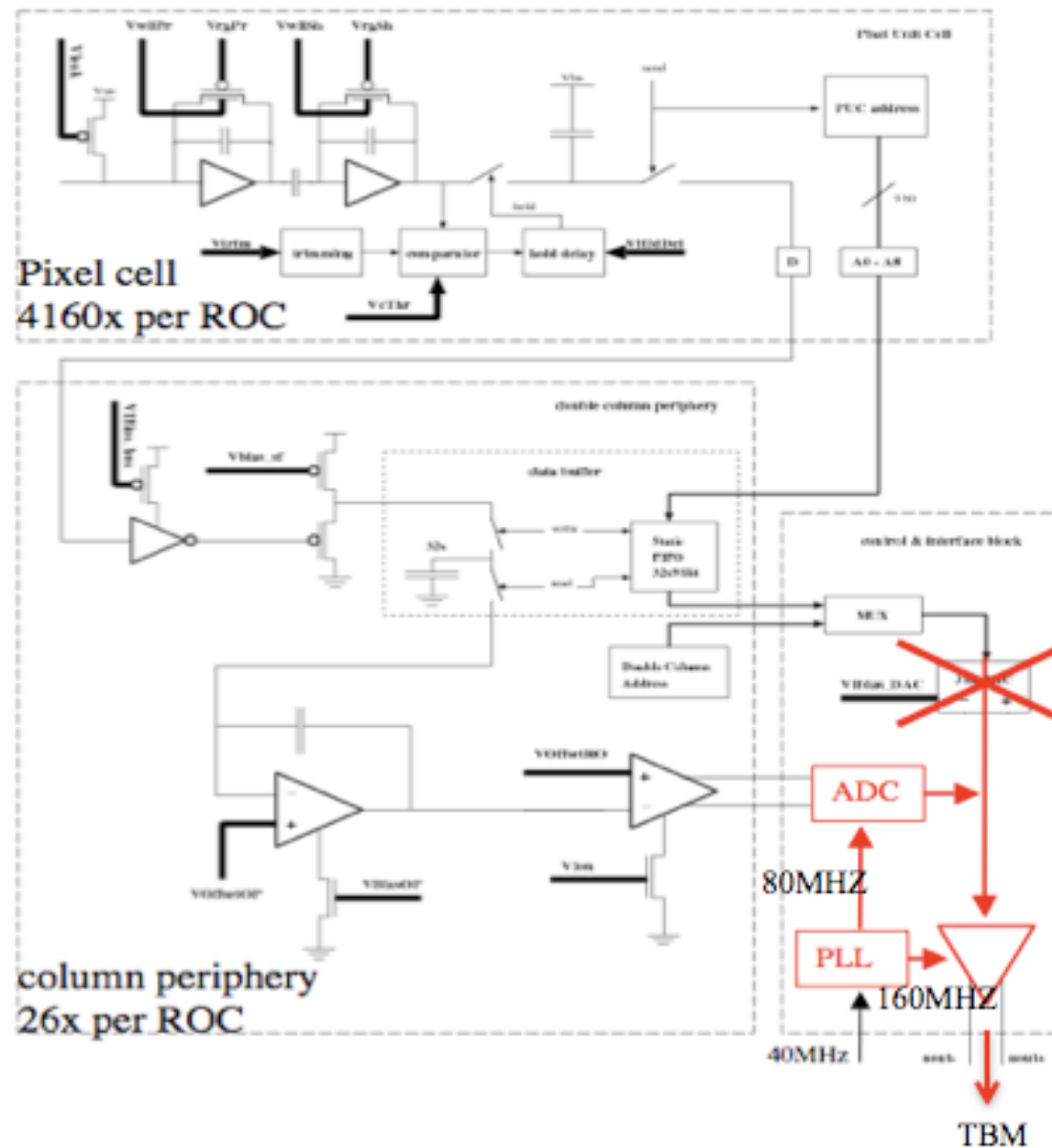


# Layout of PLL



Circuit for  
Input and Outputs to be taken

Test Setup for periphery Board

 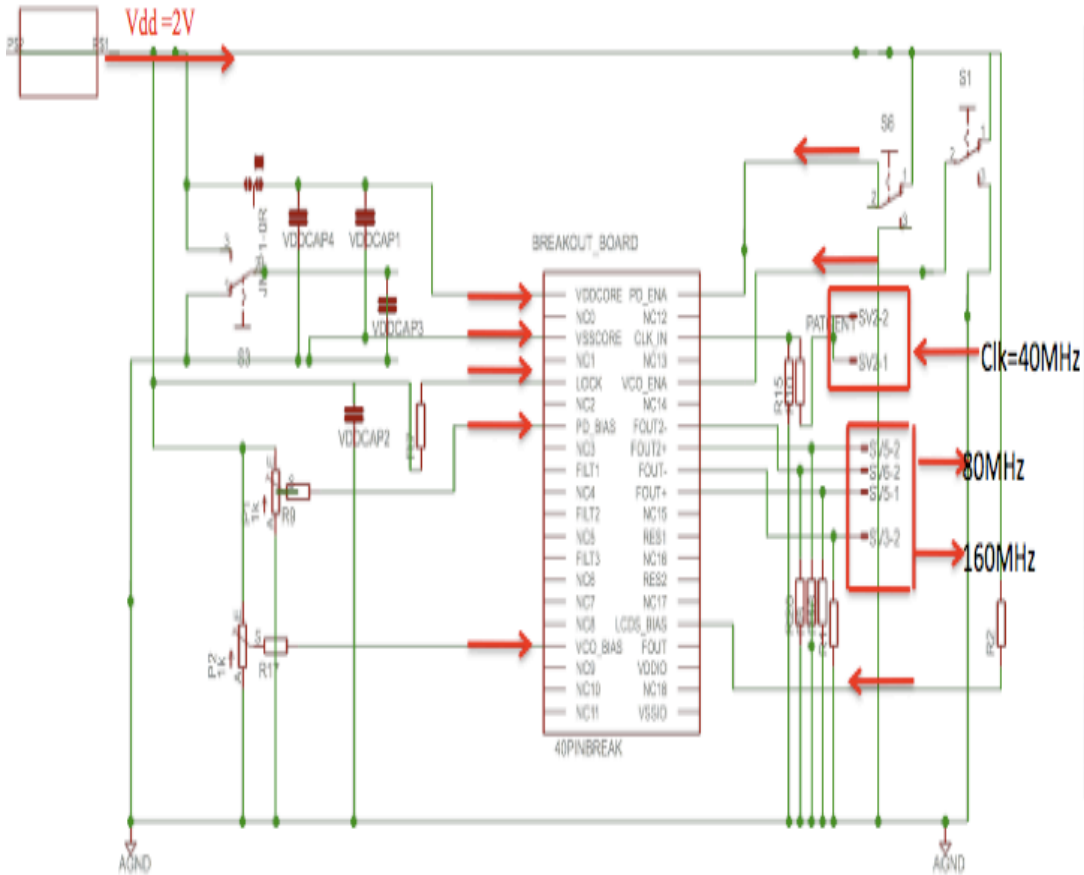




## Results from PLL

### Power Consumption



Ref Frequency(40MHZ)	I(mA)	Power Consumption (mW)
Without 50Ω resistances	0.773	1.546
Without 50Ω and 8.2KΩ	0.728	1.456
With all 50Ω and 8.2KΩ	4.783	9.566

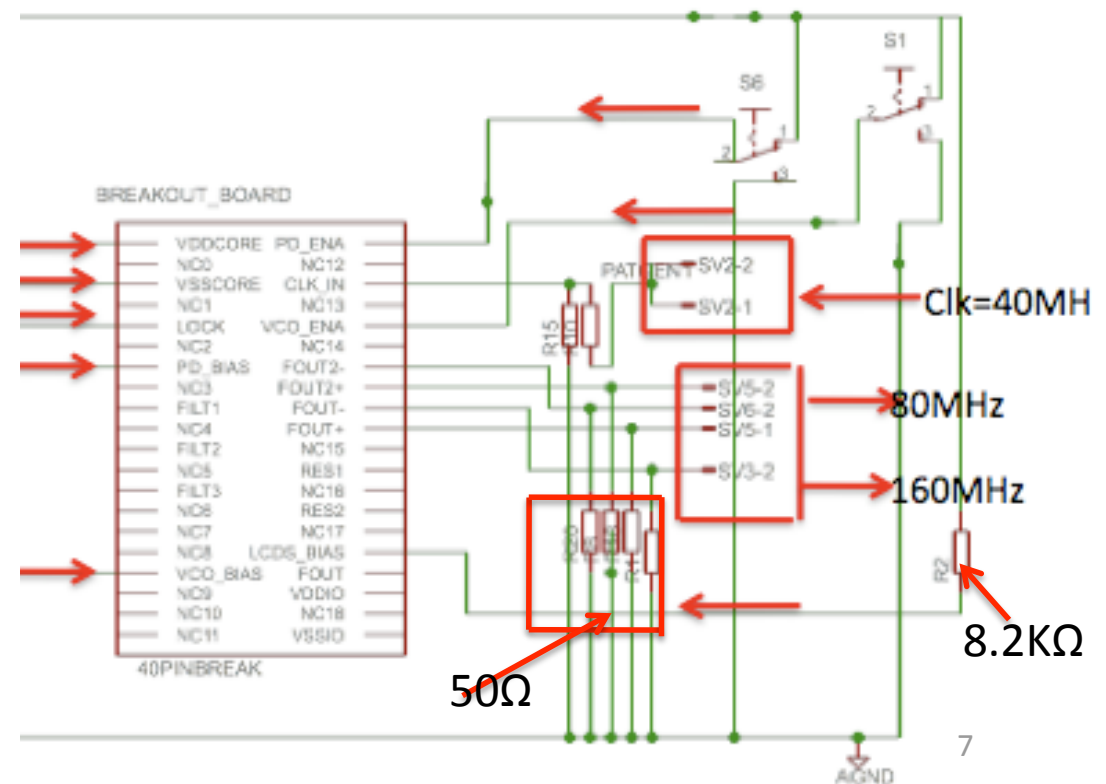

# Calculation of Locking time PLL



**Locking time:**

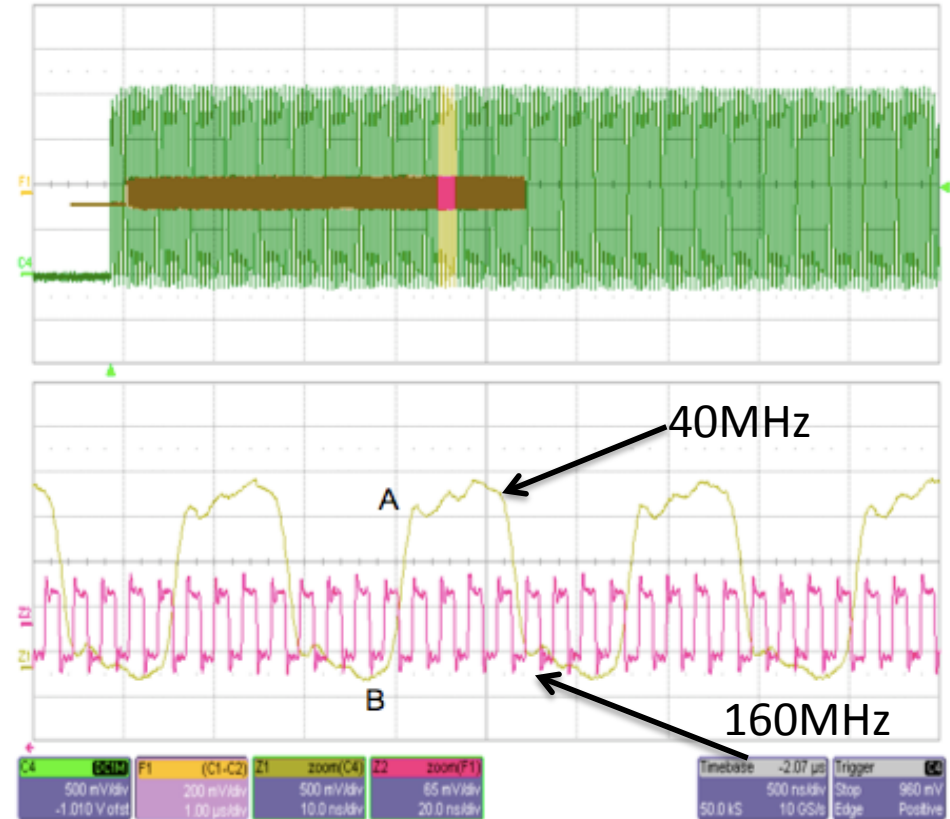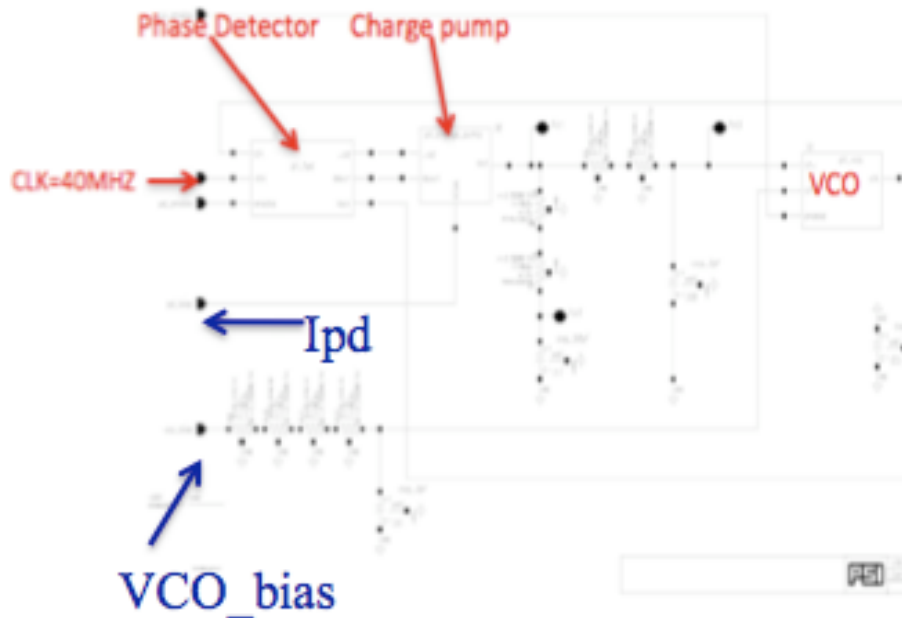

Variation parameters taken for calculating locking time are Ipd and VCO\_bias




# Results from PLL



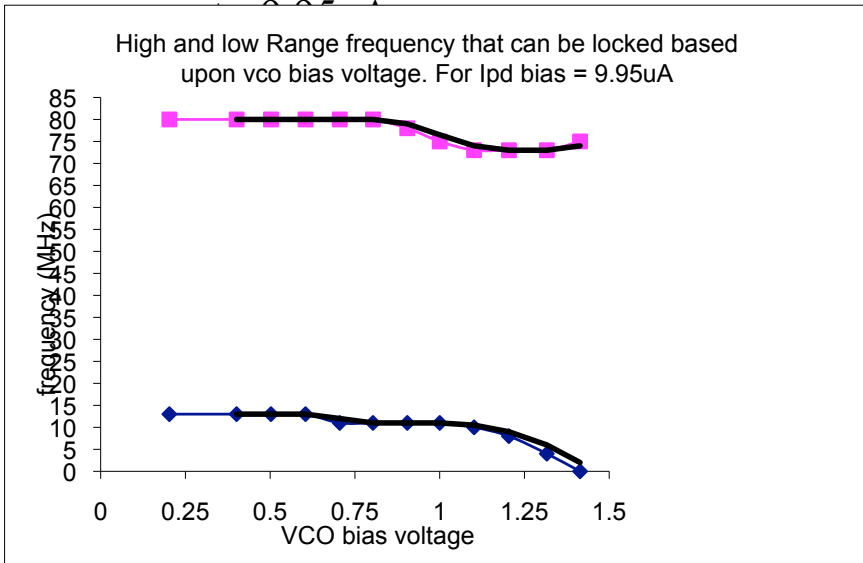
## Locking time

Study of Range of Frequency that can be locked based upon VCO bias voltage for I<sub>pd</sub> bias



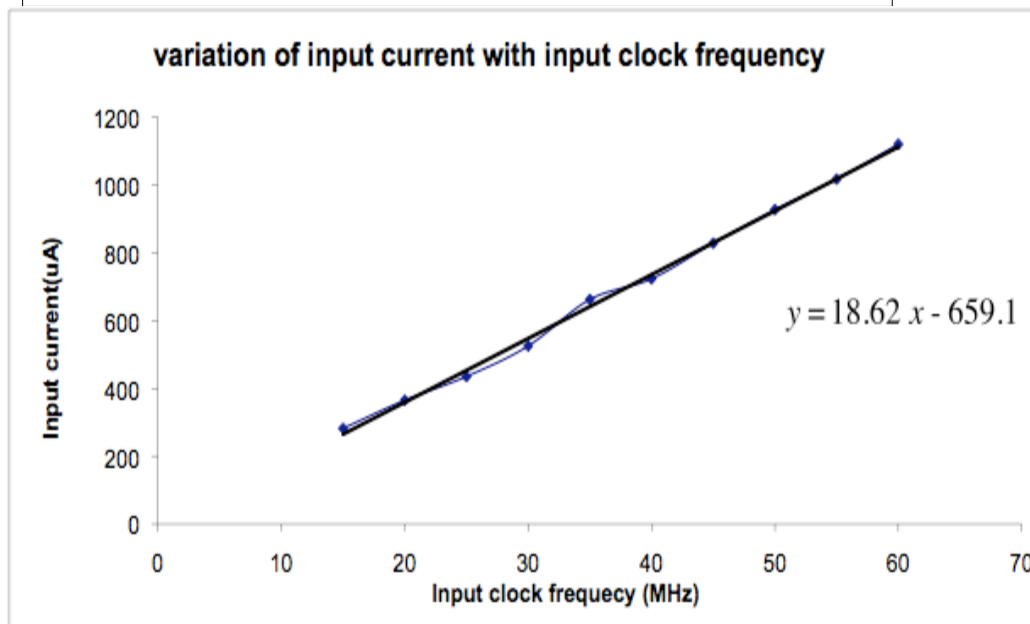From 80MHz output, PLL locks from 10MHz - 75MHz Reference Input frequency.



When F<sub>ref</sub> = 0 , I = -659uA  
Observed when F<sub>ref</sub> = 0, I = 134uA


# Results from PLL




## Locking time:

Standard Fref = 40MHz and VCO = 0.8V
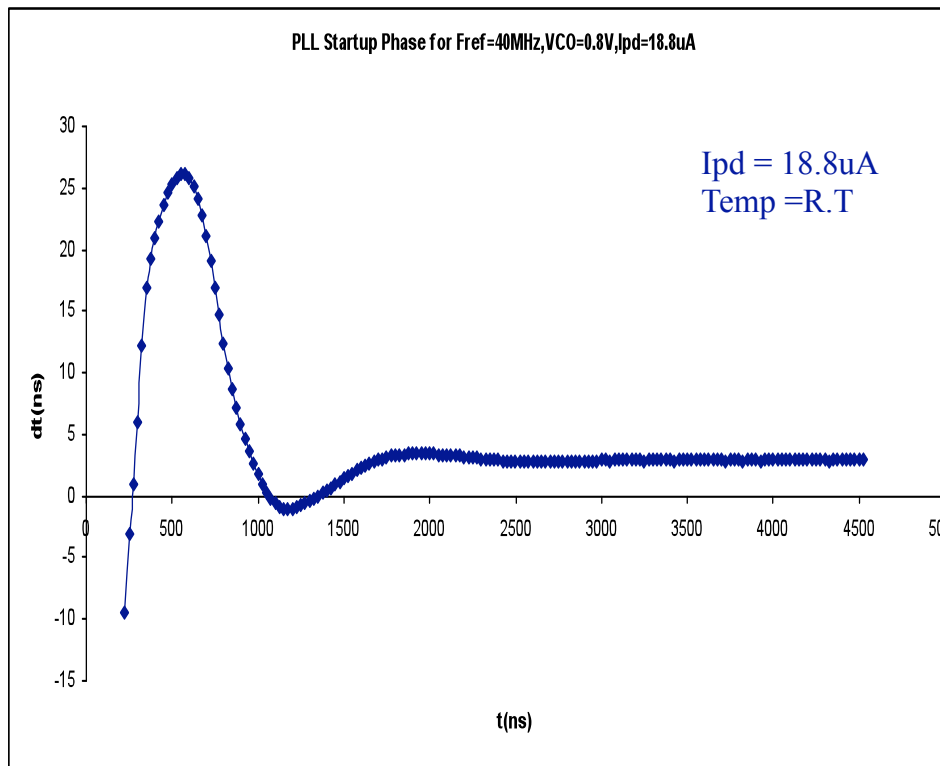
## Comparison Plots for temperature for different Ipd



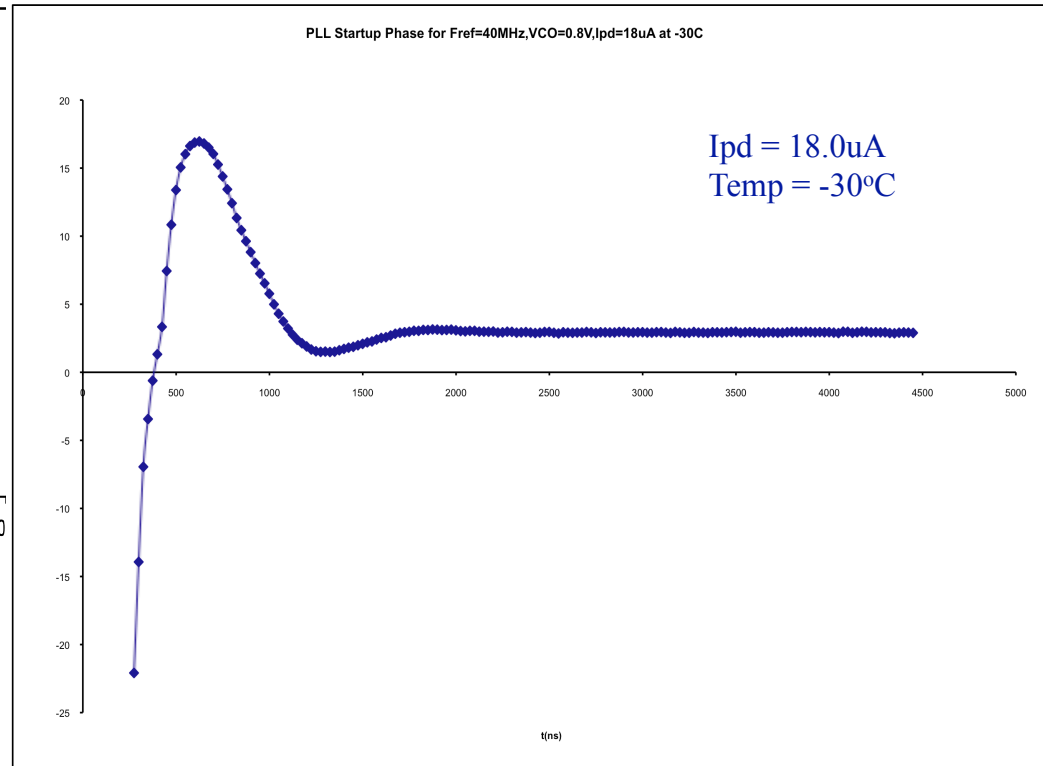1st overshoot 23ns at 600ns  
1st undershoot -3.9ns at 1100ns  
2nd overshoot 0.6ns at 1900ns  
Damping = 38  
Locking time ~3.5us



1st overshoot 14ns at 625ns  
1st undershoot -1.4ns at 250ns  
2nd overshoot 0.1ns at 1800ns  
Damping = 140  
Locking time ~2.5us


# Results from PLL



## Locking time:

Standard Fref = 40MHz and VCO = 0.8V
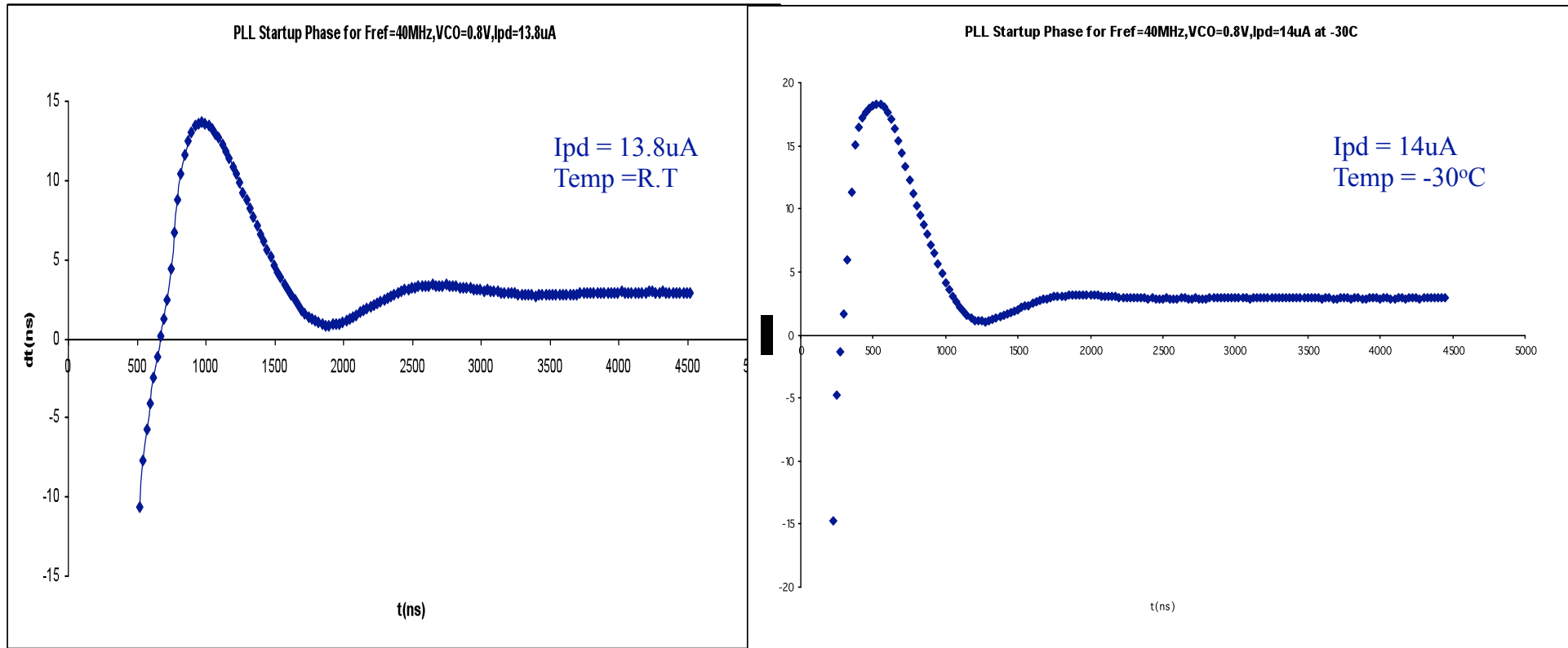
## Comparison Plots for temperature for different Ipd



1st overshoot 10ns at 945ns  
1st undershoot -2.0ns at 1845ns  
2nd overshoot 0.4ns at 2600ns  
Damping = 25  
Locking time ~3.7us

1st overshoot 15.5ns at 542ns  
1st undershoot -1.8ns at 1200ns  
2nd overshoot 0.2ns at 1800ns  
Damping = 77.5  
Locking time ~ 3.0us


# Results from PLL




## Locking time:

Standard Fref = 40MHz and VCO = 0.8V
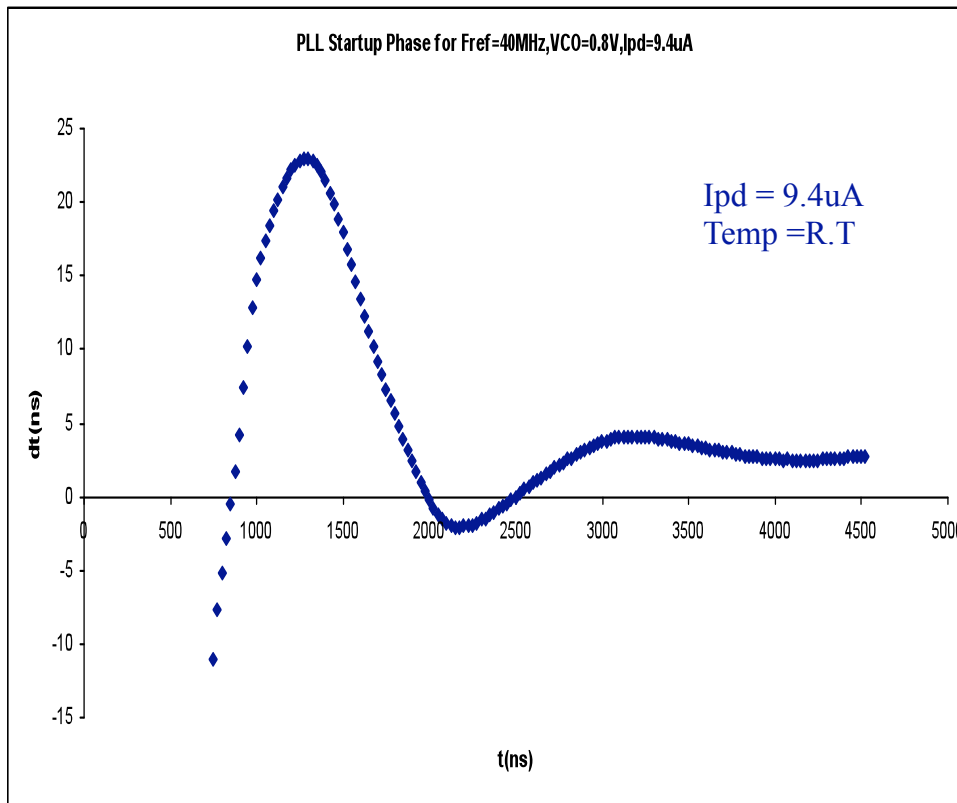
## Comparison Plots for temperature for different Ipd



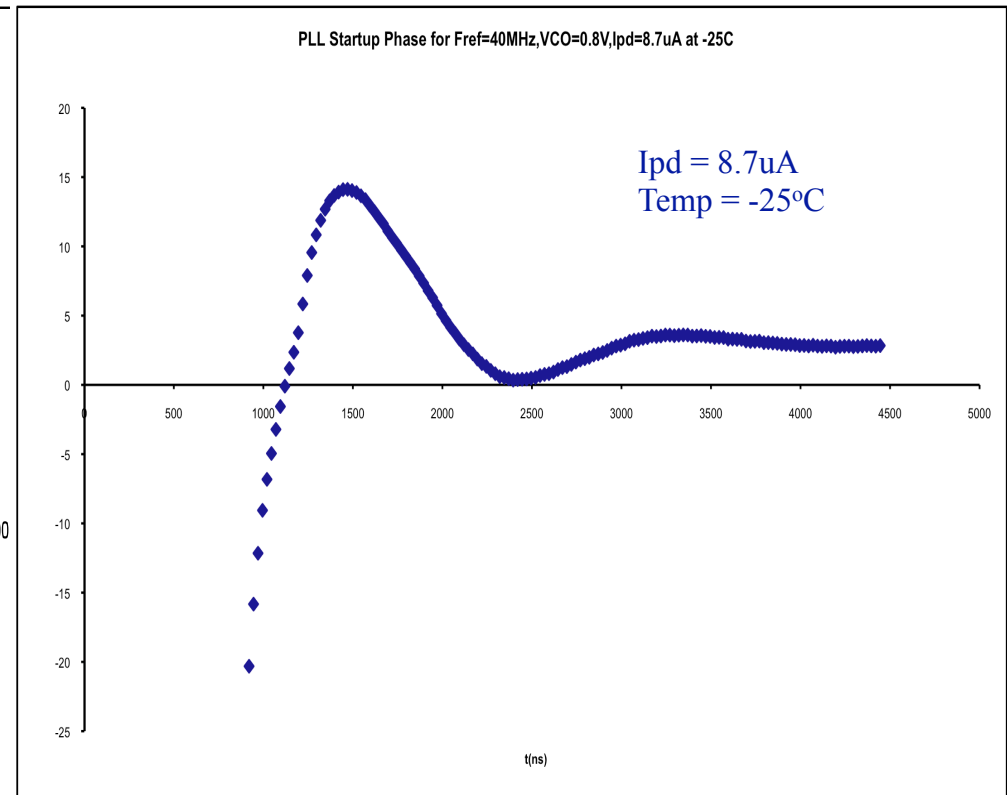1st overshoot 20ns at 1273ns  
1st undershoot -4.4ns at 2200ns  
2nd overshoot 1.6ns at 3200ns  
2nd undershoot 0.1ns at 4200ns  
Damping = 12.8  
Locking time >4.5us



1st overshoot 11.3ns at 1445ns  
1st undershoot -2.4ns at 2420ns  
2nd overshoot 0.7ns at 3220ns  
Damping = 16  
Locking time >4.5us

# Results from SIMetrix Simulation



For the study of K parameter for VCO using relation  $V_{out} = K.V_{in}$  for the test

Using the Simetrix simulation



$I_{ref} = f(\text{phase difference between two input signals})$

$K_{pd} = 0.89 \text{ uA/rad}$  for  $I_{pd} = 5.6 \text{ uA}$

$K_{pd} = 1.5 \text{ uA/rad}$  for  $I_{pd} = 9.4 \text{ uA}$

$K_{pd} = 2.2 \text{ uA/rad}$  for  $I_{pd} = 13.8 \text{ uA}$

 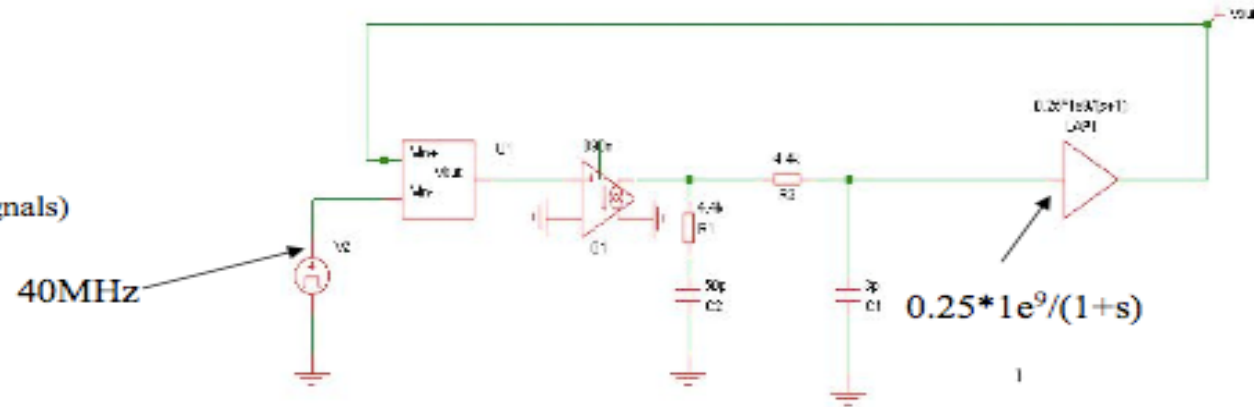$K_{pd} = 3 \text{ uA/rad}$  for  $I_{pd} = 18.8 \text{ uA}$



# Study of ADC



In Upgrade ROC




## Working Principle : Successive approximation

SAR initialized so that MSB =1 → DAC which supplies the analog  $\sim$  of this digital code ( $V_{ref}/2$ ).

Comparator to compare with  $V_{in}$ .

If analog voltage  $> V_{in}$ , the comparator leads SAR to reset this bit and set the next bit to a digital 1.

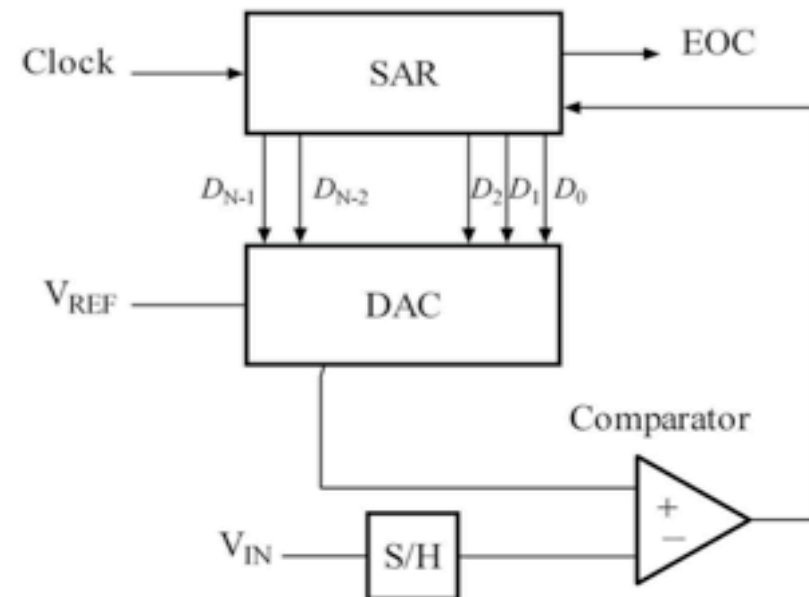
This binary search continues until every bit in SAR is tested. The resulting code is the digital approximation of  $V_{in}$  and is finally output by the DAC at EOC.



# Study of ADC





## 4 bit ADC

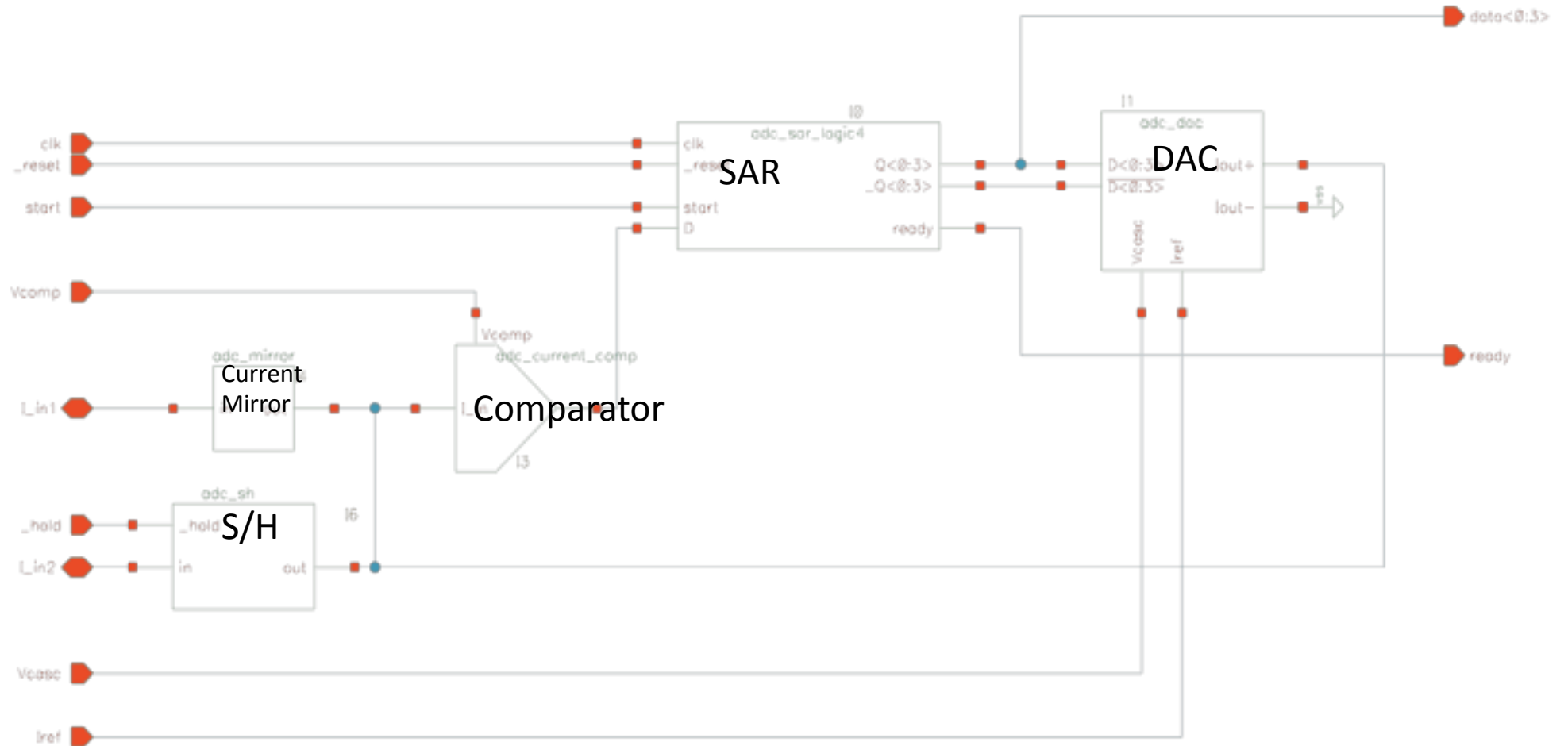

# Study of ADC


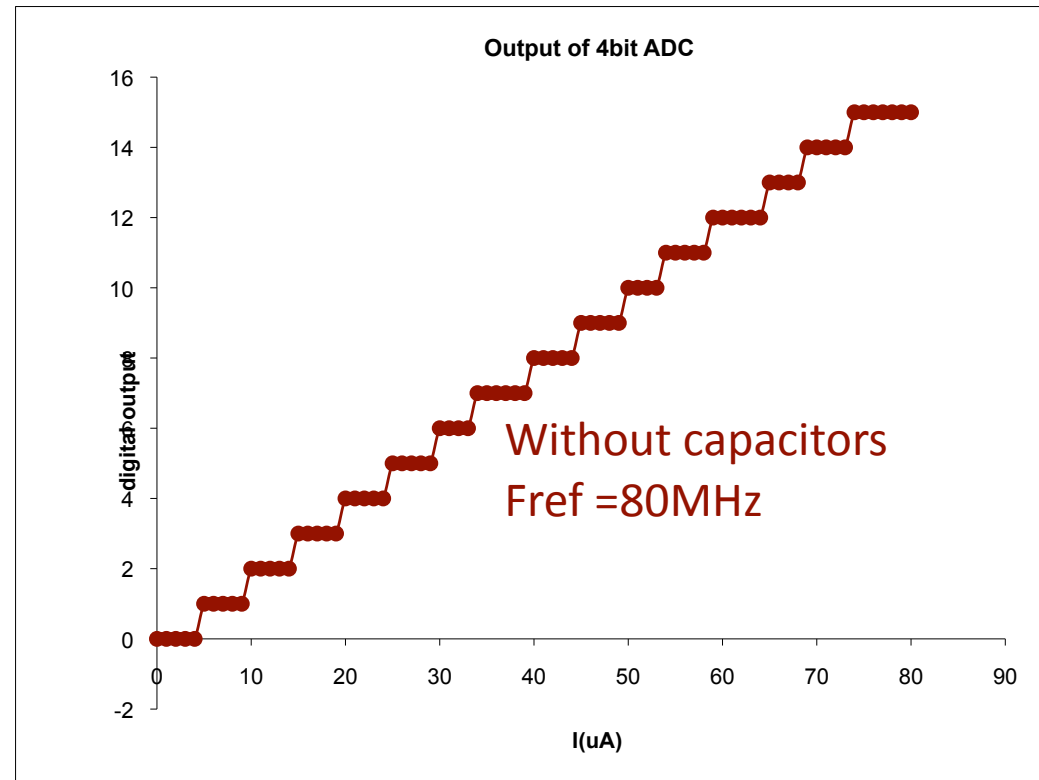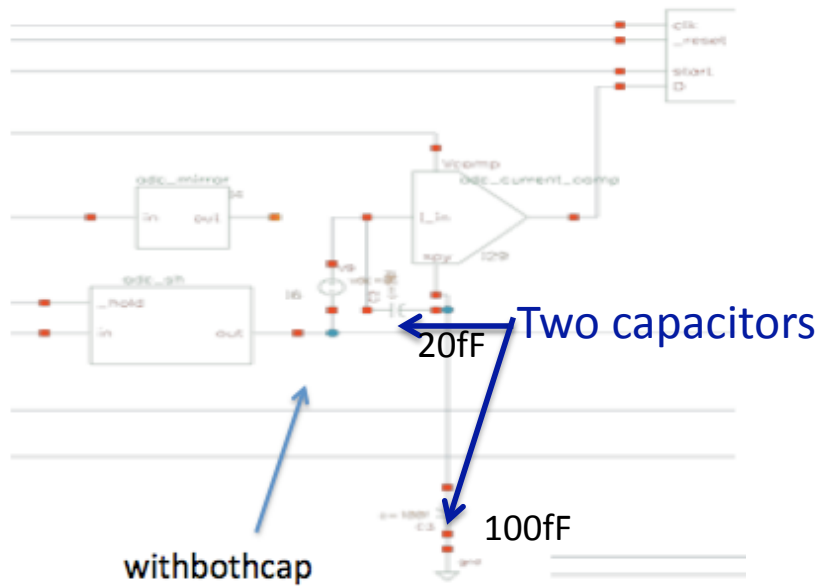
## Study of unequal step with testing the 4 bit ADC with the help of Simulation







## Next Step




For ADC, need to take some more measurements by connecting microprobe to the spy pad to understand the unequal step.

For PLL, calculate locking time using irradiated chip.
 
# Back up Slide



Test Set up for calculation of Locking time at low temperature.



1,1,1,2-Tetrafluoroethane