

Low noise preamplifier


**Upgrade of the front end electronics of the
LHCb calorimeter**

Calorimeter upgrade meeting – LAL /Orsay – December 17th 2009

- I. Introduction
- II. LAPAS chip for ATLAR LAr calorimeter
- III. Voltage output vs current output
- IV. Current output / mixed feedback
- V. Current output / current feedback
- VI. Discussion

I. Introduction: requirements

- Requirements as agreed during last year (PM gain 1/5):

	Value	Comments
Energy range	0-10 GeV/c (ECAL) Transverse energy	1-3 Kphe / GeV Total energy
Calibration	4 fC / 2.5 MeV / ADC cnt	4 fC input of FE card: assuming 25 Ω clipping at PMT base 12 fC / ADC count if no clipping
Dynamic range	4096-256=3840 cnts :12 bit	Enough? New physic req.? Pedestal variation? Should be enough
Noise	≈ 1 ADC cnt or ENC < 5 -6 fC	< 0.7 nV/ $\sqrt{\text{Hz}}$ 
Termination	50 \pm 5 Ω	Passive vs. active
AC coupling	Needed	Low freq. (pick-up) noise
Baseline shift Prevention	Dynamic pedestal subtraction (also needed for LF pick-up)	How to compute baseline? Number of samples needed?
Max. peak current	4-5 mA over 25 Ω 1.5 mA at FE input if clipping	50 pC in charge
Spill-over correction	Clipping	Residue level: 2 % \pm 1 % ?
Spill-over noise	<< ADC cnt	Relevant after clipping?
Linearity	< 1%	
Crosstalk	< 0.5 %	
Timing	Individual (per channel)	PMT dependent

See talk about noise in June's meeting:

<http://indico.cern.ch/materialDisplay.py?contribId=1&sessionId=0&materialId=slides&confId=59892>

I. Introduction: active line termination

- Electronically cooled termination required:

- 50 Ohm noise is too high
- e. g. ATLAS LAr (discrete component)

- Common gate with double voltage feedback

- Inner loop to reduce input impedance preserving linearity and with low noise
- Outer loop to control the input impedance accurately

$$Z_i \approx \frac{1/g_{m1}}{G} + R_{C1} \frac{R_1}{R_1 + R_2}$$


- Transimpedance gain is given by R_{C1}

- Noise is $< 0.5 \text{ nV}/\sqrt{\text{Hz}}$

- Small value for R_1 and R_2
- Large g_{m1} and g_{m2}

- Need ASIC for LHCb

- 32 ch / board: room and complexity

 

II. LAPAS chip for ATLAS LAr upgrade


- TWEPP 09

LAPAS: A SiGe Front End Prototype for the Upgraded ATLAS LAr Calorimeter

Mitch Newcomer

On Behalf of the ATLAS LAr Calorimeter Group*

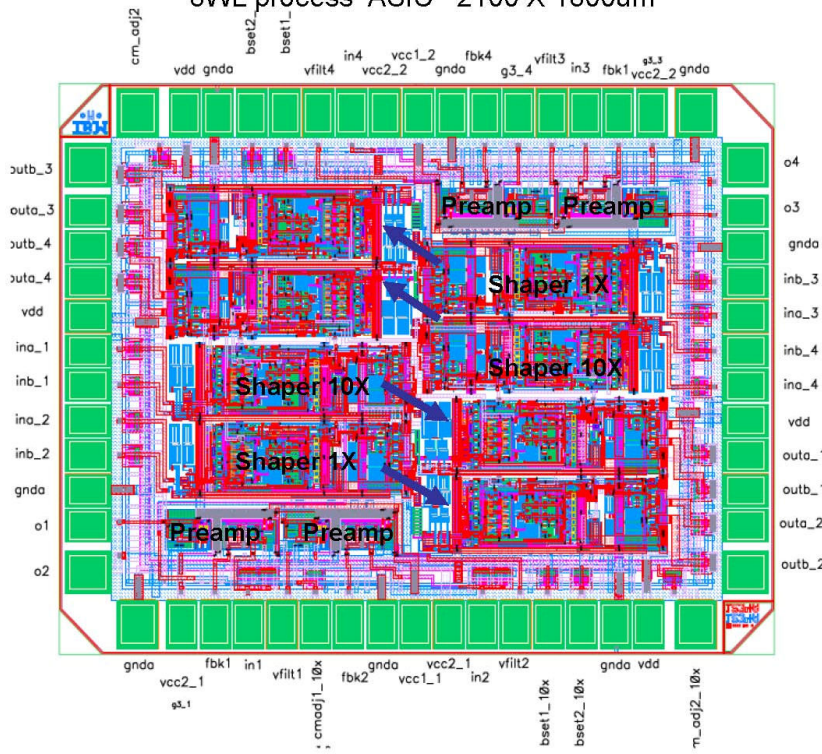LAPAS: Liquid Argon PreAmplifier Shaper
8WL process ASIC 2100 X 1800um



Special Acknowledgment of the significant contributions of Emerson Vernon, Sergio Rescia (BNL) and Nandor Dressnandt (Penn) to this work.


II. LAPAS chip for ATLAS LAr upgrade

- Technology:

- IBM 8WL SiGe BiCMOS
- 130 nm CMOS (CERN's techno)
- More radhard than needed:
 - FEE Rad Tolerance TID~ 300Krad,
 - Neutron Fluence $\sim 10^{13}$ n/cm²

- Circuit is "direct" translation

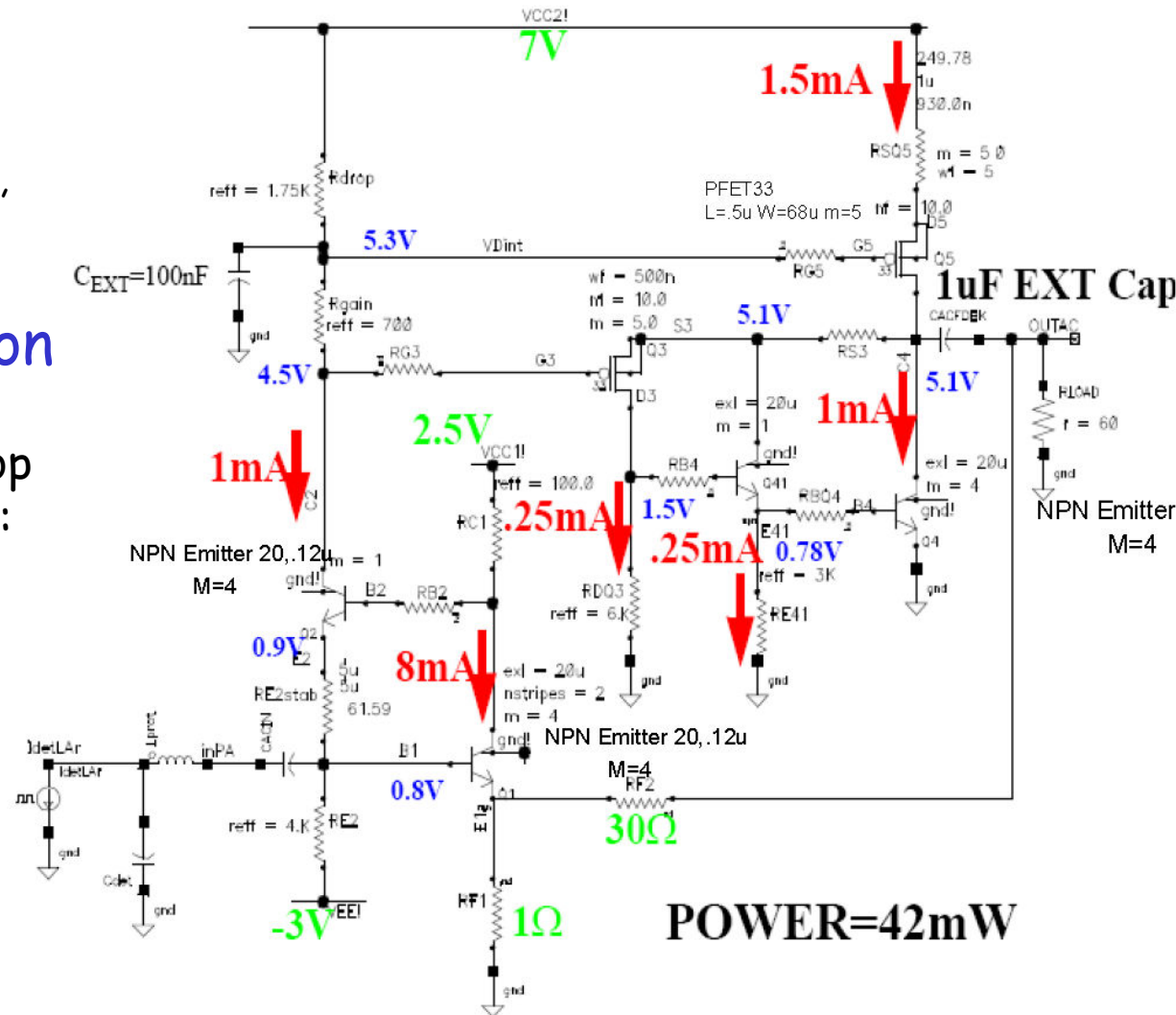- Need external 1 μ F AC coupling capacitor for outer feedback loop
- Three pads per channel required:
 - Input
 - Two for AC coupling capacitor
- Voltage output



III. Voltage output versus current output


- Voltage output:

- Pros:

- Tested

- Cons:

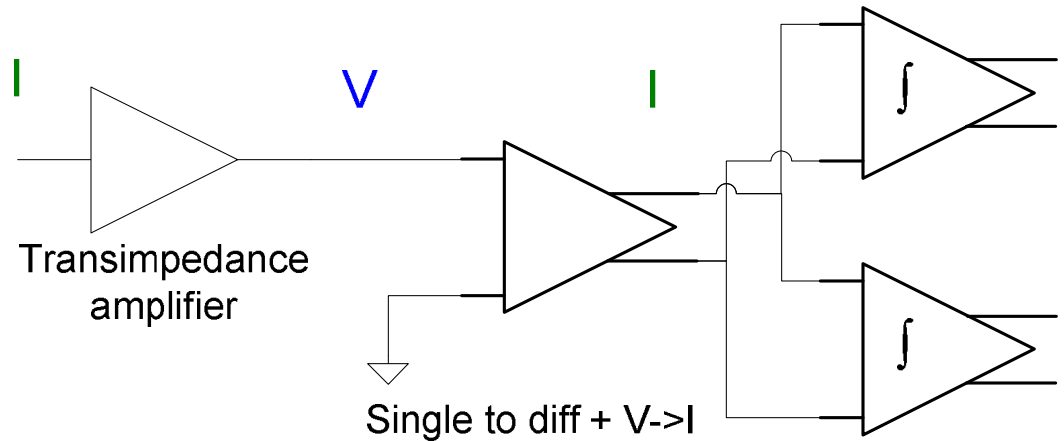- I (PMT) $\rightarrow V$ and $V \rightarrow I$ (integrate)
 - Larger supply voltage required
 - External components
 - 2 additional pads per channel




- Current output ("à la PS")

- Pros:

- "Natural" current processing
 - Lower supply voltage
 - All low impedance nodes:
 - Pickup rejection
 - No external components
 - No extra pad

- Cons:

 
- Trade-off in current mirrors: linearity vs bandwidth



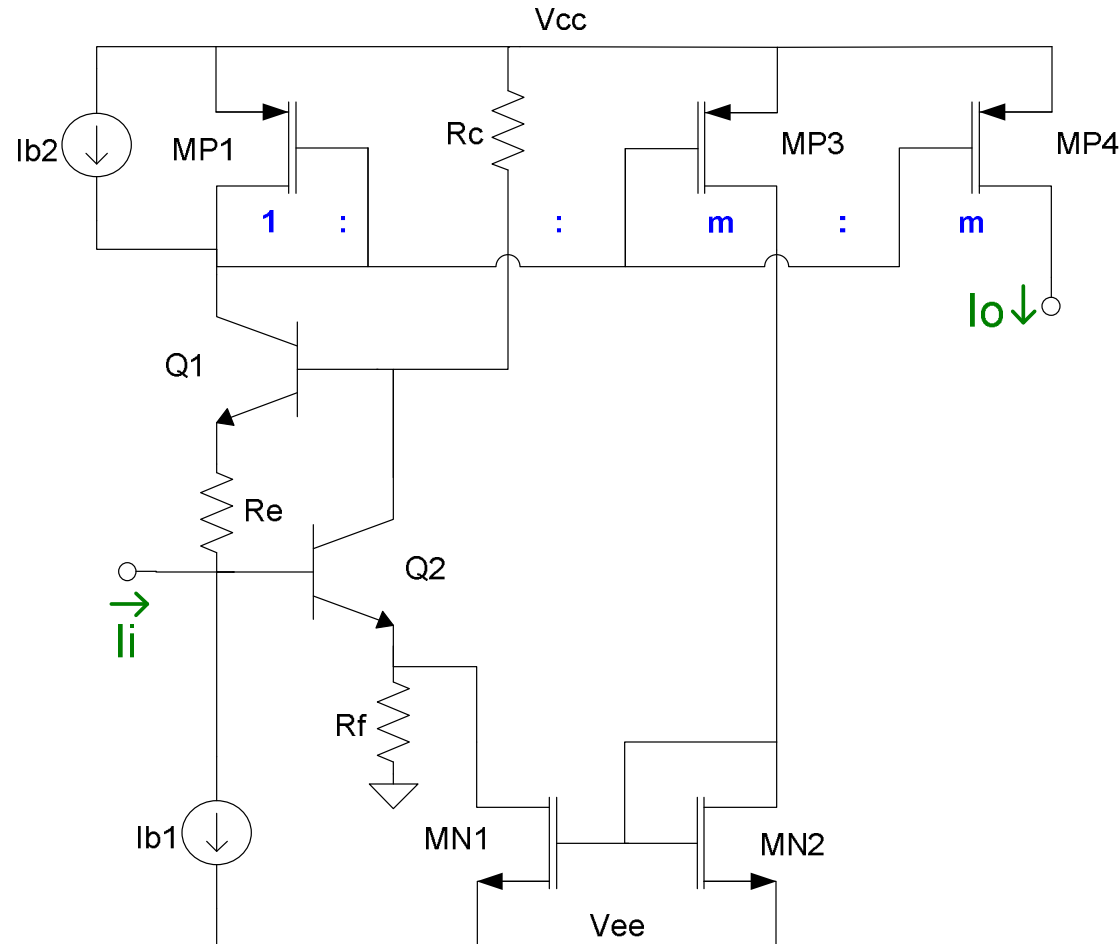IV. Current output / mixed feedback


- **Mixed mode feedback:**
 - Inner loop: lower input impedance
 - Voltage feedback (gain): Q2 and Rc
 - Outer loop: control input impedance
 - Current feedback: mirrors and Rf
- Variation of LAr preamplifier
- Current gain: m
- Input impedance

$$Z_i \approx \frac{1/g_{m1} + R_e}{g_{m2} R_c} + m R_f$$




IV. Current output / mixed feedback

- AC simulation

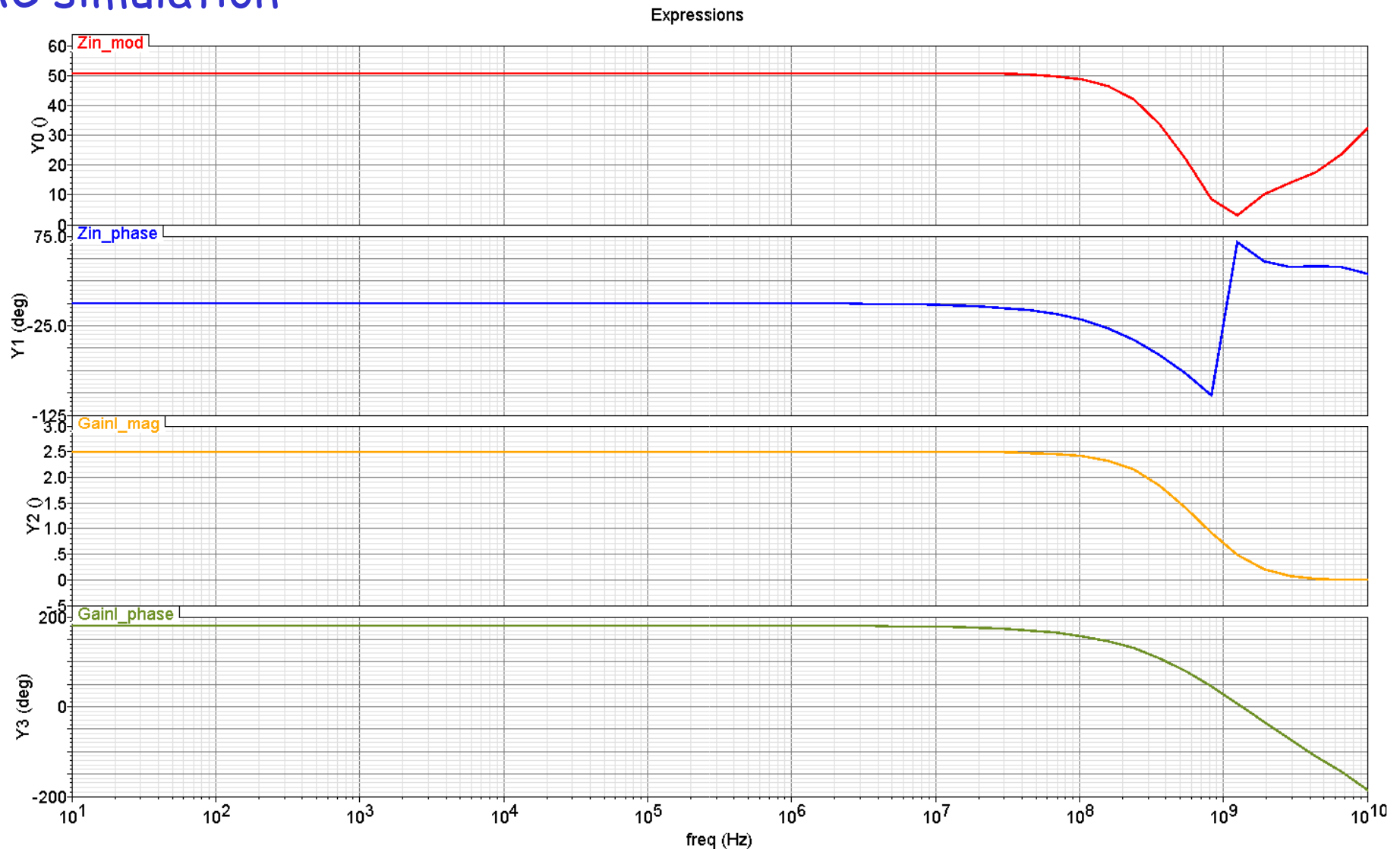


IV. Current output / mixed feedback

- Transient simulation

 

 
IV. Current output / mixed feedback

- Dynamic input impedance and linearity (mirrors to be optimized)




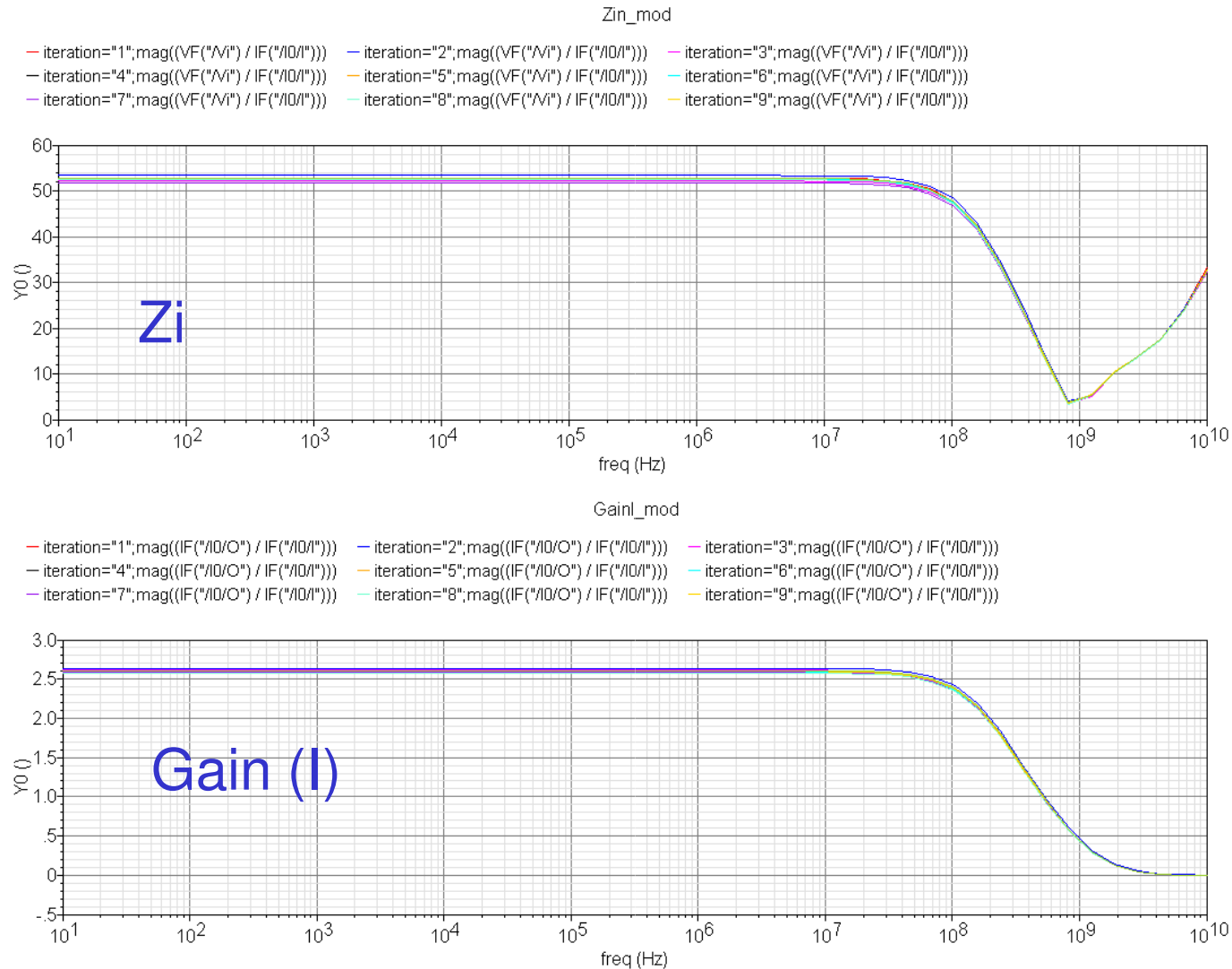
IV. Current output / mixed feedback

- Monte Carlo simulations: mismatch variation



  IV. Current output / mixed feedback



- Monte Carlo simulations: process variation



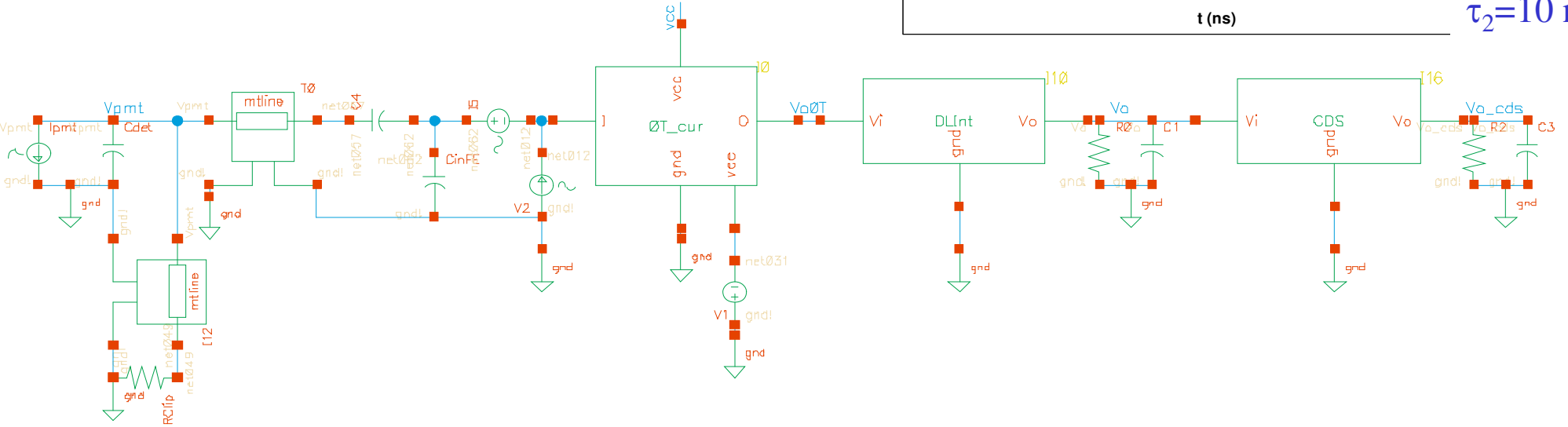 IV. Current output / mixed feedback


- Full channel simulation:

- Delay line clipping
- 12 m cable between PMT and FE
- Preamplifier (transistor level)
- Integrator (ideal)
- Pedestal subtraction (ideal)
 - Skin effect taken into account in cable



 
IV. Current output / mixed feedback

- Full channel simulation: transient response



IV. Current output / mixed feedback

- Full channel simulation: noise

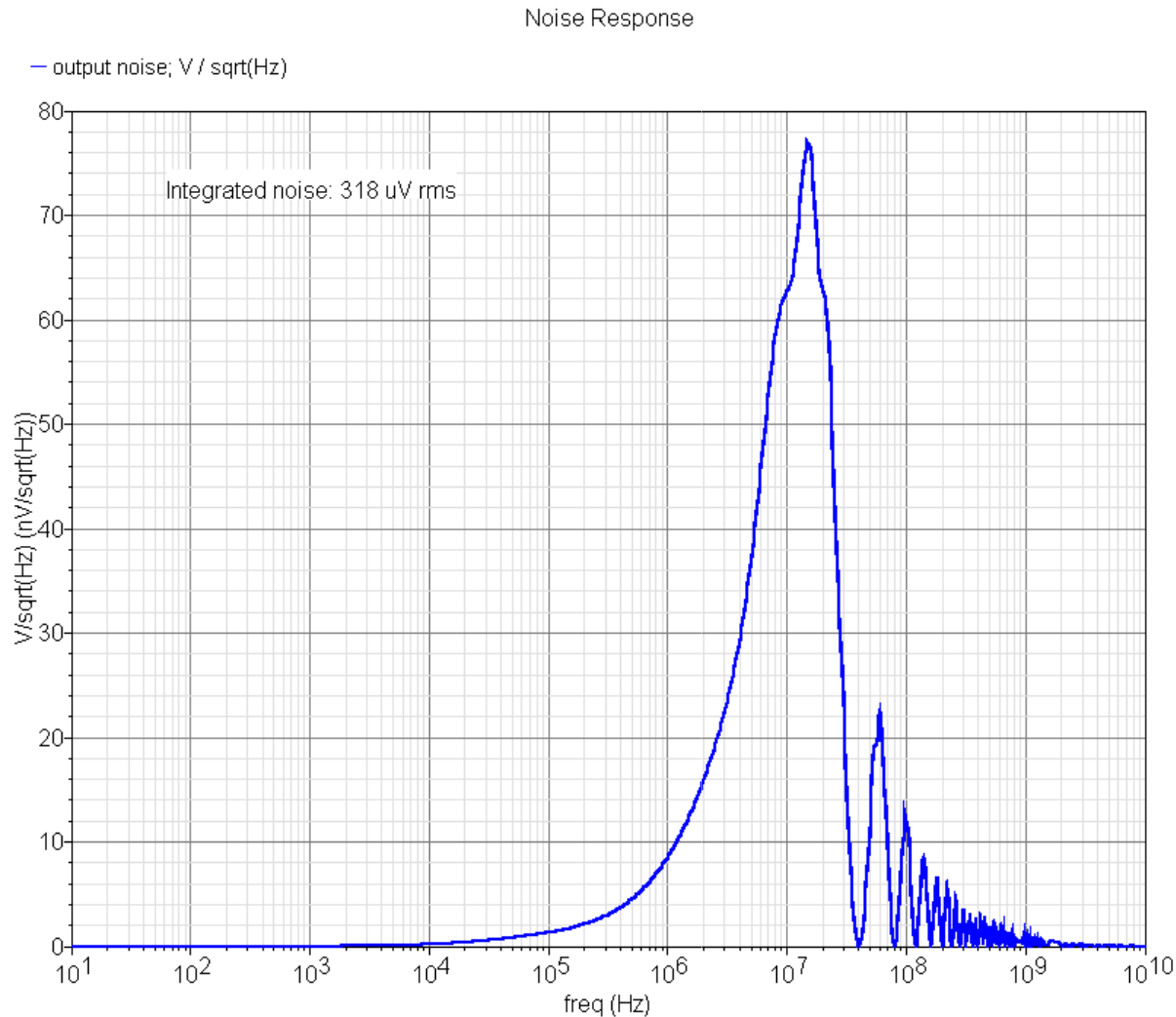

V. Current output / current feedback

- Current mode feedback:

- Inner loop: lower input impedance
 - Current feedback (gain): mirror: K
- Outer loop: control input impedance
 - Current feedback: mirror: m

- Current gain: m

- Input impedance


$$Z_i \approx \frac{1/g_{m1} + \text{Re}}{1 + K} + \frac{K}{1 + K} mR_f$$

- Current mode feedback

- Optical communications
- SiPM readout


- Better in terms of ESD:

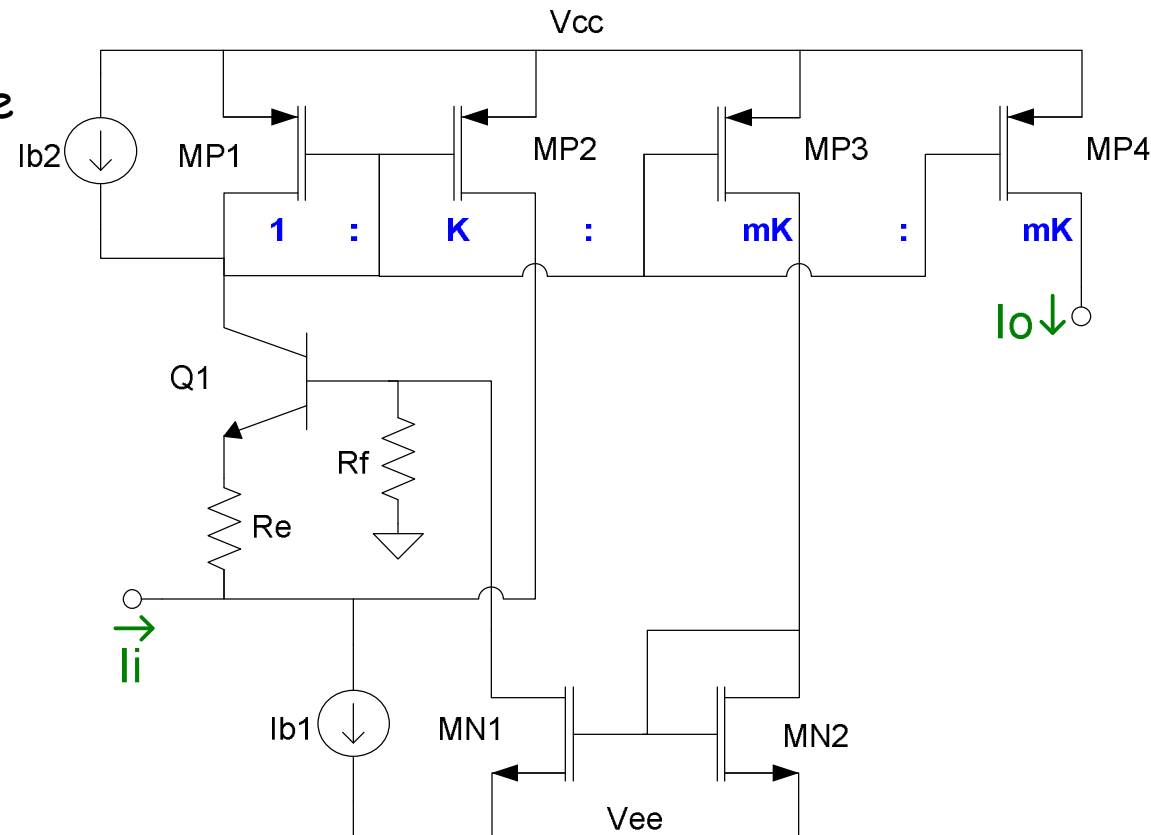- No input pad connected to any transistor gate or base




IV. Current output / current feedback

- AC simulation

 


IV. Current output / current feedback

- Transient simulation

 



IV. Current output / current feedback

- Dynamic input impedance and linearity

 

  
IV. Current output / current feedback

- Monte Carlo simulations: mismatch variation



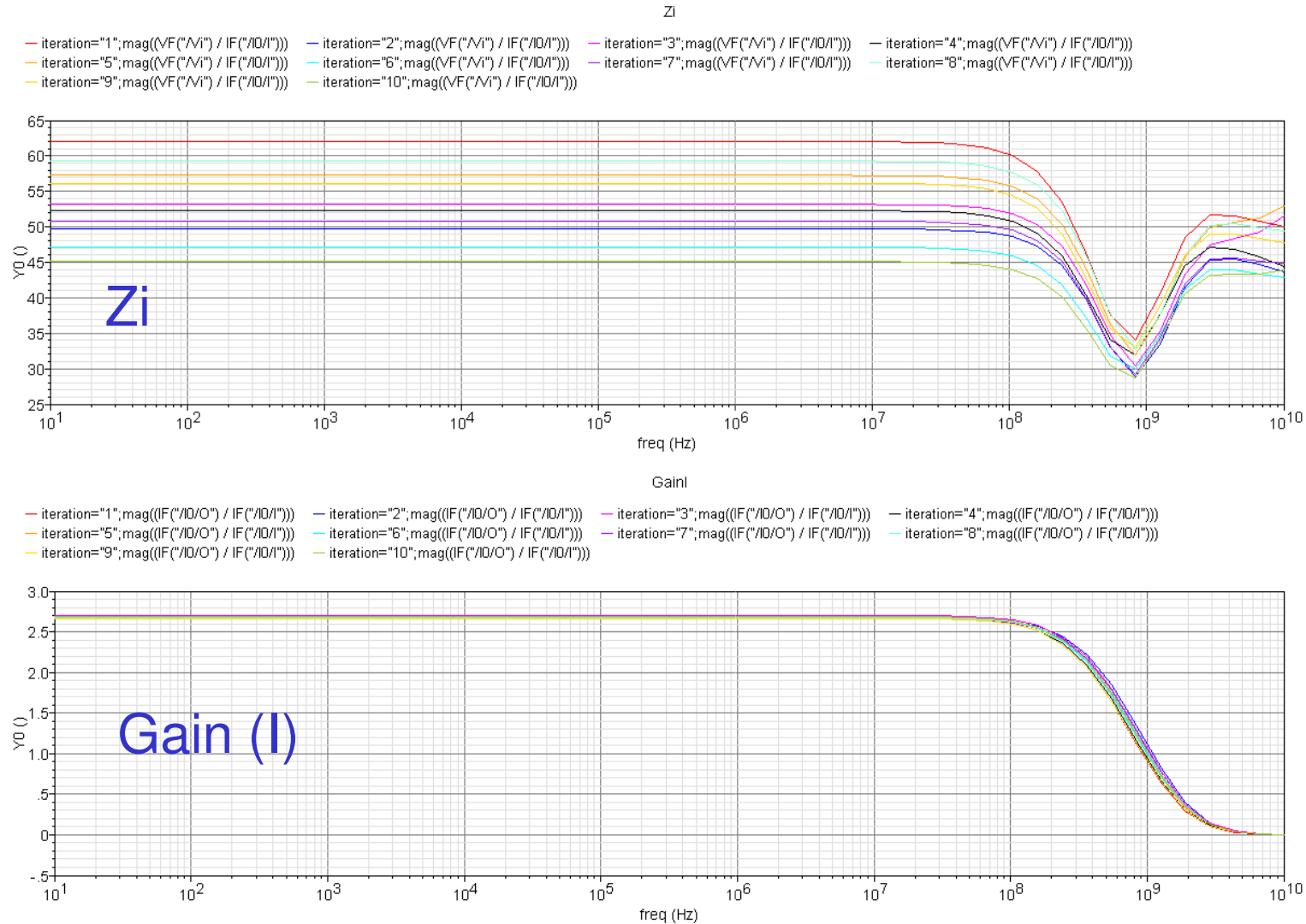
IV. Current output / current feedback

- Monte Carlo simulations: process variation



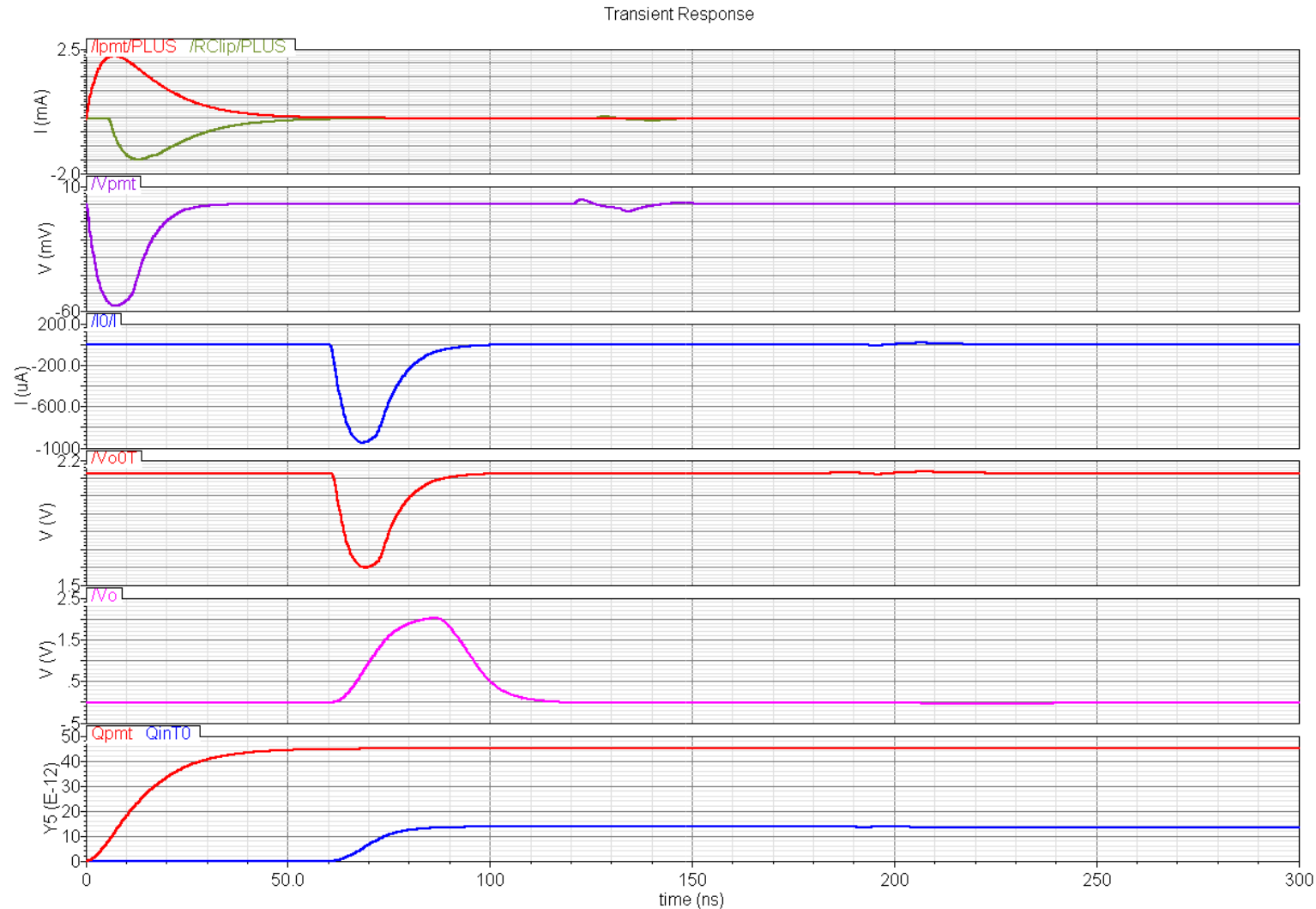
IV. Current output / current feedback

- Full channel simulation: transient response



IV. Current output / current feedback

- Full channel simulation: noise

 

VI. Discussion

- First simulations of current amplifiers are promising:
 - $Z_{in}=50\ \Omega$ for full dynamic and BW=100 MHz
 - Noise: 400 μV rms after integration and pedestal subtraction
 - MAIN ISSUE: linearity: 2-3 % error (mirrors not optimized)
 - Trade off: linearity / BW / noise
- Precise analysis:
 - Precise analysis of feedback loops: stability !
 - Noise
- Optimize current mirrors: linearity / dynamic Z_i !
- Effect of process variation discussed in general talk
- Plans:
 - Finalize study/optimization
 - Decide to send voltage output or current output (or both)
 - When? March (not mini@sic run) / June