



# Analog FE ASIC: first prototype

Upgrade of the front end electronics of  
the LHCb calorimeter

E. Picatoste, A. Sanuy, D. Gascón


Universitat de Barcelona  
Institut de Ciències del Cosmos ICC-UB

Calorimeter upgrade meeting – CERN – June 22<sup>th</sup> 2010

# Outline

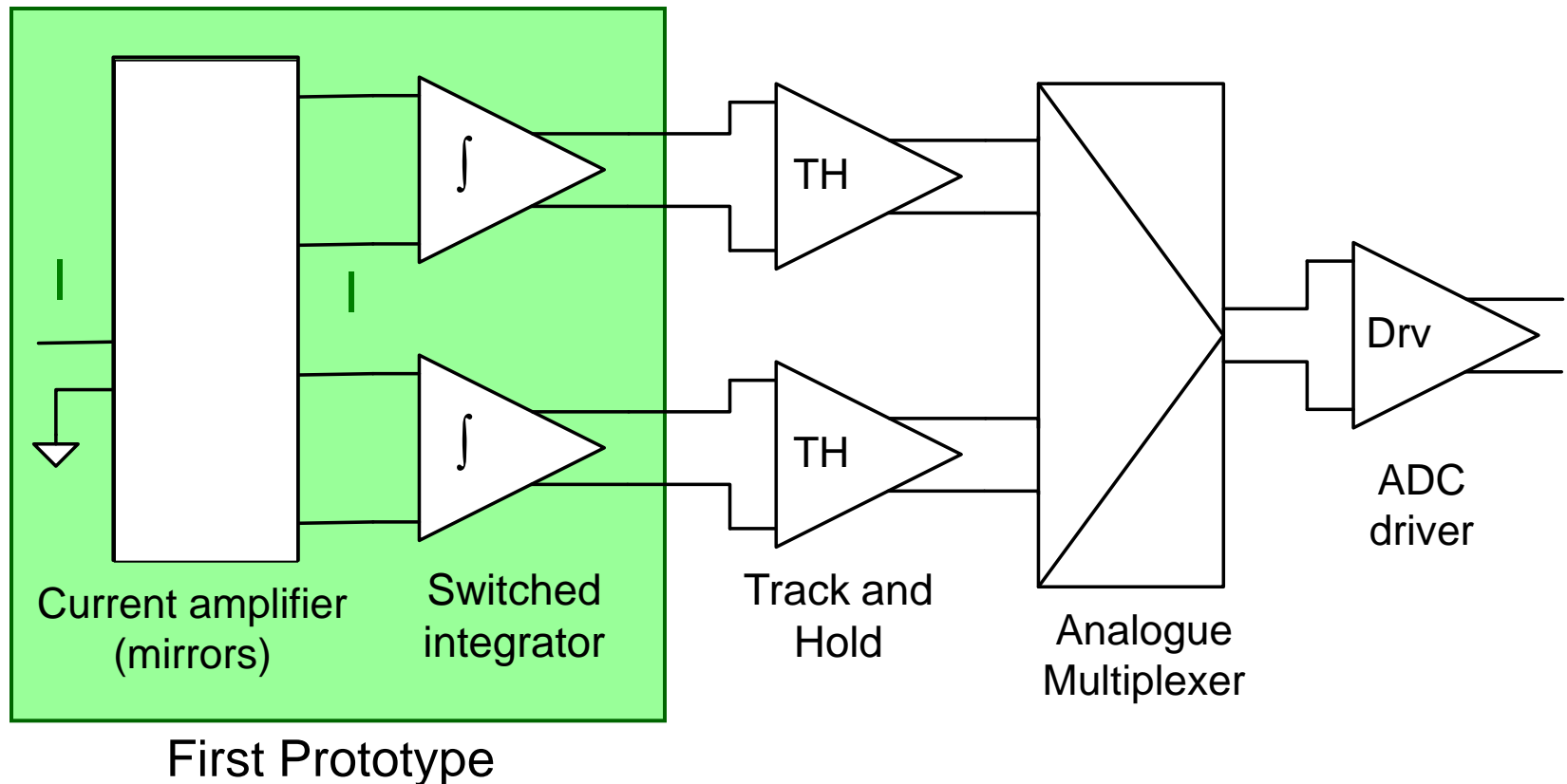- (1) Introduction
- (2) Current Mode Preamplifier
- (3) Integrator
  - FDOA
  - Switched Integrator
- (4) Linearity
- (5) Noise
- (6) IC Implementation Details

- ECAL analogue FE IC: channel architecture




# Introduction

- IC sent: ICECAL


Current preamp

Integrators

 
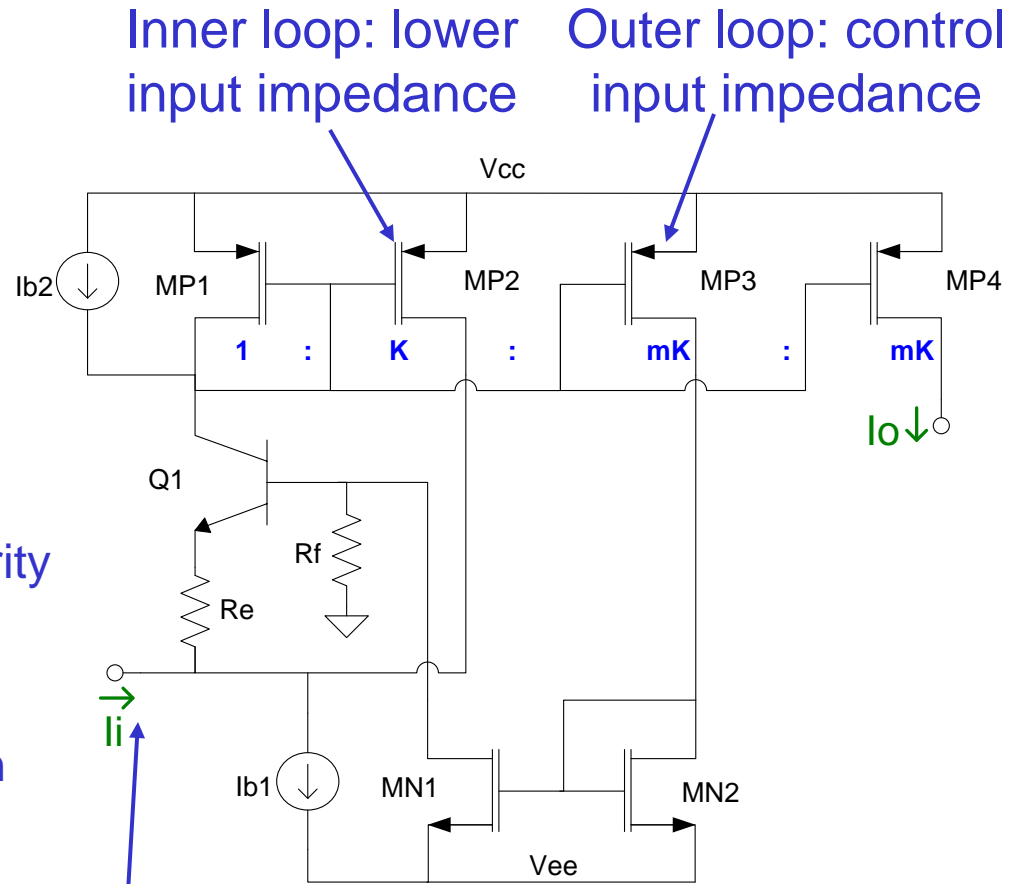
# Current mode preamplifier

- Pros:
  - “Natural” current processing
  - Lower supply voltage
  - All low impedance nodes:
    - Pickup rejection
  - No external components
  - No extra pad
- Cons:
  - Trade-off in current mirrors: linearity vs bandwidth
- Low voltage
  - Only 1 V<sub>be</sub> for the super common base input stage
- Better in terms of ESD:
  - No input pad connected to any transistor gate or base




$$Z_i = \frac{1/g_{m1} + R_e}{1 + K} + \frac{K}{1 + K} mR_f$$

# Current mode preamplifier

- Simulations based on the extracted RC


Possible compensations:

- Parallel R
- current ladder

 

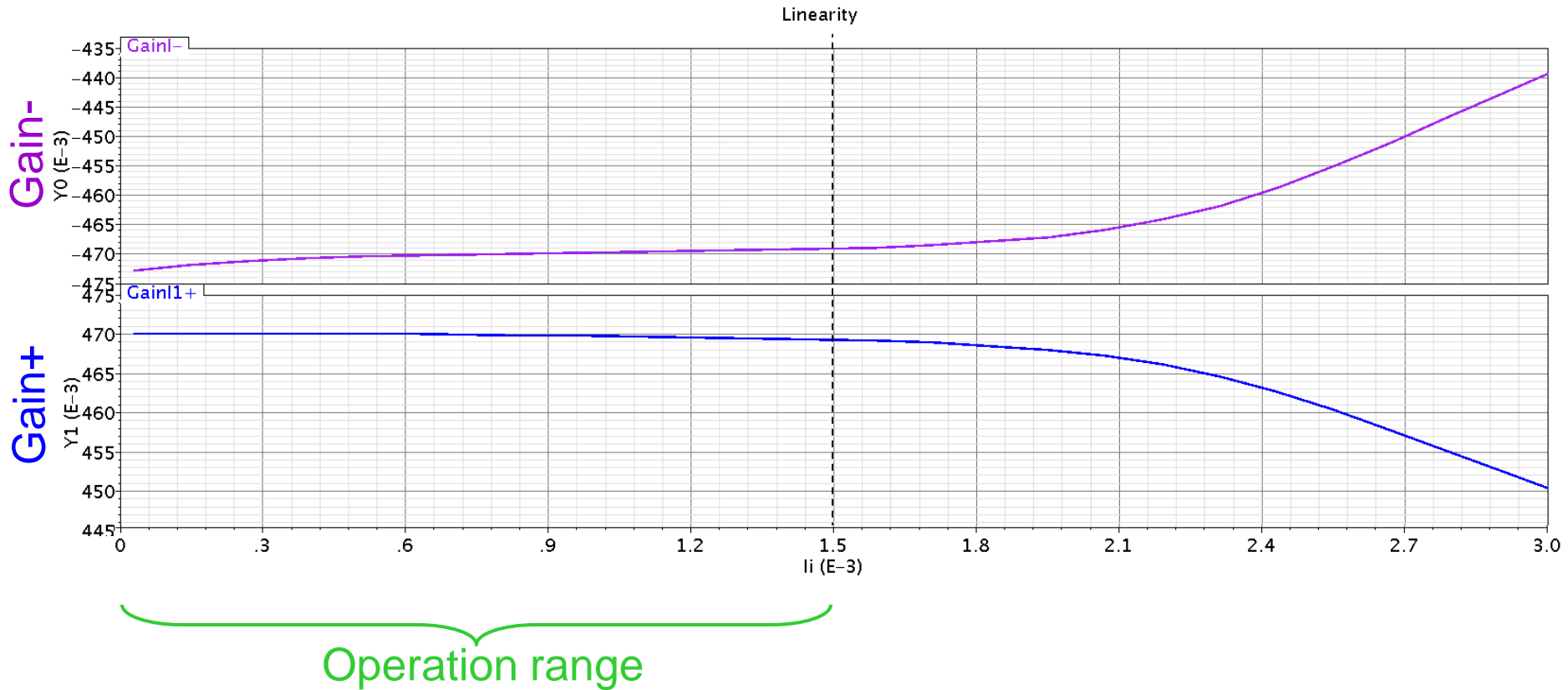
# Current mode preamplifier

- Simulations based on the extracted RC: linearity vs.  $I_{i,peak}$


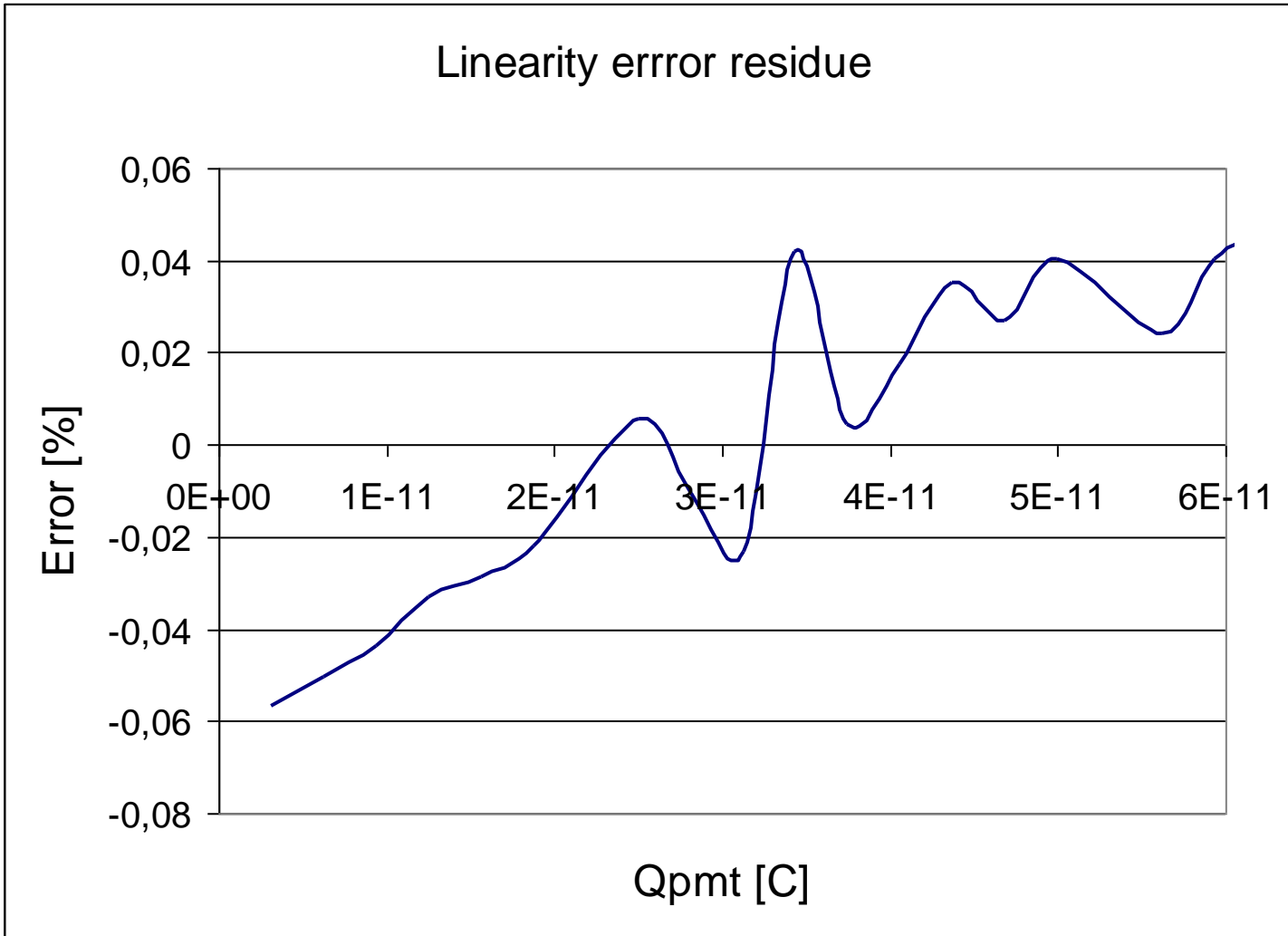
# Current mode preamplifier

- Linearity error after integration (ideal) vs input charge






# Integrator


- Switched integrator architecture

FDOA specifications	
Parameter	Value
Gain bandwidth	500 MHz
Phase margin	> 65°
Slew rate	> 2 V/ $\mu$ s
$V_{CM}$	1.65 V

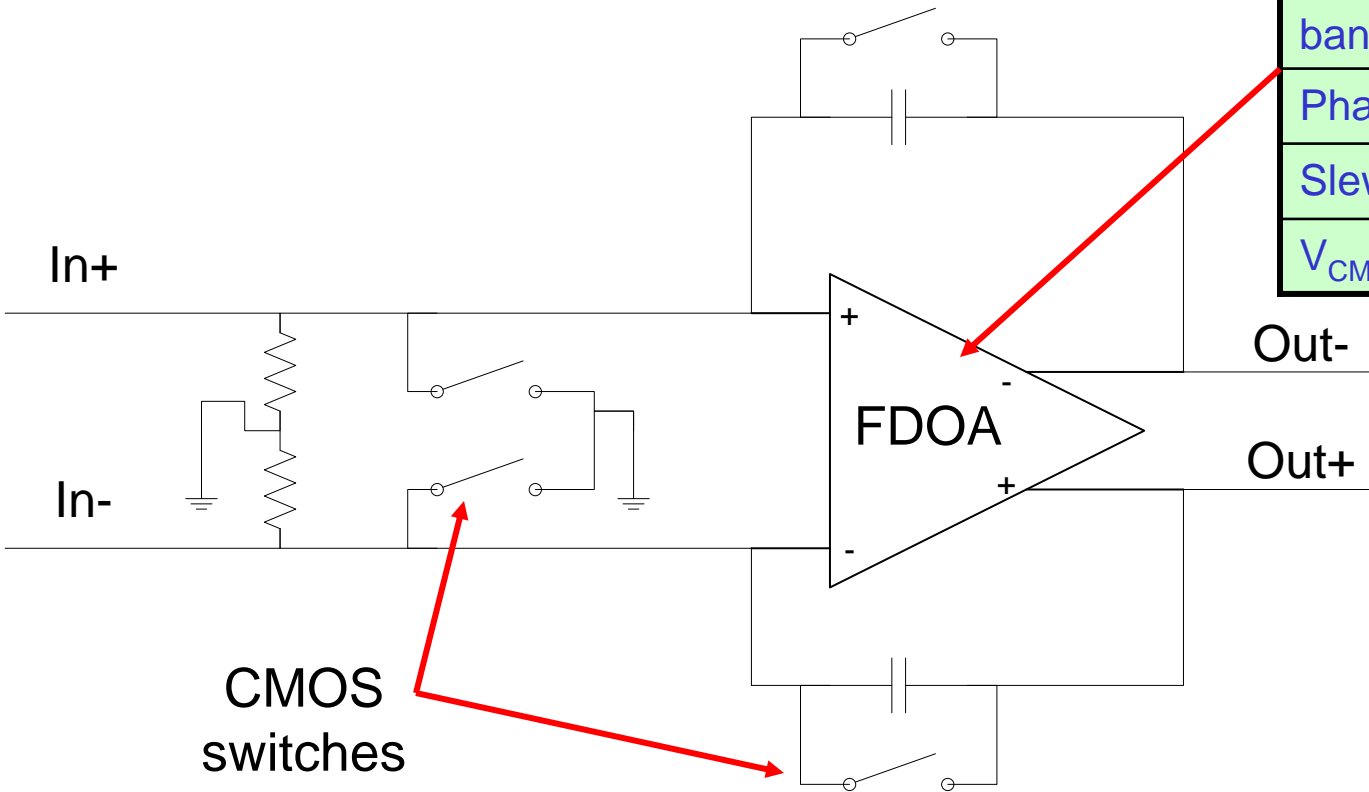


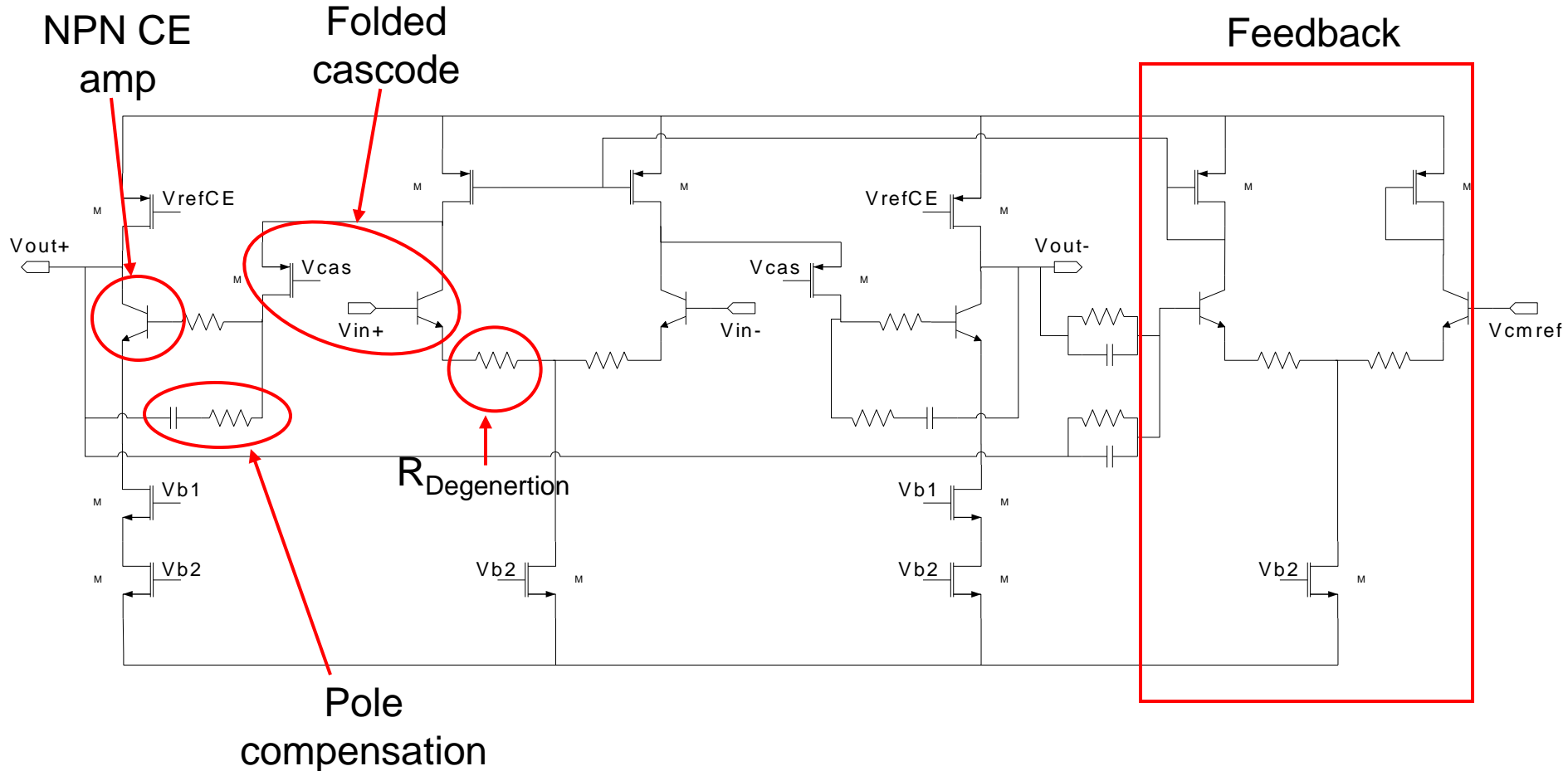
# FDOA: design

- Fully differential Operational Amplifier



 
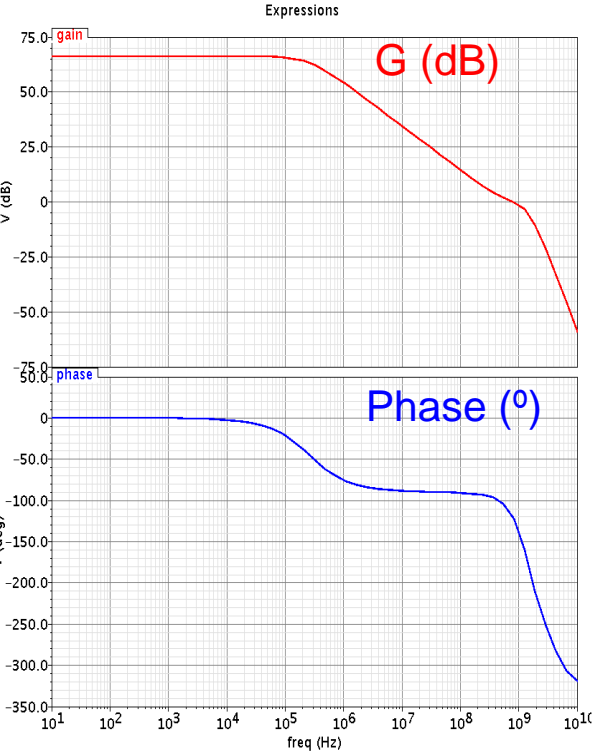
# FDOA: open loop post layout simulations

- $I_{bCE} = 900\mu A$
- Load capacitor between 150fF and 5.1pF



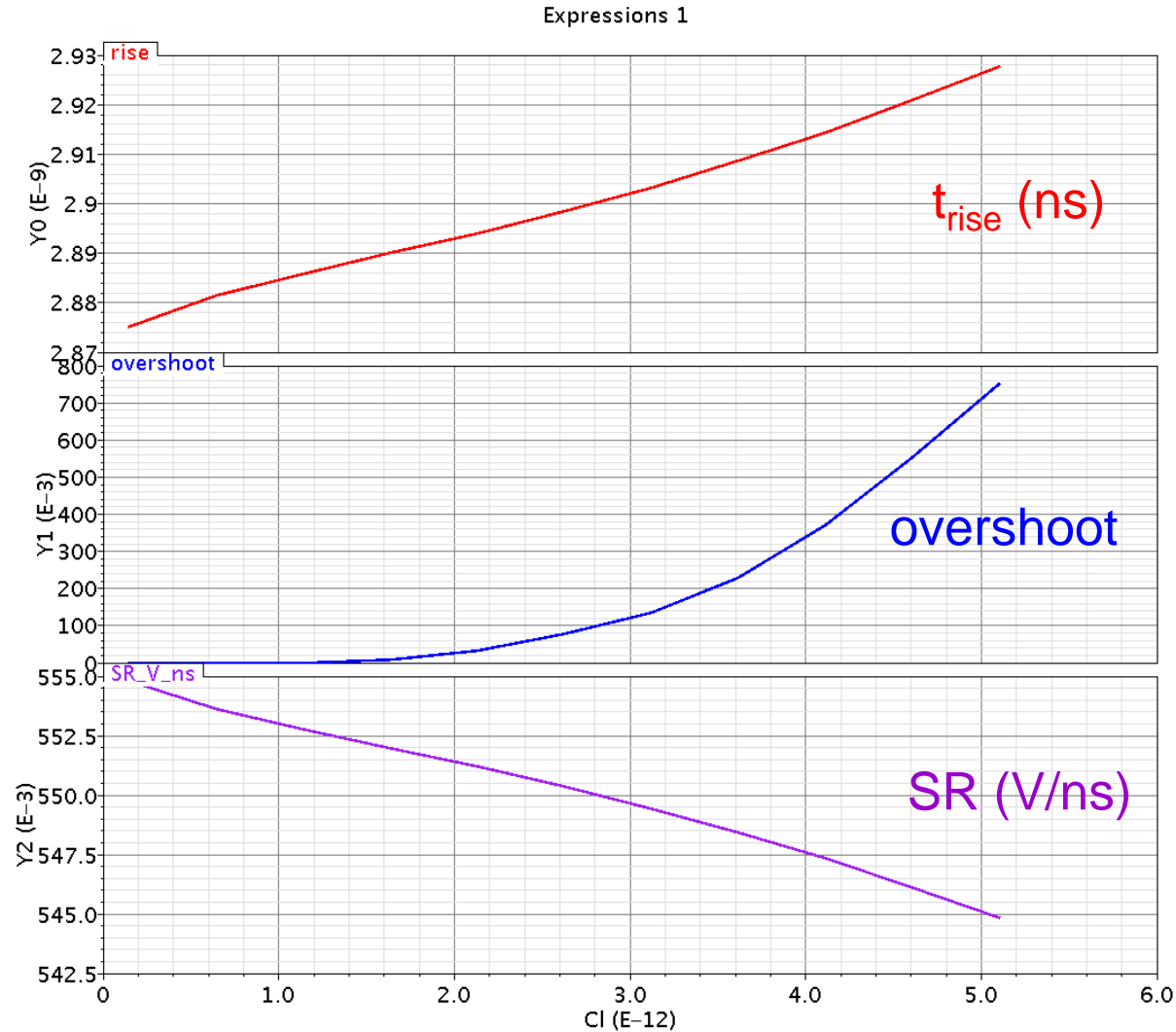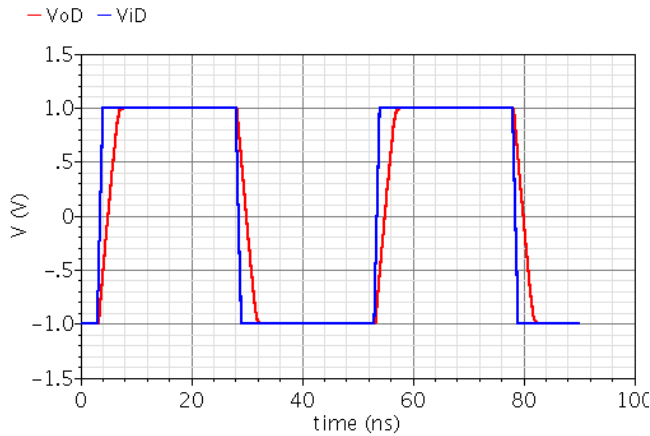
# FDOA: closed loop post layout simulations

- $I_{bCE} = 900\mu A$
- Load capacitor between 150fF and 5.1pF



 
# Integrator: pulse response

- Simulations based on extracted RC
- $C_1 = 5\text{pF}$



 
# Integrator: Linearity

- Simulations based on extracted RC
- $C_1 = 5\text{pF}$



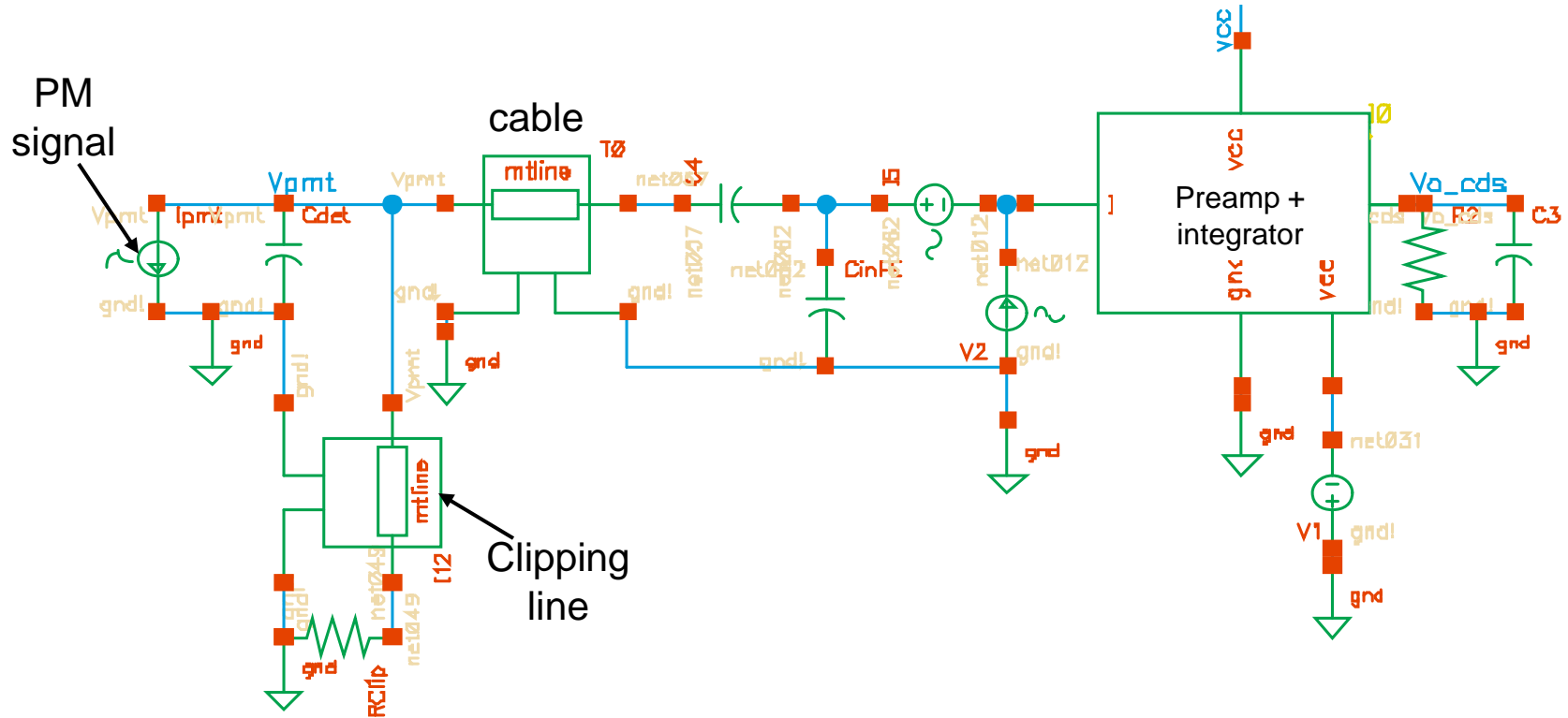
# Front End simulations (Preamp+integrator)

- Simulations based on extracted RC of complete IC
- Includes PM signal (TDR) and cable effects



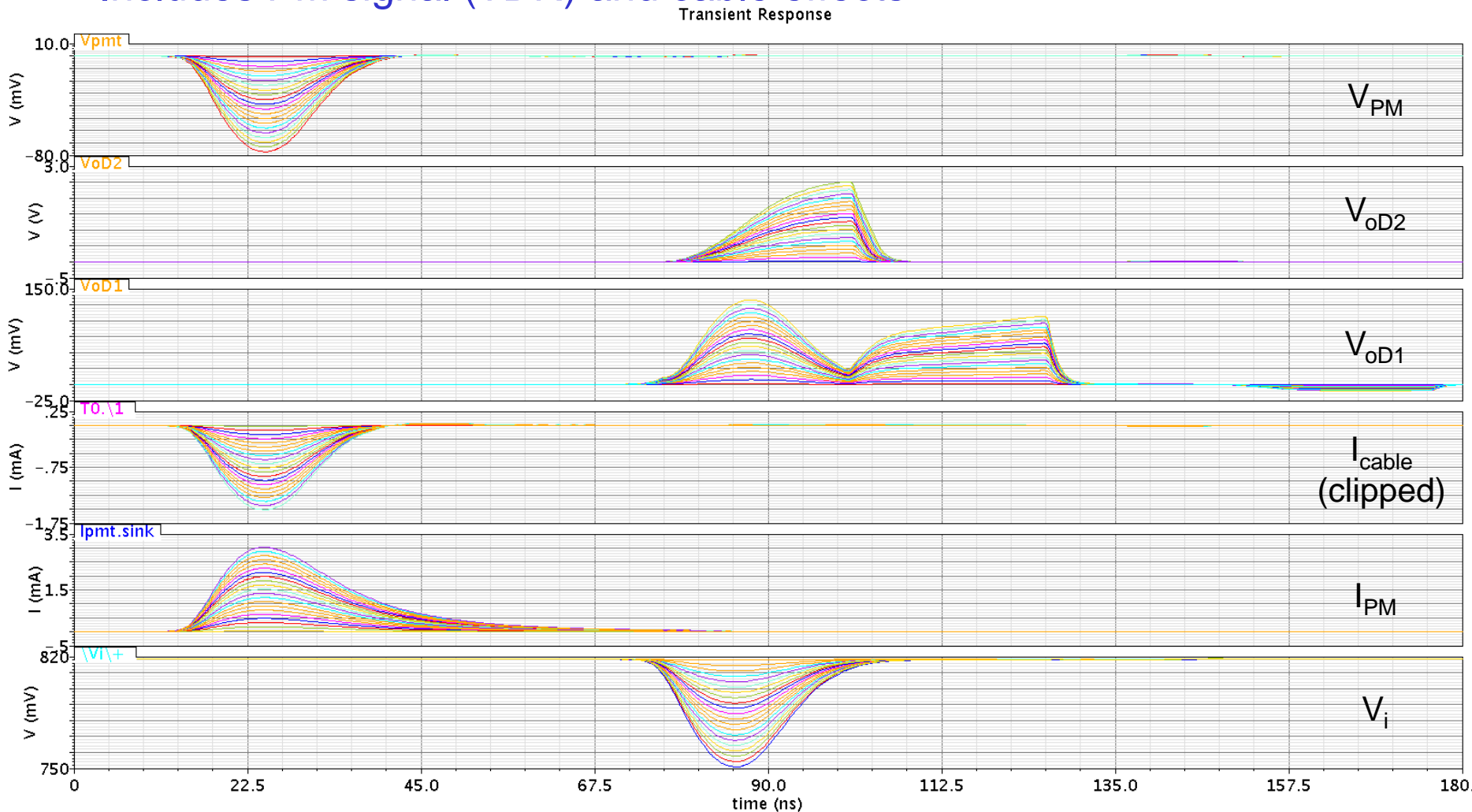
# Front End simulation (Preamp+integrator)

- Simulations based on extracted RC of complete IC
- Includes PM signal (TDR) and cable effects







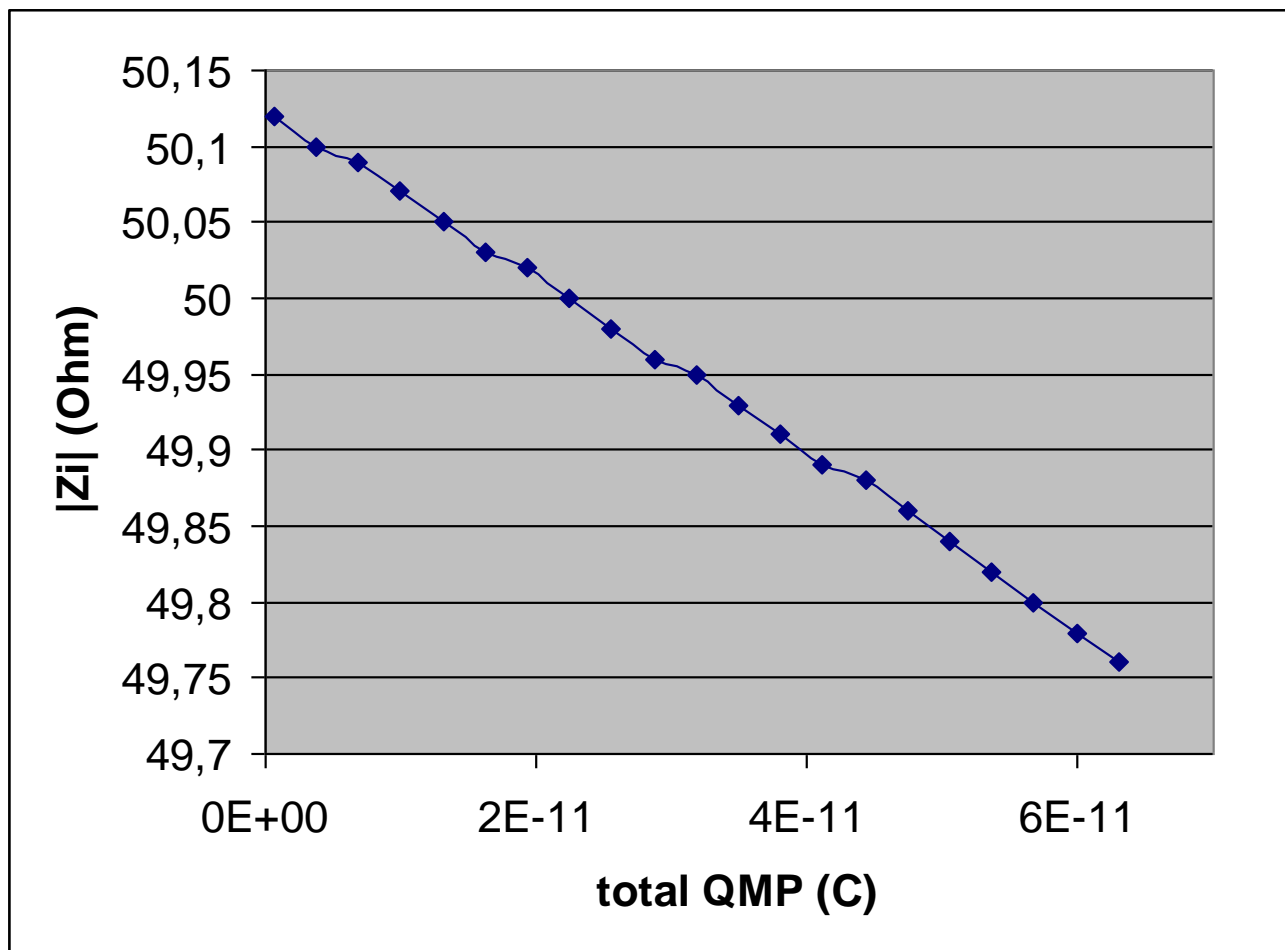
## Dynamic deviation of the input impedance



# Front End simulation: linearity


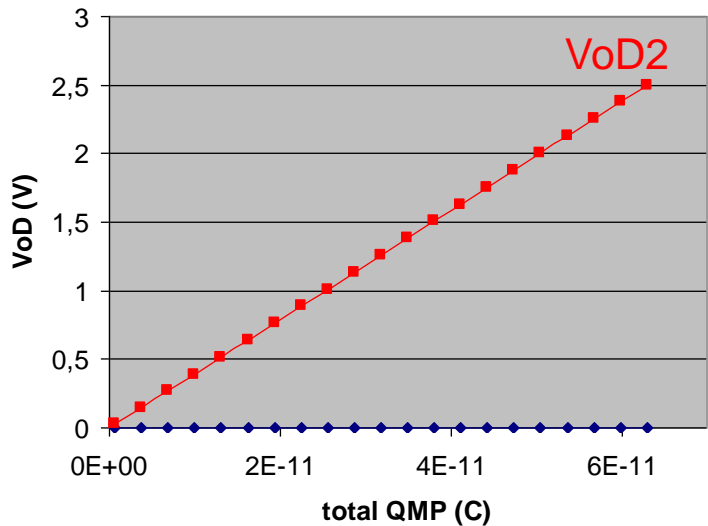
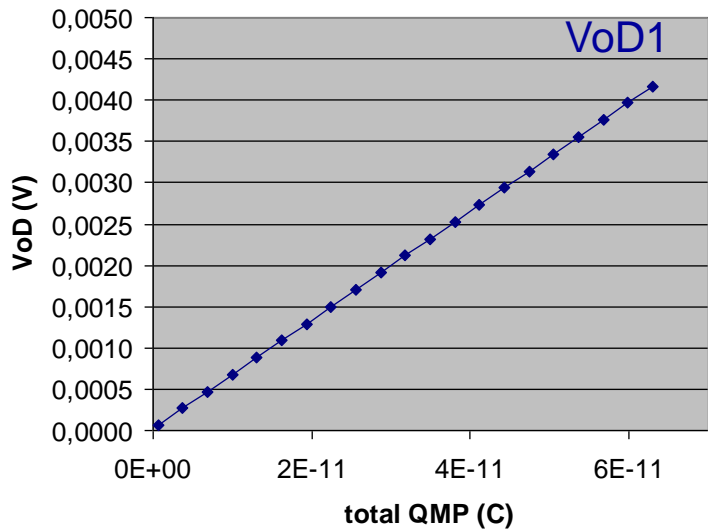


Linear error

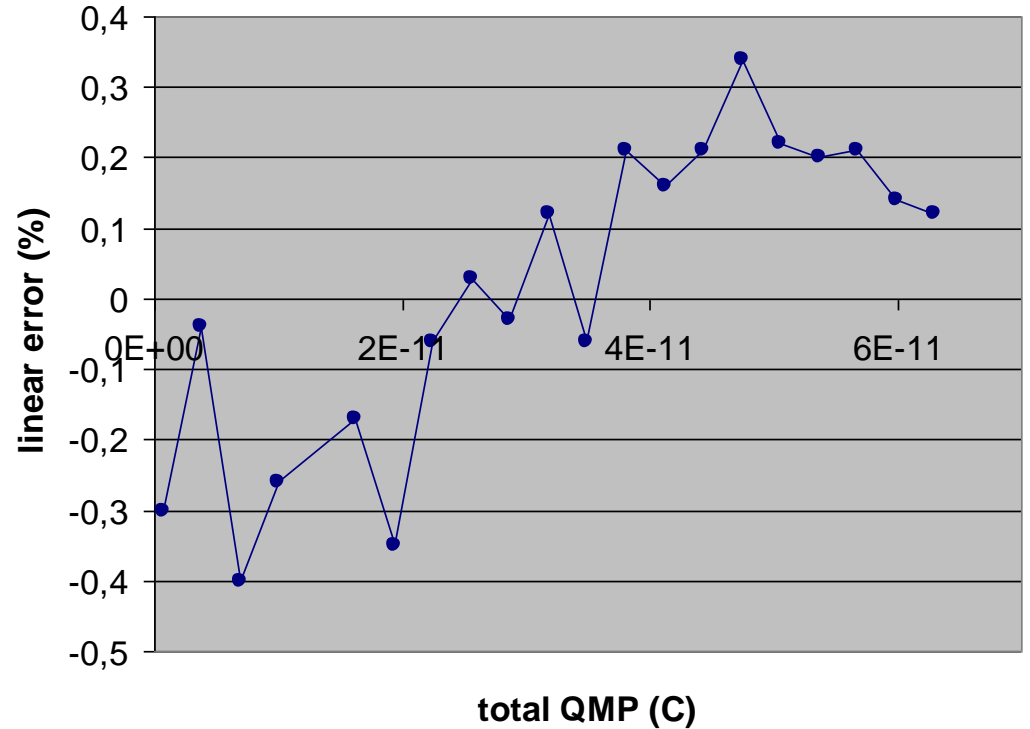

# Front End simulation: noise

- Transient noise analysis

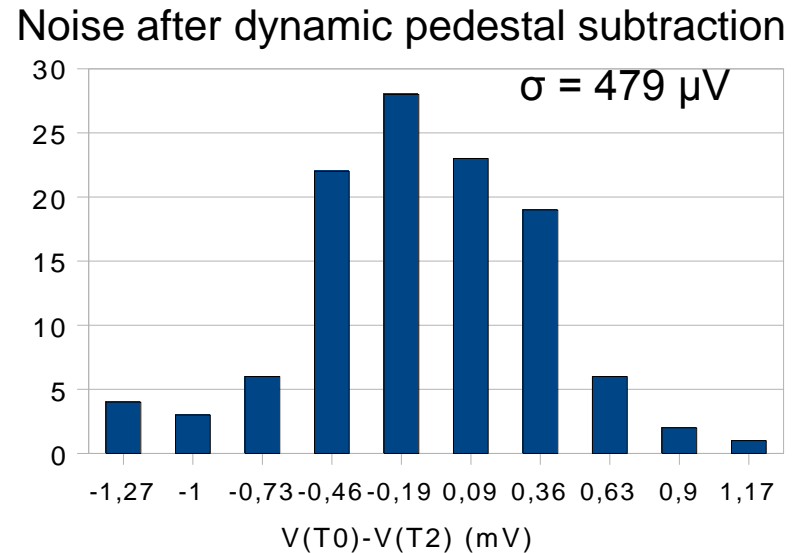  

- Noise at output: distribution of  $V(t_2)$
- Noise after dynamic pedestal subtraction: distribution of  $V(t_1) - V(t_2)$

# IC Implementation details

- AMS SiGe BiCMOS s35
- QFN package
  - Substrate connected to central pad (gnd)
- When taking into account the bonding parasitics:
  - $3 * \text{nominal } L \Rightarrow \text{danger of ringing}$
- Solutions:
  - Include R in series with decoupling capacitor of  $V_{ref}$
  - Increase number of gnd pins
  - Downbonds for gnd

