

Powering R&D at Aachen IB

Lutz Feld, Rüdiger Jussen, Wacław Karpinski,
Katja Klein, Jennifer Merz, Jan Sammet

CMS Tracker Upgrade Power WG
CERN, 7. 10. 2008

- Introduction
- Commercial Buck Converters
- APV25 Features
- CERN Buck Converter
- BNL Charge Pump
- Summary and Outlook

- CMS-R&D Proposal 07.01 „[R&D on Novel Powering Schemes for the SLHC CMS Tracker](#)” approved in October 2007
- **workplan:**
 - establish test bed for novel powering schemes:
one petal (prototype, currently 4 modules) + read-out system DONE
 - set up Electromagnetic Interference test stand to measure
conductive (calibrated pick-up coils) and radiated (near field probes) noise DONE
 - assemble and test DC-DC converters from commercial components ~DONE
 - develop and test radiation hard DC-DC converters ONGOING
 - investigate alternative schemes (serial powering) NOT STARTED
 - simulate implications for material budget ONGOING
 - “...development of a detector sub-system which is supplied at a voltage much higher than the actual ASIC supply voltage and therefore much reduced current”
- **people:** Feld, Jussen, Karpinski, Klein, Merz, Sammet

DC-DC Power Conversion

Power Supplies
HV / GND / V

$V_1 = V / g$ with conversion factor g assume n modules powered in parallel

$$P_{\text{modules}} = n V_1 I_{\text{module}}$$

$$P_{\text{cable}} = R_{\text{cable}} \left(n \frac{I_{\text{module}}}{g} \right)^2 = R_{\text{cable}} \left(\frac{P_{\text{modules}}}{g V_1} \right)^2 \sim \frac{1}{g^2}$$

Power Group

- + reduction of cable losses, i.e. copper
- + minimal changes to system design
- switching may induce noise

V



GND

HV






DC-DC Converters

- many different designs
- inductor based converters
 - current capacity up to several amps
 - ferrite cores saturate in 4 Tesla field
→ need to use air core coils
- capacitor based converters
 - are limited in current to few 100 mA at most
 - no inductors needed, can be very compact and may be even included in FE ASIC
- all need rad-hard “high voltage” transistors as switches
- efficiency typically 70 – 90 %
- switching noise is a concern

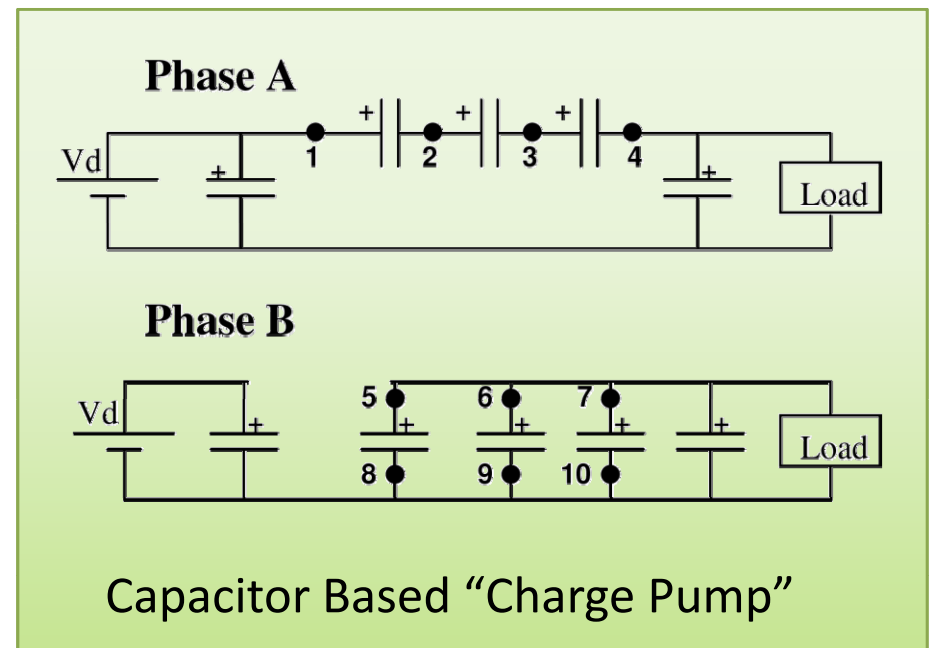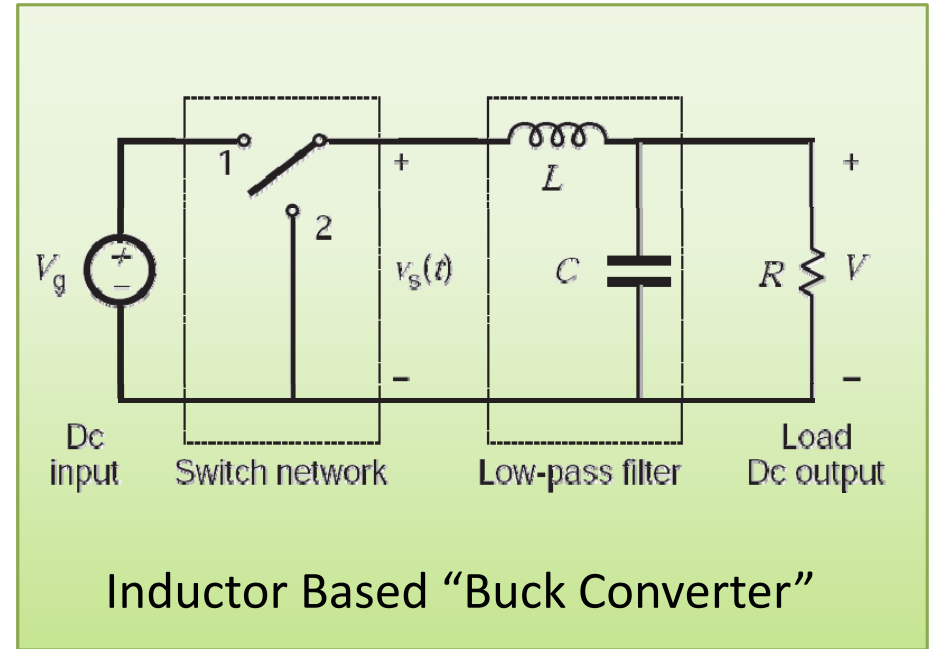


System Test with a TEC Petal

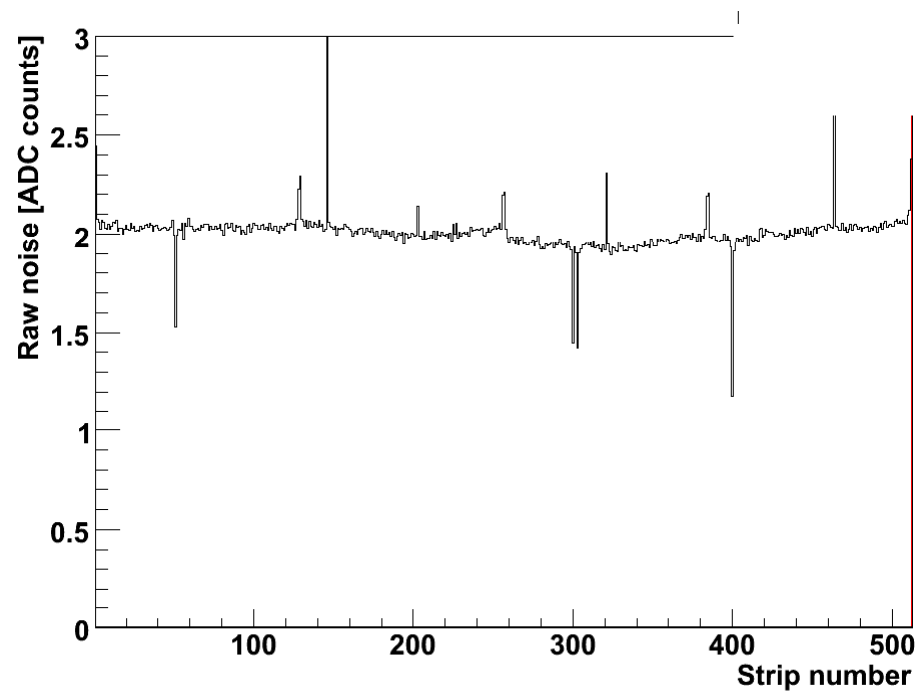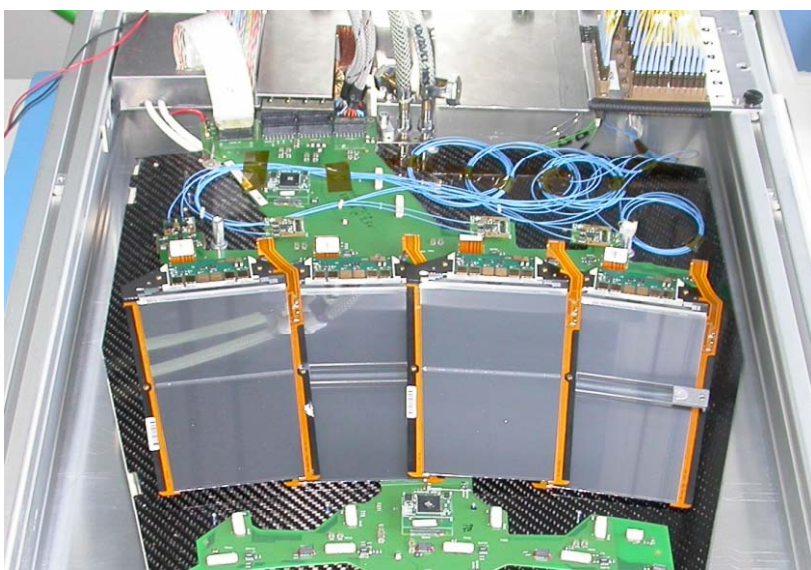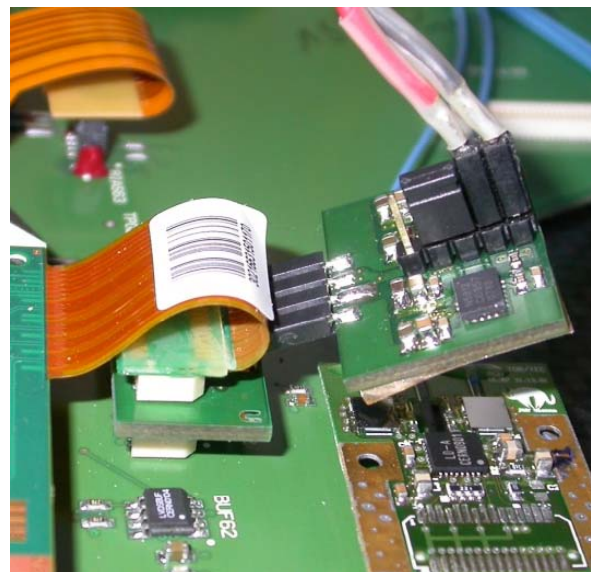

Commercial Inductor Based DC-DC Converters

○ Enpirion EN5312QI

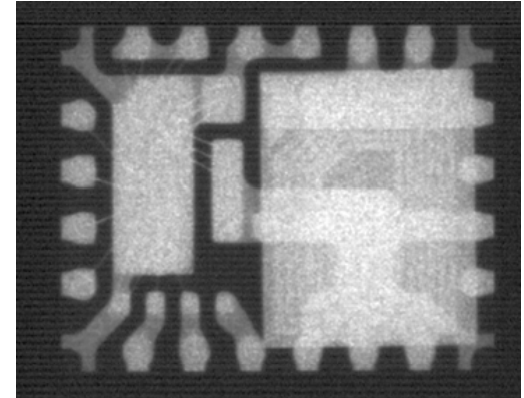- switching frequency $f_s \approx 4 \text{ MHz}$
- $V_{in} = 2.4\text{V} - 5.5\text{V (rec.)} / 7.0\text{V (max.)}$
- $I_{out} = 1\text{A}$
- integrated planar inductor



○ Enpirion EN5382D (similar to EN5312QI)

operated with external inductor


- air-core inductor Coilcraft 132-20SMJLB (538nH)
- ferrite-core inductor Murata LQH32CN1R0M23 (1 μ H)



○ 4-layer PCB with 2 converters provides 1.25V and 2.5V

- Input power ($V_{in} = 5.5\text{V}$) provided externally or via TEC motherboard
- Various designs: type L: larger board with integrated connector, type S: smaller board with separate connector

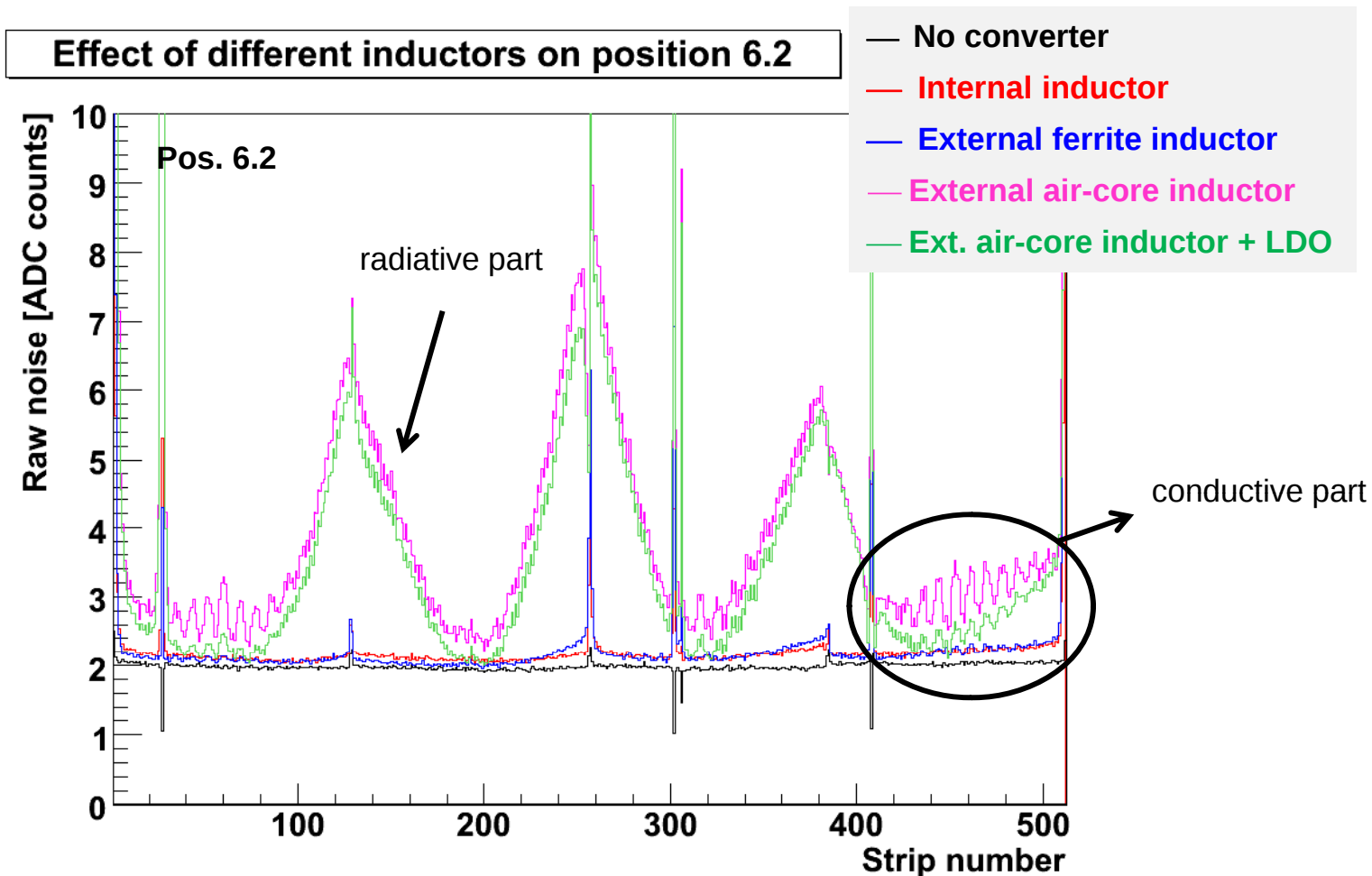
System Test with Commercial DC-DC Converters



- internal or external ferrite core inductor: 10% noise increase
- air-core inductor: huge noise increase, interference with module both radiative and conductive
- “radiative part” can be reproduced by an air core coil converter (not connected to a module) above hybrid
- “conductive part” can be reproduced by noise injection into the cables (see later)


Channel-to-channel Correlation with internal Ferrite-core Coils

With converters on 6.3 and 6.4

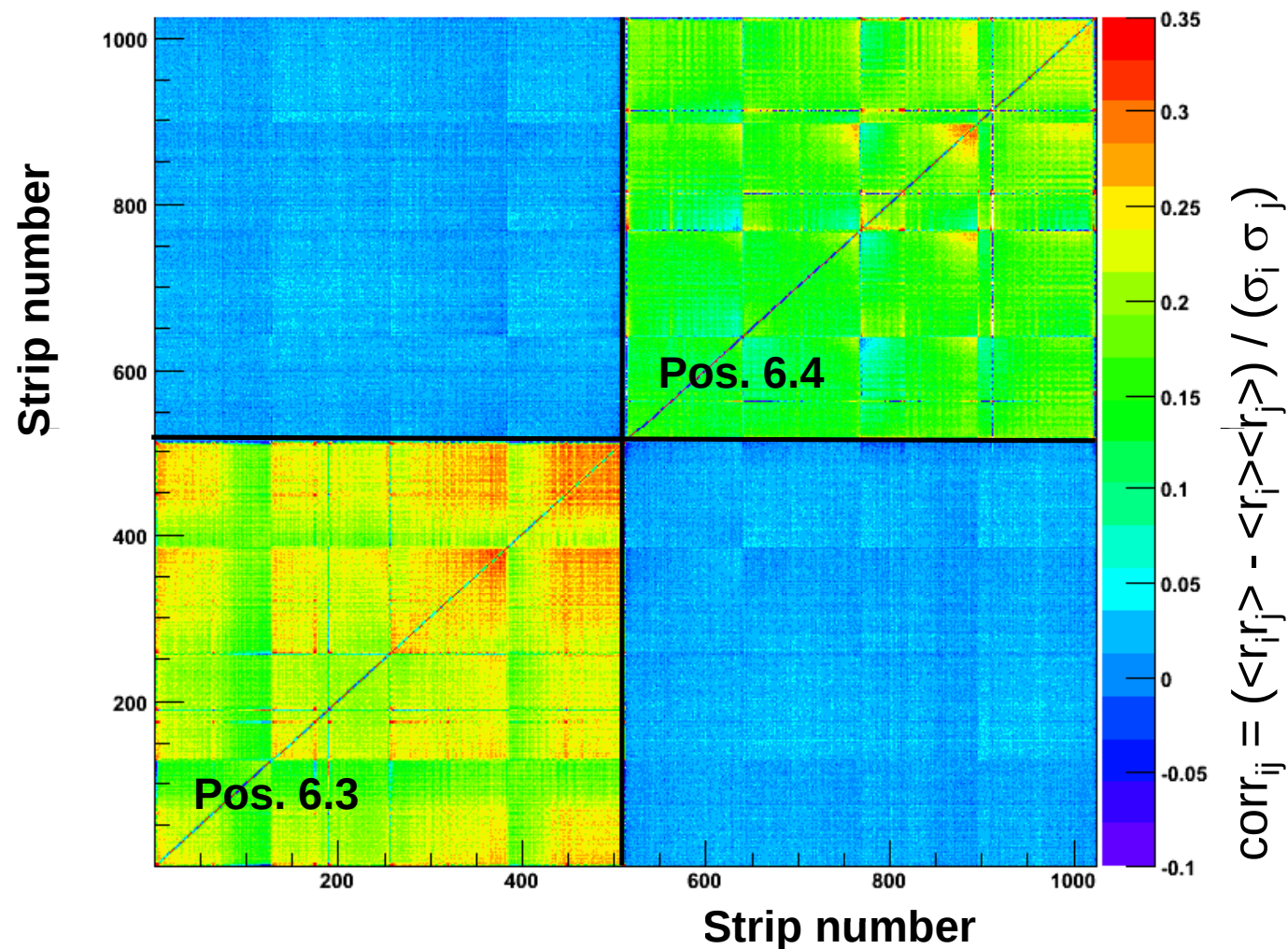



- correlated noise within each module
- no correlation between modules

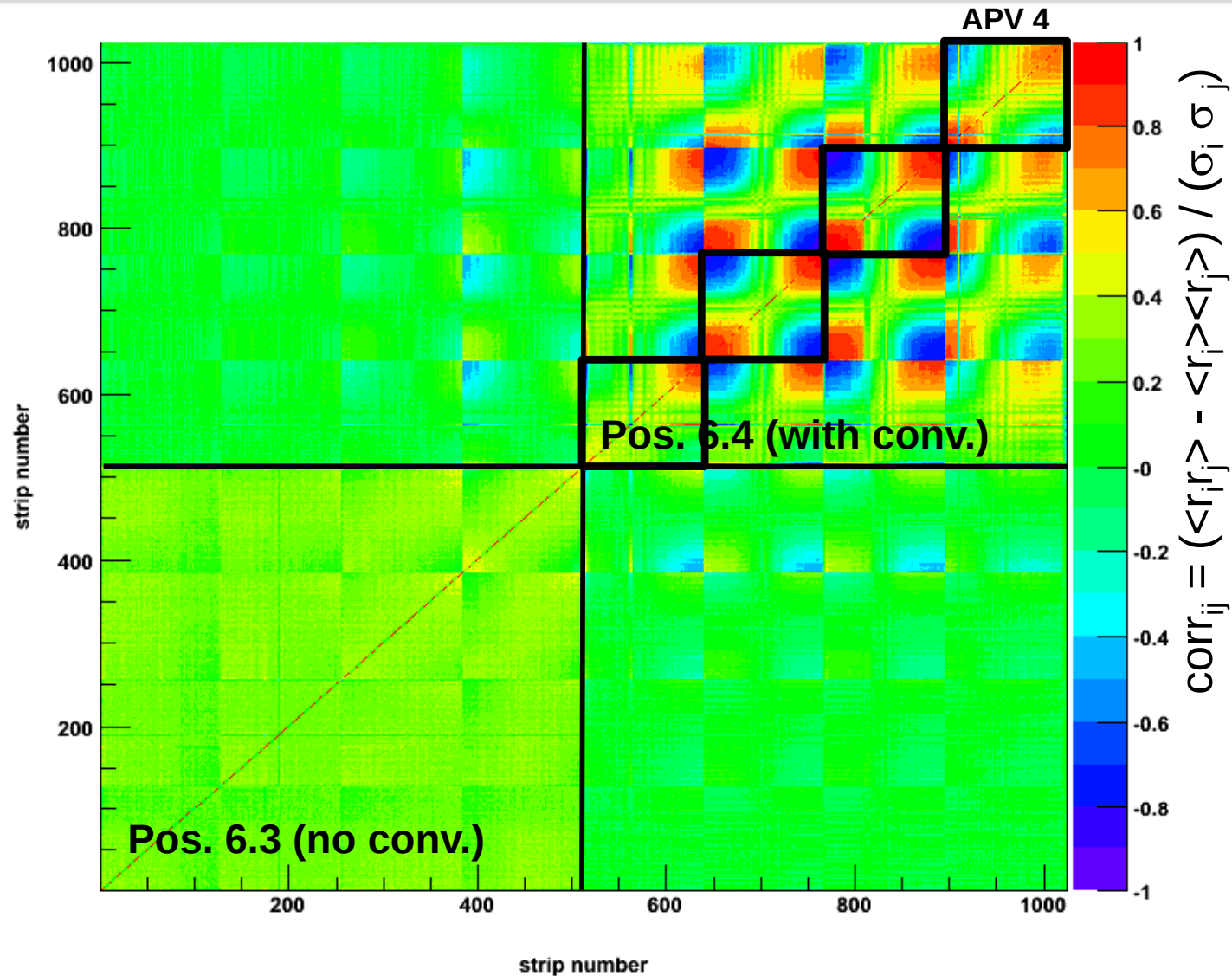Channel-to-channel Correlation with Air-core Coils




- left and right side of each APV are strongly anti-correlated
→ linear common mode with slope changing event-by-event
- correlated noise also on neighboring module

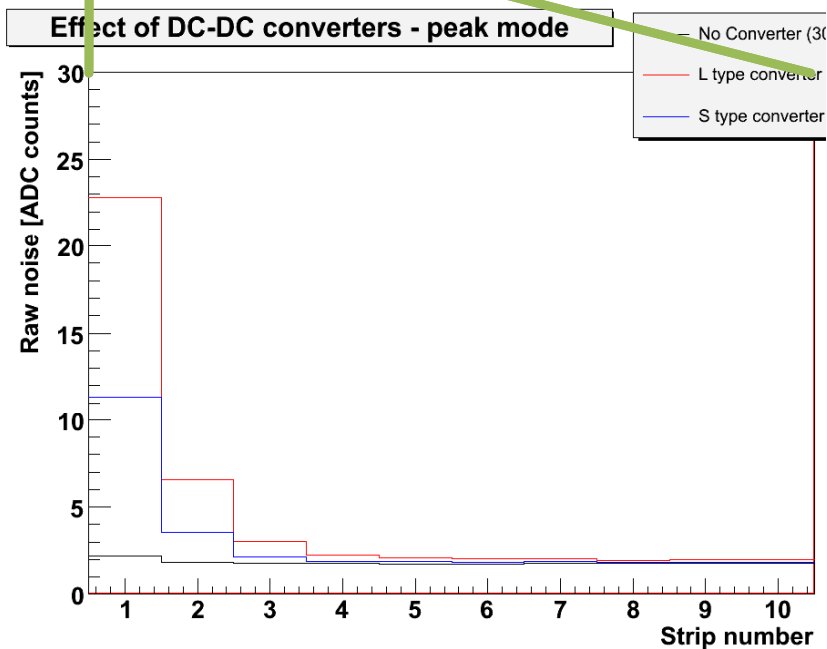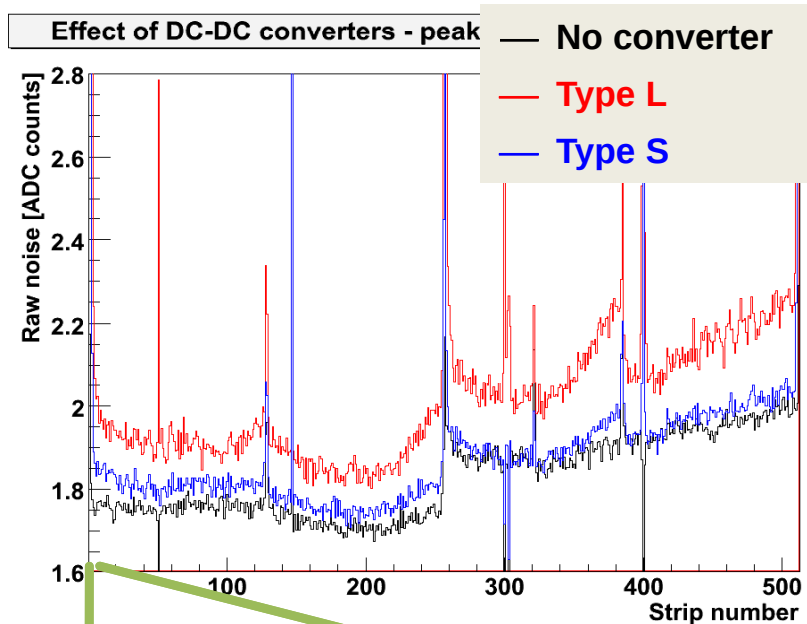APV Lesson 1: on chip common mode subtraction





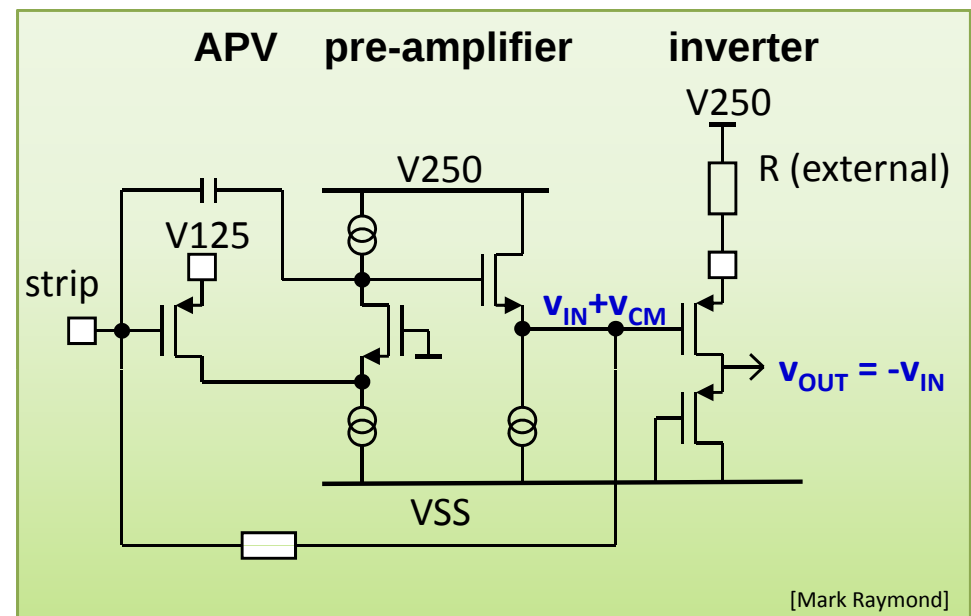- APV contains on-chip common mode noise subtraction
- there can be more common mode noise than the output data show
- output for irregular channels is affected by this common mode subtraction:
 - un-bonded (low noise) channels become noisy
 - higher common mode on edge channels is not fully subtracted
- un-bonded channels indicate true common mode noise




APV Lesson 2: module edge strip noise

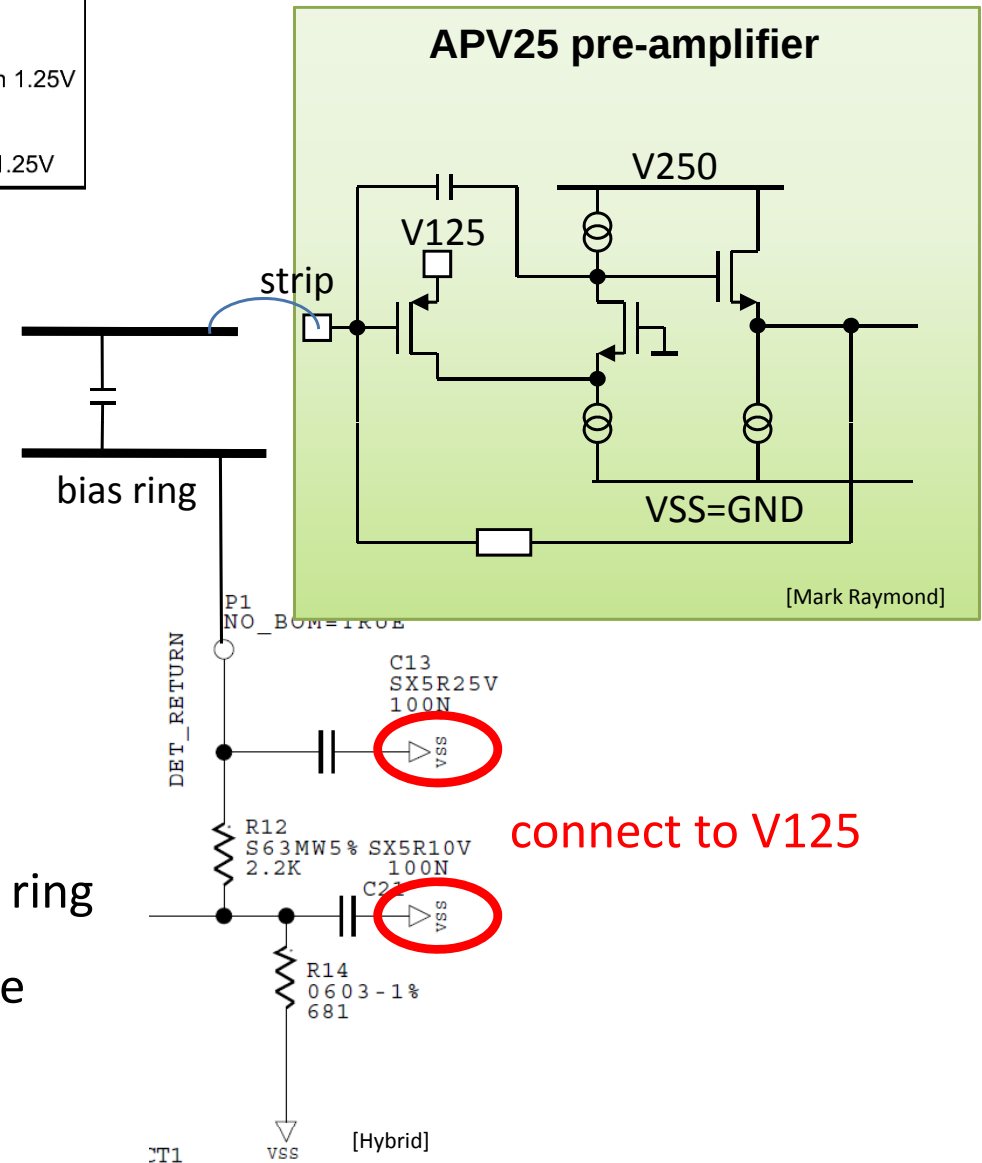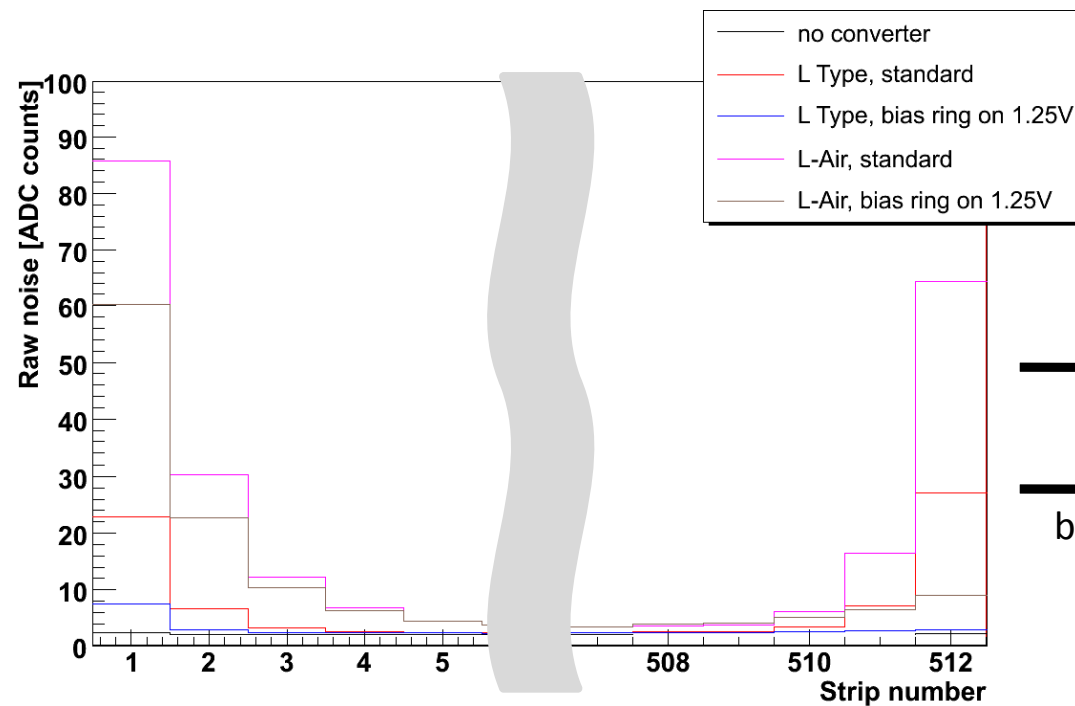- compare AC referencing of sensor bias ring to either GND or V125 on the hybrid





- module edge strips are noisier because of their capacitive coupling to the sensor bias ring which is AC referenced to hybrid GND in the current CMS tracker

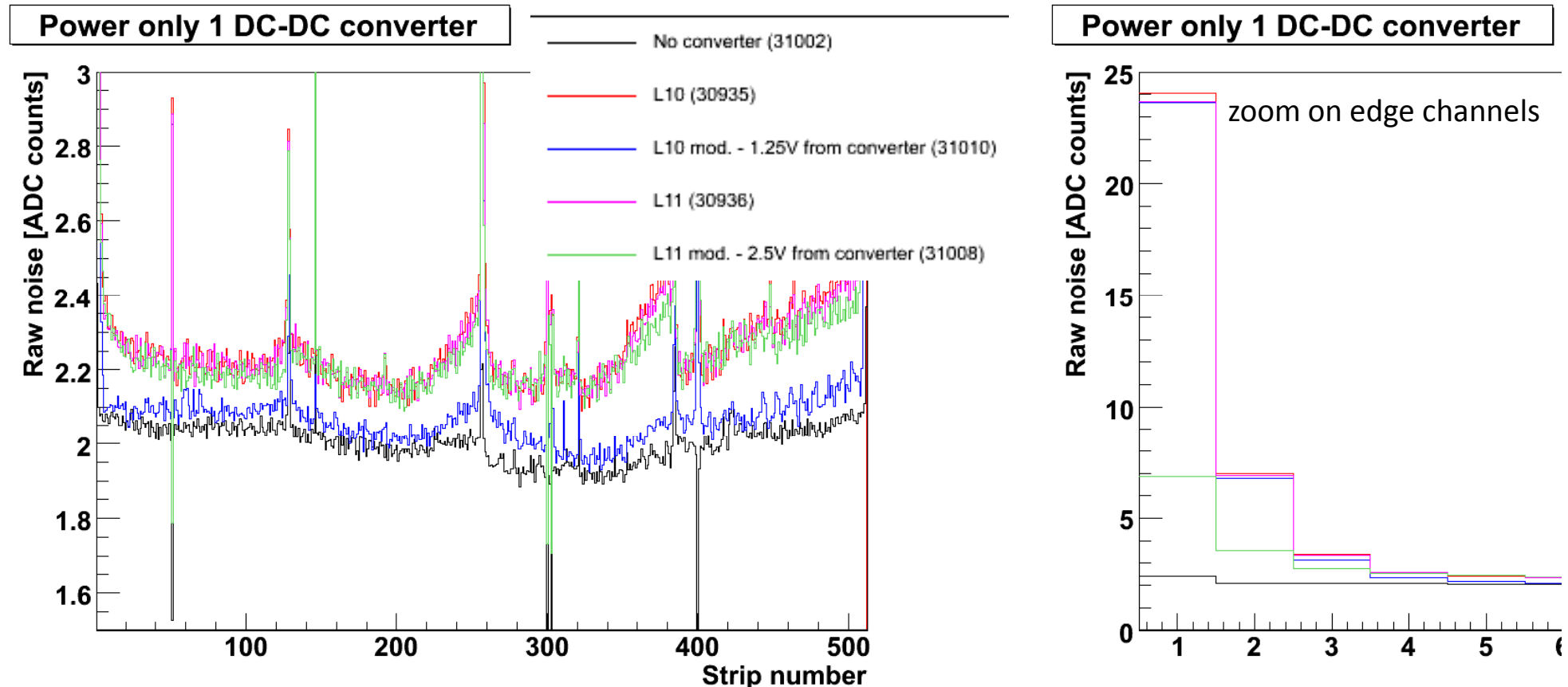APV Lesson 3: compare noise on 2.5 V and 1.25V line



- power via converter either on 1.25 V or 2.5 V line (other line powered normally)
- overall noise increase is caused by noise on 2.5 V line
explanation: noise on 1.25 V line affects mostly the input stage and will be strongly reduced by on chip common mode subtraction
- module edge strip noise most sensitive to 1.25 V line
explanation: APV lesson 2



Low Drop-Out Regulator

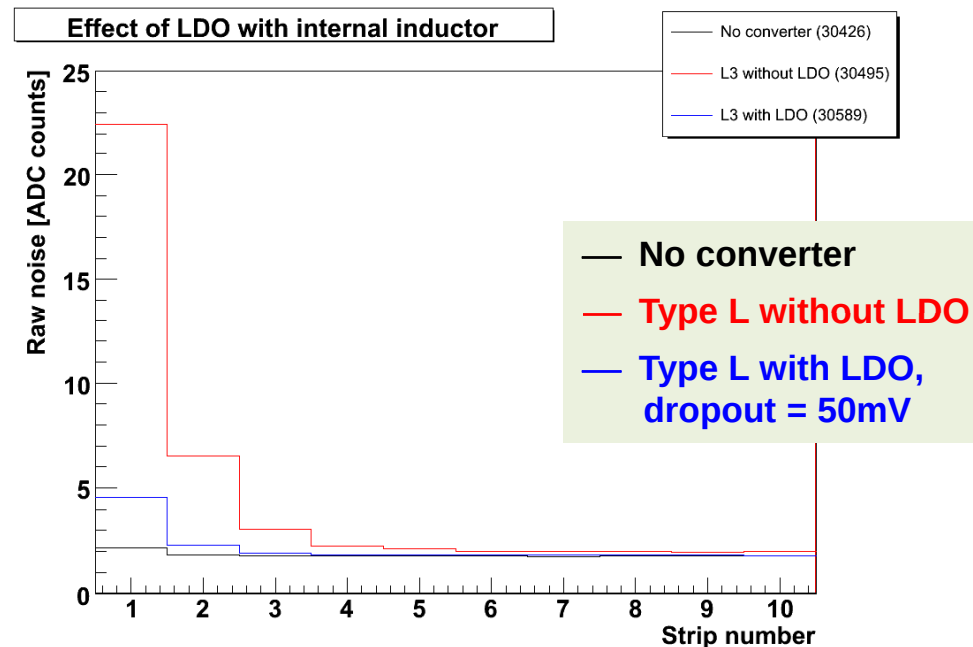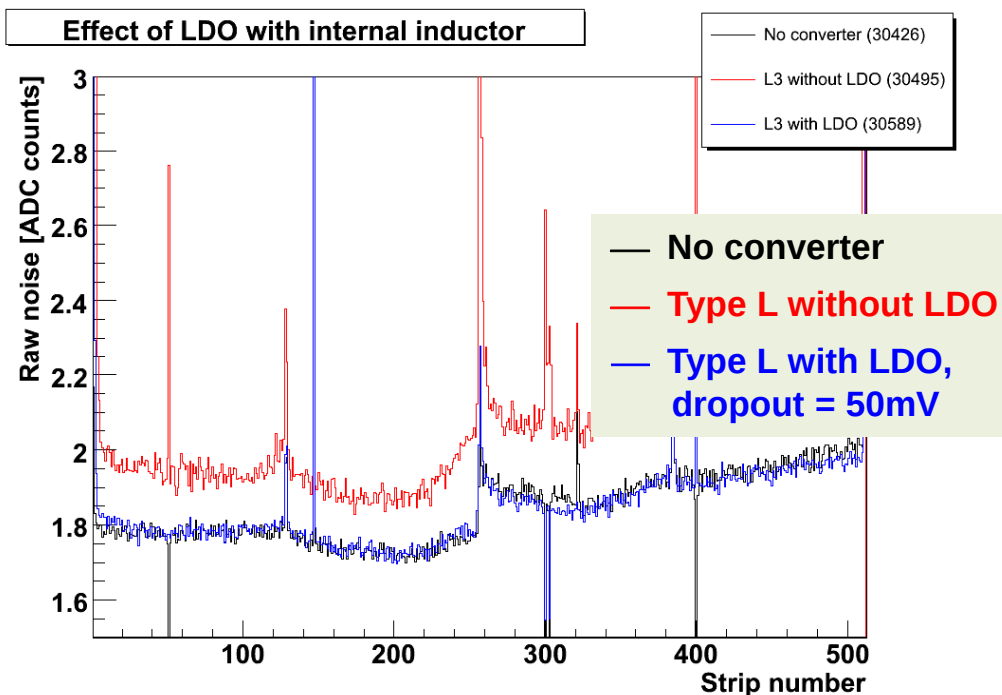

- measurements with ferrite core coils
- connect LDO regulator LTC3026 to output of EN5312QI DC-DC converter
- observation: with ferrite core inductors noise is mainly conductive and differential mode
- radiation hard LDO required




Radiative Interference

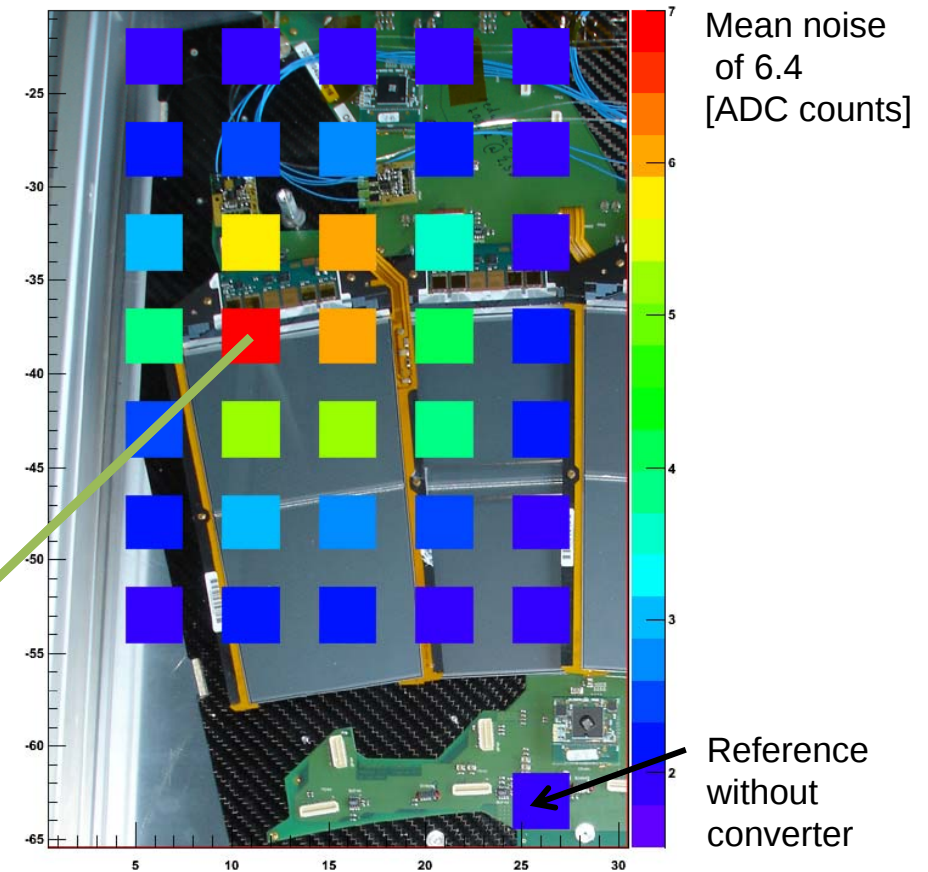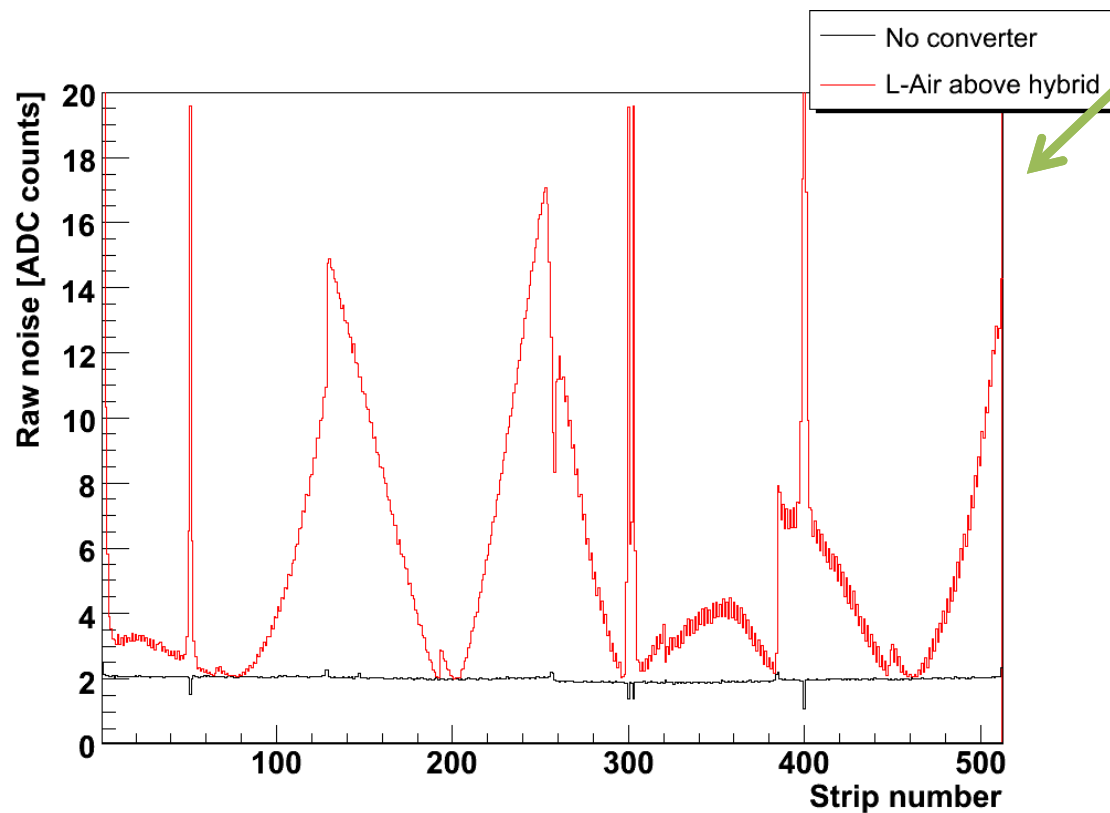- scan across petal with an air-core inductor converter (modules powered w/o converter)
- noise increase due to radiated EM fields, strongest interference close to hybrid




Shielding

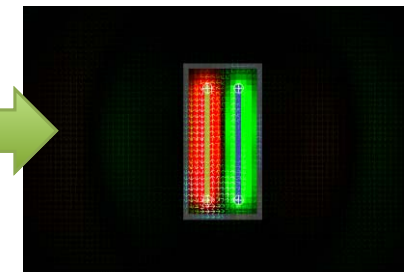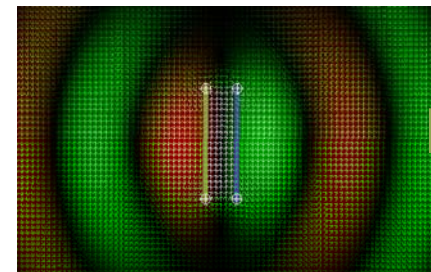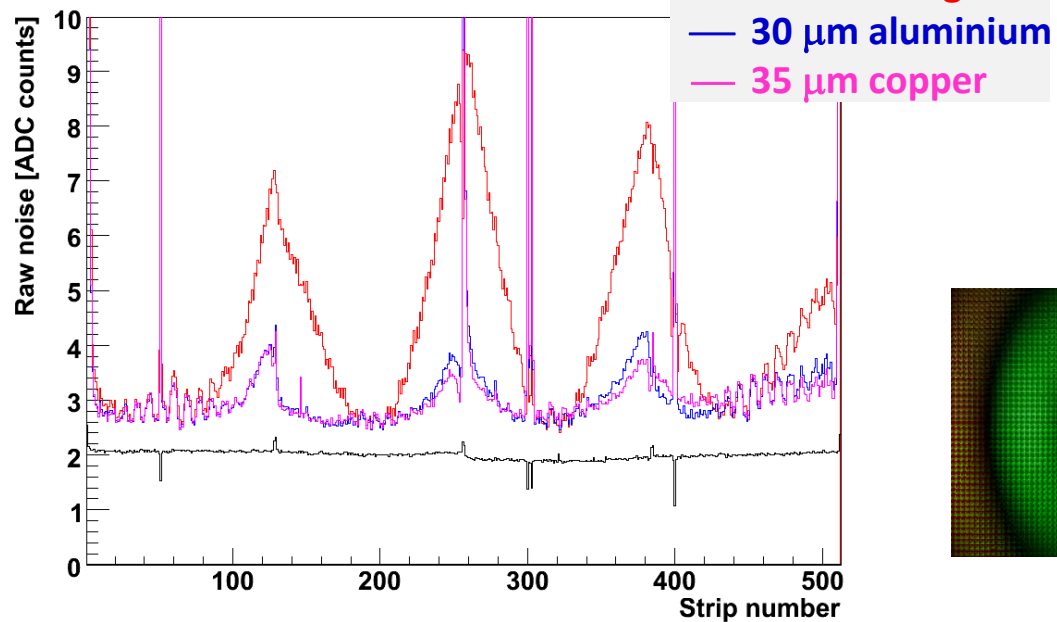Air-core inductor with aluminium and copper shielding



[<http://www.falstad.com/emwave2/>]


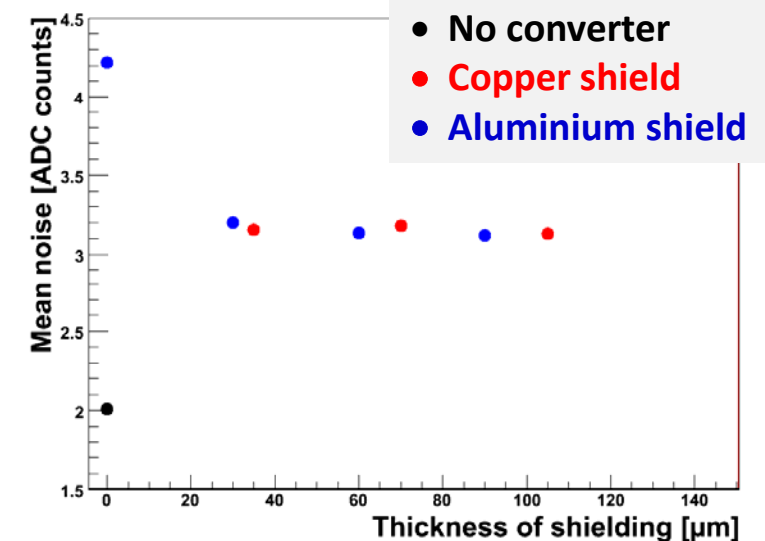
- radiative interference can be eliminated to a large extent by shielding the converter with 30 μm aluminium (no further improvement for thicker shield)
- contribution of 3x3x3cm³ box of 30 μm alum. for one TEC: 1.5kg (= 2 per mille of a TEC)



Converter Placement

- measurements with air core solenoids
- noise level depends strongly on distance between converter and hybrid

Type S' 4cm further away

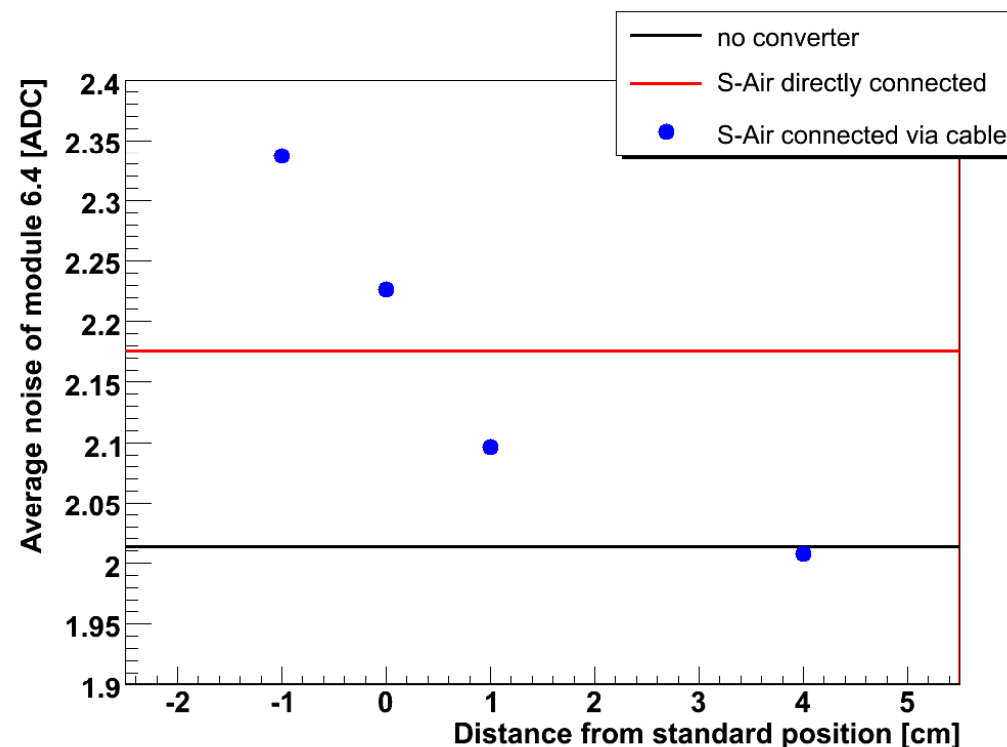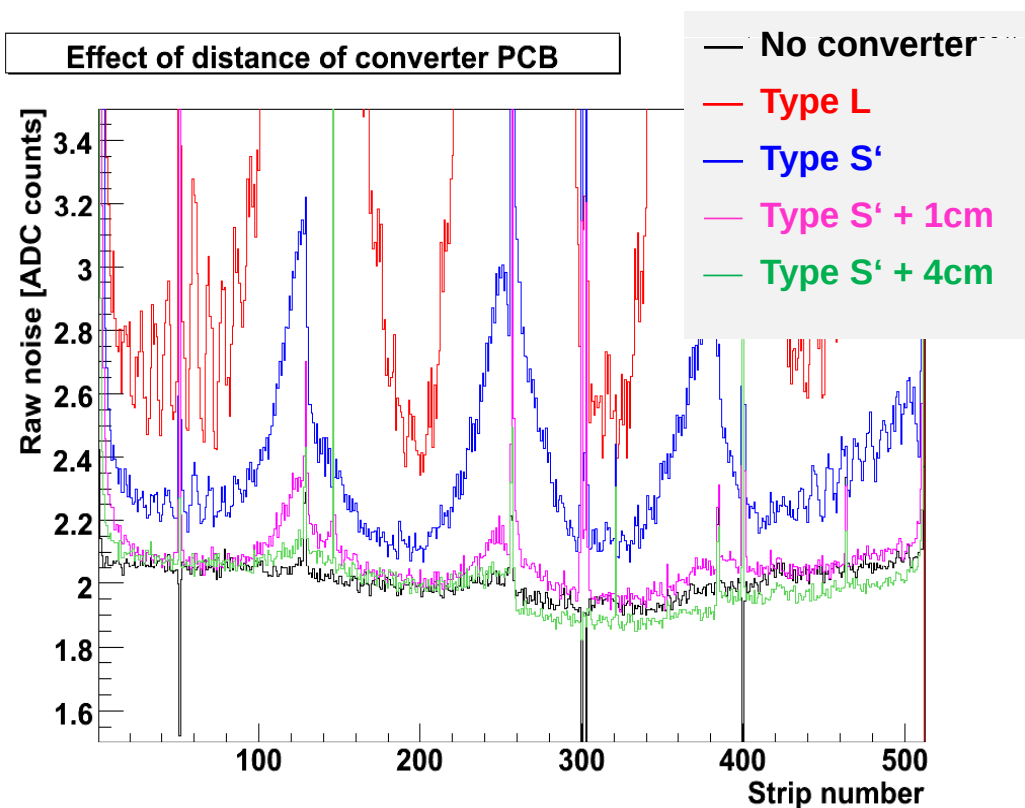


Toroid Inductors

Toroid wound from copper wire




Toroid wound from copper strip

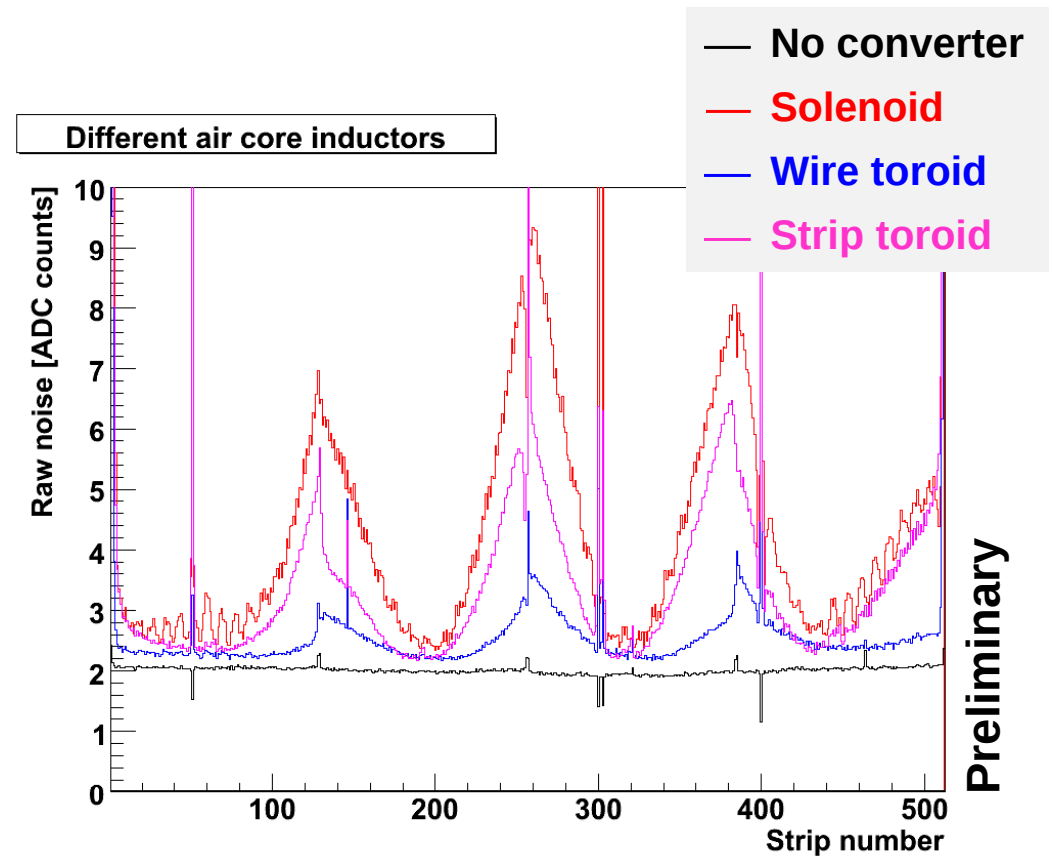

- toroid inductors may radiate less power
- nota bene: interference also depends on location of inductor
- Bristol group working on PCB based toroids

Optmizing the Converter

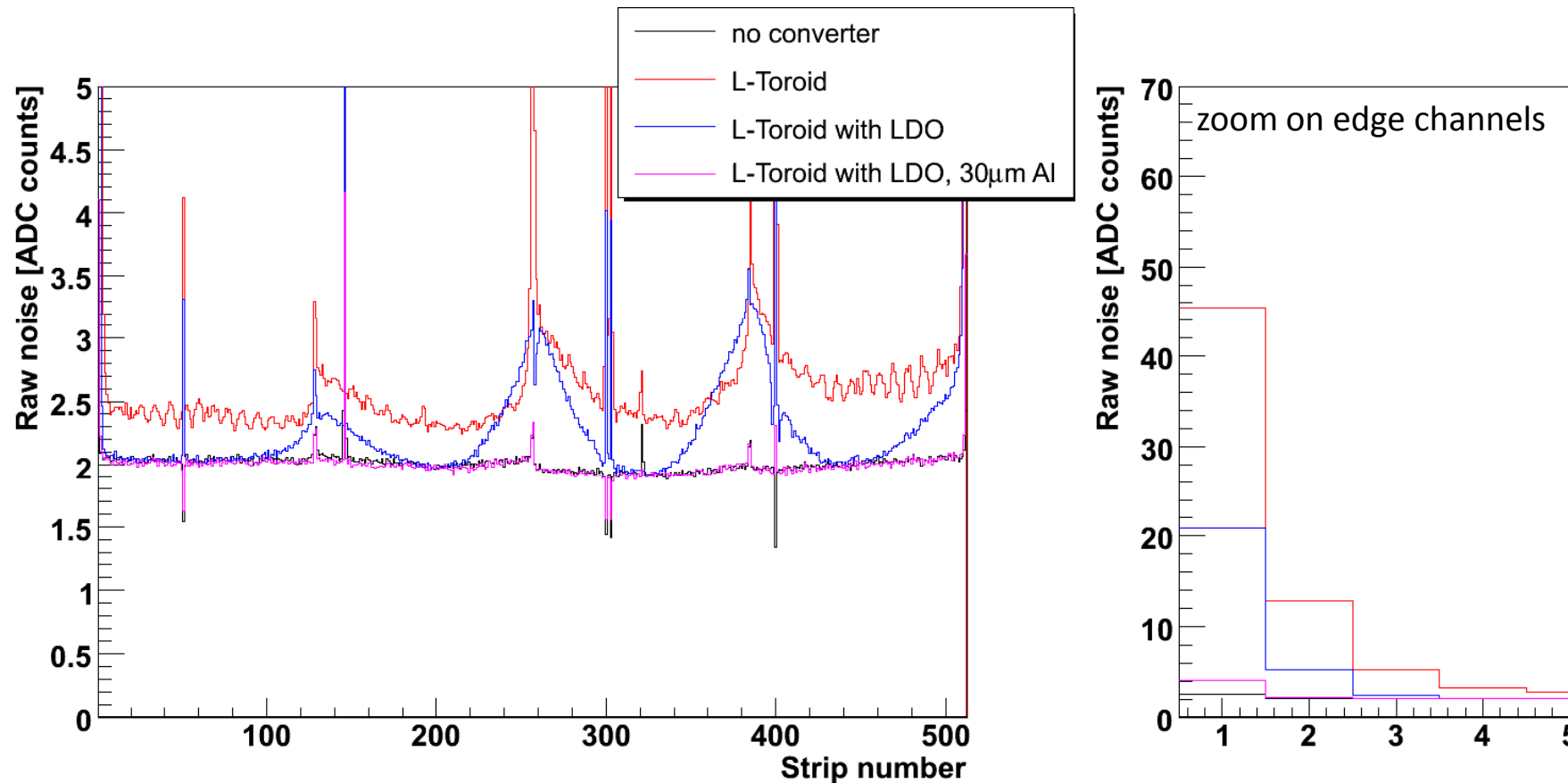

- Toroid: radiative and conductive noise
- Toroid with LDO: radiative noise
- Toroid with LDO and 30µm aluminum shield: hardly any noise increase (!)
- need to test solenoid with LDO and shielding

CERN Buck Converter

- collaboration with CERN PH-ESE group (F. Faccio et al.)
- CERN: ASIC development
RWTH: converter PCB, system tests

- first prototype “SWREG2”

(AMIS I3T80 0.35 μ m CMOS) received in August

[S. Michelis (CERN) et al., *Inductor based switching DC-DC converter for low voltage power distribution in SLHC, TWEPP 2007.*]



$$V_{in} = 3.3 - 20V$$

$$V_{out} = 1.5 - 3.0V$$

$$I_{out} = 1 - 2A$$

$$f_s = 250kHz - 3MHz$$

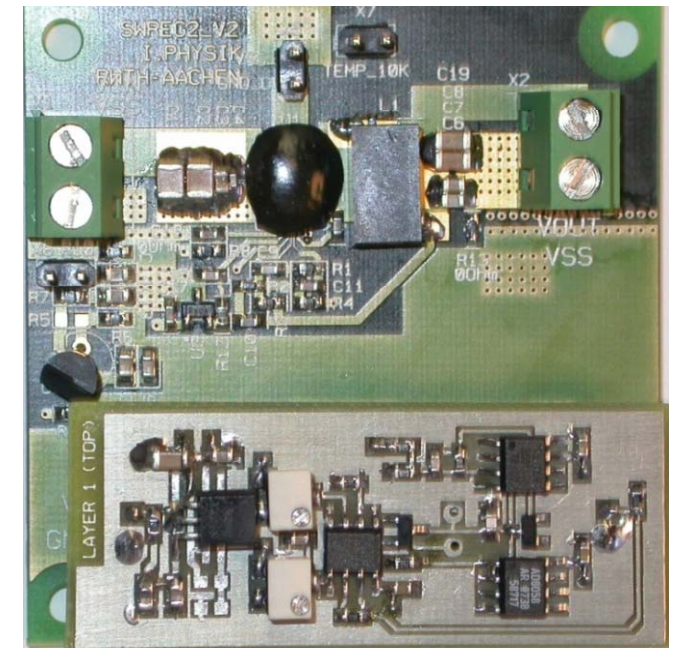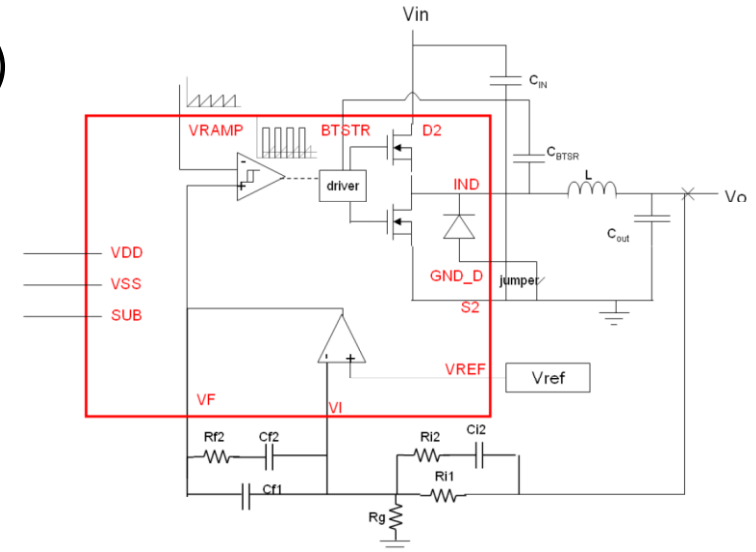
- rad-hard to X-rays, but not to charged particles
→ CERN looking into more rad-hard designs/processes
- first system test results



System Tests with SWREG2

- PCB with air-core coil, but located far away from module $\Rightarrow$ noise is conductive
- SWREG2 provides 2.5V to chips, 1.25V taken from ICB motherboard
- $V_{in} = 5.5V$

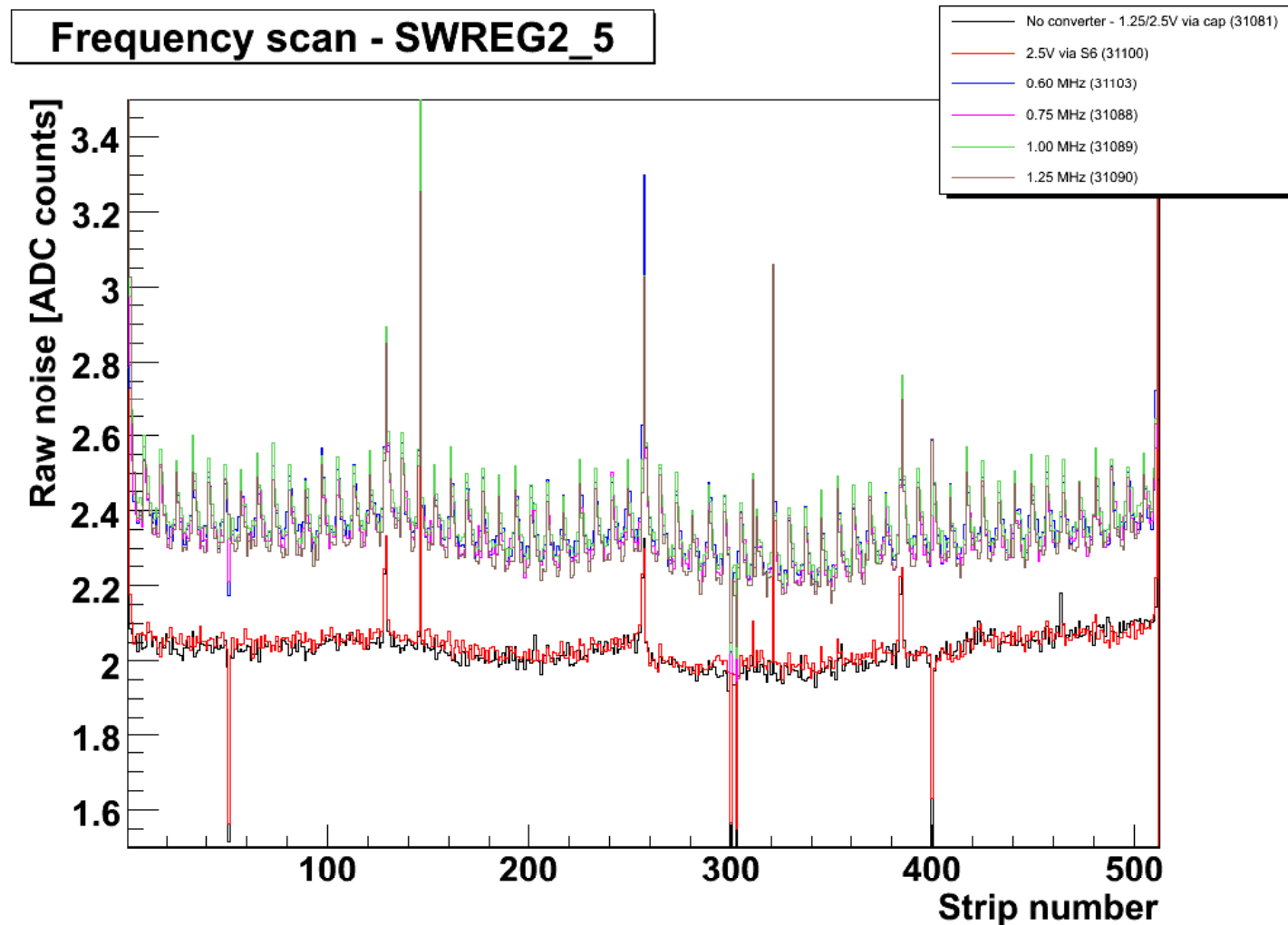- 15% noise increase
- sawtooth structure introduced by APV multiplexing (APV Lesson 4)
- noise performance not satisfactory






Capacitor Based DC-DC Converter

- **LBNL Charge Pump:** $n = 4$ prototype IC in $0.35\ \mu\text{m}$ CMOS process (H35) with external $1\ \mu\text{F}$ flying capacitors (0.5A, 0.5MHz)





[P. Denes, R. Ely and M. Garcia-Sciveres (LBNL), *A Capacitor Charge Pump DC-DC Converter for Physics Instrumentation*, submitted to IEEE Transactions on Nuclear Science, 2008.]

- noise performance not satisfactory

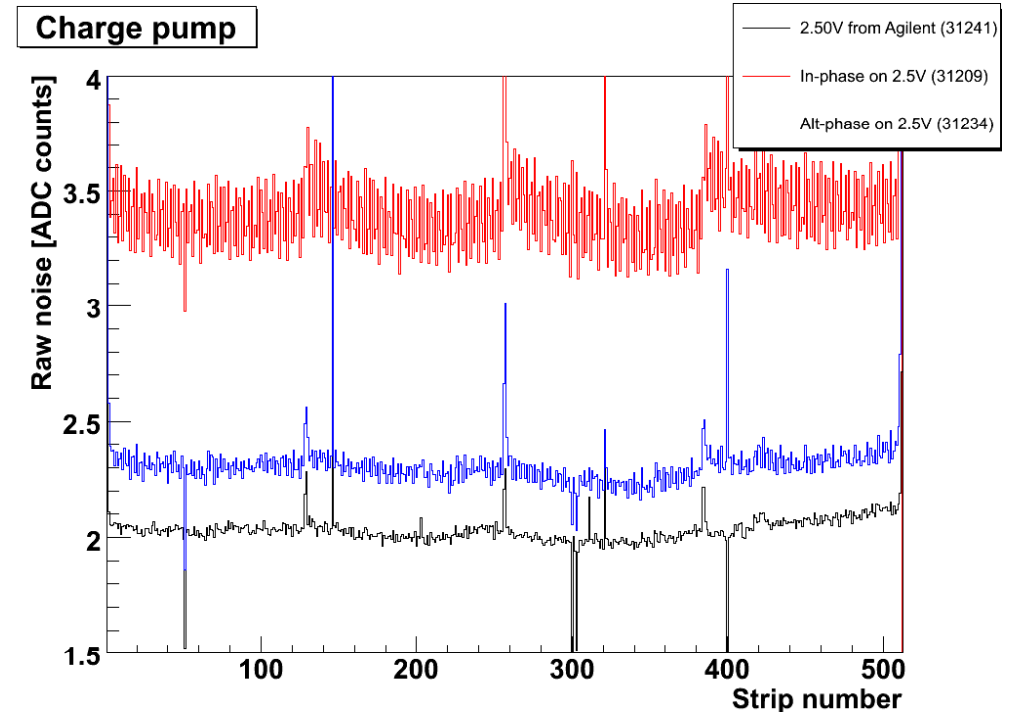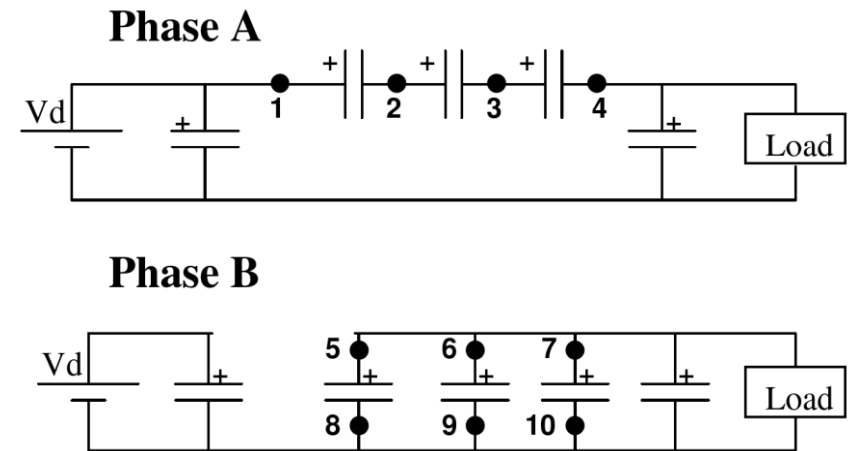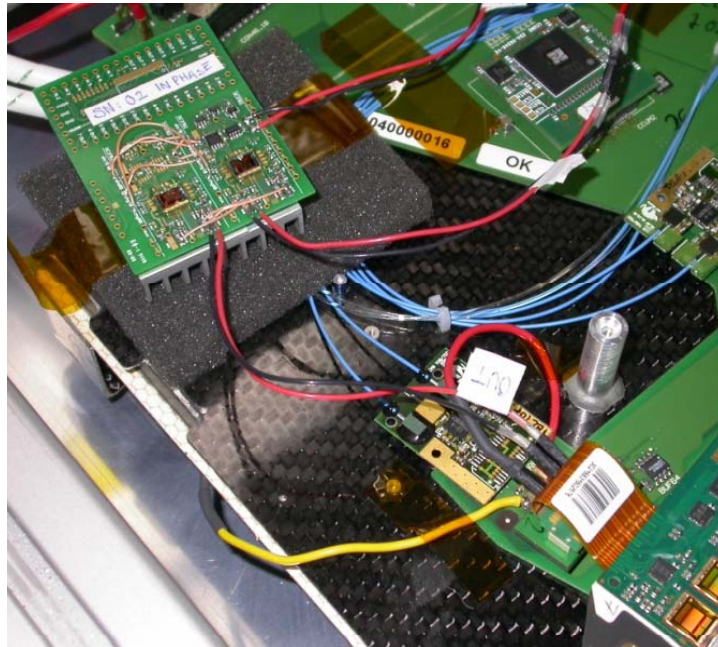

EMI Test Stand

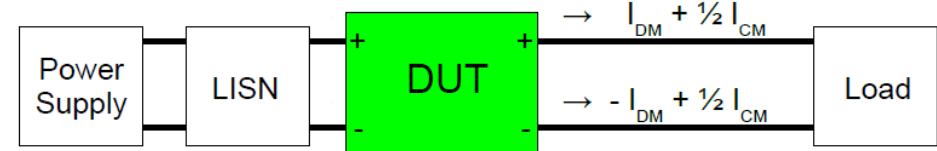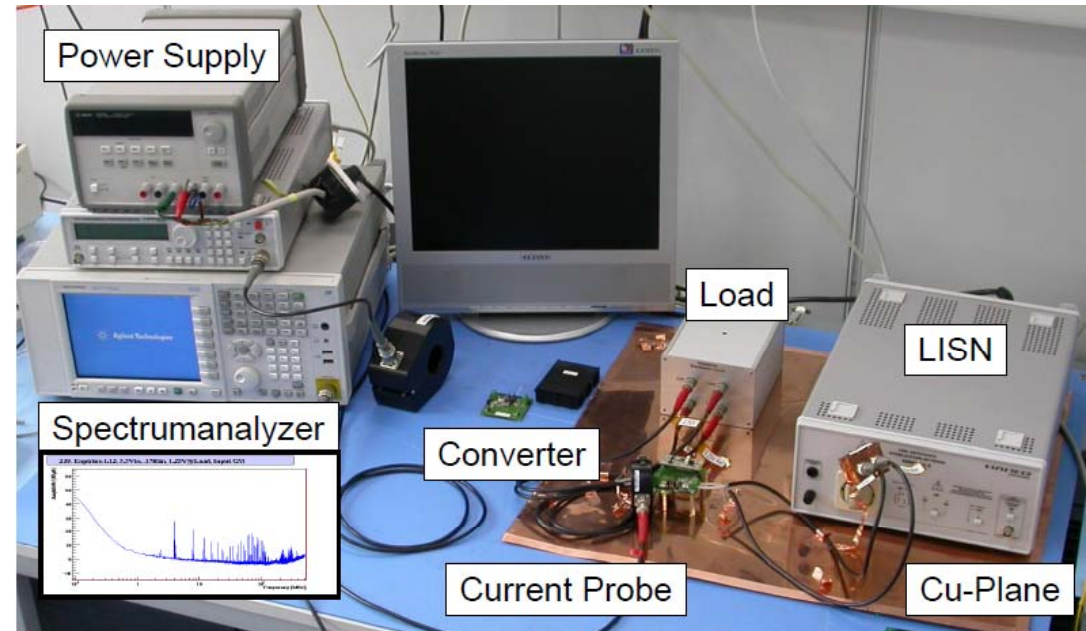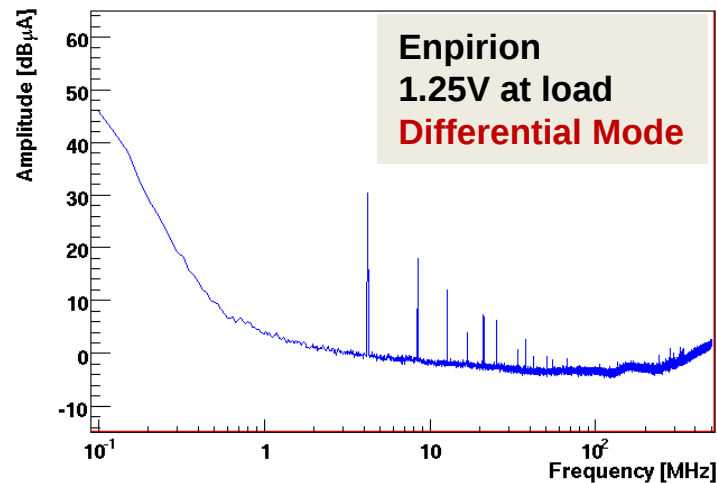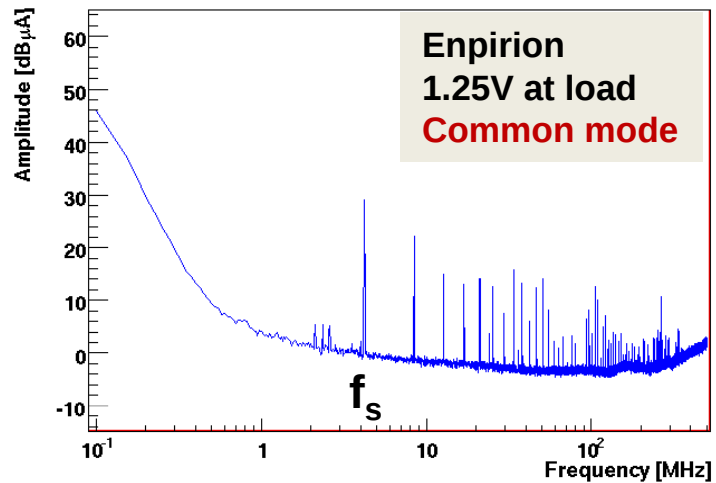Standardized EMC set-up to measure **Differential & Common Mode** noise spectra (similar to set-up at CERN)



CM-Setup:

$$I_{DM} + \frac{1}{2} I_{CM} - I_{DM} + \frac{1}{2} I_{CM} = I_{CM}$$

Current Probe $\rightarrow$
Spectrum analyzer

The diagram shows a current probe connected to a wire. The equation shows that the common mode current I_{CM} is measured by the current probe.

DM-Setup:


$$I_{DM} + \frac{1}{2} I_{CM} - (-I_{DM} + \frac{1}{2} I_{CM}) = 2 \cdot I_{DM}$$

Current Probe $\rightarrow$
Spectrum analyzer

The diagram shows a current probe connected to a wire. The equation shows that the differential mode current $2 \cdot I_{DM}$ is measured by the current probe.



Differential Noise Injection into Power Lines

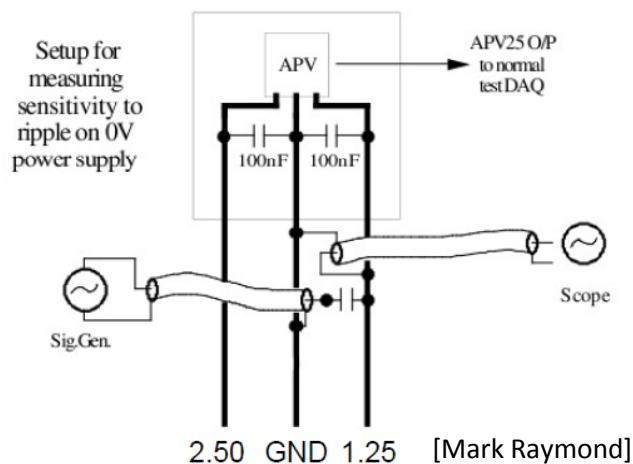Example configuration for 1.25V ripple injection



1.25V Injection:
→ 100mV_{PP}


Mean raw noise of 2nd APV

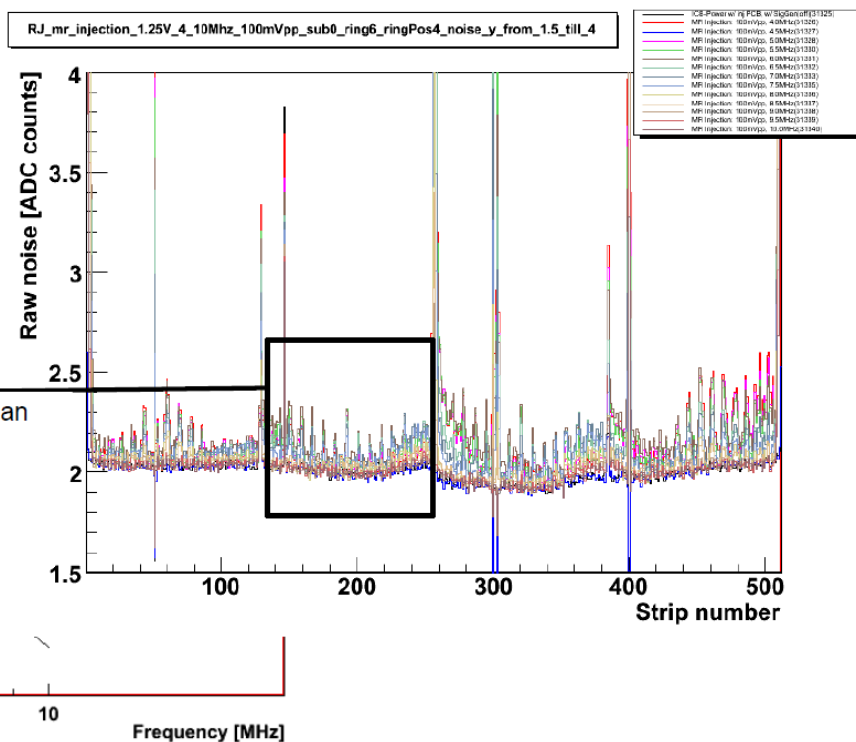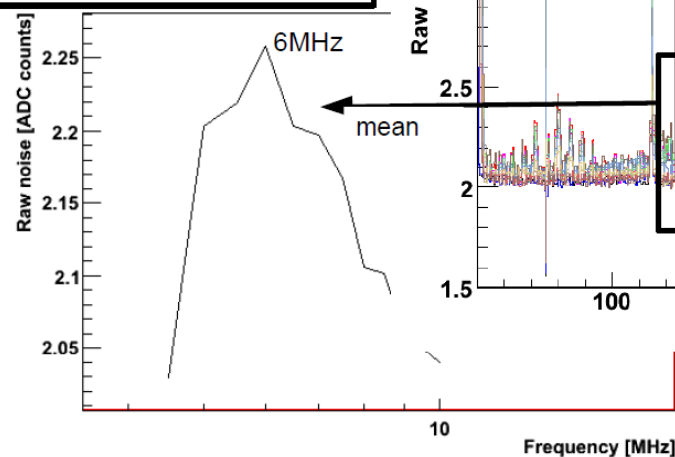


- inject differential noise into 1.25 V line via capacitor
- modules on a petals appear to be most sensitive to noise around 6 MHz
- similar result for injection into 2.5 V line

Frequency Spectrum vs. Noise


Effect of DC-DC converters - peak mode

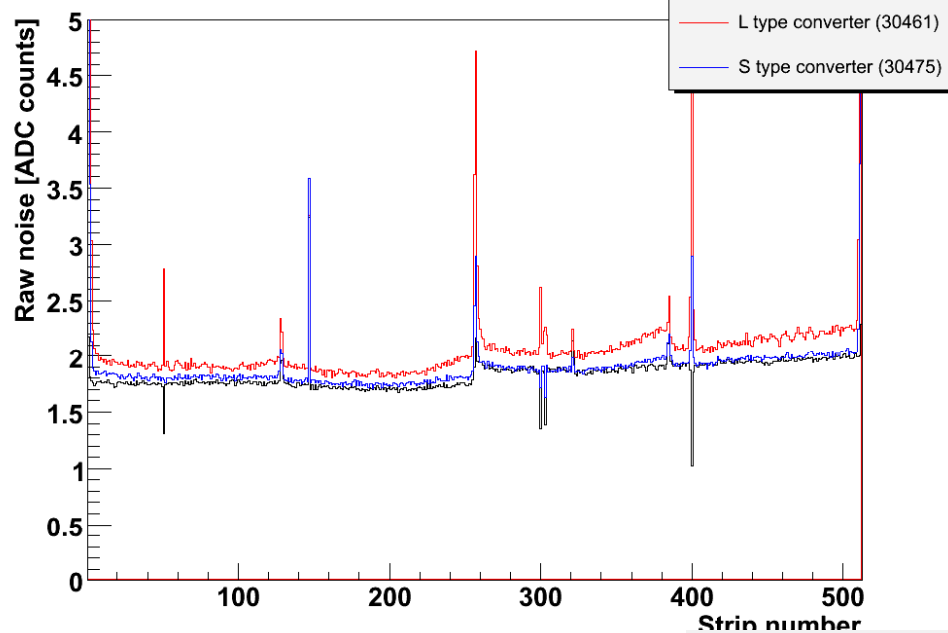

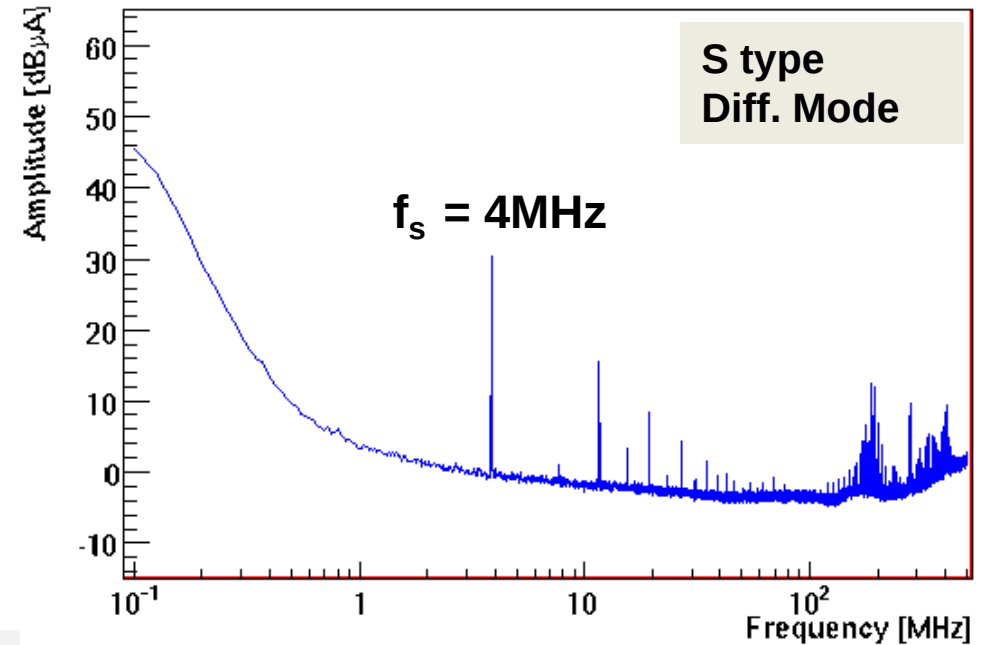
530. Enpirion S2, 5.5Vin, .306lin, 2.50V@Load, Output DM



Frequency scan - SWREG2_5

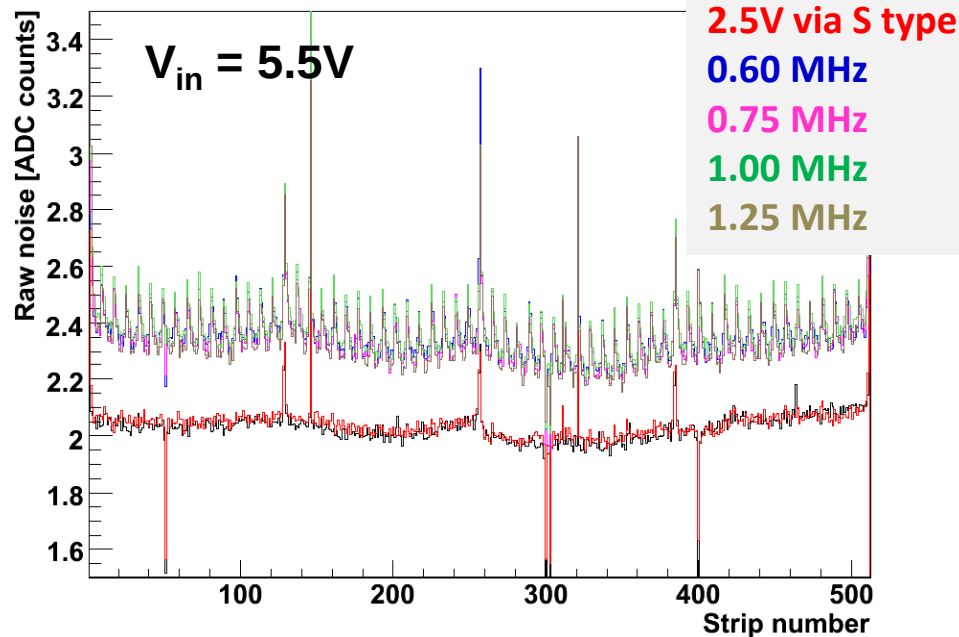


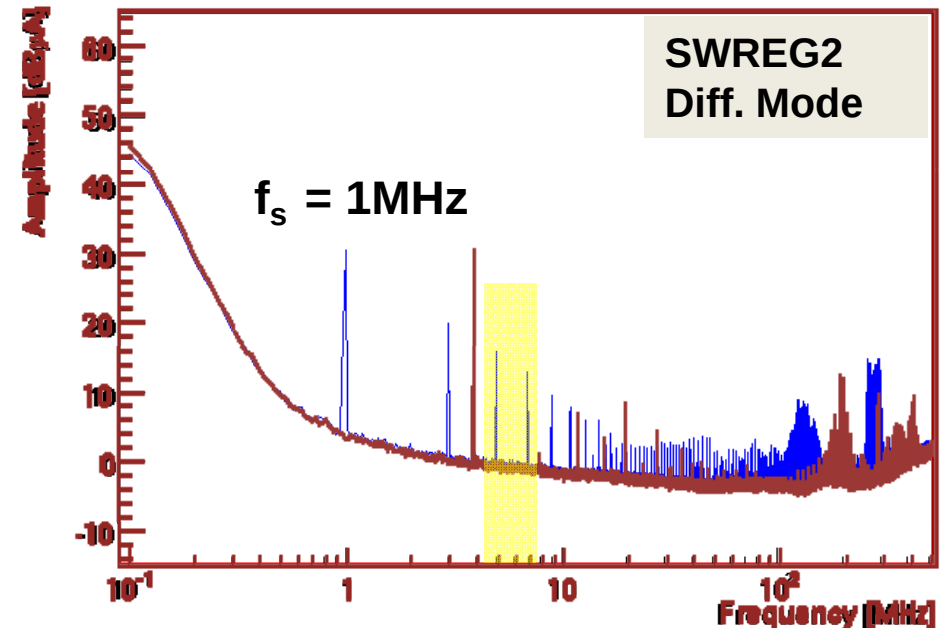530. Enpirion S2, 5.5Vin, .306lin, 2.50V@Load, Output DM










Possible Power Distribution of a SLHC Tracker Sub-Structure

- n:1 conversion at edge of sub-structure using buck converter
 - seems feasible from EMI point of view
 - power loss in supply cables decreased by factor $n^2 * (\text{conversion efficiency})^2$
- additional 2:1 conversion at each module/FE-ASIC would further decrease cable losses and allow for reduction of copper on sub-structure ICB
 - for buck converter EMI might be tolerable with shielding and LDO
 - charge pump ?

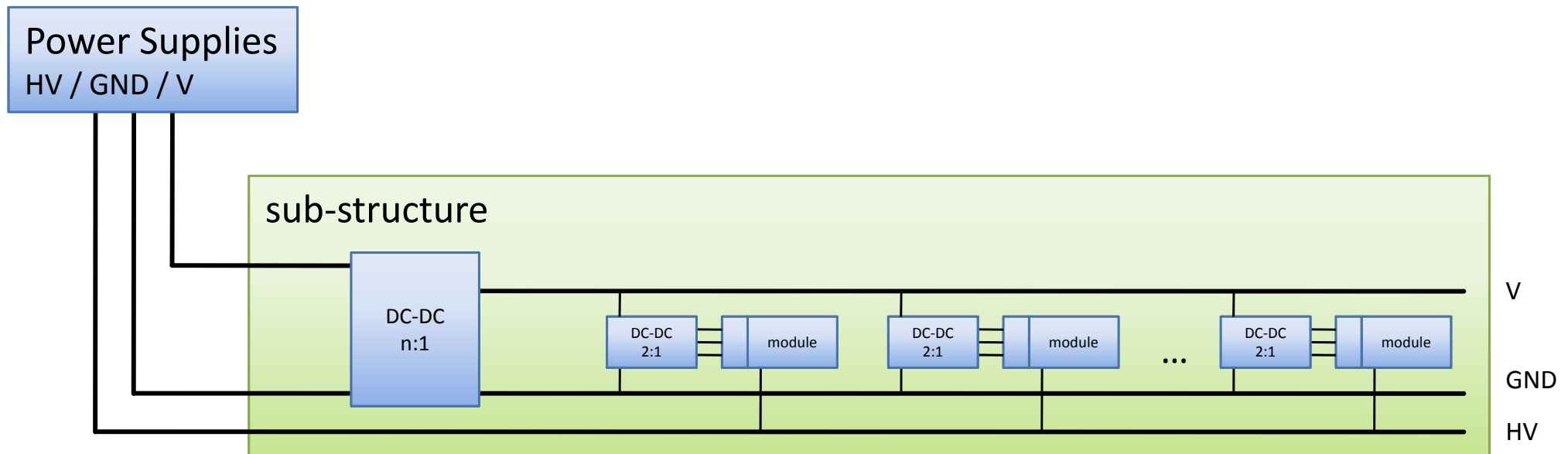

Material Budget

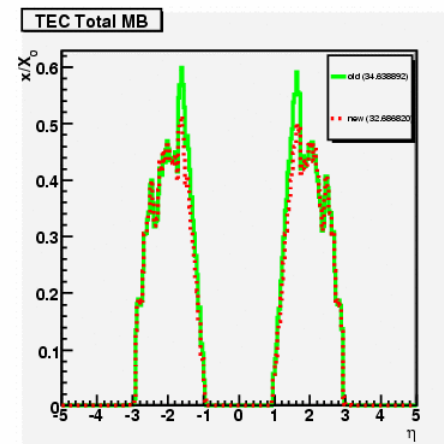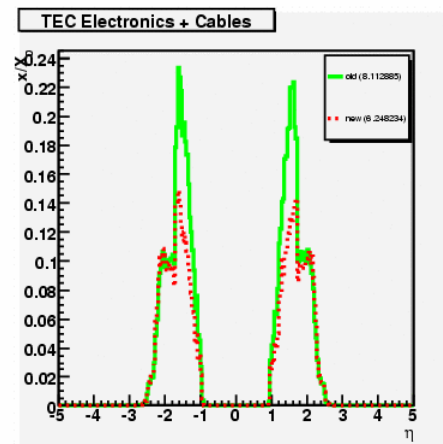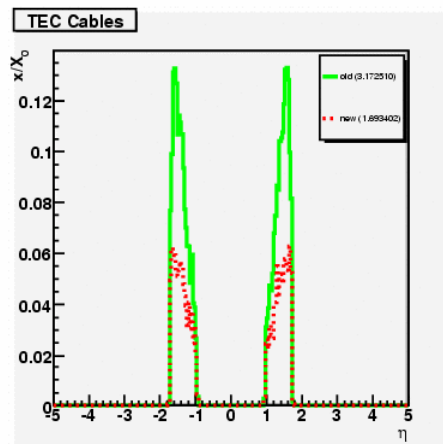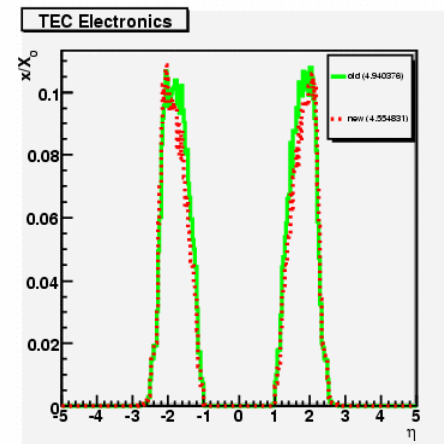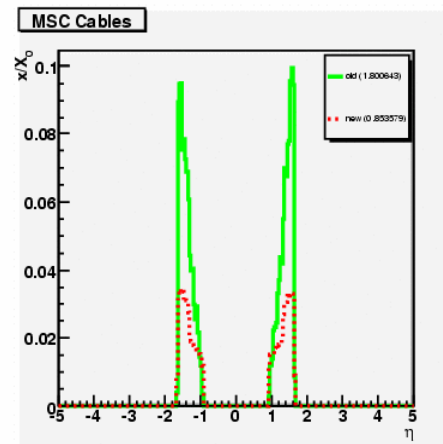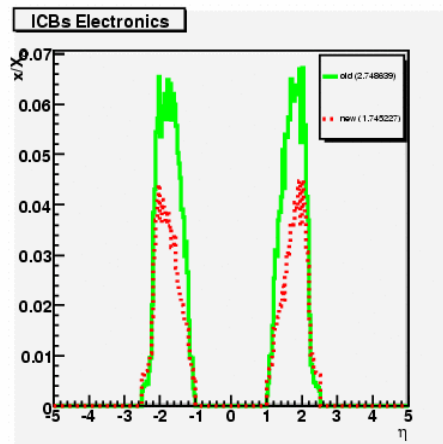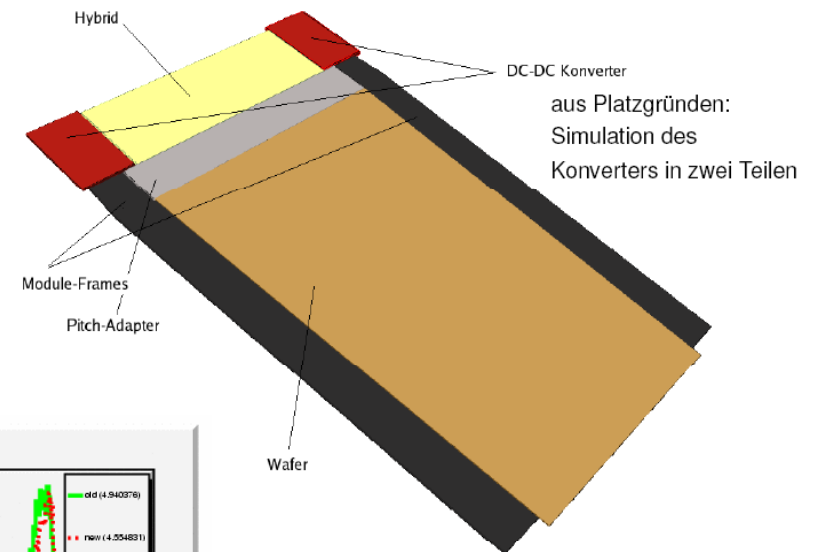- implement changes to material budget into Geant4 model of current tracker (so far only TEC considered)
- in this example one 10:1 converter per module: total TEC material budget reduced by 5.6%



Summary

- novel powering schemes are mandatory for SLHC tracker
- DC-DC conversion offers required supply currents while keeping system layout simple
- system test measurements with DC-DC converters have been performed
- many symptoms in current test system are due to actual APV25 (and hybrid) layout
 - might be different for the SLHC FE ASIC
 - some understanding achieved
- switching noise of buck converters can be controlled even with air core inductors when converter is not too close to FE hybrid and/or shielded
- radiation hard switch still to be developed

- gain better understanding of correspondence between converter noise spectra and noise induced into the modules
- optimize buck converter by improved inductor and shielding design
- evaluate “interleaved buck converter”
- develop radiation hard converter ASIC (CERN)
- further tests of charge pumps
- follow closely the developments on serial powering