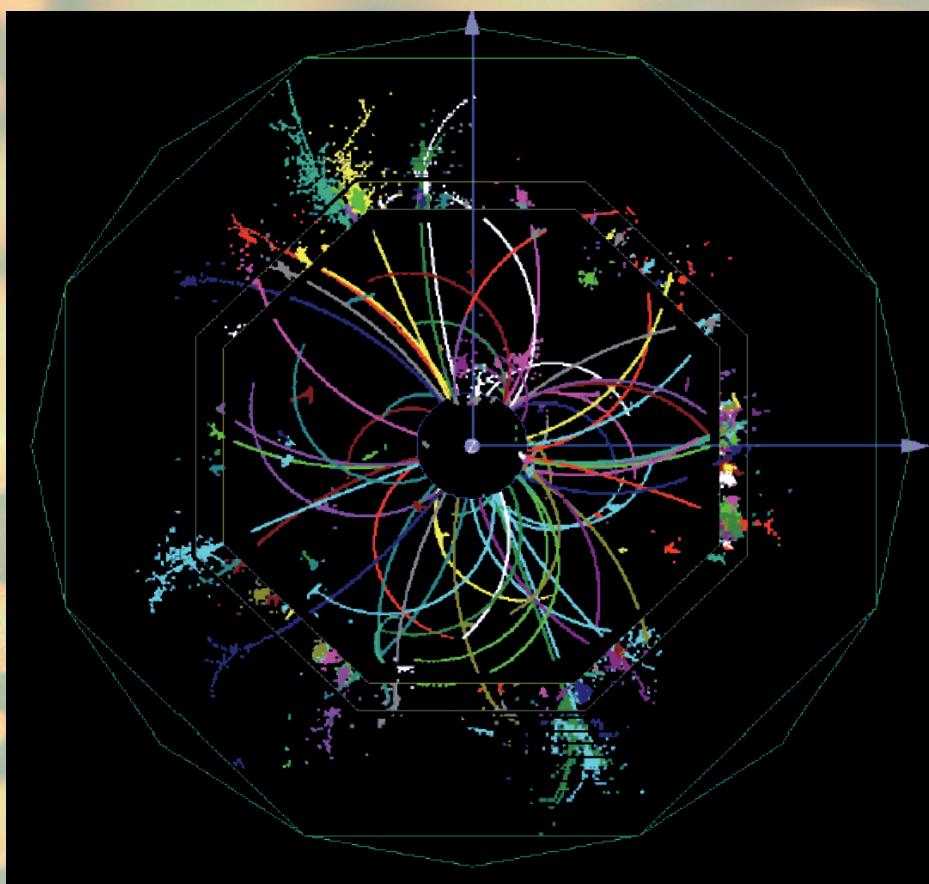


# Omega



Electronics  
in particle  
physics

EDIT school  
CERN 2011



C. de LA TAILLE

IN2P3

Taille@lal.in2p3.fr

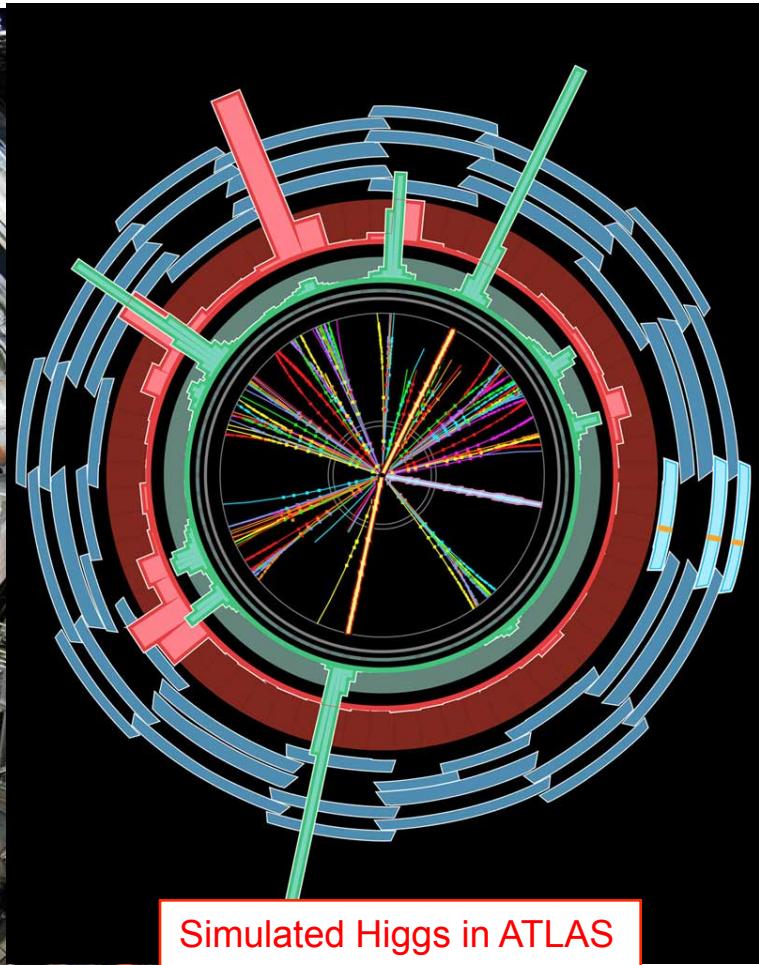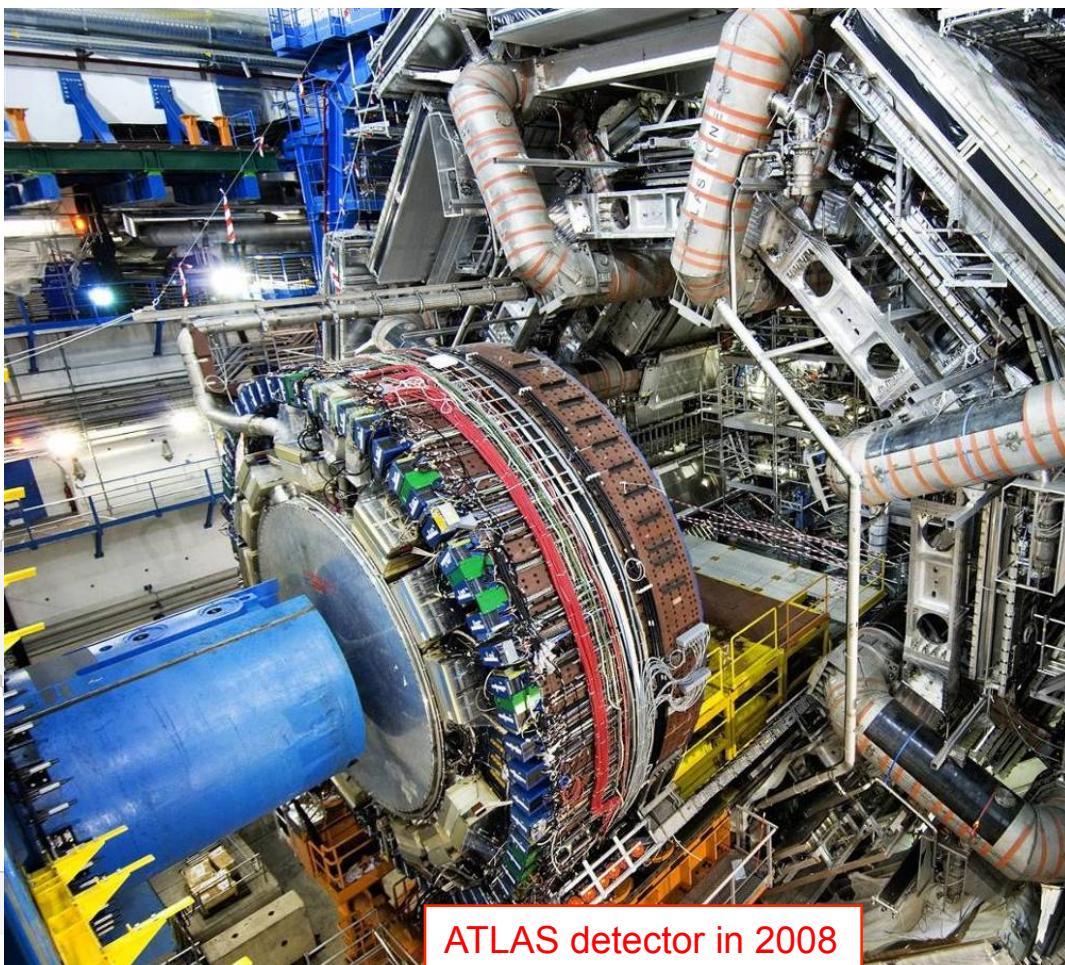
## Electronics in experiments

- A lot of electronics in the experiments...
  - The performance of electronics often impacts on the detectors
  - Analog electronics (V,A,A...) / Digital electronics (bits)



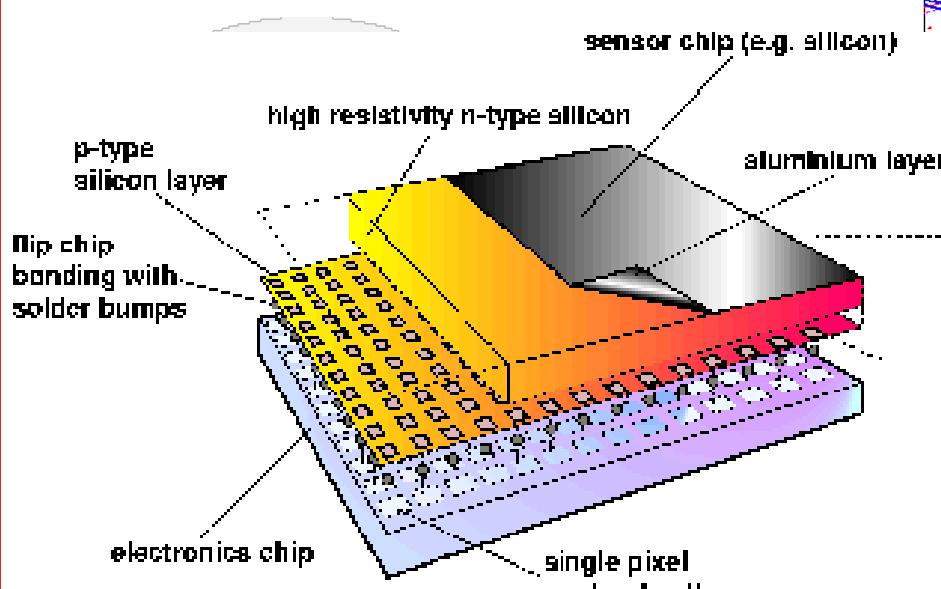
# Electronics enabling new detectors : trackers


- Measurement of (charged) particle tracks
  - millions of pixels ( $\sim 100 \mu\text{m}$ )
  - binary readout at 40 MHz
  - High radiation levels
  - Made possible by ASICs



Pixel detector and readout electronics

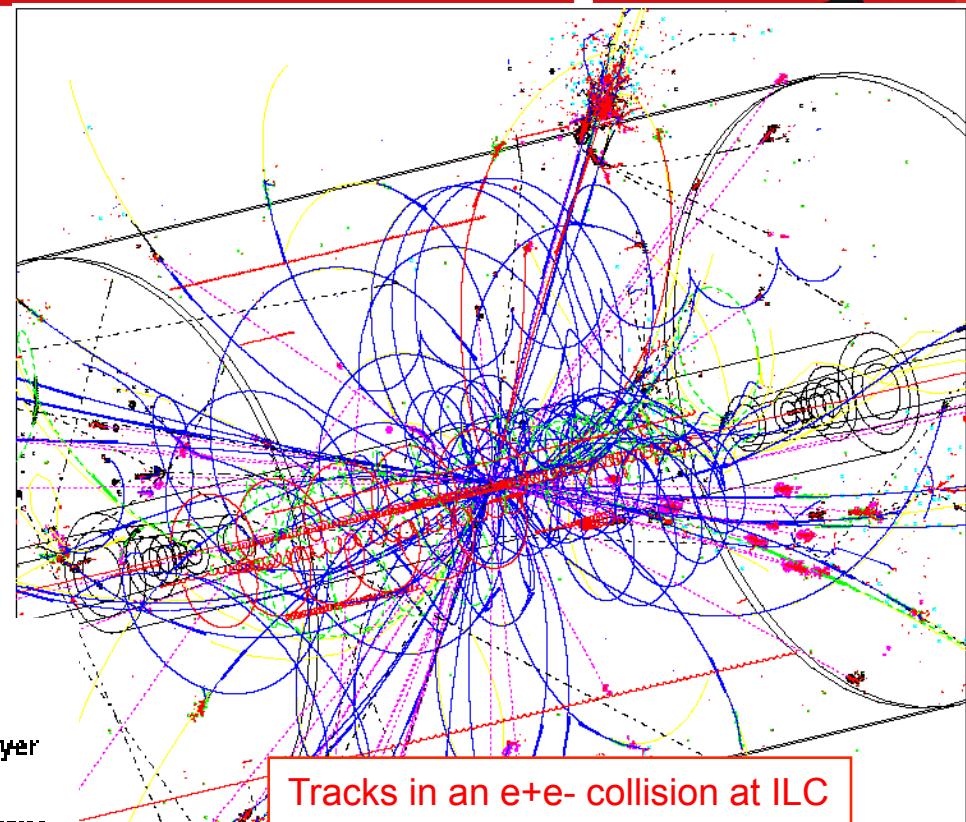

Tracks in an e+e- collision at ILC



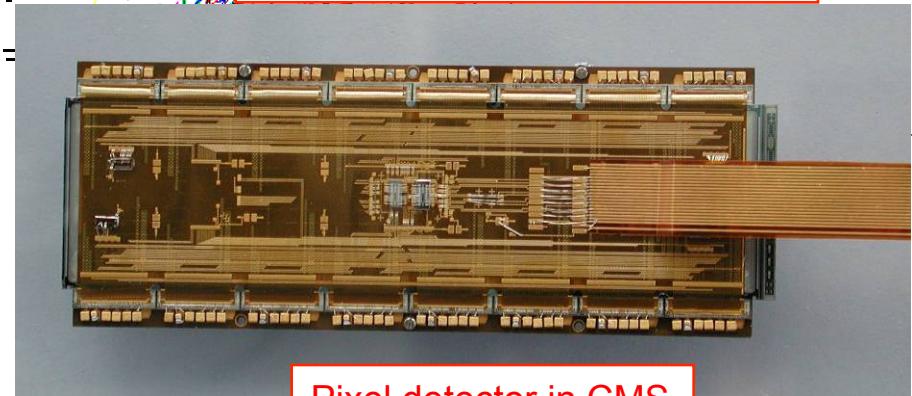


Pixel detector in CMS
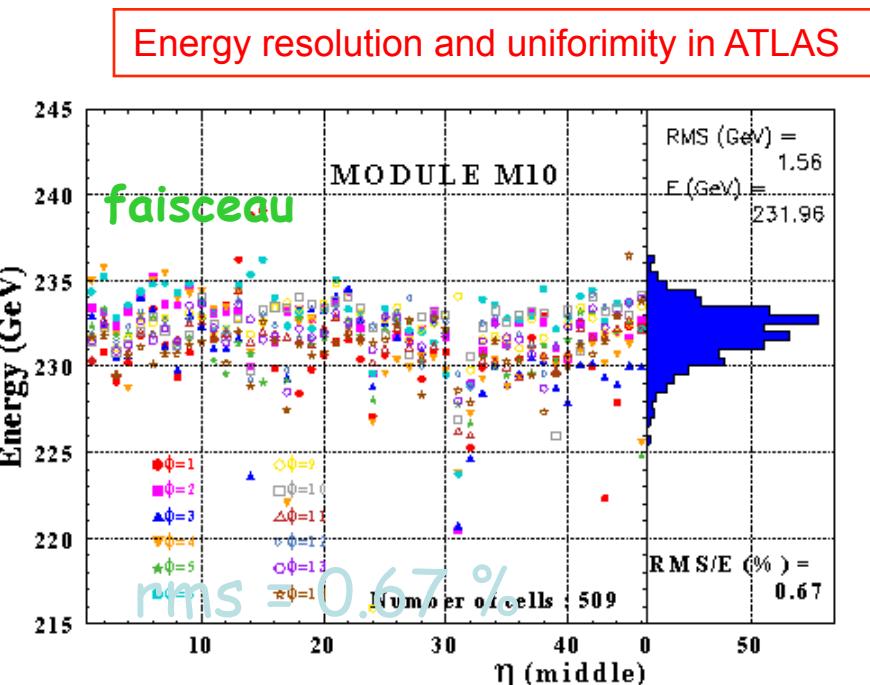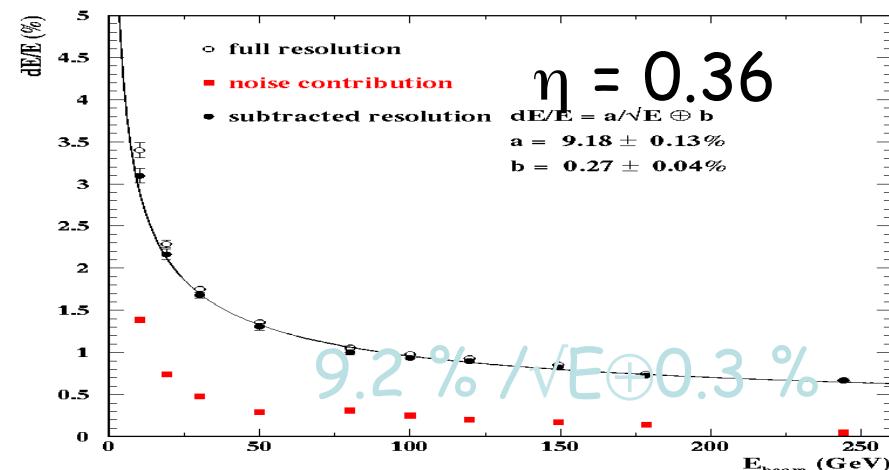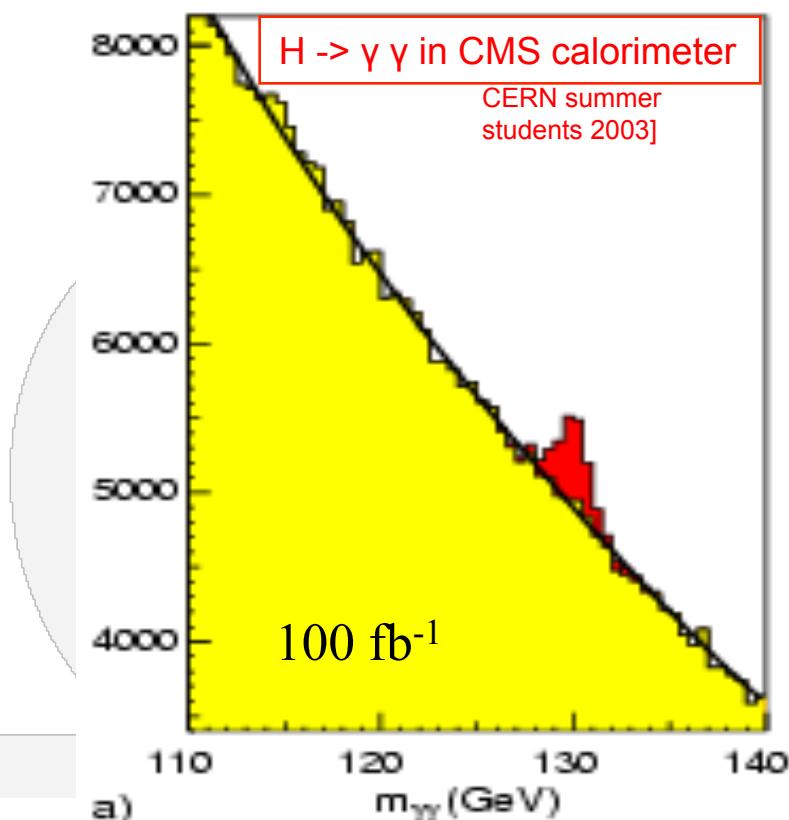
# Importance of electronics : calorimeters


*Omega*

- Large dynamic range ( $10^4$ - $10^5$ )
- High Precision  $\sim 1\%$ 
  - Importance of low noise, uniformity, linearity...
  - Importance of calibration



# A large variety of detectors...


Omega

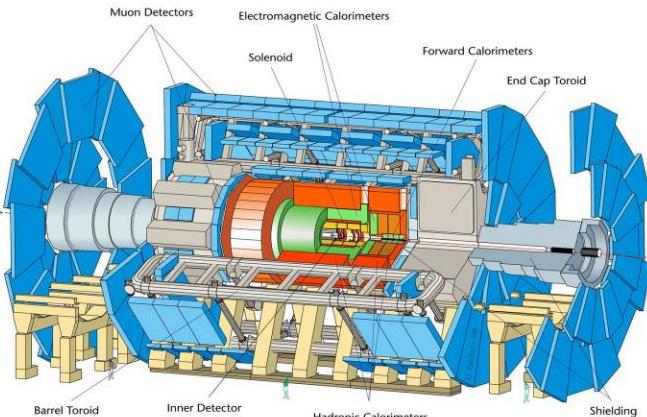

ATLAS : Higgs boson




Planck : CMB

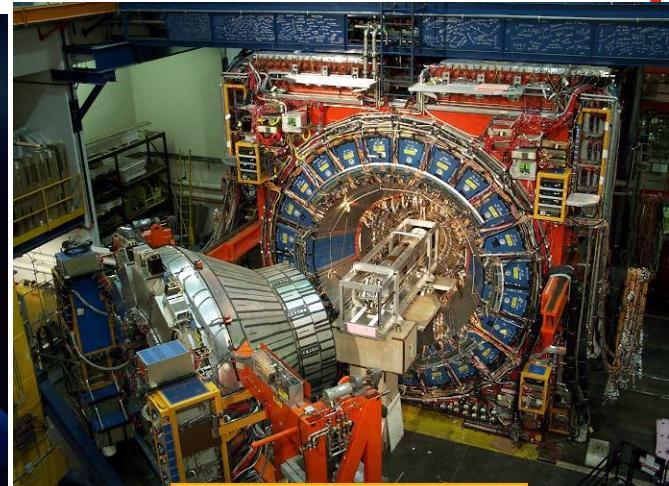

CDF : top quark



Edelweiss : dark matter

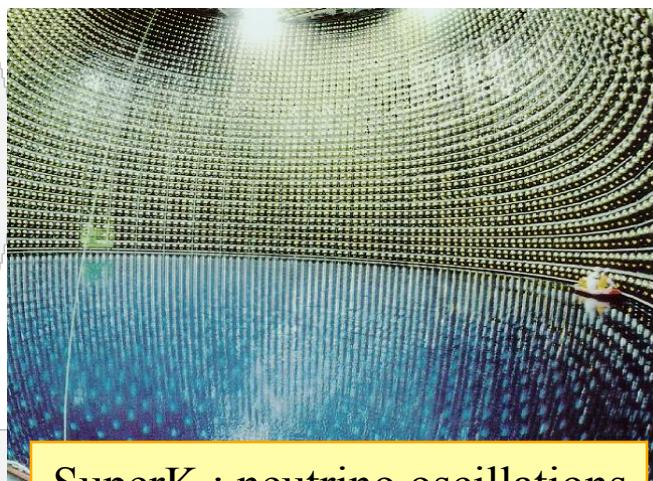

SuperK : neutrino oscillations







AUGER : cosmic rays  $10^{20}$ eV
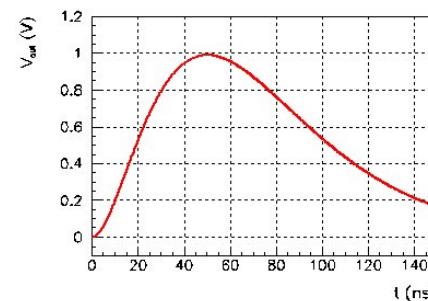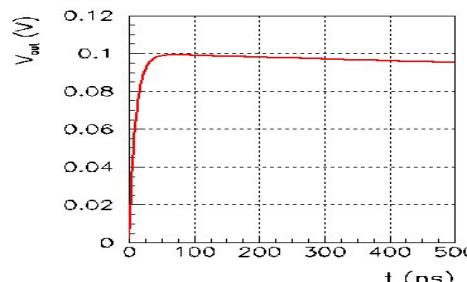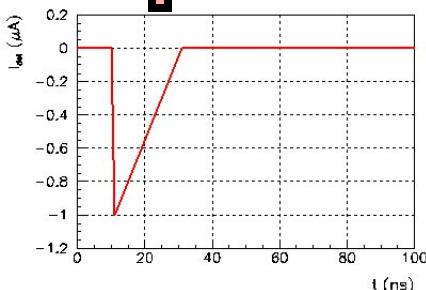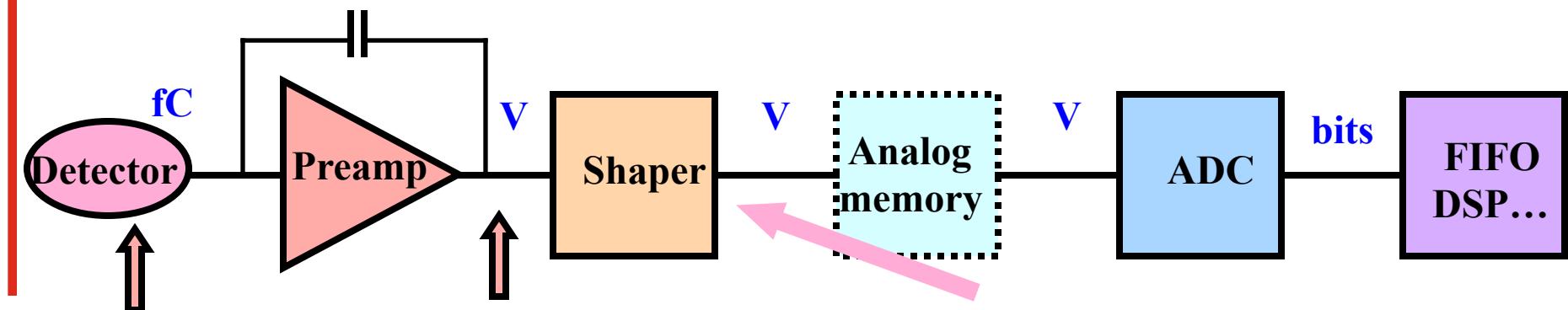
# Overview of readout electronics

Omega


- Most front-ends follow a similar architecture



- Very small signals (fC) -> need **amplification**
- Measurement of **amplitude** and/or **time** (ADCs, discriminators, TDCs)
- Several thousands to millions of channels


# Readout electronics : requirements

Omega

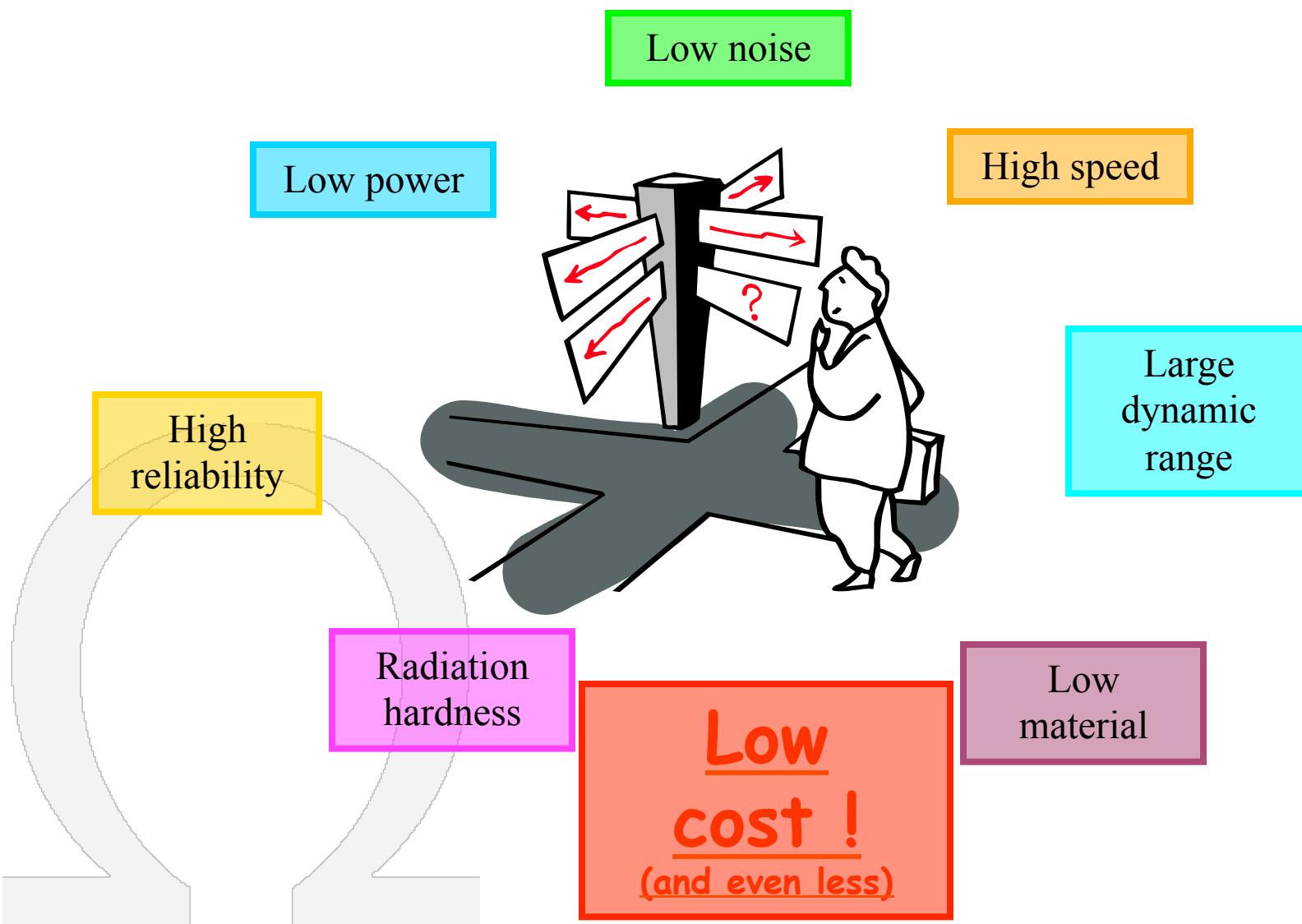

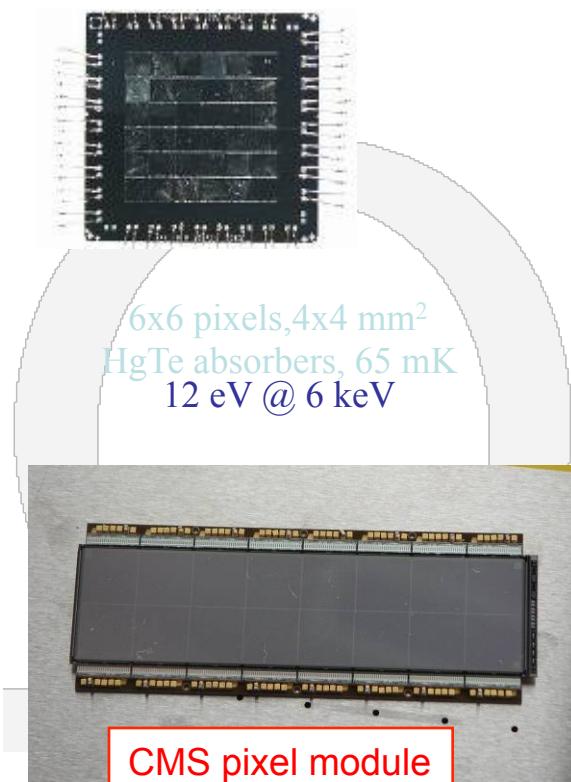
## Detector(s)

- A large variety
- A similar modelization




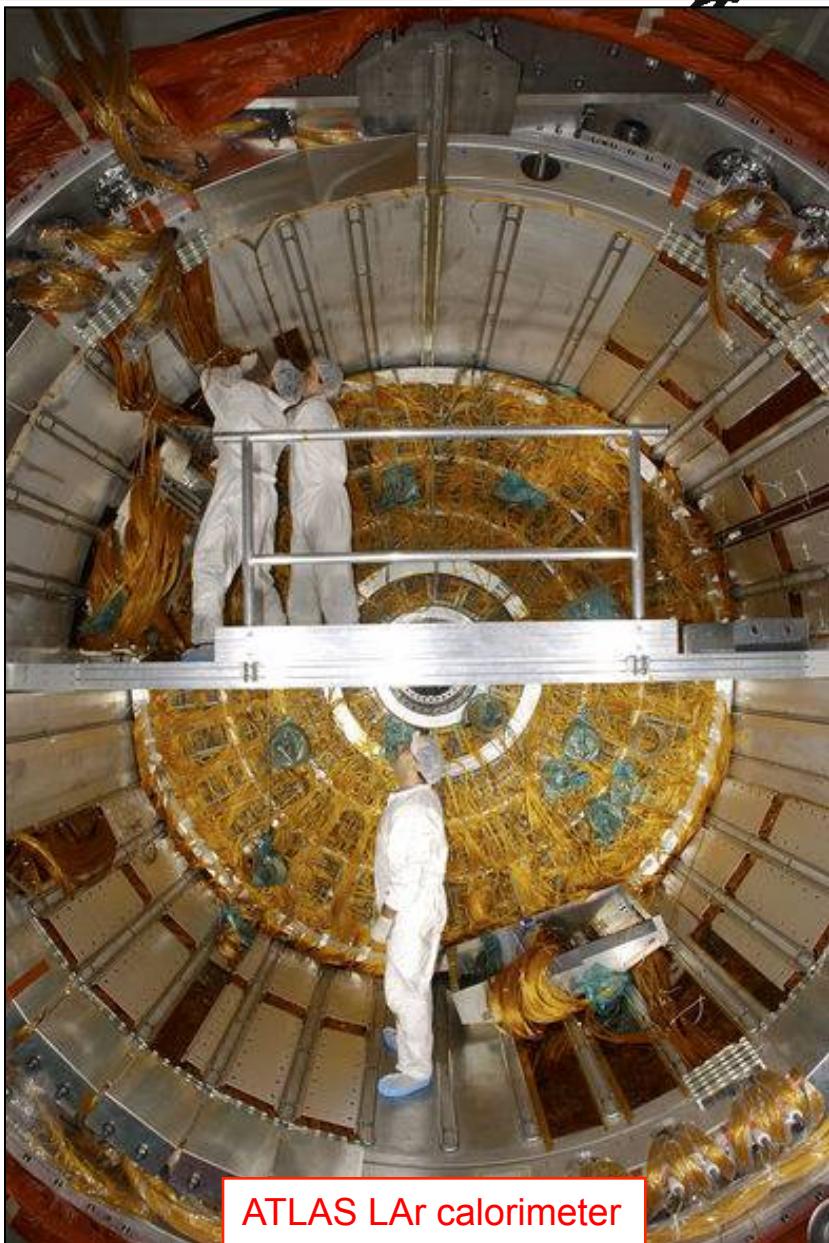6x6 pixels, 4x4 mm<sup>2</sup>  
HgTe absorbers, 65 mK  
12 eV @ 6 keV



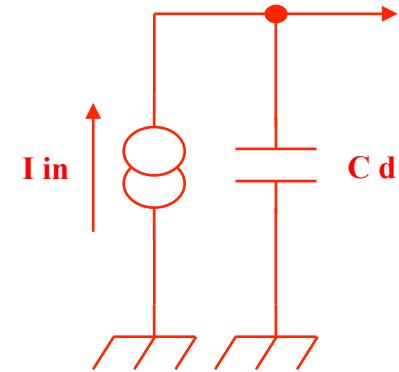
# Detector modelization

- Detector = capacitance  $C_d$ 
  - Pixels : 0.1-10 pF
  - PMs : 3-30 pF
  - Ionization chambers 10-1000 pF
  - Sometimes effect of transmission line
- Signal : current source
  - Pixels :  $\sim 100 e^-/\mu m$
  - PMs : 1 photoelectron  $\rightarrow 10^5-10^7 e^-$
  - Modelized as an impulse (Dirac) :  $i(t)$
- Missing :
  - High Voltage bias
  - Connections, grounding
  - Neighbours
  - Calibration...




Detector modelization

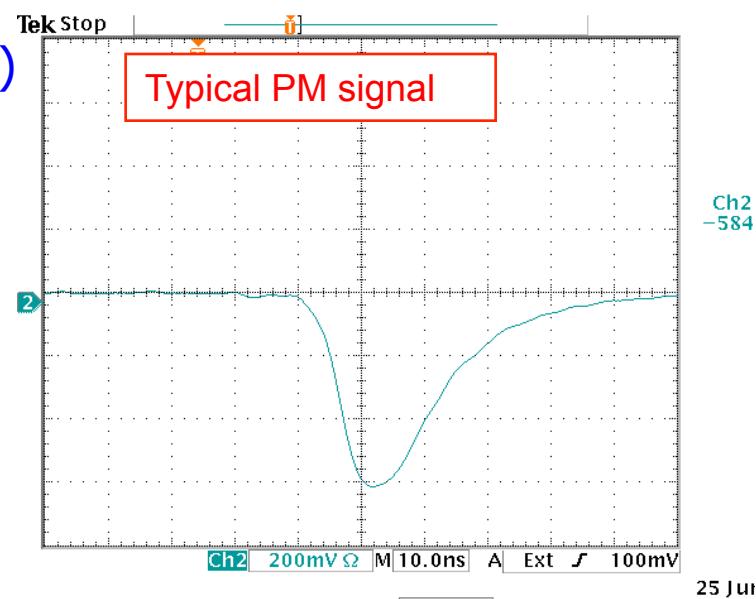


25 Jul  
15-11
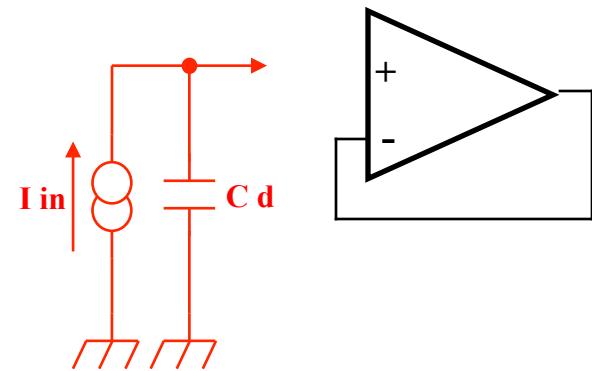
# Reading the signal

- Signal
  - Signal = current source
  - Detector = capacitance  $C_d$
  - Quantity to measure
    - Charge => integrator needed
    - Time => discriminator + TDC





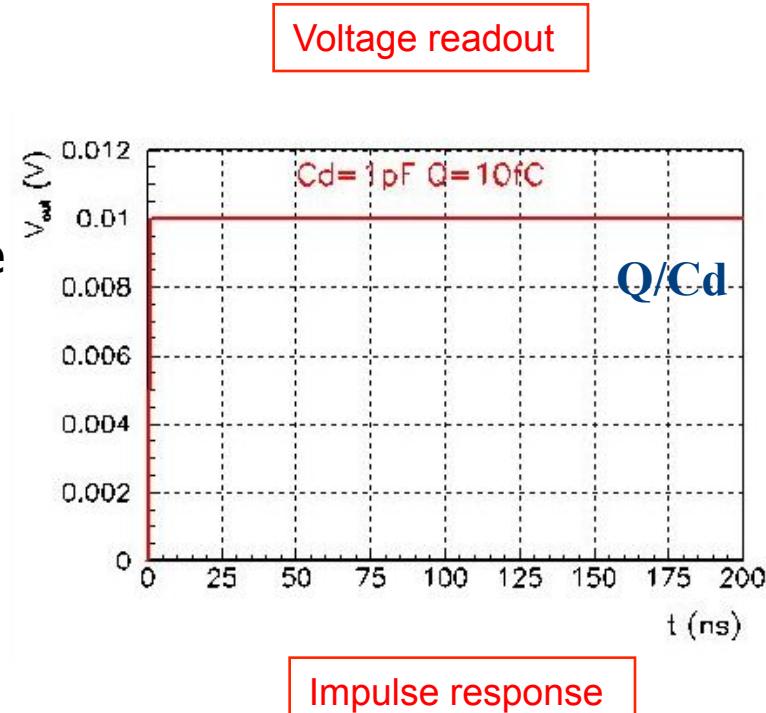- Integrating on  $C_d$ 
  - Simple :  $V = Q/C_d$
  - « Gain » :  $1/C_d$  : 1 pF -> 1 mV/fC
  - Need a follower to buffer the voltage => parasitic capacitance
  - Gain loss, possible non-linearities
  - crosstalk
  - Need to empty  $C_d$ ...


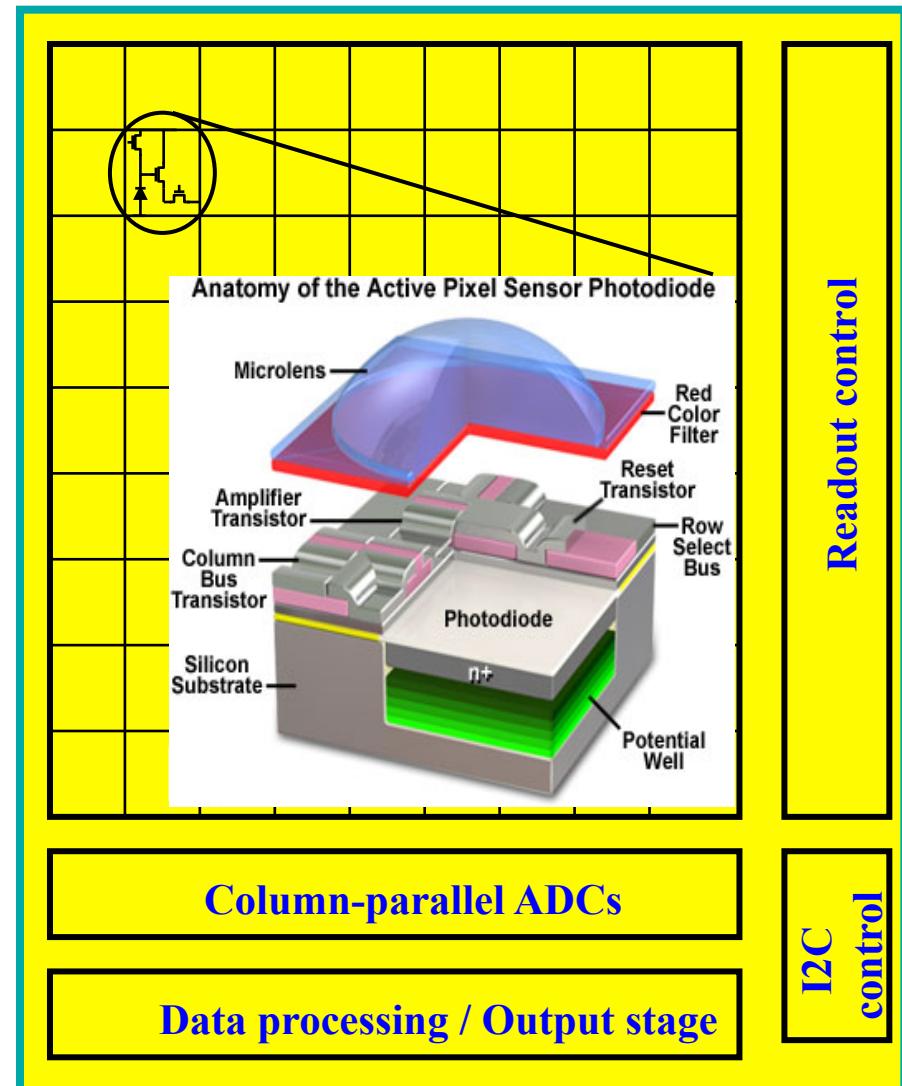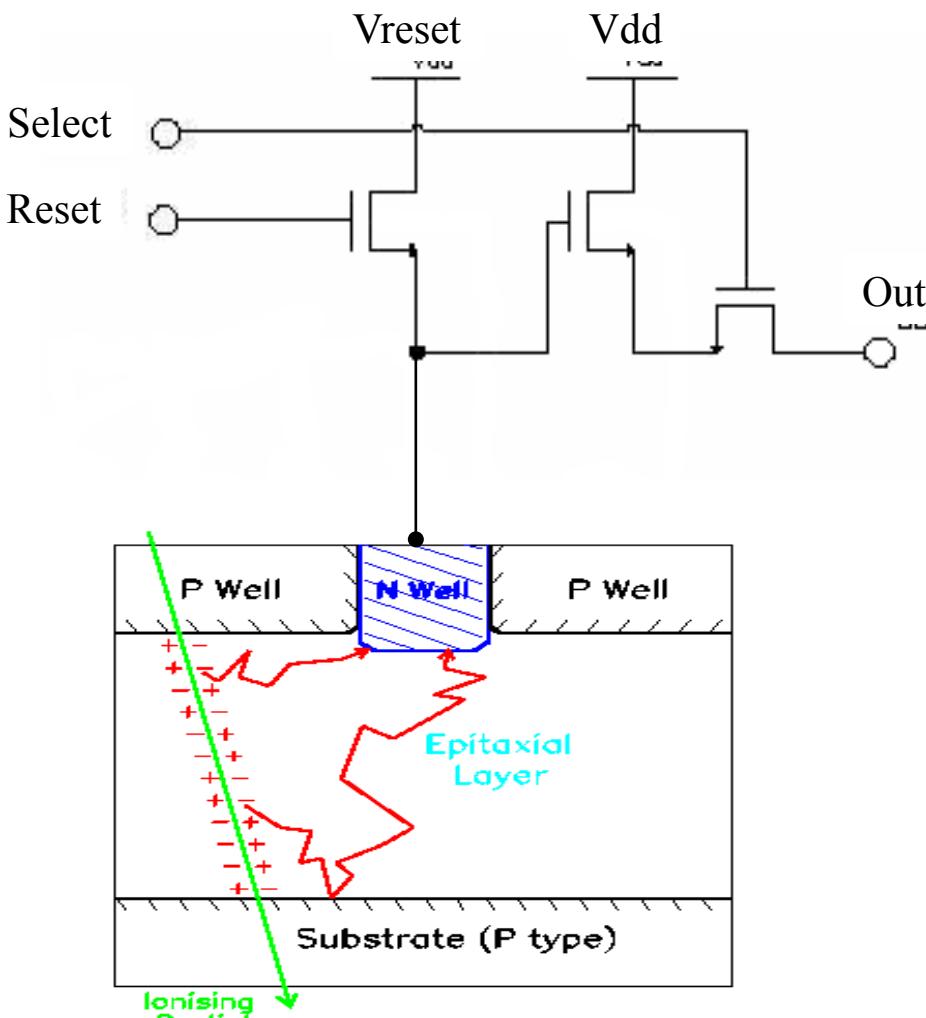
# Monolithic active pixels

- Collect charge by diffusion
- Read  $\sim 100$  e<sup>-</sup> on  $C \sim 10fF$  = few mV




# Ideal charge preamplifier

- ideal opamp in transimpedance
  - Shunt-shunt feedback
  - transimpedance :  $v_{out}/i_{in}$
  - $V_{in}=0 \Rightarrow V_{out}(\omega)/i_{in}(\omega) = -Z_f = -1/j\omega C_f$
  - **Integrator** :  $v_{out}(t) = -1/C_f \int i_{in}(t)dt$


$$v_{out}(t) = - Q/C_f$$

- « Gain » :  $1/C_f$  : 0.1 pF  $\rightarrow$  10 mV/fC
- $C_f$  determined by maximum signal

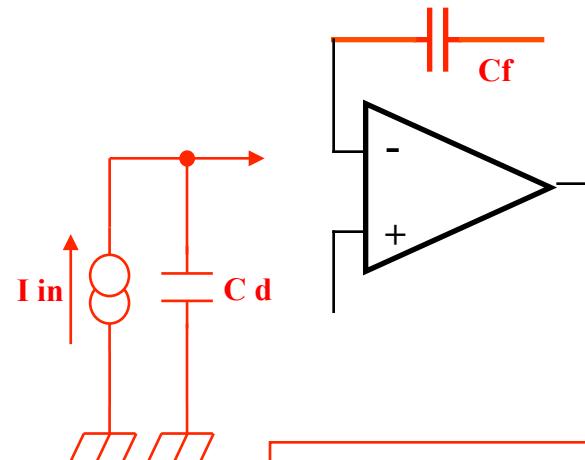- Integration on  $C_f$ 
  - Simple :  $V = - Q/C_f$
  - Un sensitive to preamp capacitance  $C_{PA}$
  - Turns a short signal into a long one
  - **The front-end of 90% of particle physics detectors...**
  - **But always built with custom circuits...**




Charge sensitive preamp

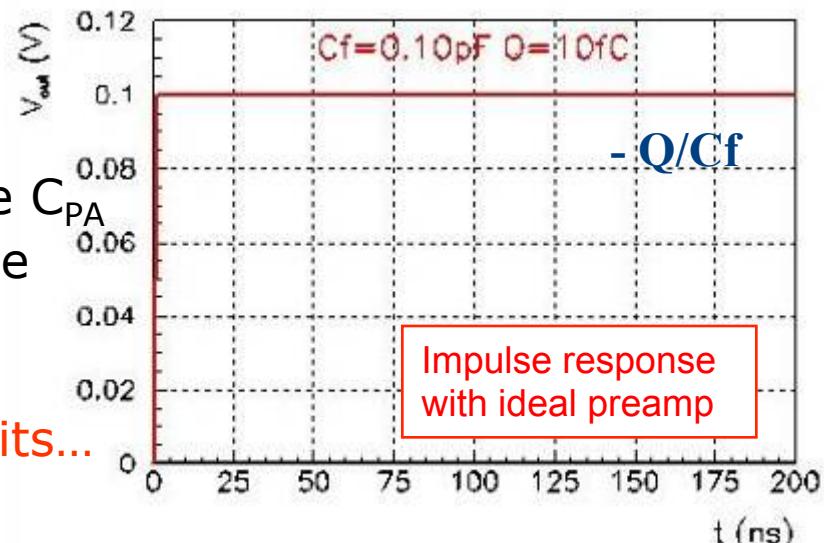
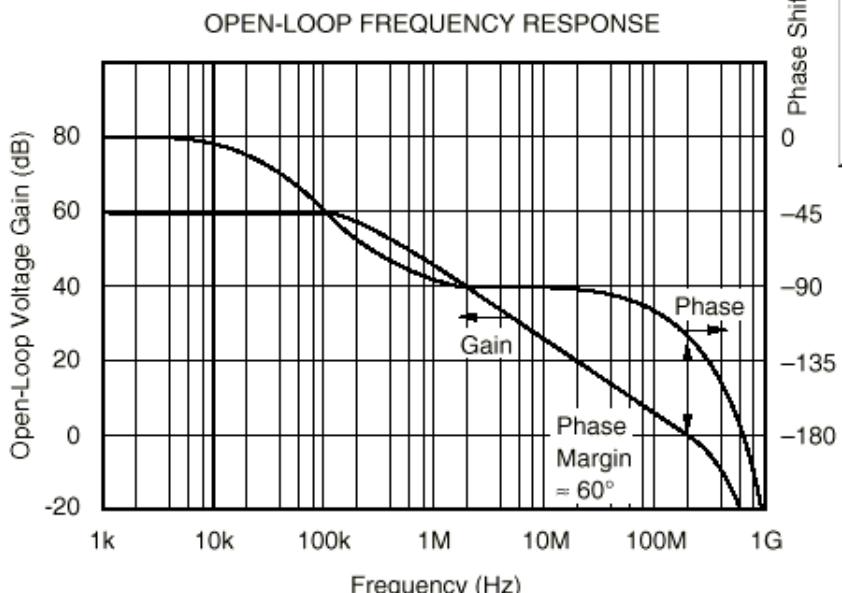
# Non-ideal charge preamplifier

- Finite opamp gain
  - $V_{\text{out}}(\omega)/i_{\text{in}}(\omega) = -Z_f / (1 + C_d / G_0 C_f)$
  - Small signal loss in  $C_d/G_0 C_f \ll 1$  (ballistic deficit)
- Finite opamp bandwidth
  - First order open-loop gain
  - $G(\omega) = G_0/(1 + j \omega/\omega_0)$ 
    - $G_0$  : low frequency gain
    - $G_0\omega_0$  : gain bandwidth product
- Preamp risetime
  - Due to gain variation with  $\omega$
  - Time constant :  $\tau$  ( $\text{tau}$ )
  - $\tau = C_d/G_0\omega_0C_f$
  - Rise-time :  $t_{10-90\%} = 2.2 \tau$
  - Rise-time optimised with  $w_C$  or  $C_f$





Impulse response with non-ideal preamp

# Charge preamp seen from the input

Omega


- Input impedance with ideal opamp
  - $Z_{in} = Z_f / G + 1$
  - $Z_{in} \rightarrow 0$  for ideal opamp
  - « Virtual ground » :  $V_{in} = 0$
  - Minimizes sensitivity to detector impedance
  - Minimizes crosstalk
- Input impedance with real opamp
  - $Z_{in} = 1/j\omega G_0 C_f + 1/ G_0 \omega_0 C_f$
  - Resistive term :  $R_{in} = 1/ G_0 \omega_0 C_f$ 
    - Exemple :  $\omega_C = 10^{10}$  rad/s  $C_f = 1$  pF  
 $\Rightarrow R_{in} = 100 \Omega$
  - Determines the input time constant :  
 $t = R_{eq} C_d$
  - Good stability = (...!)
  - Equivalent circuit :

Input impedance or charge preamp

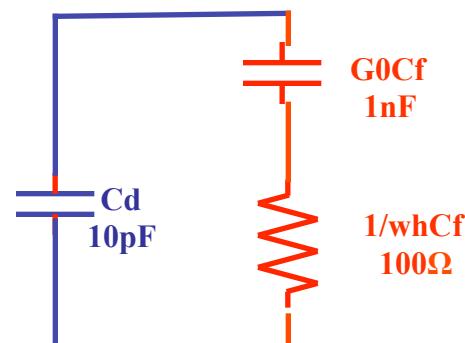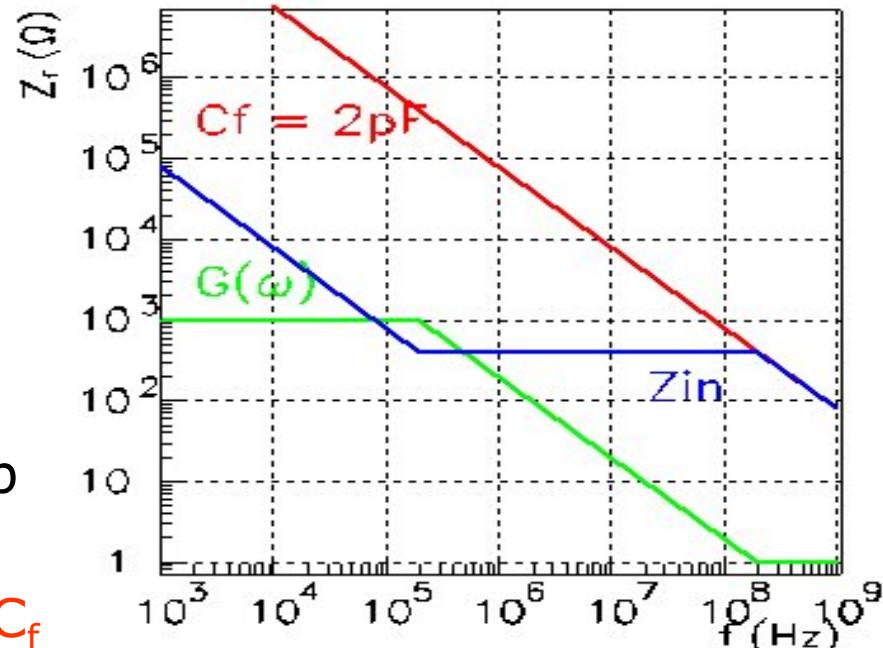

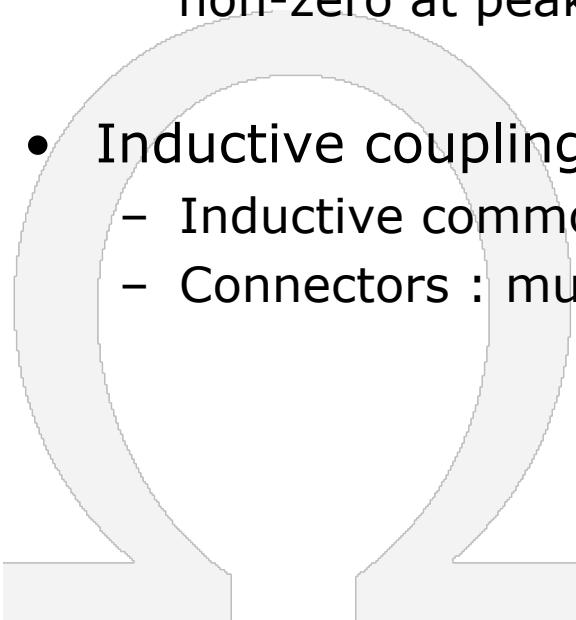
# Crosstalk


- Capacitive coupling between neighbours
  - Crosstalk signal is **differentiated and with same polarity**
  - Small contribution at signal peak
  - Proportionnal to  $C_x/C_d$  and preamp input impedance
  - Slowed derivative if  $R_{in}C_d \sim t_p \Rightarrow$  non-zero at peak



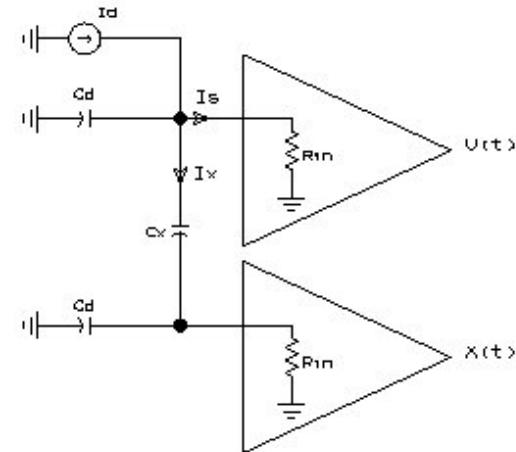- Inductive coupling
  - Inductive common ground return
  - Connectors : mutual inductance




Crosstalk electrical modelization

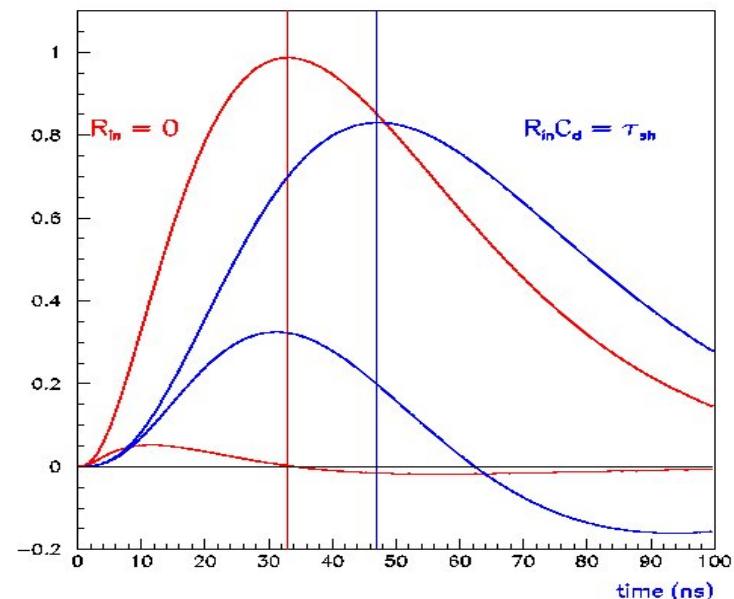



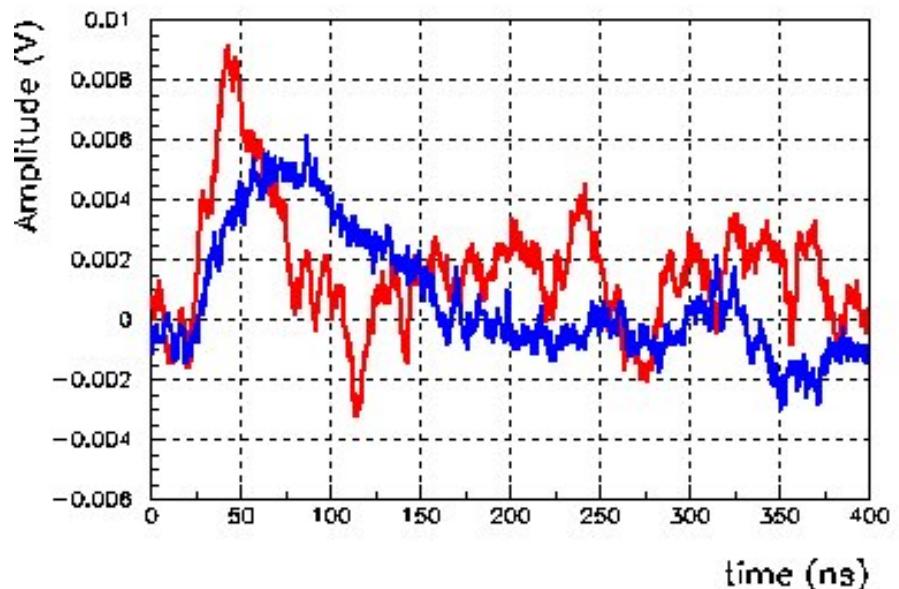
# Electronics noise

- Definition of Noise
  - Random fluctuation superposed to interesting signal
  - Statistical treatment
- Three types of noise
  - Fundamental noise  
(**Thermal noise, shot noise**)
  - Excess noise ( **$1/f$  ...**)
  - Parasitics -> **EMC/EMI**  
(**pickup noise, ground loops...**)



# Electronics noise


- Modelization
  - Noise generators :  $e_n$ ,  $i_n$ ,
  - **Noise spectral density** of  $e_n$  &  $i_n$   
 $S_v(f)$  &  $S_i(f)$
  - $S_v(f) = | \mathcal{F}(e_n) |^2$  (V<sup>2</sup>/Hz)
- Rms noise  $V_n$ 
  - $V_n^2 = \int e_n^2(t) dt = \int S_v(f) df$
  - White noise ( $e_n$ ) :  $v_n = e_n \sqrt{\frac{1}{2}\pi f_{-3dB}}$

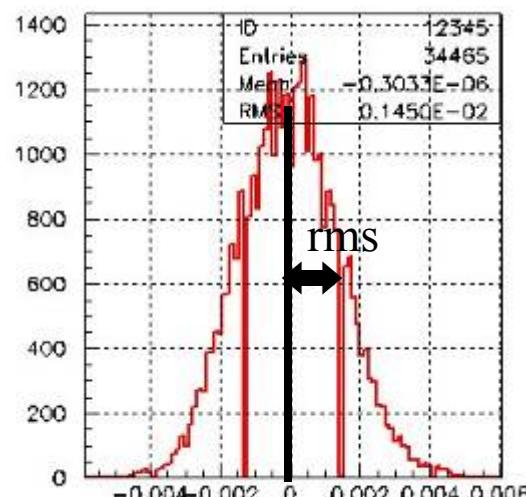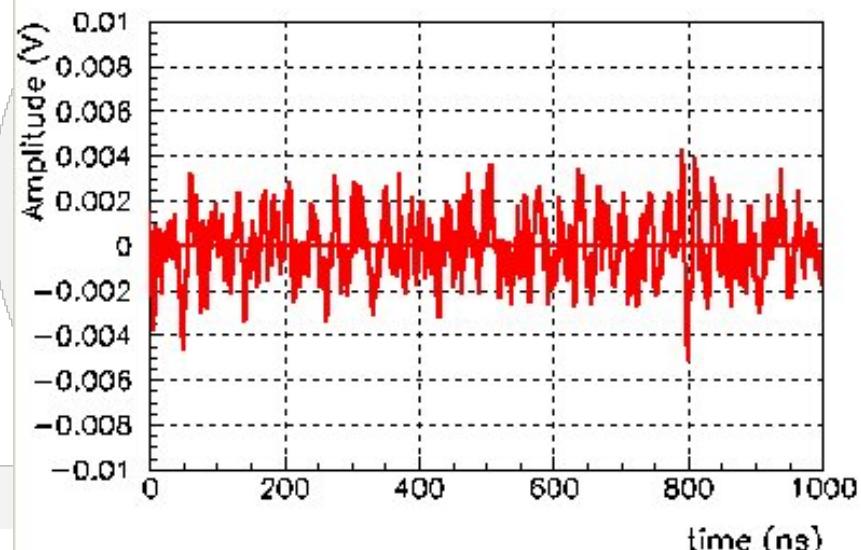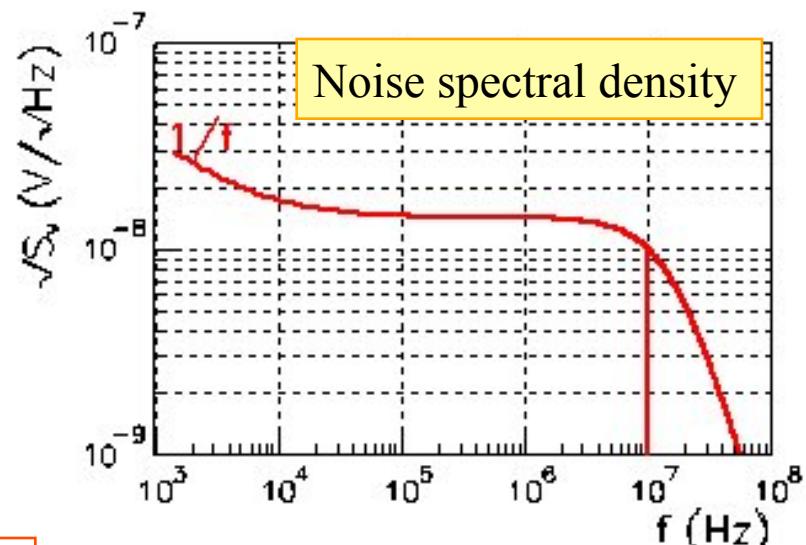

Rms noise  $v_n$
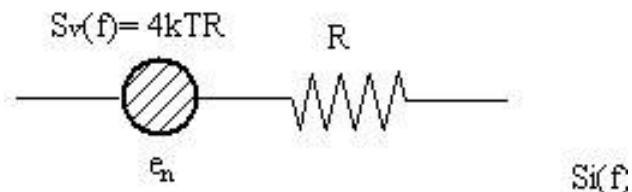
# Calculating electronics noise

- Fundamental noise
  - Thermal noise (resistors) :  $S_v(f) = 4kTR$
  - Shot noise (junctions) :  $S_i(f) = 2qI$





- Noise referred to the input
  - All noise generators can be referred to the input as **2** noise generators :
  - A voltage one  $e_n$  in series : **series noise**
  - A current one  $i_n$  in parallel : **parallel noise**
  - Two generators : no more, no less...

To take into account the Source impedance

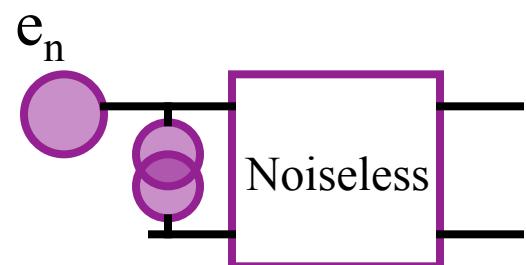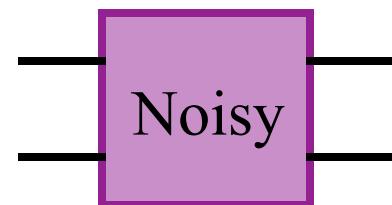**Golden rule**

Always calculate the signal before the noise  
what counts is the signal to noise ratio




Noise generators  
referred to the input


# Noise in charge pre-amplifiers

Omega

- 2 noise generators at the input
  - Parallel noise :  $(i_n^2)$  (leakage currents)
  - Series noise :  $(e_n^2)$  (preamp)
- Output noise spectral density :
  - $Sv(\omega) = (i_n^2 + e_n^2/|Z_d|^2) / \omega^2 C_f^2$   
 $= i_n^2 / \omega^2 C_f^2 + e_n^2 C_d^2 / C_f^2$
  - Parallel noise in  $1/\omega^2$
  - Series noise is flat, with a « noise gain » of  $C_d/C_f$
- rms noise  $V_n$ 
  - $V_n^2 = \int Sv(\omega) d\omega / 2\pi \rightarrow \infty (!)$
  - Benefit of shaping...


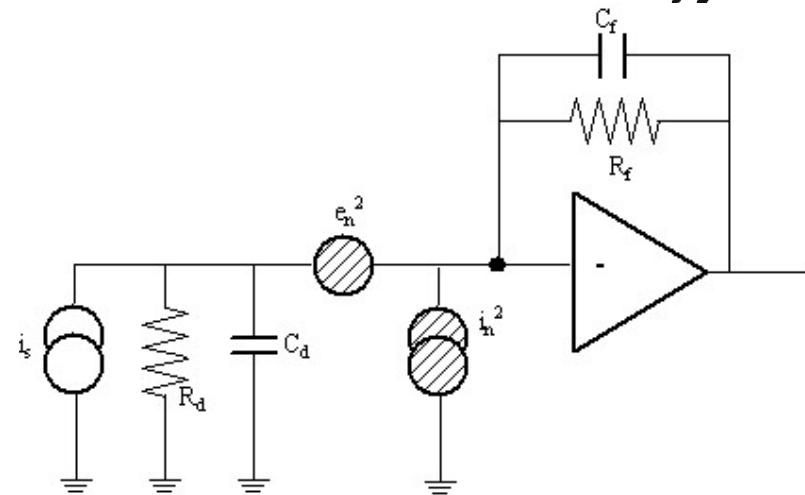


Noise generators in charge preamp

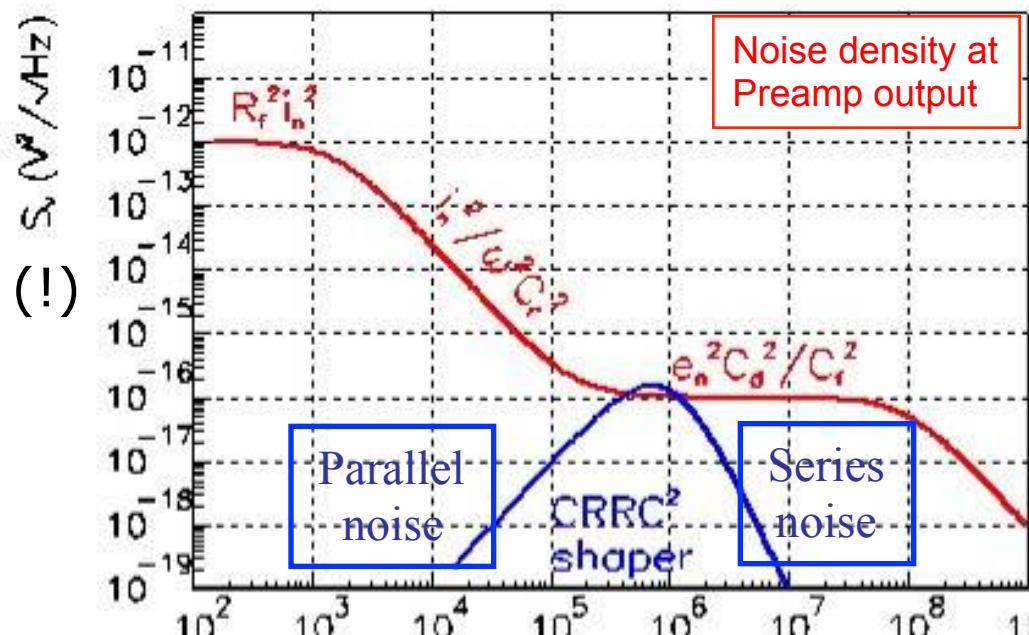
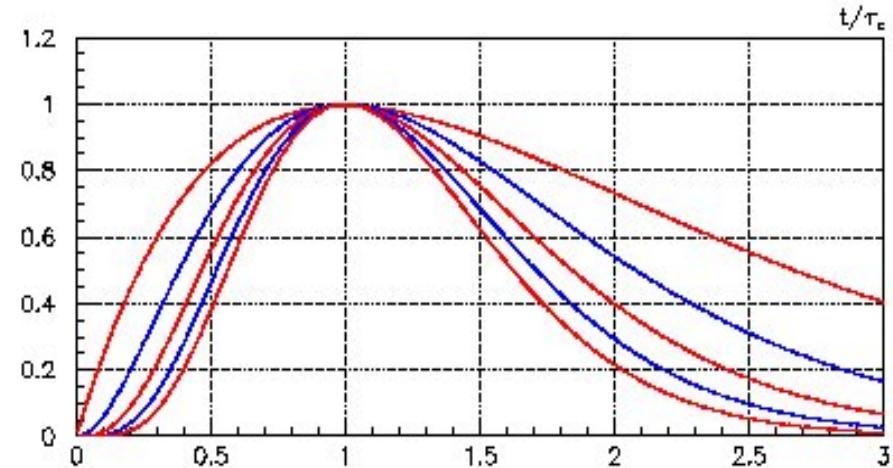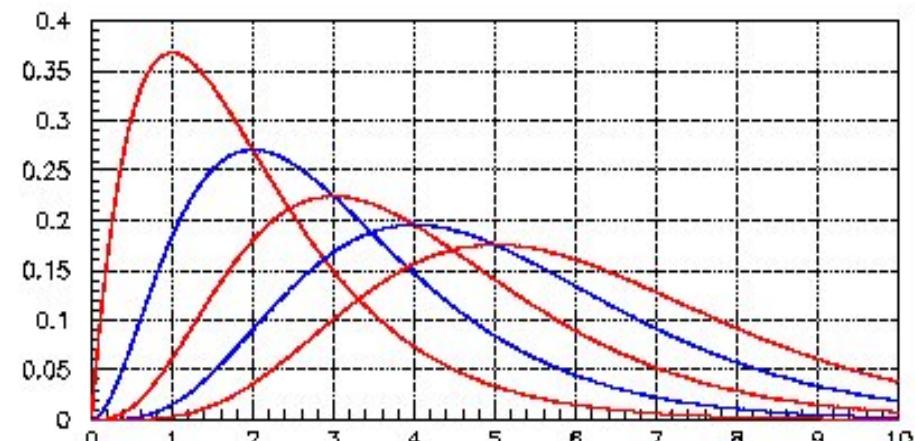
# Equivalent Noise Charge (ENC) after CRRC<sup>n</sup>

- Noise reduction by optimising useful bandwidth
  - Low-pass filters (**RC<sup>n</sup>**) to cut-off high frequency noise
  - High-pass filter (**CR**) to cut-off parallel noise
  - -> pass-band filter CRRC<sup>n</sup>
- Equivalent Noise Charge : **ENC**
  - Noise referred to the input in electrons
  - $\text{ENC} = I_a(n) e_n C_t / \sqrt{T}$   
 $\oplus I_b(n) i_n * \sqrt{T}$
  - Series noise in  $1/\sqrt{T}$
  - Parallel noise in  $\sqrt{T}$
  - 1/f noise independant of  $T$
  - Optimum shaping time  $T_{\text{opt}} = T_c / \sqrt{2n-1}$





Step response of CR RC<sup>n</sup> shapers
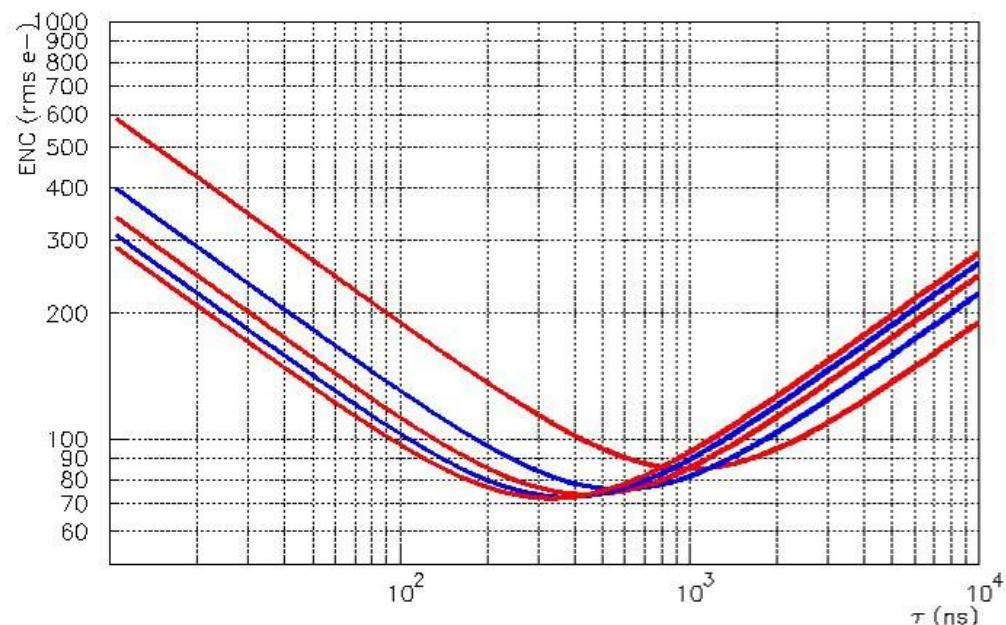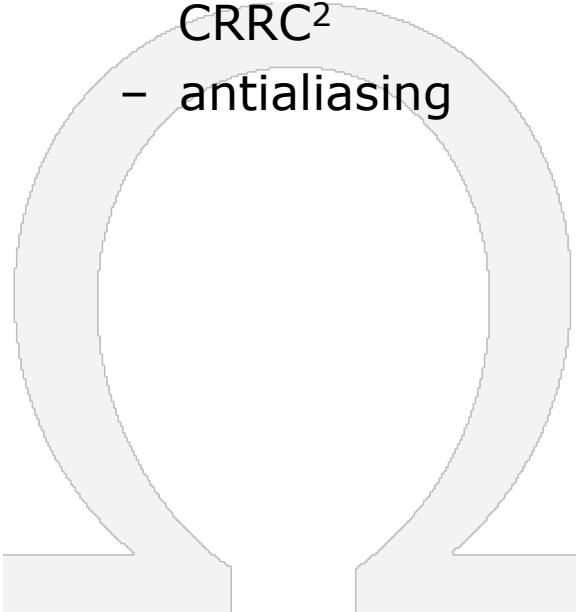
# Equivalent Noise Charge (ENC) after CRRC<sup>n</sup>

Omega

- Peaking time  $t_p$  (5-100%)
  - $\text{ENC}(t_p)$  independent of  $n$
  - Also includes preamp risetime
- Complex shapers are **obsolete** :
  - Power of **digital filtering**
  - Analog filter = CRRC ou CRRC<sup>2</sup>
  - antialiasing



ENC vs tau for CR RCn shapers

# Equivalent Noise Charge (ENC) after CRRC<sup>n</sup>

Omega


- A useful formula : **ENC (e- rms) after a CRRC<sup>2</sup> shaper :**

$$\text{ENC} = 174 e_n C_{\text{tot}} / \sqrt{t_p(\delta)} + 166 i_n \sqrt{t_p(\delta)}$$

- $e_n$  in nV/  $\sqrt{\text{Hz}}$ ,  $i_n$  in pA/  $\sqrt{\text{Hz}}$  are the **preamp** noise spectral densities
- $C_{\text{tot}}$  (in pF) is dominated by the detector ( $C_d$ ) + input preamp capacitance ( $C_{\text{PA}}$ )
- $t_p$  (in ns) is the shaper peaking time (5-100%)

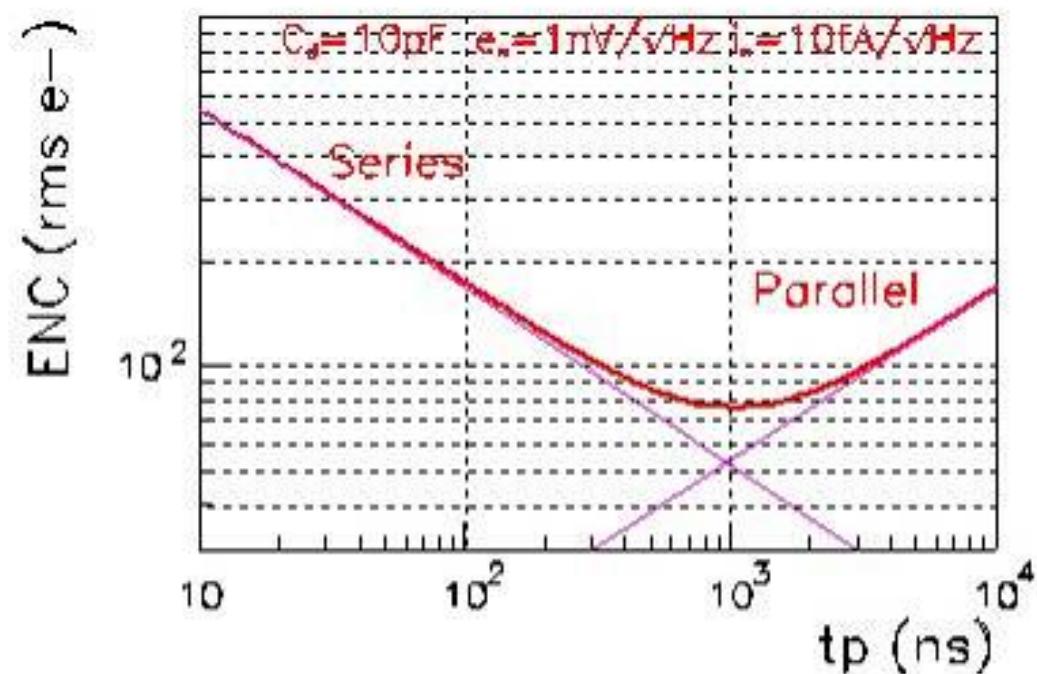
## Noise minimization

- Minimize source capacitance
- Operate at optimum shaping time
- Preamp series noise ( $e_n$ ) best with high transconductance ( $g_m$ ) in input transistor  
=> large current, optimal size


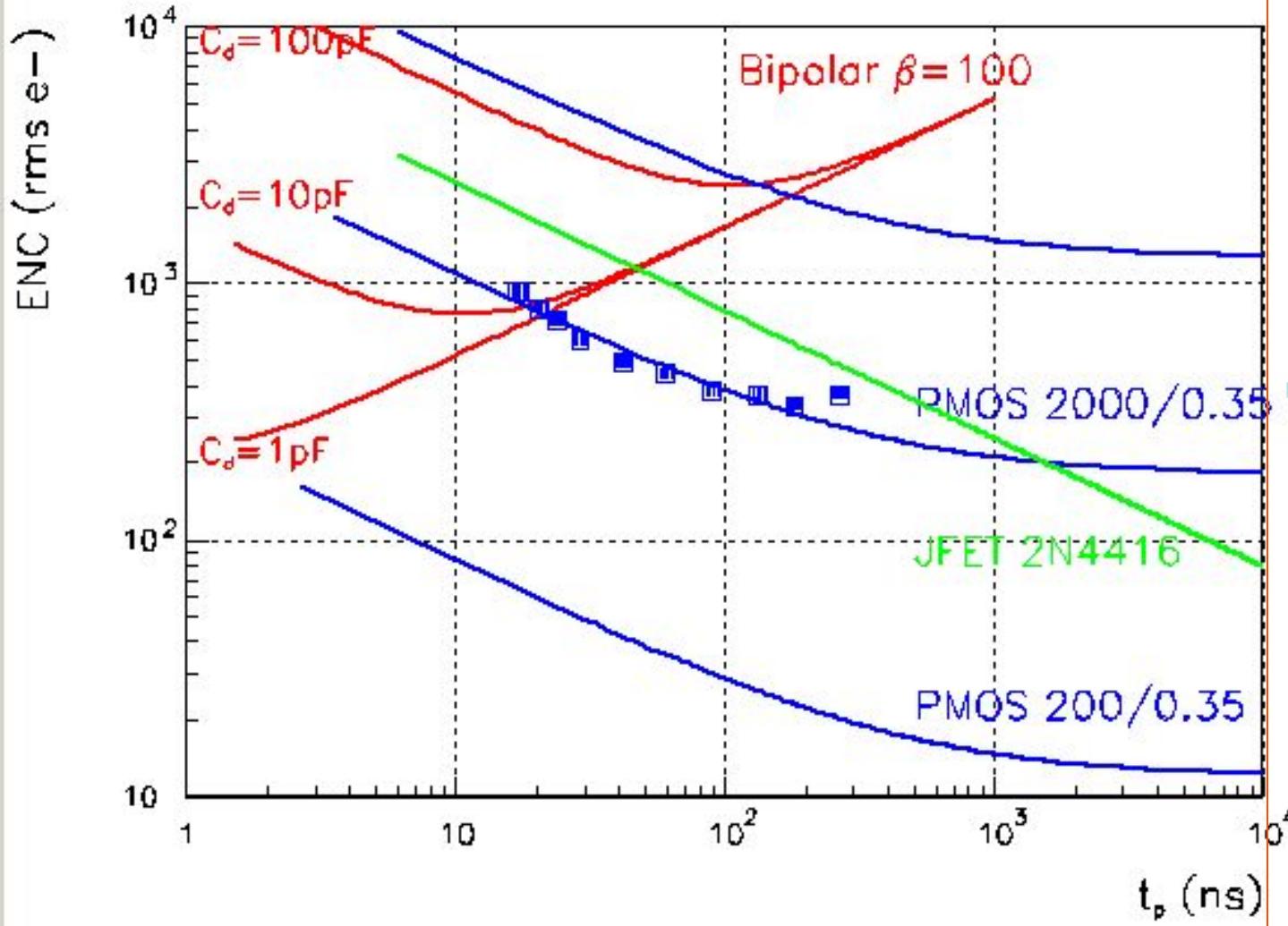
# ENC for various technologies



- ENC for Cd=1, 10 and 100 pF at  $I_D = 500 \mu A$ 
  - MOS transistors best between 20 ns – 2  $\mu s$



Parameters
Bipolar :
$g_m = 20 \text{ mA/V}$
$R_{BB} = 25 \Omega$
$e_n = 1 \text{ nV}/\sqrt{\text{Hz}}$
$I_B = 5 \mu A$
$i_n = 1 \text{ pA}/\sqrt{\text{Hz}}$
$C_{PA} = 100 \text{ fF}$
PMOS 2000/0.35
$g_m = 10 \text{ mA/V}$
$e_n = 1.4 \text{ nV}/\sqrt{\text{Hz}}$
$C_{PA} = 5 \text{ pF}$
$1/f :$
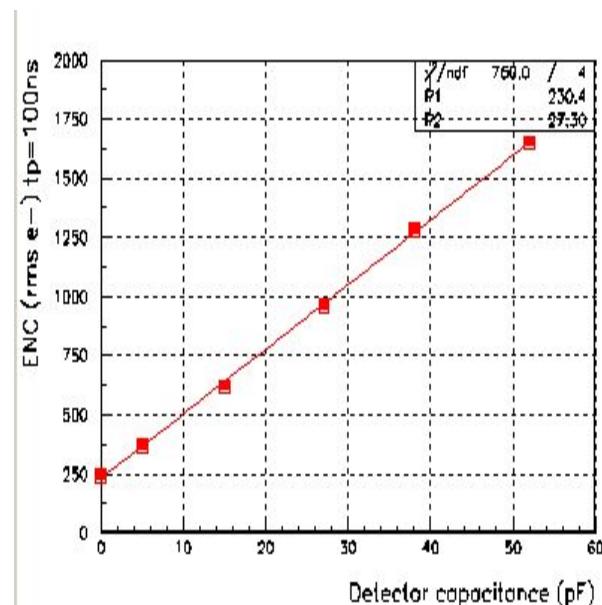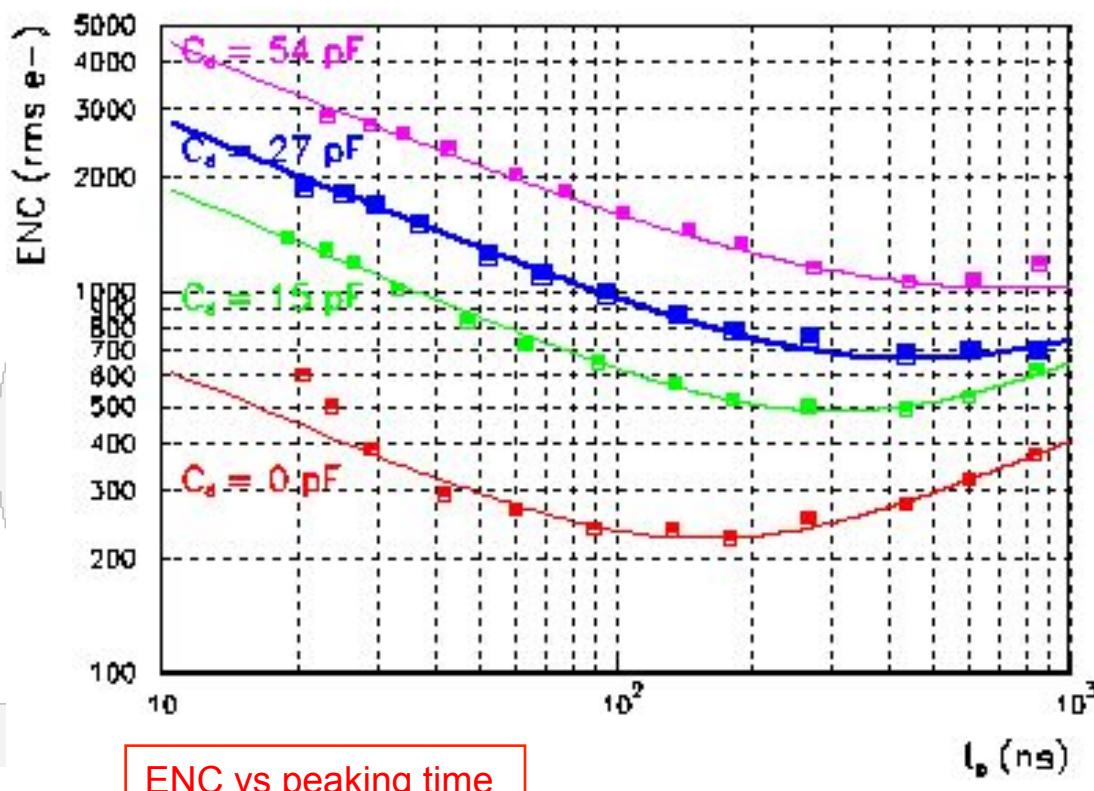
# Example of ENC measurement


- SKIROC ASIC (ILC readout) :  $0.35\mu\text{m}$  SiGe
  - Series :  $\text{en} = 1.4 \text{ nV}/\sqrt{\text{Hz}}$ ,  $C_{\text{PA}} = 7 \text{ pF}$
  - **1/f noise** :  $12 \text{ e-}/\text{pF}$
  - Parallel :  $\text{in} = 40 \text{ fA}/\sqrt{\text{Hz}}$



ENC vs Capacitance tp=100ns

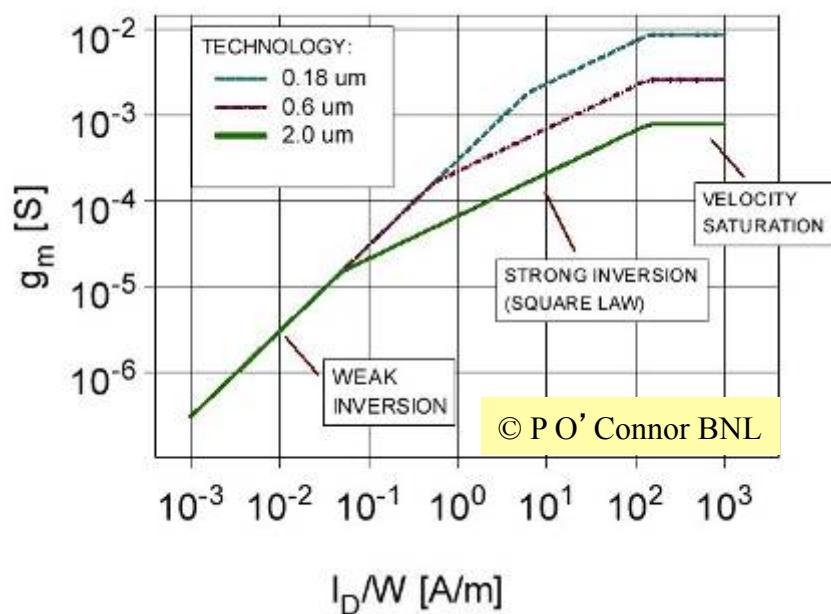
# MOS input transistor sizing

- Capacitive matching : strong inversion
  - $g_m$  proportionnal to  $W/L \sqrt{I_D}$
  - $C_{GS}$  proportionnal to  $W*L$
  - ENC proportionnal to  $(C_{det} + C_{GS})/\sqrt{gm}$
  - Optimum  $W/L$  :  $C_{GS} = 1/3 C_{det}$
  - Large transistors are easily in moderate or weak inversion at small current
- Optimum size in weak inversion
  - $g_m$  proportionnal to  $I_D$  (indep of  $W,L$ )
  - ENC minimal for  $C_{GS}$  minimal, provided the transistor remains in weak inversion



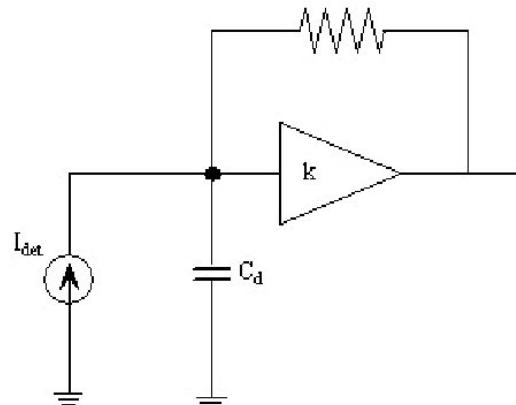
# Current preamplifiers :

- Transimpedance configuration
  - $V_{out}(\omega)/i_{in}(\omega) = - R_f / (1 + Z_f/GZ_d)$
  - Gain =  $R_f$
  - High counting rate
  - Typically optical link receivers
  
- Easily oscillatory
  - Unstable with capacitive detector
  - Inductive input impedance
 
$$L_{eq} = R_f / \omega_c$$
  - Resonance at :  $f_{res} = 1/2\pi \sqrt{L_{eq}C_d}$
  - Quality factor :  $Q = R / \sqrt{L_{eq}/C_d}$ 
    - $Q > 1/2 \rightarrow$  ringing
  - Damping with capacitance  $C_f$ 
    - $C_f = 2 \sqrt{(C_d/R_f G_0 \omega_0)}$
    - Easier with fast amplifiers




Current sensitive preamp

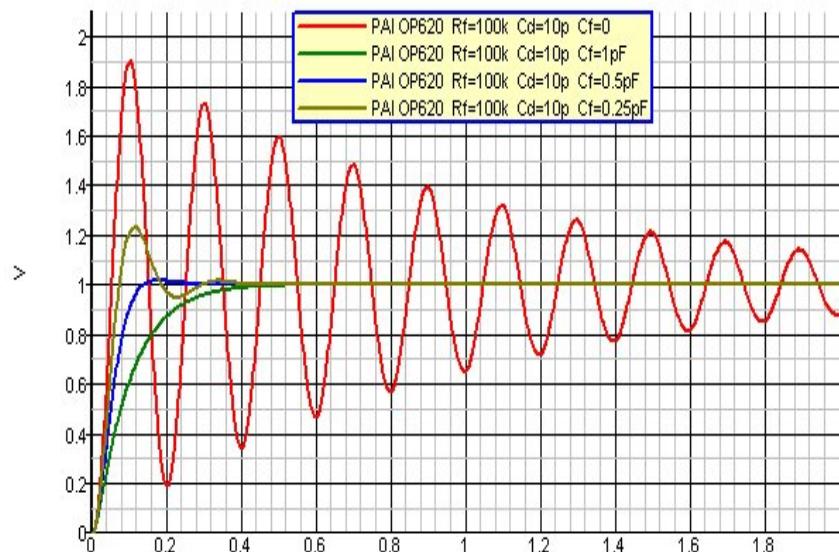

Step response of current sensitive preamp
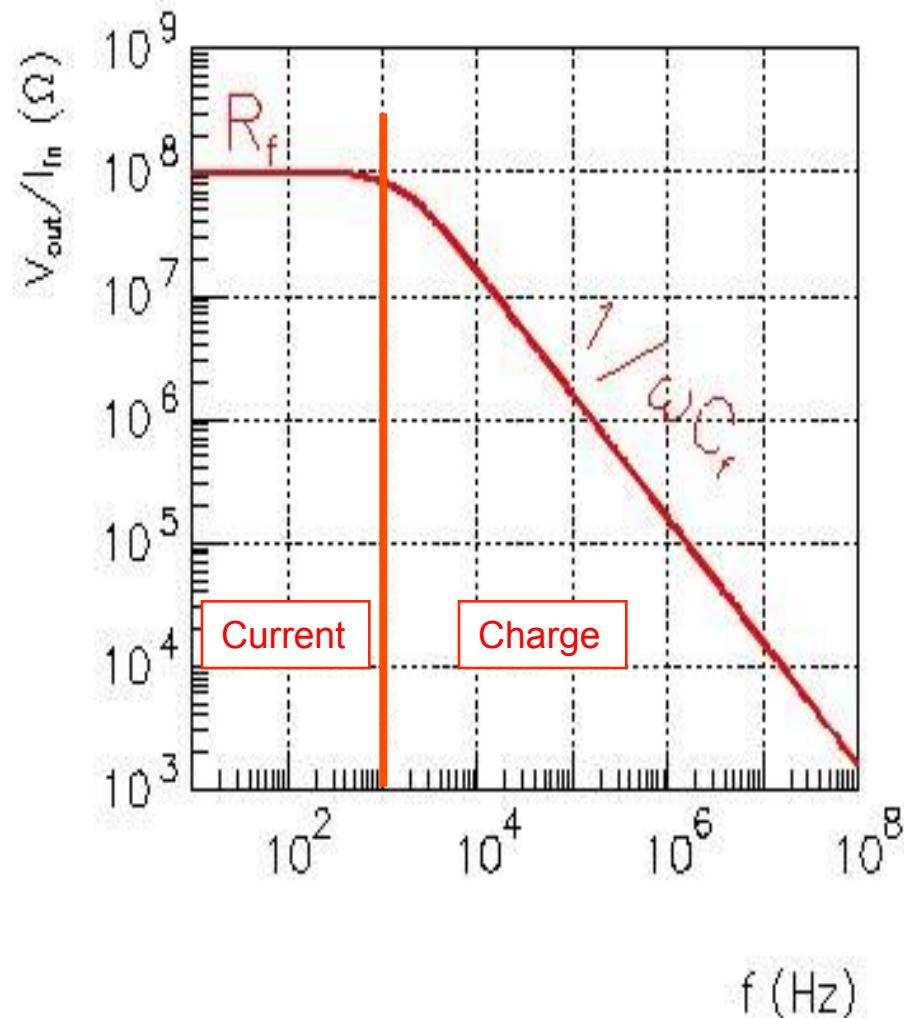
# Charge vs Current preamps


- Charge preamps
  - Best noise performance
  - Best with short signals
  - Best with small capacitance
- Current preamps
  - Best for long signals
  - Best for high counting rate
  - Significant parallel noise
- Charge preamps are not slow, they are long
- Current preamps are not faster, they are shorter (but easily unstable)



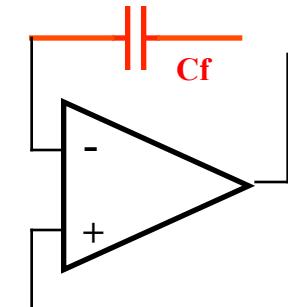
# Charge preamp design

Omega


- From the schematic of principle
  - Using of a fast opamp (OP620)
  - Removing unnecessary components...
  - Similar to the traditionnal schematic «Radeka 68 »
  - Optimising transistors and currents



Charge preamp

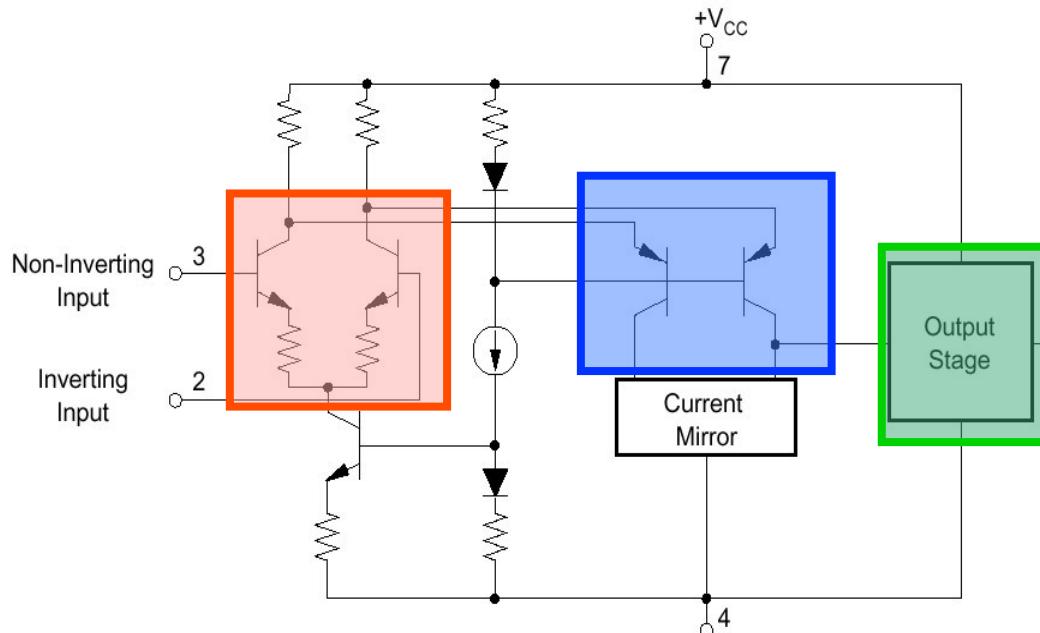


Schematic of an OP620 opamp ©BurrBrown

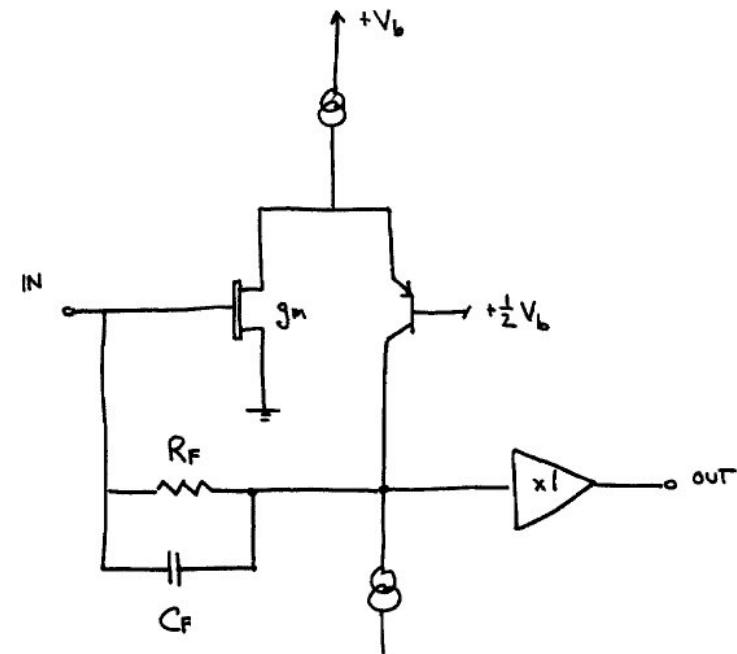

Original charge preamp ©Radeka 1968
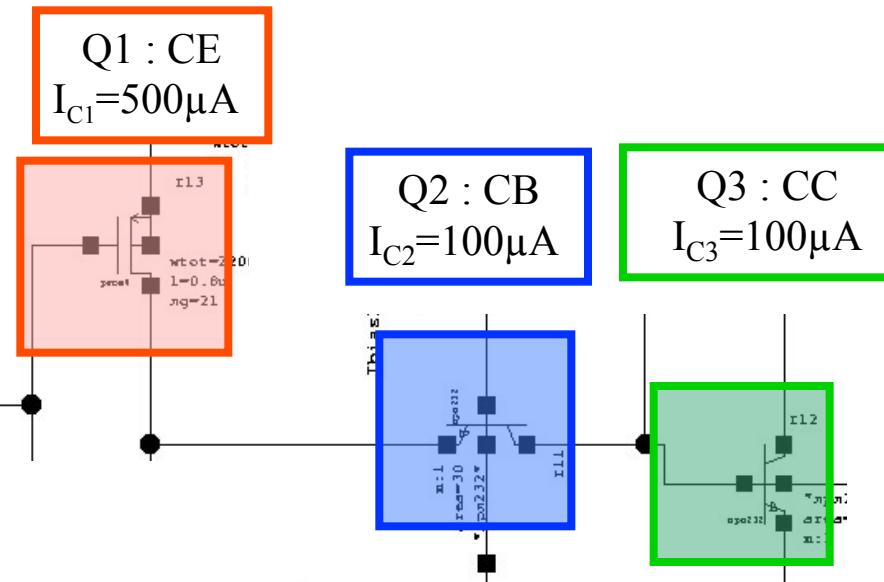
# Example : designing a charge preamp (2) *Omega*


- Simplified schematic
- Optimising components
  - What transistors (PMOS, NPN ?)
  - What bias current ?
  - What transistor size ?
  - What is the noise contributions of each component, how to minimize it ?
  - What parameters determine the stability ?
  - What is the saturation behaviour ?
  - How vary signal and noise with input capacitance ?
  - How to maximise the output voltage swing ?
  - What the sensitivity to power supplies, temperature...



Simplified schematic of charge preamp


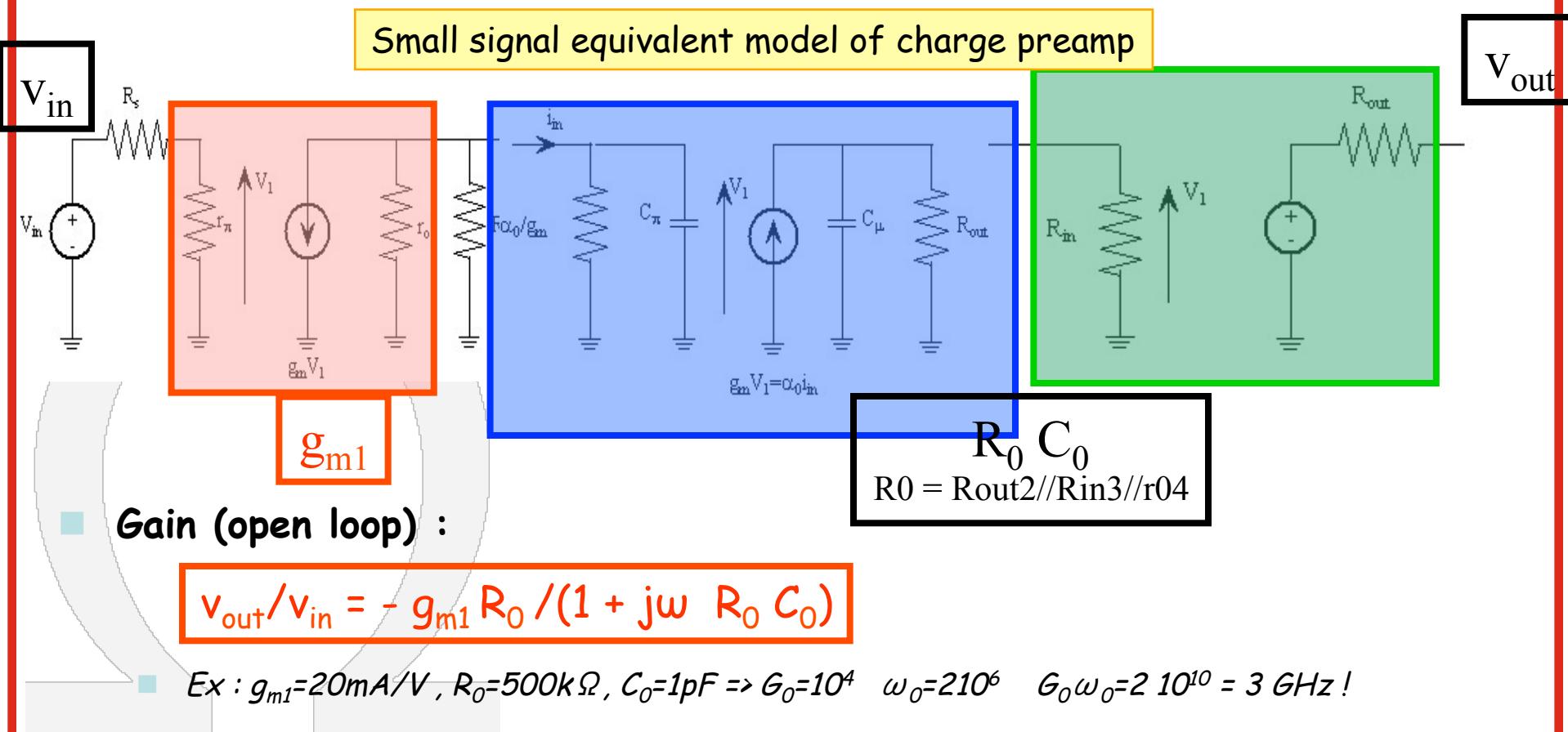
# Example : designing a charge preamp (3) Omega

- Small signal equivalent model
  - Transistors are replaced by hybrid  $\pi$  model
  - Allows to calculate open loop gain



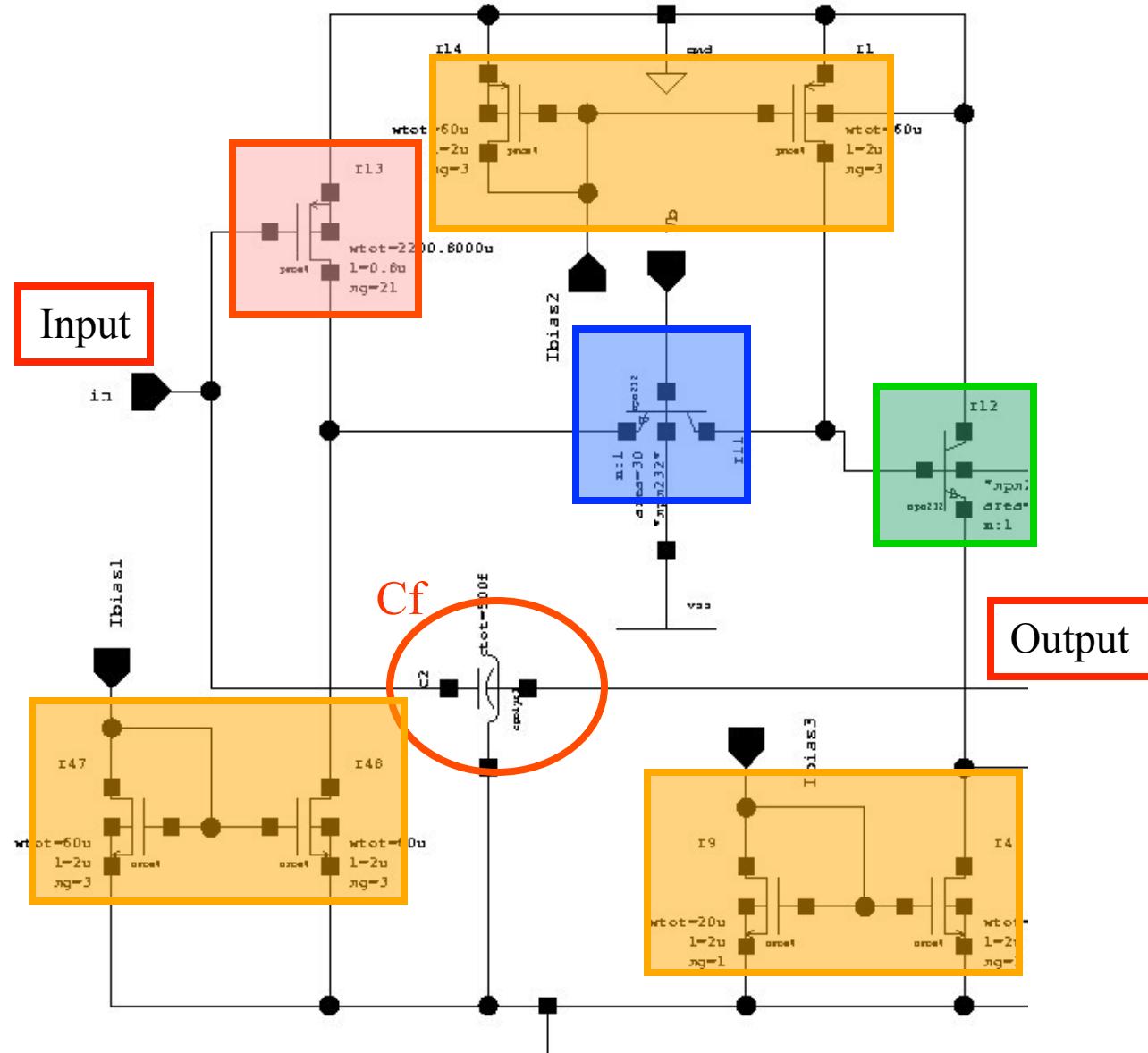
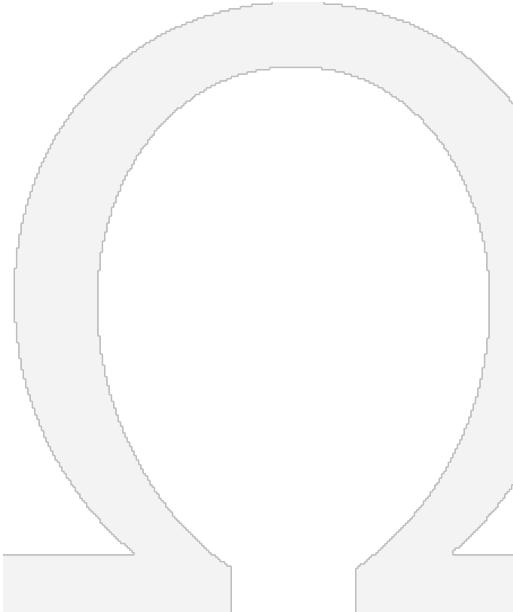
# Example : designing a charge preamp (4) Omega

- Complete schematic
  - Adding bias elements



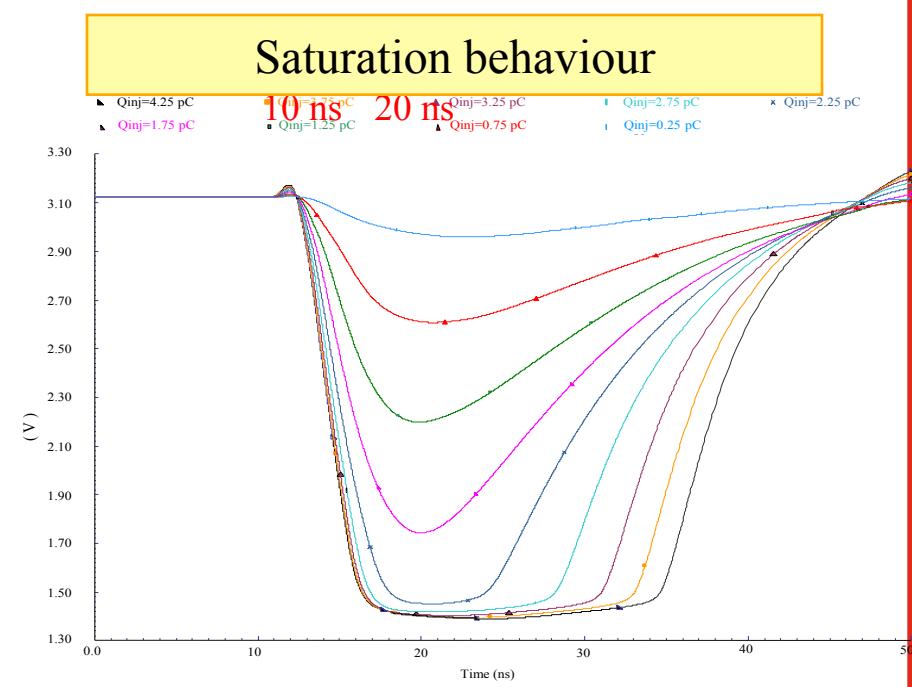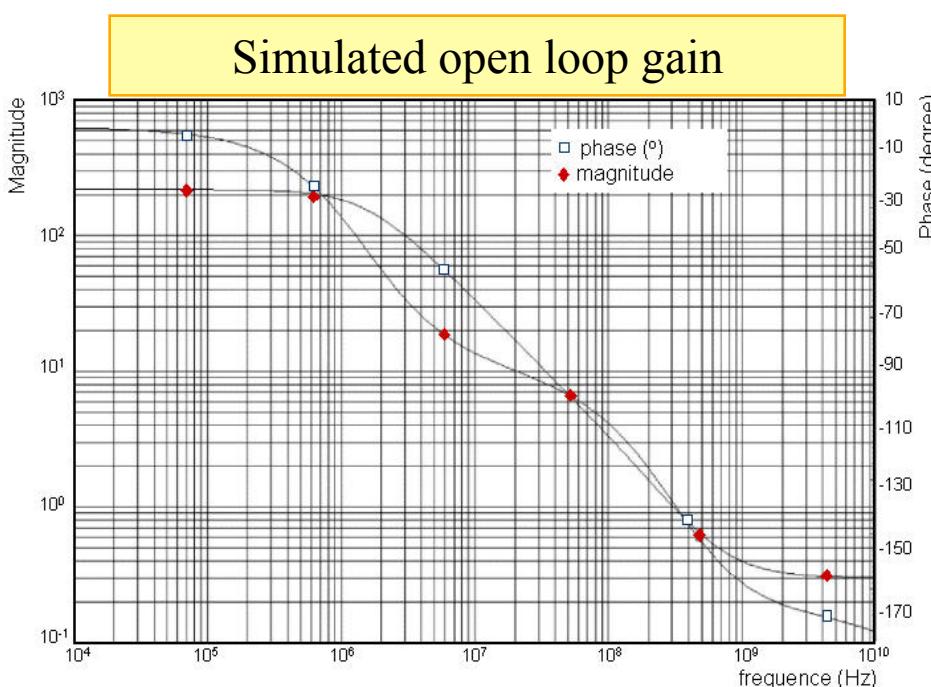
# Example : designing a charge preamp (5) *Omega*

- Complete simulation
  - Checking hand calculations against 2<sup>nd</sup> order effects
  - Testing extreme process parameters (« corner simulations »)
  - Testing robustness (to power supplies, temperature...)


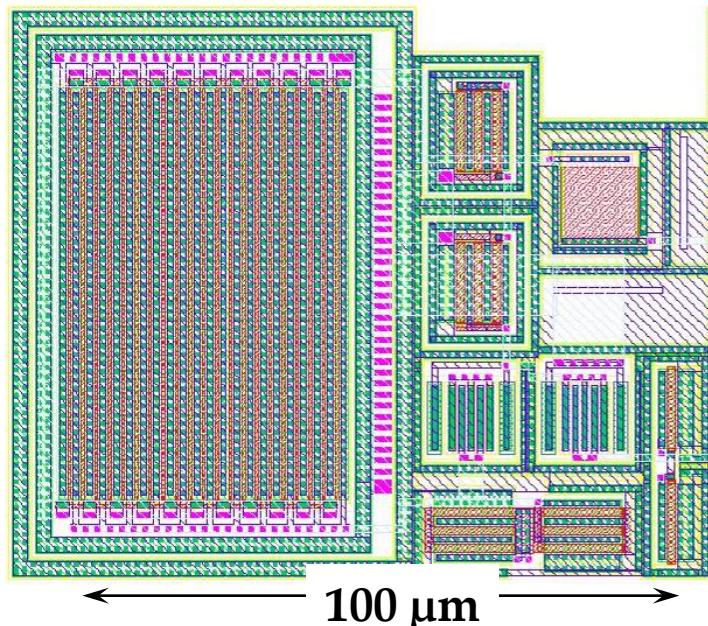
# Example : designing a charge preamp (6) *Omega*


- Layout
  - Each component is drawn
  - They are interconnected by metal layers
- Checks
  - DRC : checking drawing rules (isolation, minimal dimensions...)
  - ERC : extracting the corresponding electrical schematic
  - LVS (layout vs schematic) : comparing extracted schematic and original design
  - Simulating extracted schematic with parasitic elements
- Generating GDS2 file
  - Fabrication masks : « reticule »



- Coexistence analog-digital
  - Capacitive, inductive and common-impedance couplings
  - A full lecture !
  - A good summary : there is no such thing as « ground », pay attention to current return





## extension slides

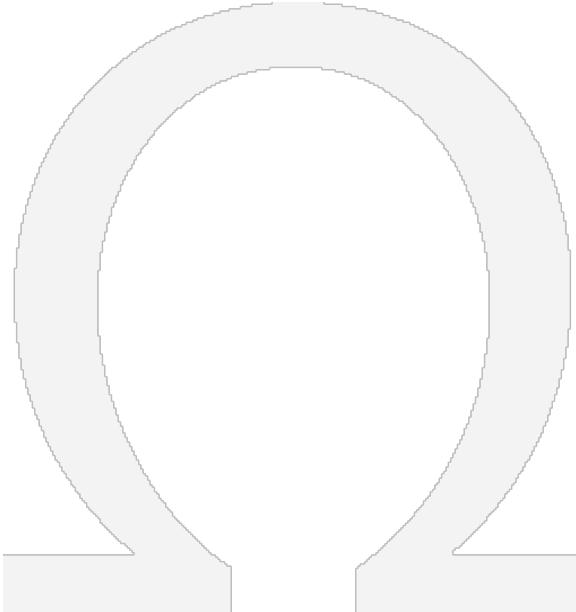
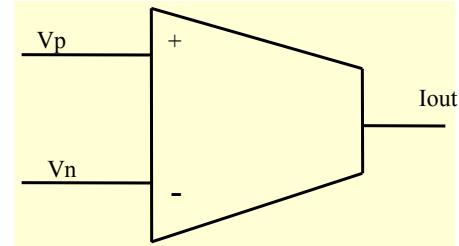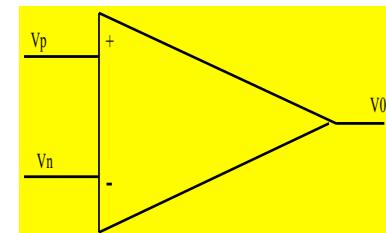
# Operational amplifiers : a large zoo

Omega


- Voltage feedback operational amplifier (VFOA)
- Voltage amplifiers, RF amplifiers (VA,LNA)
- Current feedback operational amplifiers (CFOA)
- Current conveyors (CCI, CCII +/-)
- Current (pre)amplifiers (ISA,PAI)
- Charge (pre)amplifiers (CPA,CSA,PAC)
- Transconductance amplifiers (OTA)
- Transimpedance amplifiers (TZA,OTZ)
- Mixing up open loop (OL) and closed loop (CL) configurations !


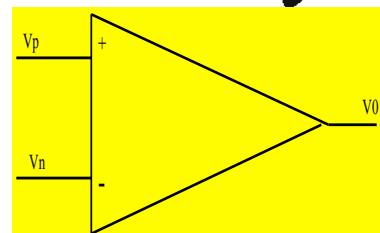
# Only 4 open-loop configurations


- Voltage operationnal amplifiers (OA, VFOA)

- $V_{out} = G(\omega) V_{in \text{ diff}}$
- $Z_{in+} = Z_{in-} = \infty$   $Z_{out} = 0$




- Transimpedance operationnal amplifier (CFOA !)

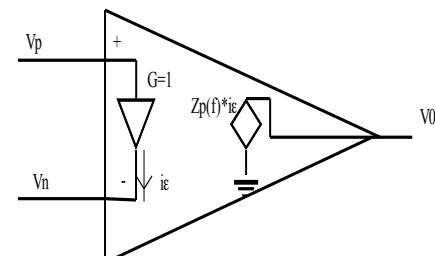- $V_{out} = Z(\omega) i_{in}$
- $Z_{in-} = 0$   $Z_{out} = 0$




- Current conveyor (CCI,CCII)

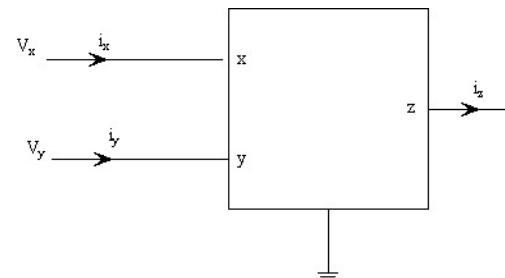- $I_{out} = G(\omega) I_{in}$
- $Z_{in} = 0$   $Z_{out} = \infty$



- Transconductance amplifier (OTA)

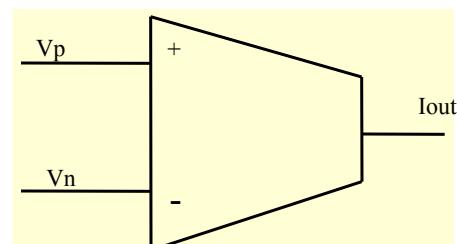
- $I_{out} = G_m(\omega) V_{in \text{ diff}}$
- $Z_{in+} = Z_{in-} = \infty$   $Z_{out} = \infty$


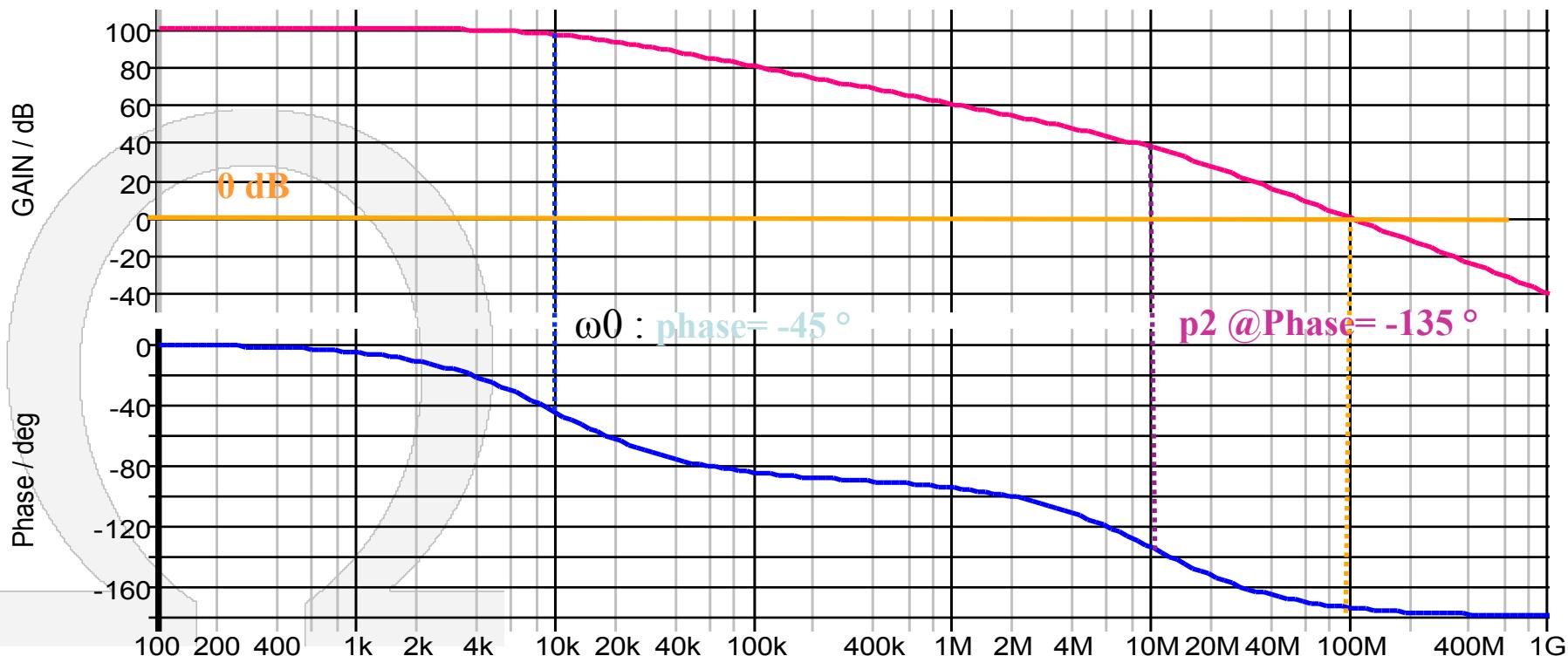
# Open loop gain variation with frequency

Omega

- Define exactly what is « gain »  $v_{out}/v_{in}$ ,  $v_{out}/i_{in}$ ...
- « Gain » varies with frequency :  $\mathbf{G}(j\omega) = \mathbf{G}_0 / (1 + j \omega / \omega_0)$ 
  - $\mathbf{G}_0$  low frequency gain
  - $\omega_0$  dominant pole
  - $\omega_c = \mathbf{G}_0 \omega_0$  Gain-Bandwidth product (sometimes referred to as unity gain frequency)



# Feedback : an essential tool

*Omega*

- Improves gain performance
  - Less sensitivity to open loop gain ( $a$ )
  - Better linearity


- Essential in low power design

- Potentially unstable


- Feedback constant :  $\beta = E/X_{out}$

- Open loop gain :  $a = X_{out}/E$

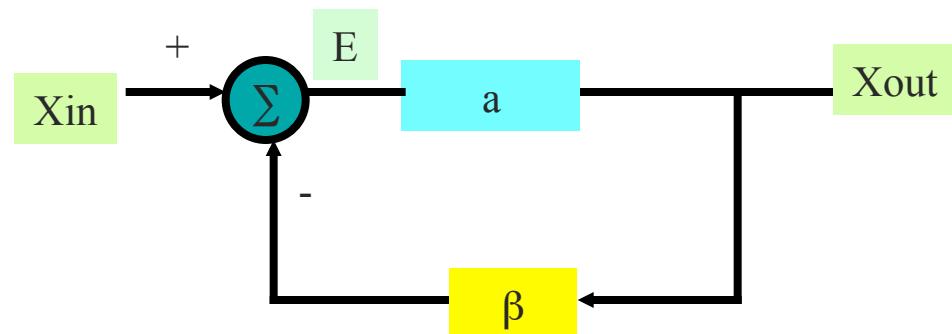- Closed loop gain :  $X_{out}/X_{in} \rightarrow 1/\beta$



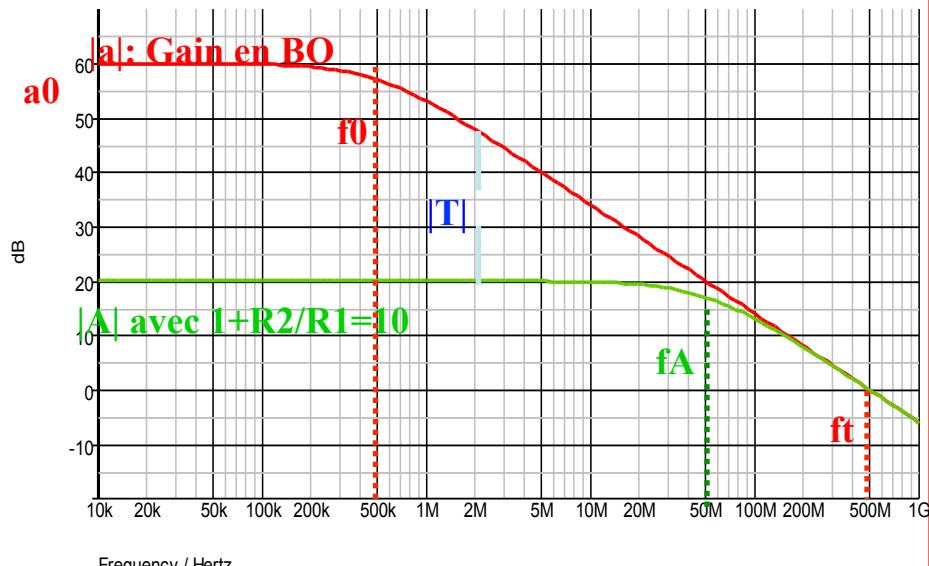
$$\frac{X_{out}}{X_{in}} = \frac{a}{1 + a\beta} = \frac{1/\beta}{1 + 1/a\beta}$$


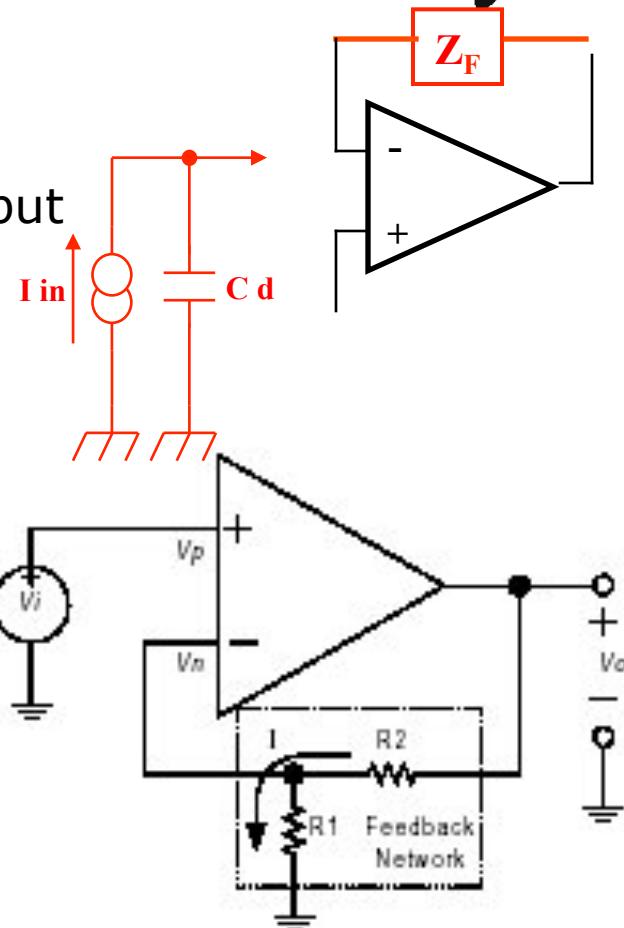
# Only 4 feedback configurations

Omega

- Shunt-shunt = transimpedance
  - Small  $Z_{in}$  ( $= Z_{in}(OL)/T$ ) -> current input
  - small  $Z_{out}$  ( $= Z_{out}(OL)/T$ ) -> voltage output
  - De-sensitizes transimpedance  $= 1/\beta = Z_f$
- Series-shunt
  - Large  $Z_{in}$  ( $= Z_{in}(OL)*T$ ) -> voltage input
  - Small  $Z_{out}$  ( $= Z_{out}(OL)/T$ ) -> voltage
  - Optimizes voltage gain ( $= 1/\beta$ )
- Shunt series
  - Small  $Z_{in}$  ( $= Z_{in}(OL)/T$ ) -> current inp
  - Large  $Z_{out}$  ( $= Z_{out}(OL)*T$ ) -> current
  - Current conveyor
- Series-series
  - Large  $Z_{in}$  ( $= Z_{in}(OL)*T$ ) -> voltage input
  - Large  $Z_{out}$  ( $= Z_{out}(OL)*T$ ) -> current output
  - Transconductance
  - Ex : common emitter with emitter degeneration





# Voltage Feedback Operationnal Amplifiers

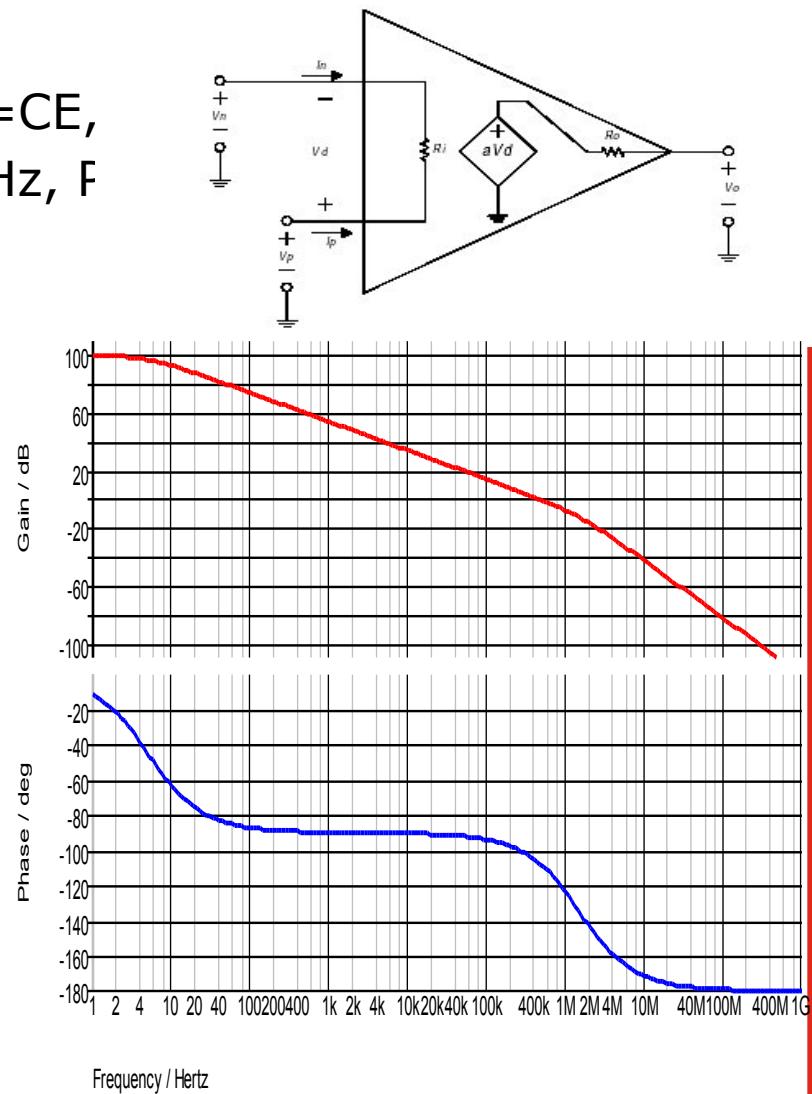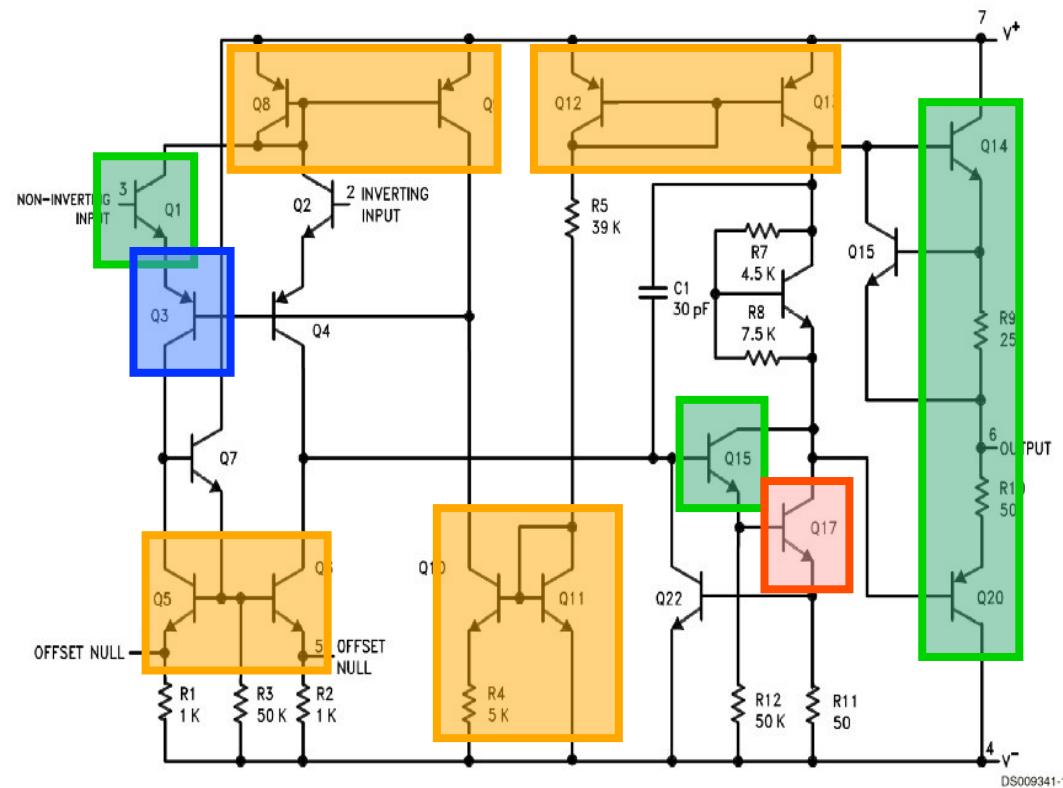(1)

Omega

- Back to the 70's : LM741
  - 3 stages : Paraphase=CE, Darlington=CE,
  - $G_0 = 200\,000$ ,  $f_0 = 5\text{Hz}$ ,  $\text{GBW} = 1\text{ MHz}$ ,  $F$






Schematic diagramm of a LM741 (1970) ©National Semiconductors

# Voltage Feedback Operationnal Amplifiers

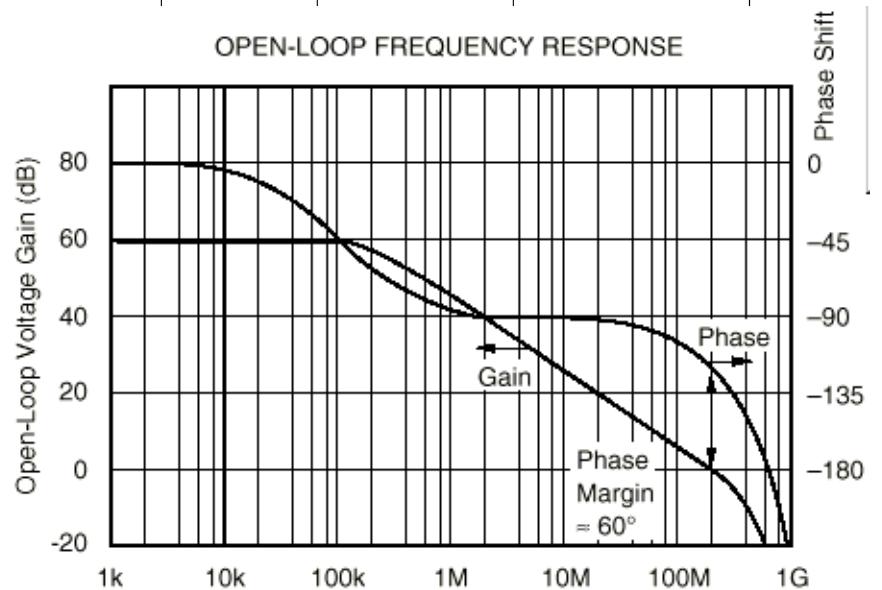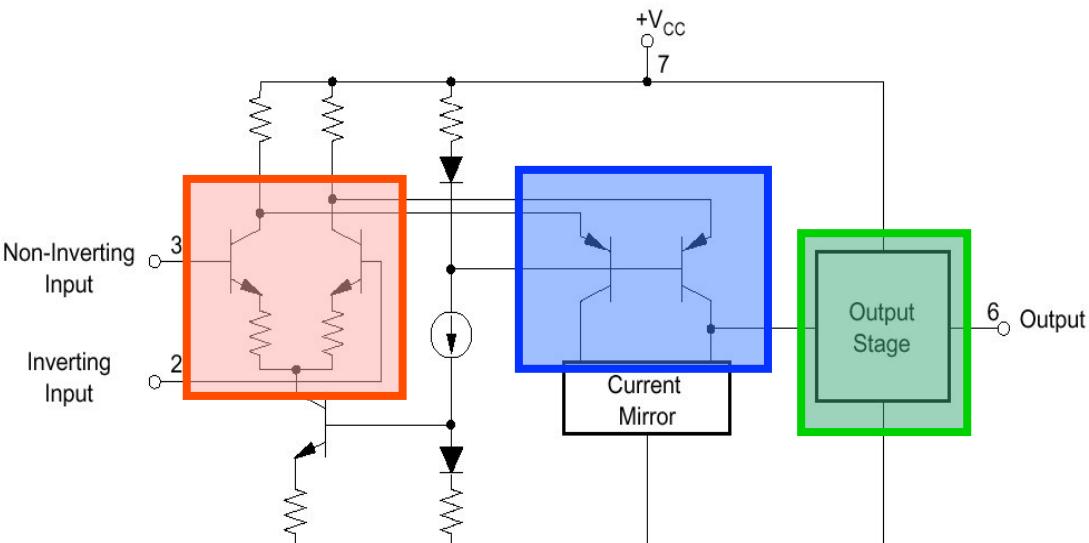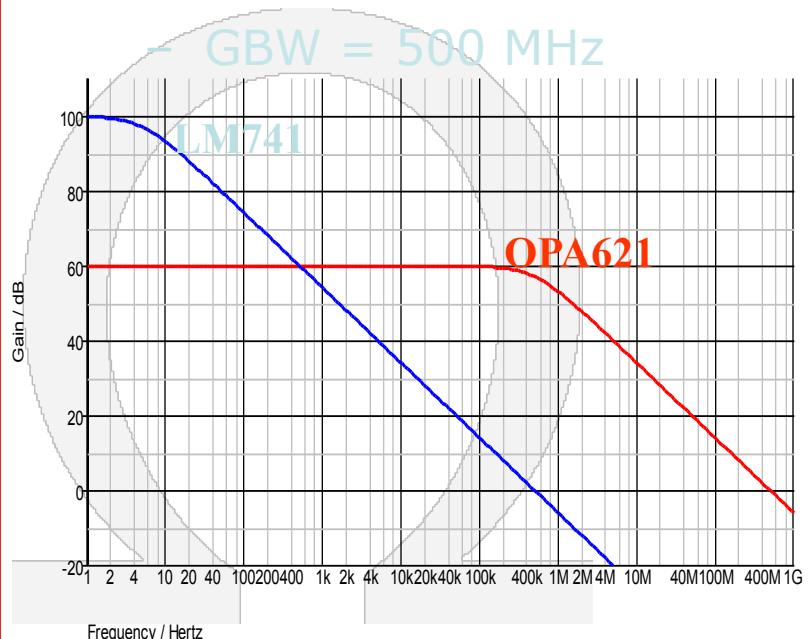(2)

Omega

- Breakthrough in the 90's : OP620-621
  - 2 stages : Cascode=CE, Push-pull = CC
  - $P_d = 250 \text{ mW}$
  - $G_0 = 1\,000$
  - $f_0 = 500\text{kHz}$




Open loop frequency response of OP620

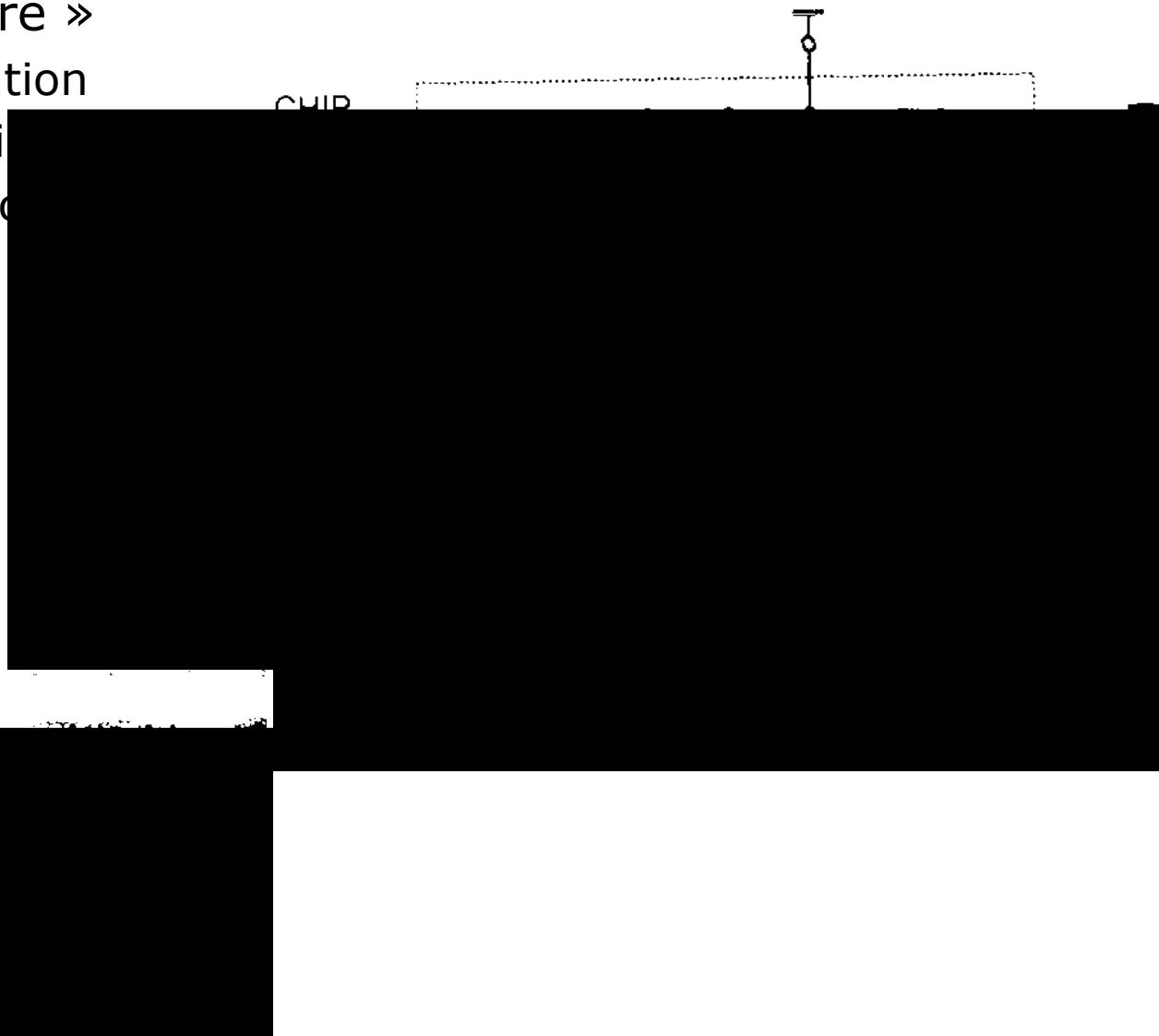
# 40 Gb/s transimpedance amplifier

Omega

- « Simple architecture »
  - CE + CC configuration
  - SiGe bipolar transistor
  - CC outside feedback
  - « pole splitting »




## Exercice slides

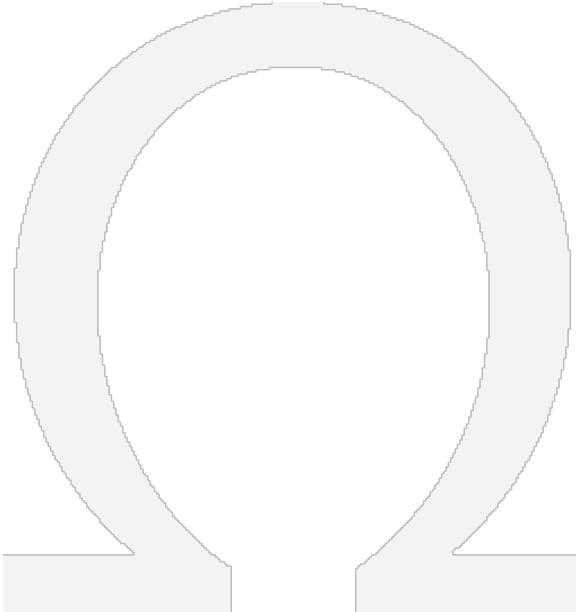


# Ideal charge preamp

Omega

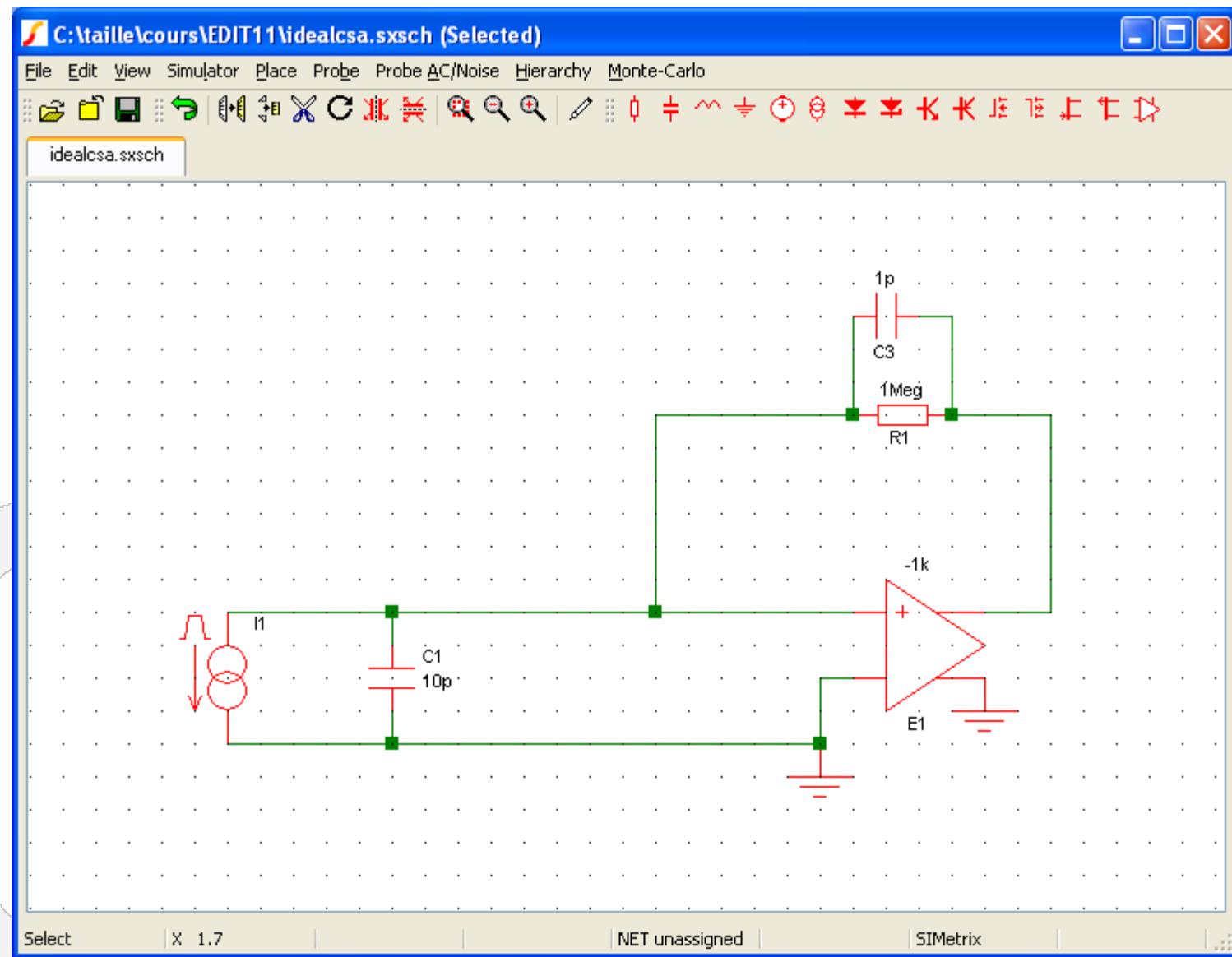

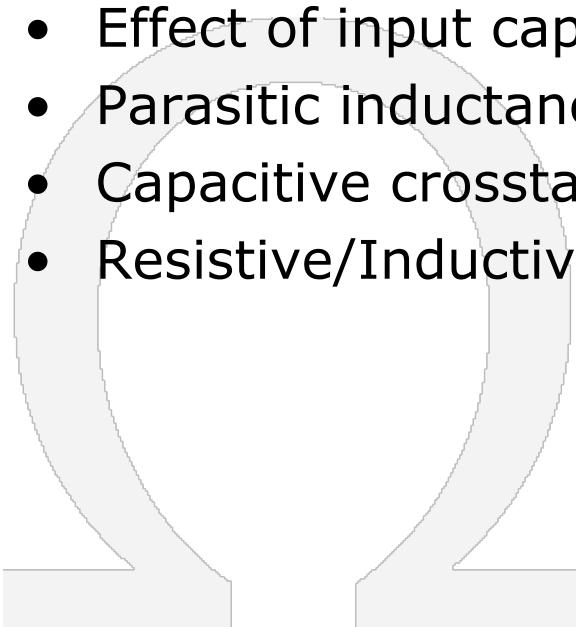
# Ideal charge preamp

- Simulate impulse response
- Frequency response
- Input impedance
- Ballistic deficit
- Effect of amplifier gain
- Effect of resistive feedback
- Test pulse injection
- Effect of input capacitance
- Parasitic inductance
- Capacitive crosstalk
- Resistive/Inductive ground return




# Non ideal charge preamp

Omega

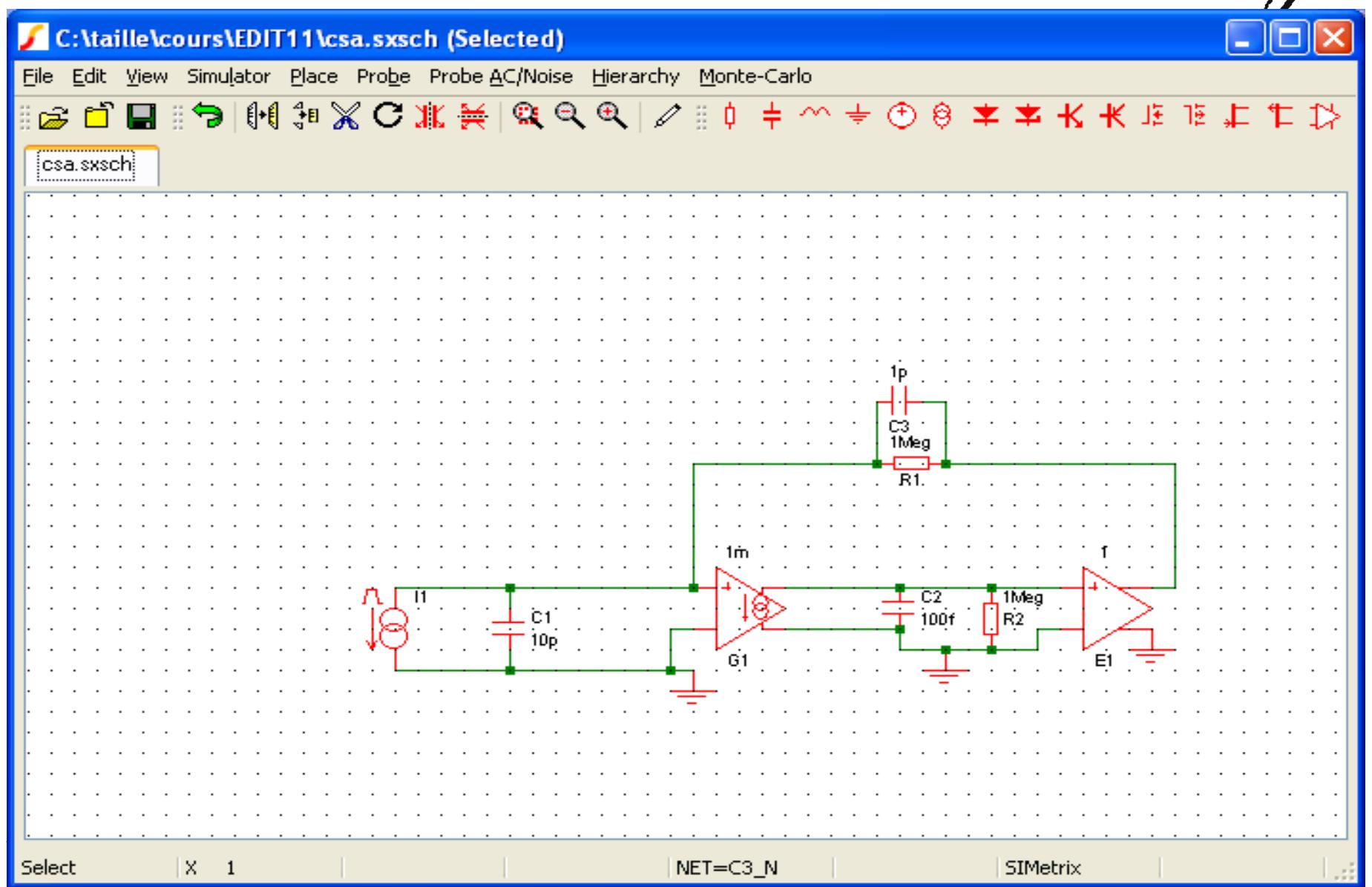


## backup slides

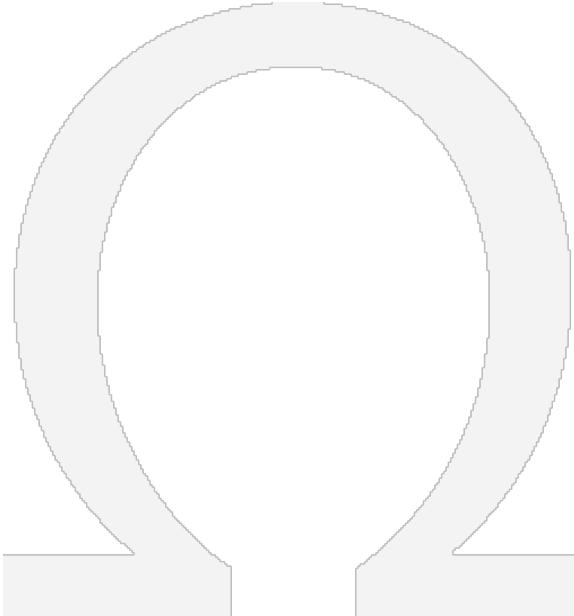
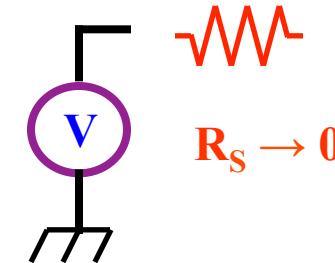
# The foundations of electronics


- Voltage generators or source

- Ideal source : constant voltage, independent of current (or load)
- In reality : non-zero source impedance  $R_s$




- Current generators

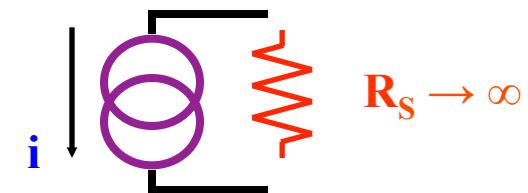- Ideal source : constant current, independent of voltage (or load)
- In reality : finite output source impedance  $R_s$


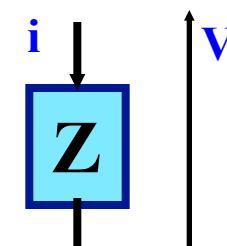
## Ohms' law

- $Z = R, 1/j\omega C, j\omega L$
- Note the **sign** convention



# Frequency domain & time domain

- Frequency domain :


- $V(\omega, t) = A \sin(\omega t + \phi)$ 
  - Described by amplitude and phase ( $A, \phi$ )
- Transfer function :  $H(\omega)$  [or  $H(s)$ ]
- = The ratio of output signal to input signal in the frequency domain assuming linear electronics

- Time domain  $V_{out}(\omega) = H(\omega) V_{in}(\omega)$

- Impulse response :  $h(t)$
- = the output signal for an impulse (delta) input in the time domain
- The output signal for any input signal  $v_{in}(t)$  is obtained by convolution : «\*» :
- $V_{out}(t) = v_{in}(t) * h(t) = \int v_{in}(u) * h(t-u) du$

- Correspondance through Fourier transforms



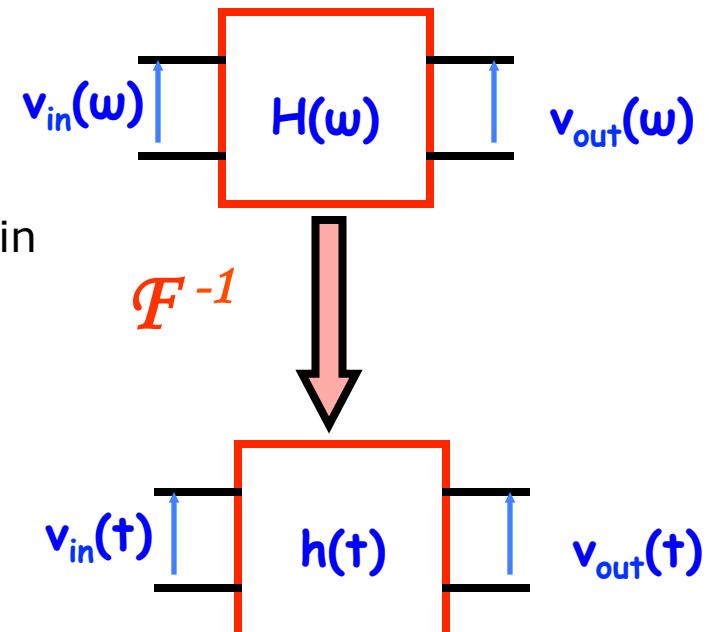
- $X(\omega) = \mathcal{F}\{x(t)\} = \int x(t) \exp(j\omega t) dt$
- a few useful Fourier transforms in appendix



- $H(\omega) = 1 \rightarrow h(t) = \delta(t)$  (impulse)
- $H(\omega) = 1/j\omega \rightarrow h(t) = S(t)$  (step)
- $H(\omega) = 1/j\omega (1+j\omega T) \rightarrow h(t) = 1 - \exp(-t/T)$
- $H(\omega) = 1/(1+j\omega T) \rightarrow h(t) = \exp(-t/T)$

# Frequency response

- Bode plot
  - Magnitude (dB) =  $20 \log |H(j\omega)|$
  - -3dB bandwidth :  $f_{-3dB} = 1/2\pi RC$ 
    - $R=10^5\Omega$ ,  $C=10\text{pF} \Rightarrow f_{-3dB}=160\text{ kHz}$
    - At  $f_{-3dB}$  the signal is attenuated by  $3\text{dB} = \sqrt{2}$ , the phase is  $-45^\circ$

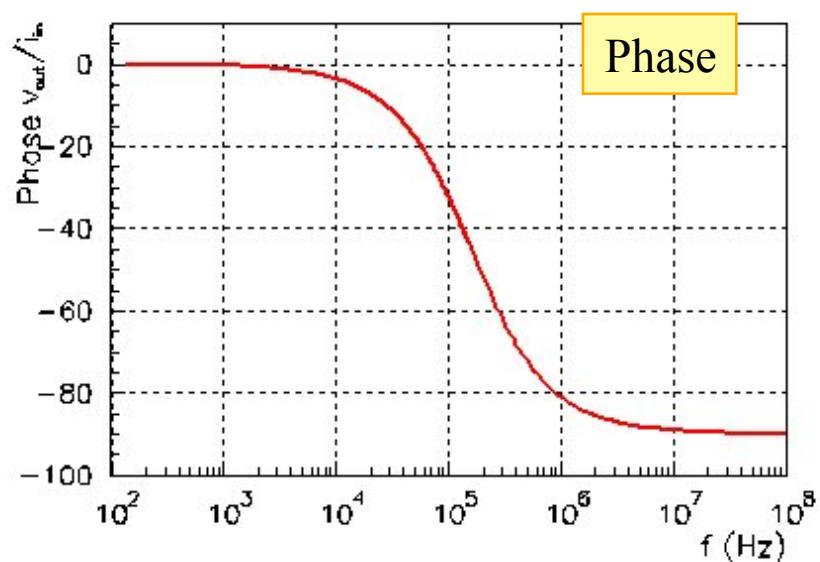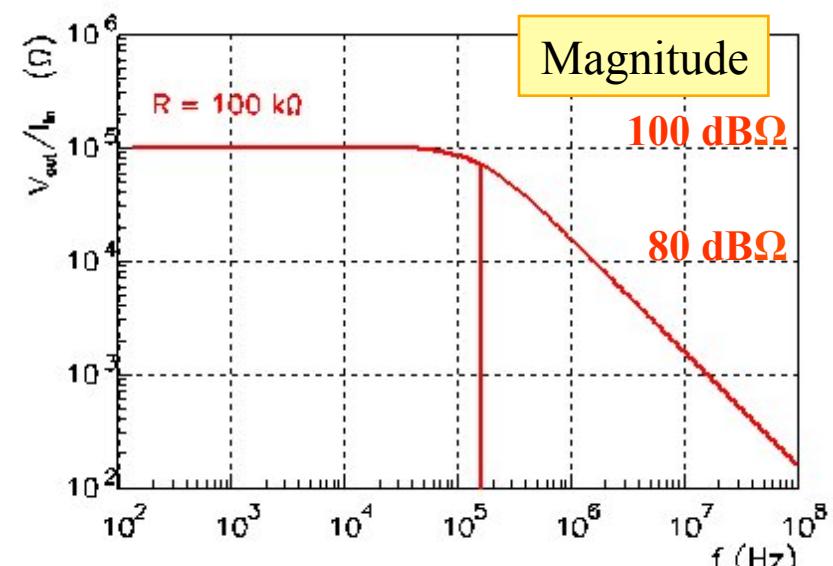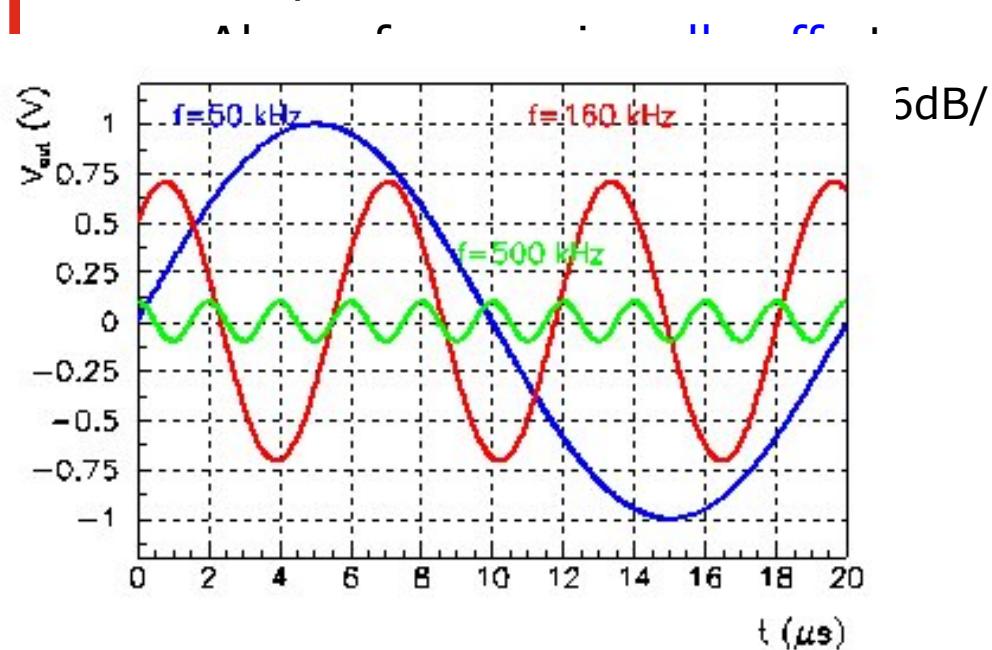

# Time response

## Impulse response

- $h(t) = \mathcal{F}^{-1} \{ R/(1+j\omega RC) \}$   
 $= R/\tau \exp(-t/\tau)$
- $\tau (\text{tau}) = RC = 1 \mu\text{s}$  : time constant

- Step response : rising exponential

- $H(t) = \mathcal{F}^{-1} \{ 1/j\omega R/(1+j\omega RC) \}$   
 $= R [ 1 - \exp(-t/\tau) ]$
- Rise time :  $t_{10-90\%} = 2.2 \tau$
- « eye diagramm »

