

Serial powering

Marc Weber, RAL

Common ATLAS CMS Electronics Workshop for SLHC

What is SP? Why is it needed?


Experimental results and why is SP not noisy?

AC-coupling

Risk analysis and over-current protection

Power efficiency; SP real estate

 **SMARP: a general-purpose custom SP
chip for ATLAS and CMS; strip and pixels**




How does SP work?

Four elements

1. Current source (external power supply)
2. Shunt regulator and power device (digital power)
3. Linear regulator (for analog power)
4. AC or opto-coupling of signals

Need to get custom, rad-hard versions of 2. to 4.

Regulators

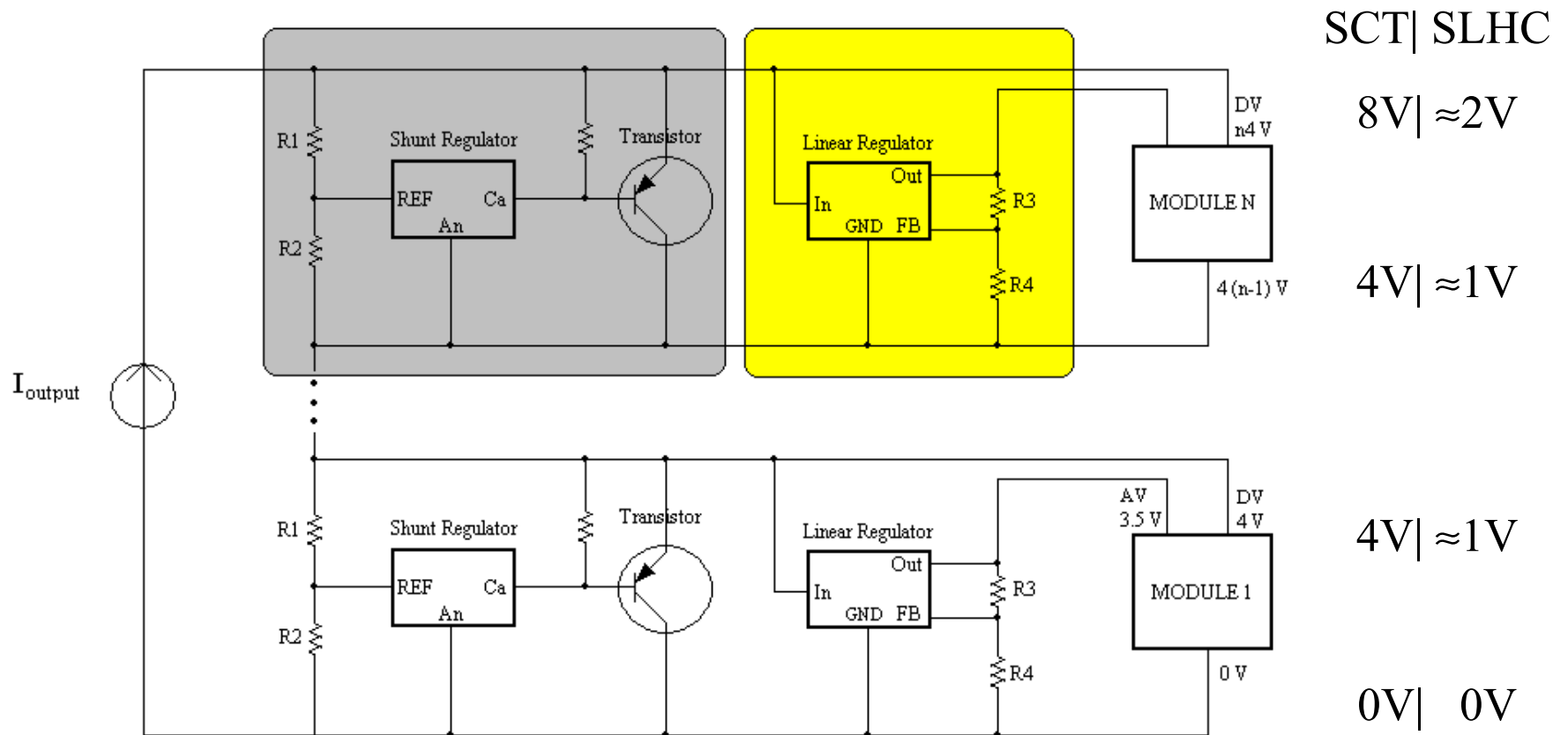

Chain of modules at different voltages; “recycle” current

Chips on a module are connected in parallel (as usual)

analog ground, digital ground and HV ground are tied together for each module (as usual) \Leftrightarrow floating HV supplies

Why independent powering fails at SLHC ?

Chip voltage goes down, current stays the same; more channels

1. Don't get 5 or 10 times more cables in
2. Power efficiency is too low (50% ATLAS SCT \Leftrightarrow \sim 15% SLHC)
3. Cable material budget: 0.2% of R.L. per layer (barrel normal incidence) \Leftrightarrow 1% or 2% SLHC
4. Packaging constraints

Each reason by itself is probably sufficient for a No-No



History

Idea is old, but was only seriously considered a couple of years ago

First pioneering work was done by Bonn group for pixels

T. Stockmanns, P. Fischer, F. Hugging, I. Peric, O. Runolfsson, N. Wermes, “Serial powering of pixel modules”, Nucl. Instr. & Meth. A511 (2003) 174–179; D. B. Ta, T. Stockmanns, F. Hugging, P. Fischer, J. Grosse-Knetter, Ö. Runolfsson, N. Wermes, “Serial Powering: Proof of Principle demonstration of a scheme for the operation of a large pixel detector at the LHC”, Nucl. Instr. Meth. A557 (2006) 445-459

RAL picked it up 2 years ago for strips


Marc Weber, Giulio Villani, Mika Lammentausta, Proceedings of the 11th workshop on electronics for LHC and future experiments, CERN-LHCC-2005-038, (2005) pp. 214-217;

Marc Weber, Giulio Villani, “Serial Powering of Silicon Strip Detectors at SLHC”, Proceedings of the 6th “Hiroshima” conference on Silicon detectors (2006); Carl Haber, “A Study of Large Area Integrated Silicon Tracking Elements for the LHC Luminosity Upgrade”, Proceedings of the 6th “Hiroshima” conference on Silicon detectors (2006).




Initially main concern was noise; focus moving to system aspects now; reliability; ASIC specs and design

Half-stave setup


Six serially powered ATLAS pixel modules

 

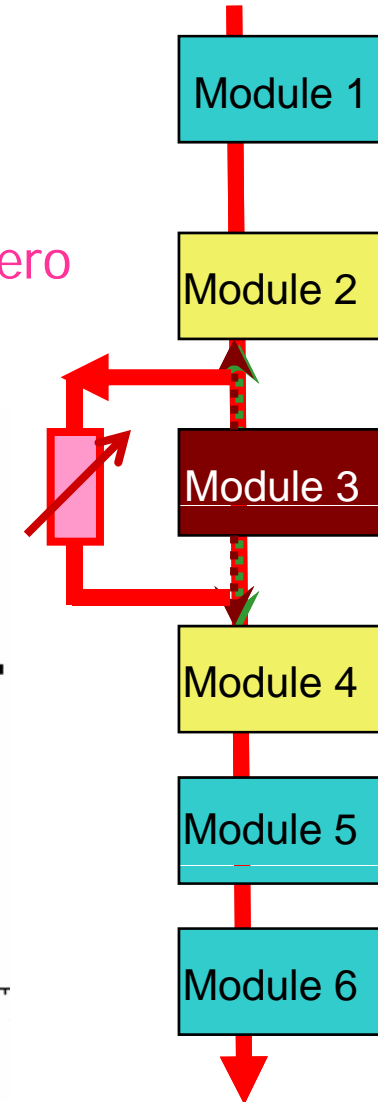 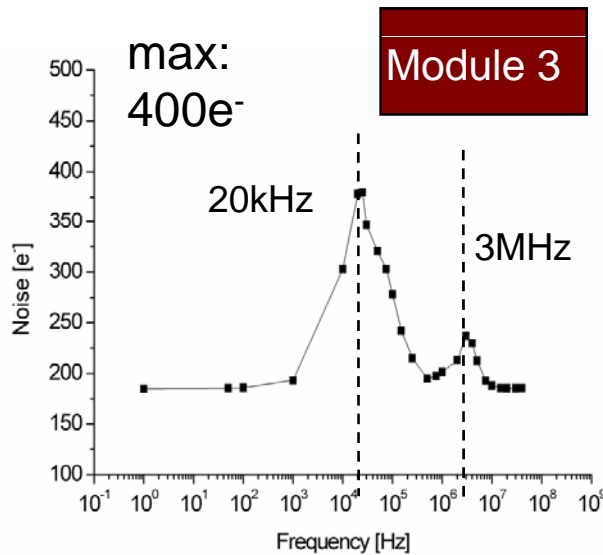- noise comparison
 - SP stave versus PP single module operation
- effect of one noisy module on the chain
 - force one module noisy by setting all thresholds to zero
- frequency dependent noise pickup negligible



Serial powering of six ATLAS SCT modules

 

SP
interface
board

RAL clean room. This was also used for QA of ~800 SCT modules

Noise performance of 6 SCT modules

For more details see my talk at the “Hiroshima” conference STD6

 


Figure 3. Average noise (ENC) for six SCT modules powered independently (IP) or in series (SP). The modules were run for more than 24h before collecting the data shown. The statistical precision of the data points varies between 1.3 and 5 e.

Conclusion is valid for all channels

Gain does not change either

Created noise sources by various means: current injection at different frequencies; HV off for 1 module; increased threshold for 1 module

⇔ SP circuitry copes nicely with it


Precise measurements; noise performance of SP is excellent

Implement SP on densely packed supermodule


For more details see Carl Haber's talk at the "Hiroshima" conference STD6

Testbed for electrical system design; allows search for noise sources and study G+S issues in challenging packaging arrangement

 LBNL SP supermodule with 6 hybrids (no sensors)



 same LBNL SP supermodule with 5 hybrids
and 1 module



- supermodule is electrically functional and noise performance is promising
- This is part of our work program for the next few months

Why is there no conductive interference (noise) between modules?

- What about **current fluctuations**?

- a) modules cannot sink current, current is conserved \Leftrightarrow no problem

- (shunt regulators can cope with current fluctuations under normal conditions)

- What about **voltage fluctuations**?

- a) IR drops are minimum (since current is constant) \Leftrightarrow no damage to regulators, minimum pick-up from power lines

- b) Module voltage fluctuations do not influence neighbouring modules since voltages are derived by local shunt regulators




SP systems tend to be intrinsically quiet; issue of different grounds in a dense environment is being studied by stave program

AC – coupling of signals

There are three ways to implement this

(slide courtesy Francis Anghinolfi)

 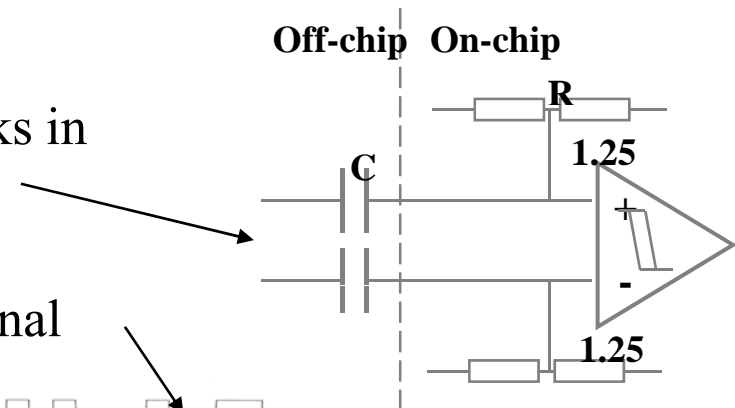 1. Use AC coupling with RC time constant longer than the longer possible “one” state \Leftrightarrow for ABCD protocol 3.6 μ s \Leftrightarrow **not** preferred solution
2. Add **hysteresis (feed-back)** to the chip LVDS receiver \Leftrightarrow works fine for pixel and strips; works in multi-drop bus configuration as well
3. adopt a RZ or a Manchester encoding on L1 signal



NRZ
one: is +1
zero: is -1

RZ
one: is pulse of duration T/2
zero: is no pulse

Manchester
one: is positive transition in center of bit-interval
zero: is negative transition in center of bit-interval
(derived by multiplying NRZ with the clock)


Miller
one: is transition in center of bit-interval
zero: is no transition, unless followed by another zero, in which case a transition is placed at the end of the bit-interval

Getting AC coupling to run took some effort, but it works


AC LVDS coupling

Tested AC LVDS coupling with dedicated test circuits for large range of duty cycles and frequencies



120 MHz

 

40 MHz

 

1 MHz

  


1 MHz

This works just fine, not only for DC balanced protocol

works for multi-drop bus cables on staves as well


We are currently studying this in more detail

Risk due to broken connections: IP vs SP

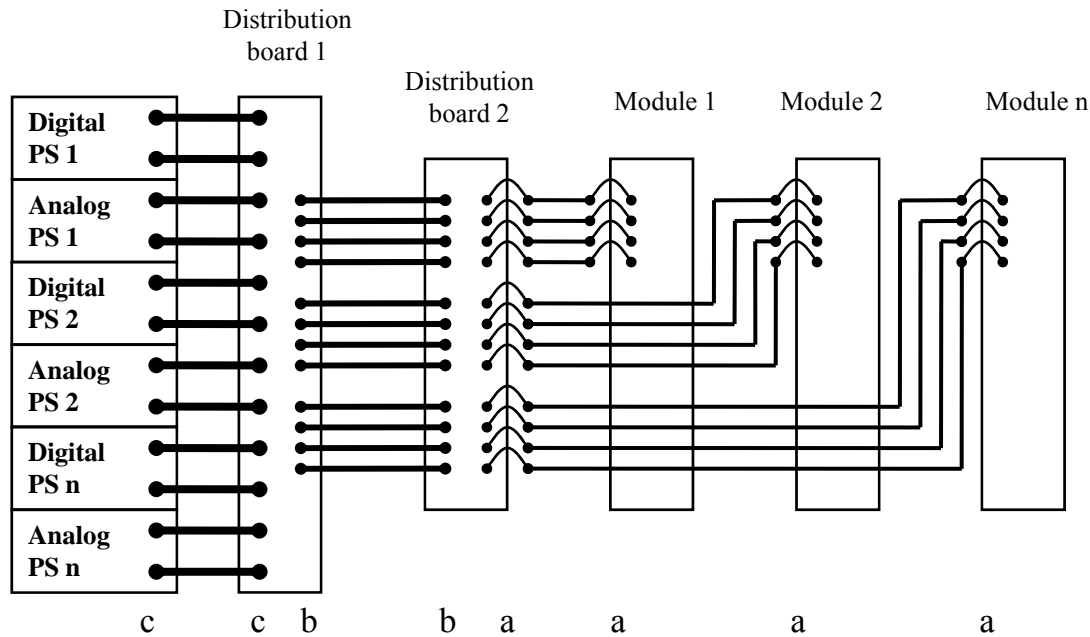

IP

Independent Powering	Wire bonds	Cables Type 1	Cables Type 2
Connections (analog + digital)	$4n + 4n$	$4n + 4n$	$4n + 4n$
Probability of a failure	a_{IP}	b_{IP}	c_{IP}
Lost modules	1	1	1

 


SP

Serial Powering	Wire bonds	Cables Type 1	Cables Type 2
connections (analog + digital)	$2(n+1)$	4	4
Probability of a failure	a_{SP}	b_{SP}	c_{SP}
Lost modules	n	n	n

SP: one broken connection loses n modules,

however much less cables (factor $2n$ less) and less connections

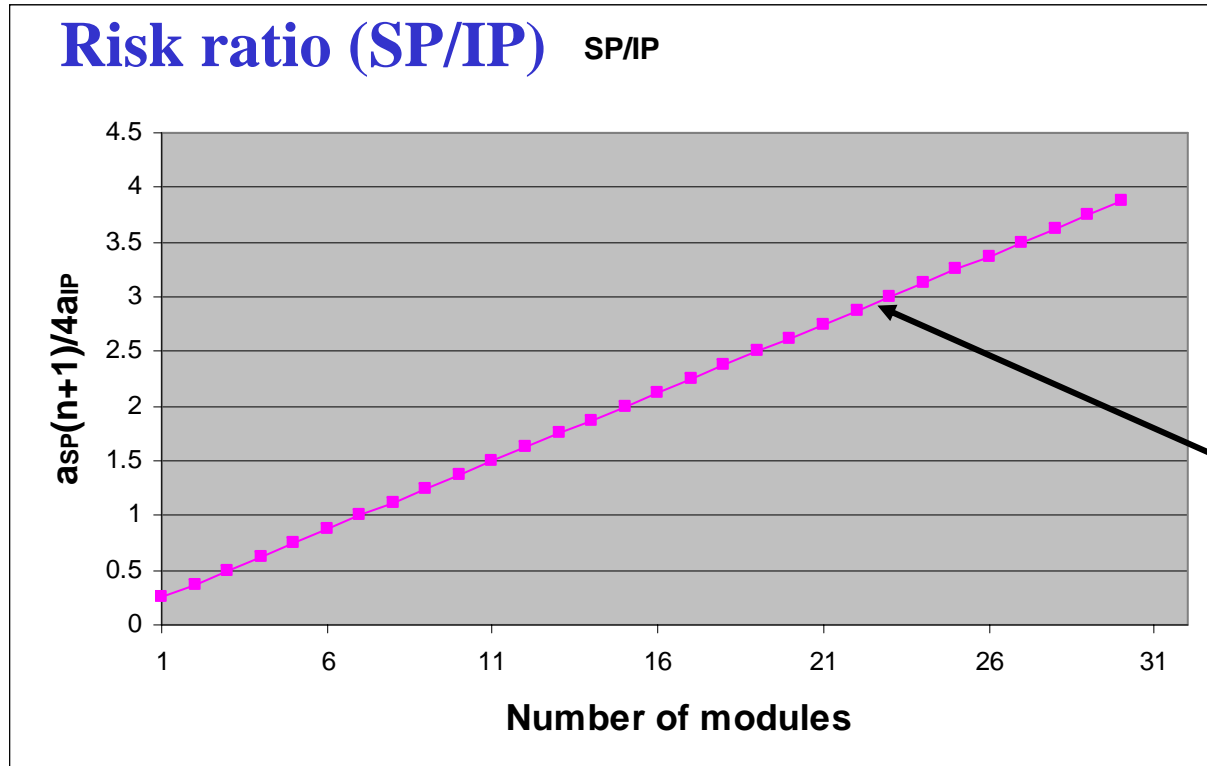Risk := (# of power connections) x (probability of a failure) x (# of modules lost per failure)



$$\frac{a_{SP}(n+1) + 2b_{SP} + 2c_{SP}}{4(a_{IP} + b_{IP} + c_{IP})}$$

Make your own choices for values of a, b, and c!

Mine are here

$$(a_{SP} = 1/2 a_{IP}; b = c = 0)$$

Risk ratio ~ number of modules/4

SP is more risky than IP, but not by much. Risk is manageable if connections are made robust (exploiting the huge real estate gains of SP)


Overcurrent protection

Power transistor is weak point of SR in case of module failure

PT carries full current in case of module open \Leftrightarrow risk of burn out if not cooled properly

Protect against this by automatically reducing SR voltage in case of overcurrent condition \Leftrightarrow same idea can be used to set module into “stand-by” mode

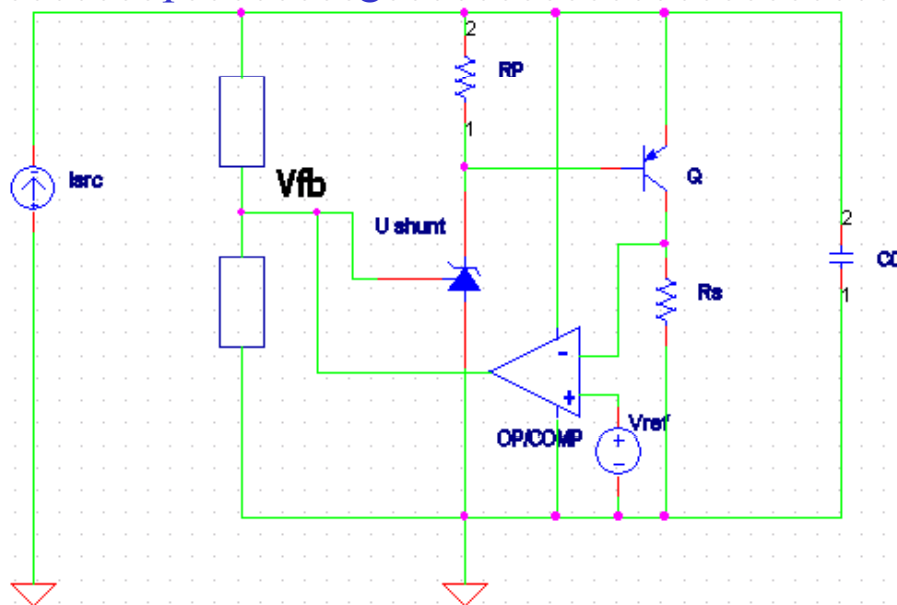Simplified diagram for illustration of overcurrent protection




Demonstrator board with discrete components performs as simulated

\Leftrightarrow voltage reduction from 4V to 1 V while standing full current (~ 1.5 A)

Overcurrent protection measurements

Basic test of the idea using discrete component circuits

Test results:

 

“Stand-by mode”
if over-current

voltage
decreases from
4V to 1V within
3 ms

due to current
increase from 40
mA to 1.5 A

Power efficiency

Consider n modules with module current and voltages I and V , off-detector cable resistance R , DC-DC gain g , define $x = IR/V$

- power consumed by n modules is always: $n I V$
- power wasted in the cable depends on powering scheme
- Low V is bad, large R and I are bad**

	I_{sm}	V_{drop}	V_{sm}	P_{cab}	Efficiency: P_{sm}/P_{total}
IP	$n I$	$I R$	V	$n I^2 R$	$1/[1 + x]$
PP	$n I$	$n I R$	V	$n^2 I^2 R$	$1/[1 + nx]$
SP	I	$I R$	nV	$I^2 R$	$1/[1 + x/n]$
DC-DC	$(n/g) I$	$(n/g) I R$	gV	$(n/g)^2 I^2 R$	$1/[1 + xn/g^2]$


← considers cable losses only for now

SP: want to have many modules in series

DC-DC: want to have few modules in parallel

Regulator power

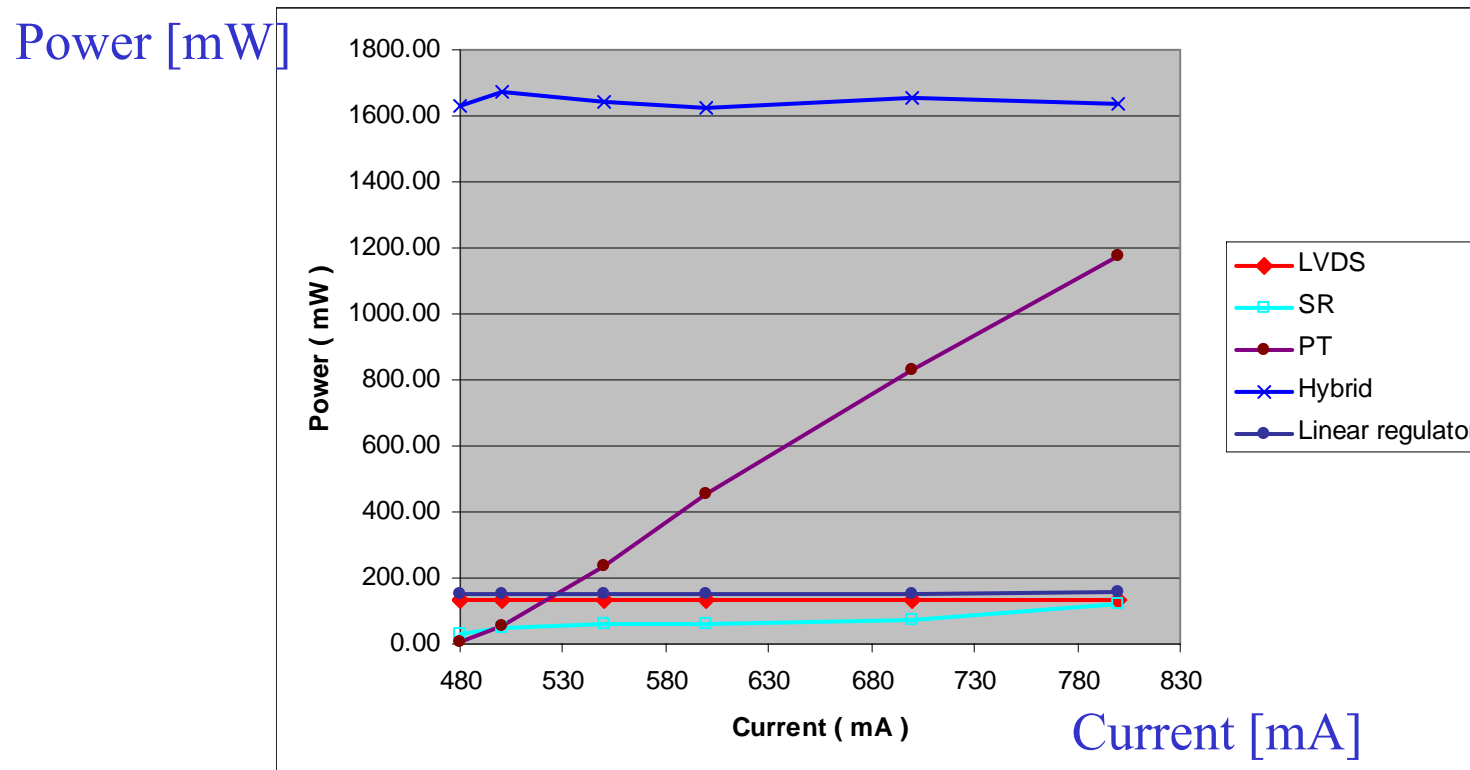
We performed a detailed breakdown of our power consumption of SP circuitry (these were made with a 4 ABCD chip hybrid)



- power consumed in PT is \sim (PS current – module current)
- power consumed elsewhere is essentially constant

Regulator inefficiency

Same data presented as an inefficiency

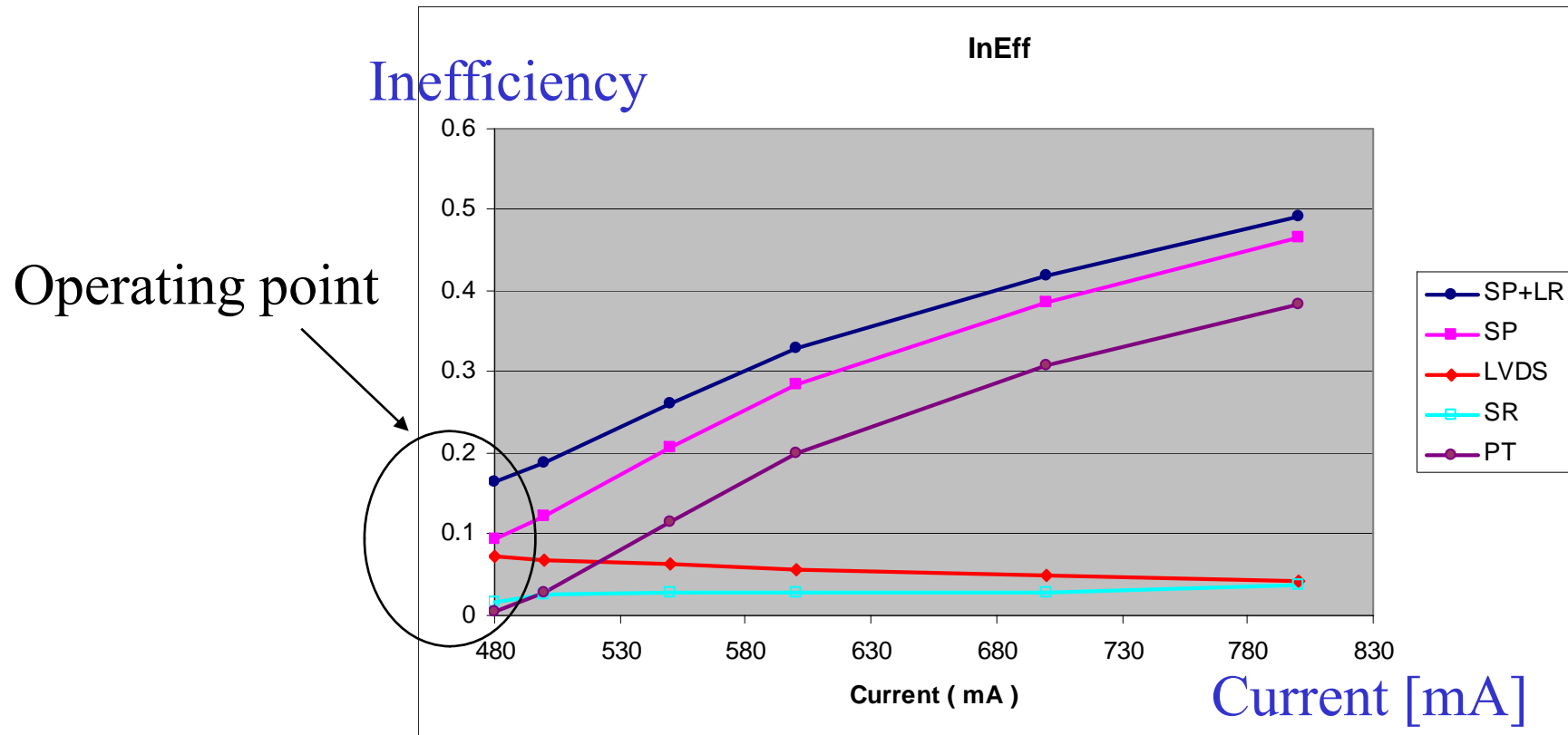


- Note that operating current depends on digital current fluctuations
- PT inefficiency dominates for large fluctuations
- we measure 10% SP inefficiency
- Inefficiency of linear regulator (for analog power) is similar

Let's work out a powering example

here $V_{ABC-N} = 2.5 \text{ V}$; $I_H = 2.4 \text{ A}$; 20 hybrids; DC-DC gain = 20

SP: $n=20$; $I_H = I_{PS} = 2.4 \text{ A}$; $V_{PS} = nV_{ABC-N} = 50 \text{ V}$

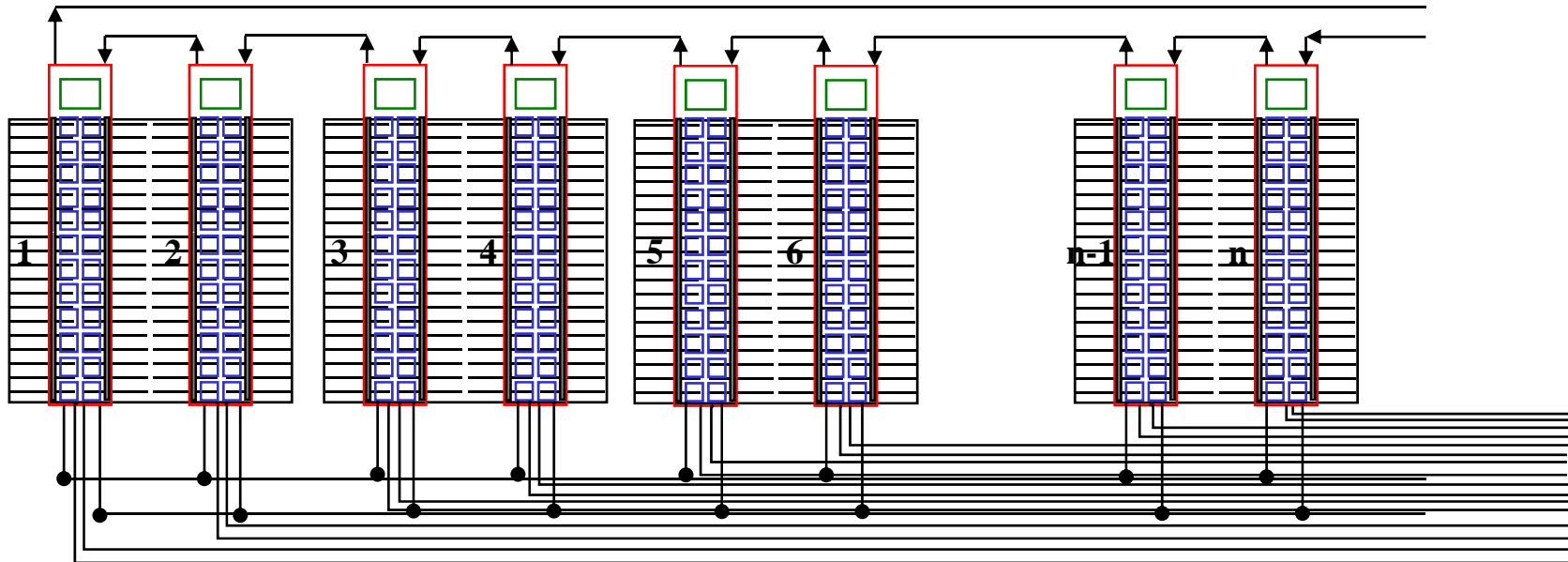Features: saves factor ~ 8 in power cables/length over SCT



DC-DC PP: $n=20$; $g = 20$; $I_{PS} = n/g I_H = 2.4 \text{ A}$; $V_{PS} = gV_{ABC-N} = 50 \text{ V}$

Features: saves factor ~ 8 in power cables as SP, watch IR drops $\Leftrightarrow R_{LMT} \sim 0.1-1 \Omega$

DC-DC IP: $n=1$; $g = 20$; $I_{PS} = I_H/g = 0.12 \text{ A}$; $V_{PS} = gV_{ABC-N} = 50 \text{ V}$

Features: 2x more cables than SCT \Leftrightarrow problematic for strips

Power efficiency


Illustration of various cases:

SCT \Leftrightarrow 4V, 1.5 A, $R=4.5\ \Omega$ \Leftrightarrow $x=1.14$; IP \Leftrightarrow $\varepsilon = 47\%$

SLHC \Leftrightarrow 2.5V, 2.4 A, $R=4.5\ \Omega$ \Leftrightarrow $x=4.3$; SP (only cable losses)

SLHC \Leftrightarrow 1.5V, 4 A, $R=4.5\ \Omega$ \Leftrightarrow $x=12$; SP (only cable losses)

 same but including SR power and LR power (extrapolated from our SCT measurements)



Keep hybrid current low!

SR inefficiency $\sim 7\%$ for 10% digital current variation



LR for analog has similar losses

SR inefficiency is reduced for $0.13\ \mu\text{m}$ CMOS

Real estate of SP circuitry

Current implementation:

  38 x 9 mm² (this is a PCB for cost reasons)
 Built 6-module stave with this set-up which is working fine;
 no redundancy, protection or slow control features



Components	Current <i>Commercial</i>	Future <i>Custom</i>	Comments
Resistor	15	<5	Integrated in ASICs
Capacitor	10	<10	
SR (die)	1	1	2 with redundancy
PT (die)	1		
LVDS (die)	3	1	
AR (die)	1	0	Included in ASICs

Future implementation:

2-3 ASICs, integrated resistors

Redundancy, protection and slow control features

Estimated real estate: <12x10 mm²

System design: slow control

For IP, we have get information on module voltage and current consumption at external power supply


This is not true for SP or PP DC-DC systems

It is desirable to implement a slow control system on SLHC silicon tracker modules \Leftrightarrow get rid of sense wires; need to control redundancy and protection features of the new powering circuitry remotely

Slow control for new power systems is not part of this talk, but needs attention.

Same goes (at later stage) for design of power supplies

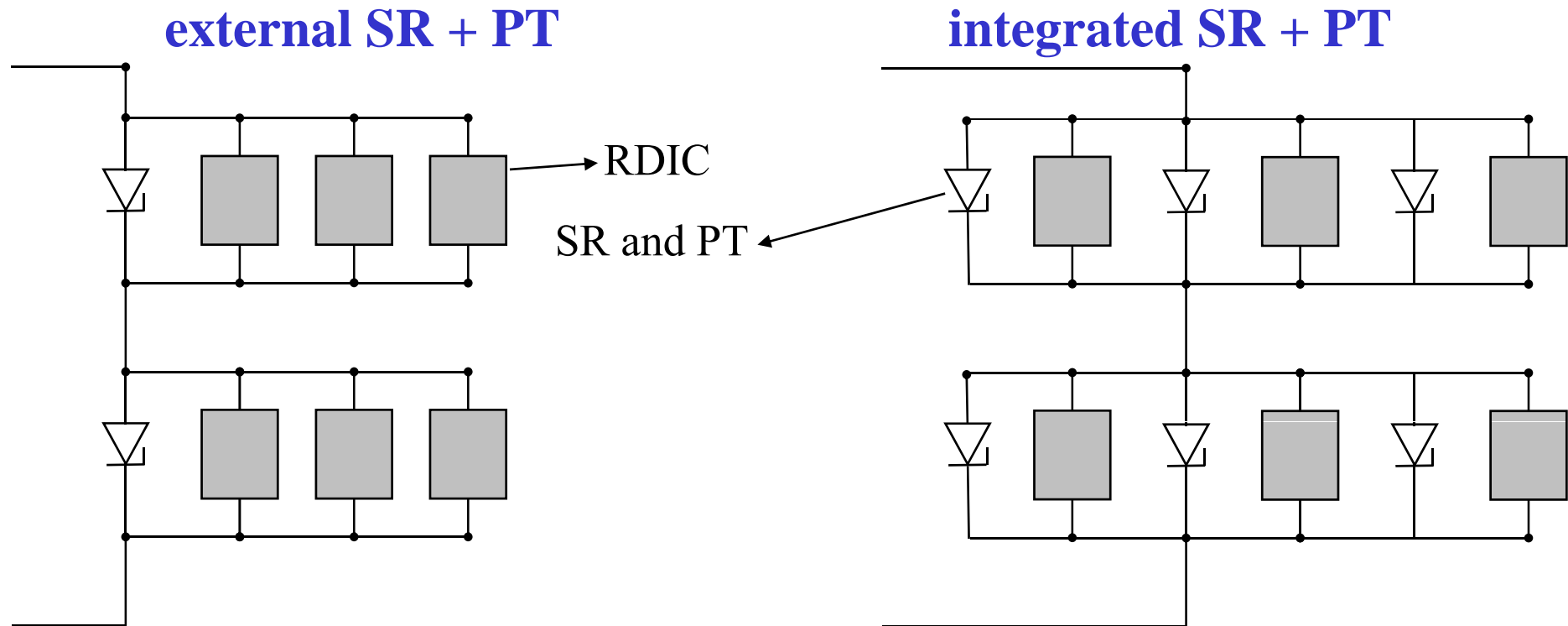Architecture: single or parallel shunt regulator





Integrated (custom) SR used for Bonn pixel results



External commercial SR, used for RAL silicon strip studies

Both options work and choice is not obvious

  - Important properties:
 - Uniformity of threshold voltage
 - Uniformity of resistance
- 3 different shunt regulators on chip:
 - Nominal 2.0V, 2.4V and 2.7V



285 chips

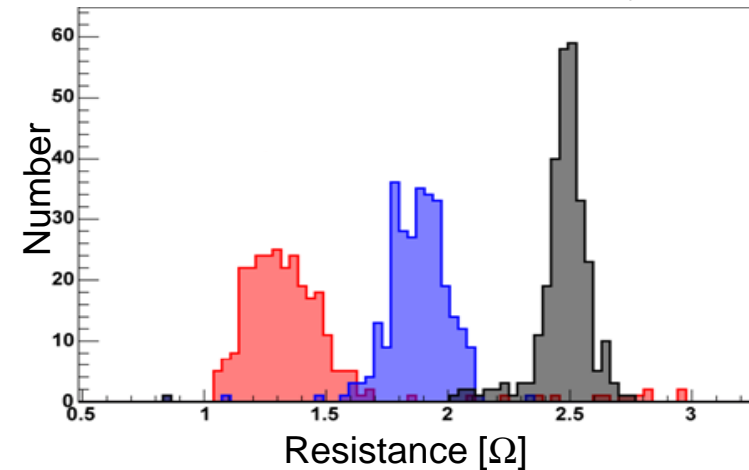 


Proposal for design of multi-purpose SP chip

SMARP1 block diagram

Estimated die size: $\sim 3 \times 3 \text{ mm}^2$

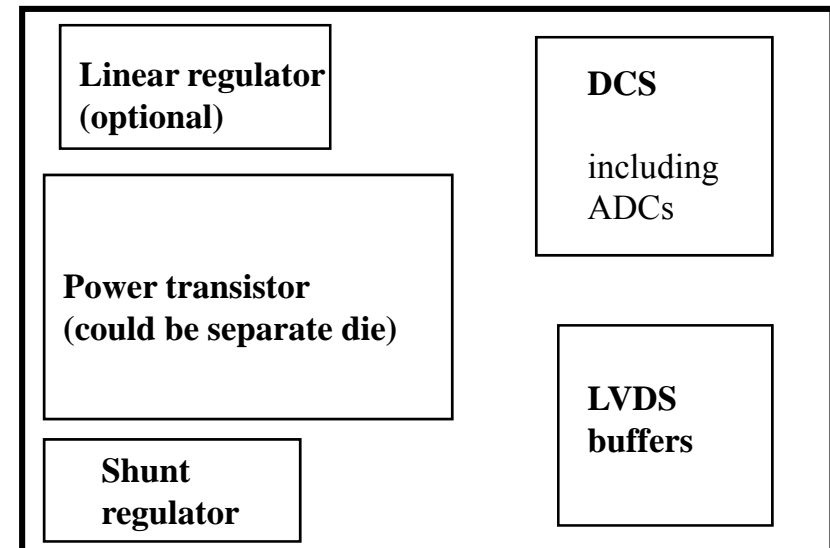- Avoids matching problems between many parallel regulators
- Simplifies system and separates functions
- Allows for cheap MPW run for SMARP
↔ reduce risk and accelerate powering R&D



We worked out detailed specs for SMARP1, excluding the slow control block


The linear regulator is optional and is integrated in the ATLAS ABC-Next

The power transistor could be a separate die removing the high-power constraints


This is a general-purpose chip, which could be used for ATLAS and CMS; strips or pixels

SMARP regulator elements

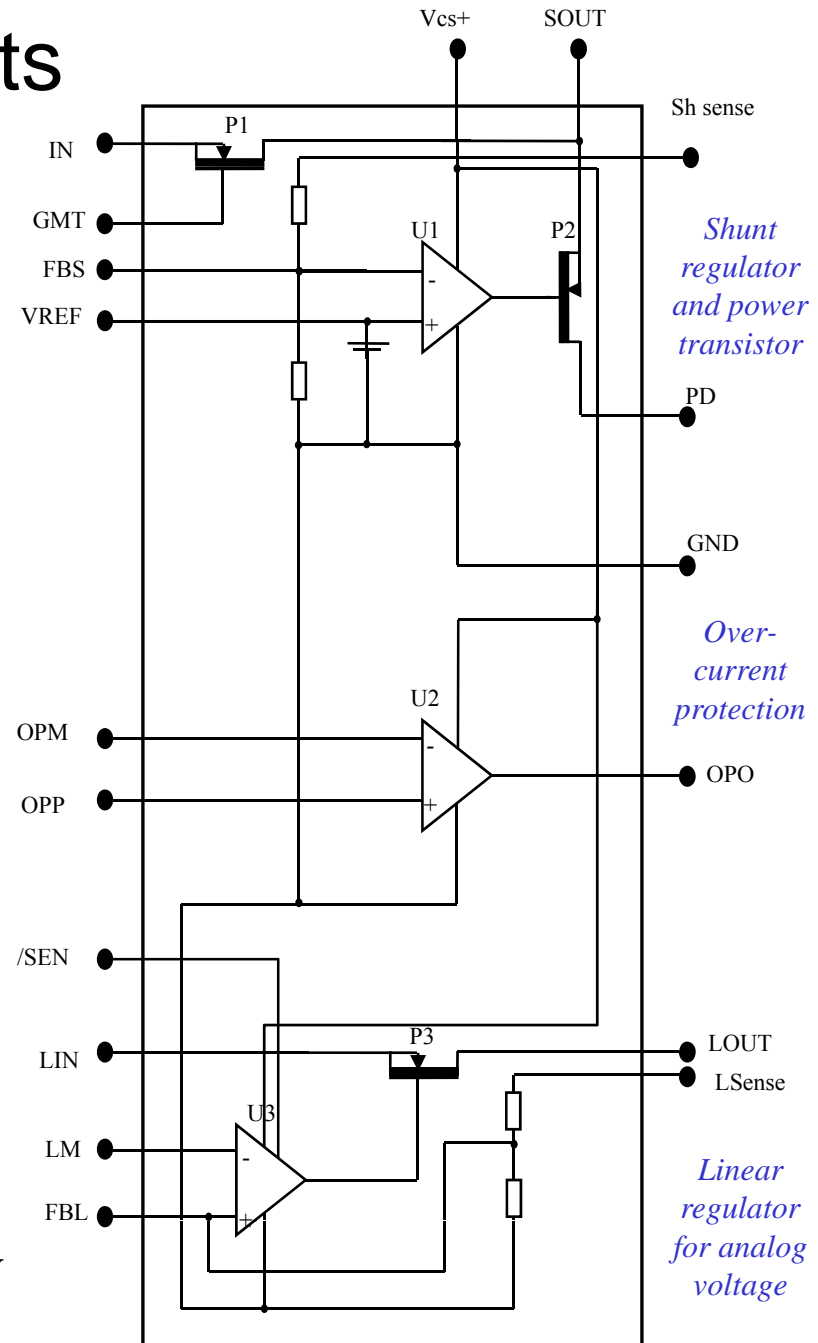- Specs are based on experience with commercial devices
- Design contains protection and slow control features plus LVDS buffer section for AC coupling (not shown here)
- The power transistor P2 could also be an external device (to decouple high and low power objects)
- Linear regulator is optional
- Additional redundancy is gained by placing 2 SMARPs in parallel



Sketch of a schematic using SMARP

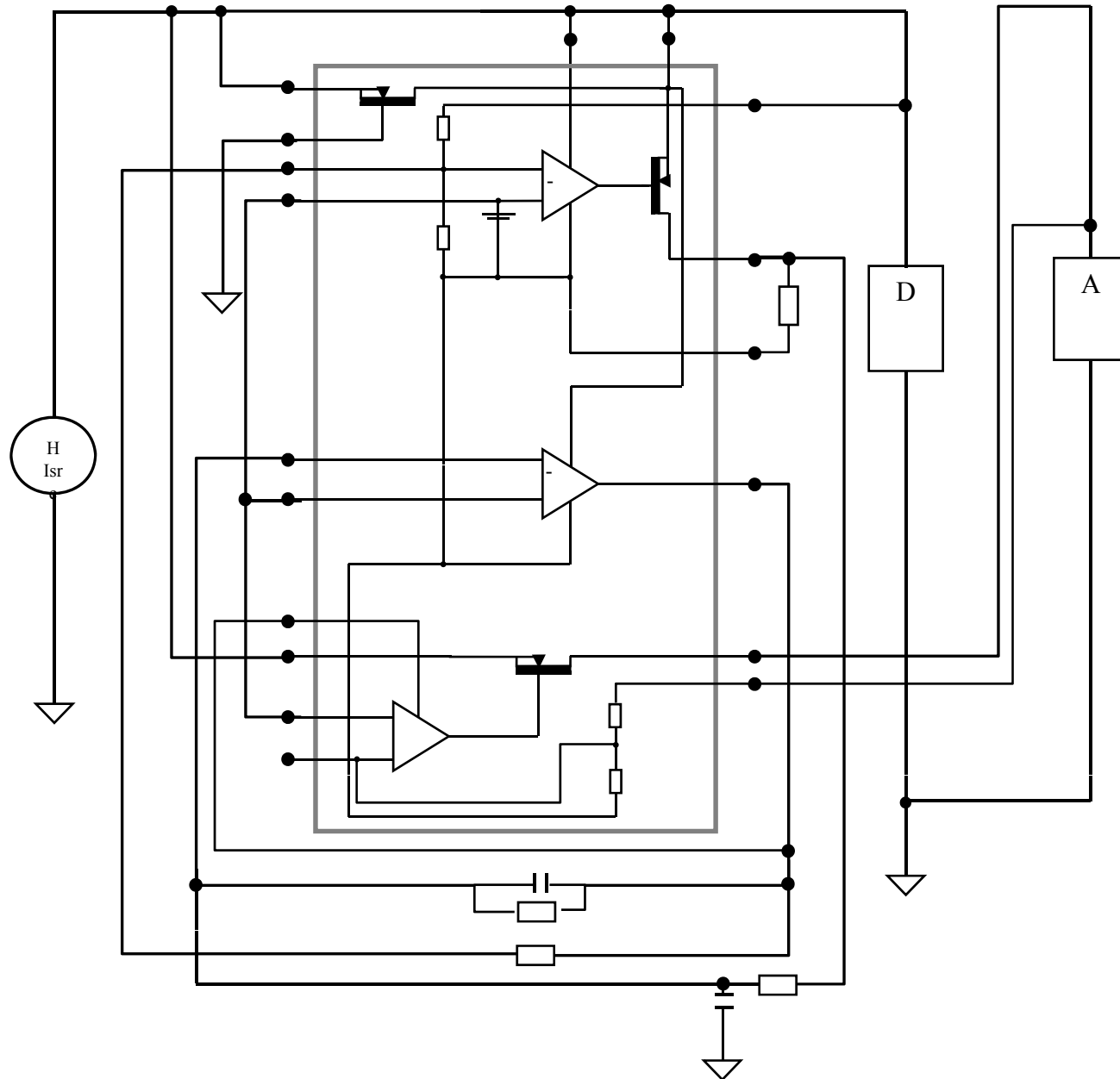

Features of IP and alternative schemes

	IP	SP	DC-DC	Comment
Power efficiency	10-20%	60-80%	60-80%	Varies with I, n (SP); gain (DC-DC)
Local regulator inefficiency	0%	~10%	Don't know yet	This is without linear regulator for analog
number of power cables	4 per hybrid	Reduction by factor $2n$	Reduction by factor $2n$	n = number of hybrids
Voltage control over ind. hybrids	Yes On/Off; fine-adjustment	Stand-by mode: 2.5V/1.5V -> 0.7 V; Limited fine-adjustment	Yes On/Off; limited fine-adjustment	New schemes have regulators; no fine adjustment needed
Hybrid current info	Yes	Yes (sensing current through power device)	Yes	Some power penalty for DC-DC
Hybrid voltage info	Yes (need sense wires)	Yes	Yes	Not strictly needed, since regulators
Floating hybrid power supplies	Yes	No, voltage chain	No	
Protection features	Separate set of cables for each hybrid	Local over-current protection; redundant regulators	Don't know yet	Protect against open (SP) and short (DC-DC)

Let's preserve the good features of IP ⇔ **have voltage control, current monitoring, and protection features** ⇔ our specs do just that

Outlook

SP offers huge gains in power efficiency, cable and material budget
It unusual to gain such significant factors in a technology as mature as
silicon detectors

Various SP systems have been running since several years now;
understanding of system properties is well advanced


Noise performance is excellent and we understand why; studies on
staves are promising and most generic system tests will be completed
this year

Next crucial step is to design a custom general-purpose ASIC
(SMARP1); this should be a common ATLAS-CMS chip; it would be
of interest for pixels and strips; it's prudent to start this effort soon

Appendix

Overcurrent protection measurements

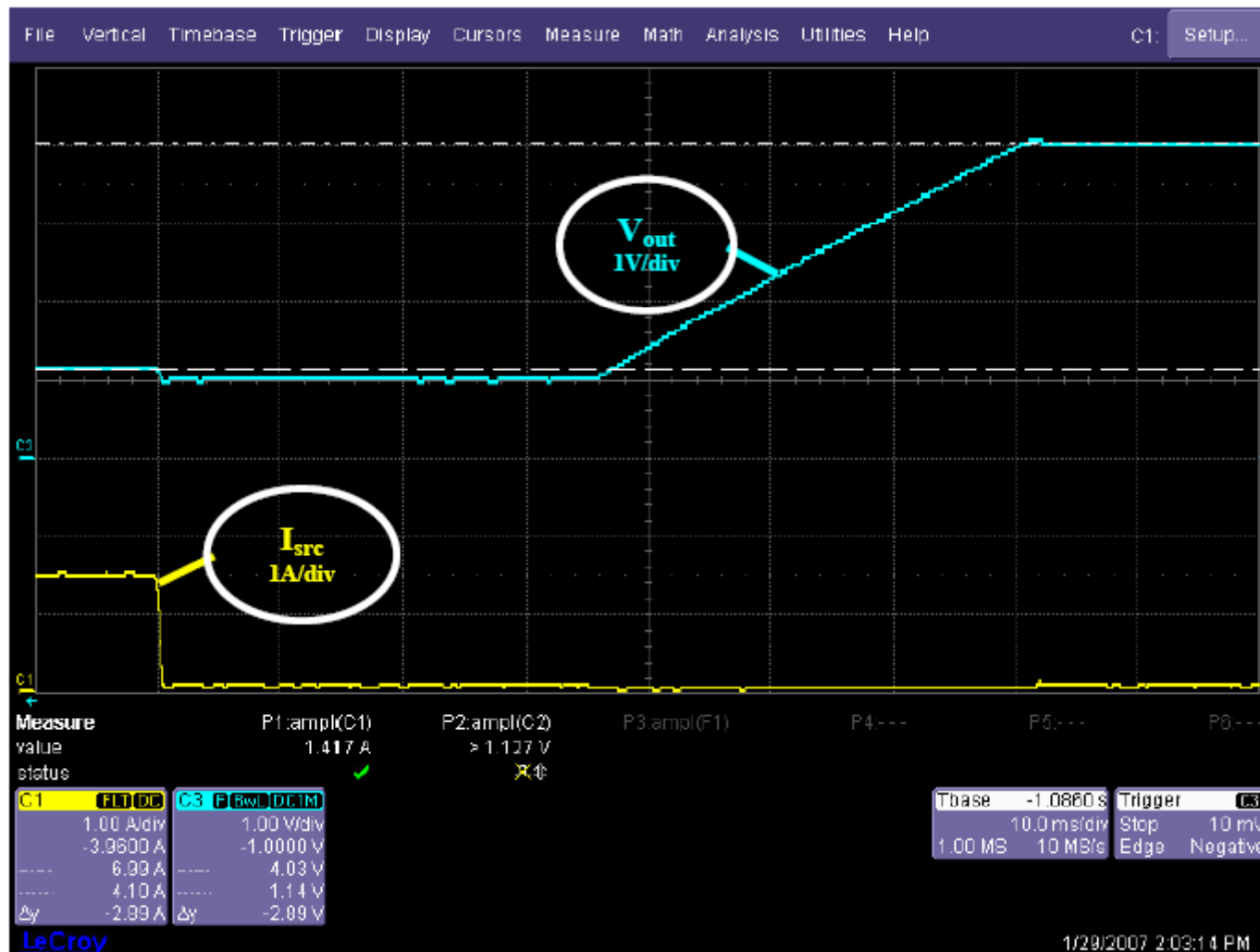Basic test of the idea using discrete component circuits



Recovery to nominal if current back to normal

voltage increase from 1V to 4V within 70 ms

due to current decrease from 1.5 A to 40 mA