



ALDO2

A multi-function rad-hard linear regulator for SiPM-based detectors

Paolo Carniti^(a,b), Claudio Gotti^(a), Gianluigi Pessina^(a)

(a) INFN of Milano Bicocca
(b) University of Milano Bicocca



VCI2022 – The 16th Vienna Conference on Instrumentation

21/02/2022

paolo.carniti@mib.infn.it



Content

- Introduction
 - [SiPM-based detectors for HEP](#)
 - [Challenges of SiPMs at HL-LHC](#)
 - [Power supplies for LHC detectors](#)
- ALDO2
 - [General scheme](#)
 - [HV regulator](#)
 - [LV regulator](#)
 - [Technology and prototyping](#)
 - [Radiation hardening techniques](#)
- Measurements
 - [HV regulator](#)
 - [LV regulator](#)
 - [Radiation hardness](#)
- Conclusions
 - [Chip production](#)

Introduction: SiPM-based detectors for HEP


- SiPMs/MPPCs are gaining more and more popularity in the HEP community, as they offer many **substantial advantages** over other classes of photodetectors like vacuum devices
 - Compactness, robustness, small pixel size, low voltage bias, excellent linearity and dynamic range, high photon detection efficiency, immunity to magnetic fields
- On the other side they also have a few, but very crucial, **drawbacks**
 - High dark current, poor radiation hardness, optical cross-talk, after-pulses, precise bias
- At HL-LHC, several detectors are planning to adopt them as the baseline photodetectors
 - In CMS: **Barrel Timing Layer** (BTL, see below) and **High-Granularity Calorimeter** (HGCal)




Introduction: Challenges of SiPMs at HL-LHC

- The main challenge of using SiPMs at HL-LHC comes from their **poor radiation hardness**
 - Dark count increases up to tens of GHz at $10^{14} n_{eq}/cm^2$
 - Power consumption up to about 50 mW/SiPM
 - Breakdown voltage shifts with radiation damage
 - On-detector I-V curves are required to set optimal working point (gain and dark current have a strong dependence on SiPM overvoltage)
- Possible mitigations only marginally improve the situation
 - Cooling (typically limited to liquid CO₂ in LHC detectors)
 - Annealing (also limited in tight detectors)
- These challenges also affects the **power supplies** of SiPMs
 - O(1000) SiPMs are connected in parallel → ~50 W load
 - Bias voltage **stability and noise** are crucial for the precise setting of the working point (but usually bias supplies are very far from the detectors)
 - Bias voltage trimming in front-end chips adds complexity due to AC coupling and added parasitics on the read-out node

 
Dark counts at -30°C with irradiated SiPMs



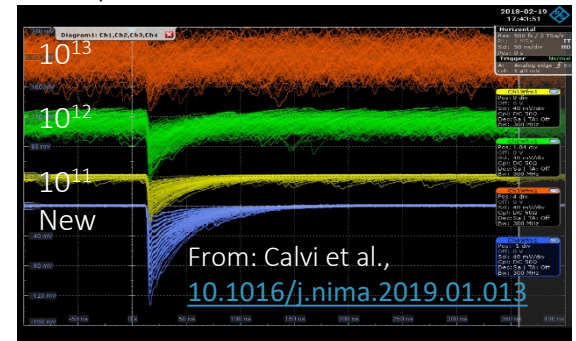Laser pulses at -30°C with irradiated SiPMs




Dark count rate vs Luminosity in BTL

 

Introduction: Power supplies for LHC detectors

- Power distribution at LHC is usually based on a [multi-stage approach](#)
 - AC-DC(HV) stage outside experimental area (>100 m from detector)
 - First DC(HV)-DC(LV) stage in experimental area (30 m from detector)
 - Point-of-load (PoL) rad-hard DC-DC stage on the front-end boards
- But...
 - ...modern front-end chips may require multiple supplies
 - ...with tighter noise and stability specifications
 - ...and chips from different technologies may coexist on the front-end
- Furthermore, as highlighted before, photodetectors like SiPMs also require precise PoL power supply for their bias voltage
- There is the need to design a [further stage](#)
 - More modularity → One ASIC per regulator, less current per channel
 - More thermal stability and less noise → Linear regulator
 - Suitable for several uses → Adjustable voltage
 - Able to provide SiPM bias voltage → “HV” technology
 - With additional features → Output current measurement, shutdown, overtemperature and overcurrent protections, etc.
 - Able to work inside detectors → Rad-hard
- We designed an ASIC for all these functions, [ALDO2](#)

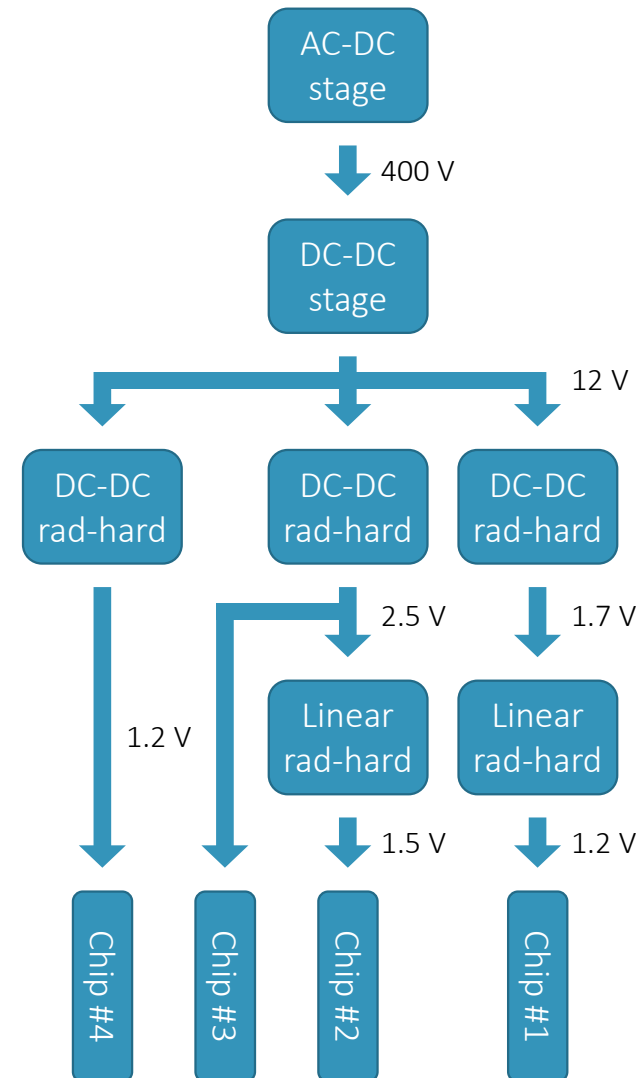


ALDO2: General scheme

ALDO2 features 4 independent and fully adjustable linear regulators


The regulator scheme is the **classic low dropout scheme**, with an error amplifier and PMOS pass element

- LV regulators
 - Voltage reference is provided with an internal bandgap
 - Output voltage can be adjusted with an external divider
- HV regulators
 - Both inputs of the error amplifier are available externally
 - The fixed range can be adjusted with an external divider
 - Output value can be changed during operation by applying an analog voltage from a DAC on the other input of the error amplifier
 - In BTL the DAC is embedded in the front-end chip, while HGICAL will use the DAC in the CERN slow control chip (GBT-SCA)

Basic scheme of the LV regulator


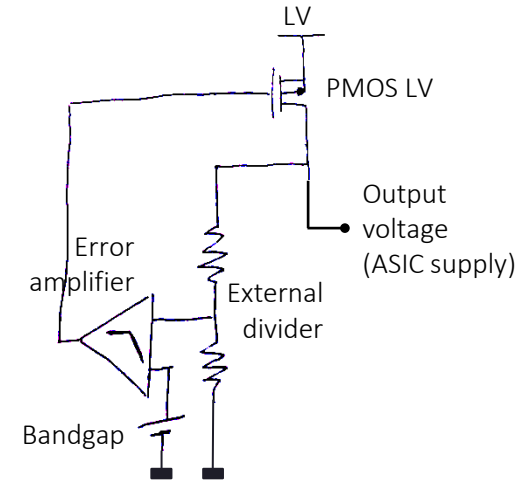


Basic scheme of the HV regulator

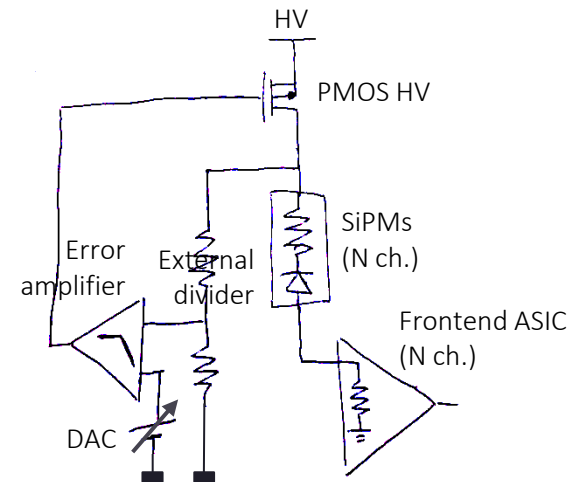


ALDO2: HV regulator

- Bias voltage generation for groups of 16 SiPMs
→ 2 channels per chip
- Input voltage: 25 V – 70 V
- The DAC used in BTL has 8 bits with two ranges:
 - Range 1: 100% – 74% of output voltage with 0.1% LSB (8 bit)
 - E.g., 44 V – 32.7 V, with 44 mV LSB (SiPM specs still floating)
 - Range 2: 95% – 82% of output voltage with 0.05% LSB (8 bit)
 - E.g., 41.8 V – 36.3 V, with 22 mV LSB (SiPM specs still floating)
- Maximum output current: 45 mA (current limit 55 mA)
- Minimum dropout:
 - <1 V on not irradiated chips (>97% efficiency @ 38 V)
 - 3 V with EOL irradiation (92% efficiency @ 38 V)
- External low ESR capacitor for stability
- Channels can be individually disabled
 - If a SiPM fails with a short, only its group of 16 SiPMs is affected
- Protected against overcurrent and overtemperature
- Allows output current measurement by mirroring output current (2 ranges available, factor x20 between the two)
 - Voltage conversion using an external resistor, range can be tuned

 
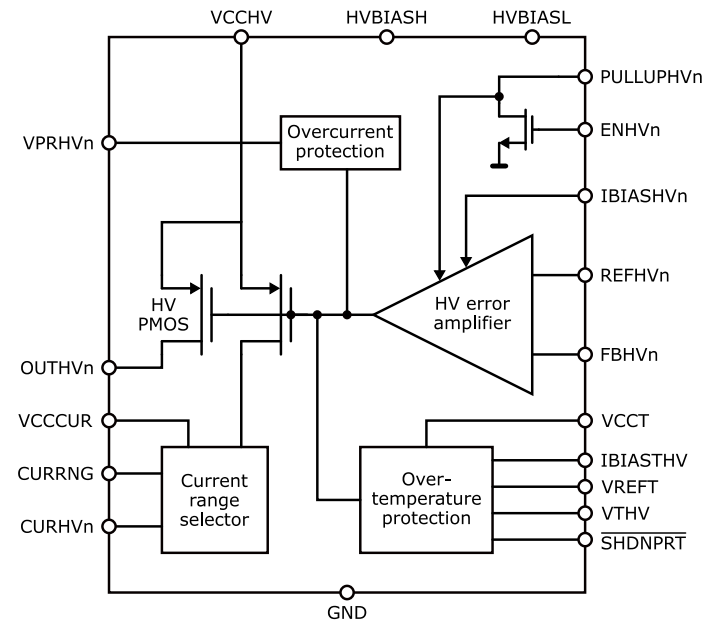


ALDO2: Technology and prototyping

 - The chip is designed in onsemi I3T80 HV CMOS technology (350 nm), which proved to be sufficiently radiation tolerant in other CERN designs (FEAST DC-DC) and publications (see Faccio et al., 10.1109/TNS.2010.2049584)
- ALDO2 was produced in 3 prototypes (ALDO2v0 in 2019, ALDO2v1 in 2020, and ALDO2v2 for production run in 2022)
- The package is QFN64 (9x9 mm²)



Die area 2.47 x 1.95 mm²

  

ALDO2: Radiation hardening techniques

BTL maximum expected radiation levels at 3000 fb⁻¹

TID	Neutron fluence (1 MeV eq.)	Charged hadron fluence
3.2 Mrad	1.9e14 cm ⁻²	1.5e13 cm ⁻²


- Target radiation levels in hottest areas of BTL is within reach of I3T80 technology (HGICAL has lower radiation levels)
- Several radiation hardening techniques adopted
 - Enclosed layout for all LV NMOS transistors
 - The HV NDMOS implements a special “enclosed/guarded” layout to reduce leakage above 100 krad (extended P+ diffusion around the source contact to avoid parasitic gate formation in the lateral oxide)
 - On resistance of HV MOSFETs increases with displacement damage
 - Not super critical for our application, effect minimized by using larger transistors
 - Wide use of guard rings
 - Increased spacing between devices and cells
 - High density of substrate contacts
 - Strict adoption of anti-latchup rules provided by the technology

Measurements: HV regulator


Selected measurements...

Line regulation

Line regulation (40 V)

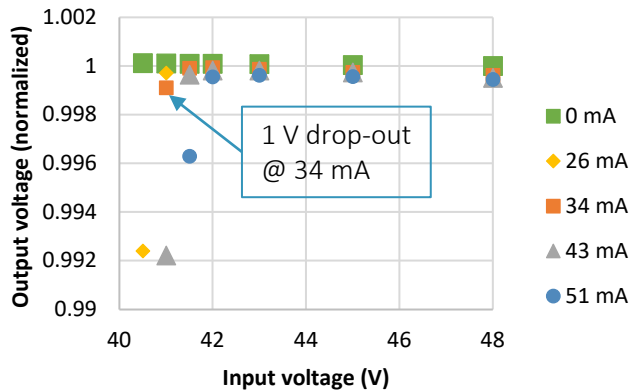


Line reg. (40 V, 43 mA)

 


Noise

Noise HV (40 V in, 38.5 V out)

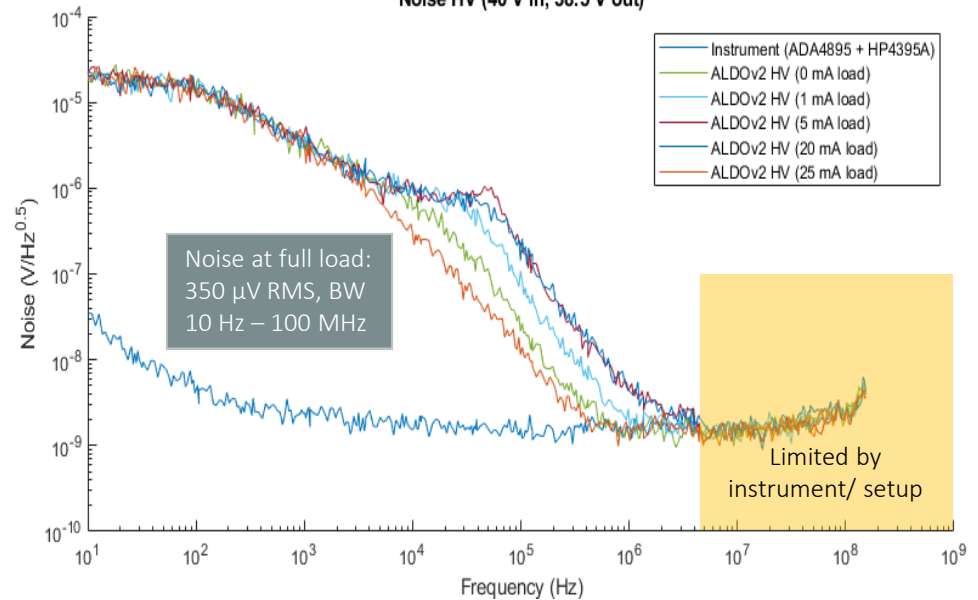


20 mA current step

 


Measurements: LV regulator

Selected measurements...


Bandgap spread and thermal stability

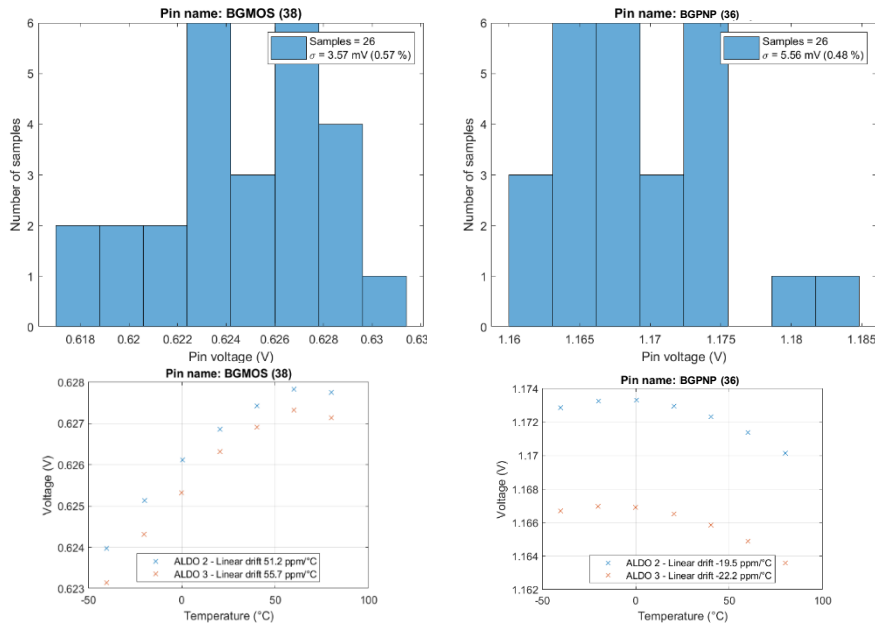


Noise

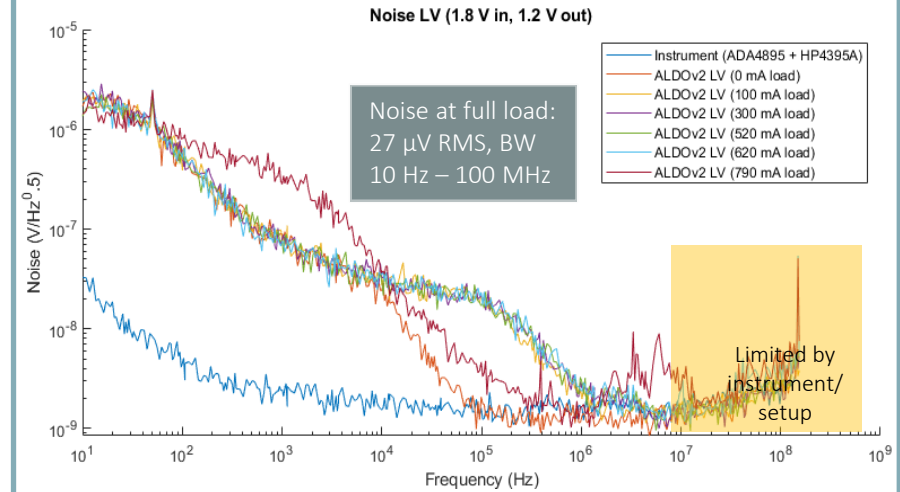

Power supply rejection ratio

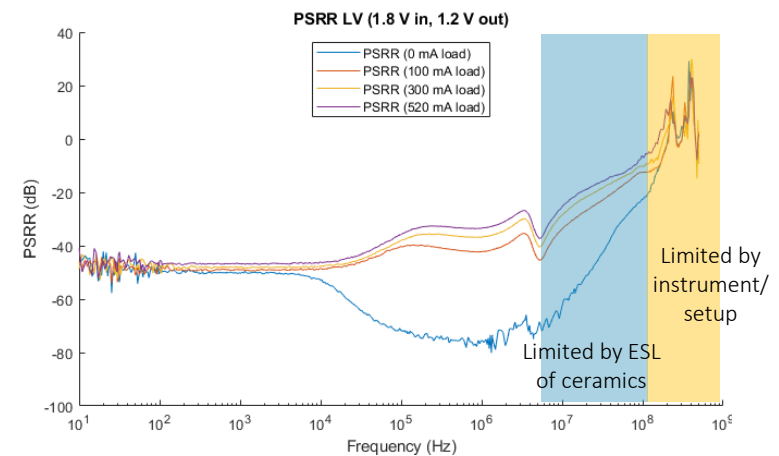


500 mA current step

 

Measurements: Radiation hardness

- The chip was successfully tested with TID (X-rays), displacement damage (neutrons in nuclear reactor) and single-event effects (heavy ions), beyond the expected radiation levels. A few selected results...



Bandgap drift with radiation

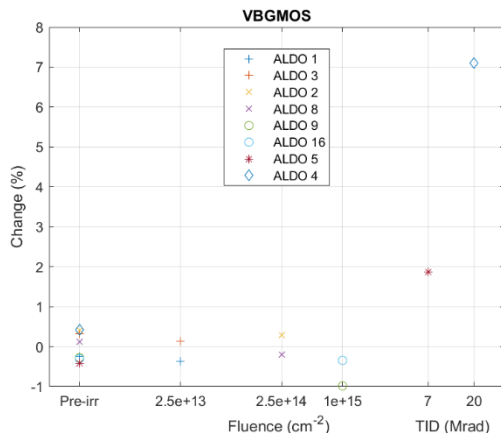

MOS	Value	Var	T Drift
Pre-irrad	625 mV	-	70 ppm/°C
2.5e14 cm ⁻²	625 mV	0%	-
1e15 cm ⁻²	621 mV	<1%	120 ppm/°C
7 Mrad	637 mV	2%	70 ppm/°C
20 Mrad	669 mV	7%	100 ppm/°C


Line regulation degradation

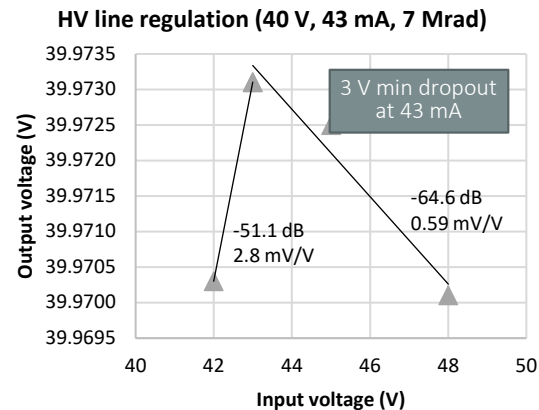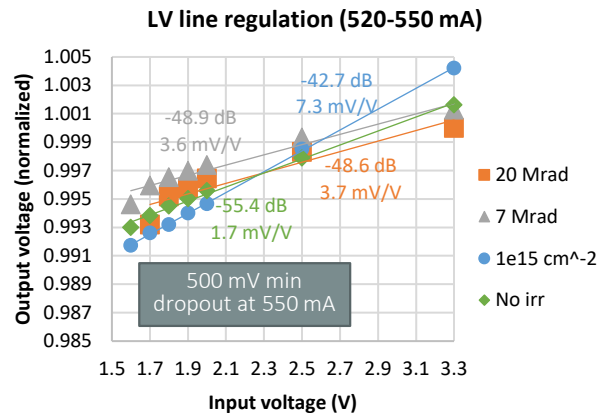Minimum dropout has to be increased after radiation damage, both on LV and HV regulator




Single event transients (SET)

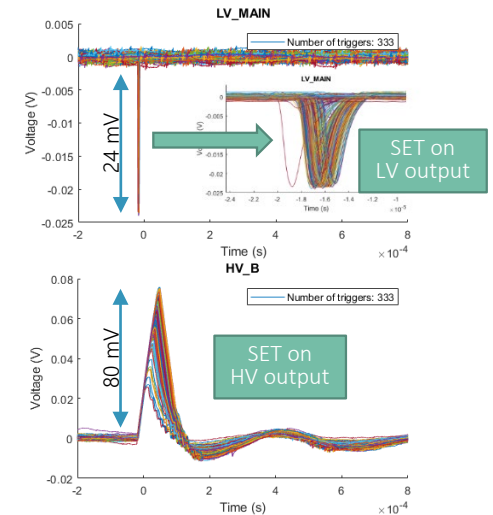Single event transients observed at high LET, cause was identified, rate in final detector is negligible (mHz) and amplitude low (few %)




 SET (single event transients) cross section



Conclusions: Chip production

- The chip has **completed** its development phase
 - Some measurements are still ongoing, like the stress tests to determine reliable operating parameters over long periods of time
 - Few minor changes proposed during PRR (production readiness review) will be implemented directly in production run (**fail-safe**)
- Production has started, chips expected in **Q3 2022**
 - Chip production **had to be anticipated** wrt HL-LHC schedule because onsemi I3T80 fab in Oudenaarde (Belgium) will be sold and has stopped MPW services in 2022
 - **45k chips** produced, more than double the needs of BTL and HGCAL (19.2k), just to be covered in case of issues in production phases
 - An alternative I3T80 fab in Gresham (USA) is available, but was not qualified for radiation hardness
 - Can be studied if ALDO2 project will continue for other detectors
 - ALDO2v1 demonstrated **very high yield** (103 out of 103) and **small spread** between wafers (< 1%) → No individual chip testing is planned

 



Thanks for reading till here