

Design of a Front-End ASIC for the New Small Wheel

Gianluigi De Geronimo


Stony Brook University, University of Michigan, DG Circuits
degeronimo@ieee.org

RD51 Collaboration Meeting and Topical Workshop, June 14-18 2021

Outline


- Front-End Design in CMOS
 - input MOSFET optimization
 - reset and charge amplification
- Overview of VMM3a
- Prospects in FE ASIC Design

Front-End Microelectronics

 


- front-end optimization for resolution
- small physical size, low parasitics
- low power consumption
- high functionality and programmability
- high channel density
- low production cost per channel
- extreme environment

 becoming the only option for modern detectors



Charge Amplifier

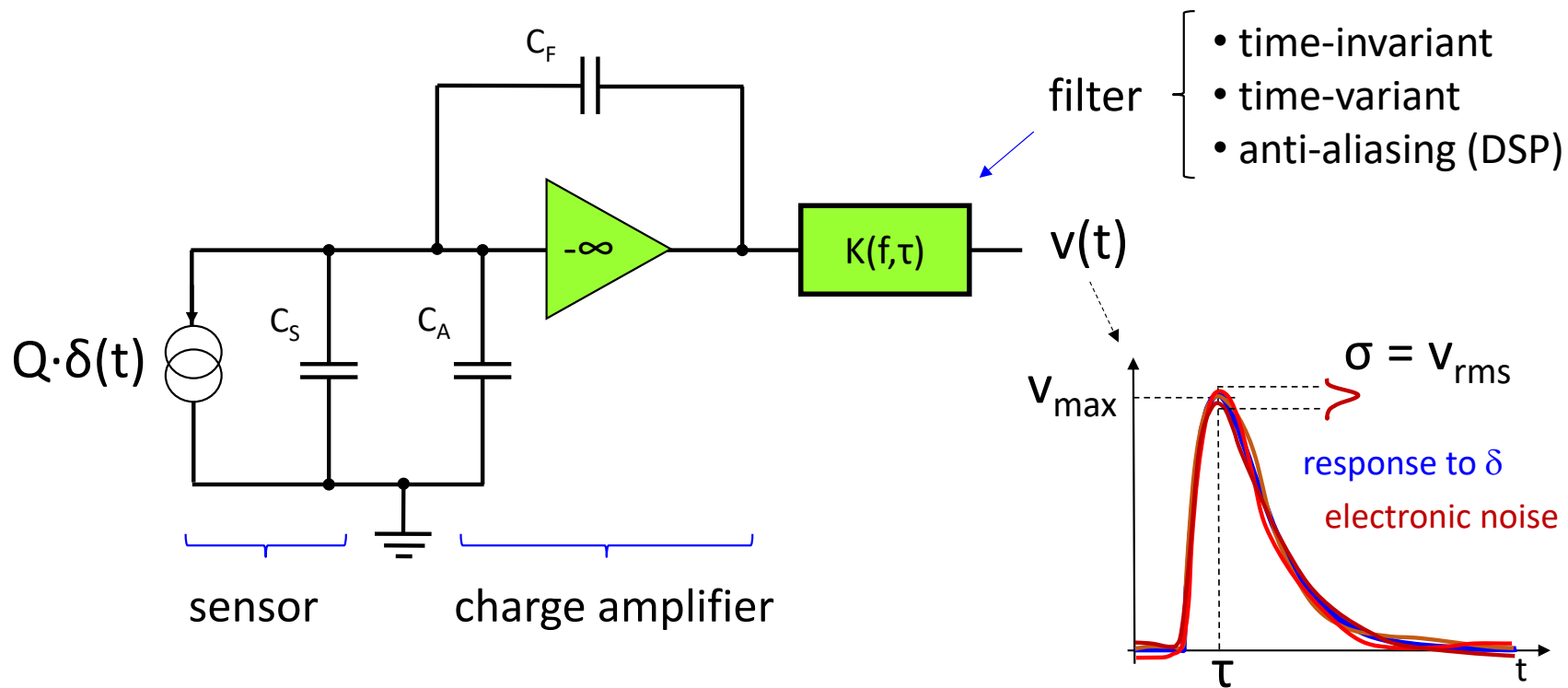


$$\text{gain} = \frac{V_{max}}{Q} \quad [\text{mV/fC}]$$

$$\text{ENC} = \frac{V_{rms}}{\text{gain}} \quad [\text{fC}] \text{ or } [\text{electrons}]$$

Equivalent Noise Charge

Noise Sources

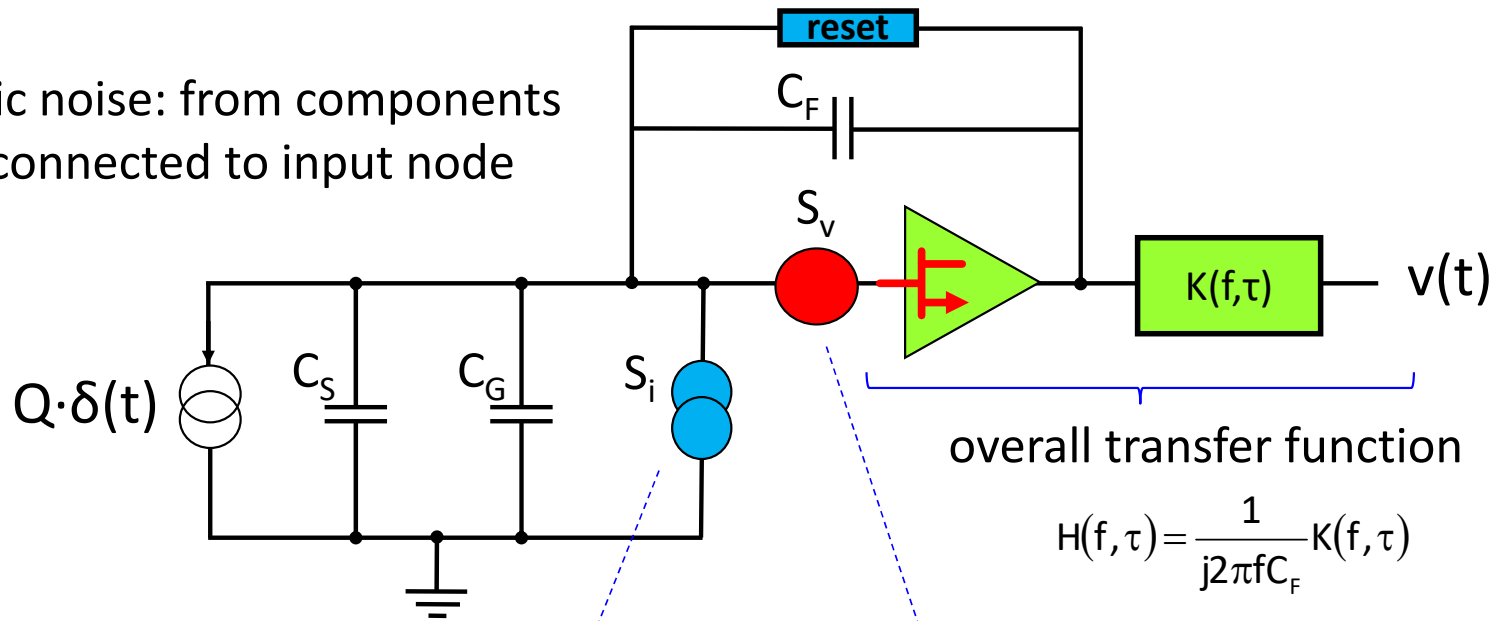
Electronic noise: from components directly connected to input node



$$ENC^2 \cong \frac{\int_0^{\infty} S_i |H(f, \tau)|^2 df + \int_0^{\infty} S_V \omega^2 (C_S + C_G)^2 |H(f)|^2 df}{h(t)_{\max}^2}$$

need minimum 2 poles in $H(f, \tau)$

Input Transistor

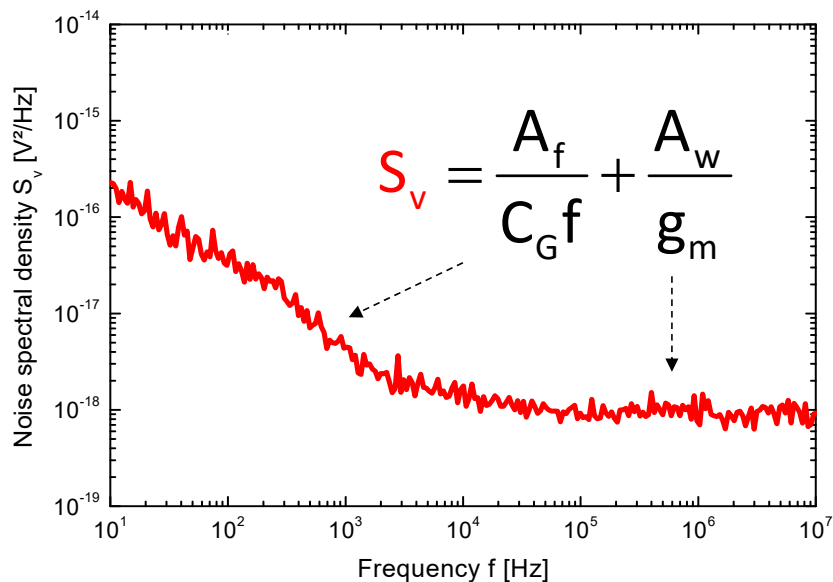

$$S_v = \frac{A_f}{C_G f} + \frac{A_w}{g_m}$$

C_G = gate capacitance
 g_m = transconductance
 }
 proportional to transistor size

transistor sized for
 $C_G = C_S$ (capacitive matching)

From S_v :

$$ENC_v^2 = a_f A_f \frac{(C_S + C_G)^2}{C_G} + \frac{a_w}{\tau} \underbrace{\frac{A_w}{g_m / C_G}}_{f_{Tmax}} \frac{(C_S + C_G)^2}{C_G}$$

For $C_S = 1\text{pF}$
1mm, 100mA !

$C_G \rightarrow \sim 1\text{fF}/\mu\text{m}$
 $I_D \rightarrow \sim 100\mu\text{A}/\mu\text{m}$

f_{Tmax} (maximum independent frequency)
 (depends on V_{GS})

Low-Power Input Transistor

white noise contribution $ENC_{vw}^2 \approx \frac{a_w}{\tau} \frac{A_w}{g_m(I_D)/C_G} \frac{(C_S + C_G)^2}{C_G}$ fix power \rightarrow fix drain current I_D


$V_{GS} \gg V_{th}$ (strong inversion)

$$g_m(I_D) \approx \sqrt{\frac{2\mu c_{ox}}{n} \frac{W}{L} I_D} \propto \sqrt{\frac{C_G I_D}{L^2}}$$

\downarrow

$$ENC_{vw}^2 \propto \frac{L}{\sqrt{I_D}} \frac{(C_S + C_G)^2}{\sqrt{C_G}}$$

- minimum L
- $C_G = C_S/3$

 

$V_{GS} \ll V_{th}$ (weak inversion)

$$g_m(I_D) \approx \frac{I_D}{nV_T} \propto I_D$$


\downarrow

$$ENC_{vw}^2 \propto \frac{(C_S + C_G)^2}{I_D}$$

- independent of L
- $C_G = 0$ pushes back towards strong inversion

$\rightarrow V_{GS} \approx V_{th}$ (moderate inversion), $C_G \ll C_S$

Low-Frequency Noise

 


low-freq. noise contribution

$$ENC_{vf}^2 = a_f(\alpha) \frac{A_f(L)}{\tau^{1-\alpha}} \frac{(C_S + C_G)^2}{C_G}$$

depends on τ !

VMM3a → p-MOS, $L=180\text{nm}$, $W=10\mu\text{m}$, $I_D=2\text{mA}$, $C_G=10\text{pF}$


Input Loop with PMOS

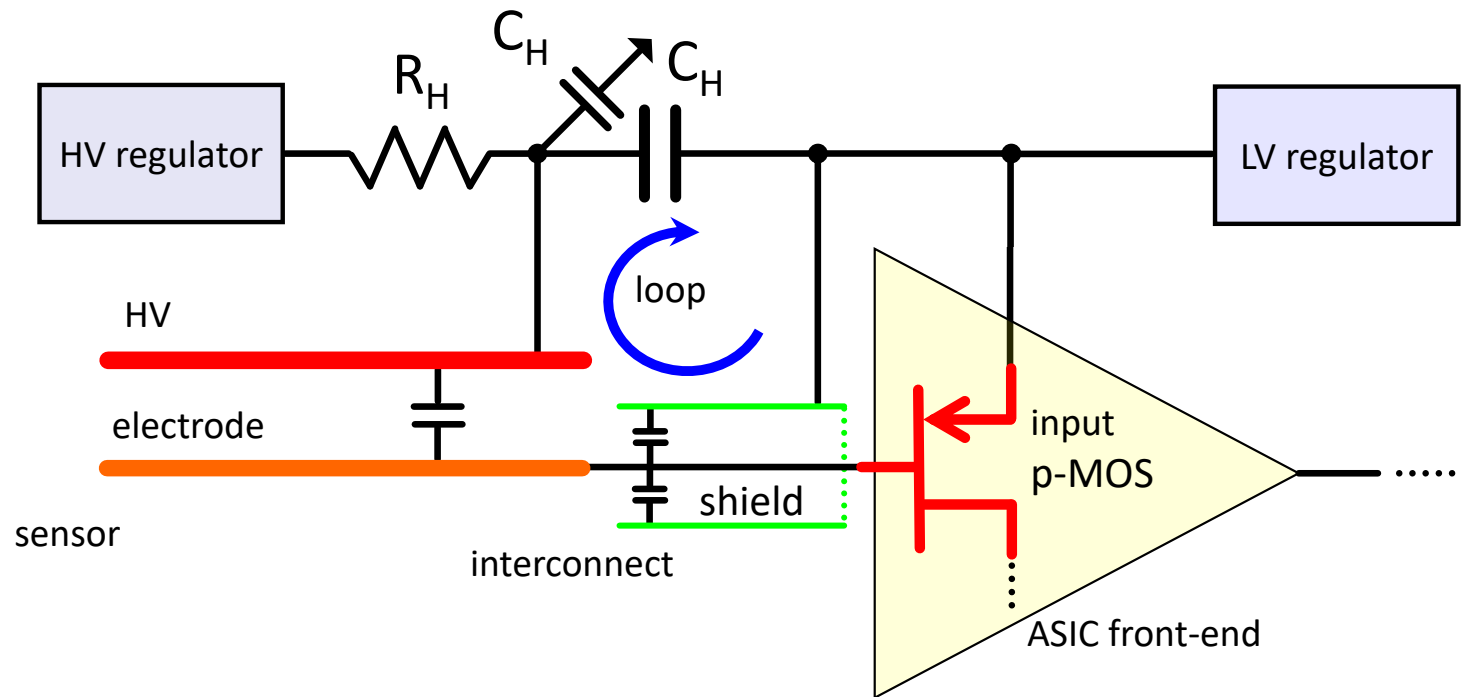

- decouple sensor supply to p-MOS supply
- decouple input shield to p-MOS supply
- minimize length and area of input loop

Charge Amplifier "Reset"

- dc stabilization
- discharge of C_F

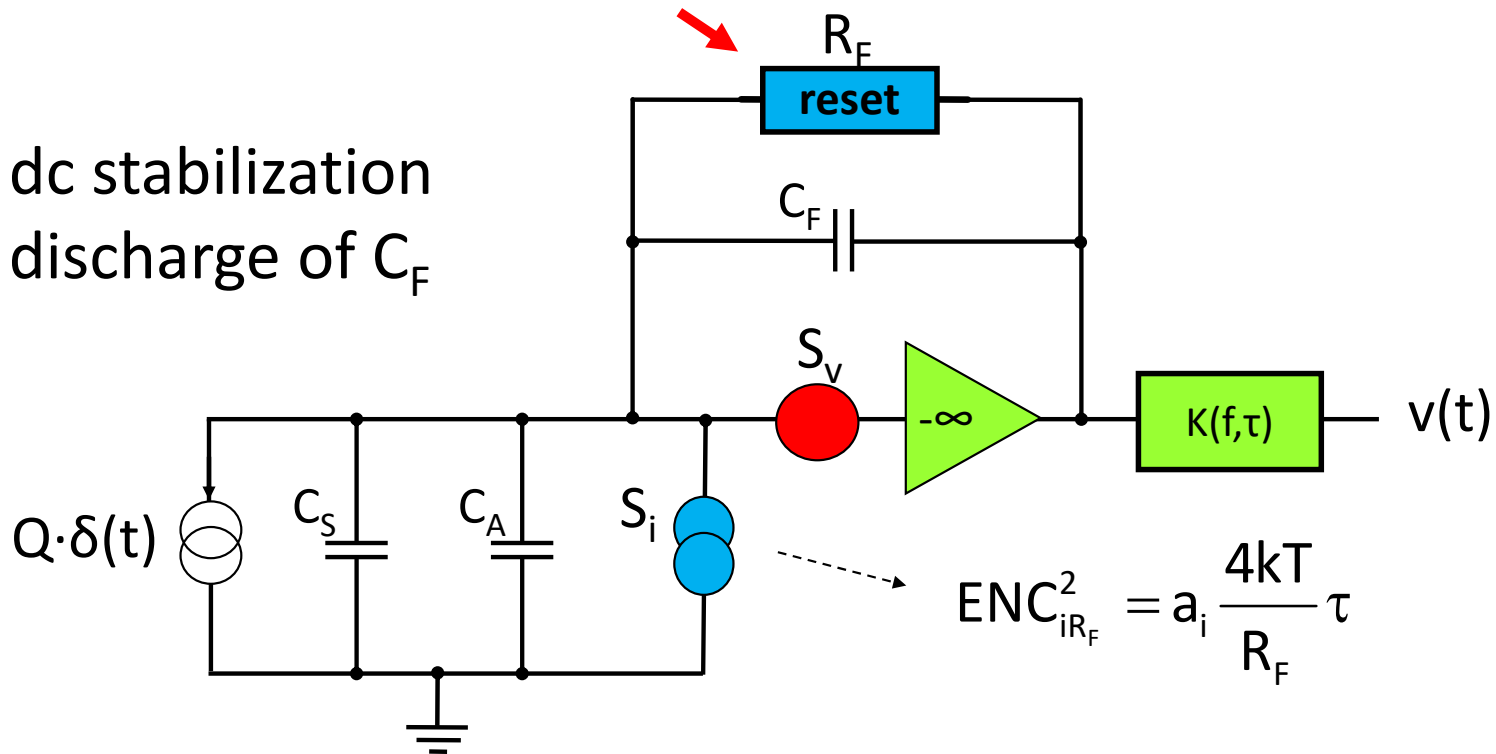

$$ENC_{iR_F}^2 = a_i \frac{4kT}{R_F} \tau$$

$$\frac{4kT}{R_F} \ll 2qI_s$$

sensor shot noise
from leakage current I_s


$$R_F I_s \gg \frac{4kT}{2q} (\sim 50\text{mV}) \quad \text{"50mV rule"}$$

examples $\left\{ \begin{array}{l} \text{CZT: } I_s = 1\text{nA} \rightarrow R_F \gg 50 \text{ M}\Omega ! \\ \text{Si: } I_s = 1\text{pA} \rightarrow R_F \gg 50 \text{ G}\Omega ! \end{array} \right.$

Reset in CMOS



M_F noise: $S_{iM_F} \approx 4kTg_m \ll 2qI_S$

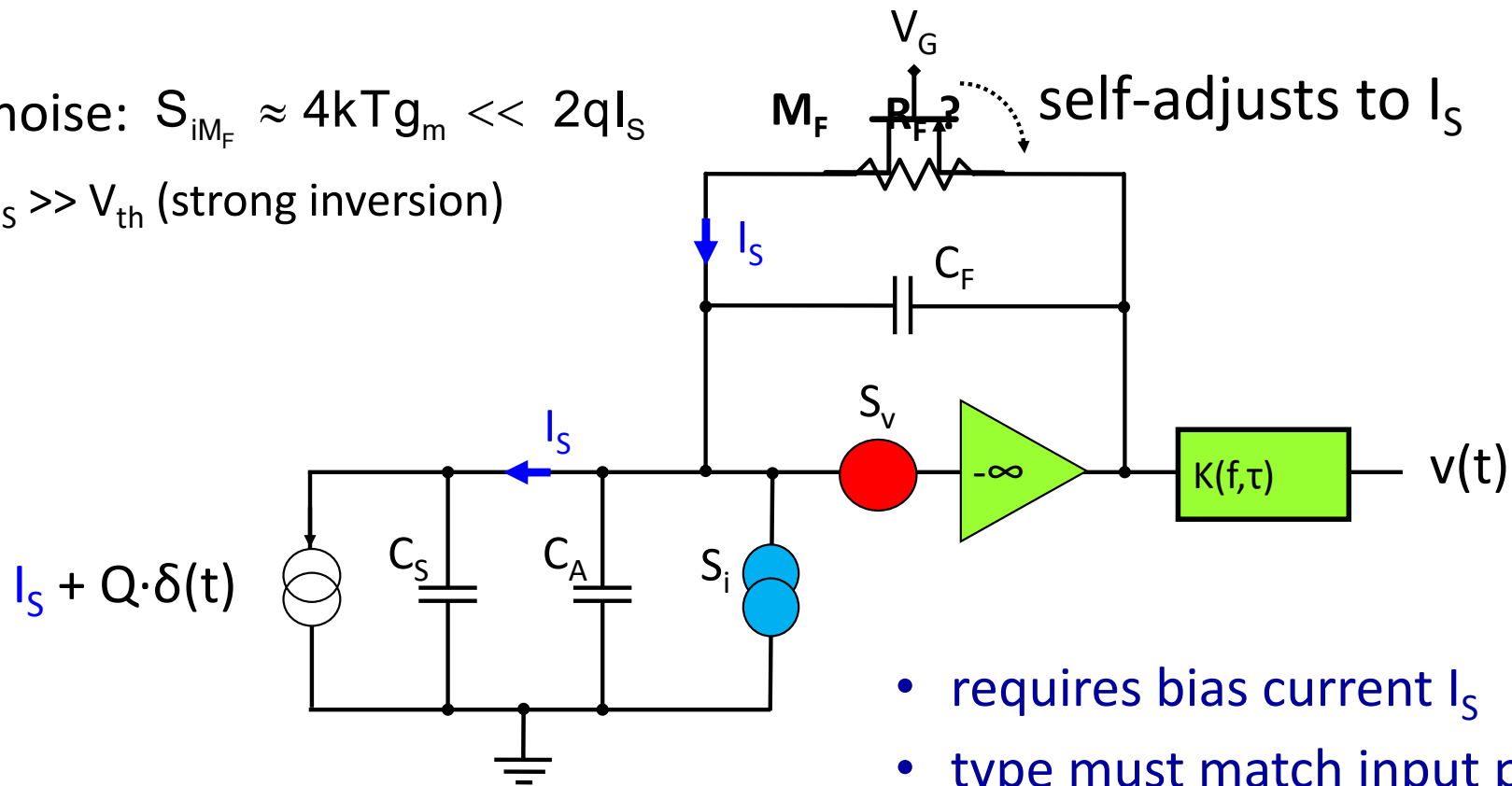if $V_{GS} \gg V_{th}$ (strong inversion)



- requires bias current I_S
- type must match input polarity
- adds noise increase at discharge


Reset Non-Linearity

  

τ_d depends on amplitude
and affects linearity


How to realize a linear configuration?

Reset Linearization

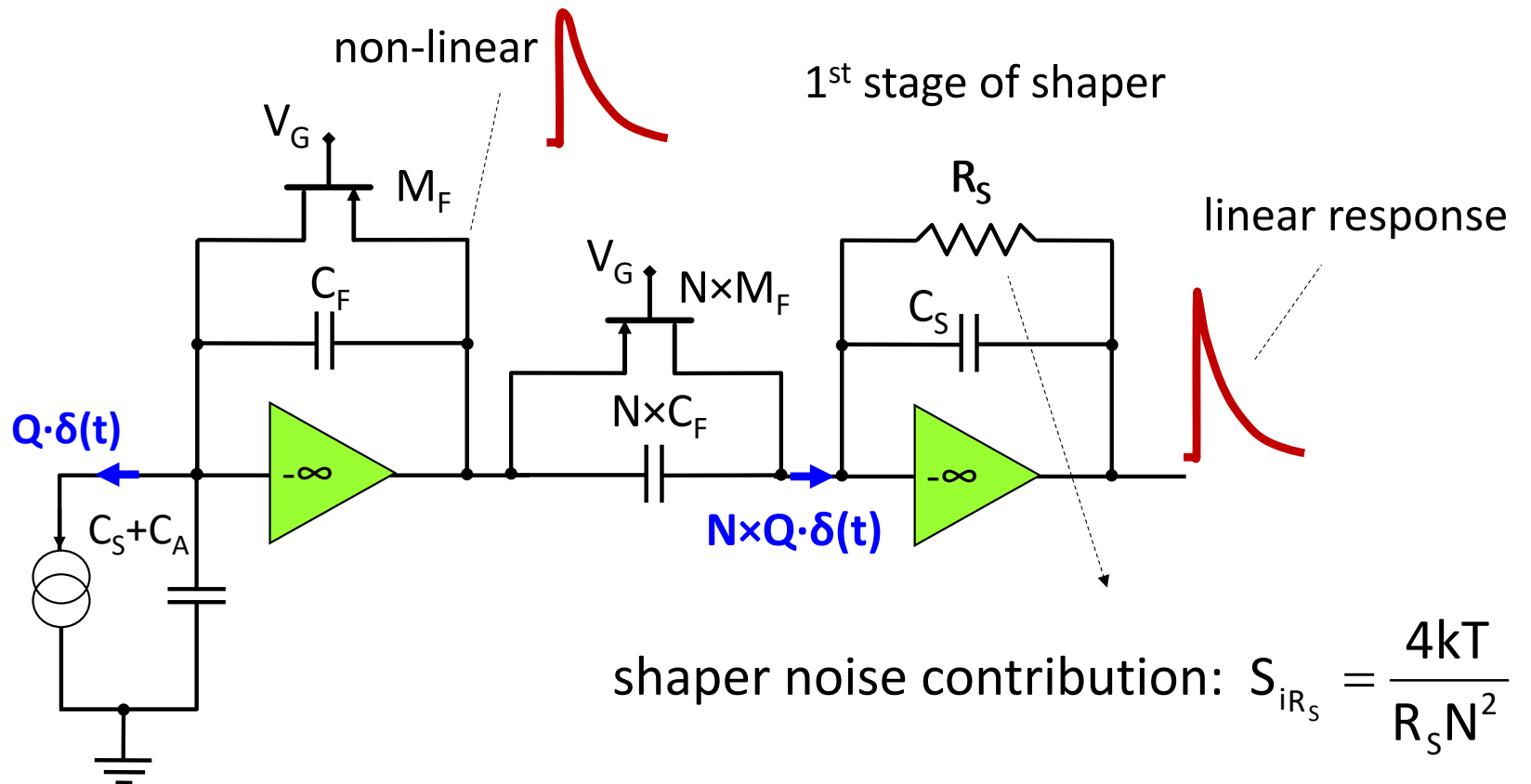

Effective linear "charge amplification" by N

Mirror Reset

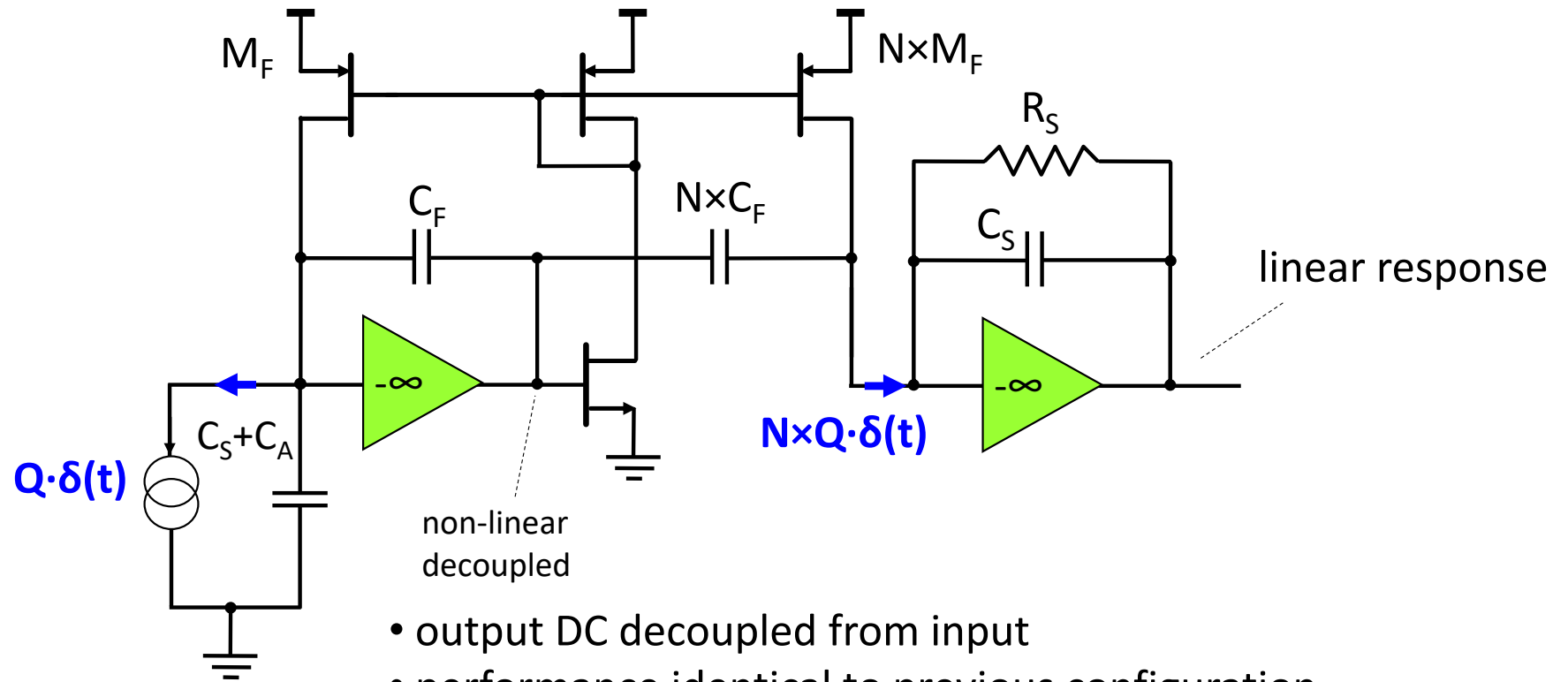


- output DC decoupled from input
- performance identical to previous configuration


CMOS reset

- Requires input bias current **VMM3a** → adjustable
- Adjust type according to signal polarity **VMM3a** → adjustable
- Cascade stages for high charge amplification **VMM3a** → 3 prog. stages


VMM3a Architecture

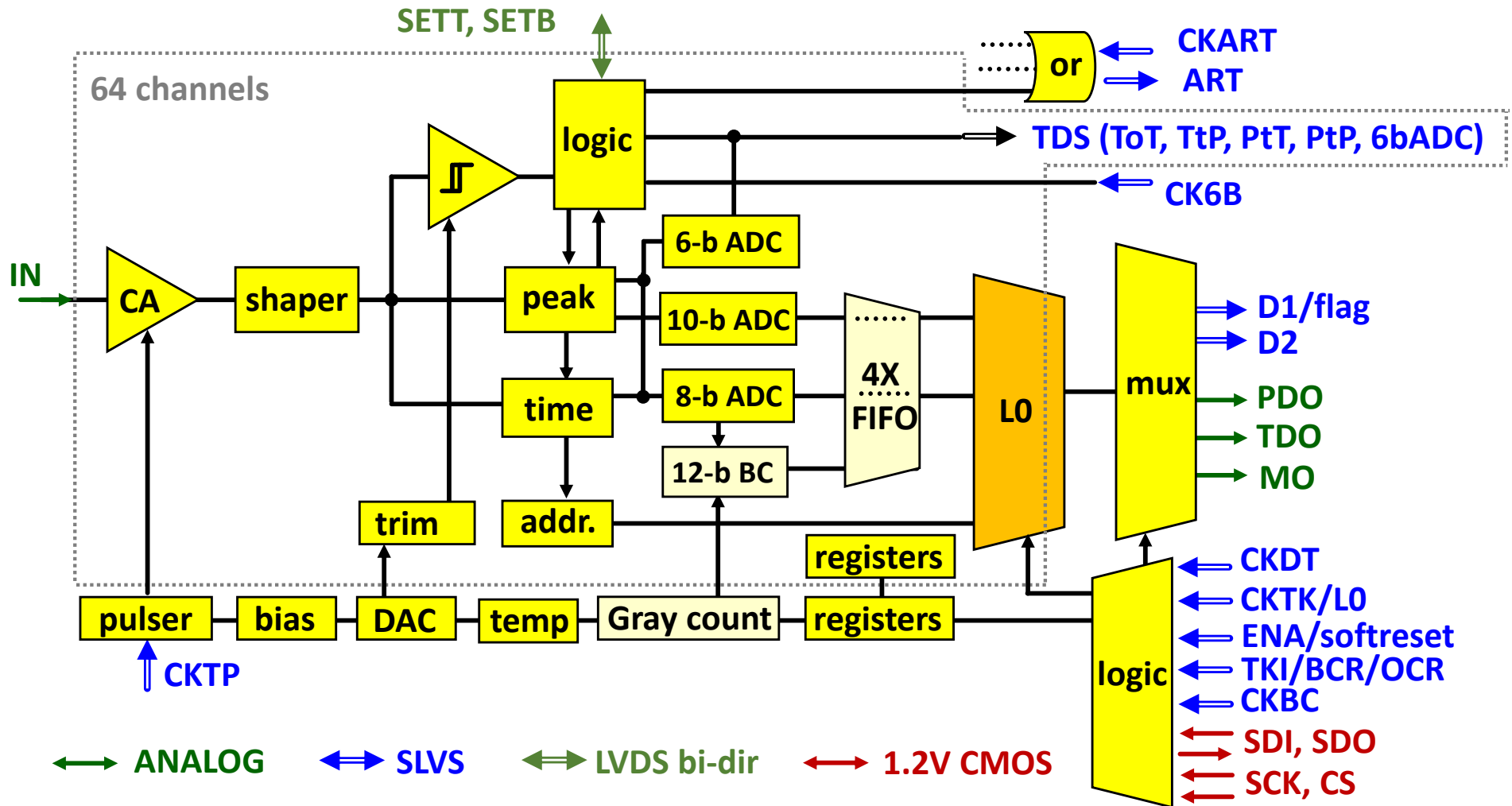


VMM3a Development Stages

 

 - mixed-signal
- **2-phase** readout
- peak and timing
- **neighboring**
- sub-hysteresis
- few timing outputs



 - mixed signal
- **continuous** fully-digital readout
- current-output peak detector
- increased range of gains
- three **ADCs** per channel
- FIFOs, **serialized** data with DDR
- serialized **ART** with DDR
- additional timing modes
- **64 direct outputs**
- additional functions and fixes



- mixed signal + pure digital core
- continuous simultaneous readout
- **SEU-tolerant** logic
- deeply revised front-end for **TGC**
(2nF, 50pC, fast recovery, ...)
- **LO** handling digital core
- **SLVS** and new configuration interface
- new **reset** control and fast reset
- **timing** at threshold
- timing ramp optimization
- pulser range extension
- ART synchronization
- 32-channel skip
- additional functions and fixes

Designers: G. De Geronimo & Sorin Martoiu (L0)

Residual issues: - baseline yield (modeling + manufacturing)
- ADC accumulation (requires redundancy)

VMM3a Physical Layout




64 channels, 6M transistors, 426 bonding pads, 13.3 x 8.4 mm²

Progress in NSW Front-End Electronics



2005 - ASM

 


2015 - VMM

- 60x sensing elements, 10x element density, 3x power dissipation
- Front-end ASIC (**VMM**)
 - data-driven, trigger primitives, peak, timing, ADCs, direct outputs
 - multiple detector types, broad range of signal charge and input capacitance
 - high programmability, dedicated L0 digital core

Front-end ASICs are becoming systems-on-chip

Prospects in Front-End ASICs

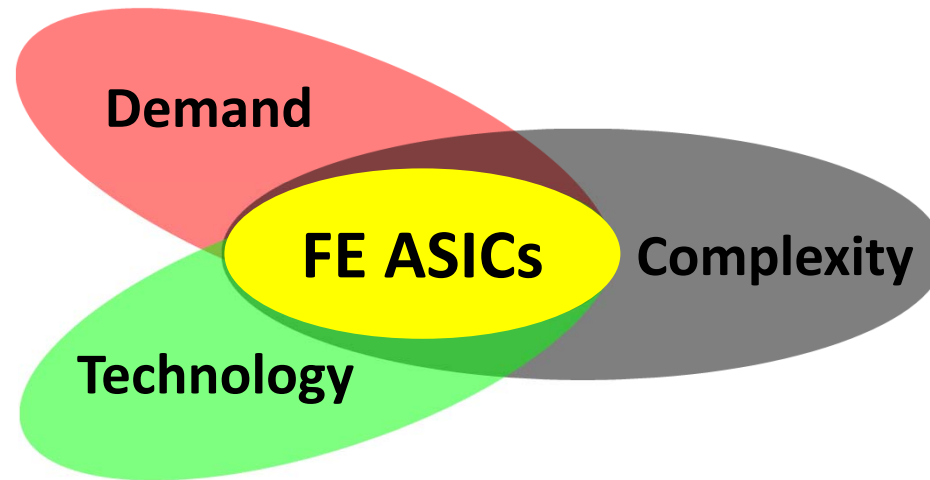

- Rapidly increasing concentration of design and review expertize
- Frequently in critical path; increasing risk of missing some specs

Progress in detectors tightly coupled to progress in FE ASICs



Organizational and design resources must keep increasing

Conclusions

- Input MOSFET operates in **moderate inversion**, far from capacitive matching
- Charge amplification in CMOS requires **active reset, biasing and linearization**
- Progress in radiation detectors **tightly coupled** to progress in front-end ASICs
- Front-end ASICs
 - rapid increase in **demand, functionality, programmability, and complexity**
 - increase in **risk of failures** with consequent need to **accept trade-offs**
 - require continuous increase in **organizational and design resources**
 - main front-end ASIC enemies: "perfection" and "general purpose"

Acknowledgment

Vinnie Polychronakos: leadership and support


George Iakovidis: measurements, debugging and documentation

Sorin Martoiu: L0 digital core design

NSW community

Backup

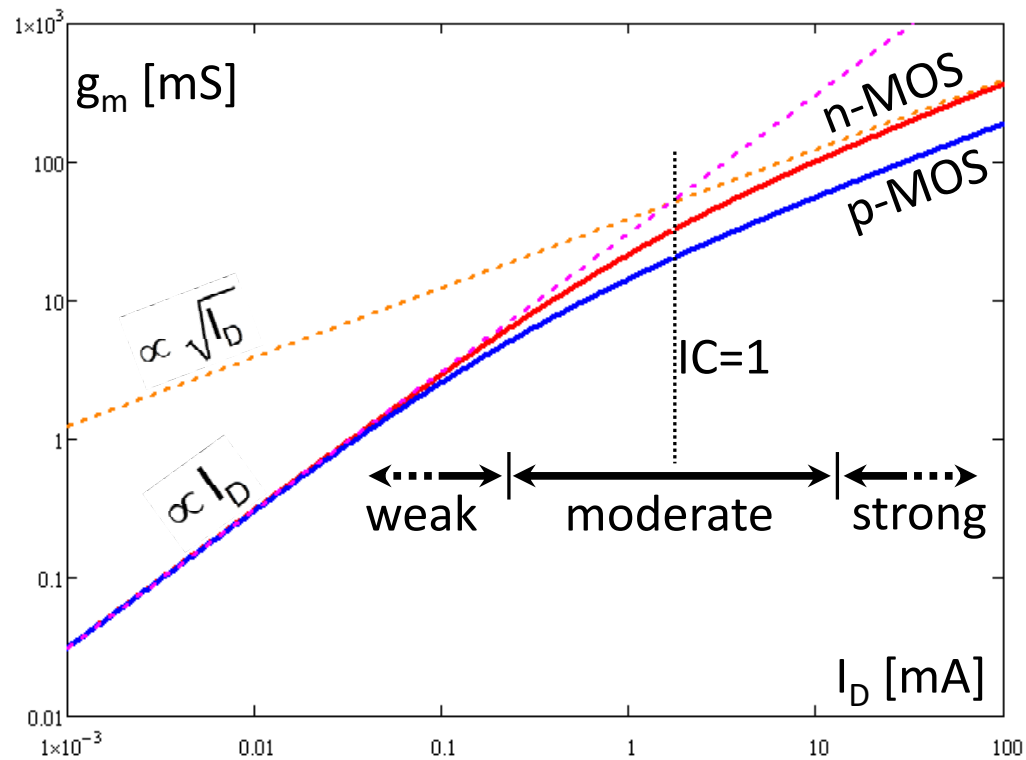
Transconductance g_m in Moderate Inversion



From EKV model
$$g_m(I_D) \approx \frac{I_D}{nV_T} \frac{\sqrt{1 + 4 \cdot IC} - 1}{2 \cdot IC}$$

$$IC = \frac{L}{W} \frac{I_D}{2nV_T^2 \mu_{ox}}$$
 inversion coefficient

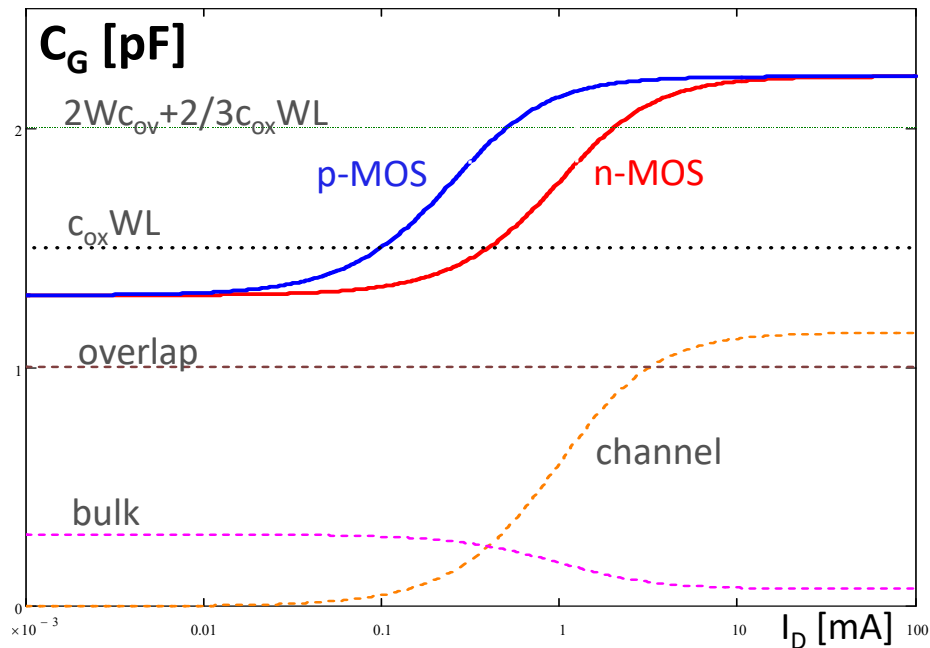Gate Capacitance C_G in Moderate Inversion




$$\propto C_{ox}WL$$

$$C_G(I_D) \approx 2c_{ov}W + C_{ox}WL \left(\gamma_c(IC) + \frac{n-1}{n} [1 - \gamma_c(IC)] \right)$$

$$\gamma_c(IC) \approx \left(\frac{3}{2} + \frac{1}{3} \frac{\sqrt{1+4 \cdot IC + 1}}{IC^2} \right)^{-2/3}$$

Both g_m and C_G push towards n-channel and $L = L_{min}$

Low-Frequency Noise vs L

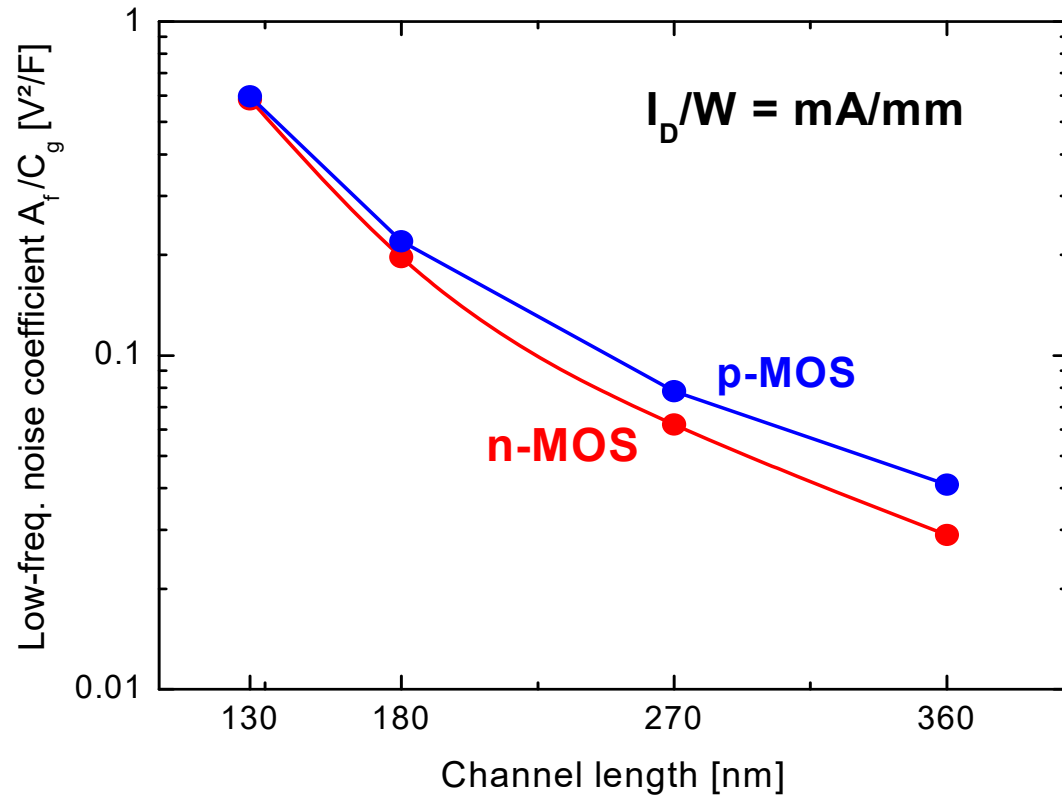



A_f/C_G decreases more rapidly than $1/L$



$$S_v = \frac{A_f(L)}{C_G f^\alpha} + \frac{A_w}{g_m}$$

Low-frequency noise pushes towards p-channel and $L > L_{\min}$


Reset Discharge Noise

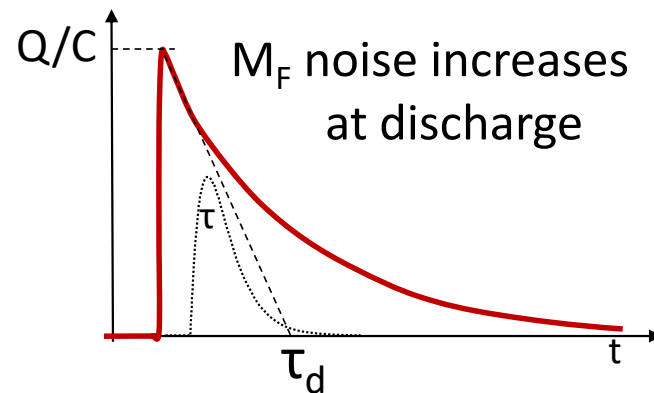 

$$\delta ENC_{id}^2 \leq \frac{a_i}{2} 2qQ \frac{\tau}{\tau_d} \quad \text{use large } \tau_d/\tau$$


De Geronimo, NIM A 421, 1999

At high rate ρ
 $\bar{\tau}_d$ decreases

 


$$\delta ENC_{idr}^2 \leq \frac{a_i}{2} 2qQ\rho\tau$$

AC Coupling

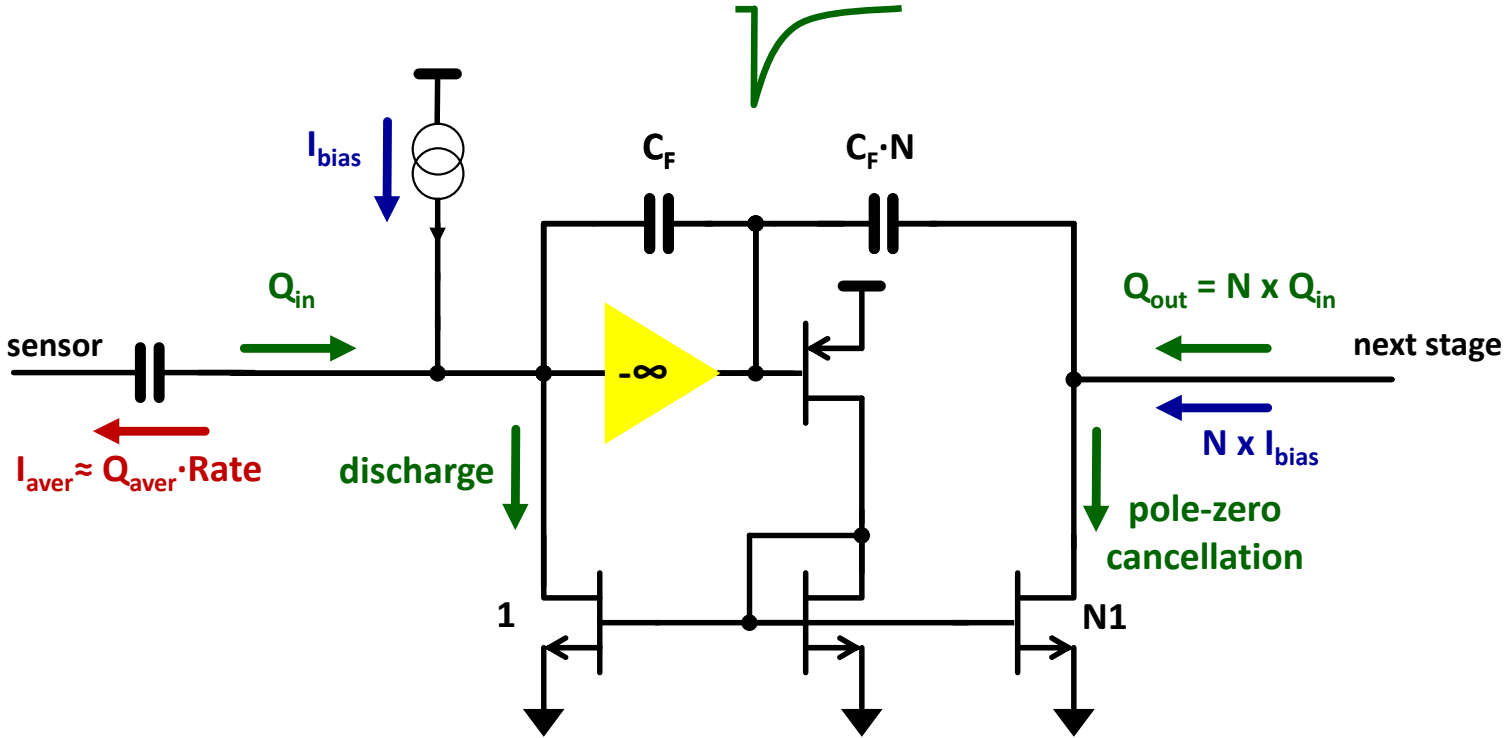

$I_{aver} > I_{bias} \rightarrow$ amplifier shuts down \rightarrow dead time


Full Mirror Reset

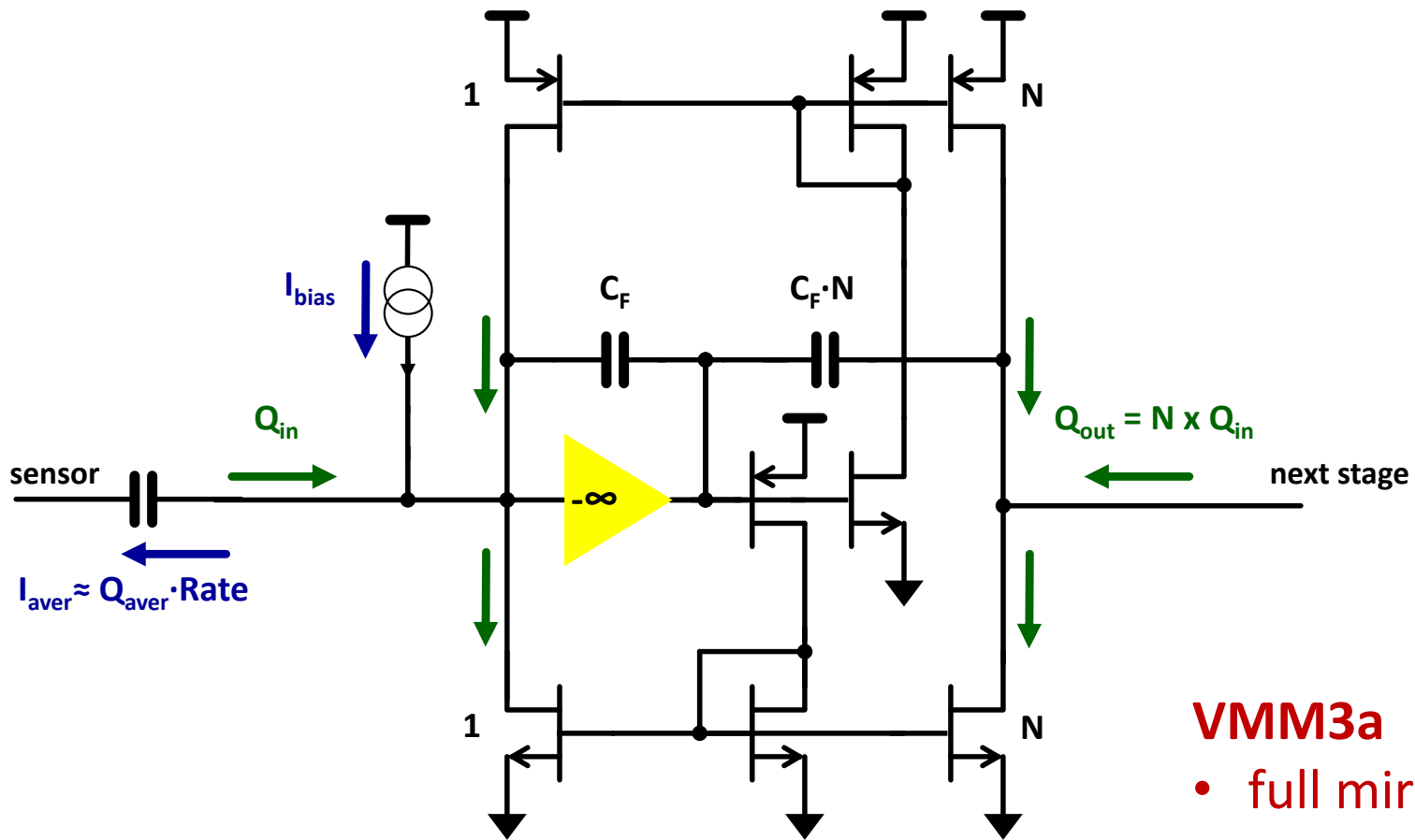

VMM3a
 • full mirror enable

Shaper in Delayed Dissipative Feedback

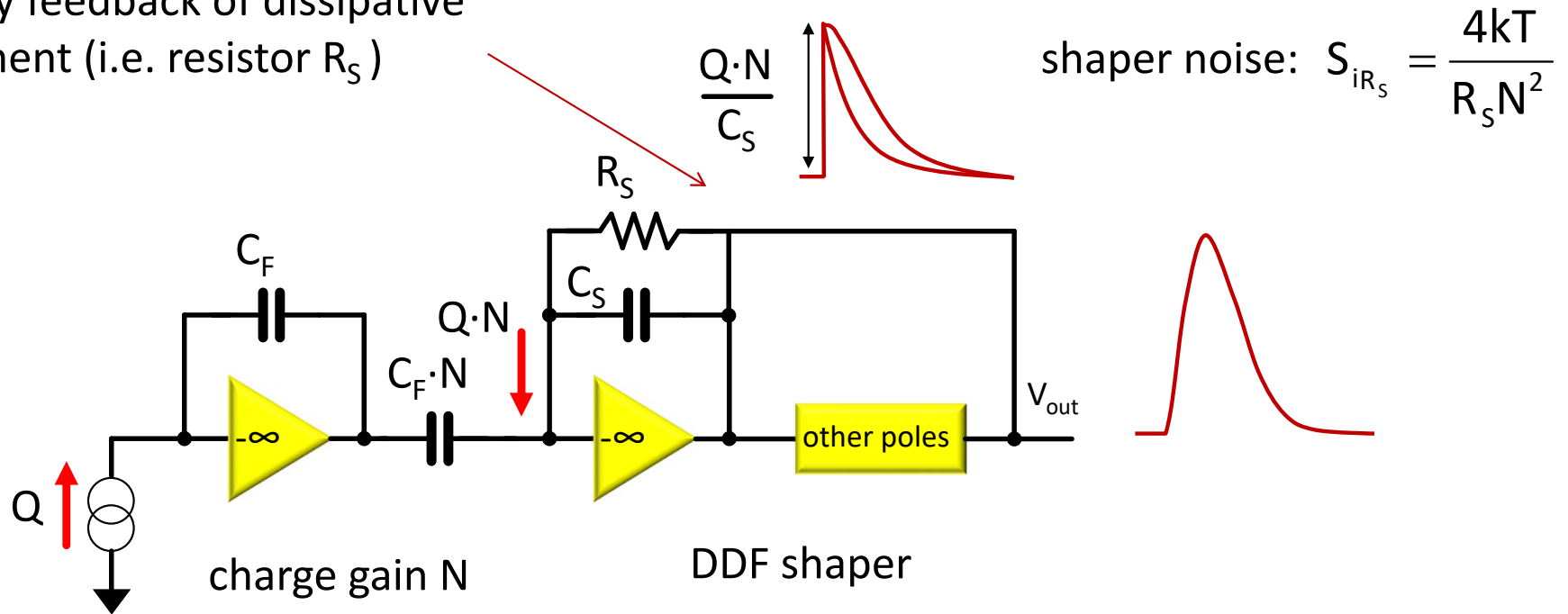
delay feedback of dissipative element (i.e. resistor R_S)



high analog dynamic range

$$DR_a \approx \frac{Q_{max}}{ENC_{ca} + ENC_{sh}}$$

VMM3a Optional Packaging

 

BGA 400 pin, 21 x 21 mm, pitch 1 mm