

# Calorimeter Upgrade Meeting

Analog Electronics  
COTS design


22/jun/2010

# Main ideas of COTS

- Commercial Off The Shelf
  - Intended to be cheaper than ASIC
  - Easy to find
  - Commercially tested, no risk of mistakes in chip design
  - Much faster and easier design and test
  - Not the same integration level
  - Not the same flexibility
  - Not the same performance

# Current CALO reminder



- Current CALO scheme [1]

 

[1] LHCb Calorimeter TDR (CERN-LHCC-2000-036)


 
 
# Current CALO reminder

- Clipping with delay lines
  - In the PMT Base



   
# Current CALO reminder

- Integration
  - Delayed Lines Integrator




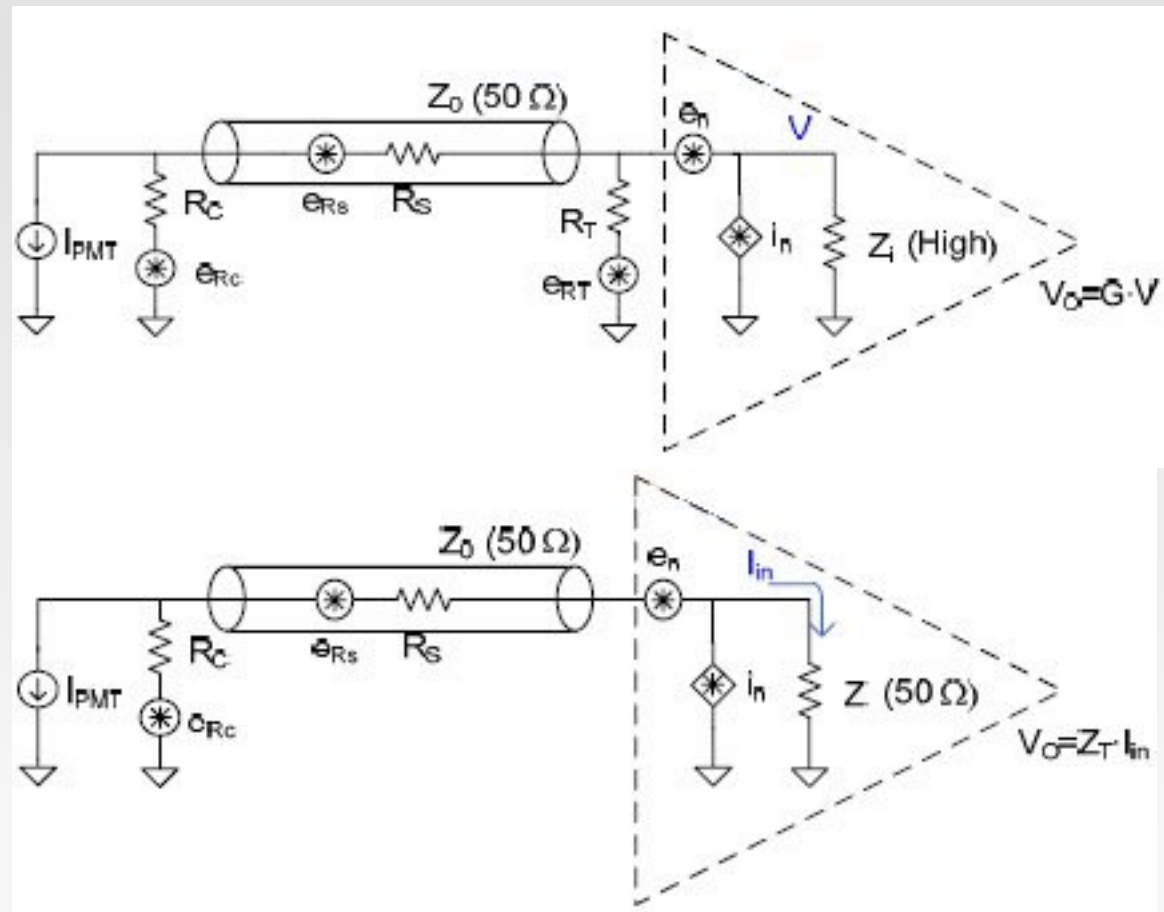
# Noise Problematic

- Reducing the gain in the PMTs → less signal and same noise!
- Low noise needed
- Difficult with COTS
- Noise in the PMT base


  
# Possible Solutions with COTS


- Super Common Based Amplifier
- ATLAS LAr CALO uses one of those (4 chan)





# Possible Solutions with COTS



- Space is not an issue (LAr Calo Board)

 


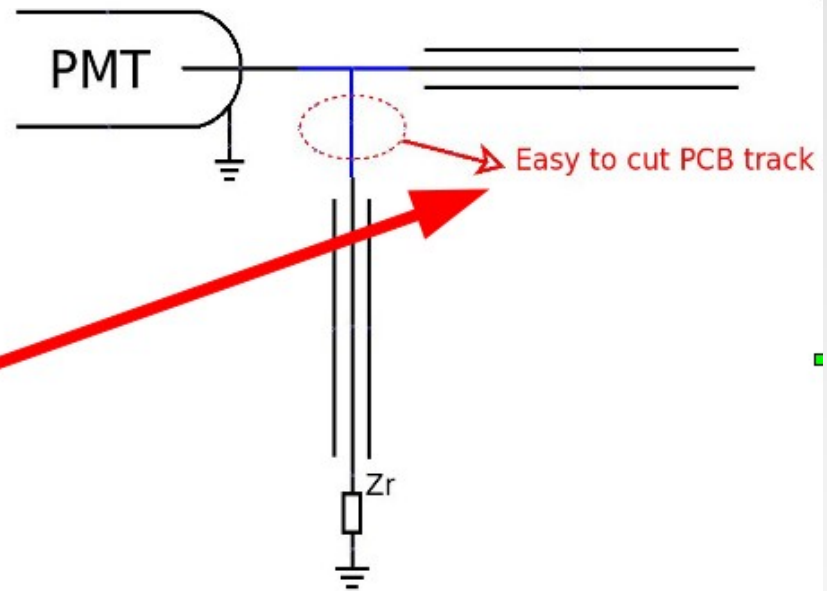 
# Possible Solutions with COTS

- Manipulate the PMT's base to reduce noise





# Possible Solutions with COTS


- Manipulate the PMT's base to reduce noise and relax system specifications
  - The resistor in the PMT's base has some contribution to noise, we could get rid of it.
  - Clipping in the base reduces useful signal, we would remove it.
  - With greater signal the signal/noise ratio would increase.
  
# Different Clipping Approach

- Clipping after amplifying  
→ Impedance problem...
- Equivalent system found,  
same impulse response  
but no impedance  
problems.




# Studied Architectures ( I )

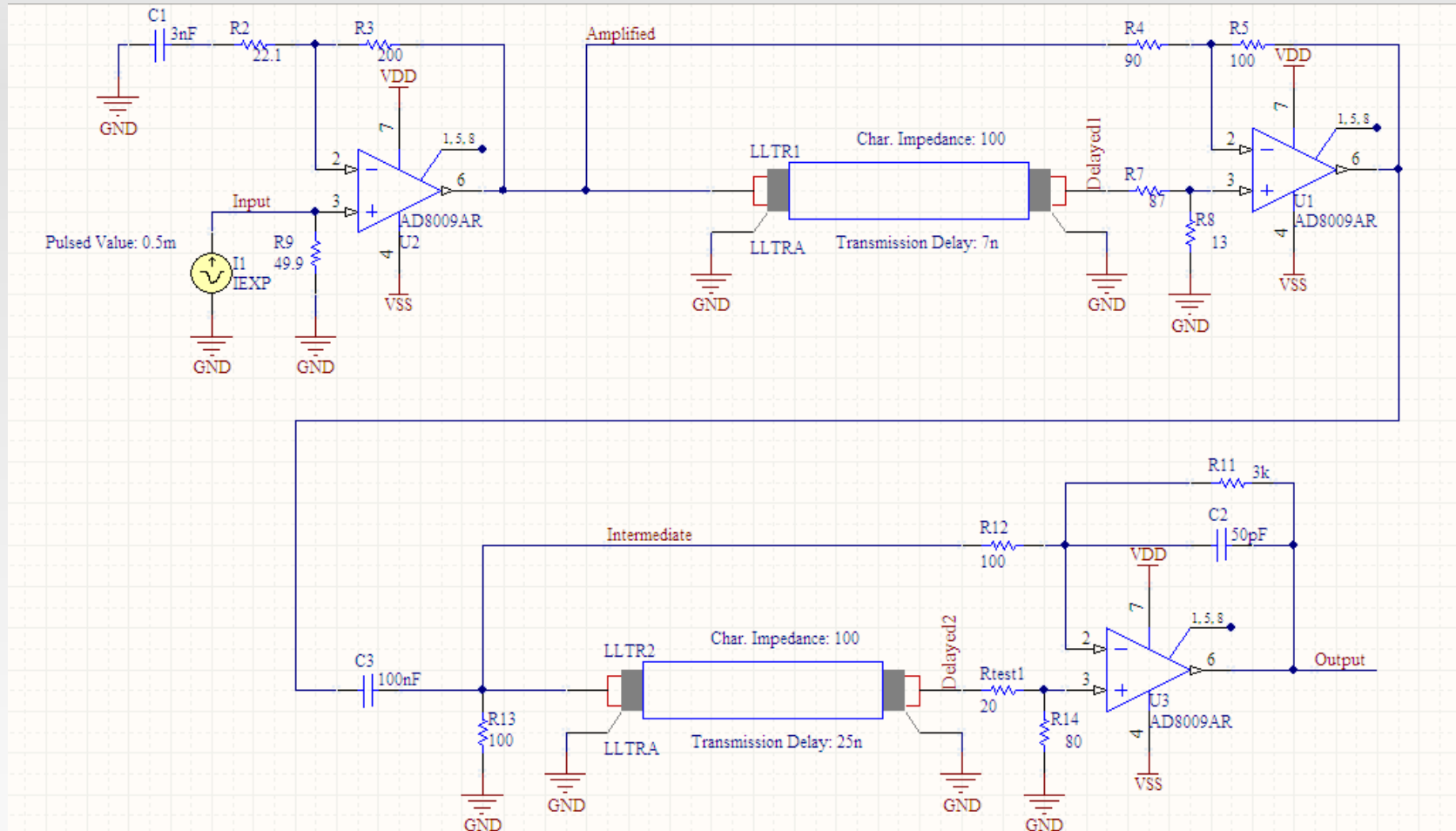




# Studied Architectures ( I )

 

$$Output = \frac{1}{\tau} \int (Intermediate - Delayed2) dt + Delayed2$$

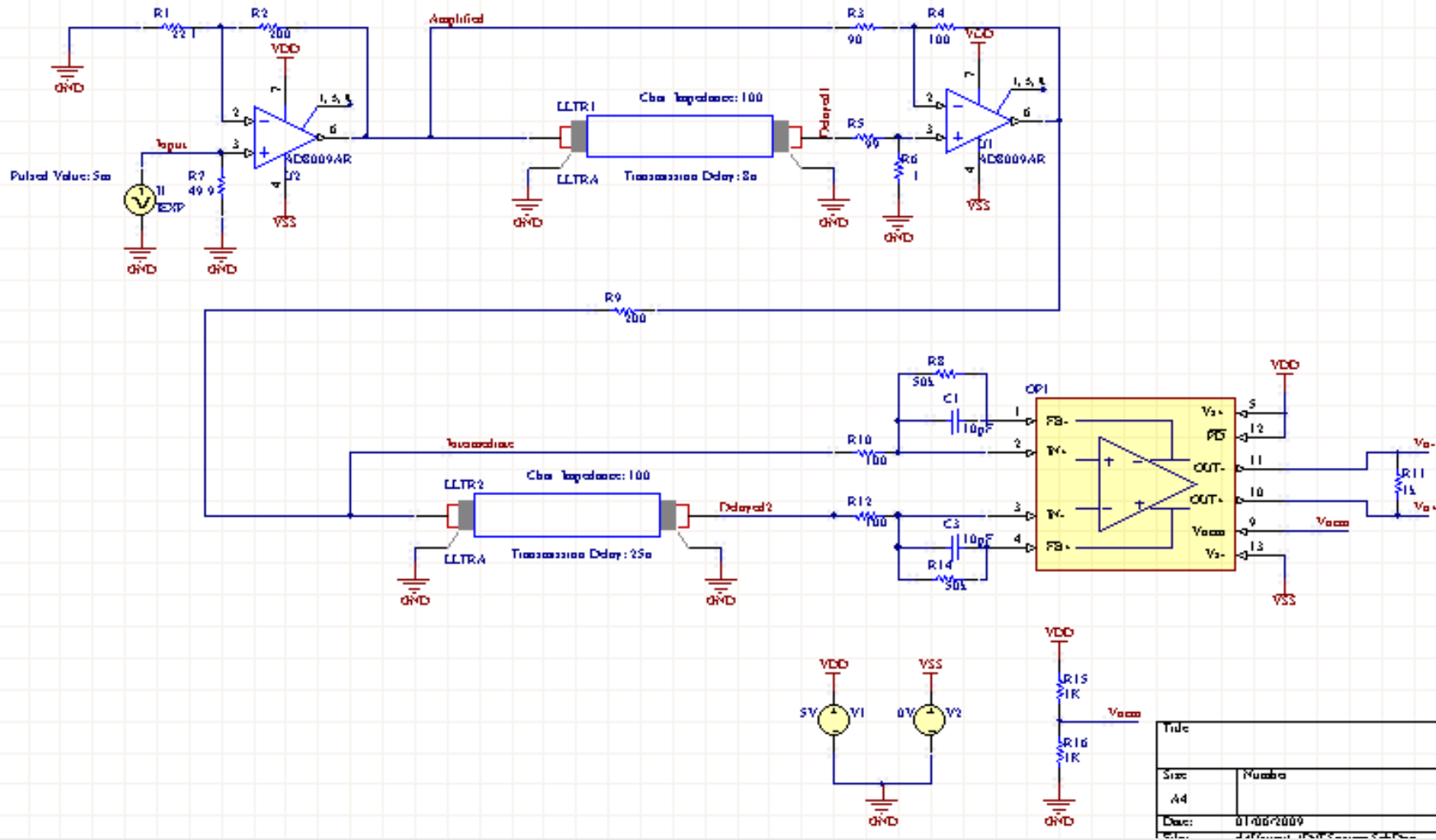
# Studied Architectures ( II )

- Scheme with Differential operational amplifier



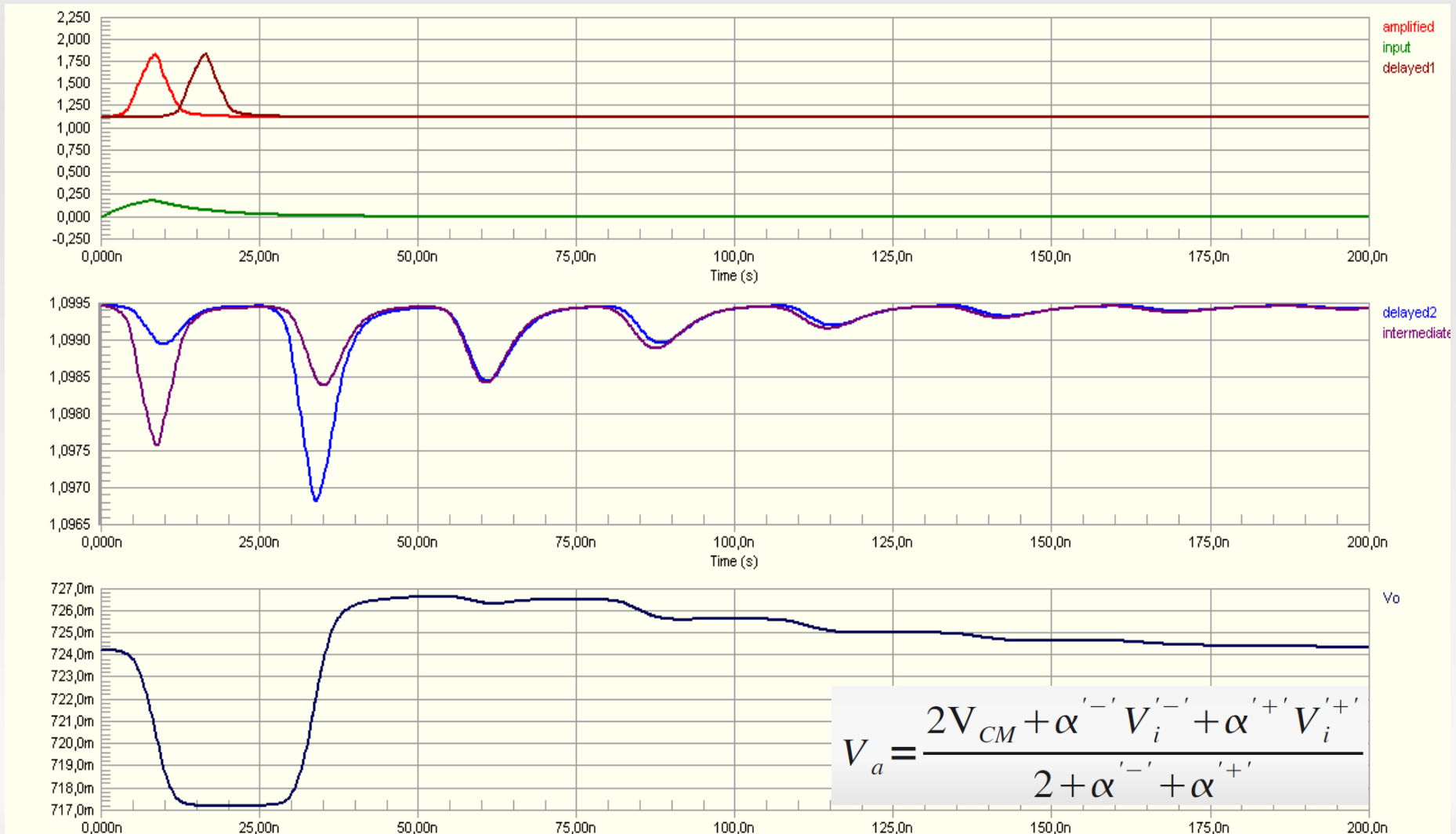
# Studied Architectures ( II )

- Scheme with Differential operational amplifier



# Studied Architectures ( II )

- Schematic of the adaptation system

 

- Equations of the system

$$Z_B = R_B \parallel (r_d + R_L)(hfe + 1) \quad hie \approx 100 \quad Z_B \approx 230K$$

$$Z_{OUT} = R_L \parallel r_d + \frac{Z_0 \parallel R_B}{hfe + 1} \quad hfe \approx 500 \quad Z_{OUT} \approx 2$$

$$r_d = \frac{hie}{hfe + 1} \quad r_d \approx 0.2 \quad Gain \approx 1$$

$$R_L \approx 1K5$$


$$R_B \approx 416K$$

$$C \approx \text{some } nF$$

$$\text{Power Consumption} \approx 3mW_{16}$$



# Studied Architectures ( III )

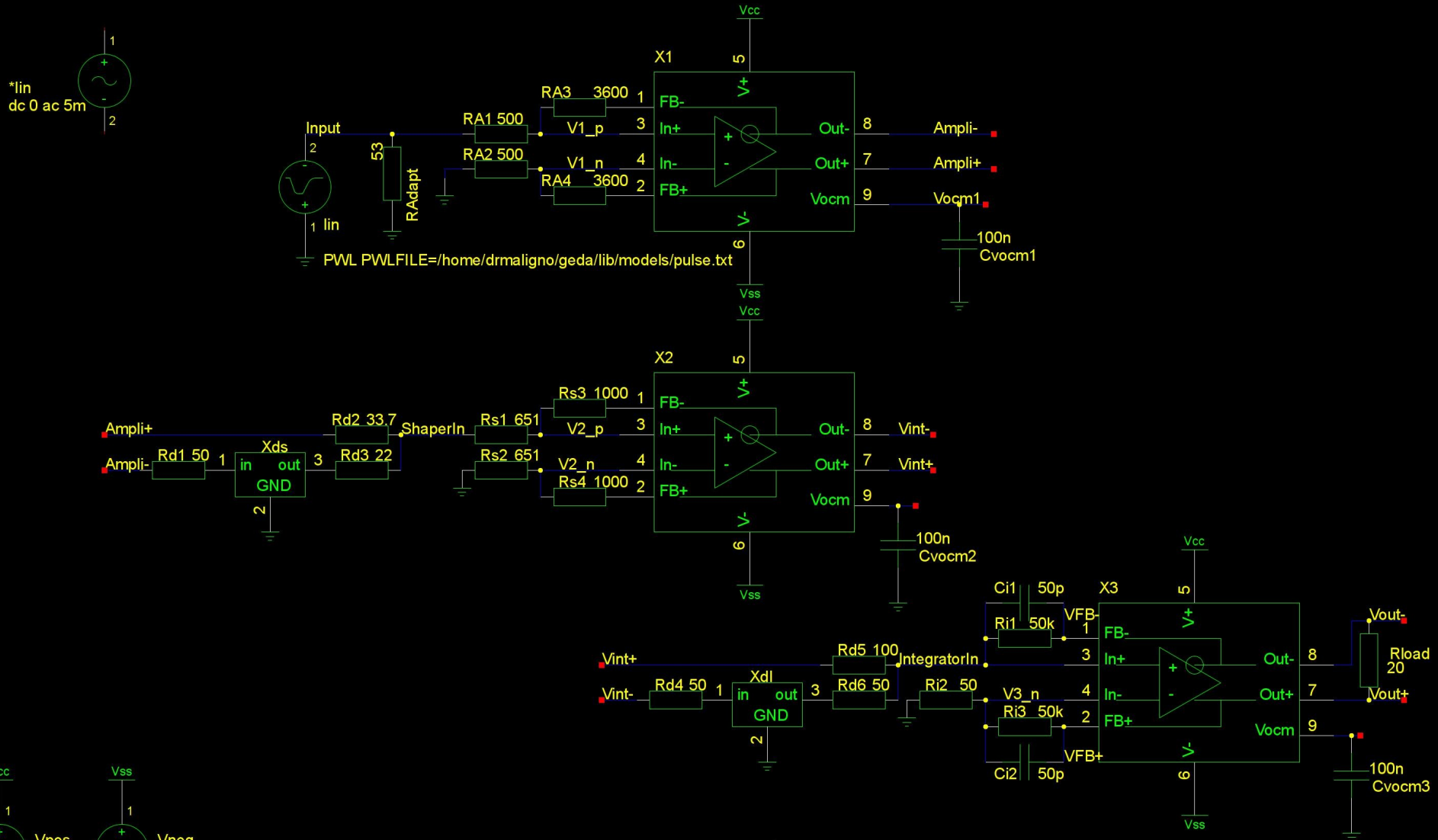

A? SPICE include

File: /home/drmaligno/geda/prj/FEB/simoptions.opt

TITLE

FILE:

PAGE


OF

REVISION:

DRAWN BY:

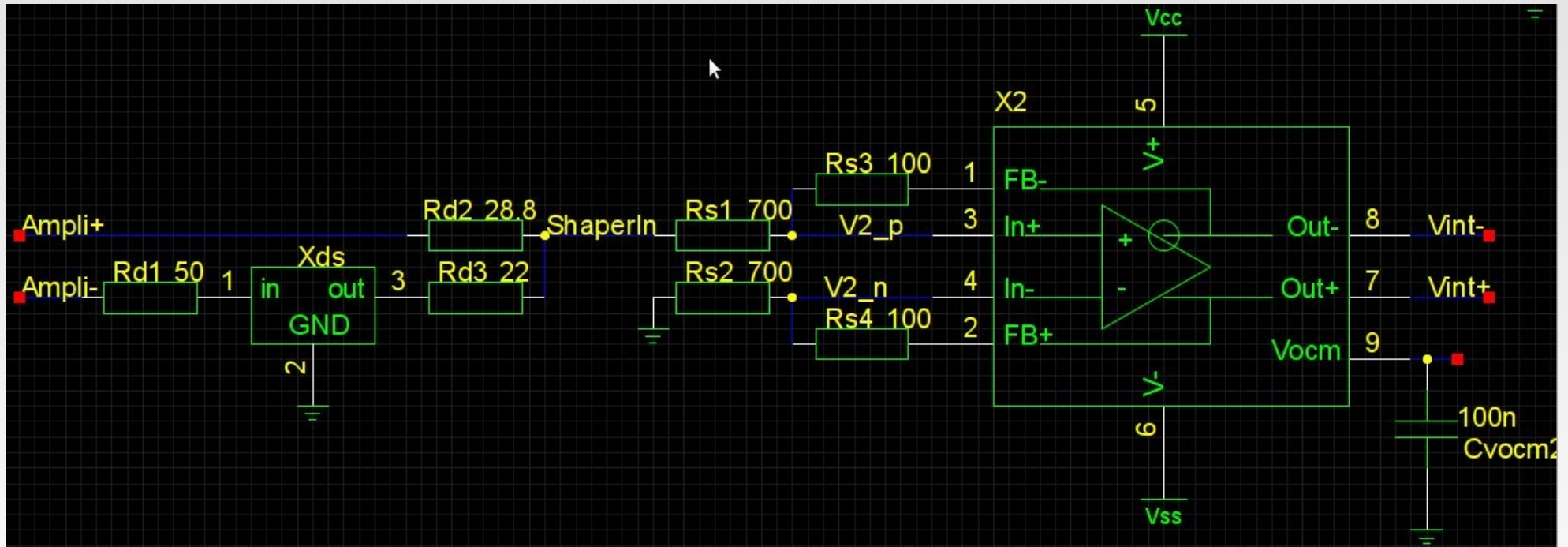
# Studied Architectures ( III )

- Different approach to same idea, no loop




# Studied Architectures ( III )

- Amplifying Stage

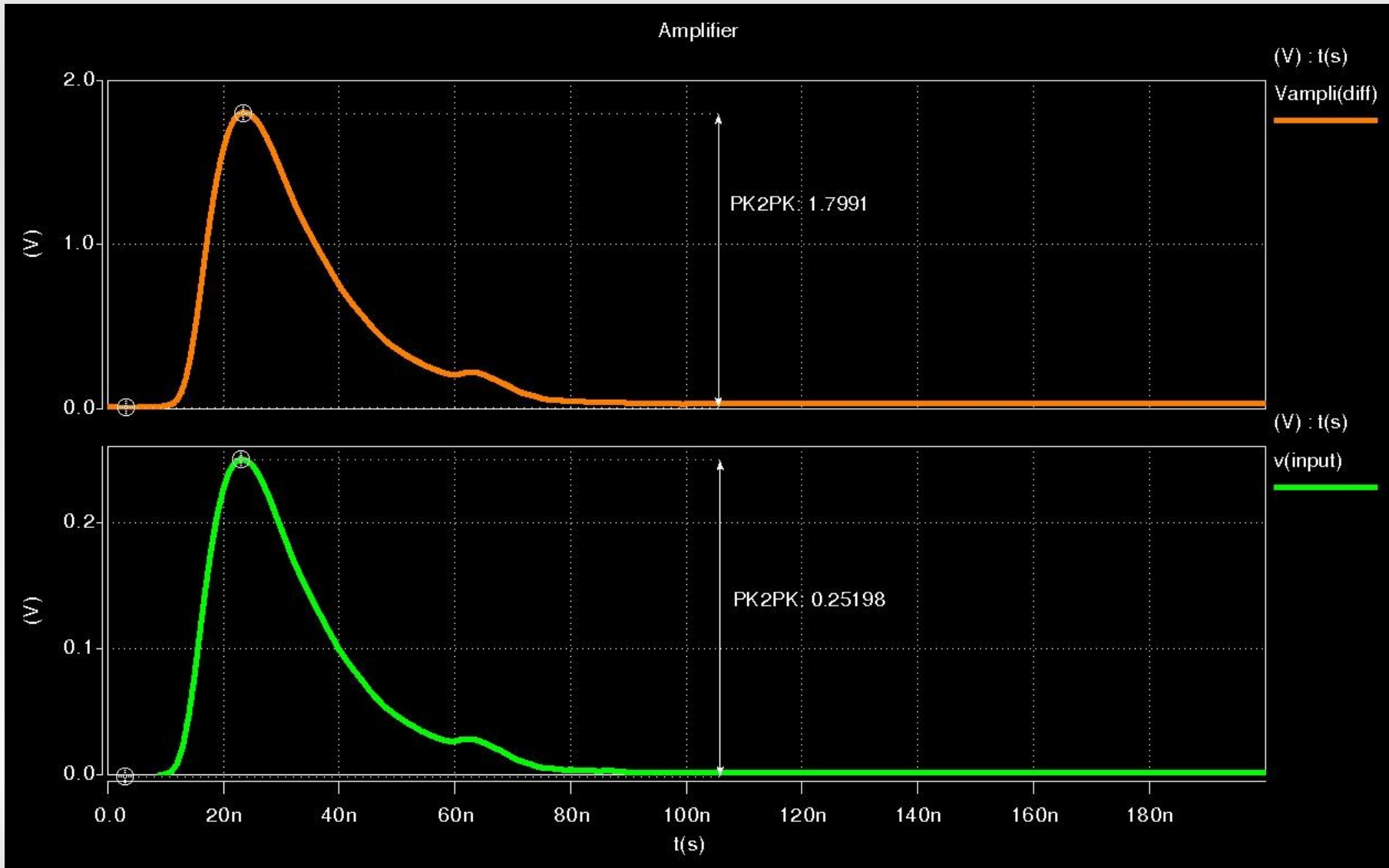

# Studied Architectures ( III )


## Clipping Stage

 




# Studied Architectures ( III )

- Integrator Input

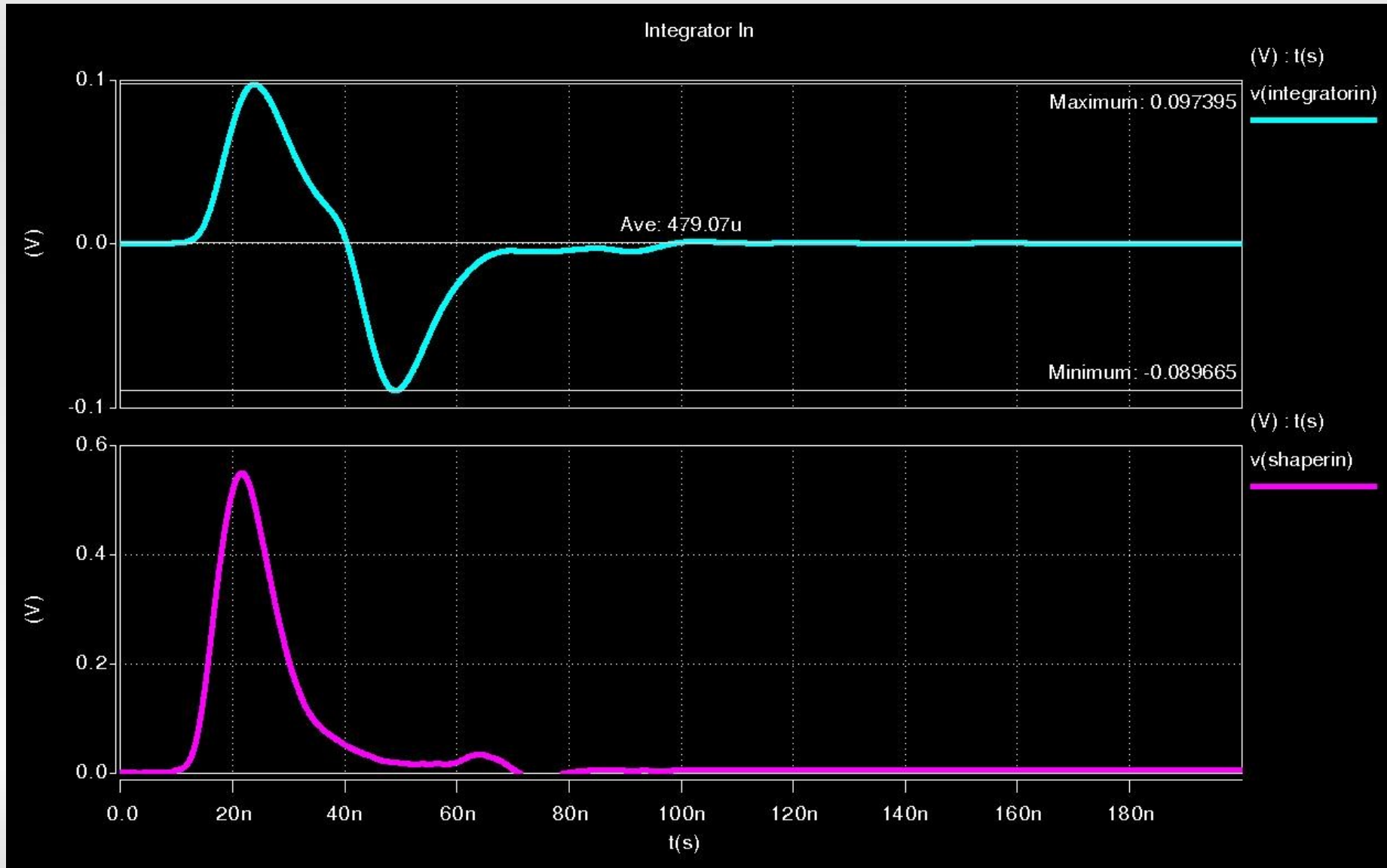

# Studied Architectures ( III )

## Integrator Output


 


# ADC Selection


- In order to make the proper interface between the analogical part and the ADC it is necessary to have it previously selected.
- Our ADC needed 12 bits resolution, at least 40MHz conversion frequency and it was also desirable a small package due to space restrictions.
- The more suitable components for our application where:
  - Texas Instruments ADS6122
    - 1 ADC/Chip but 5x5mm only, LVDS, DDR!
  - Texas Instruments ADS6222
    - 2 ADC/Chip, LVDS, DDR!
  - Analog Devices AD9238
    - 2 ADC/Chip, LVTTTL.
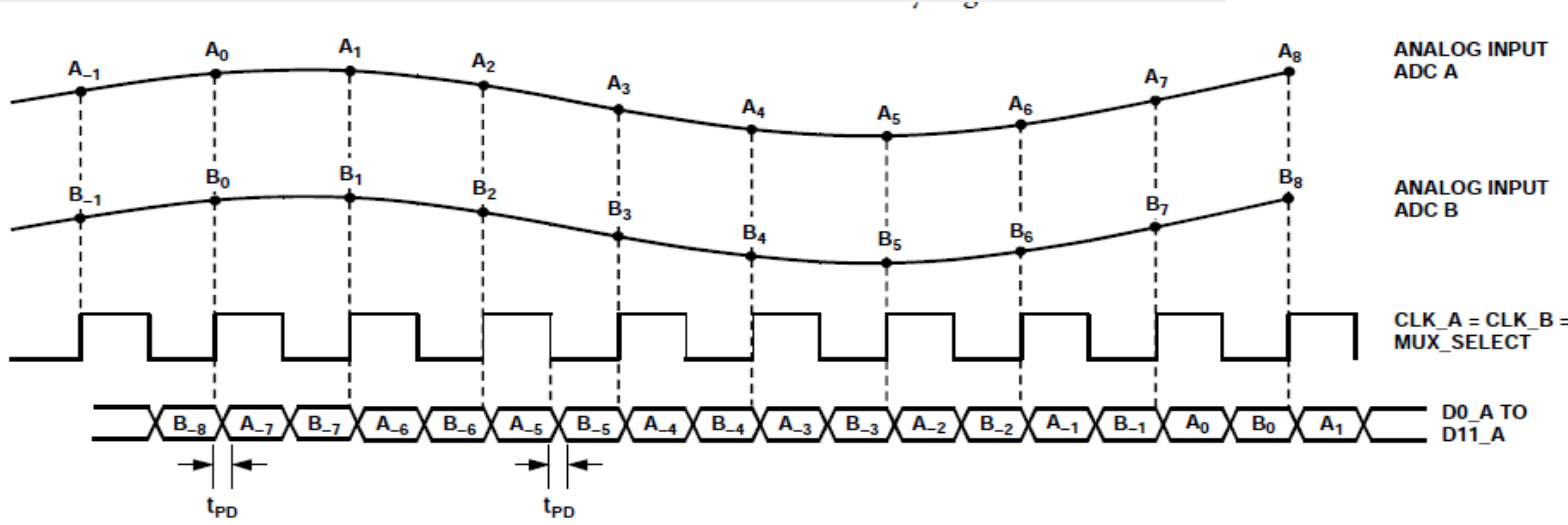 
# ADC Selection

- Analog Devices AD9238
  - One sampling clock per channel
  - Optional multiplexing
  - No RAM configuration




# First Set of Prototypes

 




# First Set of Prototypes

 




# First Set of Prototypes

 




# First Set of Prototypes

 


# Some Measurements

- Gain

 

# Some Measurements

- Zin

 

# Further Steps

- Finish the prototype and measure all the real life effects
- Perform noise measurements and tradeoff with reflection coefficient
- Fine tune shaping method
- Measure ADC response
- Tests with digital part


# Backup Slides

- If more information needed...




# Backup Slides

## Input Stage Gain

 


# Backup Slides

## Input Stage Impedance

 


# Backup Slides

## Input Stage Reflection Coefficient

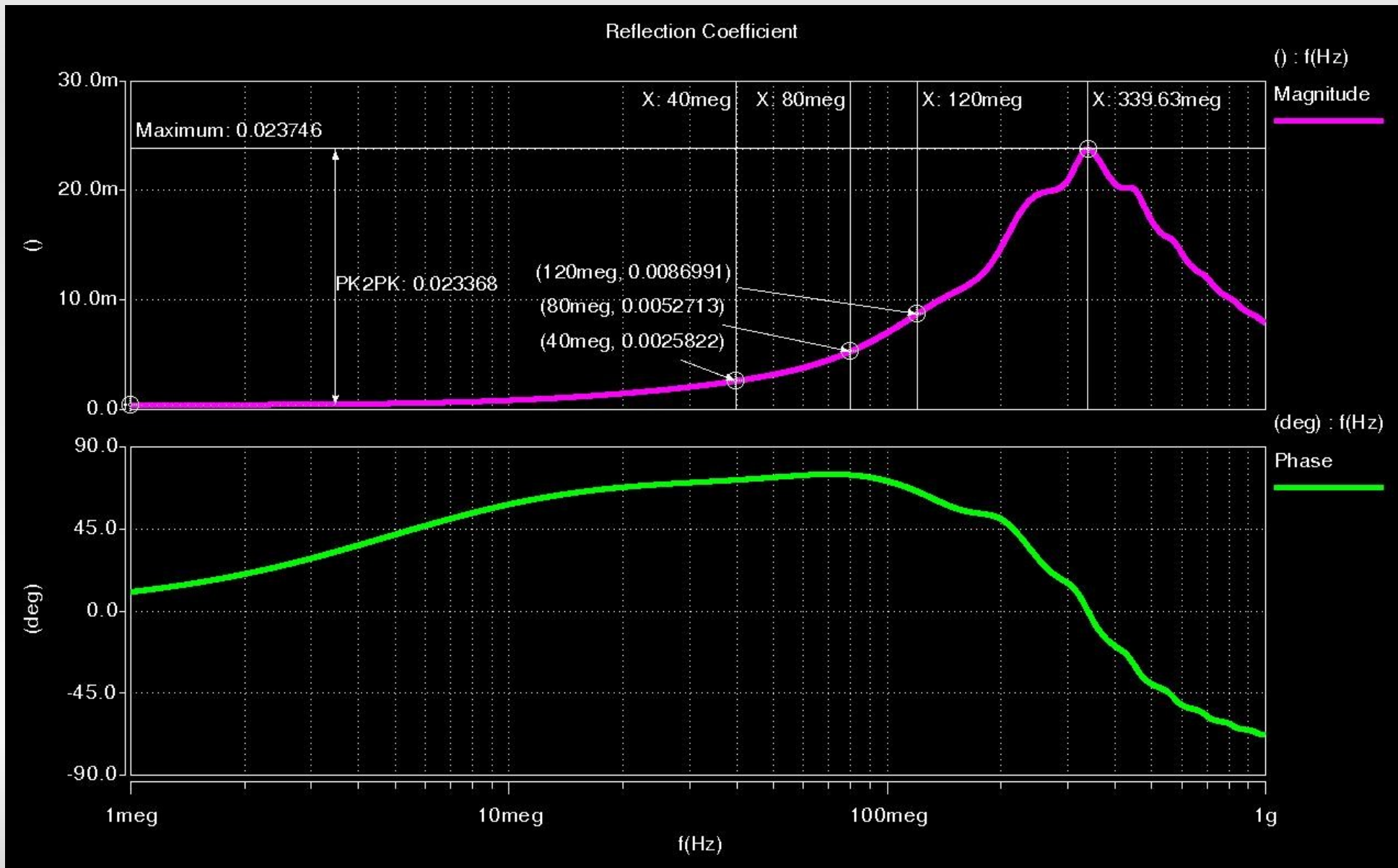


# Backup Slides

## Output Zoom

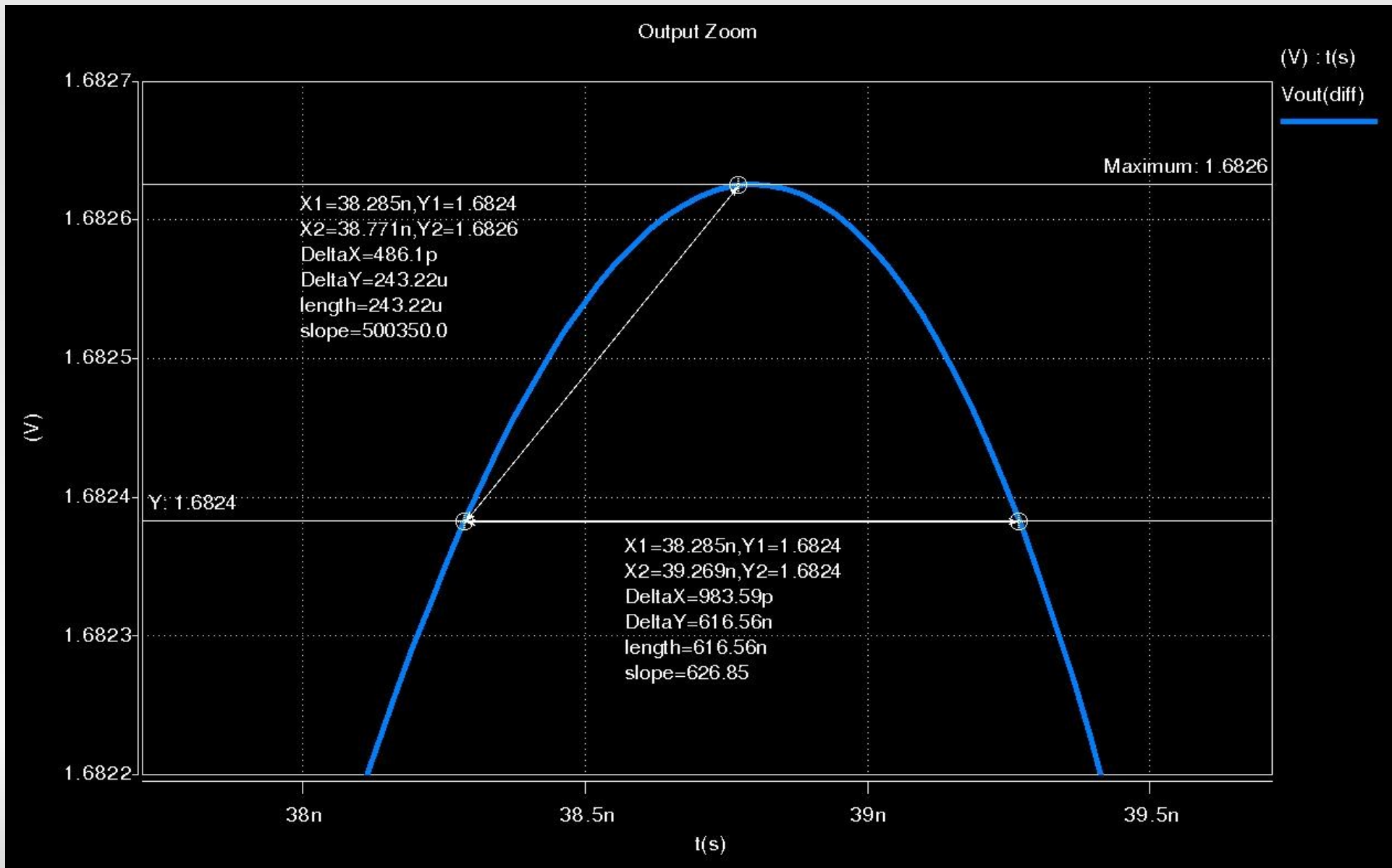

# Backup Slides

- Theoretical Noise vs  $R_f$

 

# Backup Slides

- Linearity
  - Definition: Charge/Voltage [C/V]
  - Simulated Linearity Error dependin on input pulse amplitude

