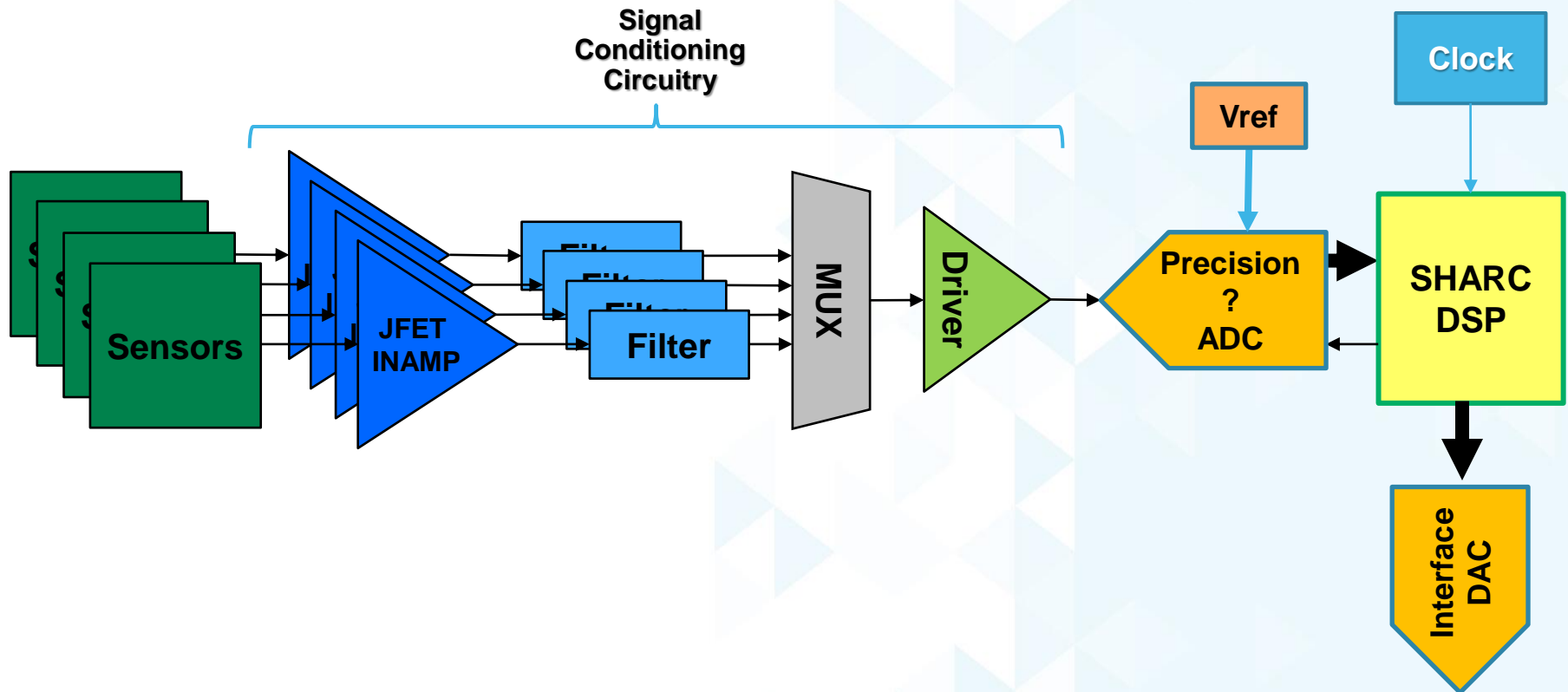


SAMPLING


From continuous time to discret time

Industrial Analog Signal Chain -> Digital




SAMPLING: *TIMING* ACCURACY

 - ΔV_s is an error from V_{in} to sampled signal
- It depends on V_{in} frequency as well as the CLK jitter and the switch resistance etc...
- It will degrade the SNR for the sampled signal
- It can be defined by: $\Delta V_s = \left(\frac{dV_{IN}}{dt} \right)_{max} \cdot \Delta t$






Analog Memory or wave recorder

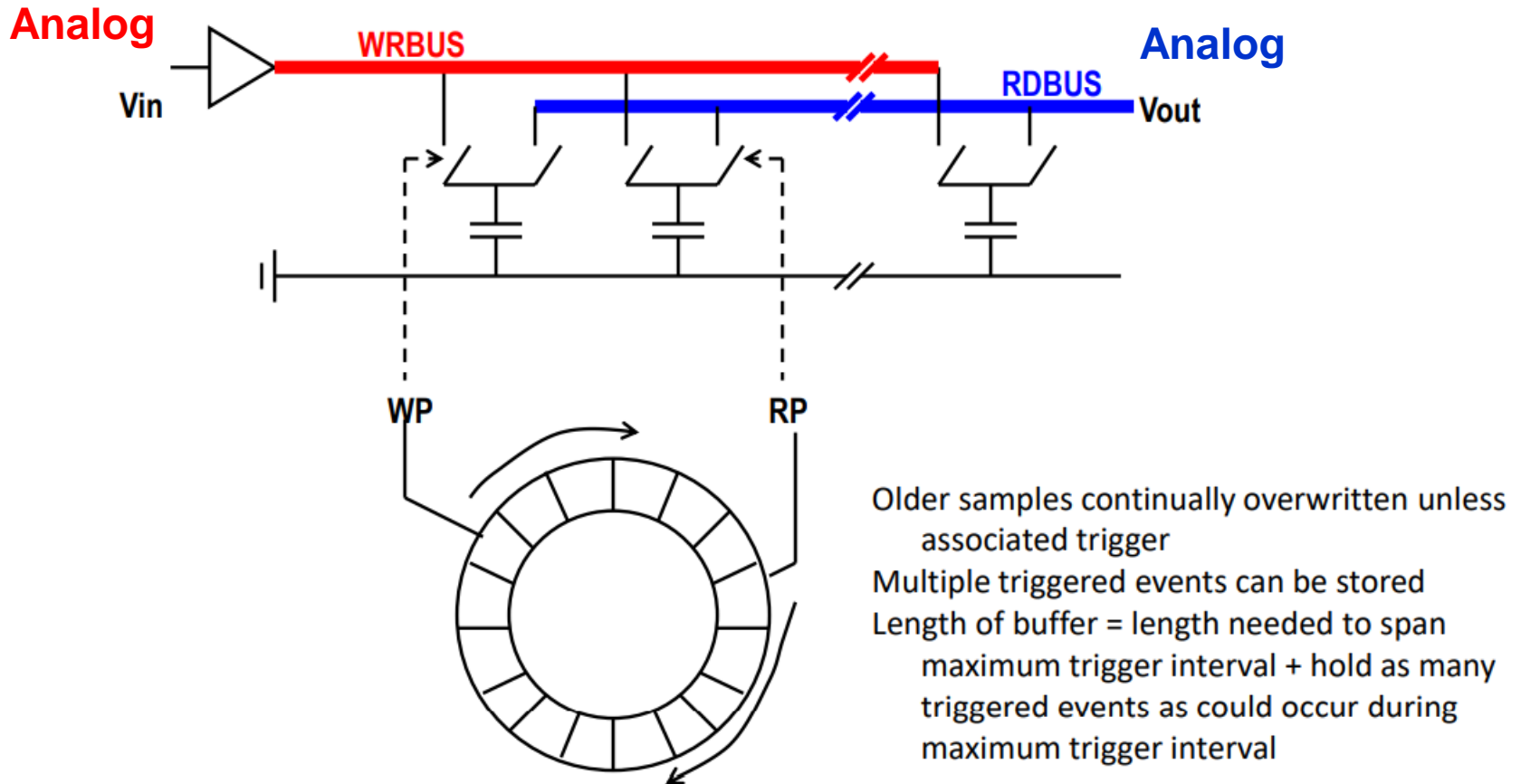

CHARGE INJECTION ISSUES: CLOCK FEEDTROUGH

- MOS switch couples the clock transitions to the sampling capacitor through its gate-drain C_{GD} or gate-source C_{GS} overlap capacitance, also denoted C_{ov} (the overlap capacitance per unit width)
- The effect introduces an error in the sampled output voltage:
 
$$\Delta V = V_{CK} \cdot \frac{W \cdot C_{ov}}{W \cdot C_{ov} + C_H}$$




CHARGE INJECTION ISSUES: CHANNEL CHARGE INJECTION

- When input signal is sampled on a capacitor by turning off the transistor, charge Q_{CH} is pushed out from the channel to either direction. For a NMOS transistor Q_{CH} is defined by:



$$Q_{CH} = WLC_{ox}(V_{DD} - V_{in} - V_{t,n})$$

 - This phenomenon is called "**channel charge injection**"
- The magnitude of Q_{CH} is a complex function of various parameters, such as the impedance seen at each terminal to ground and the transition time of the clock




CHANNEL CHARGE INJECTION: COMPENSATION TECHNIQUES

  - **Bottom plate sampling** scheme is another technique to eliminate the charge injection error
- Two switches are used and the signal is sampled when M_2 turns off
- M_2 turns off slightly before M_1 injecting a constant charge
- Signal dependent charge from M_1 does not enter C_H because there is no path to ground




SAMPLING: CLK'S JITTER LIMITATIONS


 
- ΔV_s can be considered as amplitude fluctuation (clk jitter)
- It will degrade the SNR of the sampling signal
- It can be defined by: $\Delta V_s = \left(\frac{dV_{IN}}{dt} \right)_{max} \cdot \Delta t$



THERMAL NOISE: KT/C

 

 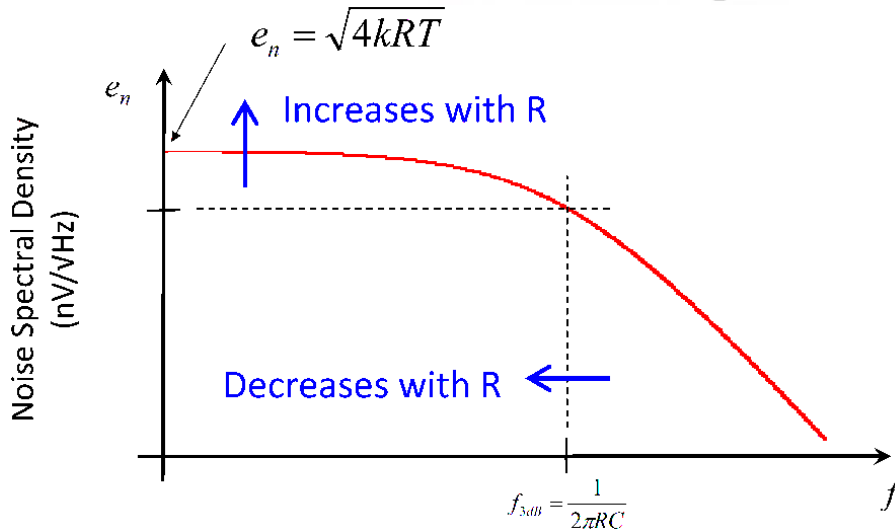• C is not the fundamental cause; just have a thermal noise (R) and the bandwidth is limited by C.



What happens:

- Increasing C?
- Increasing W/L of the switch?
- Increasing both?

C	Eq. Noise
1 pF	64.34 μ V rms
10 pF	20.35 μ V rms
100 pF	6.43 μ V rms
1 nF	2.03 μ V rms

Thermal noise KT/C

- From the switch capacitor circuit and the resistance of the switch, we can define the transfer function $\frac{V_{out}}{V_{in}}$ as:


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + RCp}$$

- PSD Noise from **resistance** is defined by:

$$S_v(f) = 4kTR$$

- The Output PSD Noise is then:

$$S_{out}(f) = 4kTR \left| \frac{V_{out}}{V_{in}} \right|^2$$

 

- The white noise spectrum of the resistor is **shaped by a low-pass RC**, and the the total noise power at the output is:



$$P_{n,out} = \int_0^{\infty} \frac{4kTR}{4\pi^2 R^2 C^2 f^2 + 1} df = \frac{kT}{C} \int_{-a}^a \frac{dx}{1 + x^2} = 2 \arctan a$$

- This noise is a function only of temperature and capacitance values

EQUIVALENT NOISE BANDWIDTH IN RC FILTER

◆ Consider a single pole RC low pass filter

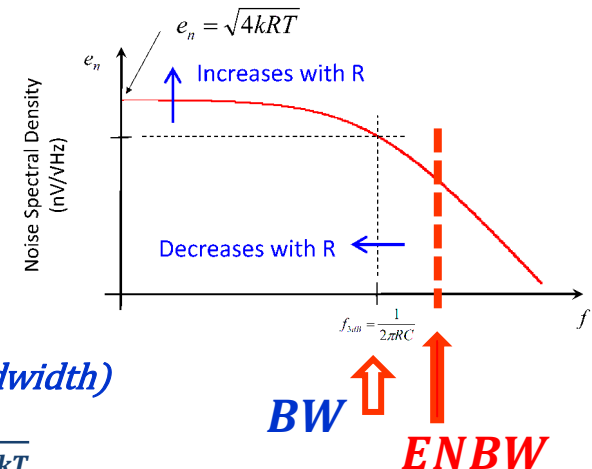 - $BW = \text{Corner frequency} = \frac{1}{2\pi RC}$
- $\text{Resistor Noise Density} = \sqrt{4kTR} \rightarrow \text{V}/\sqrt{\text{Hz}}$
- $\text{Gain}=1$
- $ENBW = \frac{\pi}{2} BW = \frac{\pi}{2} \frac{1}{2\pi RC} = \frac{1}{4RC}$ (Equivalent Noise Bandwidth)
- $\text{Total output Noise} = \text{Noise Density} * \sqrt{ENBW} = \frac{\sqrt{4kTR}}{\sqrt{4RC}} = \sqrt{\frac{kT}{C}}$



Magnitude



Value	Noise
1 pF	64.34 $\mu\text{V rms}$
10 pF	20.35 $\mu\text{V rms}$
100 pF	6.43 $\mu\text{V rms}$
1000 pF	2.03 $\mu\text{V rms}$

	Noise
1 k Ω resistor with BW limited to 1 MHz	5.1 $\mu\text{V rms}$
A LNA: $E_N = 2 \text{ nV}/\sqrt{\text{Hz}}$, Unity gain buffer BW limited to 1 MHz	2.55 $\mu\text{V rms}$

BOOTSTRAP SWITCH PRINCIPLE

- Channel charge injection is a function of input signal V_{in}
 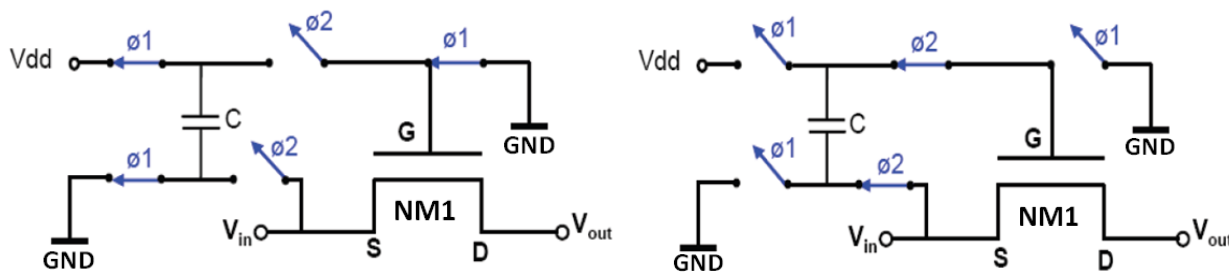
$$Q_{CH} = WLC_{ox}(V_{GS} - V_{t,n}) = WLC_{ox}(V_{DD} - V_{in} - V_{t,n})$$
- Bootstrapping technique suppresses this dependence by making V_G varying as V_{in} , then $V_{GS} = \text{constante}$.




- Distorsion issues are also reduced


Simulation: sampling Linearities issues

Bootstrapped switch :

Hold mode :

 


 
$V_{gs} \text{ constant} \Rightarrow Q_{CH} \text{ constant}$



$Q_{CH} \text{ constant}$

Low Sampling INL

Track mode :

 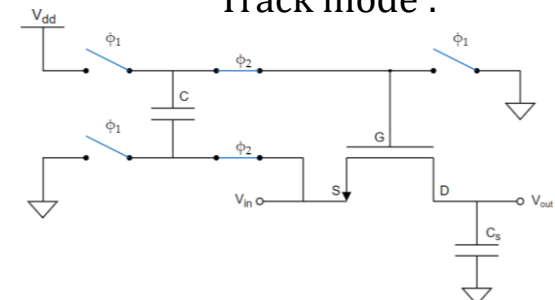



Analog to Digital Converters ADC

ARCHITECTURES & SPECIFICATIONS

What is an ADC?

- Mixed signal circuit:
 - Analog input signal
 - Digital output signal
- ADC **discretize** the **continuous input signal** in **time** and **amplitude**
- Output Code is defined by:
 - $\sum_{i=0}^N \frac{2^i(G \cdot V_{in})}{V_{ref}}$
 - G is the gain factor, N the resolution, V_{in} the input signal and V_{ref} is the dynamic range of the converter

High speed ADC: general overview

  


ADC architecture timeline
(source: Analog Devices)

1939: Counting ADC (Reeves)
 1946: Successive approximation
 1948: Flash (electron tube coders)
 1956: Bit-per-stage (binary and folding-Gray)
 1956: Sub-ranging
 1964: Sub-ranging with error correction
 1966: Pipe line with error correction


ADC Architectures

- Slope type converters
- Successive approximation
- Flash
- Time-interleaved / parallel converter
- Folding
- Residue type ADCs
 - Two-step
 - Pipeline
 - ...
- Oversampled ADCs

From Analog signal to digital codes

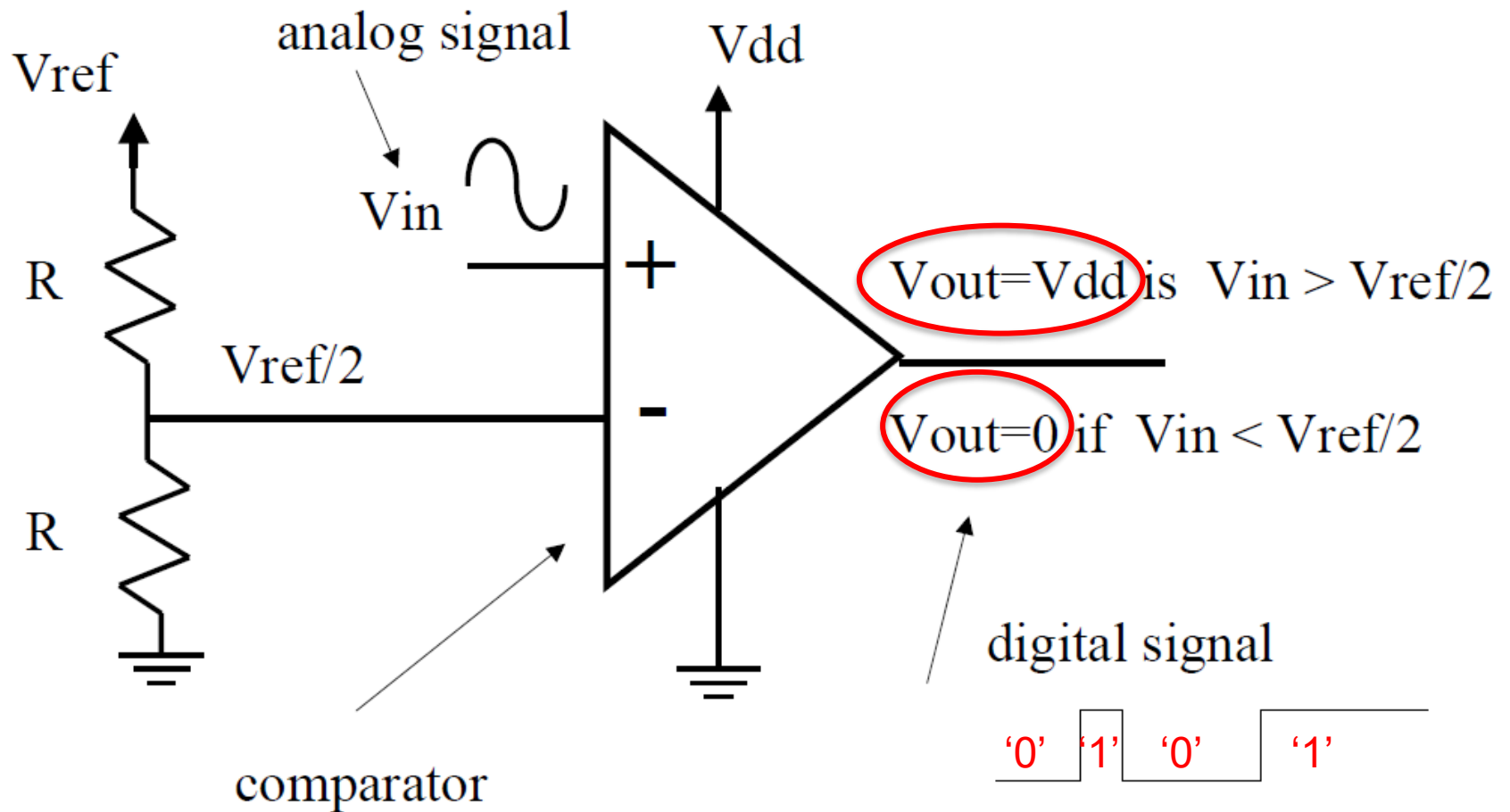


ADC inputs and outputs

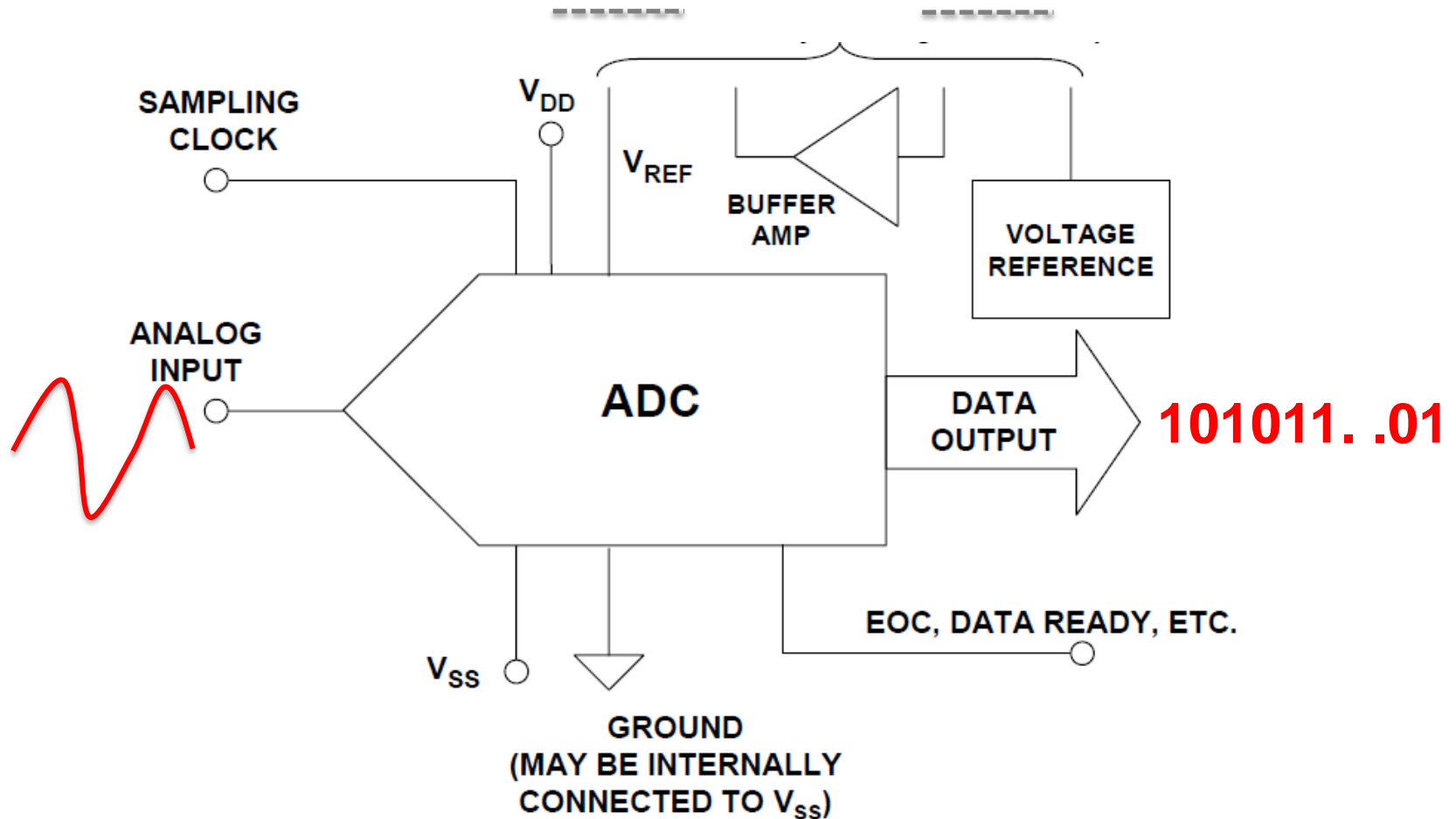

definition

 - **LSB:** Least Significant Bit
- **MSB:** Most Significant Bit



Bit Weights of an 8-Bit Word

MSB							LSB
B7	B6	B5	B4	B3	B2	B1	B0
128	64	32	16	8	4	2	1

LSB – Resolution – V_{ref}

V_{REF}	Resolution	1 LSB
1.00V	8	3.9062 mV
1.00V	12	244.14 μV
2.00V	8	7.8125 mV
2.00V	10	1.9531 mV
2.00V	12	488.28 μV
2.048V	10	2.0000 mV
2.048V	12	500.00 μV
4.00V	8	15.625 mV
4.00V	10	3.9062 mV
4.00V	12	976.56 μV

Digitization of Pulse Height – Analog to Digital Conversion

For data storage and subsequent analysis the analog signal at the shaper output must be digitized.

Important parameters for ADCs used in detector systems:

1. Resolution

The “granularity” of the digitized output

2. Differential Non-Linearity

How uniform are the digitization increments?

3. Integral Non-Linearity

Is the digital output proportional to the analog input?

4. Conversion Time

How much time is required to convert an analog signal to a digital output?

5. Count-Rate Performance

How quickly can a new conversion commence after completion of a prior one without introducing deleterious artifacts?


6. Stability

Do the conversion parameters change with time?


Instrumentation ADCs used in industrial data acquisition and control systems share most of these requirements. However, detector systems place greater emphasis on differential non-linearity and count-rate performance. The latter is important, as detector signals often occur randomly, in contrast to measurement systems where signals are sampled at regular intervals.

Static parameters: DNL/INL

 - Measure the linearity issue
 - Define how the gain can keep constant
- **DNL**: Differential Non Linearity
 - Proximity error between two successive codes
- **INL**: Integral Non Linearity
 - Deviation from a straight line on the whole dynamic



D/A

 

$V_{REF} = 2.0V$

ADC Parameters

- Static

- DNL $DNL(k) = \frac{(X_{k+1} - X_k) - \Delta}{\Delta}$



- INL $INL(k) = \sum_{i=0}^k DNL(i)$

- Dynamic

$$SNR_{dB} = 10 \cdot \log_{10} \left(\frac{P_s}{P_n} \right)$$

$$SFDR_{dB} = 10 \cdot \log_{10} \left(\frac{P_s}{P_h} \right)$$
  
$$ENOB = \frac{SINAD_{dB} - 1.76}{6.02}$$




$$FoM = \frac{P}{2^{ENOB} \cdot f_s} \cdot V_{DD}$$

Quantization noise

- The fact that the input signal is *quantized* means that noise is added to it
- Quantization noise is less with higher resolution as the input range is divided into a greater number of smaller ranges
- It has a uniform distribution ranging from $-Q/2$ to $+Q/2$
- This error can be considered a quantization noise with **RMS**


➡ Summing the energy

 


$$v_{qn} = \sqrt{\frac{1}{Q} \cdot \int_{-Q/2}^{+Q/2} x^2 dx} = \sqrt{\frac{1}{Q} \cdot \left[\frac{x^3}{3} \right]_{-Q/2}^{+Q/2}}$$

$$v_{qn} = \sqrt{\frac{Q^2}{2^3 \cdot 3} + \frac{Q^2}{2^3 \cdot 3}} = \frac{Q}{\sqrt{12}}$$


Noise issues in tranfert function

 

Ideal tranfert function curve

 


 Tranfert function curve with 1LSB_{PP} transition noise




THE Track "Sample" and Hold

Charge redistribution

 

- + single ended to differential
- + less sensitive to CM error
- + Offset cancelled (differentially)
- Noise (a factor $\sqrt{2}$ more)
- Gain mismatch


Flip Flop

 

- + Mismatch insensitive; gain=1
- + Less noise
- + Offset cancelled (differentially)
- Sensitive to CM fluctuations
- Need full differential inputs

ADC ARCHITECTURES

Flash Converter Sources of Error

 

- Comparator input:
 - Offset
 - Nonlinear input capacitance
 - Kickback noise (disturbs reference)
 - Signal dependent sampling time
- Comparator output:
 - Sparkle codes (... 111101000 ...)
 - Metastability

Pros & Cons about Flash ADC

Flash is fast,



$2^b - 1$ comparators simultaneously sample the input signal

But, for high resolution,

Number of comparators increases exponentially with b

- very large ICs, high power dissipation, difficulty in matching components, and, the increasingly large input capacitance reduces analog input bandwidth
- currently available, $b \leq 8$

Rampe ADC

  



Widely used for CIS:

-inherently simple, scalable to small pitch

However: slow, sensitive to the noise of the common ramp driver and comparator, and the clock jitter while close to the threshold voltage and the noise estimator.

Successive Approximation ADC

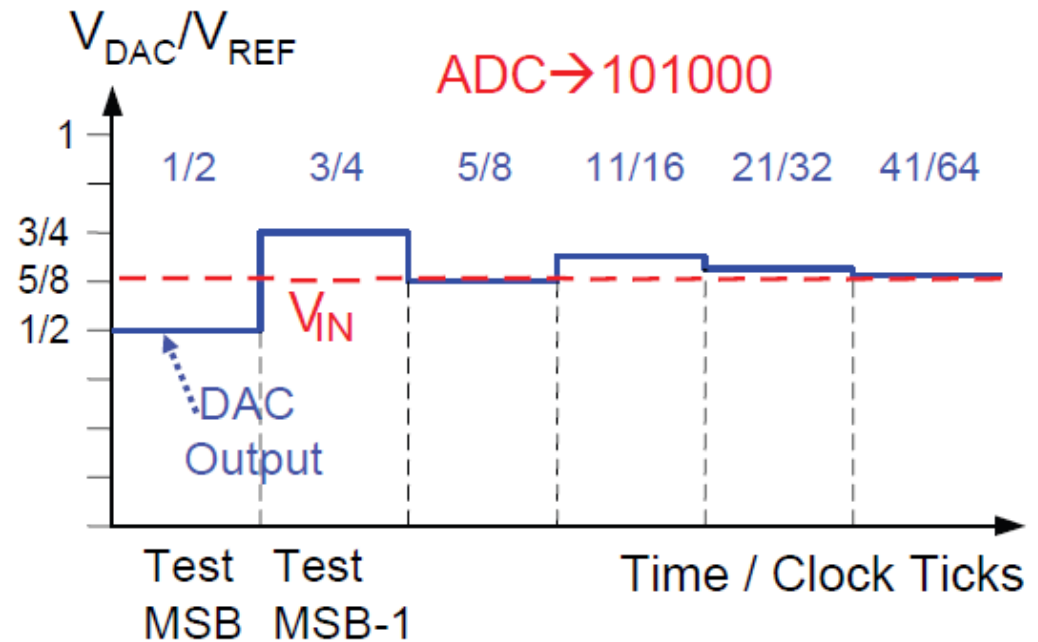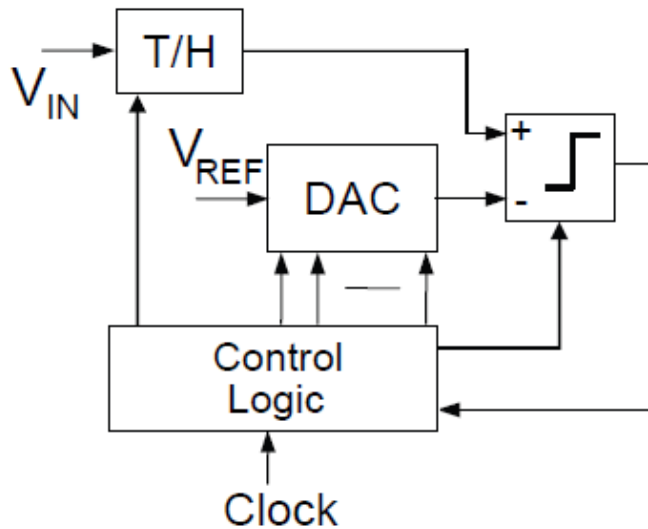
Example: 6-bit ADC & $V_{IN} = 5/8 V_{REF}$




- High accuracy achievable (16+ Bits)
- Required N clock cycles for N-bit conversion (much faster than slope type)

Low power SAR \Rightarrow ADC with sampling capacitors


Binary Weighted Capacitor

 

Segmented-Binary Weighted Capacitors

 


Differential SAR ADC

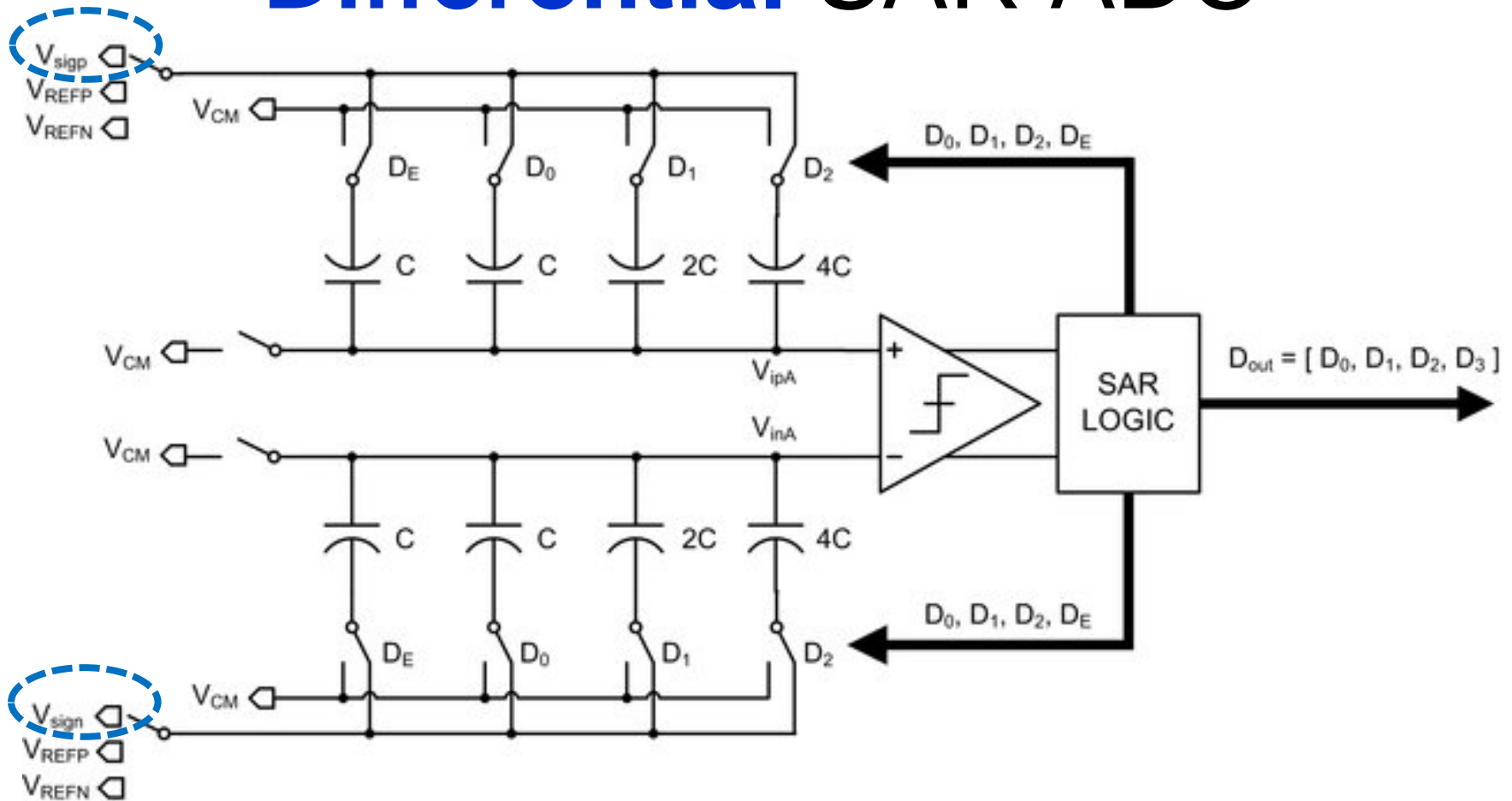

Lead to a better compensation of first order charge parasitics

Sub-ranging ADC

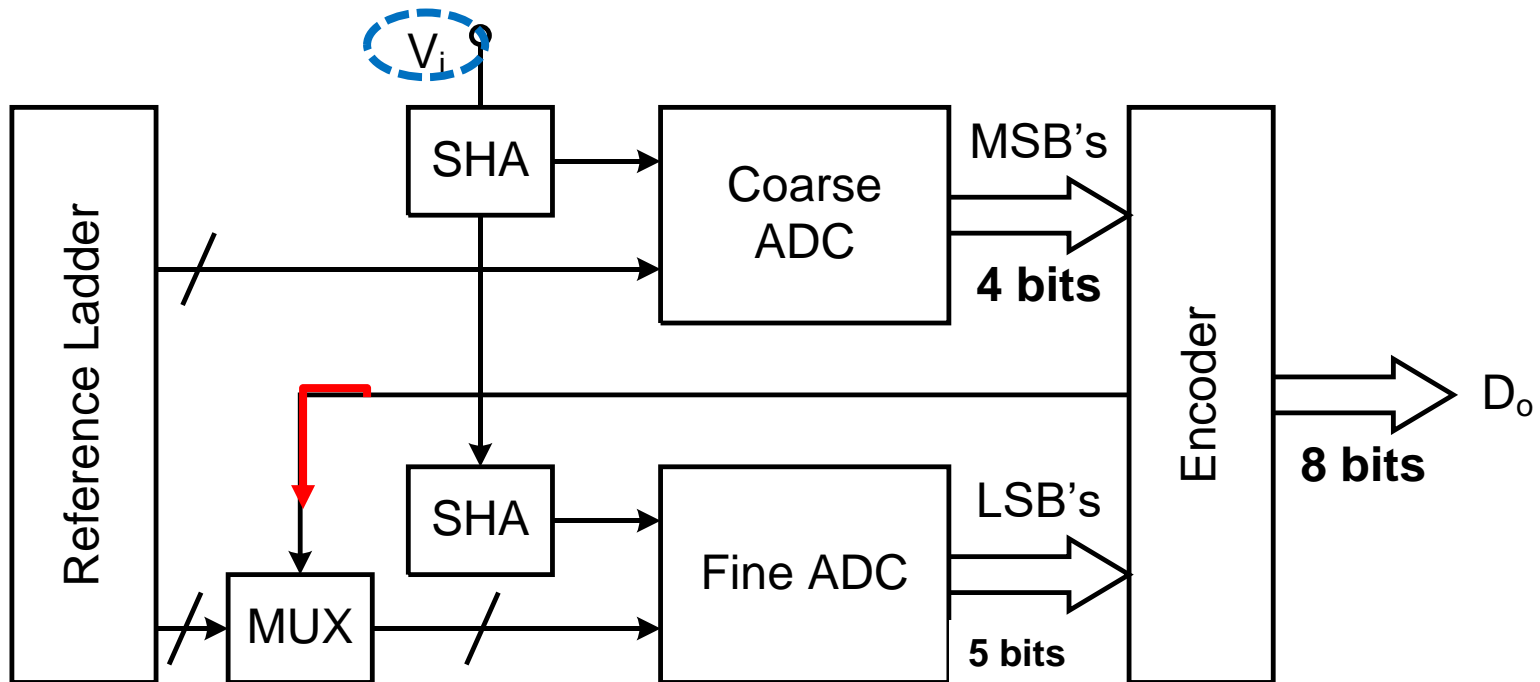
Sub-ranging ADC also **doesn't require OpAmp** and suitable for LV operation. However it requires **high accuracy devices** , for the “fine ADC”.




Pipe line ADC design: the baseline

Very very critical

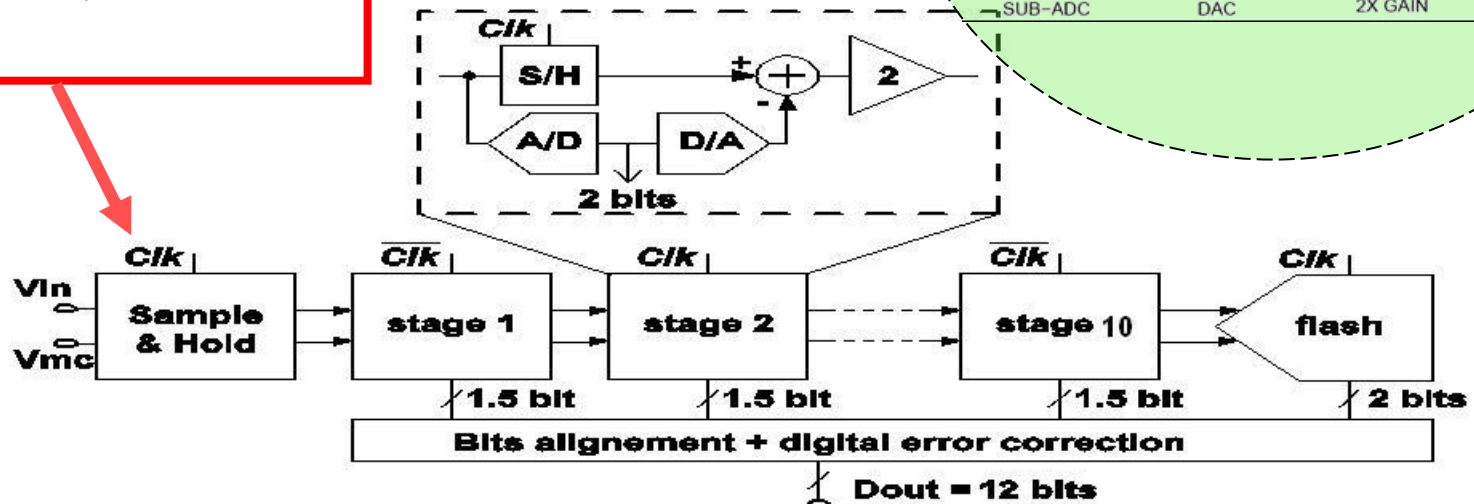Low signal amplification
Offset compensation
CM control
Noise issue, distortion
.....




MDAC Function: Multiplier & DAC

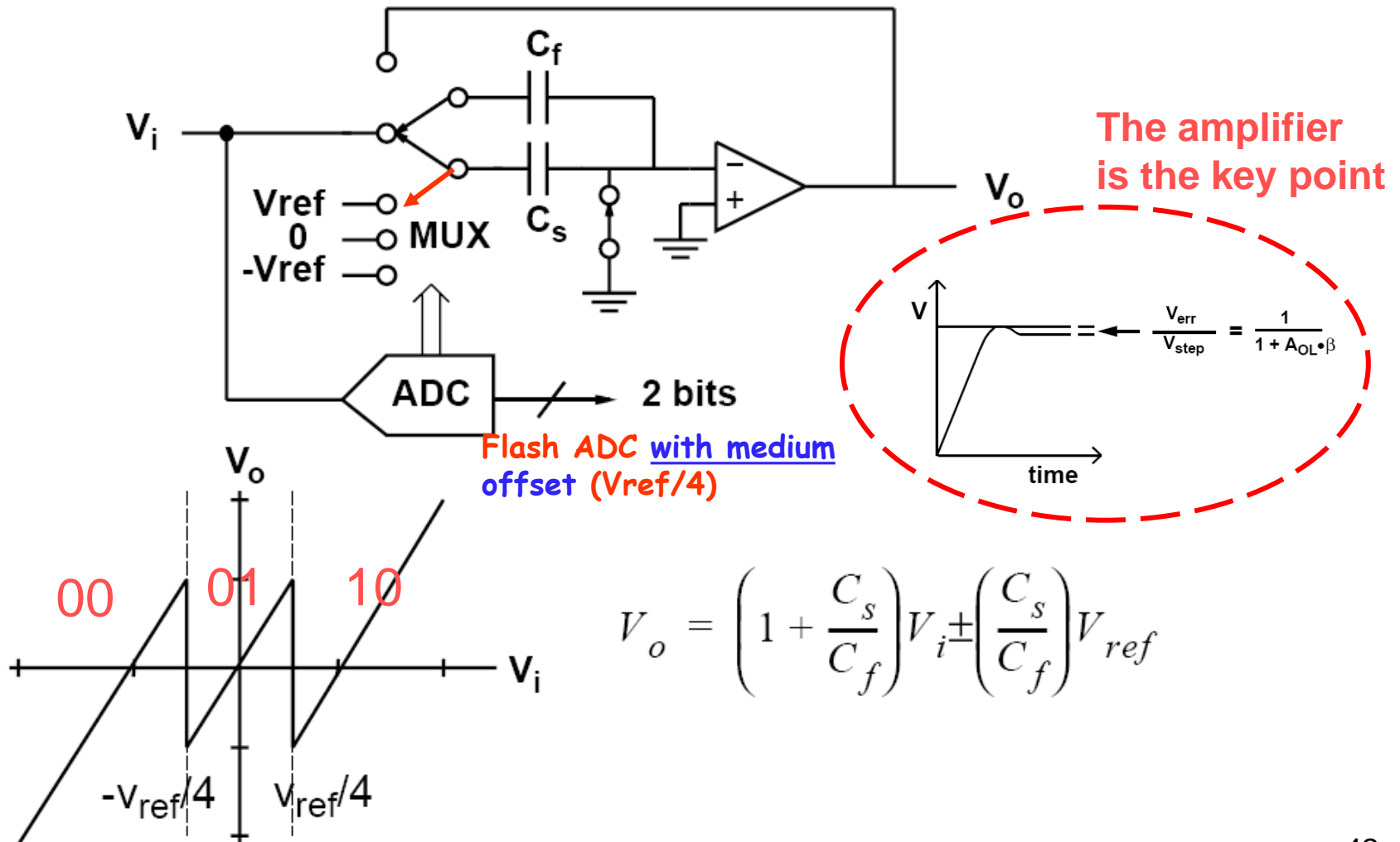

Differential MDAC scheme
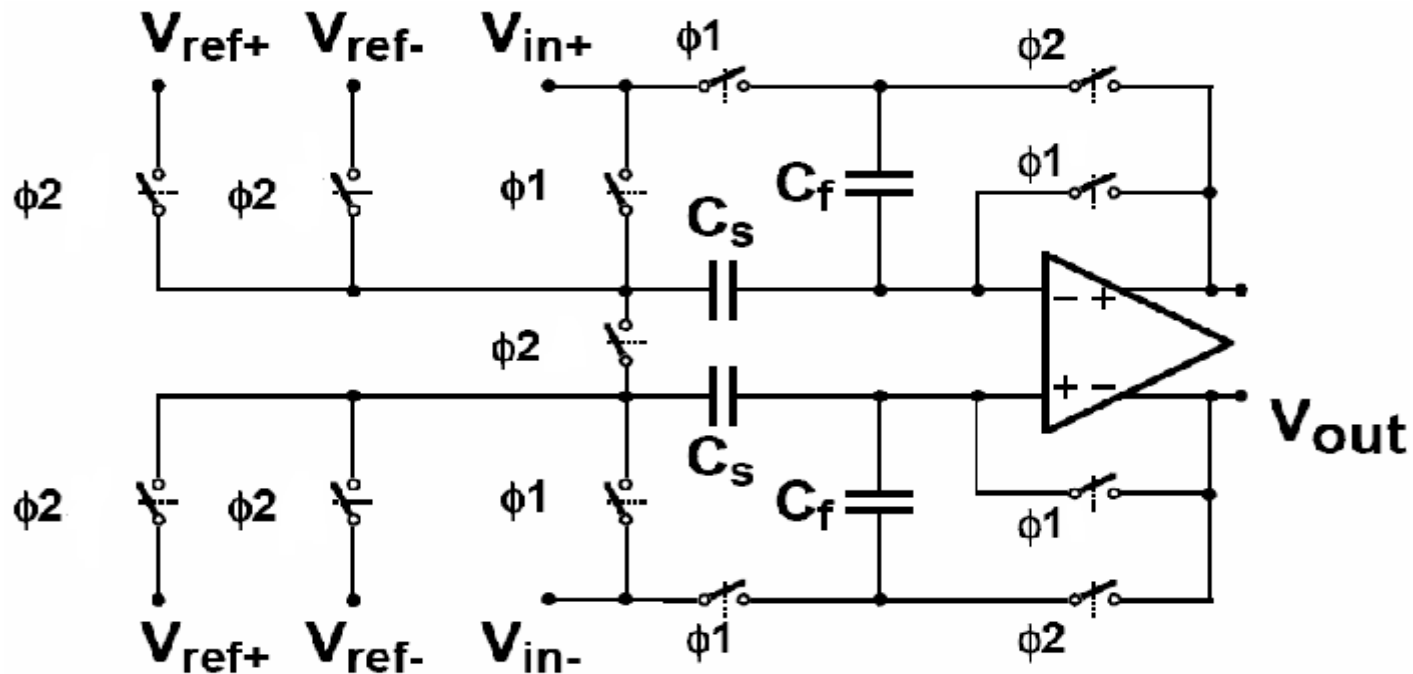
$$V_{out} = 2 * V_{in} \pm \alpha * V_{ref}; \text{ with } \alpha = \pm 1; 0$$



Pipeline ADC Model (1)

– 1.5 bit MDAC stage

– 2.5 bit MDAC stage

Error sources:

Switches linearity


Clock distribution: (Sampling instant + Jitter)

Gain

OTA: A_{dB}


MDAC gain (capacitors)

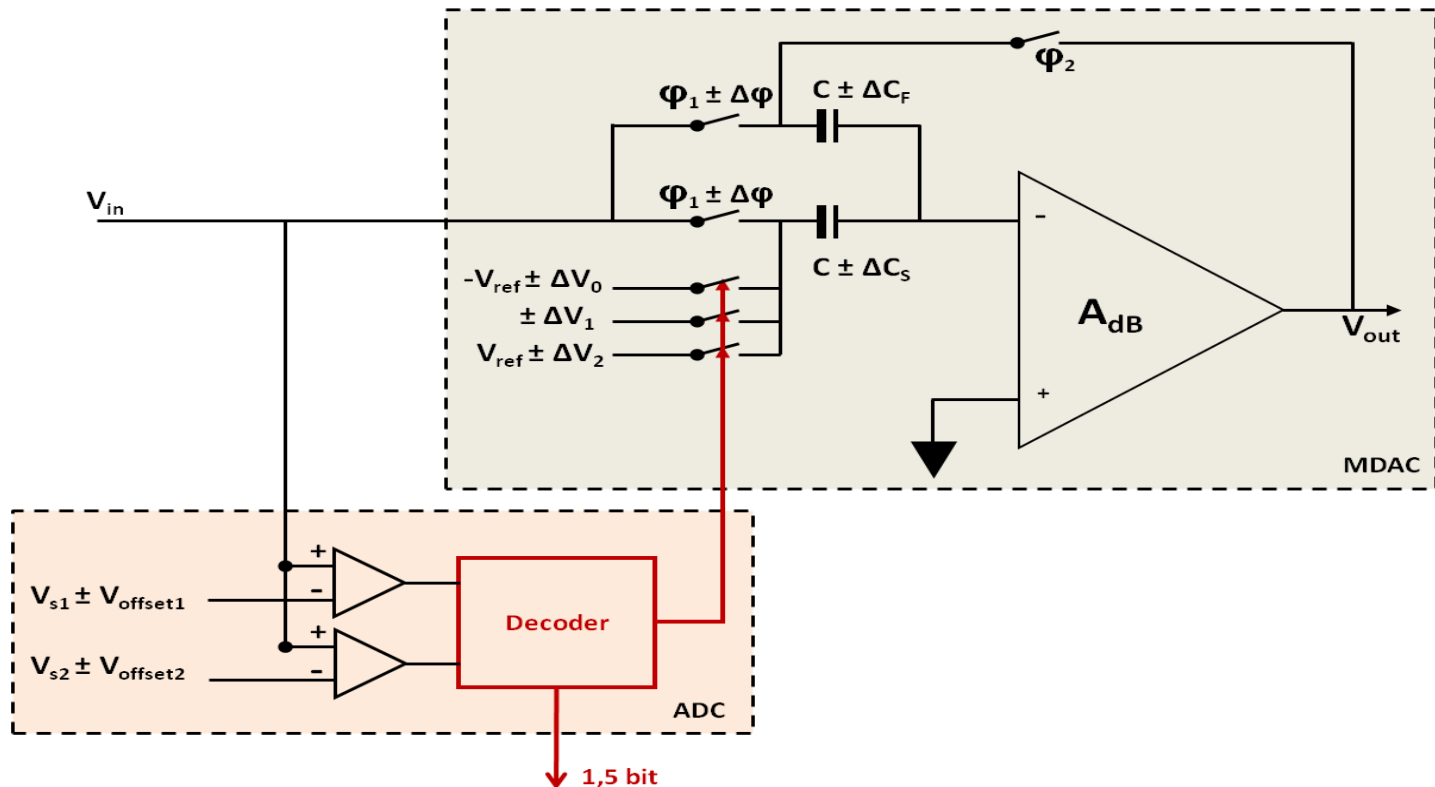Reference voltages ($\pm V_{ref}$): drift & noise



MDAC Transfer function

 
- 1.5 bit MDAC $V_{out} = 2 \cdot V_{in} - D_i \cdot V_{ref}$



$$D_i = [0, \pm 1]$$

$$V_{out} = 4 \cdot V_{in} - K_i \cdot V_{ref}$$

- 2.5 bit MDAC

 


$$K_i = [0, \pm 1, \pm 2, \pm 3]$$


Pipelined ADC

- OTA Open loop gain issues
 
$$V_{out} = (2 \cdot V_{in} - D_i \cdot V_{ref}) \cdot \frac{1}{1 + \frac{1}{A_0 \cdot F_{fb}}} \quad \text{with, } F_{fb} = \frac{C_f}{C_f + C_s + C_{in}}$$




Fundamentals in Sigma Delta Modulators

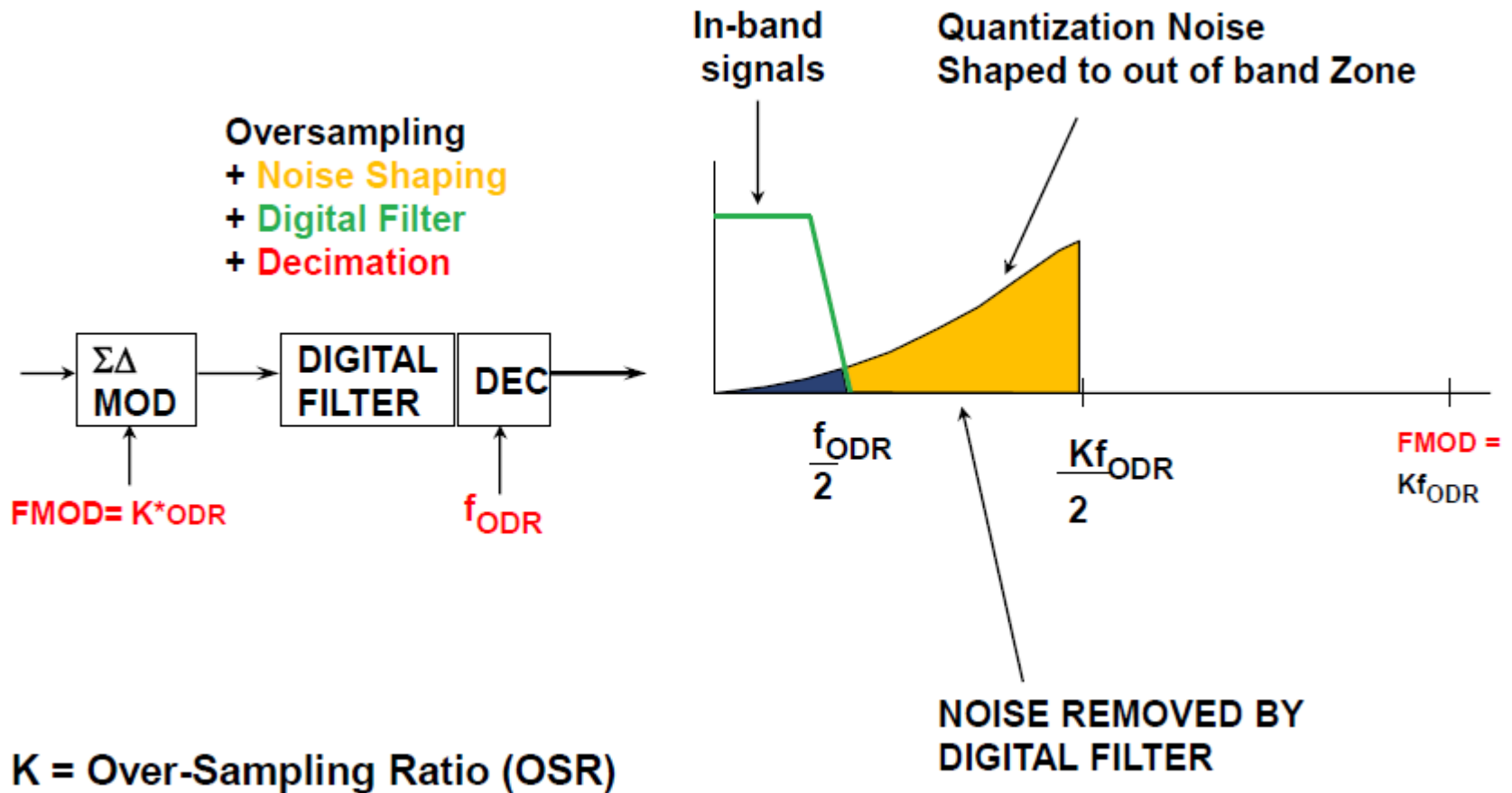

Oversampling ADC: Sigma delta modulator

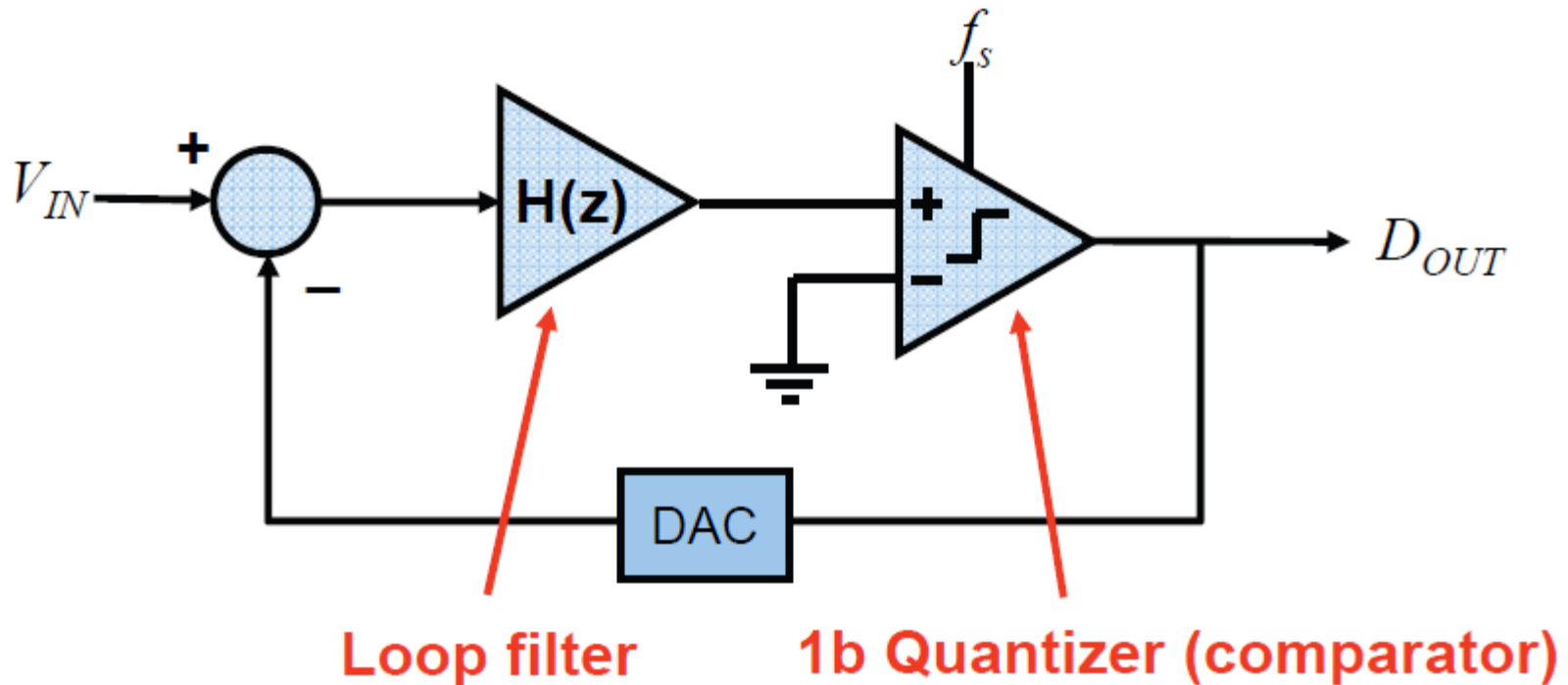Analog 1-Bit $\Sigma\Delta$ modulators convert a continuous time analog input v_{IN} into a 1-Bit sequence D_{OUT}



Transfer Function: **signal** & **bruit**

In the simplest cases:



Loop filter response $H(f)$ is low pass:

- Very high gain at low frequency.

Usually,

The filter is a simple integrator or a cascade of integrators.

  Note: noise is 'shaped' by the $1/[1 + H(f)]$ function.



Input Transfer Function

$$H(f)/[1 + H(f)]$$


Noise Transfer Function

$$1/[1 + H(f)]$$

Noise Shaped



Sigma Delta Modulator

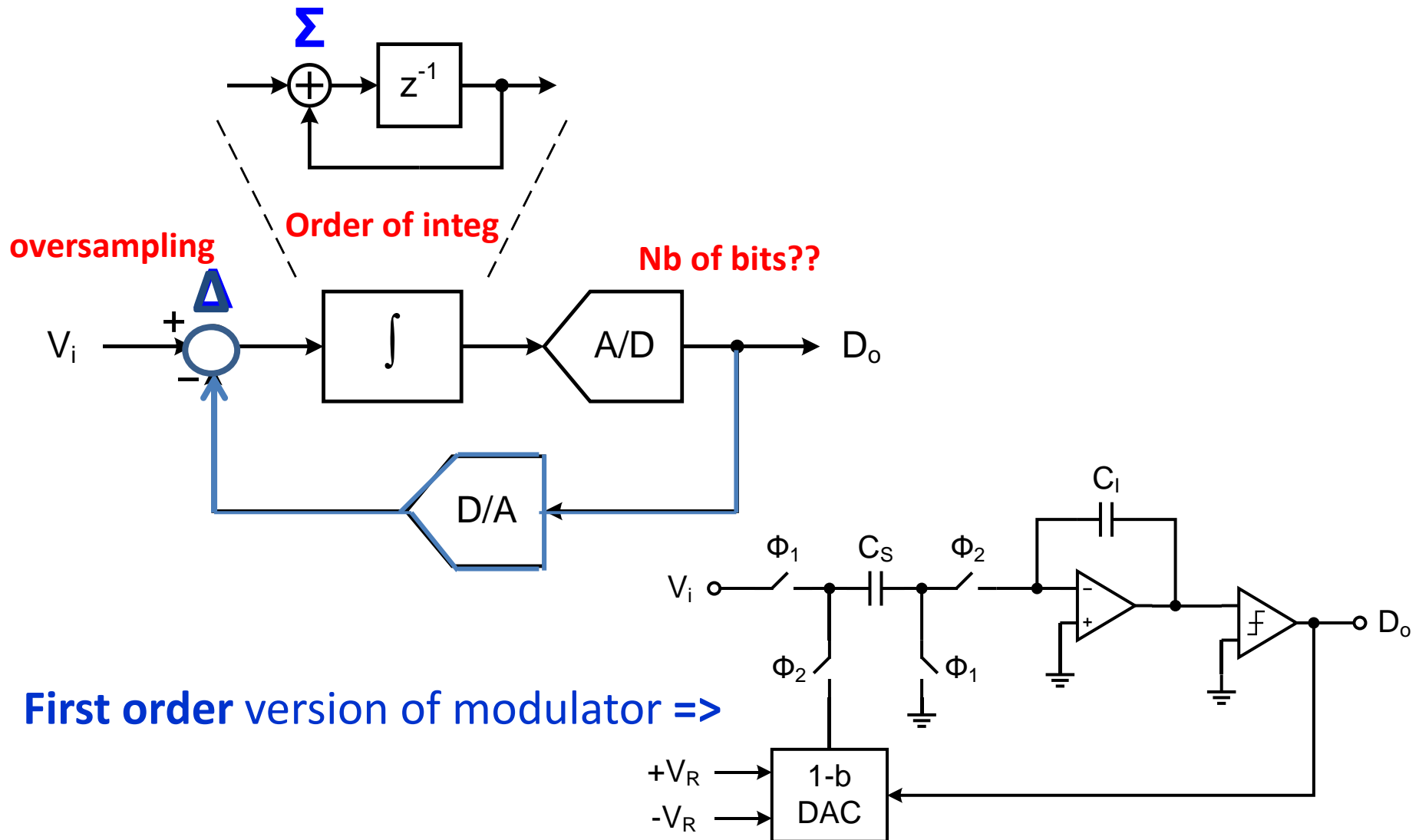


First order version of modulator =>

3D IT simplify view for SPECT-Xray CT

What we expect !

Large surface FOV=20x20 cm²

Megapixel Sensor

 

- ✓ Direct γ conversion CdZnTe/CdTe...
- ✓ 1-10 Megapixels – Pitch < 50 μm

- ✓ Amplifier
- ✓ Discriminator: two thresholds for “energy selection” or windowing for two simultaneous tracer imaging

- ✓ Fast readout-Photon counting strategy : $\sim 10^6$ ph/pixel/s for X-ray; Medipix or XPAD3 like architecture
- ✓ Time stamping

- ✓ Gating capability for X-ray and
- ✓ Fast readout for dynamical imaging (cardiac movements)

Thanks !!