

# Introduction to Field Programmable Gate Arrays

Lecture 3/3

CERN Accelerator School on Digital Signal Processing  
Sigtuna, Sweden, 31 May – 9 June 2007  
Javier Serrano, CERN AB-CO-HT

# Outline




- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - Interfacing to the outside world.
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# Outline




- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - Interfacing to the outside world.
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# Reminder: basic digital design

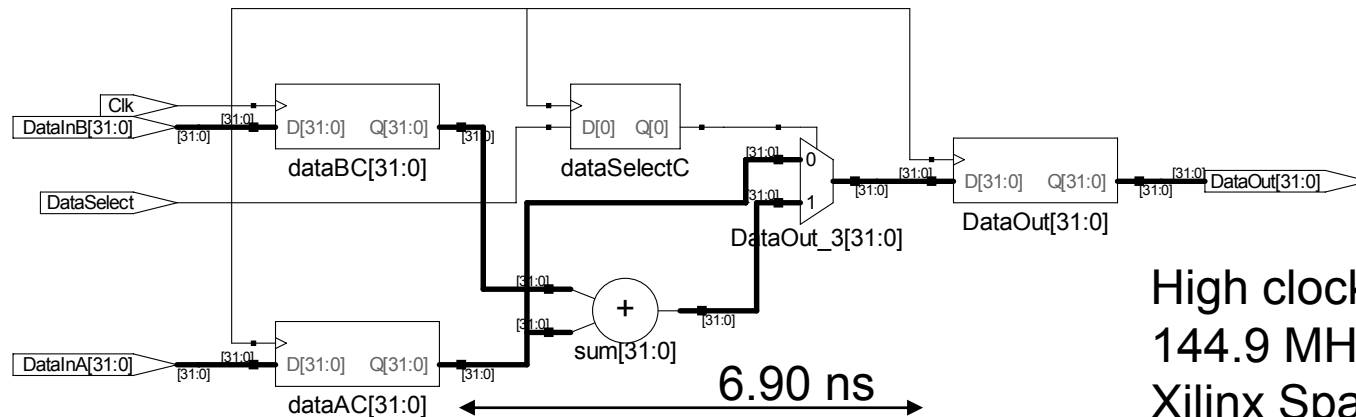

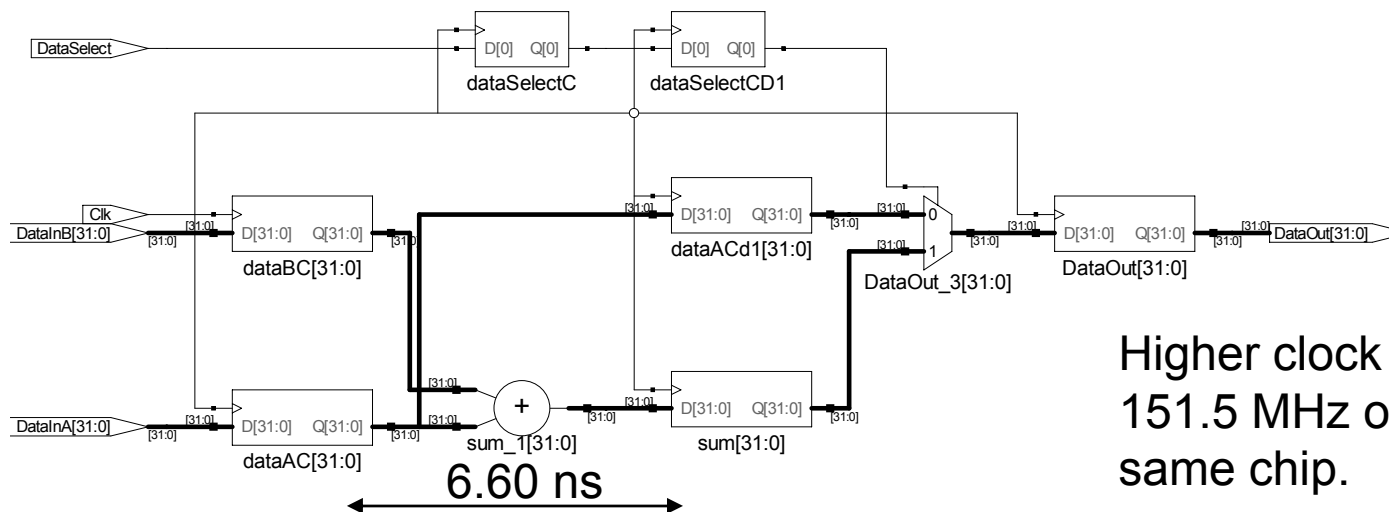
High clock rate:  
144.9 MHz on a  
Xilinx Spartan IIE.





Higher clock rate:  
151.5 MHz on the  
same chip.
 
# Buffering


- Delay in modern designs can be as much as 90% routing, 10% logic. Routing delay is due to long nets + capacitive input loading.
- Buffering is done automatically by most synthesis tools and reduces the fan out on affected nets:



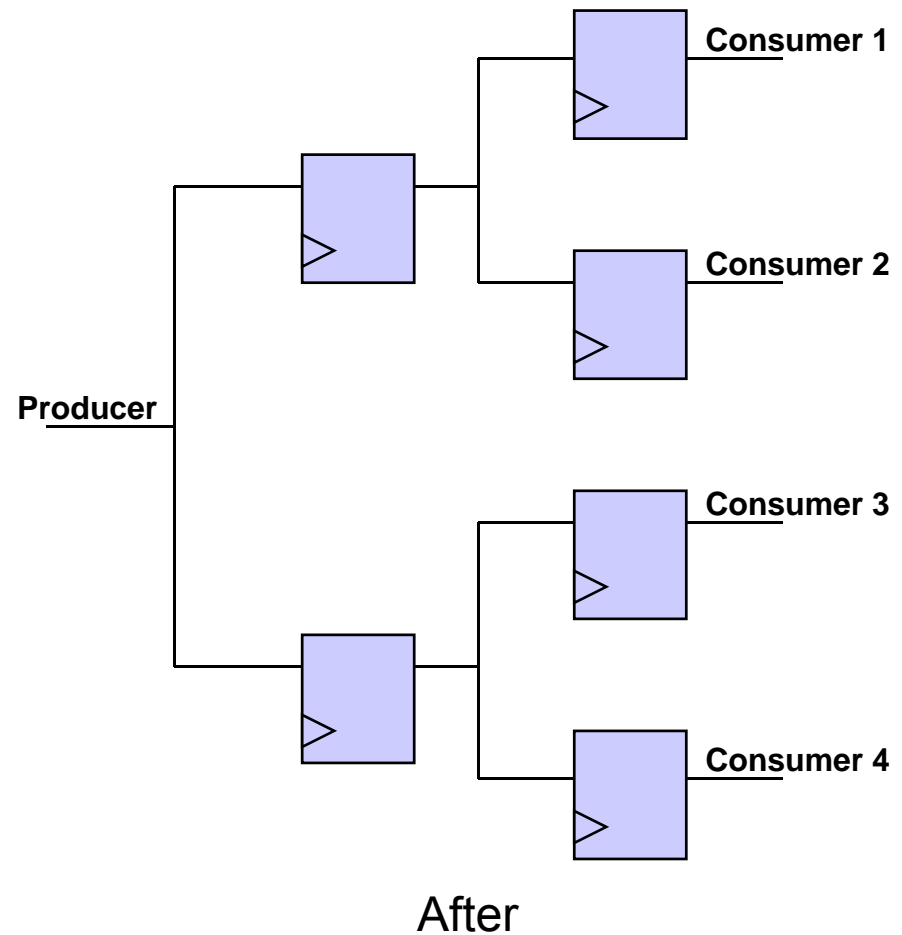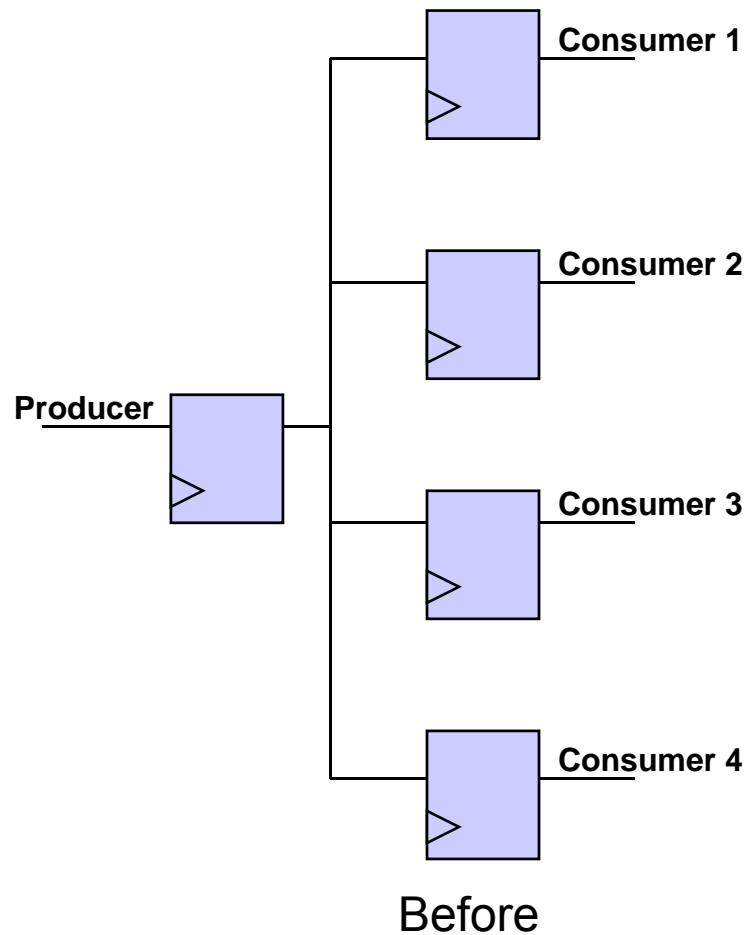
# Replicating registers (and associated logic if necessary)



# Retiming (a.k.a. register balancing)

 


Before

 

After

# Pipelining

 


Before



After




# Time multiplexing

 

# An example: boosting the performance of an IIR filter (1/2)

Simple first order IIR:  $y[n+1] = ay[n] + b x[n]$

 Problem found in the phase filter of a PLL used to track bunch frequency in CERN's PS




Performance bottleneck in the feedback path

# An example: boosting the performance of an IIR filter (2/2)

Look ahead scheme:


From  $y[n+1] = ay[n] + b x[n]$  we get
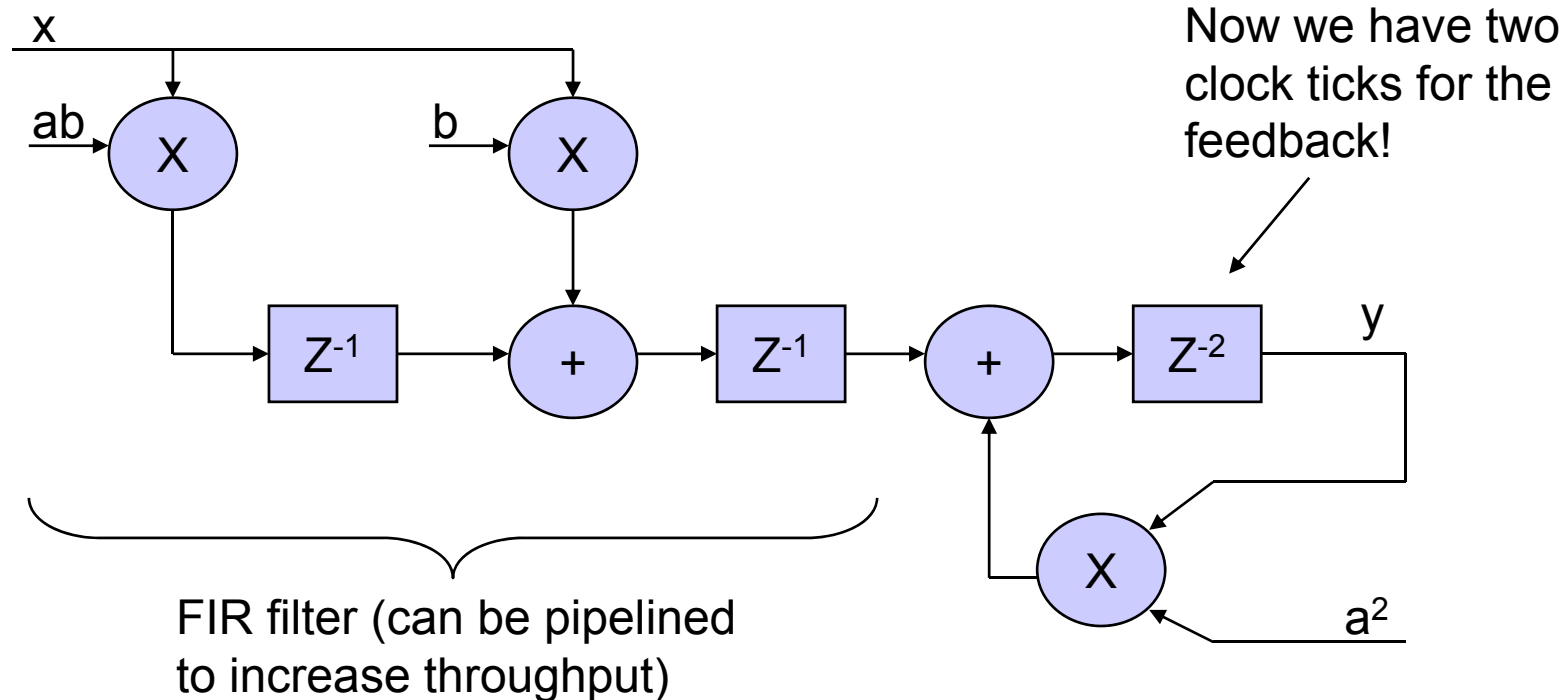
$$y[n+2] = ay[n+1] + bx[n+1] = a^2y[n] + abx[n] + bx[n+1]$$



# Another example: being smart about what you need exactly.

- $u \times v = u_x v_y - u_y v_x$
- $|u \times v| = |u| \times |v| \sin\theta = \varepsilon \text{ IcFwd}$
- $u = V_{\text{acc}}, v = \text{IcFwd}$

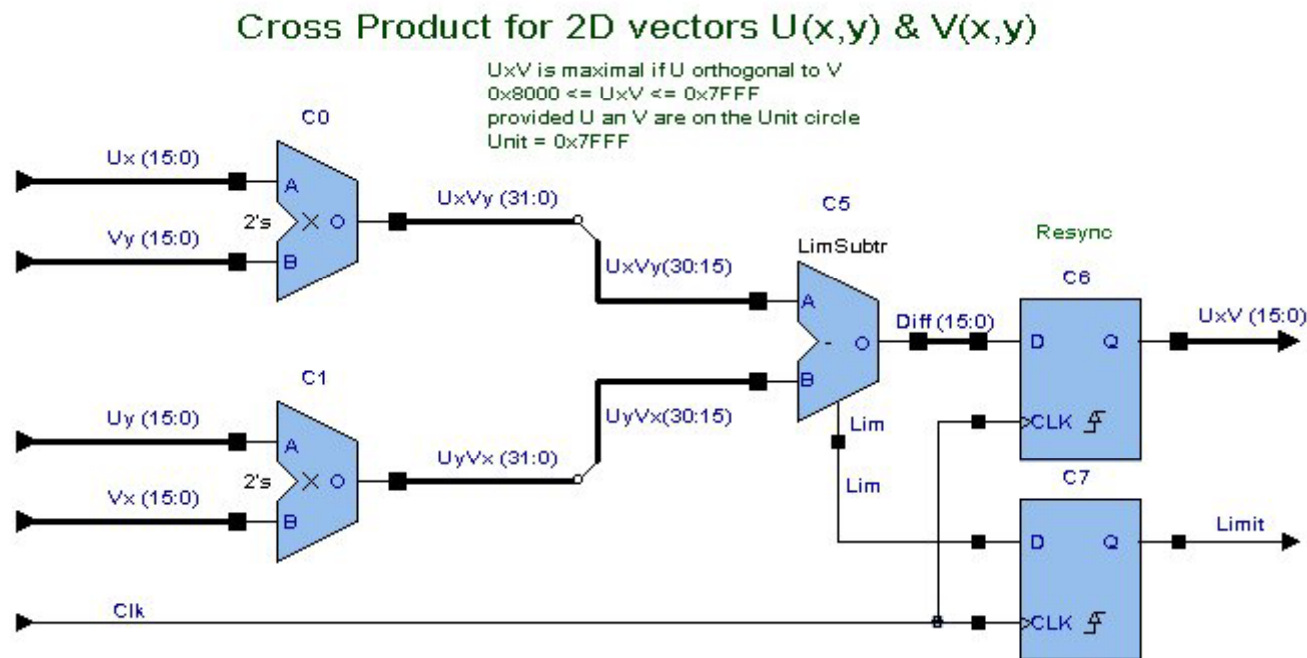

Cross product used as phase discriminator by John Molendijk in the LHC LLRF.

# Outline



- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - Interfacing to the outside world.
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# Floating point designs




- To work in floating point you (potentially) need blocks to:
  - Convert from fixed point to floating point and back.
  - Convert between different floating point types.
  - Multiply.
  - Add/subtract (involves an intermediate representation with same exponent for both operands).
  - Divide.
  - Square root.
  - Compare 2 numbers.
- The main FPGA companies provide these in the form of IP cores. You can also roll your own.

# Format

Bit significance (i)

Bit position

 

s: sign.

e: exponent.

f: fractional part ( $b_0.b_1b_2b_3b_4\dots b_{w_f-1}$ )

Convention: normalized numbers have  $b_0=1$

Exponent value:  $E = e - (2^{w_e-1} - 1)$

$$e = \sum_{i=0}^{w_e-1} e_i 2^i$$

Total value:  $v = (-1)^s 2^E b_0.b_1b_2\dots b_{w_f-1}$

IEEE-754 standard single format: 24-bit fraction and 8-bit exponent ( $w=32$  and  $w_f=24$  in the figure).

IEEE-754 standard double format: 53-bit fraction and 11-bit exponent.

# Some performance figures (single precision)

Table 26: Characterization of Single-Precision Format on Virtex-5 FPGA

Operation	Resources				Maximum Frequency (MHz) <sup>1</sup>
	Embedded		Fabric		Virtex-5
	Type	Number	LUTs	FFs	-1
Multiply	DSP48E (max usage)	3	88	177	450
	DSP48E (full usage)	2	126	209	429
	DSP48E (medium usage)	1	294	390	375
	Logic	0	641	698	357
Add/Subtract	DSP48E (speed optimized, full usage)	2	267	375	410
	Logic (speed optimized, no usage)	0	429	561	395
	Logic (low latency)	0	536	625	372
Fixed to float	Int32 input		131	226	398
Float to fixed	Int32 result		218	237	373
Float to float	Single to double		44	101	466
Compare	Programmable		80	24	393
Divide	C_RATE=1		738	1,370	365
	C_RATE=26		227	233	316
Sqrt	C_RATE=1		542	787	398
	C_RATE=25		175	204	388

1. Maximum frequency obtained with map switches -ol high and -cm speed, and par switches -pi high and -rl high.




# Some performance figures (double precision)

Table 29: Characterization of Double-Precision Format on Virtex-5 FPGA

Operation	Resources				Maximum Frequency (MHz) <sup>1</sup>
	Embedded		Fabric		Virtex-5
	Type	Number	LUTs	FFs	-1
Multiply	DSP48E (max usage)	13	416	654	431
	DSP48E (full usage)	12	424	669	369
	Logic	0	2,309	2,457	237
Add/Subtract	DSP48E (speed optimized, full usage)	3	821	976	356
	Logic (speed optimized, no usage)	0	804	1,060	316
	Logic (low latency, no usage)	0	1,045	1,185	291
Fixed to float	Int64 input		402	504	306
Float to fixed	Int64 result		396	446	297
Float to Float	Double to single		107	131	438
Compare	Programmable		142	24	346
Divide	C_RATE=1		3,228	6,002	254
	C_RATE=26		354	399	252
Sqrt	C_RATE=1		1,940	3,234	284
	C_RATE=25		355	391	278

1. Maximum frequency obtained with map switches -ol high and -cm speed, and par switches -pl high and -rl high.


# Rolling your own. Example:

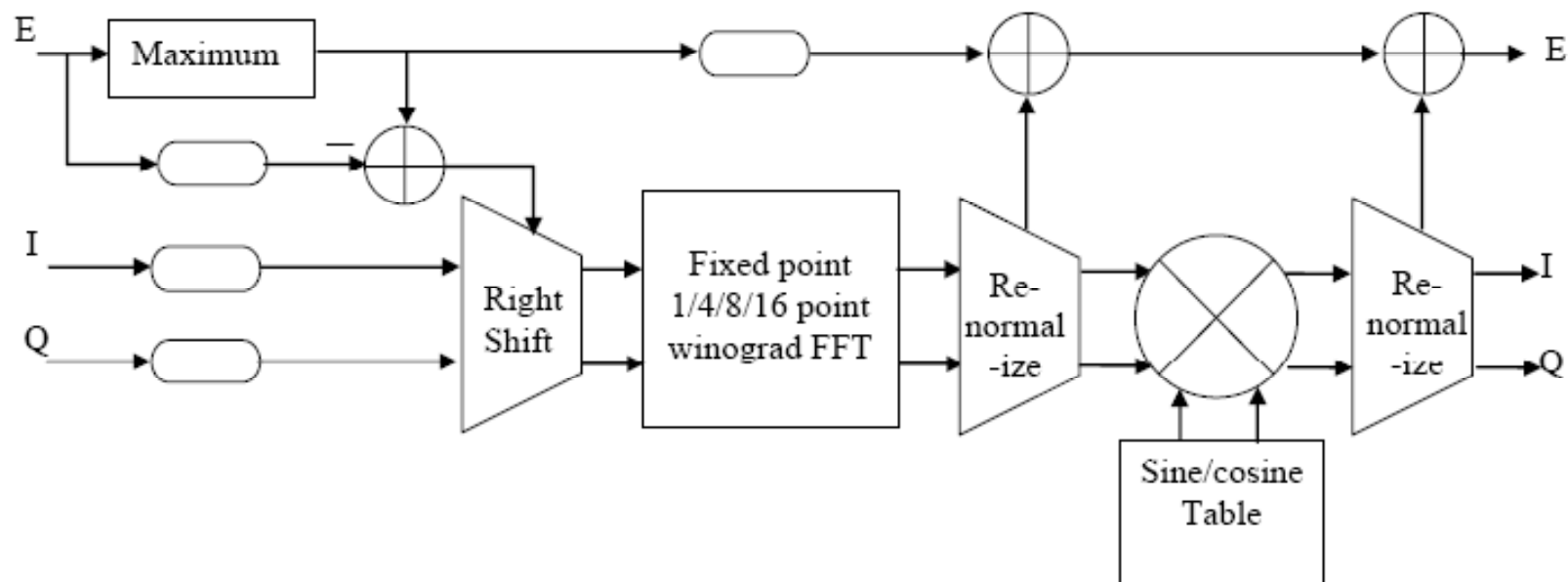

Ray Andraka, "Hybrid Floating Point Technique Yields 1.2 Gigasample Per Second 32 to 2048 point Floating Point FFT in a single FPGA."

<http://www.andraka.com/files/HPEC2006.pdf>
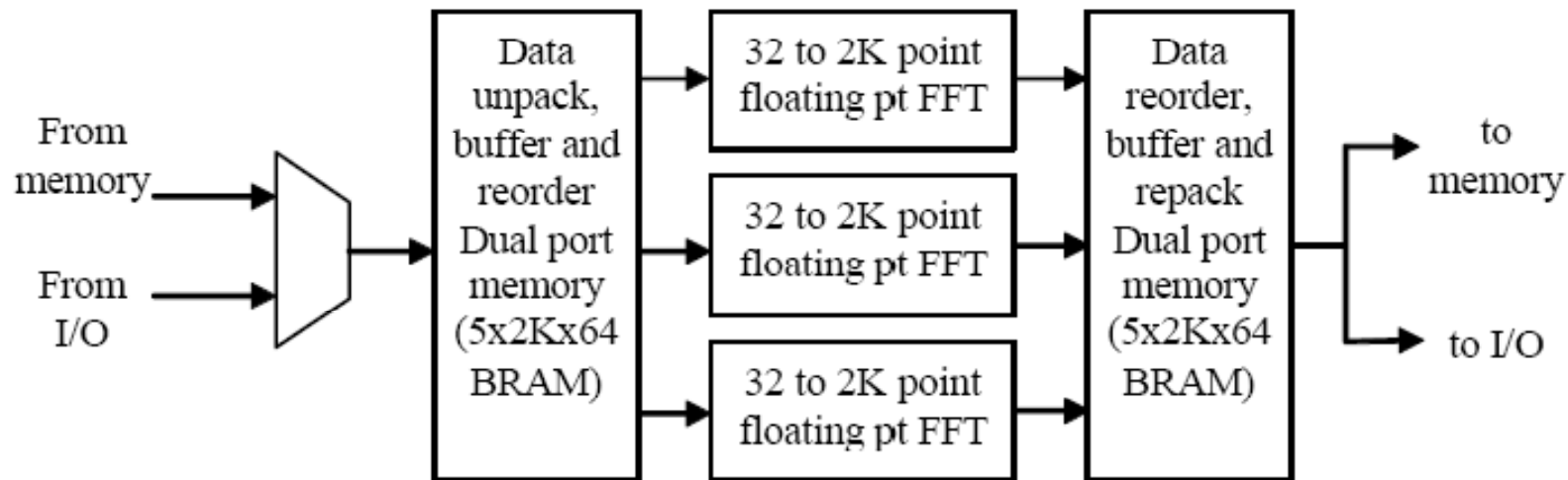
# Put three of these together and triplicate throughput!



Limited by DSP48 max. clock rate in Virtex 4 XCV4SX55-10: 400 MHz.  
Total throughput: 1.2 Gs/s



# Outline

- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - **Powering FPGAs.**
  - Interfacing to the outside world.
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# FPGA power requirements (1/2)


- Voltage: different voltage rails: core, I/Os, AUX, SERDES, PLL...
- Tolerance: typically +/- 5%.
- Monotonicity: Vcc must rise steadily from GND to desired value (could work otherwise but FPGAs are not tested that way).

# FPGA power requirements (2/2)

- Power-on current. Watch out for PCB capacitor in-rush current:  $I_c = C \cdot \Delta V / \Delta T$ . Slow down voltage ramp if needed.
- Sequencing: required for old technologies and recommended for new ones. Read datasheet. Example for Virtex-4/5: VCCINT → VCCAUX → VCCO. Use Supply Voltage Supervisor (SVS) to control sequencing.
- Power-on ramp time. Devices specify a minimum and a maximum ramp time. Again, this is how they are tested.


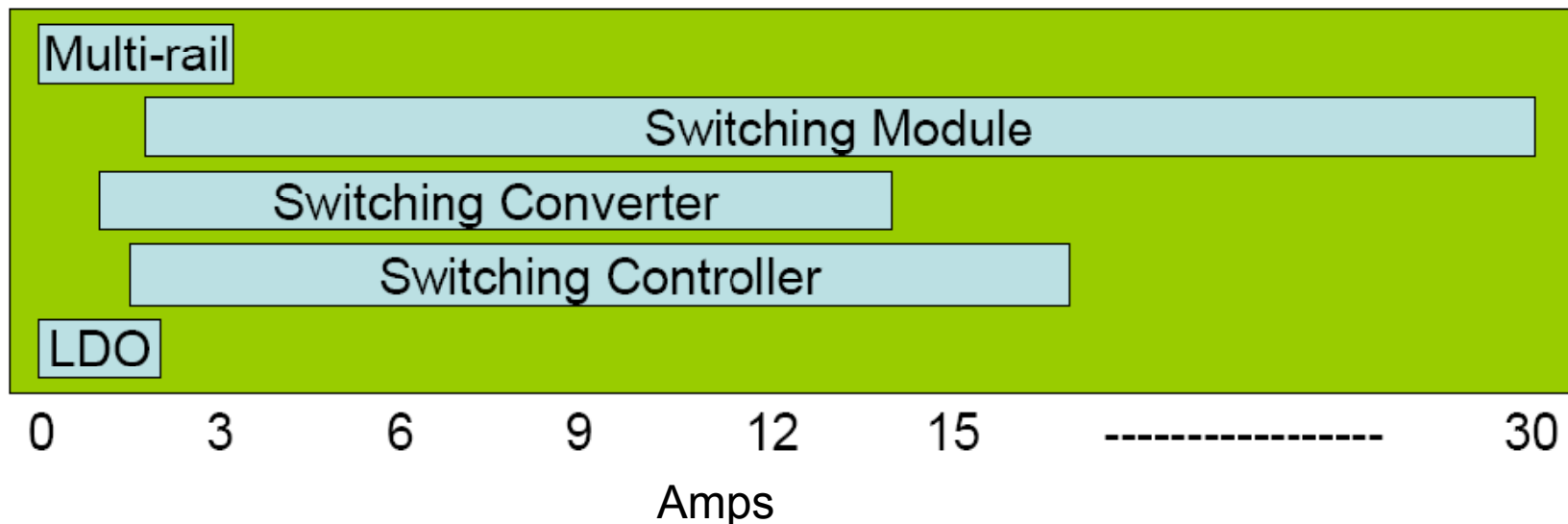
# Power solutions

- Low Drop-Out (LDO). Linear. Unbeatable for quietness. Inefficient.
- Switching solutions (some have external clk pins that you can drive at a frequency you can easily filter afterwards)
  - Controller (external FET)
  - Converter (built-in FET)
  - Module
- Multi-rail solutions



# LDO: Be aware - Under-voltage lockout

  - Problem: LDO with non-monotonic voltage output.
- Cause:
  - 5V primary supply was powering on at the same time.
  - Caps and 3 LDOs caused the 5V to droop.
- Result:
  - Primary 5V current-limiter shut it down.
  - LDO's under-voltage lockout tripped, shutting down the LDO.
- How can we fix this?




18 Jul 2003  
13:16:10



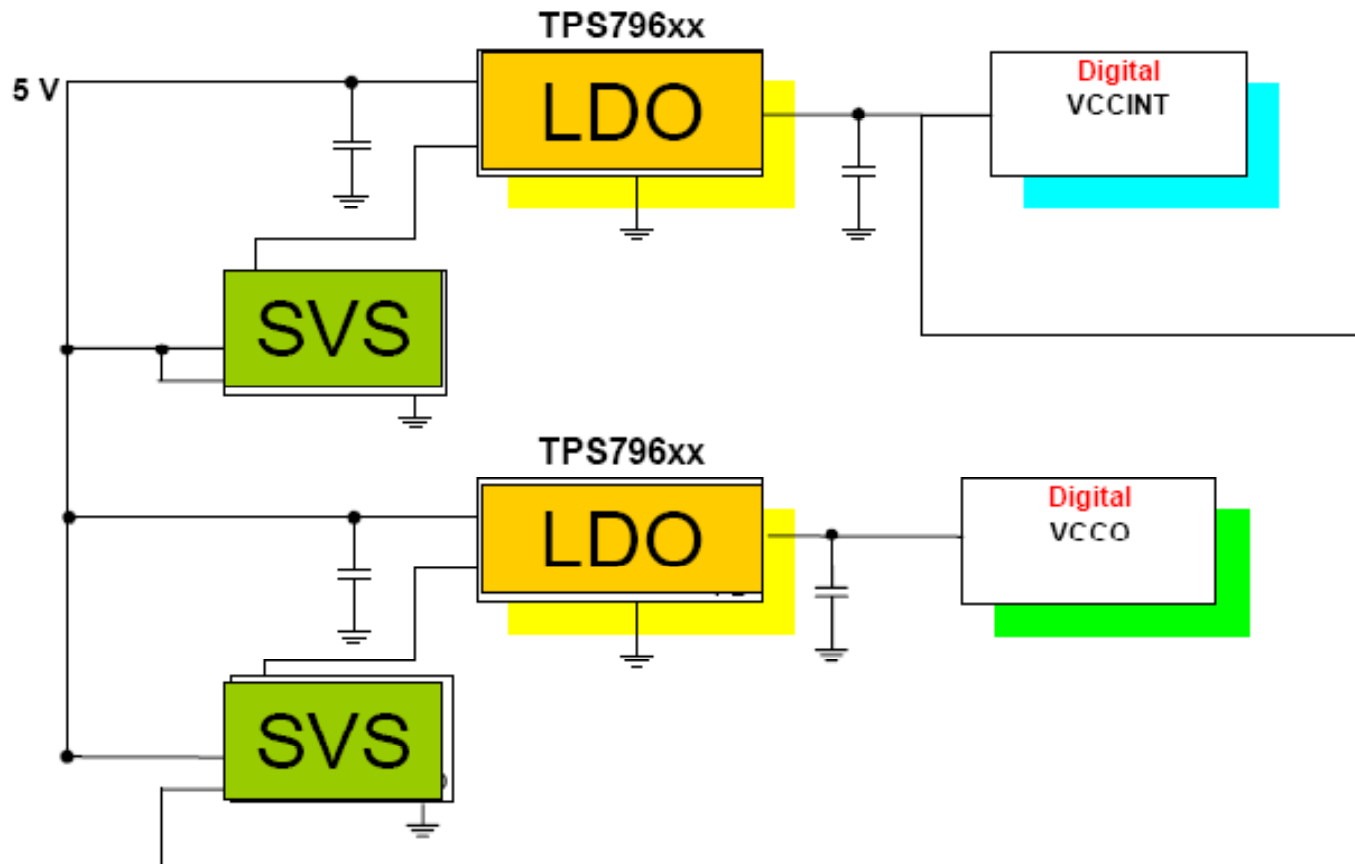
# LDO: under-voltage lockout solution

- Use SVS to sequence regulators after caps are charged.




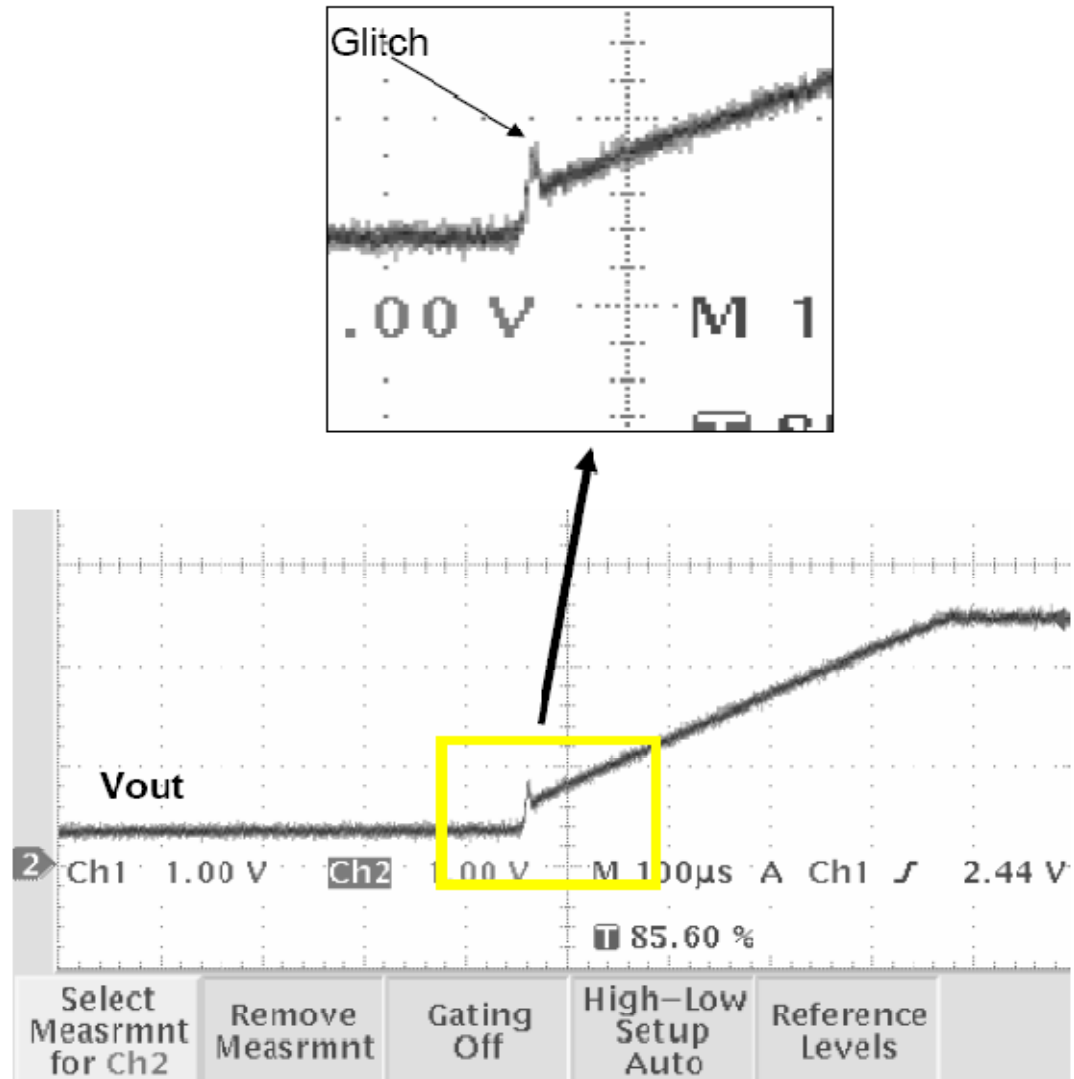
# LDO: be aware – in-rush and current limit

- A fast-starting LDO induces a huge in-rush current from charging capacitors (remember  $I_c = C \cdot \Delta V / \Delta T$ )
- LDO enters current-limit mode due to capacitor in-rush.
- The transition to current-limit mode causes a glitch.
- What to do?


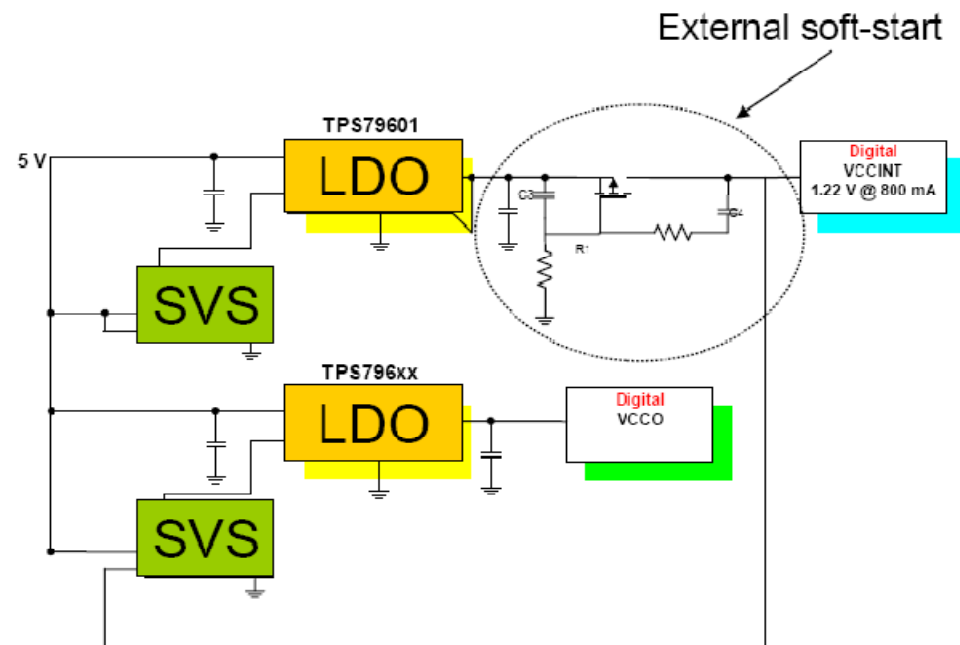 
# LDO: in-rush and current-limit solution


- Slow down the ramp time using a soft-start circuit.
  - Reduces  $\Delta V/\Delta t$  which reduces capacitor in-rush current.
  - Regulator never hits current-limit and stays in voltage mode.
  - Good for meeting FPGA minimum ramp time specs.
  - External or built-in.



Note: in-rush FPGA current during configuration is a thing of the past thanks to the introduction of proper housekeeping circuitry.

How much current is our design consuming

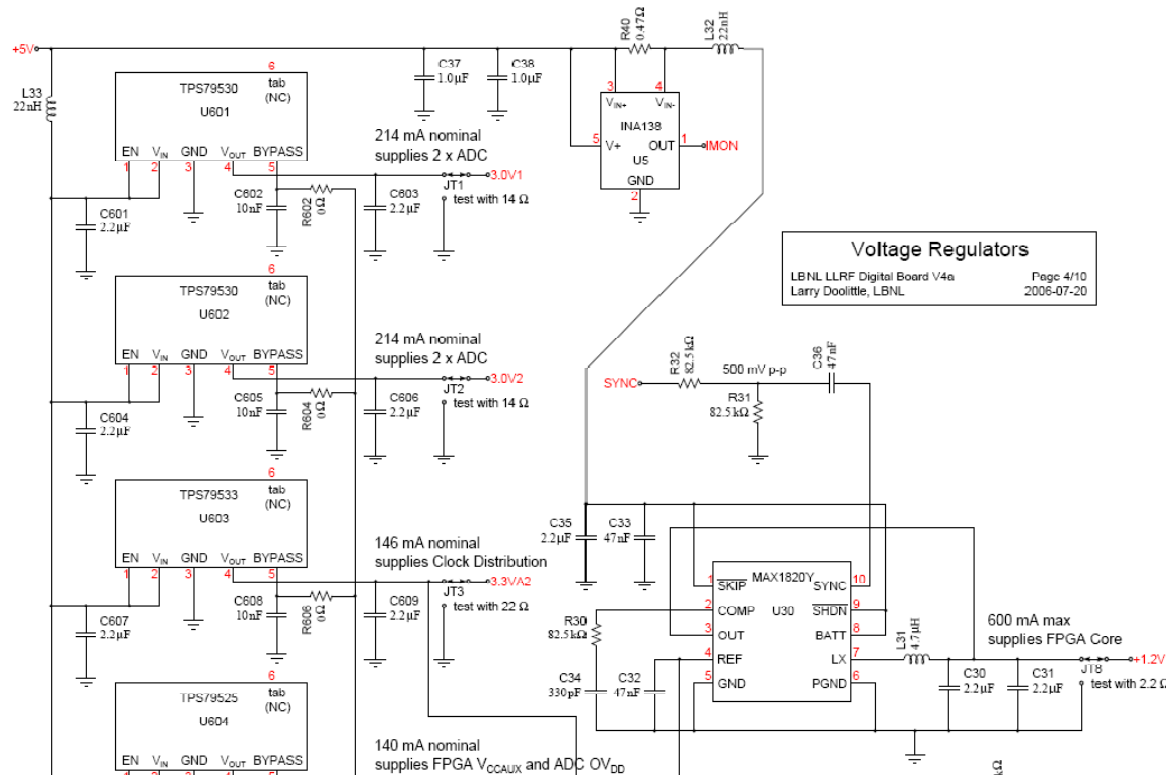
- Insert a small high-precision resistor in series with primary voltage source *before* the regulator, and measure the voltage drop with a differential amplifier. Below an example from a LLRF board designed by Larry Doolittle (LBNL).



- Then compare with the predicted power consumption from your vendor's software tool ;)

 
# Decoupling capacitors

- Capacitors are not ideal! They have parasitic resistance and inductance:


 
# Decoupling capacitors

- Knee frequency in the spectrum of a digital data stream is related by the rise and fall times ( $T_r$ ) by:  $F_{\text{knee}} = 0.5/T_r$  (1).
- We want our Power Distribution System to have low impedance at all frequencies of interest → low voltage variations for arbitrary current demands.
- Solution: parallel combination of different capacitor values. For more info: Xilinx XAPP623.



Quantity	Symbol	Package	Capacitive Values (μF)	Parasitic Inductance (nH)	Parasitic Resistance (ohms)
2	❖	E	680	2.8	0.57
7	⤿	0805	2.2	2.0	0.02
13	◆	0603	0.22	1.8	0.06
26	■	0402	0.022	1.5	0.20

(1) Howard W. Johnson, Martin Graham. High Speed Digital Design, A Handbook of Black Magic. Prentice Hall, 1993.


# Outline



- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - **Interfacing to the outside world.**
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# FPGAs have very versatile connectivity.

## Example: Xilinx Spartan 3 family.

 

- Single ended and differential.
  - 784 single-ended, 344 differential pairs.
  - 622 Mb/sec LVDS.
  - 24 I/O standards, 8 flexible I/O banks.
  - PCI 32/33 and 64/33 support.
  - Eliminate costly bus transceivers.
- 3.3V, 2.5V, 1.8V, 1.5V, 1.2V

Chip-to-Chip Interfacing:

LVDS

LVC MOS

LV TTL

Backplane Interfacing:

GTL

GTL+

PCI

BLVDS

High-speed Memory Interfacing:

HSTL

SSTL




# Interfacing with ADCs and DACs


- Large parallel busses working at high clock rates → potential for timing and noise problems.
- Possible solutions:
  - ADCs nowadays have analog bandwidths well above twice their maximum sampling rate → sample band pass signals at slower rates (in other Nyquist zones).
  - Use high speed differential serial links for ADCs and DACs (so far, no embedded clock: clk + data on two separate LVDS links).
  - Run digital supply in parallel ADCs as low as possible: 2.0-2.5V feasible.
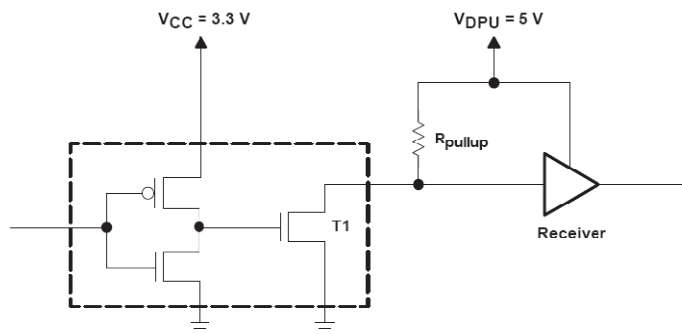
# Interfacing with busses using 5V signaling (e.g. VME)

- Dual supply level translators are the most flexible solution.
- Alternatives:
  - 5V compliant 3.3V buffers exist, such as the LVTH family. They also provide more current than standard FPGA I/Os.
  - Open-drain devices (uni-directional, can do wired-or).
  - FET switches (very fast, no active drive).



Open-drain 3.3V  $\rightarrow$  5V

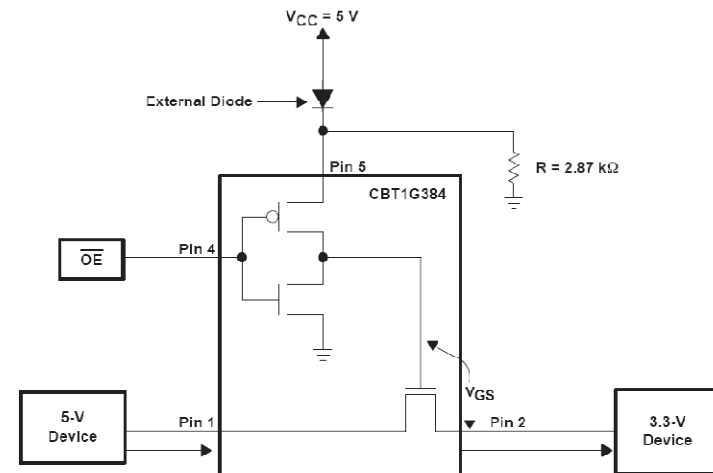



FET-based 5V  $\rightarrow$  3.3V

# Outline



- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - Interfacing to the outside world.
  - **Clock domains and metastability.**
  - Safe design and radiation hardness.

# Characterizing metastability

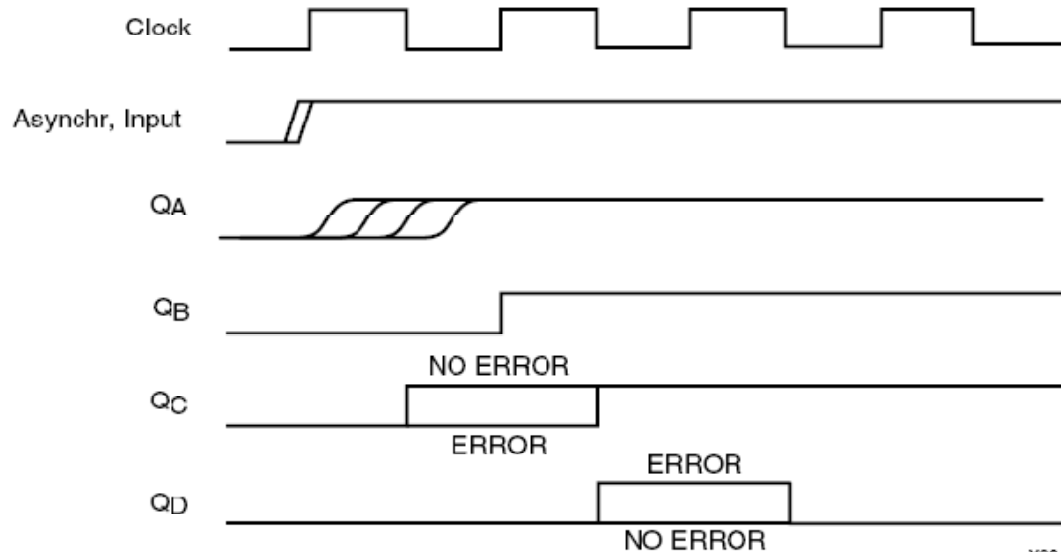 


Use measurements with this setup to find K1 and K2, assuming an MTBF of the form:

$$\text{MTBF} = \frac{e^{K2 \cdot \tau}}{F1 \cdot F2 \cdot K1}$$
 
# Virtex II Pro Metastability results


XC2VP4 Metastable Recovery  
~300MHz Clock, 50MHz Data



From Xilinx XAPP094
 
# Synchronizer circuit

- Place the two flip-flops close together to minimize net delay.
- When a signal comes on-chip, synchronize it first then fan-out (don't fan-out then synchronize at multiple places).
- Make sure clk period is OK for desired MTBF. E.g. for Virtex II Pro, giving the flip-flop 3 ns to resolve will give you an MTBF higher than 1 Million years!







# Crossing clock domains

- For single-bit signals, use the double flip-flop synchronizer.
- For multi-bit signals, using a synchronizer for each bit is *wrong*.
  - Different synchronizers can resolve at different times.
  - No way to know when data is valid, other than waiting a long time.
  - For slow transfers, you can use 4-phase or 2-phase handshake (a single point of synchronization). Otherwise, give up acknowledgement and make sure system works “by design”. FIFOs are also useful.

# Four phase handshake

 
 


[Adapted from VLSI Architectures Spring 2004 [www.ee.technion.ac.il/courses/048878](http://www.ee.technion.ac.il/courses/048878) by Ran Ginosar]

The VALID signal is synchronous to the source clock and gets synchronized at the receiving end by a double flip-flop synchronizer. The same happens in the opposite sense with the ACK signal.




# Two phase handshake

  

[Adapted from VLSI Architectures Spring 2004 [www.ee.technion.ac.il/courses/048878](http://www.ee.technion.ac.il/courses/048878) by Ran Ginosar]

# A complete circuit

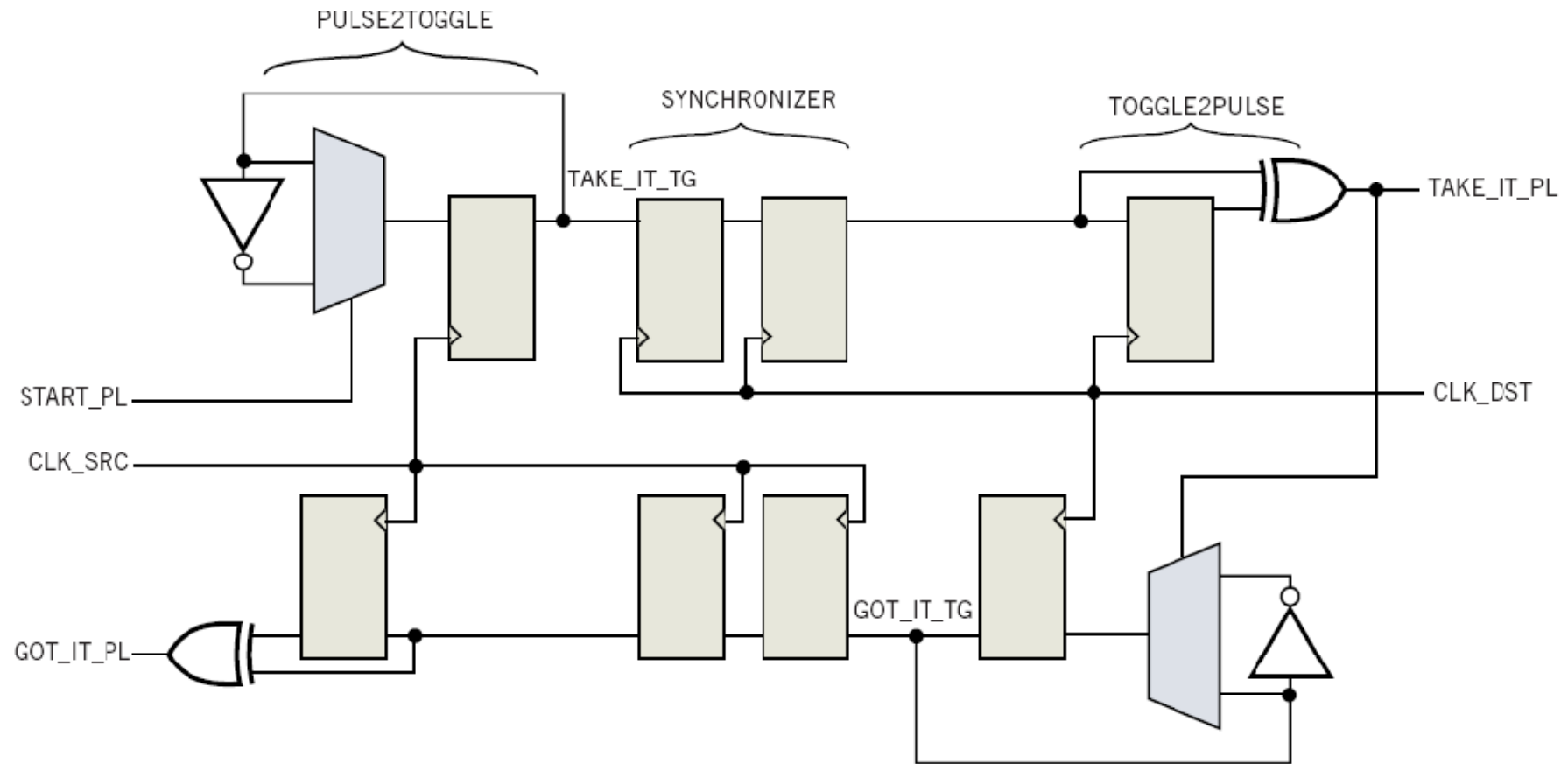




*Michael Crews and Yong Yuenyongsgool, Practical design for transferring signals between clock domains. EDN magazine, February 20, 2003.*

# Outline



- Using FPGAs in the real world
  - Performance boosting techniques.
  - Floating point designs.
  - Powering FPGAs.
  - Interfacing to the outside world.
  - Clock domains and metastability.
  - Safe design and radiation hardness.

# Reset strategies

   


- Different flip-flops see reset de-asserted in different clock cycles!

- It matters in a circuit like this.

- You can fix this problem with a proper reset generator.

Even better if you can use this as a synchronous reset

# Safe state machines

 

One-hot encoding:

s0 => 0001

s1 => 0010


s2 => 0100

s3 => 1000


12 “illegal states” not covered, or covered with a “when others” in VHDL or equivalent.

→ Use option in synthesis tool to prevent optimization of illegal states.

 
# Single Event Effects (SEE) created by neutrons



# Classification of SEEs

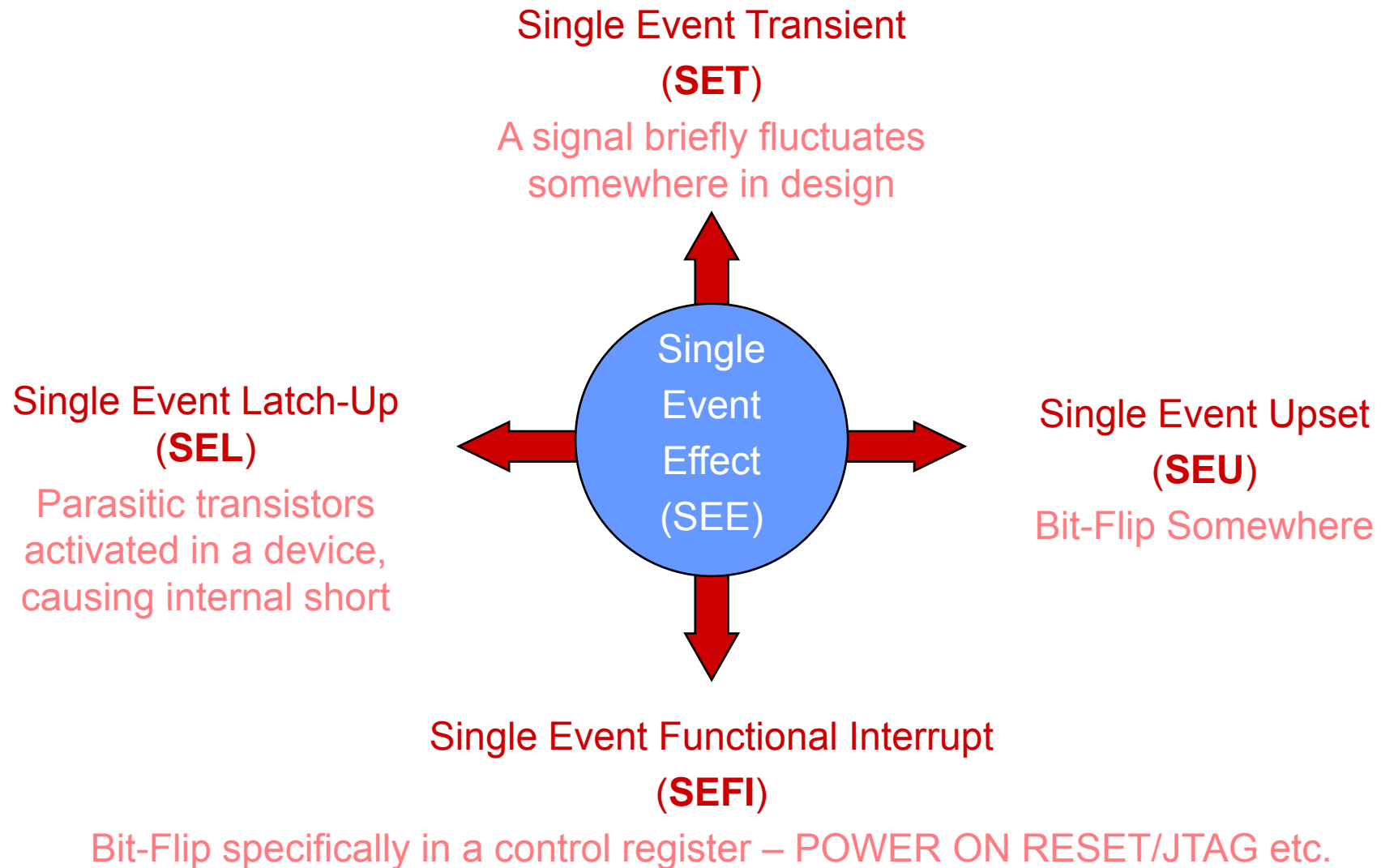

# SEL description

 

Activation of either of these transistors causes a short from  $V+$  to  $V-$

- Has virtually disappeared in new technologies (low  $V_{ccint}$  not enough to forward bias transistors).
- Only cure used to be epitaxial substrate (very expensive).



# SEU Failures in Time (FIT)


- Defined as the number of failures expected in  $10^9$  hours.
- In practice, configuration RAM dominates. Example:

**Virtex XCV1000 memory Utilization**

Memory Type	# of bits	%
Configuration	5,810,048	97.4
Block RAM	131,072	2.2
CLB flip-flops	26,112	0.4

- Average of only 10% of FPGA configuration bits are used in typical designs
  - Even in a 99% full design, only up to 30% are used
  - Most bits control interconnect muxes
  - Most mux control values are “don’t-care”
- Must include this ratio for accurate SEU FIT rate calculations.


**FPGA Interconnect**

 

○ ON      ✗ DON'T-CARE  
■ OFF      — Active Wire
 
# Not all parts of the design are critical

- Average of only 40% of circuits in FPGA designs are critical
  - Substantial circuit overhead for startup logic, diagnostics, debug, monitoring, fault-handling, control path, etc.
- Must also include this ratio in SEU FIT rate calculations



# Actual FIT


	SEUPI Ratio	CC Ratio
Name	“SEU Probability Impact” Ratio	“Critical Circuit” Ratio
Definition	% of total configuration bits that impact a given customer design	% of total design that is critical for standard system operation
Typical Range <sup>1</sup>	1% - 30%	20% - 80%
Average <sup>1</sup>	10%	40%

Note 1: From analysis of real FPGA designs

$$\text{Actual FIT} = \text{Base FIT} * \text{SEUPI Ratio} * \text{CC Ratio}$$
 
# Half-latches (weak keepers) in Virtex devices

- Provide constants
- Save logic resources
- Used throughout device
- Subject to SEU upset
  - Can reset over time
- Not observable
  - Not defined by configuration bits
- Reinitialized as part of device initialization
  - Full reconfiguration required




# Mitigation techniques: scrubbing

- Readback and verification of configuration.
  - Most internal logic can be verified during normal operation.
  - Sets limits on duration of upsets.
- Partial configuration
  - Not supported by all FPGA vendors/families.
  - Allows fine grained reconfiguration.
  - Does not reset entire device.
    - Allows user logic to continue to function.
- Complete reconfiguration
  - Required after SEFI.
  - No user functionality for the duration of reconfiguration.
- Verification by dedicated device
  - Usually radiation tolerant antifuse FPGA
  - Secure storage of checksums and configuration an issue
    - FLASH is radiation sensitive
- Self verification
  - Often the only option for existing designs
  - Not possible in all device families
    - Utilizes logic intended for dynamic reconfiguration
    - Verification logic has small footprint
      - Usually a few dozen CLBs and 1 block RAM (for checksums).
 
# Triple Module Redundancy (TMR)

- Feedback TMR

- Three copies of user logic
  - State feedback from voter
    - Counter example
- Handles faults
- Resynchronizes
  - Operational through repair
- Speed penalty due to feedback
- Desirable for state based logic



# Alternatives

- Antifuse
  - Configuration based on physical shorts
    - Invulnerable to upset
    - Cannot be altered
  - Over 90% smaller upset cross section for comparable geometry
  - Signal routing more efficient
    - Much lower power dissipation for similar device geometry
  - Lags SRAM in fabrication technology
    - Usually one generation behind
    - Latch up more of a problem than in SRAM devices
- Rad-hard Antifuse
  - All flip-flops TMRed in silicon
    - Unmatched reliability
    - High (extreme) cost
    - Unimpressive performance
      - Feedback TMR built in
      - Usually larger geometry
      - Not available in highest densities offered by antifuse
- FLASH FPGAs
  - Middle ground in base susceptibility
  - Readback/Verification problematic
    - Usually only JTAG (slow) supported
  - Maximum number of write cycles an issue

# Acknowledgements



- Many thanks to Jeff Weintraub (Xilinx University Program), Eric Crabill (Xilinx), John Molendijk (CERN), Ben Todd (CERN), Matt Stettler (LANL), Larry Doolittle (LBNL) and Silica for some of these slides.