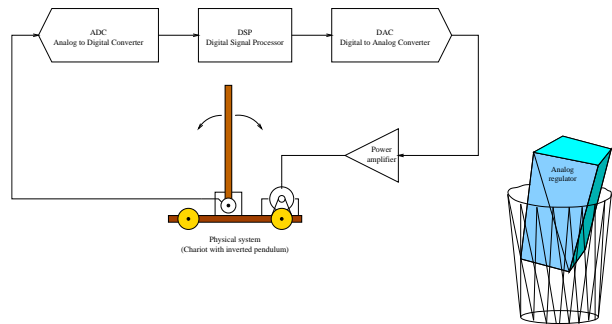




From analog to digital


and back again...




What does an ADC do?

Analog to Digital Converter

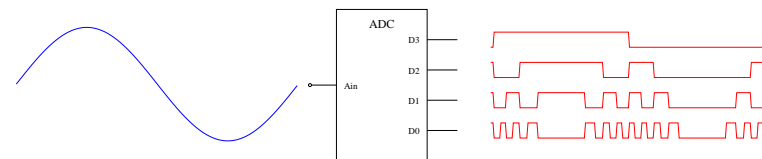An ADC converts a continuously variable signal, a voltage or a current, into a sequence of numbers, represented by logic levels on a group of wires.



Amplitude quantization

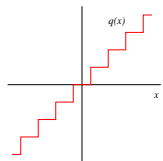

- Quantization replaces a range of continuous values by a set of discrete ones.
- Usually the number of levels is a power of 2.
- The difference between the original signal and the discrete representation is the quantization error



Amplitude quantization

Power in original signal:

$$P_s = \frac{A^2}{T} \int_0^T \sin^2 \omega t dt = \frac{A^2}{2}$$

Quantized to n bits, one quantum is:


$$q = \frac{2A}{2^n} = A \cdot 2^{-(n-1)}$$

Maximum quantization error:

$$\epsilon = \frac{\pm q}{2} = \pm A \cdot 2^{-n} \text{ (with } p(\epsilon) = \frac{1}{q} \text{)}$$

Power in quantization error:
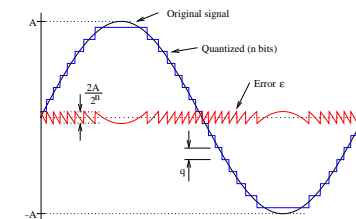
$$P_\epsilon = \int_{-q/2}^{q/2} p(\epsilon) \epsilon^2 d\epsilon \approx \frac{A^2 \cdot 2^{-2n}}{3}$$



$$\text{Thus } SNR = \frac{P_s}{P_\epsilon} = 1.5 \cdot 2^{2n}$$

$$\text{In dB: } 10 \cdot \log_{10} \frac{P_s}{P_\epsilon} = 1.76 + 6.02n$$



Multiplication of the signal by a train of impulses $w(t)$ with period $T_s (= 1/F_s)$:

$$g(t) = u(t) \cdot w(t)$$


$$g(t) = u(t) \sum_{n=-\infty}^{\infty} \delta(t - nT_s)$$

$$g(t) = \sum_{n=-\infty}^{\infty} u(nT_s) \delta(t - nT_s)$$

Fourier transform of $w(t)$:

$$W(f) = \int_{-\infty}^{\infty} w(t) e^{-j2\pi f t} dt$$
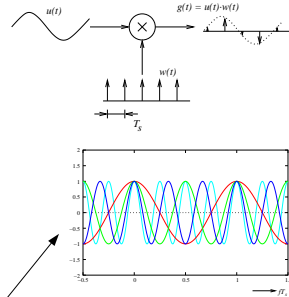
$$W(f) = \sum_{n=-\infty}^{\infty} e^{-j2\pi n f T_s} = 1 + 2 \sum_{n=1}^{\infty} \cos 2\pi n f T_s = \sum_{n=-\infty}^{\infty} \delta(f - \frac{n}{T_s})$$



The spectrum of the sampled signal is the convolution of $U(f)$ and $W(f)$


$$G(f) = U(f) * W(f) = \int_{-\infty}^{\infty} U(\phi) W(f - \phi) d\phi$$

$$G(f) = \int_{-\infty}^{\infty} U(\phi) \sum_{n=-\infty}^{\infty} \delta(f - \frac{n}{T_s} - \phi) d\phi$$

$$G(f) = \sum_{n=-\infty}^{\infty} \int_{-\infty}^{\infty} U(\phi) \delta(f - \frac{n}{T_s} - \phi) d\phi$$

$$G(f) = \sum_{n=-\infty}^{\infty} U(f - \frac{n}{T_s})$$

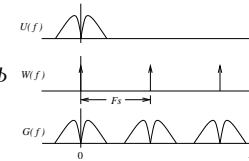After sampling, the signal spectrum repeats for all multiples of F_s




If the sampling rate F_s is less than twice the signal bandwidth, the spectral images overlap. To avoid this, the following condition must be fulfilled:

$$F_s > 2 \cdot BW$$

This is the Nyquist criterion

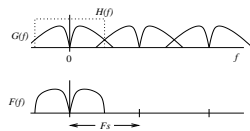
One way this condition can be fulfilled is by filtering the analogue signal prior to digitizing it, using what is called an anti-aliasing filter. Since brick-wall filters cannot be made, the sampling rate should usually be quite a bit greater than twice the signal bandwidth.



Each of the images in the spectrum of the sampled signal contains all the information needed to reconstruct the original. They are *aliases*.

We might reconstruct the original signal with a filter that rejects everything except the original frequency band. After filtering, the spectrum is exactly that of the original signal, in other words, no information is lost. We have recovered the original signal exactly.

This is Shannon's theorem

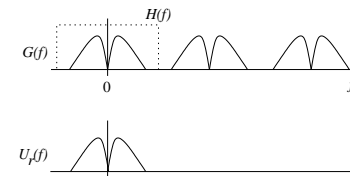



Filter the baseband using a rectangular filter $H(f)$. The filter time-domain response is the inverse Fourier transform of its frequency-domain shape:

$$h(t) = \mathcal{F}^{-1}\{H(f)\} = \int_{-\infty}^{\infty} H(f) e^{j2\pi f t} df = \int_{-F_s/2}^{F_s/2} e^{j2\pi f t} df = F_s \frac{\sin \pi F_s t}{\pi F_s t}$$


Convolution of filter with sample stream:

$$u_r(t) = g(t) * h(t)$$

$$u_r(t) = \int_{-\infty}^{\infty} \sum_{n=-\infty}^{\infty} u(\tau) \cdot \delta(\tau - nT_s) \cdot h(t - \tau) d\tau$$


$$u_r(t) = \sum_{n=-\infty}^{\infty} u(nT_s) \cdot h(t - nT_s)$$
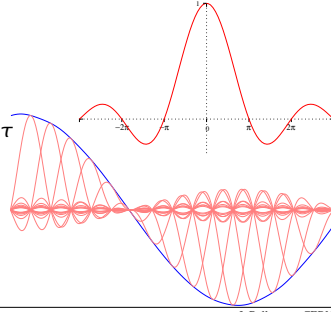
$$u_r(t) = \sum_{n=-\infty}^{\infty} u(nT_s) \cdot F_s \frac{\sin \pi F_s (t - nT_s)}{\pi F_s (t - nT_s)}$$



Note that exactly the same spectrum results for any signal frequency band displaced by $m \cdot F_s$ (for integer m)

This goes by the name of *sub-sampling*

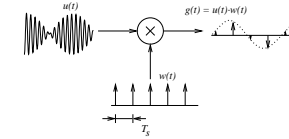


$$G(f) = \int_{-\infty}^{\infty} U(\Phi + mF_s) W(f - \Phi) d\Phi$$

$$G(f) = \sum_{n=-\infty}^{\infty} U(f - \frac{n}{T_s} + mF_s)$$

$$G(f) = \sum_{n=-\infty}^{\infty} U(f + \frac{m-n}{T_s})$$
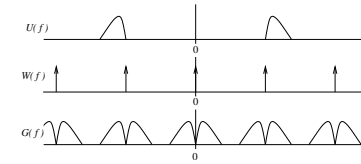
$$G(f) = \sum_{n=-\infty}^{\infty} U(f - \frac{n}{T_s})$$



We could also choose a different spectral image to (re)construct the signal:

First work out the time-domain representation of the filter:



$$H(f) = 1 \quad \text{for } F_s < |f| < \frac{3}{2} F_s$$

$$H(f) = 0 \quad \text{everywhere else}$$

$$h(t) = \mathcal{F}^{-1}\{H(f)\} = \int_{-\infty}^{\infty} H(f) e^{j2\pi f t} df$$

$$h(t) = \int_{-\frac{3}{2}F_s}^{-F_s} e^{j2\pi f t} df - \int_{F_s}^{\frac{3}{2}F_s} e^{j2\pi f t} df$$
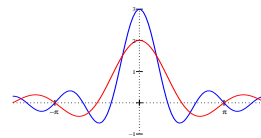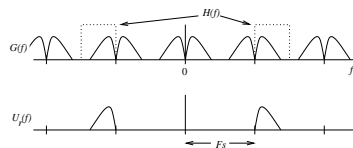
$$h(t) = 3F_s \text{sinc}(3\pi t F_s) - 2F_s \text{sinc}(2\pi t F_s)$$



Then convolve the sample stream with the filter function:


$$u_r(t) = g(t) * h(t)$$

$$u_r(t) = \int_{-\infty}^{\infty} g(\tau) \cdot h(t - \tau) d\tau$$

$$u_r(t) = \int_{-\infty}^{\infty} \sum_{n=-\infty}^{\infty} u(\tau) \cdot \delta(\tau - nT_s) \cdot h(t - \tau) d\tau$$

$$u_r(t) = \sum_{n=-\infty}^{\infty} u(nT_s) \cdot h(t - nT_s)$$
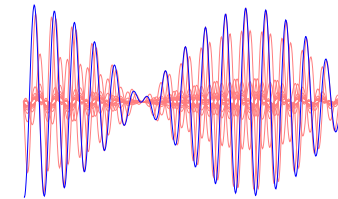
$$u_r(t) = \sum_{n=-\infty}^{\infty} u(nT_s) \{3F_s \text{sinc}(3\pi(t - nT_s)F_s) - 2F_s \text{sinc}(2\pi(t - nT_s)F_s)\}$$





1915: E.T. Whittaker : Interpolation theory

Couldn't get my hands on that one. Everyone refers to him, so I mention him as well.

1928: H. Nyquist : Telegraph transmission theory

Classic! Deals with signal distortion in transmission channels like undersea cables, which were a hot subject, at the time.

1933: V.A. Kotelnikov : Carrying capacity of the ether

Detailed demonstration that band-limited signals can be represented by a sum of sinc functions, apparently independently from Nyquist and Whittaker.

1949: C. Shannon : Communication in the presence of noise


Classic! Gives transmission capacity of a channel as a function of bandwidth and signal to noise ratio. The sampling theorem is dealt with in section II.

Other names: R.V.L. Hartley, J.M. Whittaker, C-J. de la Vallée Poussin, ...




Although mathematically Dirac deltas, brick-wall filters and infinite sums are quite nice to handle, in real electronic circuitry, you can't have them.

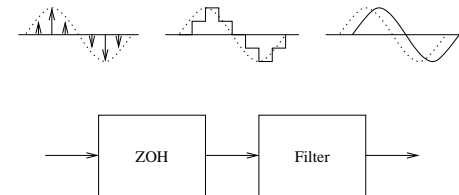The Dirac δ is replaced by an (almost) rectangular pulse of one sampling period duration, and filters are described by finite polynomials, with finite-slope band edges. So, the output is held constant during each sampling period, which is functionally called a zero-order hold, and a low-pass filter smooths over the steps.




As a consequence, the reconstructed signal spectrum is convolved with a $\text{sinc}(f/F_s)$ function and some energy from adjacent spectral images leaks into the desired band. Note that at the Nyquist frequency, $F_N = F_s/2$, the response is down by 3.9dB.

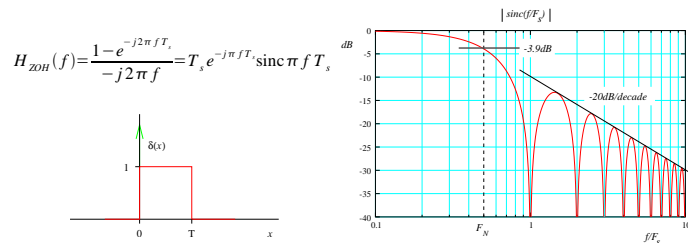If this is a problem, the reconstruction filter may be designed to compensate. (You can also pre-compensate in the digital domain.)



For 'large enough' and 'busy enough' signals, the quantization error is a random variable with a flat distribution.

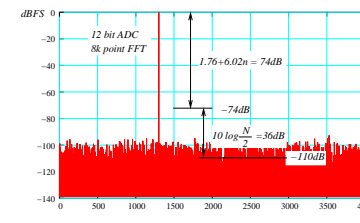→ Quantization noise is white and spread out evenly over $0 < f < F_s/2$.



$$\text{FFT Noise floor: } - \left(1.76 + 6.02n + 10 \log_{10} \frac{N}{2} \right) \text{ dBFS}$$

(N = number of samples)



Unfortunately, quantization noise isn't always white:


- Simple ratios between F_{in} and F_s cause some of the quantization noise power to concentrate in discrete spectral lines
- ADC non-linearities cause harmonics of the input signal

Spurs appear in the spectrum:

SFDR is the distance between the input signal and the greatest spur.


A little bit of dither can help to reduce spurs.

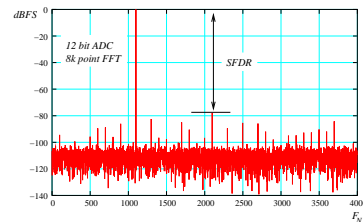(Dither is the intentional injection of a little bit of noise.)



Non-linearity creates harmonics

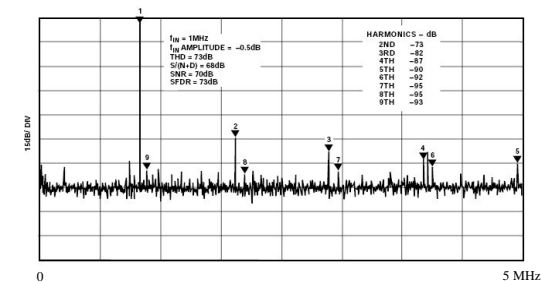THD is the rms sum of the first 6 harmonics compared to the input signal, in dB




AD872A FFT plot, $f_{in}=1$ MHz, -0.5dBFS



In real ADCs, the quantization function isn't perfectly uniform


For an input signal with a uniform distribution, the distribution of output values is no longer uniform.

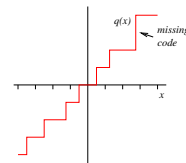The DNL measures the normalized error of the nominal size of each quantization step.



Missing codes



Non-monotonicity

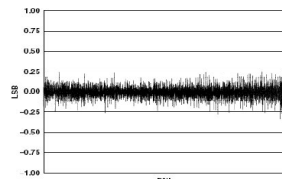

AD9432 12-bit 105MS/s pipeline ADC



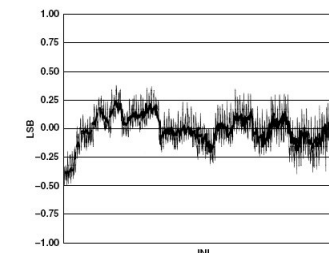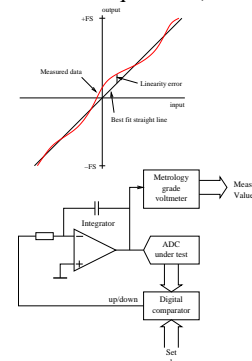INL measures the deviation of the ADC characteristic from a straight line through the end points (or sometimes from a least squares fit)



AD9432 12-bit 105MS/s pipeline ADC



Apply a nearly full-scale sinusoidal signal.
Measure P_ϵ as the rms sum over all frequencies, ignoring DC and the first five harmonics, and solve for n :

$$SNR = \frac{P_s}{P_\epsilon} = 1.5 \cdot 2^{2n}$$

If you choose to also add in all harmonics into the calculation of P_ϵ , you would get the SINAD.
(Signal over Noise-And-Distortion)
(Which looks a little bit worse, of course)


SNR and SINAD are usually expressed in dBc or dBFS



Non-linearity also causes inter-modulation distortion. (Creating sum and difference frequencies from two applied tones $f_{imd} = \pm n f_1 \pm m f_2$.)

IMD is the rms sum of the inter-modulation products compared to the rms sum of the input signals (usually in dB).

The order of an IMD product is $|n|+|m|$

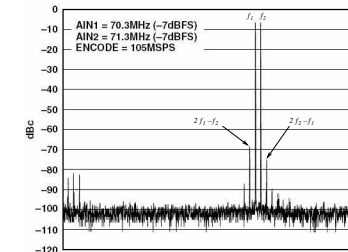

AD9432, IMD FFT plot




Importance of clock jitter depends on rate of change of analogue input signal

A clock timing error Δt yields an amplitude error:

$$\Delta U = \frac{du(t)}{dt} \cdot \Delta t$$

This is a severe condition!

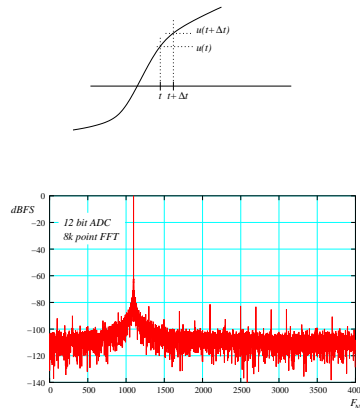

Tolerable jitter:

$$\Delta t = \frac{1}{\frac{du(t)}{dt} \cdot 2^n}$$

Ex: Suppose we digitize a 100MHz sinusoid to 10 bits:

$$u(t) = \sin 2\pi 10^8 t \quad \Rightarrow \quad \frac{du(t)}{dt} = 2\pi 10^8 \cos 2\pi 10^8 t$$


So at the steepest slope:

$$\Delta t = \frac{1}{2\pi 10^8 \cdot 2^{10}} \approx 1.6 \text{ ps} \quad \Rightarrow \quad \text{A good quartz or ceramic resonator oscillator is needed}$$



$$SNR = 20 \log_{10} \frac{1}{2\pi f \Delta T}$$
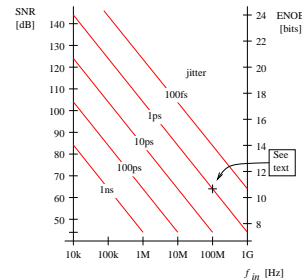
$$ENOB = \log_2 \frac{1}{2\pi f \Delta T}$$




With 1 ps of jitter, a 100 MHz signal can only be digitized to 10.5 bits


Relaxed by root(decimation ratio) for Σ - Δ converters



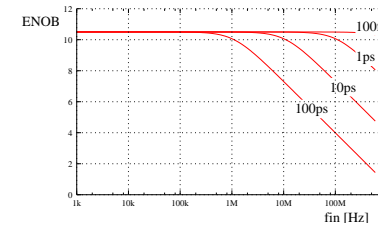
Even using the best clock, the resolution reaches a limit. For example, for an actual 12-bit ADC, the ENOB vs. F_m plot might look like this:



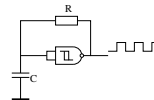
RC and logic gate oscillators
Poor
Jitter >100ps



LC oscillators
Fair
Jitter 10 - 100ps

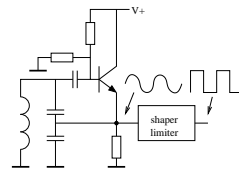

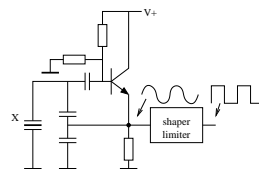Pierce oscillator
Good.
Usually better than 1ps




Upconverted thermal, schottky and 1/f noise

$$\Delta t_{rms} = \frac{T_0}{2\pi} \sqrt{\int_0^\infty S_\phi(f) \cdot 4 \sin^2(\pi f \tau) df}$$

$S_\phi(f)$ is the spectral density of the phase noise

$\sin^2(\pi f \tau)$ is a weighting function

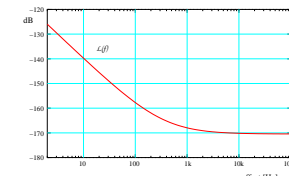The term $\frac{T_0}{2\pi}$ converts phase into time




SSB phase noise of an oscillator

(Function of Fourier frequency f and sum of both sidebands)


(For low frequencies of S , the phase can't drift very far, when $\tau = n/f$, the contribution cancels, and there are maxima in between.)



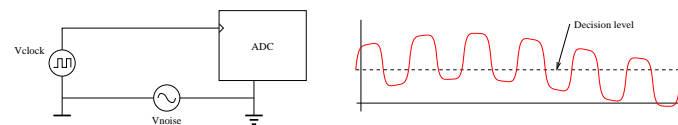
Ground noise between clock source and ADC aggravates jitter



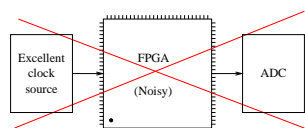
Noise may be due to magnetic interference or common impedance coupling. Possible remedy: Differential clock.



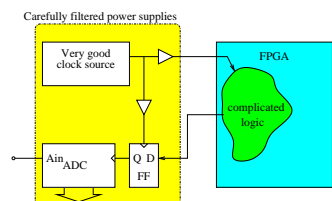Don't route clocks through FPGAs!
(Complex logic circuits cause all sorts of interference)



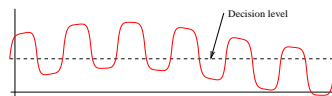But if you must, then resynchronize with the original clean clock



- ADCs (and DACs too!) need good quality clock sources
- Digital electronics is not optimized for low crosstalk
- PLLs in FPGAs usually have *very* poor jitter specs

Treat your clock oscillator like a sensitive analogue circuit

- Filter and bypass clock generation & distribution power supply extra carefully
- Keep PCB layout tight and compact, minimize loop areas
- Refer clock source to the same GND as the ADC
- Do not route an ADC clock through an FPGA
- Don't use left-over gates in clock buffer package for other purposes



Straight binary

1111 1111 — max
...
0000 0000 — 0

Offset binary

1111 1111 — max/2
... — 0
...
0000 0000 — -max/2


Two's complement

0111 1111 — max/2 -1
...
0000 0000 — 0
1111 1111 — -1
...
1000 0000 — -max/2


Note: To convert offset binary into 2's complement, simply invert the most significant ADC bit.



You were expecting this:

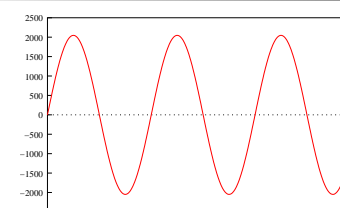


but you got this:

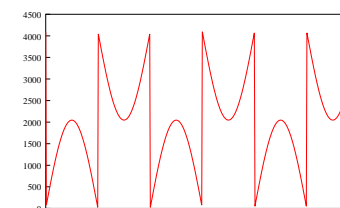


Reason: The ADC delivers 2's complement numbers and the sign bit is not in the right place.





The sign bit isn't in the right place:

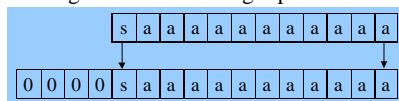

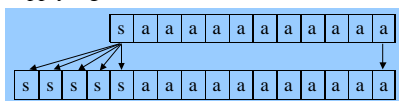Apply sign extension: $a = (a \wedge 0x800) - 2048;$





or logical left shift: $a \ll 4;$

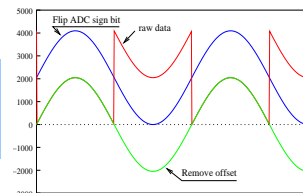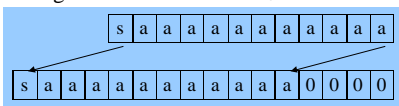

BCD and display driver outputs. Handy for stand-alone instruments, panel meters, hand-held multi-meters.

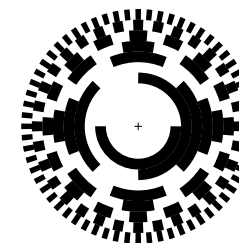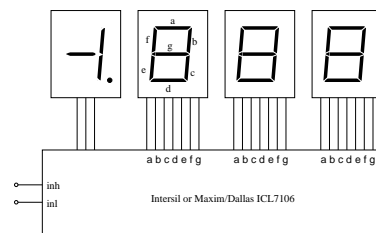Gray code: Only one bit changes between adjacent values. No glitches. Resolver disks. Angular and linear transducers.



... or how to get your signal digitized cleanly:

Interference (comes from elsewhere) and noise (inherent in the circuit)

Coupling paths:

• Common impedance coupling




(Use generously dimensioned conductors or a star layout)

• Inductive coupling


(Keep loop areas small and put distance between them)

• Capacitive coupling

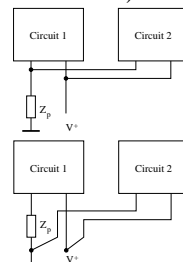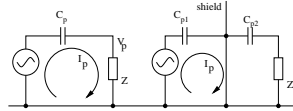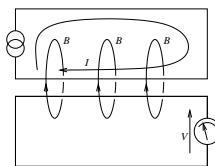
(Keep high-Z nodes and nodes with high dE/dt far apart, or put grounded shields between them)



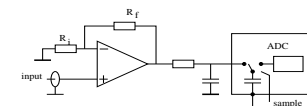
Buffer amplifier adapts signal to ADC and prevents sampler kickback
RC circuit at ADC input isolates amplifier from ADC input capacitance



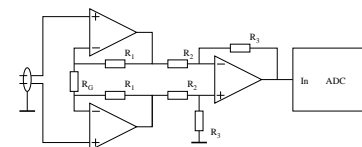Instrumentation amplifier: Good common mode rejection, high gain, but only at low frequency




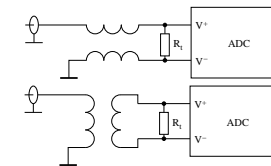Baluns and transformers: Good common mode rejection at high frequencies






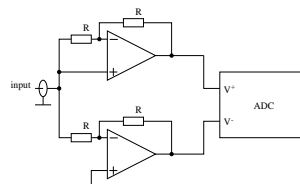Single-ended to differential conversion
(Often used for high-performance or low voltage ADCs)



Baluns and transformers can also be used for this.

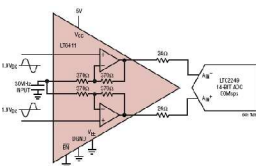Or use monolithic differential buffer amplifiers (ADA4941, AD8351, LT6411, THS4503, etc.)



Summary:


- Adapting signal range to ADC input range (Scaling & level shifting)
- Conversion between single-ended and differential signals
- Protecting the ADC input from overload
- Terminate long cables into their characteristic impedance...
- ...or, to the contrary, provide a high impedance to avoid loading the source
- Rejecting interference
- Filtering out-of-band frequencies (Anti-alias filter, noise reduction)
- Holding input constant while conversion takes place



Architecture	Speed	Resolution	Linearity	Applications
Flash	Very fast (GS/s)	Poor (8 bits)	Poor	Oscilloscopes
Successive approximation	Fast (MS/s)	Fair (14 bits)	Fair	Transient recorders
Σ - Δ	Slow (kS/s)	Excellent (24 bits)	Excellent	DSP, video, digital receivers, instrumentation
Dual-slope Integration	Very slow (S/s)	Very good (18 bits)	Very good	Process control, audio, weight, pressure, temperature measurement
				Bench-top and hand-held measuring instruments, battery powered devices

Other architectures:

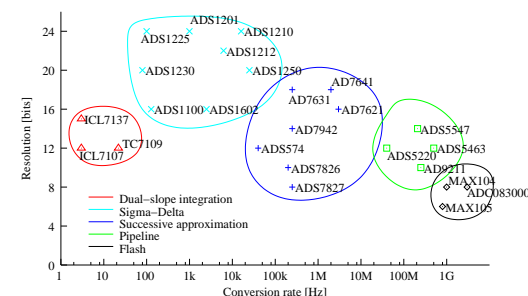- Mixed forms (E.g. flash with SA, or flash with Σ - Δ)
- Tracking ADC
- Voltage-to-frequency converters






Sequence of operation:

- Compare input with half scale, keep if greater.
- Add one quarter and compare, keep if input greater.
- Add 1/8 etc...

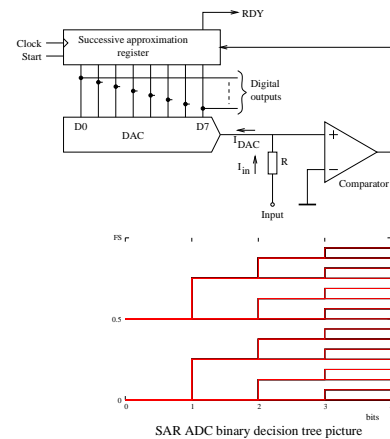
Usually clocked or strobed
Serial data interface
Often fixed conversion rate
Sometimes poor DNL



SAR ADC binary decision tree picture




12-bit, 1 MS/s, serial interface SAR ADC

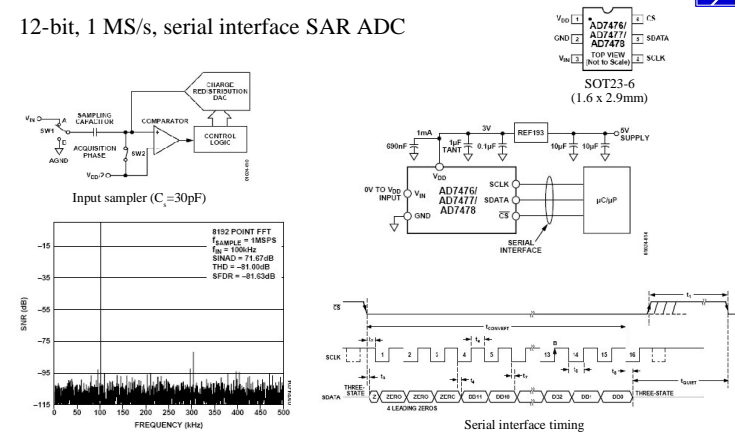


Flash ADCs are the fastest:

- A resistor divider chain creates all possible decision levels from a single reference.
- $2^n - 1$ comparators compare each level with the input signal.
- Digital logic converts "thermometer" code into binary.
- Sensitive to 'sparkle' codes
- Metastability
- Input capacitance

Usually 8 bits, rarely more than 10

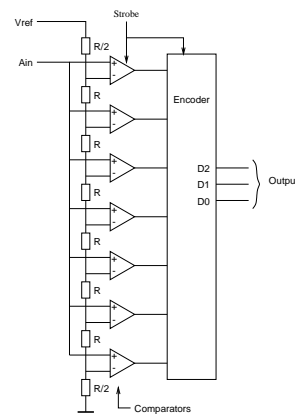

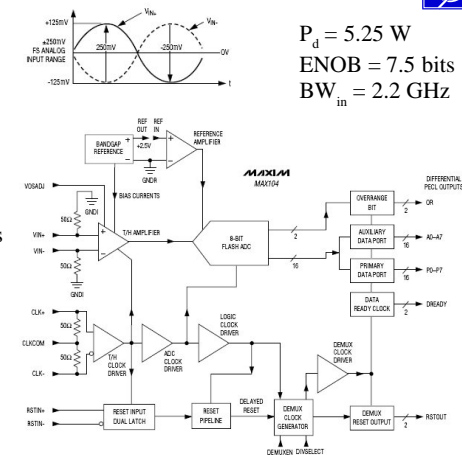
8-bit, 1 GS/s flash ADC
50 Ω differential inputs
 ± 250 mV input range
Metastability error rate 10^{-16}
Differential PECL outputs
De-multiplexer
Needs 3 supply voltages
 ± 5 V and 3.3V
Many GND and Supply pins





Segmented or pipelined ADC:

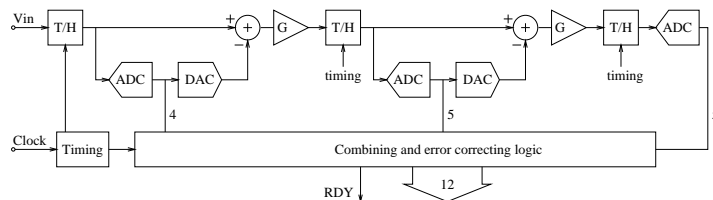- Sample rate comparable to flash ADCs, but with several clock periods of latency.
- Resolution comparable to successive approximation architecture.



From analog to digital

CAS, June 2007

J. Belleman - CERN



12-bit, 250 MS/s, 5-stage pipeline ADC


Differential LVDS or

de-multiplexed outputs

2pF sampling capacitance

Differential analogue

input, BW 1.2 GHz

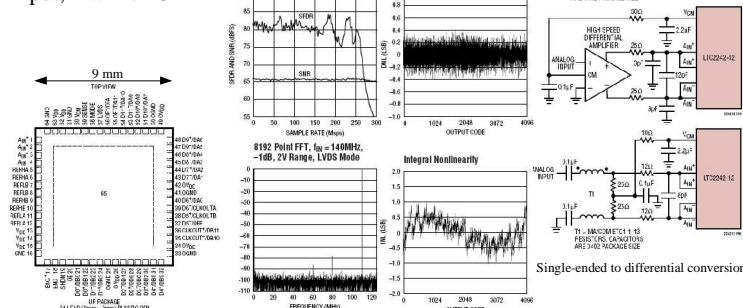

From analog to digital

CAS, June 2007

J. Belleman - CERN




Increase sample rate:

- Quantization noise is spread over a larger BW.
- Numerically low-pass filter the sample stream:
- Out-of-band quantization noise power is removed.

Conclusion:

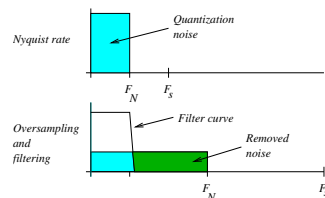
- SNR gets better by 3dB/octave of oversampling rate.
Dither may be necessary for very quiet ADCs.



From analog to digital

CAS, June 2007

J. Belleman - CERN

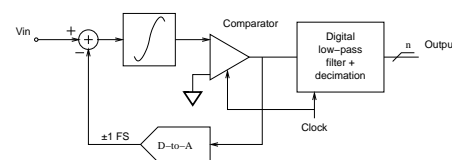

Average duty cycle of comparator output reflects input value.

Digital low-pass decimation filter trades sample rate for resolution.

Good DNL, good resolution, slow.


From analog to digital

CAS, June 2007

J. Belleman - CERN



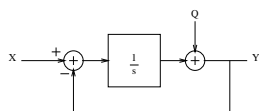
For the input: $\frac{Y}{X} = \frac{1}{s+1}$



Pretend that quantizer contributes random uncorrelated noise:

For the noise: $\frac{Y}{Q} = \frac{s}{s+1}$

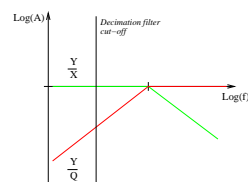
Input signal is low-pass filtered
Quantization noise is high-pass filtered
Decimation filter rejects high frequency
→ Resolution is improved



Noise shaping!





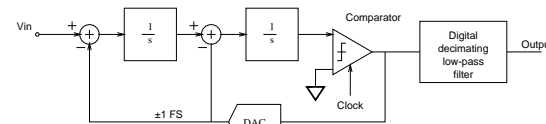Higher order loops and noise shaping, E.g., a 2nd order modulator:



For the input: $\frac{Y}{X} = \frac{1}{s^2 + s + 1}$

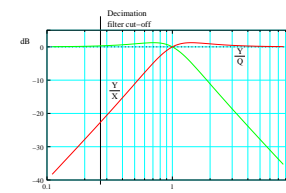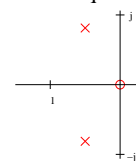For the quantization noise: $\frac{Y}{Q} = \frac{s^2}{s^2 + s + 1}$




Decimating filter rejects noise



Side tones, idling patterns, birdies


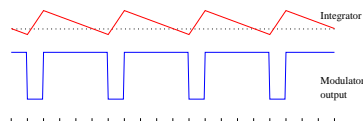
- For some input values, the Σ/Δ modulator can produce repeating patterns with repetition rates well below the sampling frequency
- These may leak through the decimation filter, causing a side tone or 'birdie'




- Possible remedies include using higher order modulators and dither, to randomize things



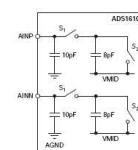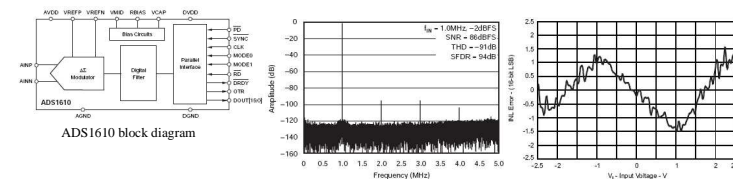
Programmable, instrumentation ADC
12-16 bits, depending on filter settings



Circuit model of inputs

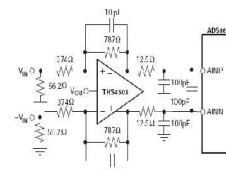


Input conditioning

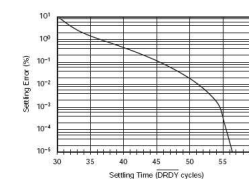




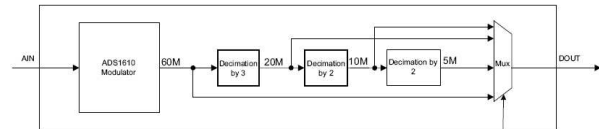Programmable, instrumentation ADC
12-16 bits, depending on filter settings



Mode 1	Mode 0	OUTPUT RATE	OSR	SNR (TYP)	BITS	SETTLING TIME (ORDY cycles)
0	0	Default 10MHz mode	6	85dBFS	16	55
0	1	20MHz	3	74dBFS	14	25
1	0	5MHz	12	91dBFS	16	55
1	1	60MHz bypass mode	1	55dBFS	12	NA

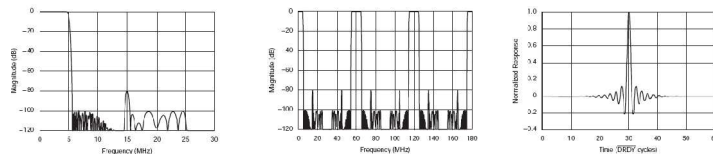

From analog to digital

CAS, June 2007

J. Belleman - CERN




Integrate input during T1

Then:

Integrate reference until
zero is reached, while
counting clock pulses

Final count is proportional to input

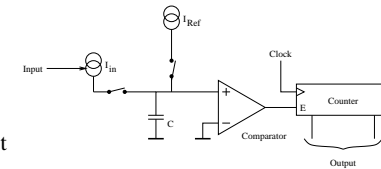


Can be built for low power operation,
good for battery power equipment
(Multimeters etc.)

Integration time often chosen to reject
power line interference

Excellent DNL

Sometimes the signal source is inherently a pulsed current source
(Photomultiplier)

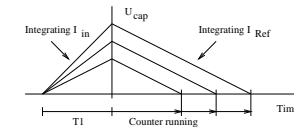Variants: Time to Digital Converter (TDC)




From analog to digital

CAS, June 2007

J. Belleman - CERN



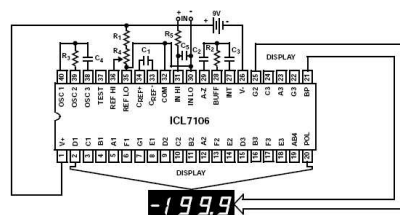Directly drives an LCD display
 ± 200 mV full scale
Conversion time 300 ms
Consumes 1 mA @ 9 V




$C_1 = 0.1\mu\text{F}$
 $C_2 = 0.47\mu\text{F}$
 $C_3 = 0.22\mu\text{F}$
 $C_4 = 100\mu\text{F}$
 $C_5 = 0.02\mu\text{F}$
 $R_1 = 24\text{k}\Omega$
 $R_2 = 47\text{k}\Omega$
 $R_3 = 100\text{k}\Omega$
 $R_4 = 1\text{M}\Omega$
 $R_5 = 1\text{M}\Omega$

From analog to digital

CAS, June 2007

J. Belleman - CERN

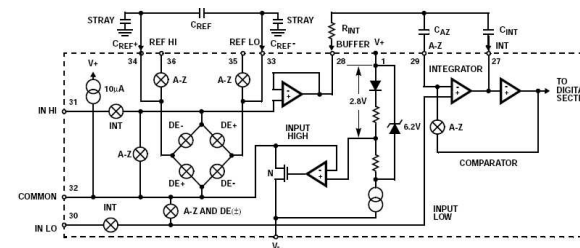

Analogue section of ICL7106


From analog to digital

CAS, June 2007

J. Belleman - CERN



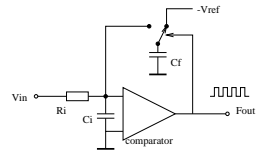Input voltage is integrated onto C_i
A fixed-size packet of charge is removed each time the switch connects C_f to the input.



Applications:

Process control

Easy to use as integrating converter (Just add a counter)

In combination with F-to-V converter: Cheap isolation amplifier

Low-cost


Slow!

Signal easy to transmit over large distances


Very good linearity



8-pin DIP
Linearity 0.003%
Fmax 10 kHz

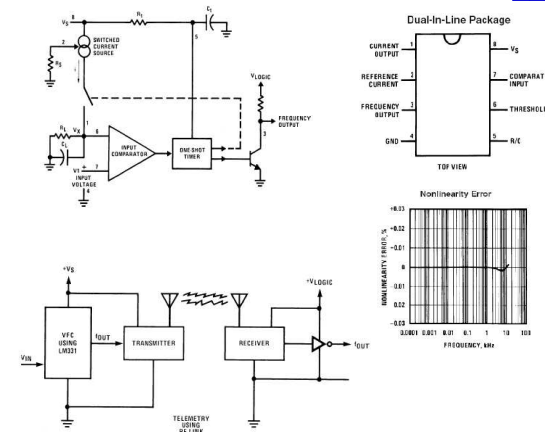

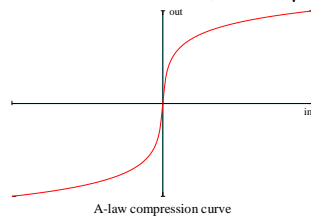Non-linear converters, A-law, μ -law, used in telephony.



Digital potentiometers (DS1669, MAX5438, AD5259, etc.)
Digital output sensors, temperature, acceleration (AD7414, AD16006)
Capacitance-to-digital converters (AD7745)



Architecture

Kelvin-Varley divider	Accurate, monotonous. Mainly as building block in integrated DACs
Thermometer DAC	Monotonous. Limited number of bits
Binary weighted ladder	Very common, but subject to glitches
R-2R ladder	Widely used. Not very power efficient
$\Sigma\Delta$	Linear, accurate, but complex.

Mixed architectures:


- Segmented DAC
- Interpolating DAC

Variants:



- Multiplying DACs
- Current or voltage output
- Differential or single-ended



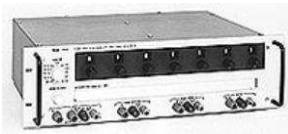- The ancestor of all DACs
- Still rivals the best modern DACs
- Available as rack mounted units (Expensive!)
- Used as sub-circuit in IC DACs
- Variable Z_{out} : Buffer amplifier needed



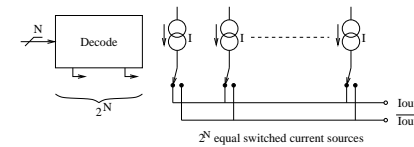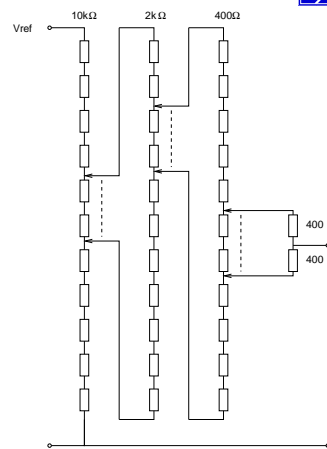Example: Fluke 720A
Linearity, resolution : 10^{-7}
Input resistance : 100 k Ω , 0.005%




- Inherently monotonic
- No glitches
- Limited number of bits (2^N current sources!)
- Used as a sub-circuit in segmented DACs




$$I_{out} = 2 \frac{V_{ref}}{R} \cdot \frac{N}{2^n}$$

Number of bits n
Applied input value N

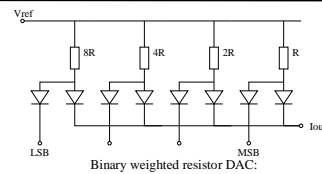

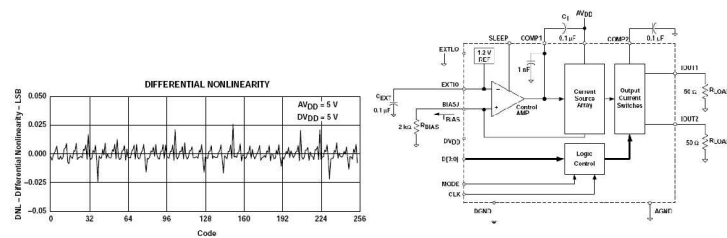
Example: THS5641, 8 bit, 100 MS/s, 35 ns settling time




- Very common architecture
- Uses only two resistor values
- Voltage or current output
- Not very power efficient
- Often as multiplying DAC


$$V_{out} = V_{ref} \frac{N}{2^n}$$

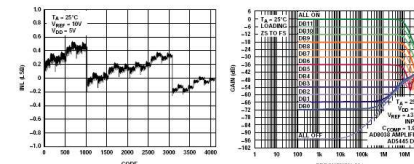Example: AD5445, 12 bit current output, 20.4 MS/s, 80 ns settling time



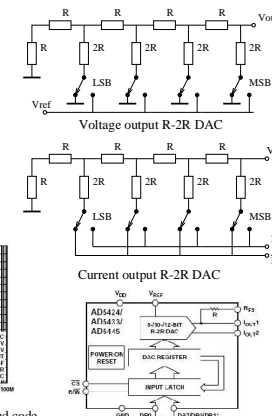Reference input response vs. frequency and code



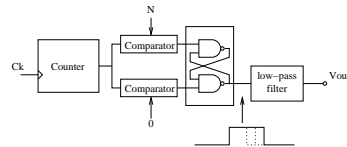


- Pulse Width Modulation
- Inherently linear
- Limited resolution
- Often used in μ -controller chips
- Applications: Motor control





Combination of other architectures, to optimize speed, linearity, SFDR, glitch energy, etc.

Common for high performance DACs used in instrumentation and communication equipment.

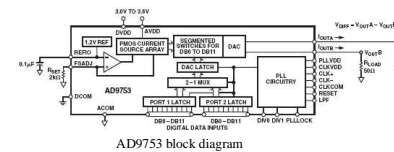Example: AD9753, (12 bit, 300 MS/s) combines two thermometer (5 and 4 bits) sections and a binary weighted stage (3 bits).




AD9753 block diagram

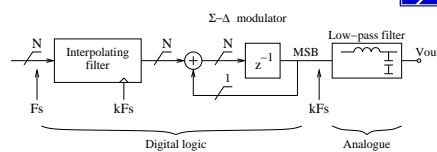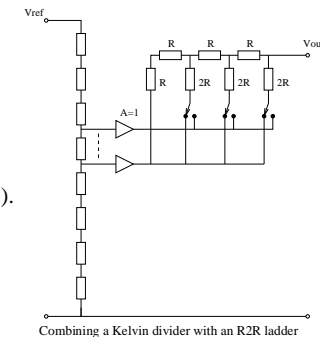

- Inherently linear
- Complex
- Σ - Δ modulator entirely digital
- Usually has a 1-bit DAC, sometimes multi-bit
- Large oversampling ratio eases output filter design

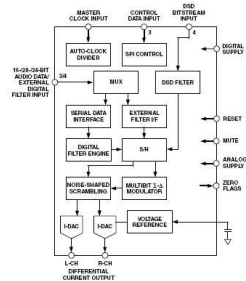Example: AD1955 audio DAC
Update rate 192 kHz, SNR 120 dB



- There are ADCs and DACs for almost any imaginable application
- Performance is ever getting better
- Prices keep going down (15 years ago, a 12 bit 10 MS/s ADC cost 1 k\$. Now it's around 10 \$)

Digital is here to stay!