



Distributed Power Architectures in Computing Systems

P. Mattavelli, P. Tenti, L. Rossetto, S. Buso, S. Saggini

Speaker: G. Spiazzi

Department of Information Engineering - DEI
University of Padova, ITALY




Outline



- Conversion system architectures for DPS
 - Unregulated Intermediate Bus Converters (IBC)
 - Regulated Intermediate Bus Converters
- Isolated Point of Load converters (POLs)
- Non isolated POL: buck interleaved
- Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova



Power Distribution Problem

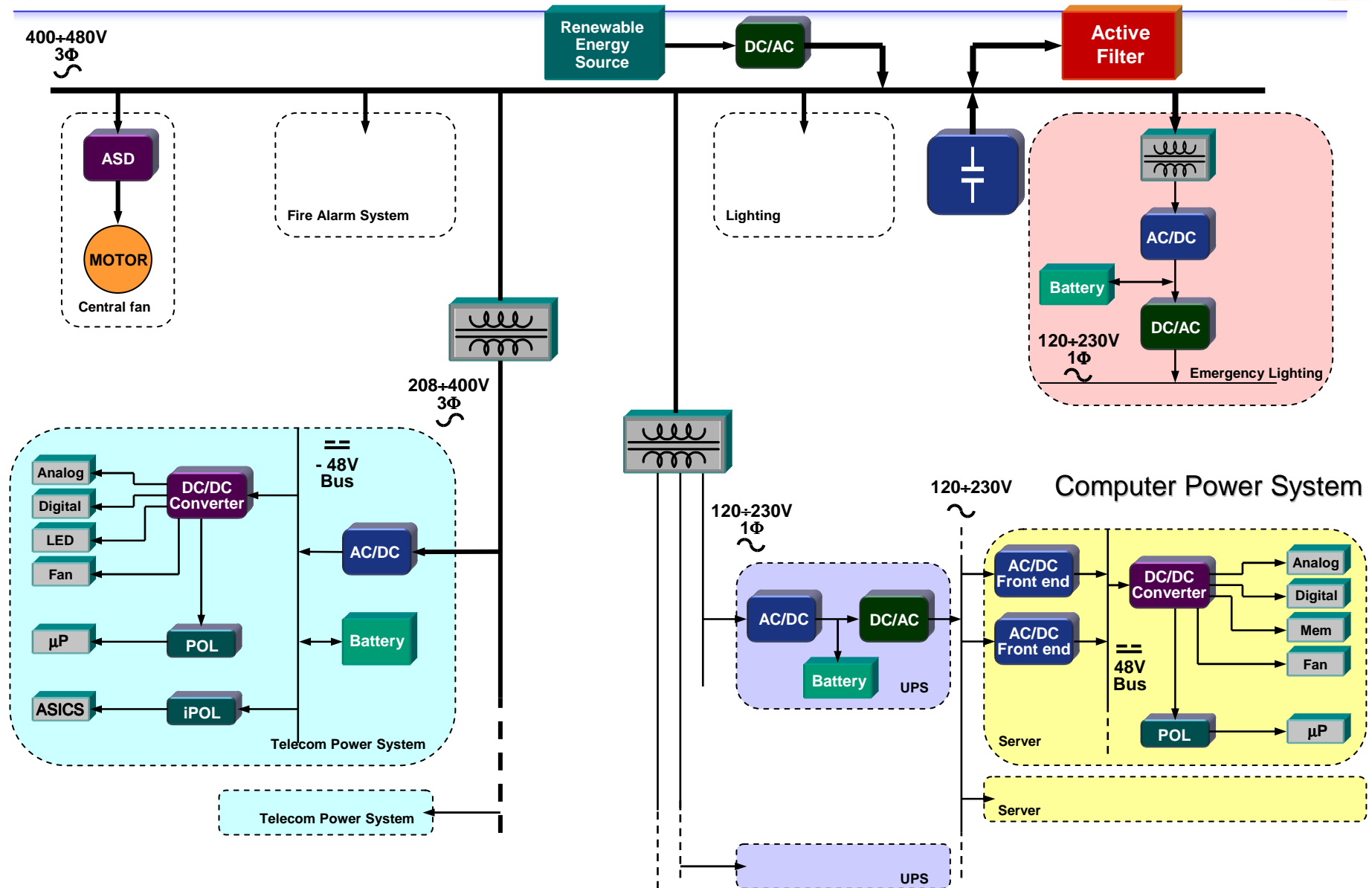




Power Distribution Problem



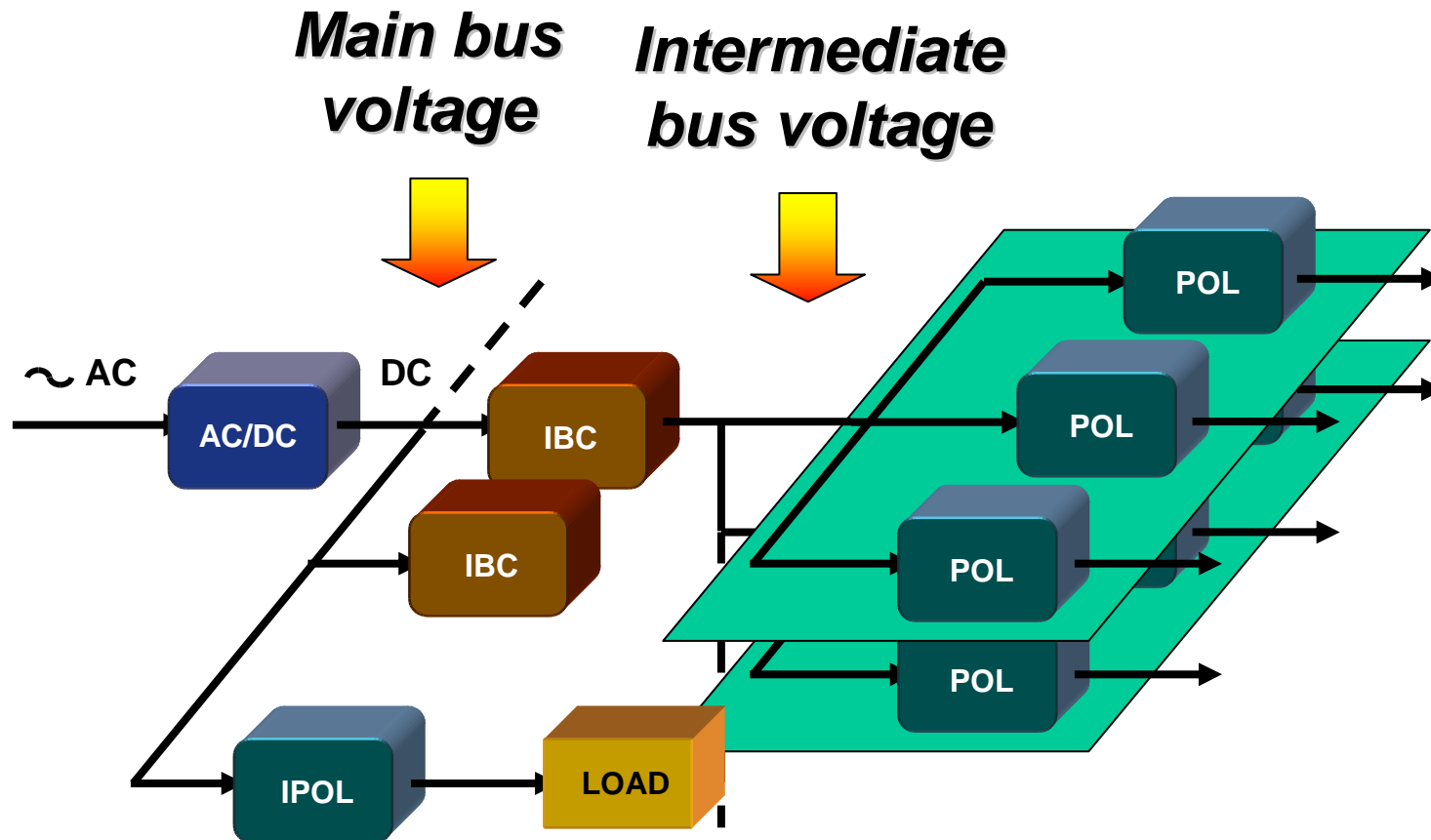
- Very complex Power Management Architectures in Computing & Networking Systems
 - Many low voltage, high current and tightly regulated voltage sources
 - Accurate management for sequencing, tracking and fault management
 - High Power density needed for real estate saving and Thermal management issues
 - Low cost always mandatory in high volume applications



IBC = Intermediate Bus Converter
POL = Point Of Load converter




AC-DC Front End

 





- **EMI filter** for attenuate high-frequency noise (both conducted and radiated) produced by the switching converters
- **High-Power-Factor (HPF)** rectifier for low-frequency harmonic standard compliance
- **Isolated DC/DC** converter for electrical isolation with the main and voltage scaling

HPF Rectifier

 

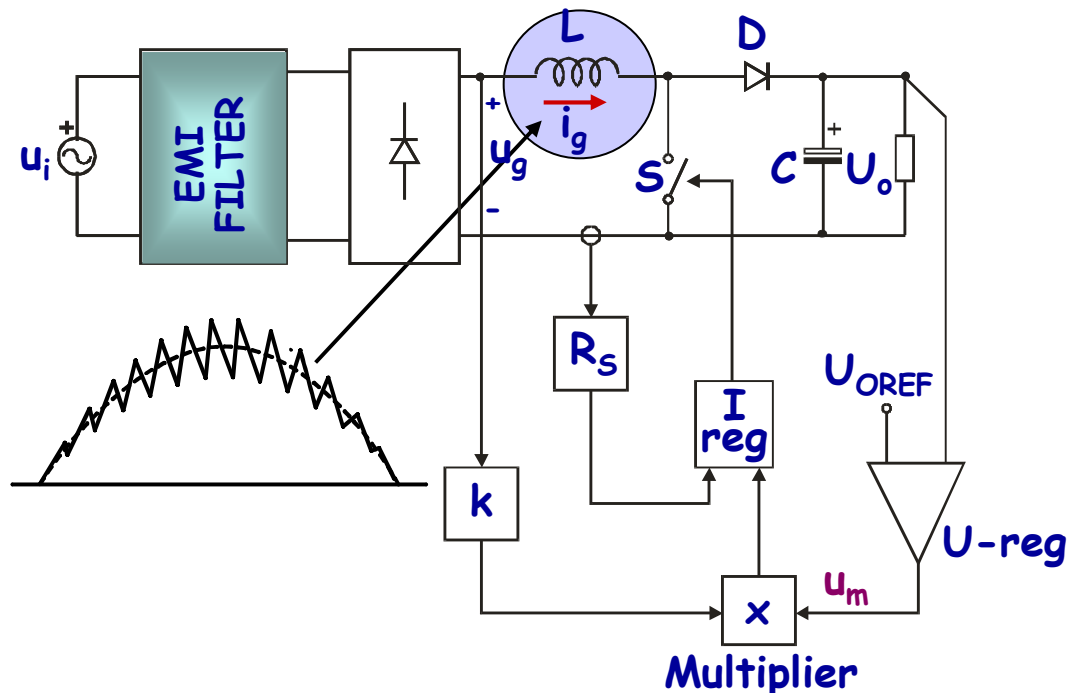
- Boost converter in *CCM*
- Average current mode
- High power factor
- Output voltage higher than peak input voltage
- Dedicated control IC available



   


- Phase-shift modulated Full-bridge converter
- Soft switching operation exploiting the transformer leakage inductance

Narrow Input IBCs

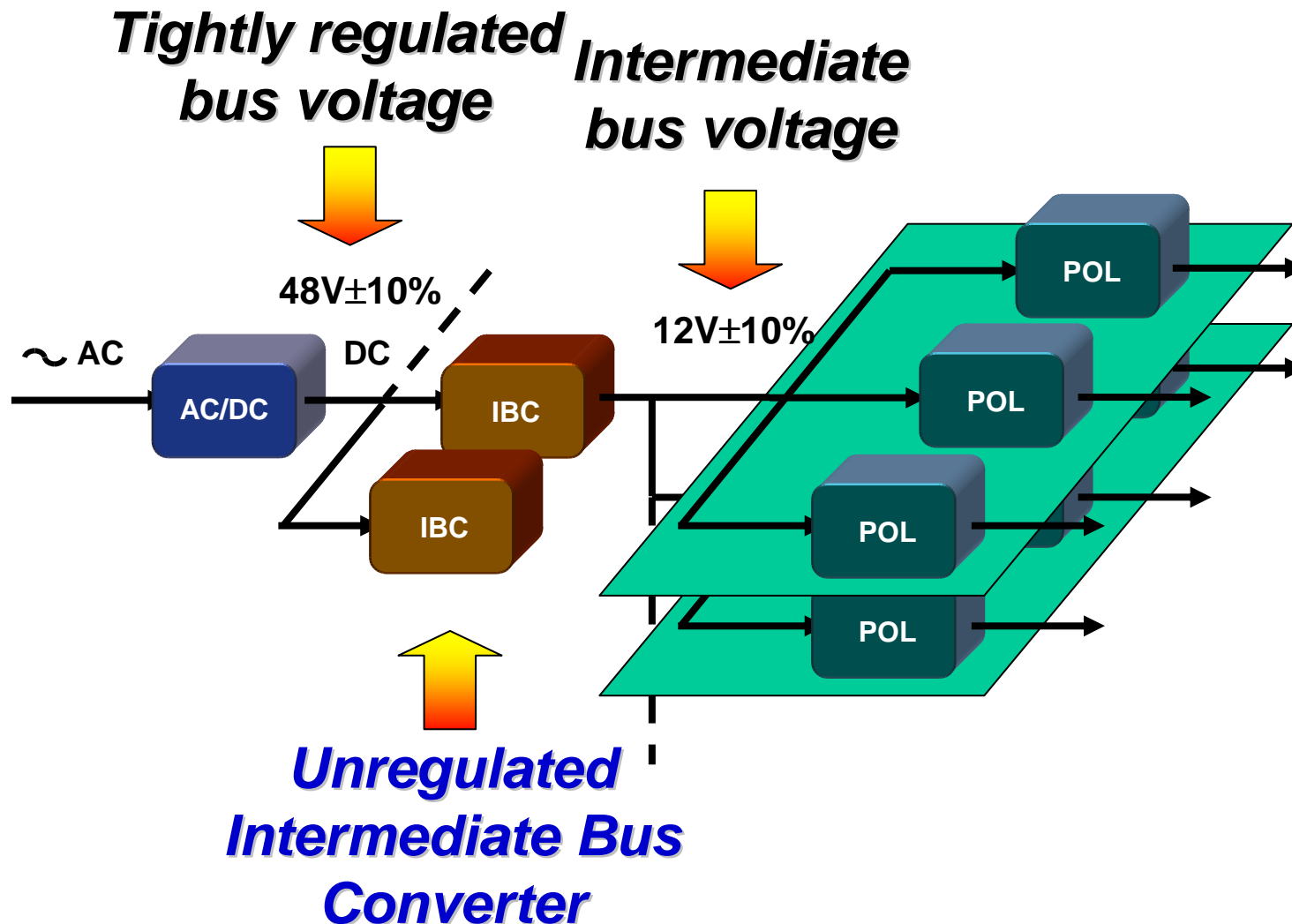

Example of Unregulated IBC

IBC

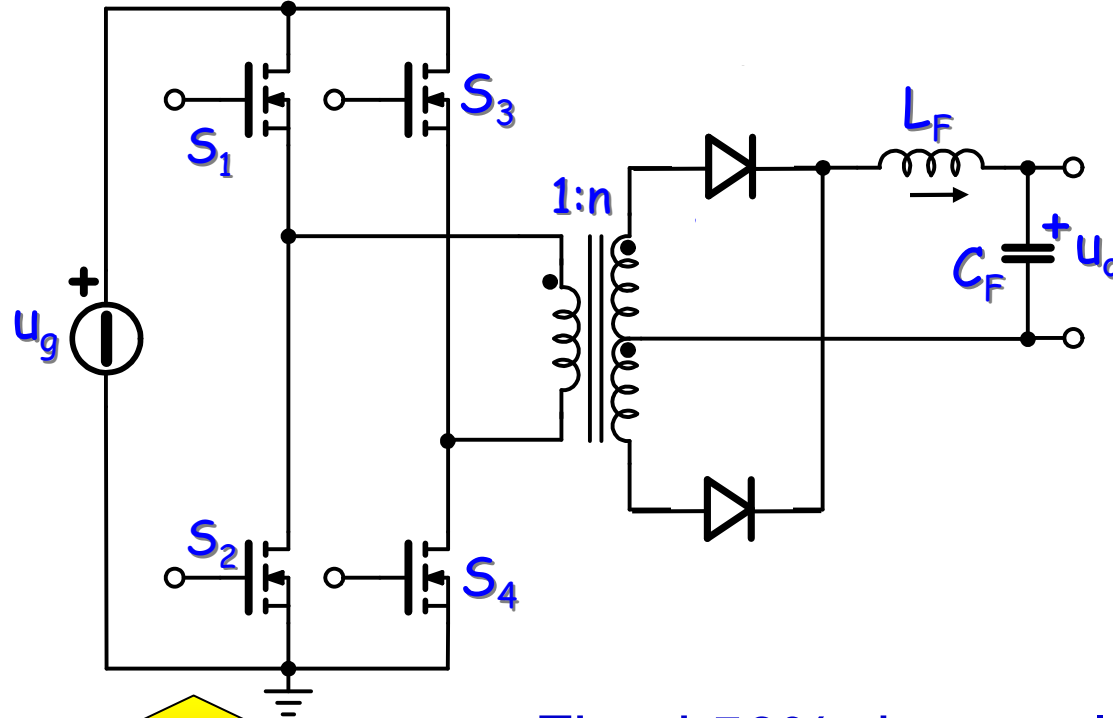


**Full-bridge, half-bridge
or push-pull primary
stage**


Fixed 50% duty-cycle:

1. Soft switching
2. Small output inductor
3. Synchronous rectification

Open-loop operation

 


Example of Regulated IBC

 


- Active-clamped for soft switching
- Synchronous rectification
- Large output inductor
- High voltage rating device (60V) for SR
- *Switching frequency of the state-of-art: ~300KHz*

No intermediate bus voltage


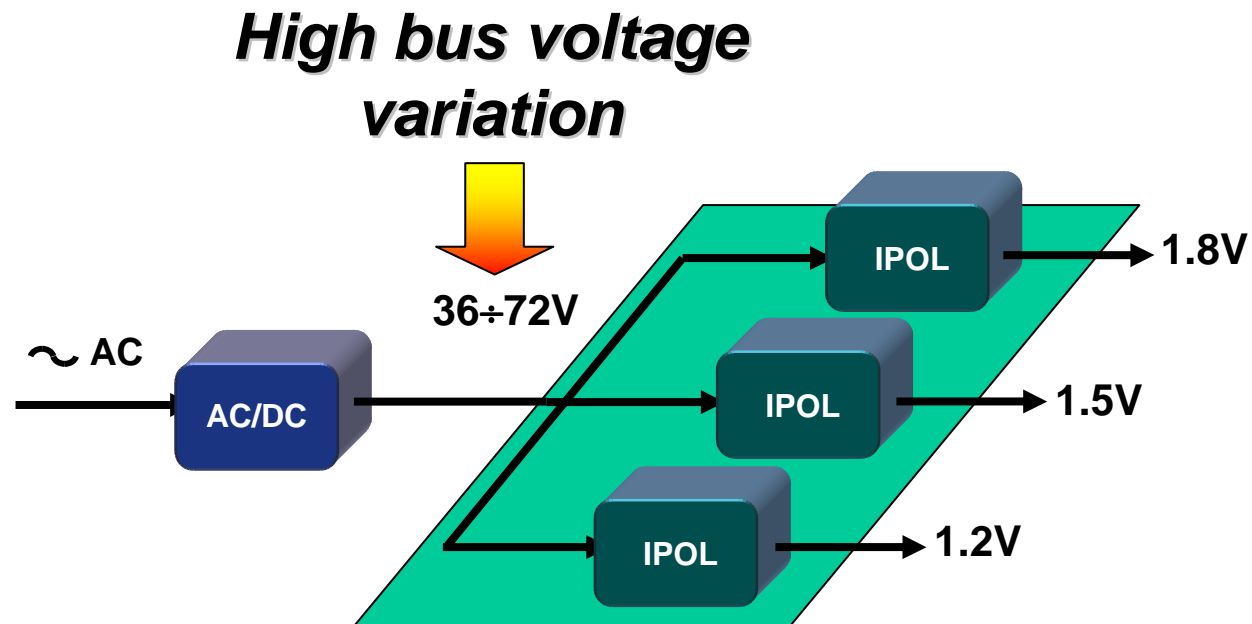


Example of Isolated POL

 

- Half bridge with current doubler
- Synchronous rectification

Current Doubler

  

- No center-tapped windings
- Current ripple cancellation
- Splitted load current between the two inductors



Non Isolated Point Of Load Converters




- Voltage Regulator Modules (VRMs)
 - Power trend
 - Interleaved buck converters
 - Current sharing
 - Adaptive voltage positioning
 - Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova



VRM Intel Specifications



Specs VRD 10.x for Intel P4 Prescott

	 VRD 10.0 – VRD 10.1
Maximum VID (Voltage Identification)	1.4V
V _{CC} Ratings (VID)	0.8375-1.6V
VID step	12.5mV
V _{CC} Tolerance Band (TOB)	± 19mV
Max Load Current	91A for VRD 10.0 115A for VRD 10.1
Voltage identification	6 bit
Over Voltage Protection	VID + 200mV (Proposed)
Over Current Protection	Not fixed (Proposed)
Maximum overshoot voltage allowed over VID	50mV
Maximum overshoot time duration over VID	25µs
Dynamic VID	Up to 61 steps (12.5mV/5µs)
dI _{OUT} /dt MAX	>50A/µs
Load Line Impedance (R _{DRROP})	1mΩ / 1.4mΩ

- Low supply voltage
- Small tolerance band
- High load current
- High current slew rate
- Resistive output impedance




Outline




- **Voltage Regulation Modules (VRM)**
 - Power trend
 - **Interleaved buck converters**
 - Current sharing
 - Adaptive voltage positioning
 - Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova

 - High load current requires the use of parallel power MOSFETs or parallel power converters





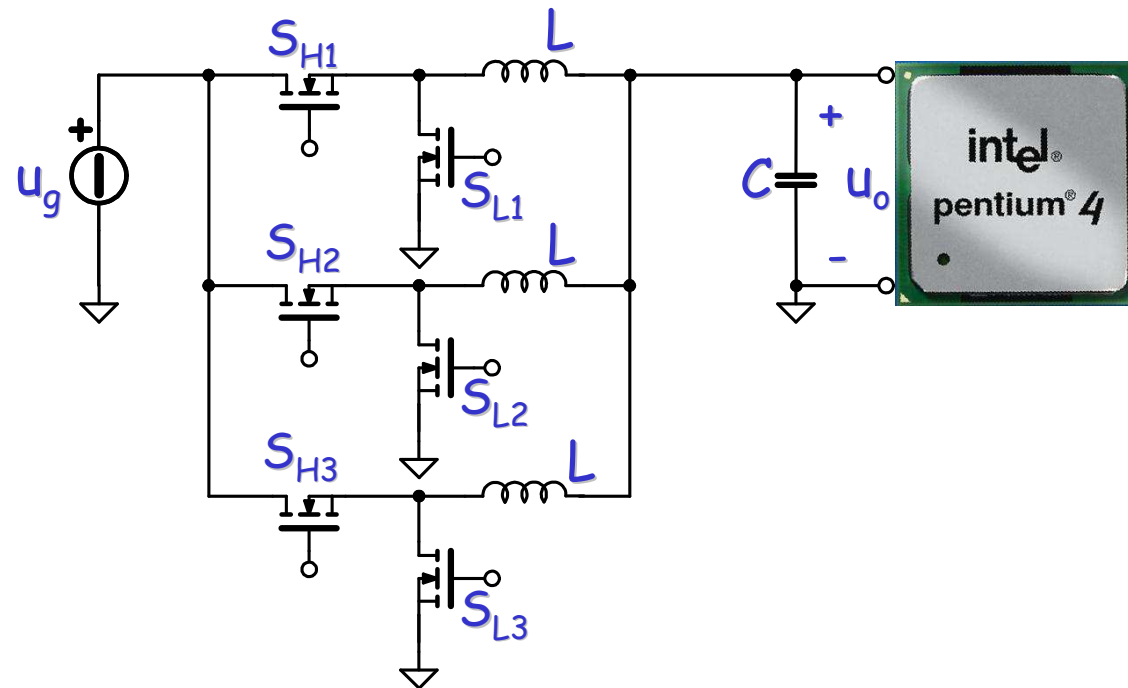Parallel device approach is not convenient since interleaved operation reduces output and input ripple



- Reduced current level per phase
- Reduced output current ripple
- Reduced input current ripple
- Increased bandwidth ($F_{eq} = N F_{sw}$)

Multi-Phase Interleaved Converters

 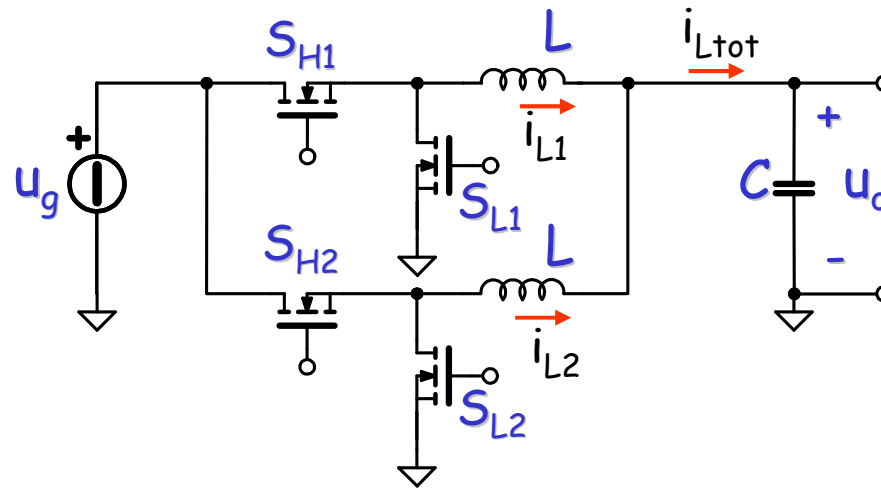


Ripple reduction
on output filter



Output Current Ripple Cancellation




Two phases


 


$D=0.5$ for the best cancellation effect

Four phases

 

 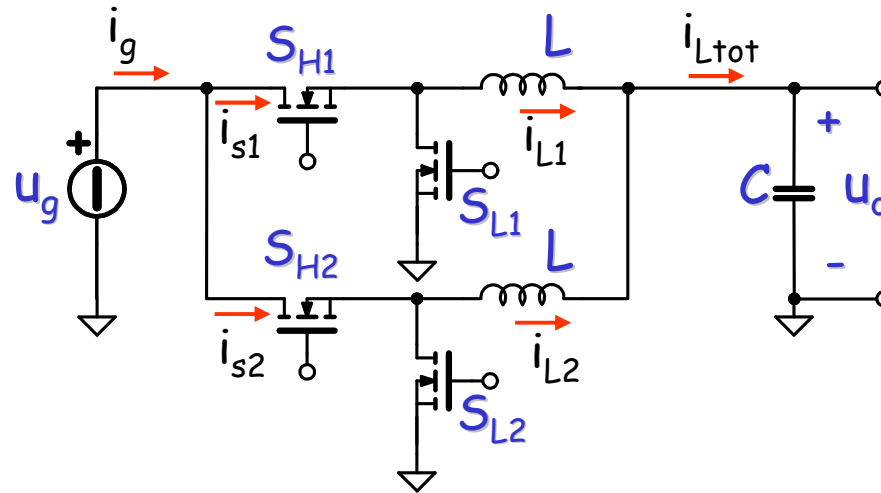$D=0.25, 0.5, 0.75$ for the best cancellation effect



Ripple reduction on input current
 (similar ripple cancellation effect)




Outline





- **Voltage Regulation Modules (VRM)**
 - Power trend
 - Interleaved buck converters
 - **Current sharing**
 - Adaptive voltage positioning
- Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova

Current Sharing in Parallel Channels

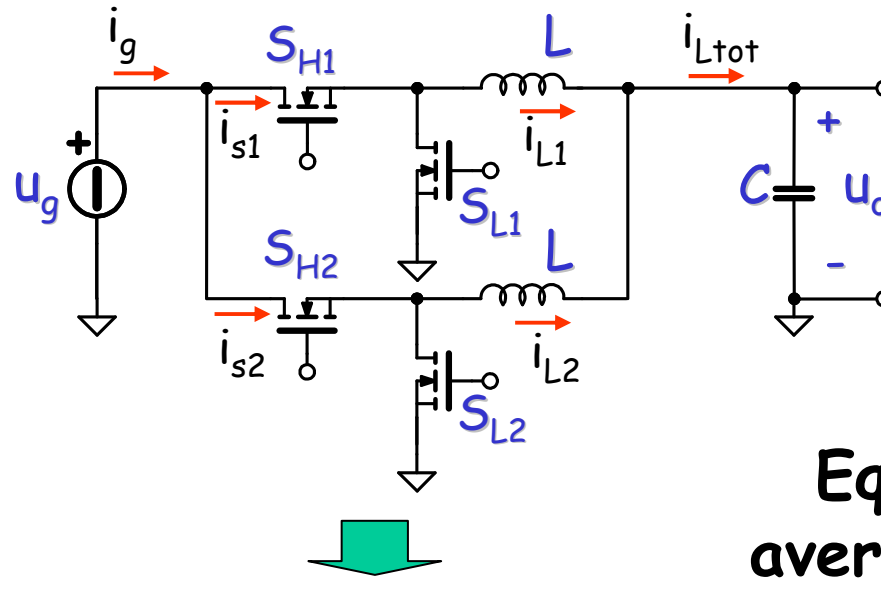

Equivalent
average model

 

 

$R_k = R_{dsonk} + R_{Lk} + R_{PCBk}$

R_{dsonk} : Mosfet R_{dson}
 R_{Lk} : inductor resistance
 R_{PCBk} : trace resistance (PCB layout)

Dc inductor current mismatch:


$$\Delta i_L = i_{L1} - i_{L2} = 2U_g \frac{\delta_1 - \delta_2}{R_1 + R_2} \left(\frac{1 + \frac{R_2 \delta_1 - R_1 \delta_2}{2(\delta_1 - \delta_2)} \cdot \frac{1}{R_L}}{1 + \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_L}} \right)$$

$R_L =$ load resistance

- Unmatched duty cycle
- Unmatched channel resistance

- Even **small mismatches** of duty-cycle or of channel resistance generate **serious current sharing issues**
- Example with unmatched duty-cycles:

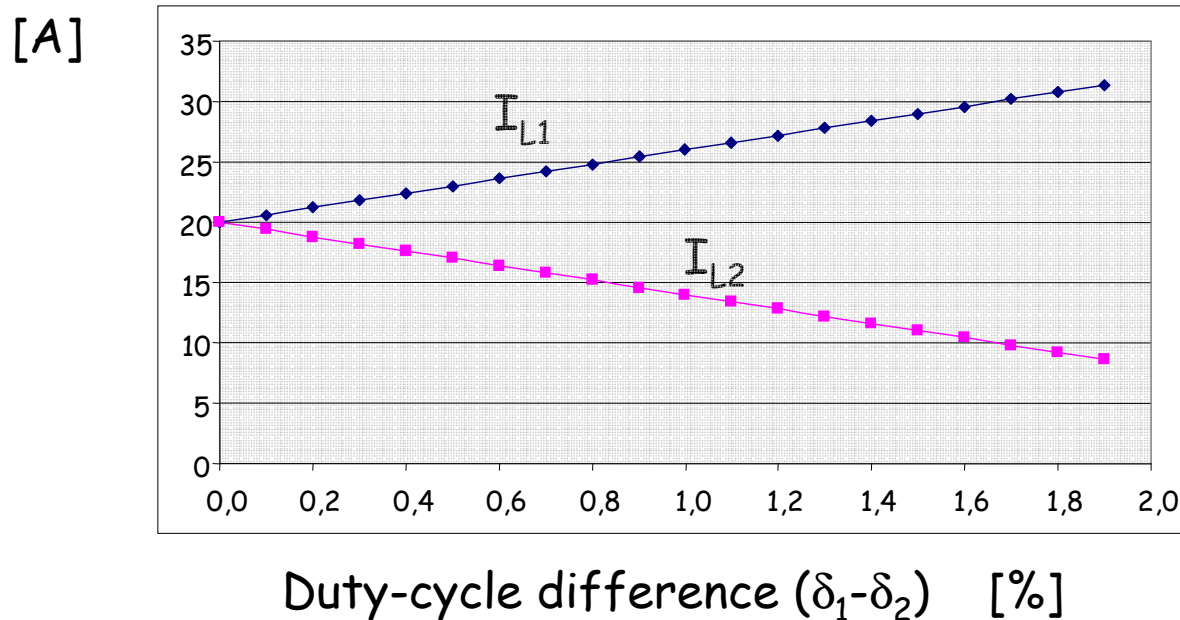$V_{in}=12V$, $R_1=R_2=10m\Omega$, $I_o=40A$, two channels



- Similar results for small unmatched channel resistances (spread of MOSFET R_{dson} , difference on PCB layout, etc..)



Outline




- **Voltage Regulation Modules (VRM)**
 - Power trend
 - Interleaved buck converters
 - Current sharing
 - **Adaptive voltage positioning**
 - Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova



VRM Intel Specifications




Specs VRD 10.x for Intel P4 Prescott

	
	VRD 10.0 – VRD 10.1
Maximum VID (Voltage Identification)	1.4V
Vcc Ratings (VID)	0.8375-1.6V
VID step	12.5mV
Vcc Tolerance Band (TOB)	± 19mV
Max Load Current	91A for VRD 10.0 115A for VRD 10.1
Voltage identification	6 bit
Over Voltage Protection	VID + 200mV (Proposed)
Over Current Protection	Not fixed (Proposed)
Maximum overshoot voltage allowed over VID	50mV
Maximum overshoot time duration over VID	25µs
Dynamic VID	Up to 61 steps (12.5mV/5µs)
dI _{OUT} /dt MAX	>50A/µs
Load Line Impedance (R _{DROOP})	1mΩ / 1.4mΩ

Resistive output impedance

$$V_{TYP,out} = VID - |TOB| - R_{DROOP} \cdot I_{load}$$

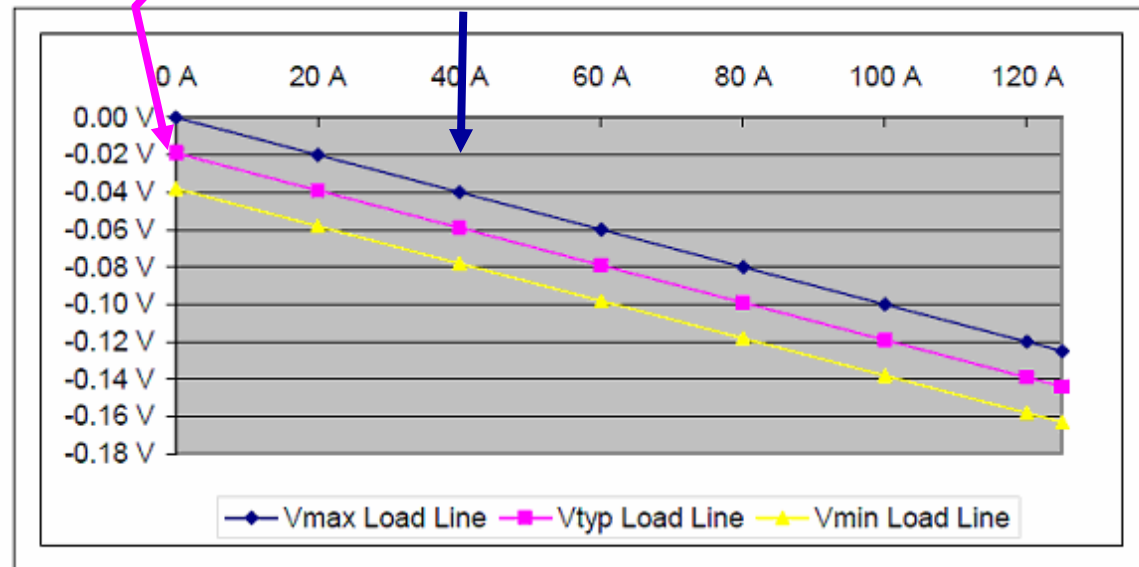

NOTE: 1: Presented as a deviation from VID

2: Socket load line Slope = 1.0 mOhms, TOB = +/-19 mV




"Droop Function" or "Adaptive Voltage Positioning"



Adaptive Voltage Positioning




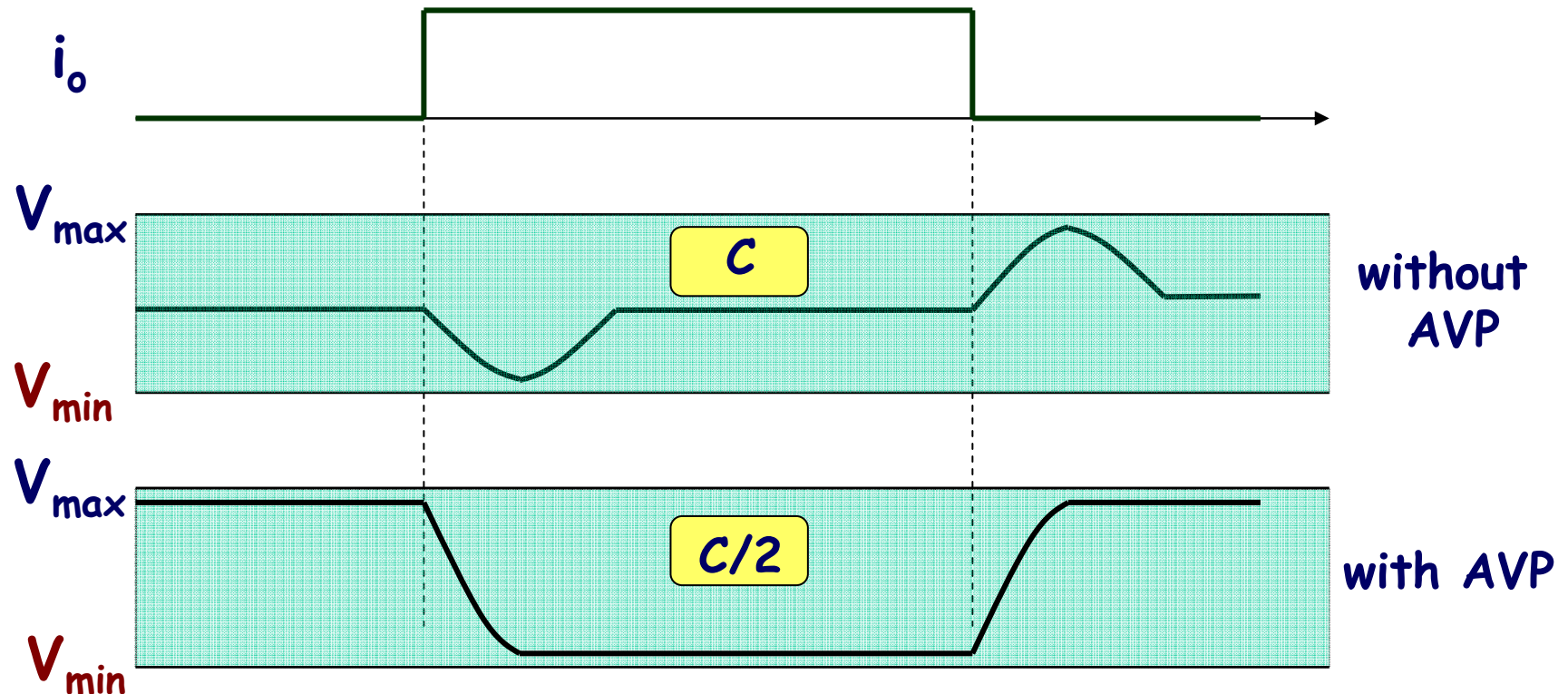- Adaptive voltage positioning (AVP) is required by VRM specs
- AVP is very effective on reducing VRM output caps:
 - For given output caps, output voltage variation is halved
 - For a given output voltage tolerance, output caps are halved




Adaptive Voltage Positioning

 - AVP is realized by VRM resistive output impedance
- Number of parallel electrolytic caps is determined by condition: $ESR = R_{\text{droop}}$




Load step variations

 


Output voltage



without Droop Function

 


with Droop Function

 


Constant Resistive Output Impedance

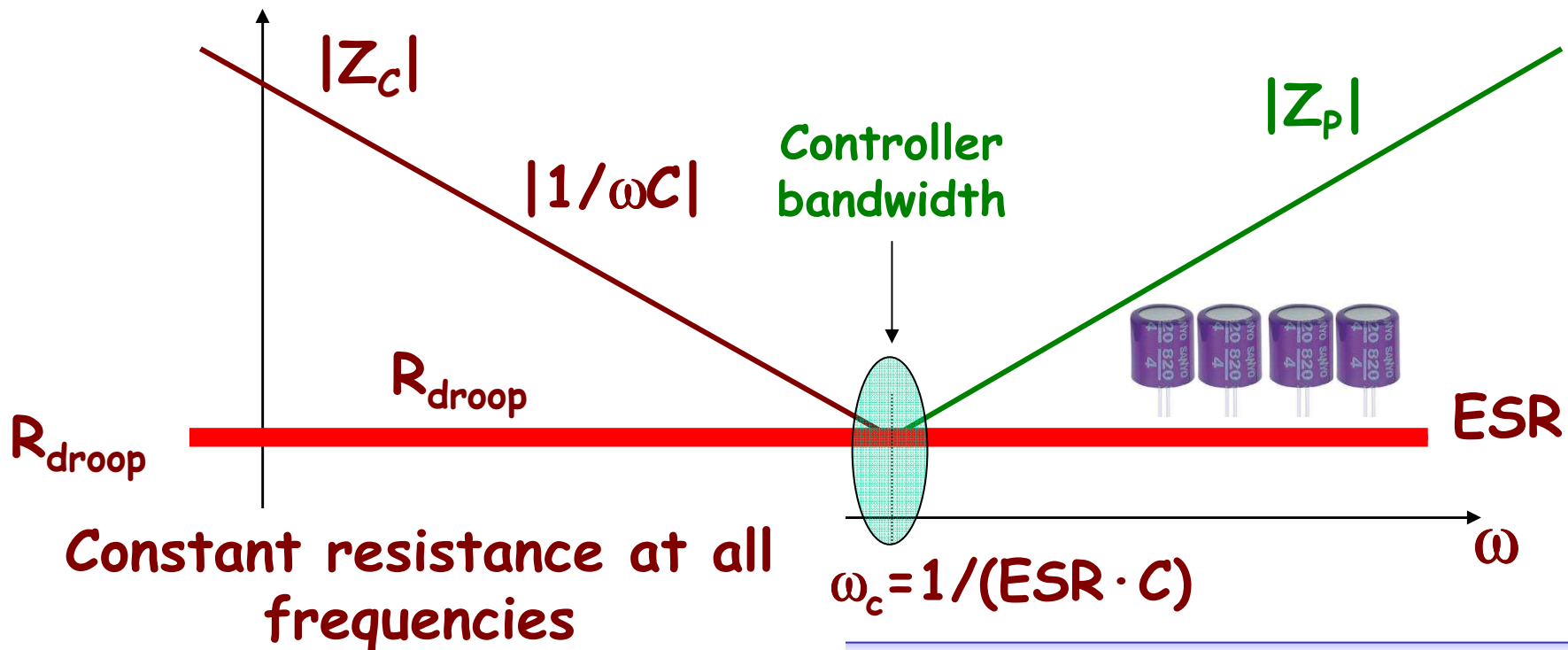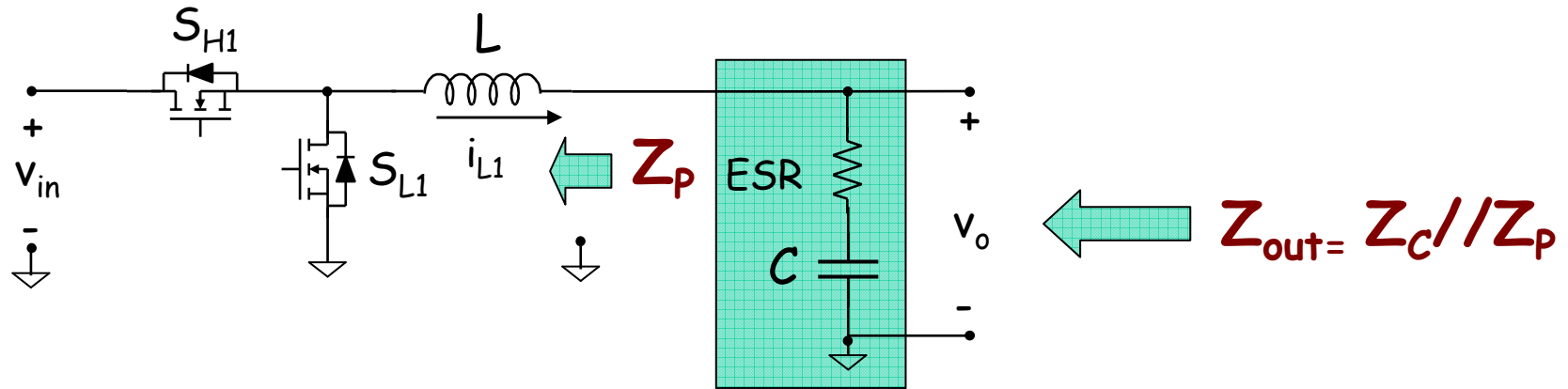

AVP: Control Block Diagram

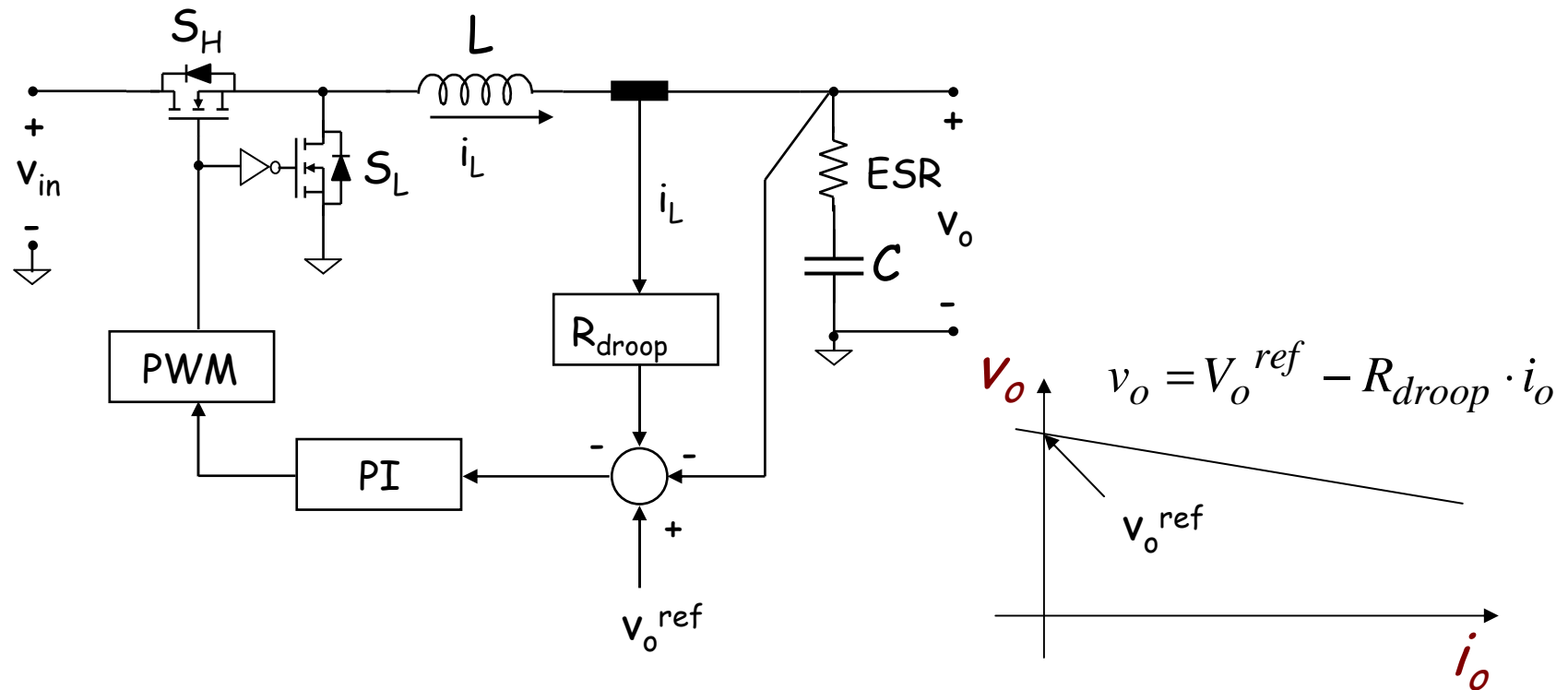

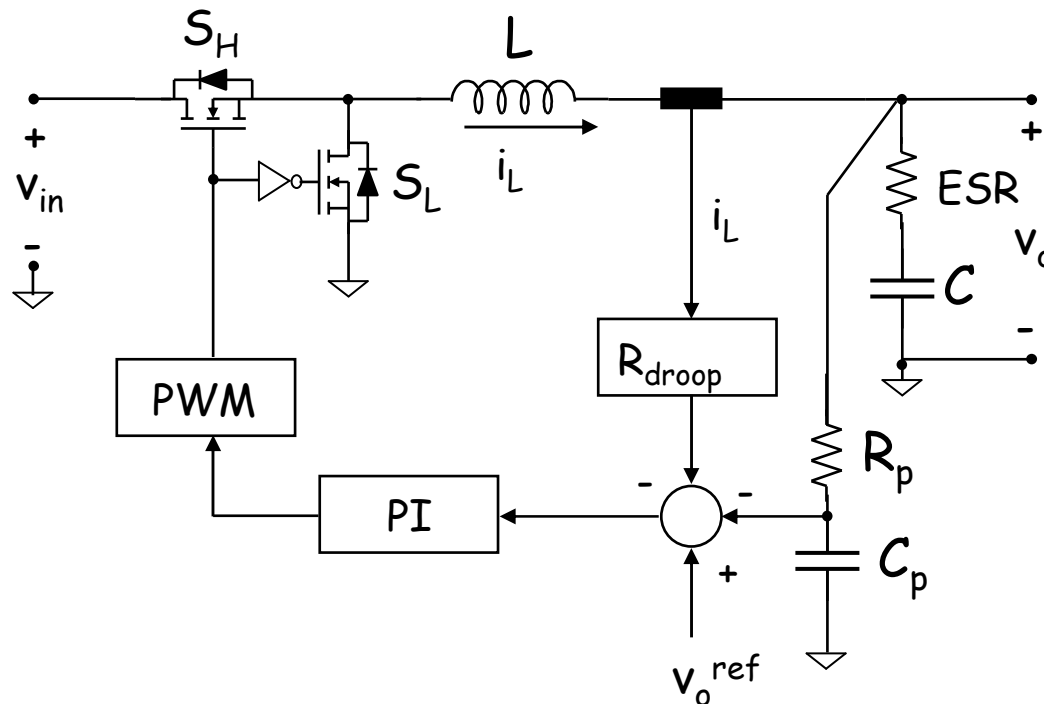
- Closed-loop control on $v_T = v_o + R_{droop} \cdot i_L$
- PI design so as to impose controller bandwidth $\omega_c = 1/(ESR \cdot C)$ (theoretically no need for high-performance controller)




- Closed-loop control on $v_T = v_o + R_{droop} \cdot i_L$
- PI design so as to impose controller bandwidth $\omega_c = 1 / (ESR \cdot C)$
- Use of an additional $R_p - C_p$ to limit **precisely** controller bandwidth


AVP with Ceramic Capacitors

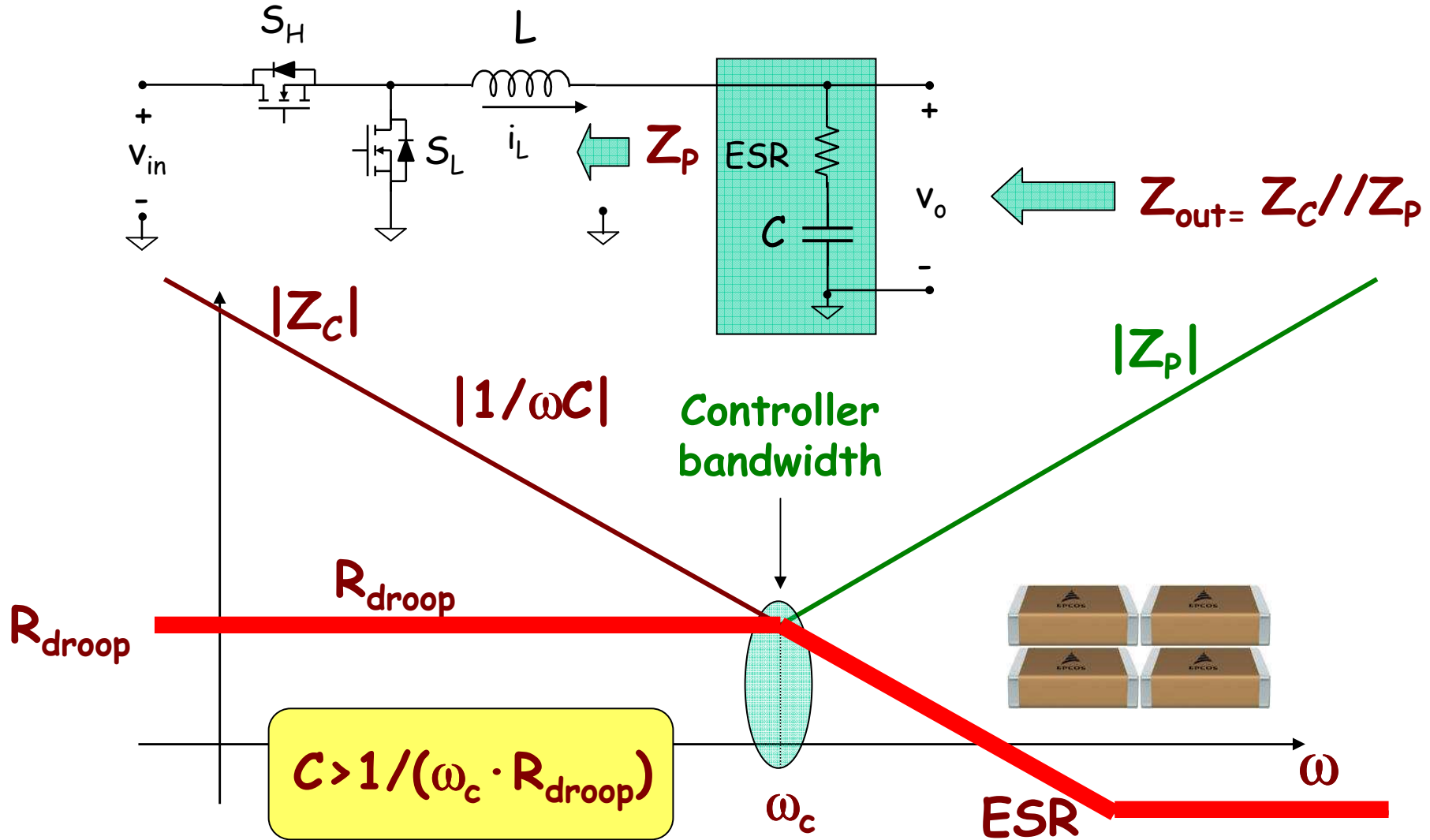- In ceramic capacitor $ESR < R_{\text{droop}}$



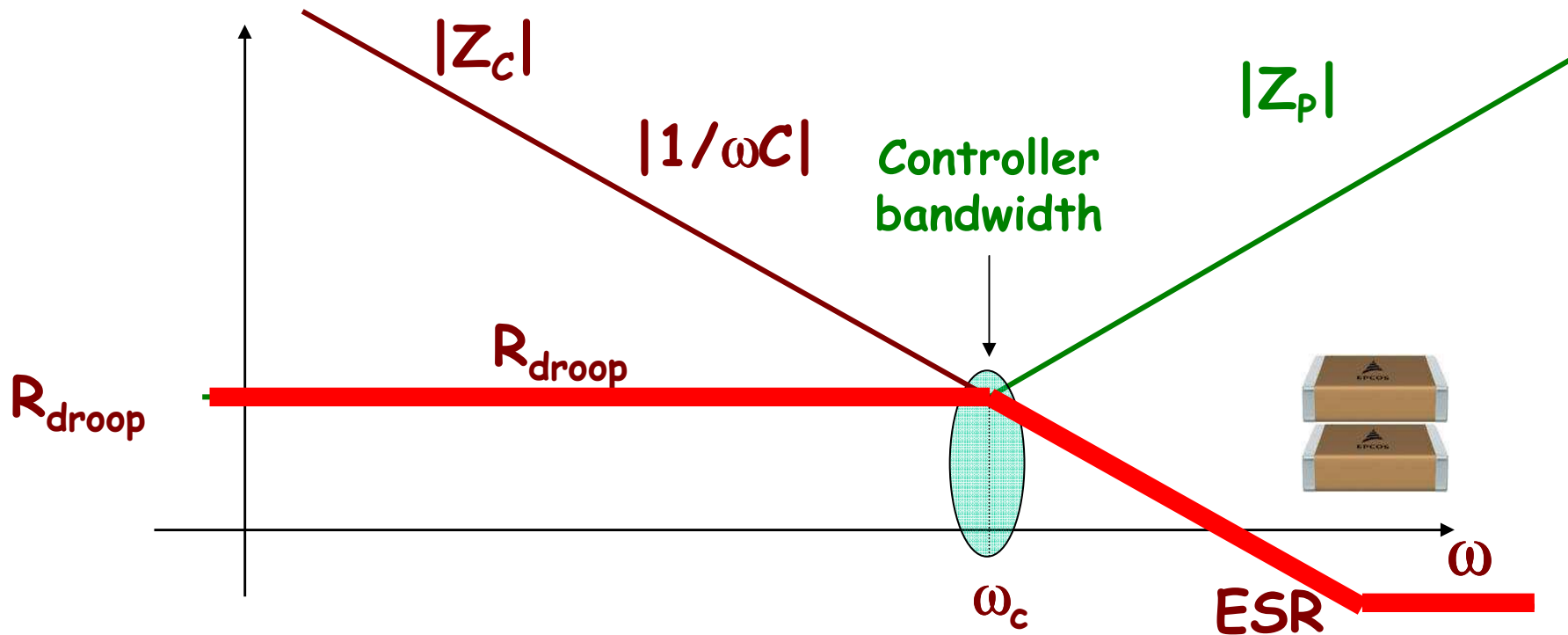- The higher the control bandwidth, the lower the output capacitor requirement: $C > 1/(\omega_c \cdot R_{\text{droop}})$
- Need for high-performance controller



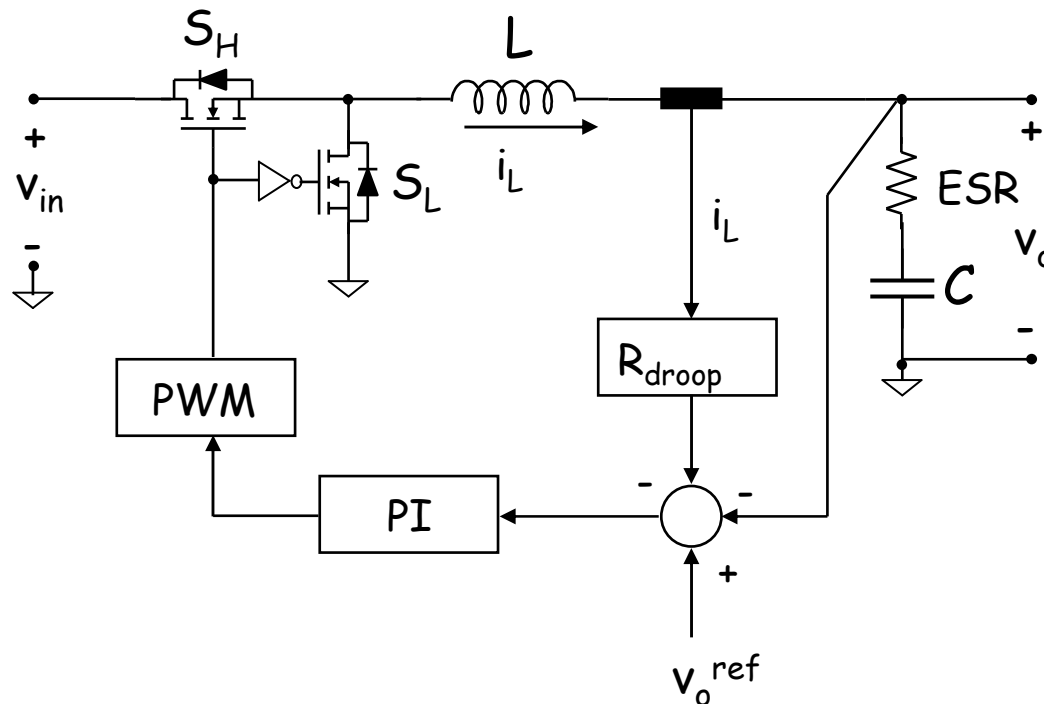

- Same scheme used for electrolytic caps
- Closed-loop control on $v_T = v_o + R_{droop} \cdot i_L$
- PI design so as to have the higher bandwidth (no limitation)



Outline



- Voltage Regulation Modules (VRM)
 - Power trend
 - Interleaved buck converters
 - Current sharing
 - Current sensing
 - Adaptive voltage positioning
- Digital control for high-frequency power conversion in Distributed Power Systems: current research activity at the University of Padova



Key Requirements



- **Tight voltage regulation**
 - Calibration for DC steady state & non linear control action for transient response
- **High level of power managing**
 - Light load efficiency
- **High level of monitoring**
 - State, I_{out} , V_{out} , Temperature and Efficiency monitoring
- **Deeply programmed fault action**




Digital Control



- Different control methods can be easily managed depending on load, input conditions and state conditions
- Offset compensation and/or auto-tuning features can be added
- Non linear response can easily be achieved
- Complex power management algorithms can be implemented

 - Complex control algorithms can be easily implemented to obtain good response



Accuracy

- Built in test for offset compensation
- Adaptive control system
- Non linear response



Digital Control




- Compensation software assisted:
 - No components used for compensation
 - Easy changing compensation, droop and settings by software
 - Auto-tuning techniques

- Technology independent design
(Hardware Description Language - HDL)

Better resources
employment

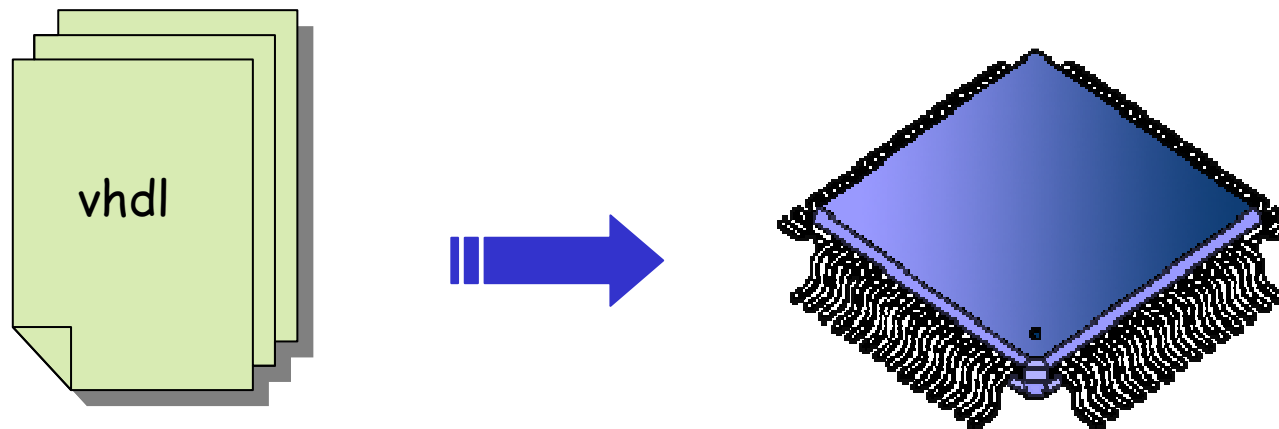- Lower Time to market (faster design process)
- Intellectual Property - IP
- Easy scaling with advances in fabrication technologies





Critical Issues of Digital Control



- *Lack of experienced people* in digital design and power electronics
- *Lack of understanding* and research on how to realize simple digital IC which comply with the cost/complexity constraints of computing/telecom applications
 - Specific dedicated digital or mixed-signal ICs are needed (no discrete uC or DSP)
- Quantization effects (limit cycles) and control delays (bandwidth limitation) has to be considered
- Conversion solutions and digital complexity
 - High resolution DPWM
 - High resolution AD and DA converters




Need of simple-mixed signal control architectures



Research Activities in Digital Control



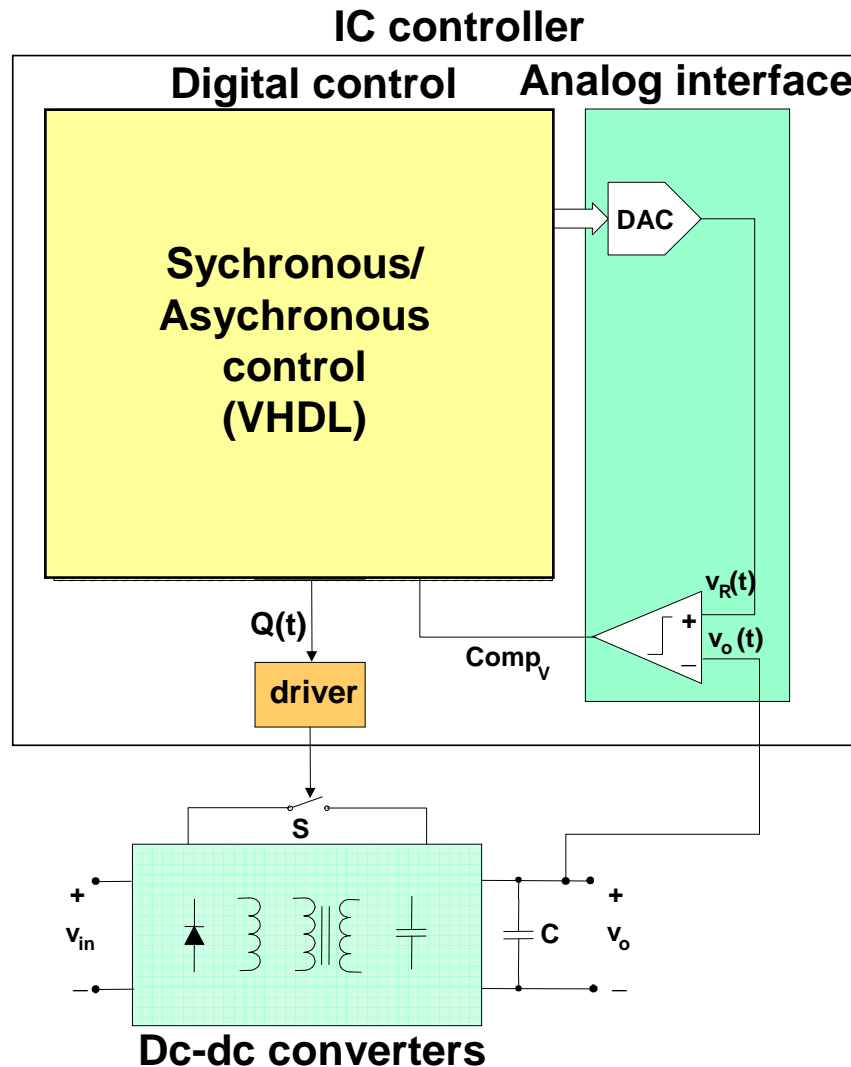
- Investigating the digital advantage
 - Auto-tuning systems
 - Complex power management
- Solving the digital trouble
 - Mixed signal control architectures




Features:

- ✓ Simple analog interface (low-resolution DAC + comparator)
- ✓ No need for ADC and DPWM
- ✓ No quantization effects
- ✓ High dynamic performance


DAC operation

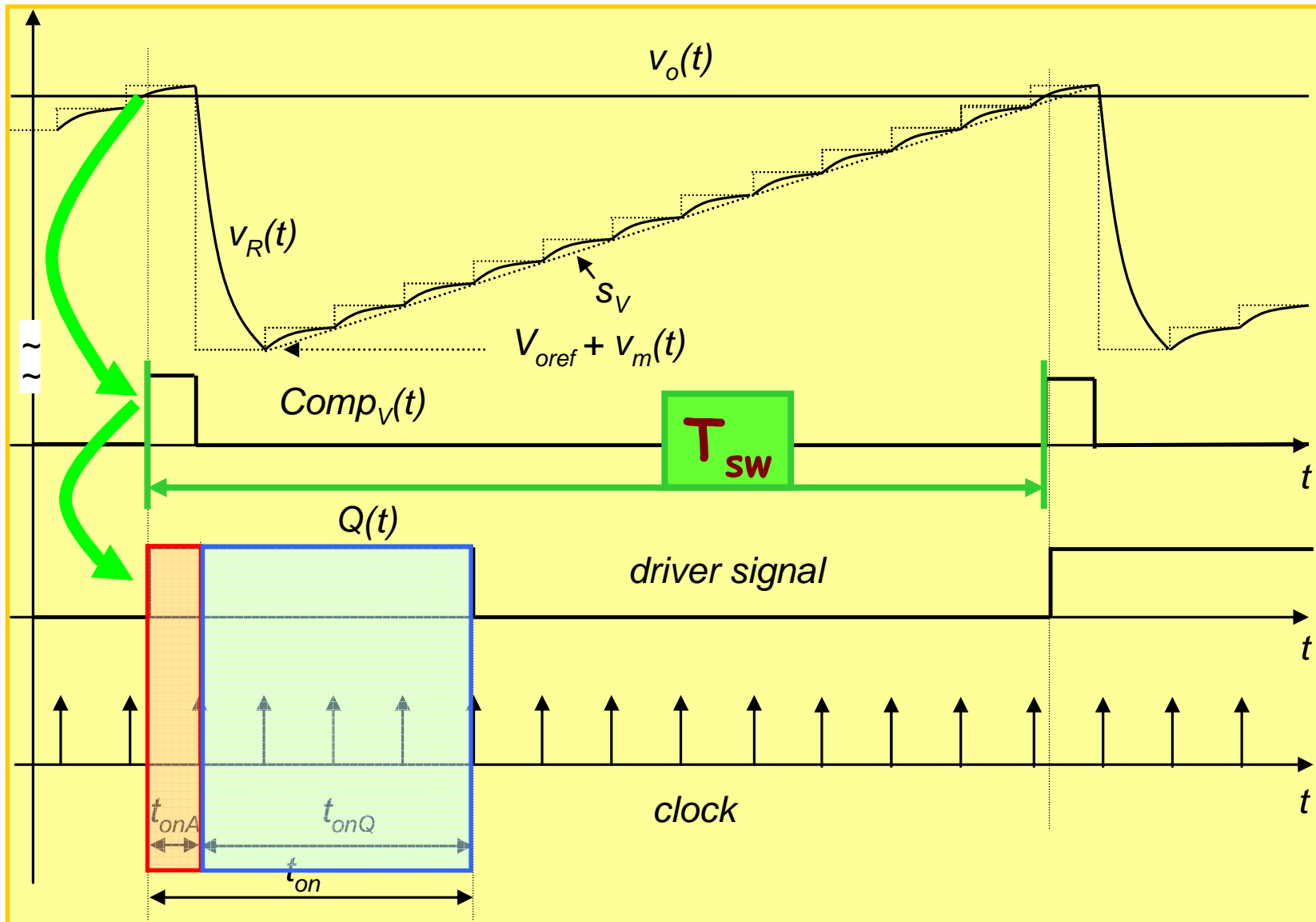

Load step variation

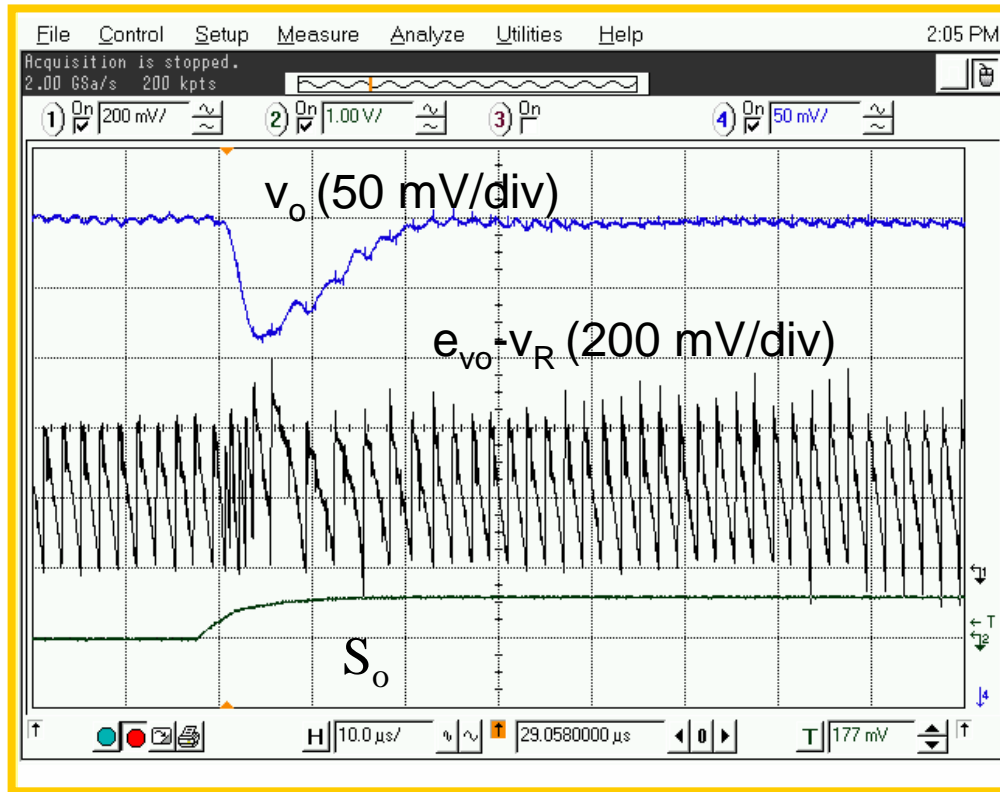

time: 10 μ sec/div

 




Auto-Tuning System



Objective:


- Investigation of **PID autotuning techniques** for digitally controlled voltage-mode synchronous buck converters
- **Features:**
 - ✓ **Closed-loop operation during autotuning**
 - ✓ Direct autotuning based on specified dynamic requirement without transfer function identification
 - ✓ Simple algorithm

Experimental Results

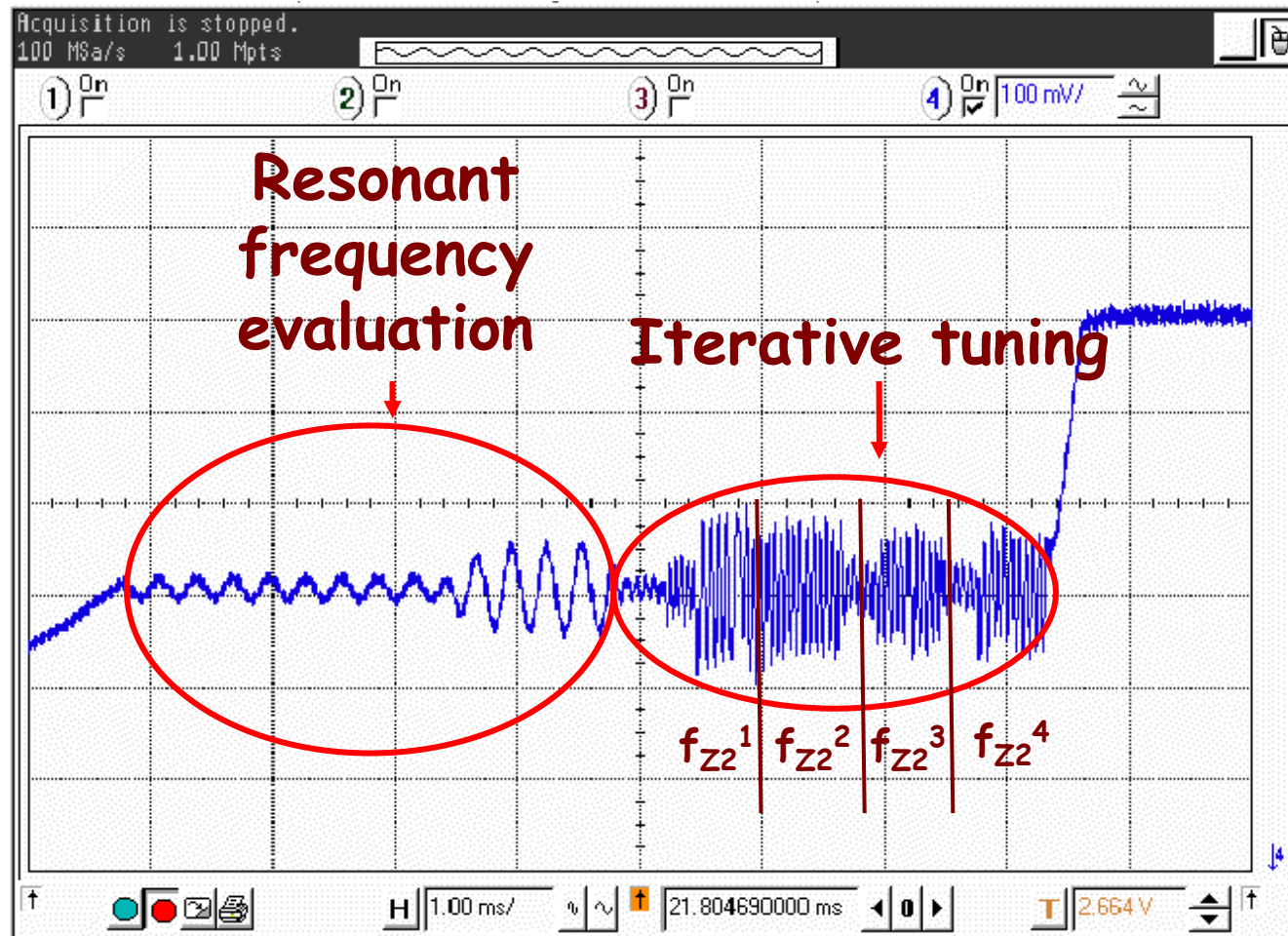

Experimental Results

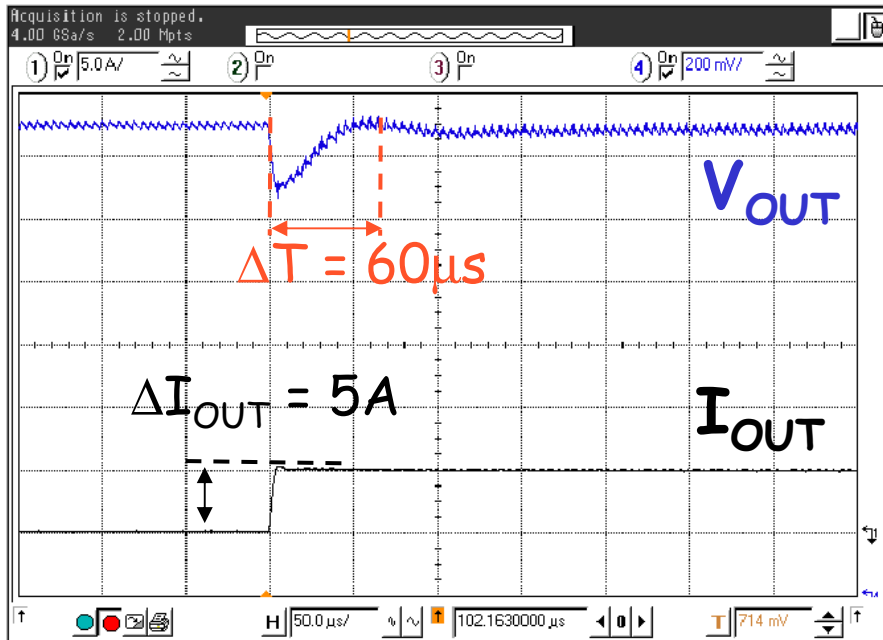
Load step variation after autotuning
($f_c = 13\text{kHz}$, $m_\phi = 60^\circ$)



$C_O = 660\mu\text{F}$

Tantalum caps


$C_O = 1320\mu\text{F}$

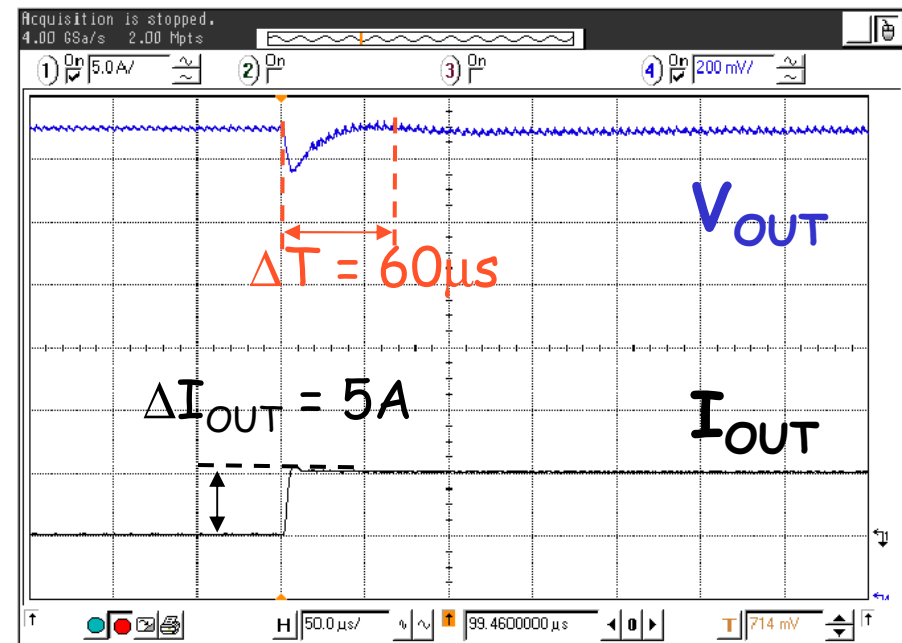



Power Line Communication

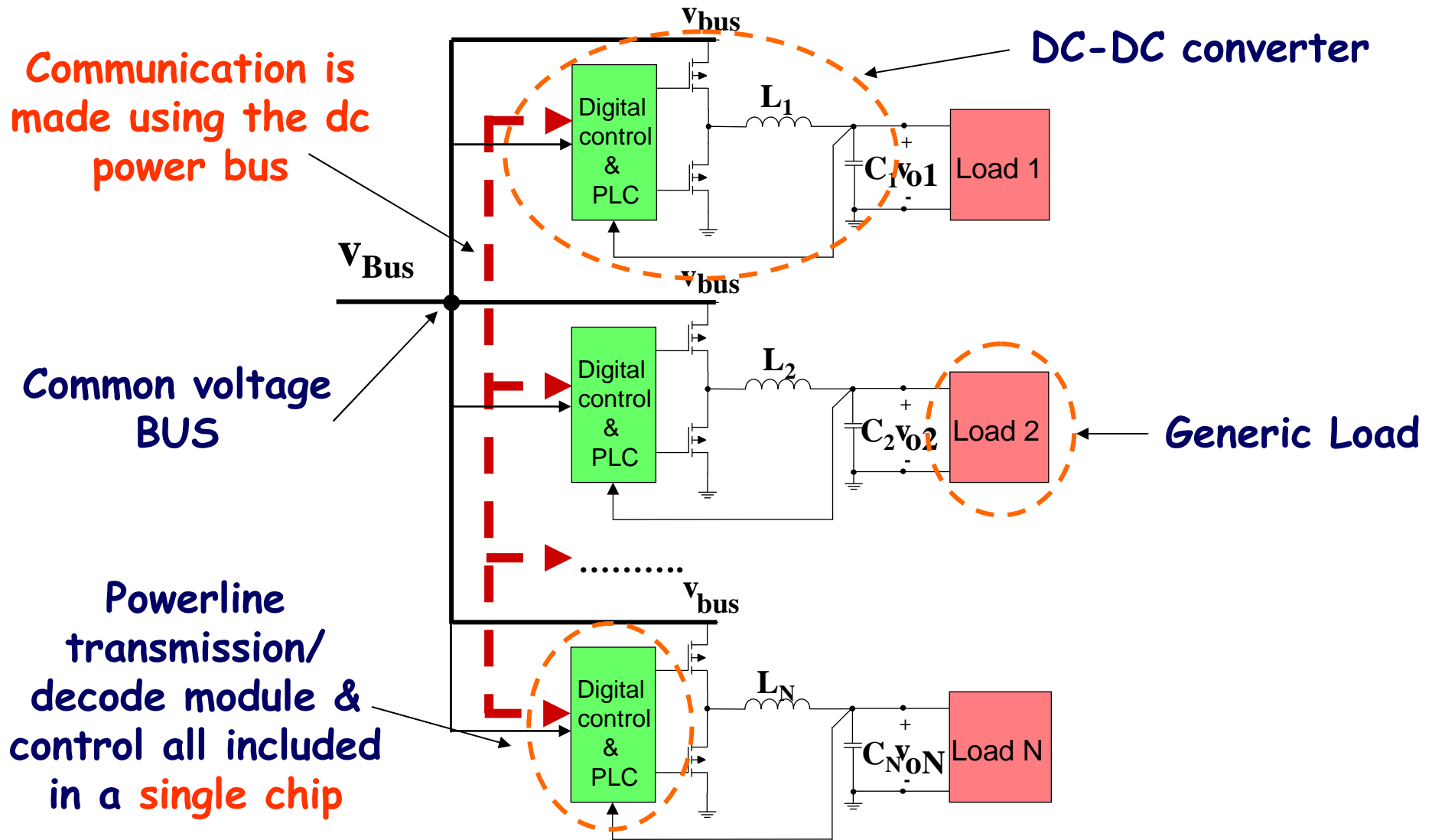Distributed dc-dc converters sharing the same voltage bus






16-Phases Interleaved Buck Converter



- High number of phases enables higher switching frequencies and lower L
- The requirement for precise timing and automatic current sharing call for digital control
- Prototype
 - 16 Phases Buck converter
 - 1.56 MHz Switching Frequency (each channel)
 - ≈ 25 MHz Sampling Frequency
 - $V_{in} = 3$ V
 - $V_{out} = 1$ V, $I_{out} = 8$ A
 - $q_{ADC} = 16$ mV
 - $L = 300$ nH
 - $C_{out} = 30$ μ F

 Project in which our Ph.D student (Daniele Trevisan) was involved during his visit at COPEC (Colorado Power Electronics Center) - Boulder





Thank you for your attention!