

# A 130nm CMOS Evaluation Digitizer Chip for Silicon Strips readout at the ILC

**Jean-François Genat**

on behalf of

J. David<sup>2</sup>, M. Dhellot<sup>2</sup>, D. Fougeron,<sup>1</sup> R. Hermel<sup>1</sup>, J-F. Huppert<sup>2</sup>,  
H. Lebbolo<sup>2</sup>, R. Sefri<sup>2</sup>, T.H. Pham<sup>2</sup>, F. Rossel<sup>2</sup>, A. Savoy-Navarro<sup>2</sup>.

*<sup>1</sup>LAPP Annecy, <sup>2</sup>LPNHE Paris*

***TWEPP Workshop, Sept. 3d-7th 2007  
Prague***

# Outline

- Silicon strips data
- Goals in 130nm CMOS
- Present results
- Chip 2 and further tests
- Next chip

# Silicon strips data at the ILC

- **Pulse height:** Cluster centroid to get a few  $\mu\text{m}$  position resolution  
10cm-1m long strips, possibly strixels  
Shaping time of the order of the microsecond  
  
Detector pulse analog sampling at 10-20MHz
- **Time:** 150-300 ns for BC identification,
- **Buffering:** Occupancy implies a few events per strip  
8-16 deep event buffer/strip
- **Power cycling:** 1 ms data taking at 5 Hz

Millions of channels:  
Integration of k-scale channels readout chips

# Outline

- Silicon strips data
- **Goals in 130nm CMOS and present Chips**
- Present results
- Chip 2 and further tests
- Next chip

# Goals and Status

Full readout chain integration in a single chip  
including digitization

	This chip
- Preamp-shaper	yes
- Zero-suppression decision (threshold analog sums)	yes
- Pulse sampling: Analog pipe-lines	yes
- On-chip digitization: ADC	yes
- Multi-event Buffering and pre-processing: Centroids, least squares fits	no
- Lossless compression and error codes	no
- Calibration and calibration management	no
- Power switching (ILC timing)	no
	4 channels

Future:

CMOS 90nm	128 ch.	2008
512-1024 channels planned		2009

# Targeted numbers

- Amplifier: 30 mV/MIP gain
- Shaper: 700ns-3  $\mu$ s
- Sparsifier: Threshold on analog sum  
auto-zero
  
- Sampler: 16-deep
- Event buffer 16-deep
- ADC: 10-bit, 10KHz
  
- Noise:

Measured with 180nm CMOS:

375 + 10.5 e-/pF @ 3  $\mu$ s shaping, 210 $\mu$ W power

# Front-end in 130nm

## 130nm CMOS:

- Smaller
- Faster
- Less power
- Will be (is) dominant in industry
- (More radiation tolerant)

## Drawbacks:

- Reduced voltage swing (Electric field constant)
- Noise slightly increased ( $1/f$ )
- Leaks (gate/subthreshold channel)
- Design rules more constraining
- Models more complex, not always up to date

# UMC CMOS Technology parameters

	180 nm	130nm
• 3.3V transistors	yes	yes
• Logic supply	1.8V	1.2V
• Metals layers	6 Al	8 Cu
• MIM capacitors	1fF/mm <sup>2</sup>	1.5 fF/mm <sup>2</sup>
• Transistors	Three Vt options	Low leakage option

Used for analog storage during < 1 ms





# 2006-7 Chips

## 130nm CMOS

Both under test


Chip #1 (4 channels)

- Preamp-shapers + Sparsifier
- Pipeline 1
- ADC
- Digital

Chip #2 (One channel)

- Preamp-shapers + Sparsifier
- DC servo
- Pipeline 2 (improved)
- DAC
- Test structures: MOSFETS, passive

# 4-channel Chip

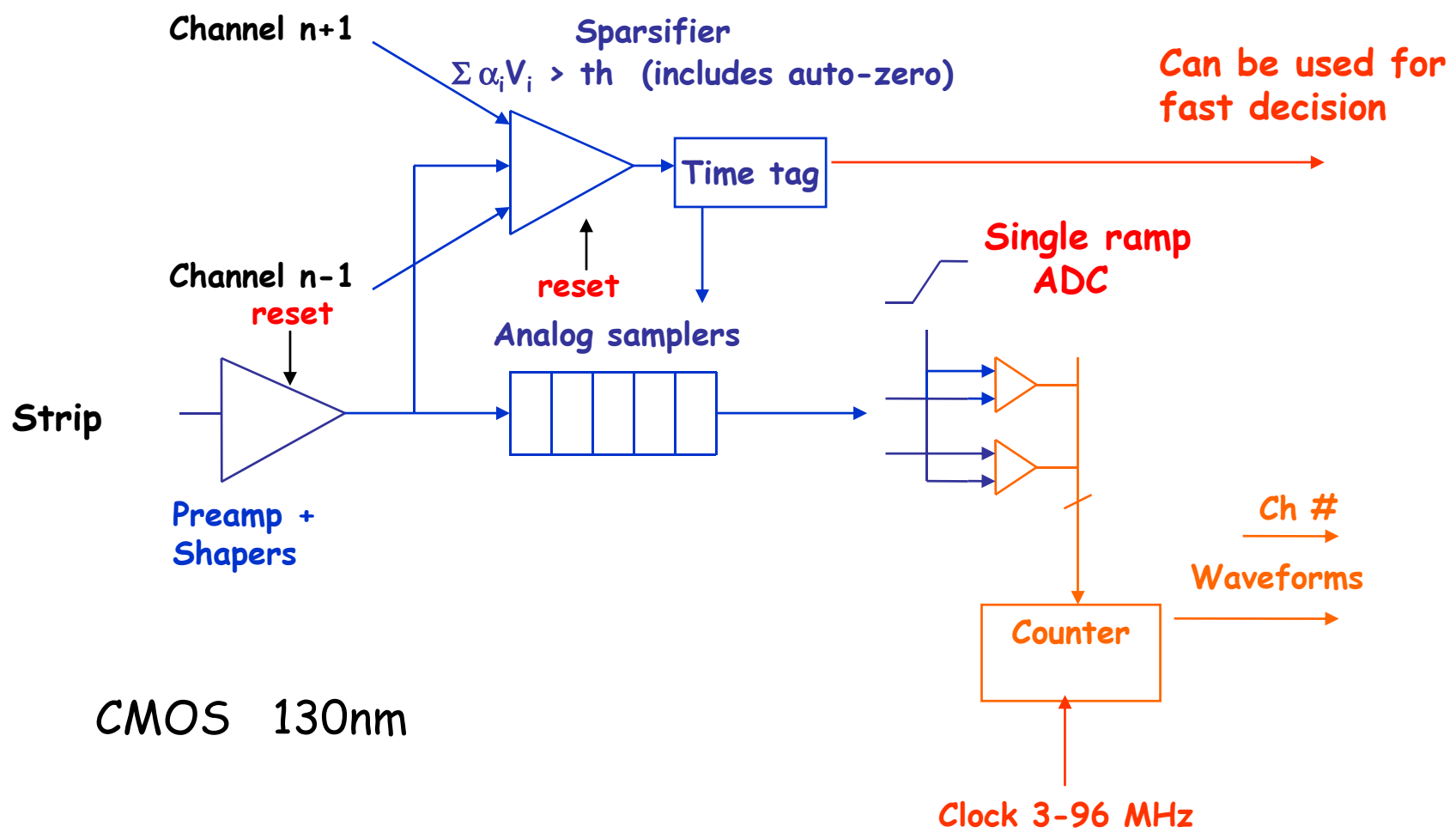


CMOS 130nm
 
# 4-channel chip layout

Amplifier, Shaper, Sparsifier  $90 \times 350 \mu\text{m}^2$


Analog sampler  $250 \times 100 \mu\text{m}^2$




A/D  $90 \times 200 \mu\text{m}^2$

Layout of the 130nm chip including sampling and A/D conversion


# 4-channel 130nm Silicon

 

180nm 130nm

 

 Layout of the 130nm chip including sampling and A/D conversion



Picture




# Outline

- Silicon strips data
- Goals in CMOS 130nm and present chips
- Present results
- Chip 2 and further tests
- Next chip

# Results

## Measured gain - linearities

Preamp output

   

Preamp and Shaper:


Gain = 29mV/MIP  
 Dynamic range = 20MIPs 1%  
 30 MIPs 5%

Peaking time = 0.8-2.5µs / 0.5-3µs expected

Shaper output
 
# 130nm vs 180nm chip noise results



Gain OK: 29 mV/MIP OK  
 Dynamics: 30 MIPS @ 5%, 20 MIPS 1% OK  
 Peaking time: 0.8 - 2.5  $\mu$ s (0.7 - 3  $\mu$ s targeted)



Power (Preamp+ Shaper) = 245  $\mu$ W

Noise:	130nm @ 0.8 $\mu$ s :	850 + 14	e-/pF	245 $\mu$ W	(150+95)
	130nm @ 2 $\mu$ s :	625 + 9	e-/pF		
	[ 180nm @ 3 $\mu$ s :	375 + 10.5	e-/pF	210 $\mu$ W	(70+140) ]

# Digitized analog pipeline output

 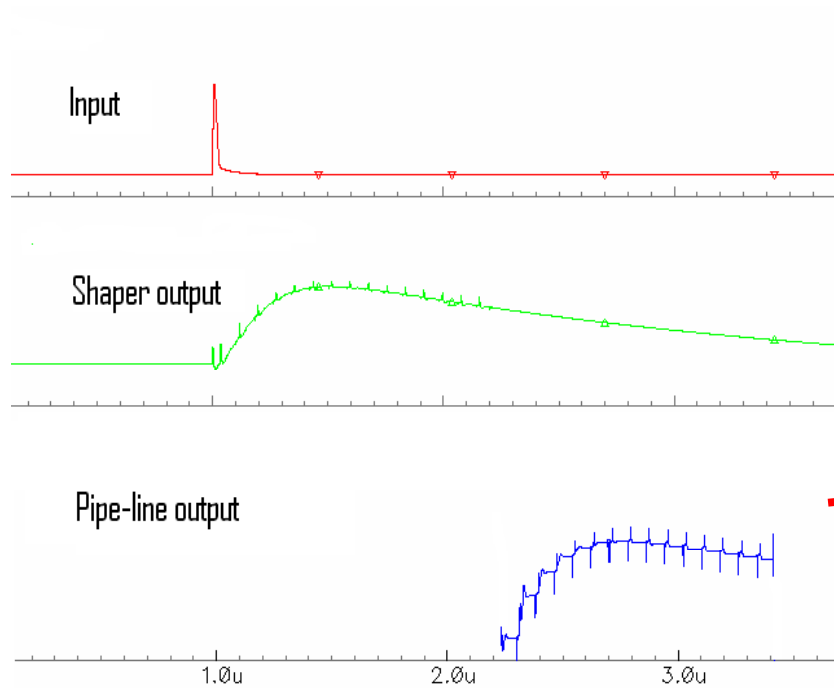

**Simulation** of the analog pipeline (analog)

**Measured** output of the ADC (pulser)

Waveform distorted due to 1pF parasitic capacitance of the output pad connected for analog diagnostics on 2 out of four channels

Traces cut using IFB to get all shaper channels operational to ADC for beam tests


Chip 2 includes a voltage buffer between shaper and ADC




# Digitized analog pipeline output

## Laser response of detector + 130nm chip

Digitized shaper output


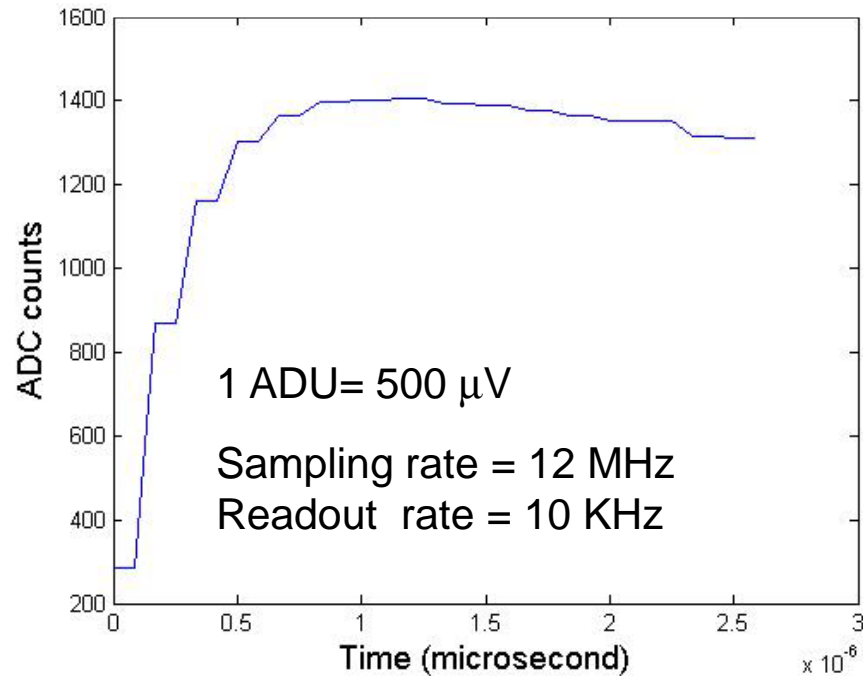


From pulser

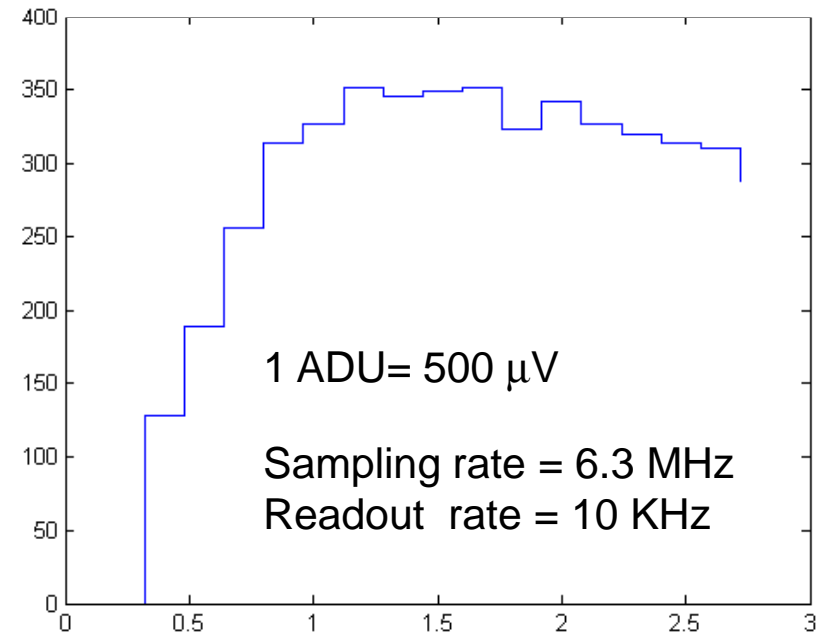

From Laser diode + Silicon detector

# ADC first look...

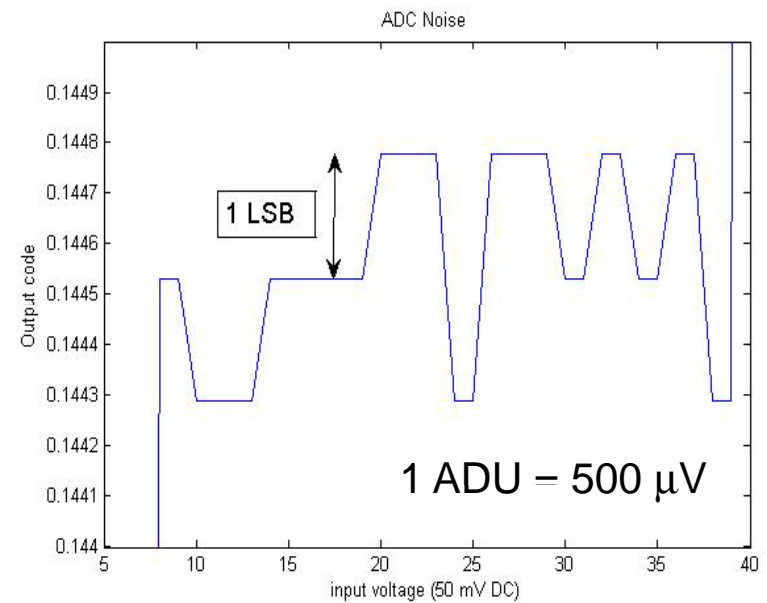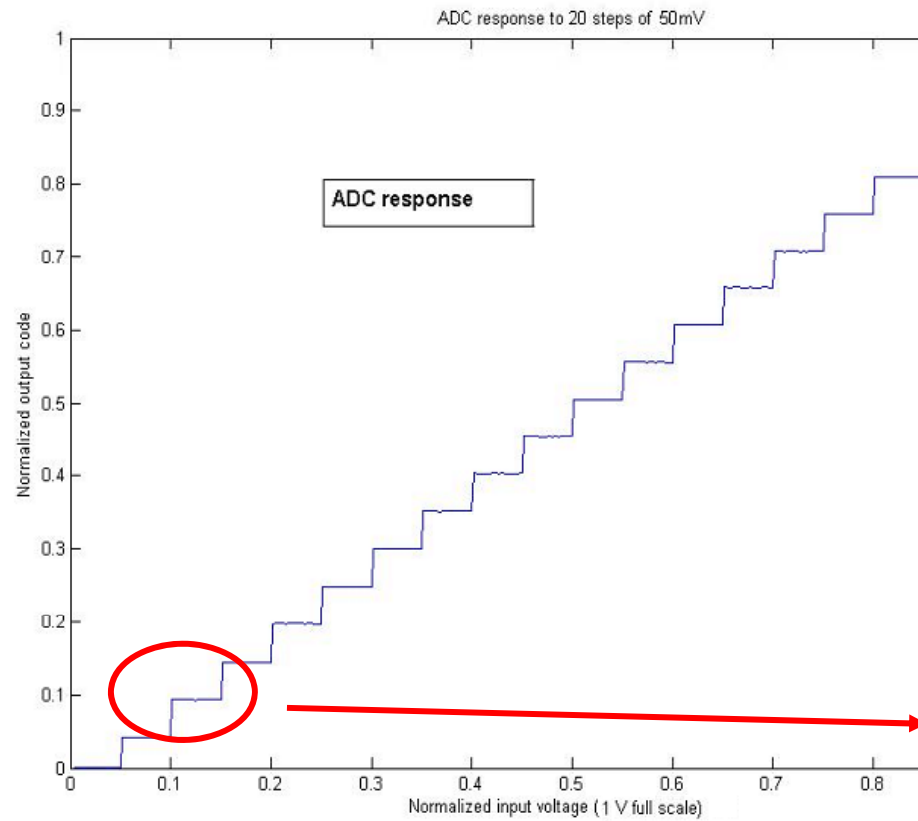

# 130nm Chip 2

LAPP Annecy le Vieux ( R.Hermel, D. Fougeron )

One channel test version in 130nm including:

- Preamp + shaper
- Improved pipeline (output buffer)
- Calibration channel (calibration caps)
- Calibration DAC

Chips 2 presently under test

If OK, all analog blocks will be validated for a multi-channel version in 130nm aiming to read a real detector in 2008

# 130-1 chip's tests to come

- Lab tests: Measure ADC extensively

- Linearities      Integral, differential
- Noise            Fixed pattern, random
- Speed            Maximum clock rate
- Accuracy        Effective number of bits

- Next beam tests at CERN end October

# Outline

- Silicon strips data
- Goals in CMOS 130nm
- Present results
- **Chip 2 and further tests**
- Next chip

# 130-2 tests under work (LAPP Annecy)

Measure improved pipeline extensively

Denis Fougeron's (LAPP) design

Linearities

Integral, differential

Noise

Pedestal fixed pattern, random noise

Maximum clock rate

Droop

Hold data for 1 ms at the ILC

# Outline

- Silicon strips data
- Goals in CMOS 130nm
- Present results
- Chip 2 and further tests
- Next chip

# Chip 130nm-3


## Equip a detector

- Experience from lab test bench (laser + source) and 2007 beam-test
- 128 channels with :
  - Preamp-shapers + sparsifier
  - Pipeline
  - ADC
  - Digital
  - Calibration
  - Power cycling


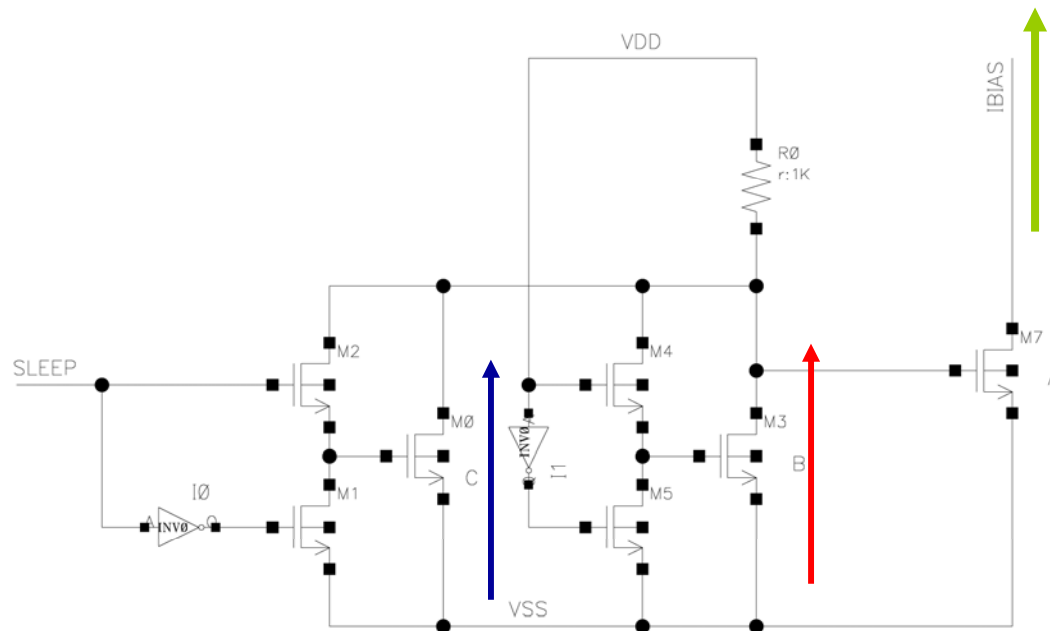
# Power cycling

Switch the current sources between zero and a small fraction ( $10^{-2}$  to  $10^{-3}$ ) of their nominal values



This option switches the current source feeding both the preamplifier & shaper between 2 values:

*Zero* or a *small fraction* (0.1% - 1%) of biasing current is held during « power off ».

Zero-power option tested on 180nm chip

# Planned Digital Front-End

- Chip control
- Buffer memory
- Processing for
  - Calibrations
  - Amplitude and time least squares estimation, centroids
  - Raw data lossless compression
- Tools
  - Cadence DSM Place and Route tool
  - Digital libraries in 130nm CMOS available
  - Synthesis from VHDL/Verilog
  - SRAM
  - Some IPs: PLLs

Need for a mixed-mode simulator

# Some issues with 130nm design

- Noise likely modeled pessimistic, but measured quite acceptable  
90nm could be less noisy (Manghisoni, Perugia 2006)
- Lower power supplies voltages reducing dynamic range
- Design rules more constraining
- Some (via densities) not available under Cadence  
Calibre (Mentor) required.
- Low Vt transistors leaky (Low leakage option available at regular Vt)



Manageable, UMC design kits user friendly,  
Europractice very helpful.

# 130-90nm noise evaluation (STM process)



## Noise and inversion region

*Manghisoni et al FE2006 Perugia*

  

- At low drain current both devices work in the weak inversion region → channel thermal noise is roughly the same for both devices
- At high drain current, a significant difference in the channel thermal noise can be detected ← device from the 90 nm technology works closer to weak inversion region
- Better 1/f noise performance provided by the STM 90 nm technology

# Conclusion

These CMOS 130 designs and first test results demonstrate the feasibility of a highly integrated front-end for Silicon strips (or large pixels) with

- DC power under  $500\mu\text{W}/\text{ch}$
- Silicon area under  $100 \times 500 \mu^2/\text{ch}$

*The End ...*