

# Switched Capacitor DC-DC in FE-I4

Dario Gnani<sup>1</sup> (design), Yunpeng Lu<sup>2</sup> (measurement and talk), Weiguo Lu<sup>2</sup> (simulation)

1-Lawrence Berkeley National Laboratory

2-Institute of High Energy Physics, Beijing


March 8th, 2011

# FE-I4 Introduction


- Designed in a 130nm feature size bulk silicon process.
  - Chip size:  $2\text{cm} \times 1.9\text{cm}$
  - Pixel array:  $80\text{col} \times 336\text{row}$  (26,880 pixels)
  - Pixel size:  $250\mu\text{m} \times 50\mu\text{m}$
  - For each pixel: free running CSA + shaping + discriminator
  - Sophisticated digital logic processing "firing time" and "time over threshold(TOT)" of each pixel, and transmitting data out of the chip via a pair of 160Mb/s differential signals.
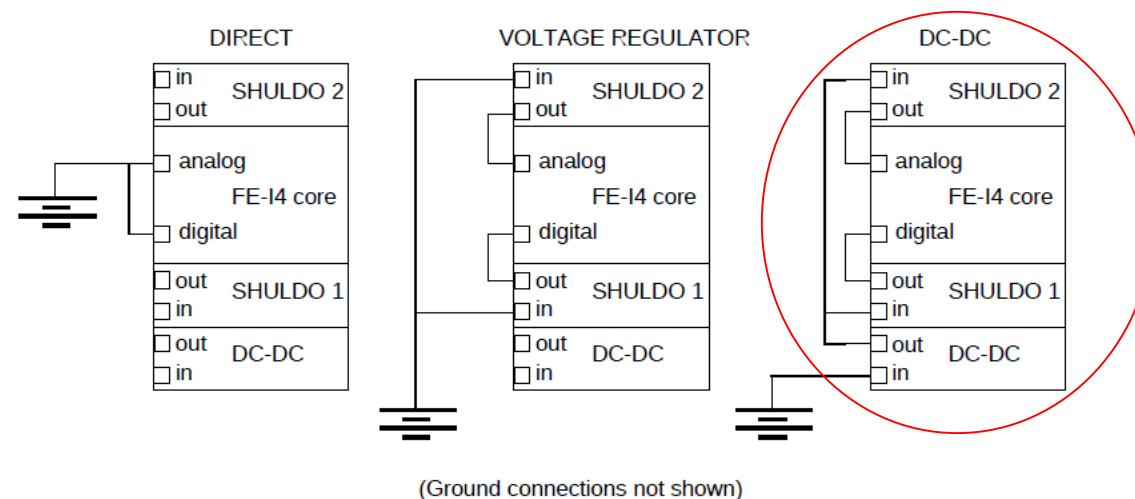
# Power Options for FE-I4

- Basically the power rail inside FE-I4 are divided into 4 groups and attached to separate pads:
  - **VDDD1/GNGD1**, **VDDD2/GNDD2**, **VDDA1/GNDA1**, **VDDA2/GNDA2**
  - In addition dedicated power nets for PLL, EFUSE and T3 isolation as well.
- 3 isolated power modules in the chip.
  - Two linear-shunt LDOs(ShuLDO)-> **Laura's talk.**
  - One switched capacitor DC-DC converter-> **this talk.**
  - Neither is hard-wired inside the chip. Thus Wire connections outside the chip needed.





# Power Modules in FE-I4 Layout

 

**FE-I4A Layout**

**DC-DC &  
ShuLDO1**

  


**ShuLDO2**

**Magnification of  
DC-DC & ShuLDO1**

**250um pads for power  
modules while 100um  
pads for signals**

DCDC\_IN  
Cpump1  
Cpump2  
REG1\_IN  
REG1\_OUT  
REG\_GND


# DC-DC configuration in FE-I4

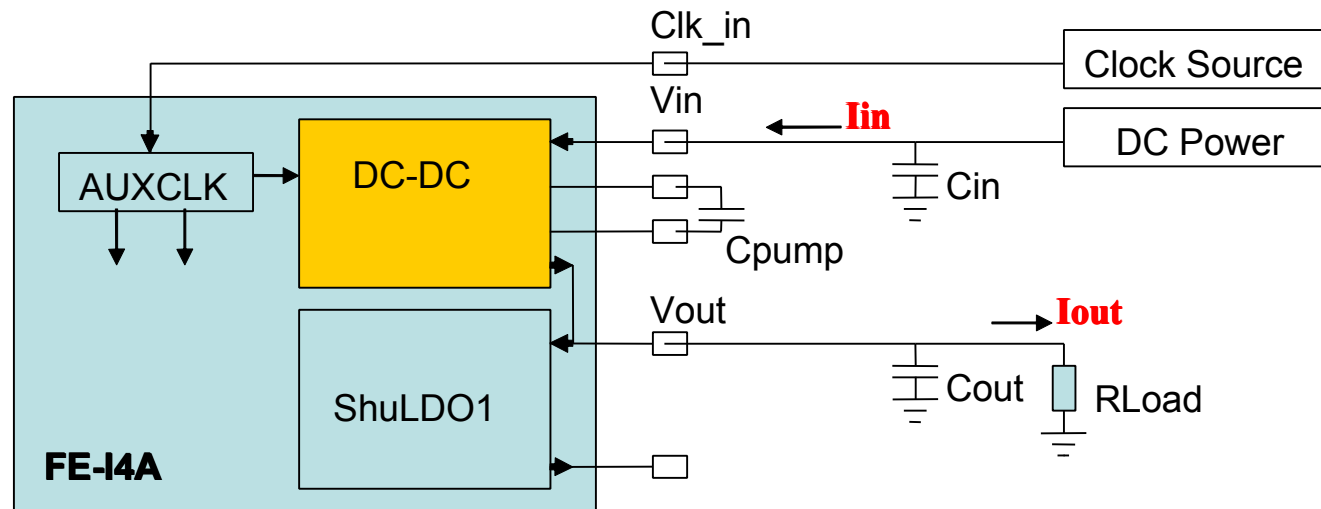

- CLOCLK is provided from outside the chip. This clock also serves as auxiliary clock for the chip.
- Ceramic capacitors used for the test. Cpump is mounted on the board as close to the chip as possible.
- DCDC\_OUT and ShuLDO1\_IN are connected in the chip and share the same pad.
- As a "divide-by-two" converter, ideally:  $I_{out}=2I_{in}$  &  $V_{out}=V_{in}/2$ .

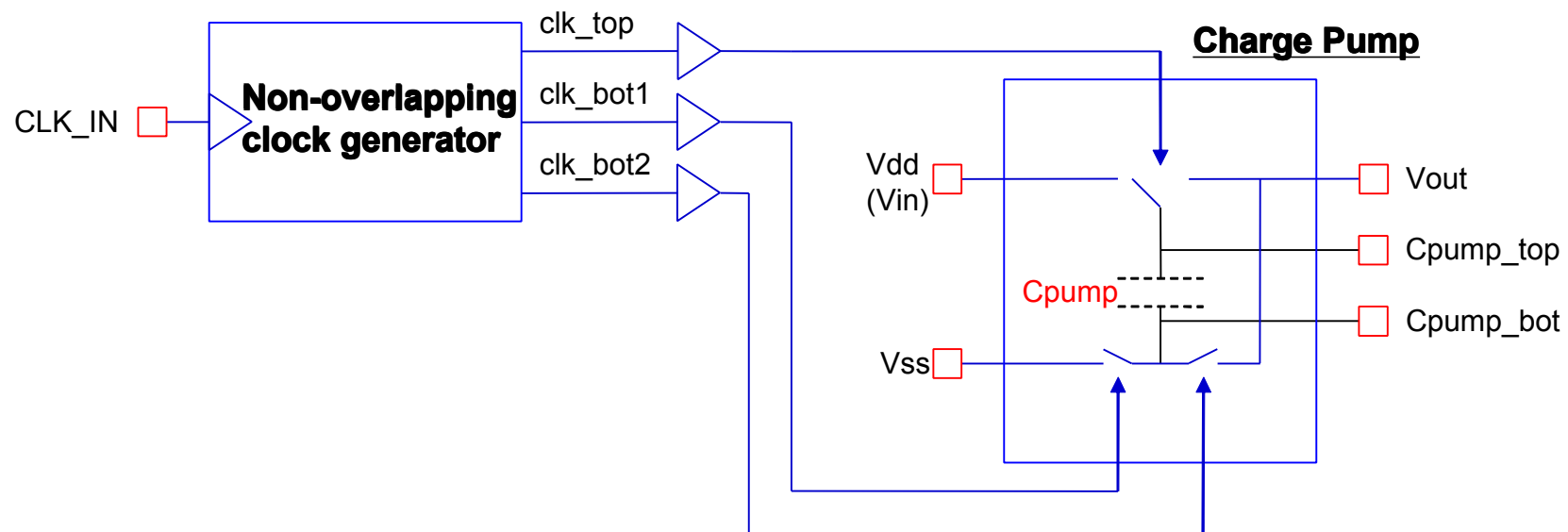
# DC-DC Schematic Diagram

- Non-overlapping Clock generator:
  - generates 3 internal clock signals from CLK\_IN
  - the same frequency but different phase.
- Charge pump:
  - consists of 4 transistors working as switches
  - manipulates the pump capacitor under control of clock signals.


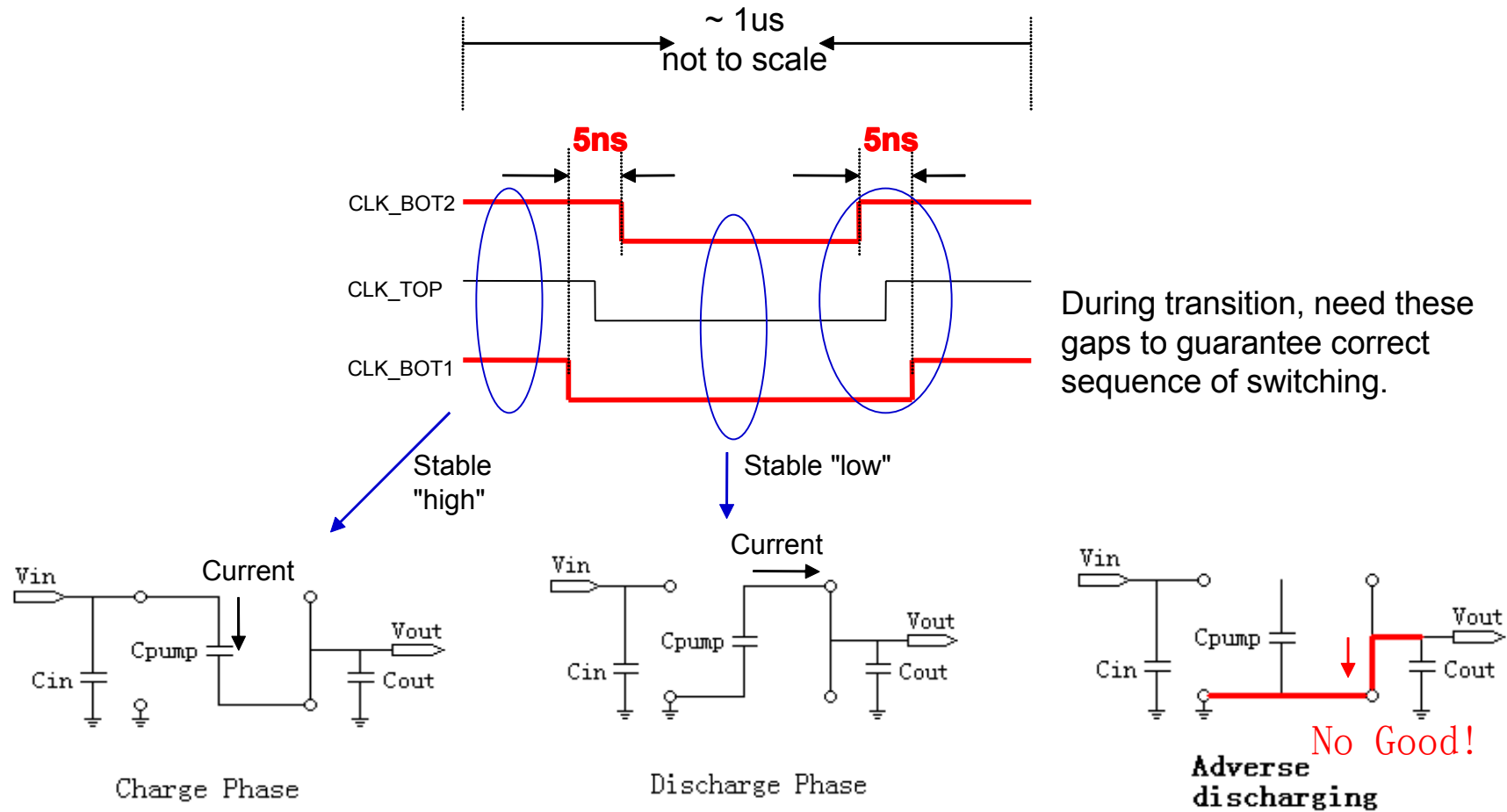
# Non-overlapping clocks

- 5ns gap between CLK\_BOT1 and CLK\_BOT2 to eliminate adverse discharging.




# Testing Results



# Efficiency vs Clock frequency


**Vin=3.3V, Rload=5Ω**

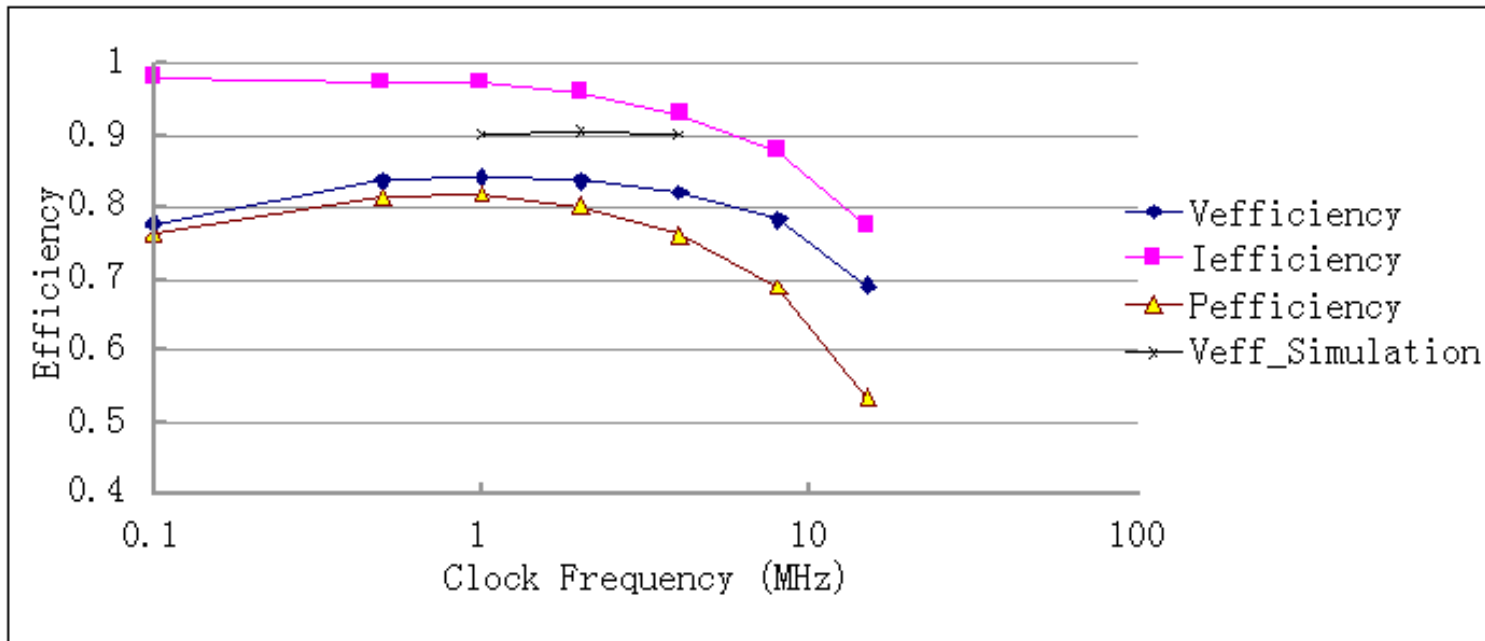


- **Simulation result** shows Vefficiency around 90%, while the **test** result shows Vefficiency of about 84%.
- Just take 1MHz as the optimal frequency for the following test.
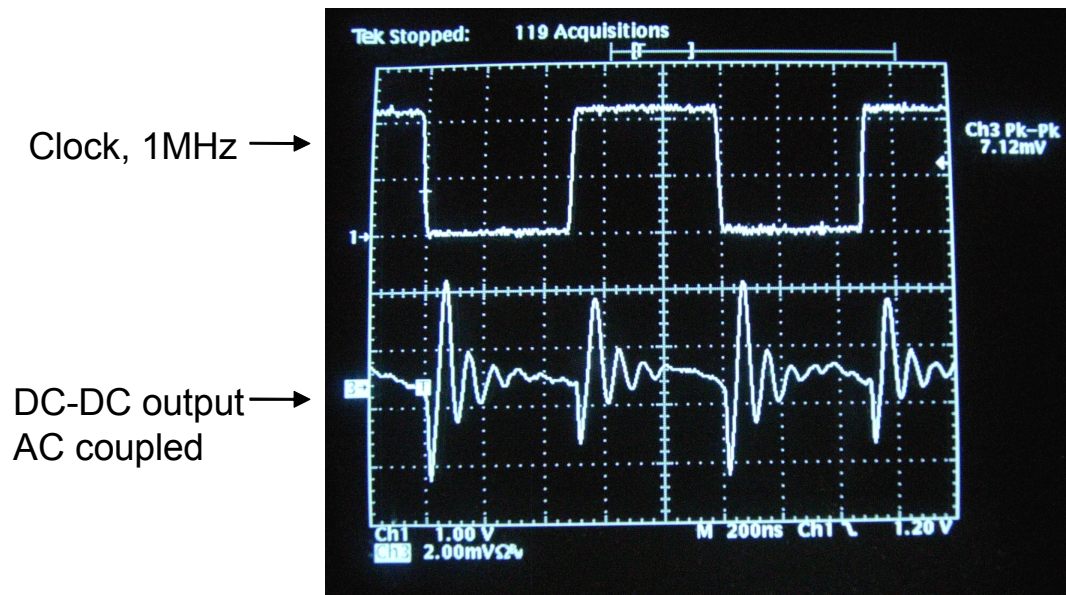
# Ripple Voltage

- Observed ripple voltage was much larger(7mV) than the value predicted by simulation(<1mV).
- Its amplitude depended on load current(as shown in pictures below).
- We can't regenerate comparable ripple voltage by simulation. Still can't understand it by now.





250mA Load Current

 

84mA Load Current
 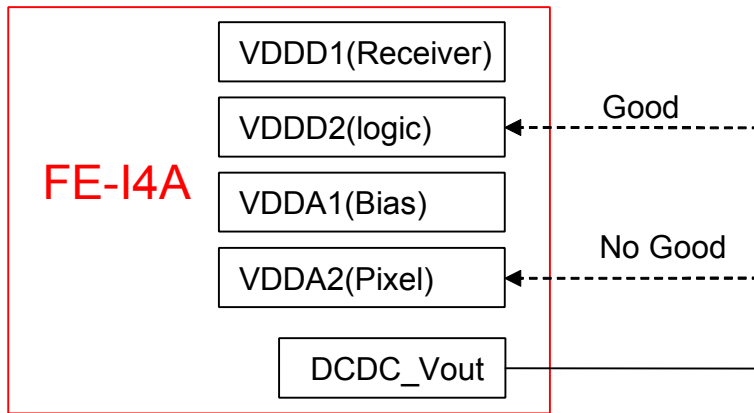
# Noise in Threshold Scan

**DC-DC powering analog-->Noise increased;  
DC-DC powering digital--> Noise seemed good;**




Power Scheme	Noise(e-)	Total Current(mA)
External_Power	72	396
DCDC_VDDD2	76	356+27=383
DCDC_VDDA2	96	121+148=269
DCDC_ (VDDA2+VDDA1+VDDD2)	104	76+169=245

**Is it safe to say:  
good for digital, but  
not good for analog?**



**Well, it depends...**

# Effect of running DC-DC standalone

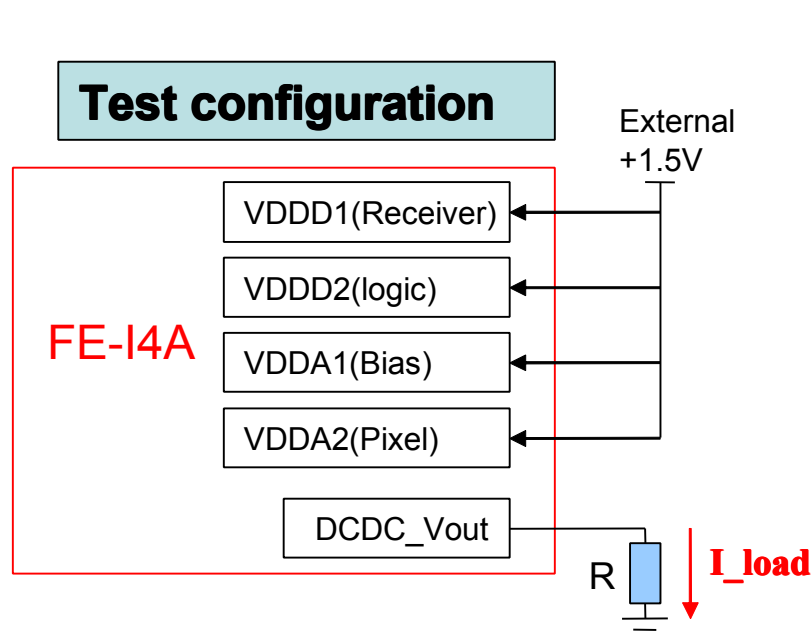


- Running DC-DC but not using it to power the chip.
- Noise depends on DC-DC current.
- Seems like that DC-DC is not well isolated from the rest of the chip as expected.
- To investigate this problem, we made a test shown on next page.

## Noise map

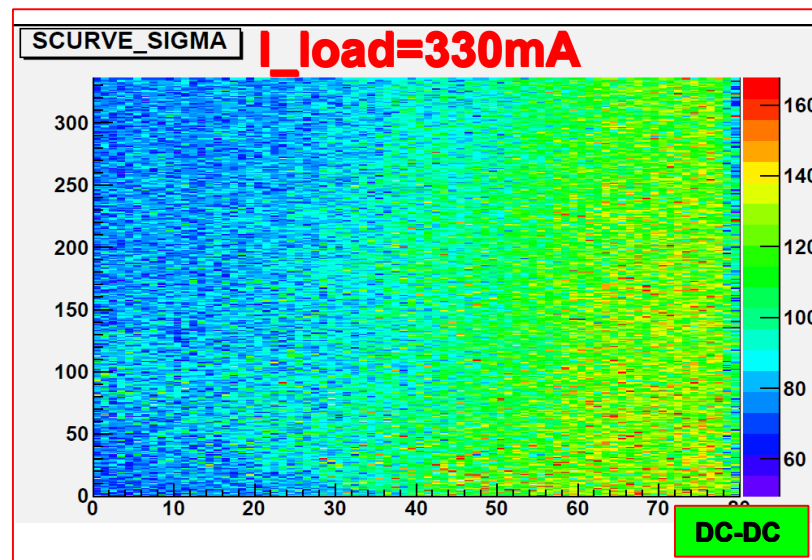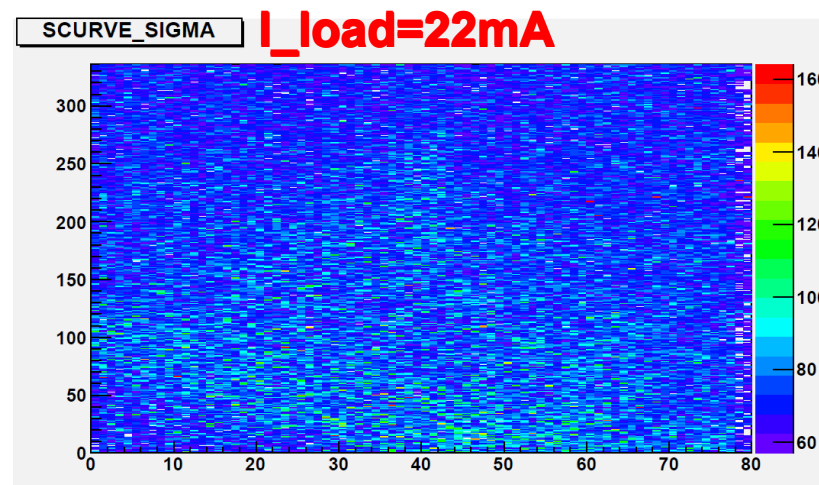

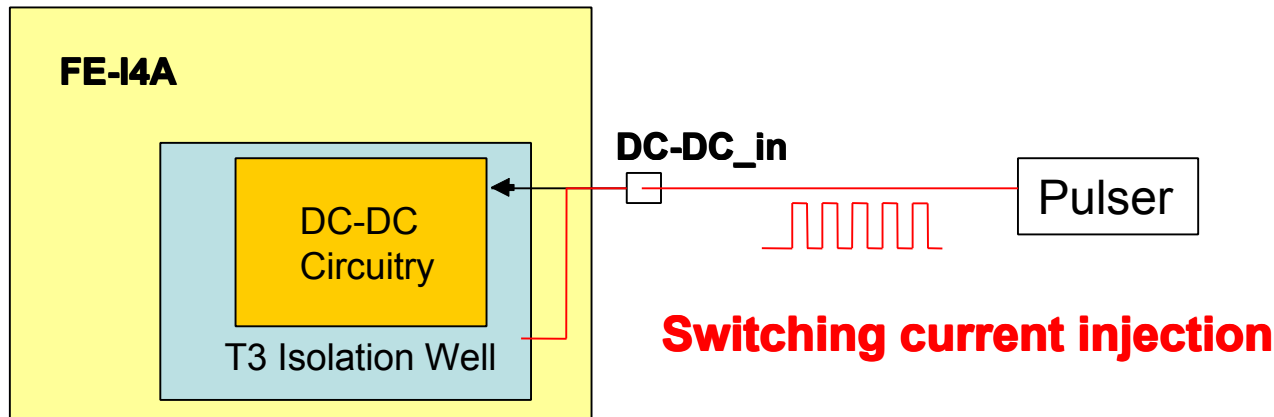
# An attempt to inject switching current via DC-DC\_T3 isolation well

- DC-DC module sits in a **T3 isolation** well.
  - which is connected to DC-DC\_in.
  - expected to be isolated from the rest of the chip by this way.
- Injecting switching current into the T3 isolation well, to see if noise from threshold scan increased.
- But it doesn't work by far. Two alleged reasons:
  - The current(tens of mA) from the pulser is not big enough.
  - The capacitance between T3 well and substrate smoothed the little switching current.



# Follow-up

 

1. To find out where does the noise come from?
  - Put more efforts into the trial of switching current injection.
2. To put the pump capacitor on the bonding pads
  - smallest package available: "0201";
  - not sure it will work or not since not clear where the noise comes from.
  - should increase operating frequency--minimum of output resistance at higher frequency due to no wire bonds.
3. To make a board to test the irradiated chips.
  - 3 chips irradiated last Dec. and under test now.
  - But no wire bonding for DC-DC can be made on the boards.
  - Plan to make a small board sitting on top of chip. DC-DC will be wire bonded to this board and further attached to wires for test.

- Thanks for paying attention!

# Backup Slides



# Power Requirments in FE-I4

- 2.2nm gate oxide for all transistors(except for DC-DC converter and EFUSE programming circuitry).
- Thickest gate oxide in the process(5.2nm) used for DC-DC converter and EFUSE programming circuitry.
- The voltage ratings are conservatively estimated according to the gate oxide thickness, area, lifetime, operation temperature, and expected failure rate.
  - 1cm<sup>2</sup> gate area is rated for 1.6V with a 1ppm failure rate after 100KPOH at temperature of 125°C.
  - The benifits from low operation temperature are not included.


**Voltage rating  
and current  
consumption**

	<b>Internal Nodes</b>	<b>Linear Regulators</b>	<b>DC-DC Converter</b>	<b>Units</b>
Min. operating voltage	1.20	1.30	2.20	V
Max. operating voltage	1.50	1.65	3.40	V
Nominal operating current	0.60	0.60	0.31	A
Max. current at max. voltage	0.90	0.90	0.46	A
Peak transients allowed	1.75	2.00	4.0	V
Max. voltage at power supply <sup>1</sup>	2.10	2.50	4.73	V
Derived R/T drop allowed in cables	0.60	0.85	1.33	V



1: The chip will see this voltage minus the cable voltage drop. This limit is chosen under the worst case assumption that a zero voltage drop in the cables can occur.
 
# Switched Capacitor DC-DC

- Merits of switching capacitor DC-DC:
  - converting "high voltage low current"(good for power cables) to "low voltage high current"(required by front-end electronics);
  - using capacitors for energy storage benefits from the the industrial trend of high capacity small shape capacitors( and therefore decreasing mass).
- Pending questions:
  - Noise imposed upon the analog part when integrated into the same chip.
  - Power efficiency degraded by irradiation, about 10% observed on a prototype.



**DC-DC & ShuLDO1**

  

**250um pads for power module**


DCDC\_IN

REG1\_IN

REG1\_OUT

REG\_GND

**ShuLDO2**

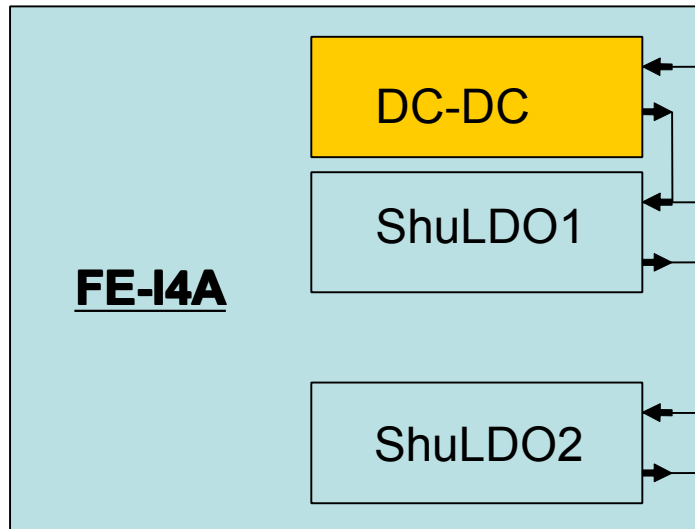

DCDC\_IN

**DCDC\_OUT & REG1\_IN**  
REG1\_OUT


REG2\_IN

REG2\_OUT

**DCDC\_OUT and REG1\_IN are connected internally and share the same pad. The same way with DCDC\_GND and REG1\_GND.**

# Charge pump core schematic

PFET:  
Ron~1.75Ω

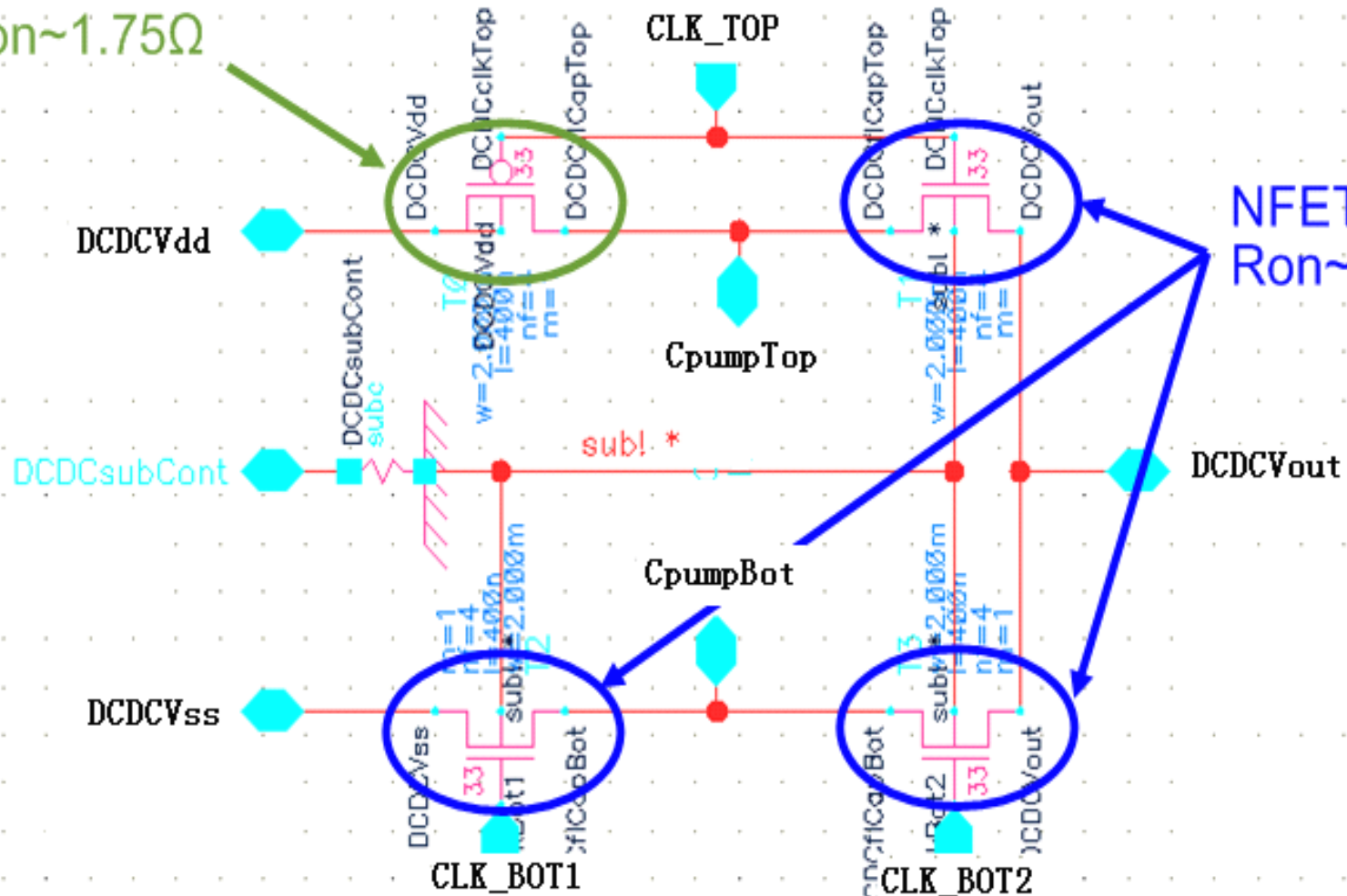

NFET:  
Ron~0.45Ω