



Rad-Hard ASICs for Optical Data Transmission



K.K. Gan, H.P. Kagan, R.D. Kass, H. Merritt,
J. Moore, A. Nagarkar, D. Pignotti, S. Smith, M. Strang
The Ohio State University

P. Buchholz, A. Wiese, M. Ziolkowski
Universität Siegen

OUTLINE

Introduction

Result on 4-channel Driver/Receiver with Redundancy

Design of new 12-channel Driver/Receiver with Redundancy

Summary/Conclusions

Why Optical Data Links?

Optical data transmission preferred over copper wire links:

- optical fibers are lower in mass than copper
- higher data transmission rate over long distances (80m)
- no ground loop between front and back end electronics

Optical Transmitter: VCSEL (vertical cavity surface-emitting laser)



Optical Receiver: PIN diode

Can be packaged in one, four, twelve channels

Work in the radiation environment of the LHC

Several detector systems in ATLAS transmit data using optical links.

(e.g. pixel & SCT)

  

- VCSEL:** Vertical Cavity Surface Emitting Laser diode
- VDC:** VCSEL Driver Circuit
- PIN:** PiN diode
- DORIC:** Digital Optical Receiver Integrated Circuit



Array Optical Links



Array solution has several major advantages over a single fiber system:

compact: more channels in less space

robust: 12-fiber ribbon stronger than individual fiber

efficient: can reserve 1 in 12 channels for redundancy instead of doubling the number of fibers for a single fiber system

VCSEL/PIN array based links are commercially available:

12-fiber ribbon, 12 channel VCSEL/PIN array, 10 Gb/s each

⇒ 120 GB/s !

12-channel VCSEL & PIN arrays available from several vendors

Vendors provide reliability and qualification info.

Situation better than in 2003 when implementing array based on-detector links for ATLAS pixel detector:

We only had to fabricate 272 array-based opto-boards for 1744 pixel modules.



Driver/Receiver with Redundancy

We designed an updated version of the VCSEL driver and PIN receiver used in the current ATLAS pixel detector.

⇒ **Added redundancy**

Possible applications include current ATLAS pixel detector and its upgrade IBL (insertable B-Layer) in 2013-14

Experience gained from the development/testing of new chips could help the development of on-detector array-based opto-links for high luminosity up grades to the LHC

Submitted 1st prototype chip in Feb. 2010

process: 130 nm CMOS



Chip Content



VCSEL: Vertical Cavity Surface Emitting Laser diode

PIN: PiN diode



The Decoder decodes bi-phase mark encoded clock & commands

Design

Photo

- VCSEL Driver (spare)
- VCSEL Driver
- VCSEL Driver with pre-emphasis
- VCSEL Driver with pre-emphasis
- CML Driver with pre-emphasis

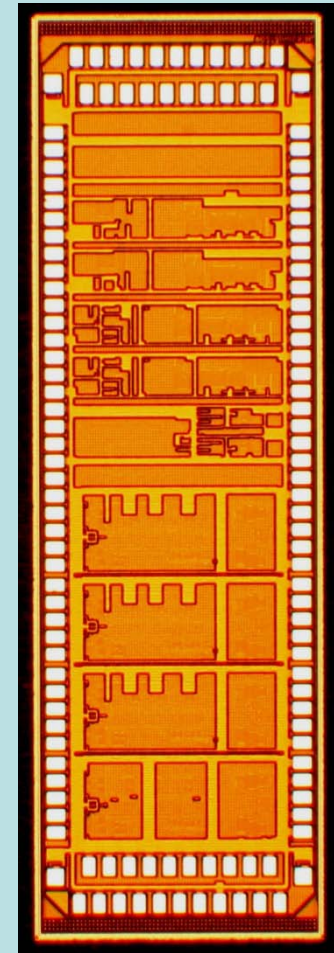 
- Decoder (40Mb/s)
- Decoder (40Mb/s)
- Decoder (40Mb/s)
- Decoder (40/80/160/320 Mb/s, spare)



1.5 mm



PIN Receiver/Decoder

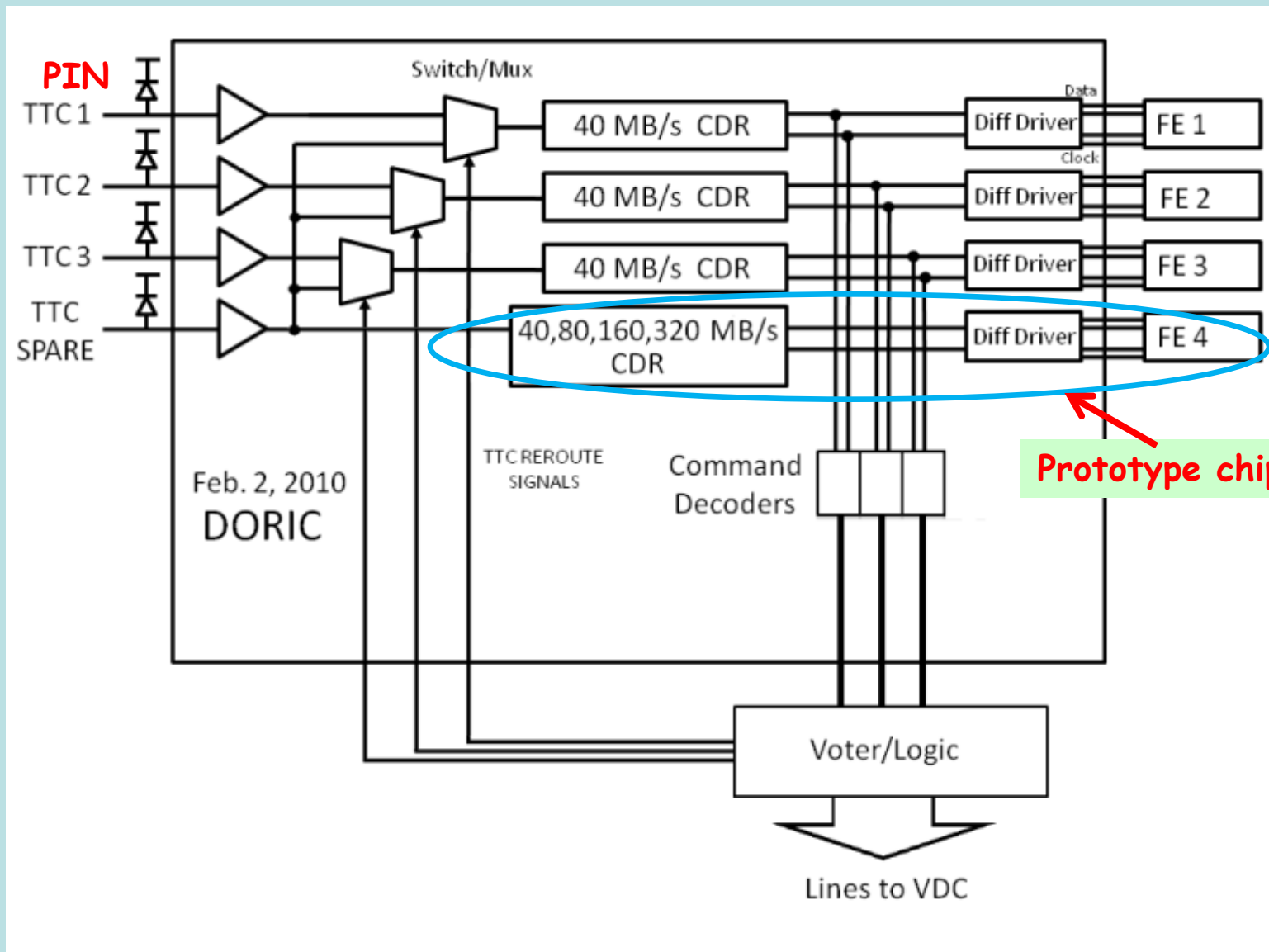


Command Decoder Interface



Courtesy of FE-I4 of IBL

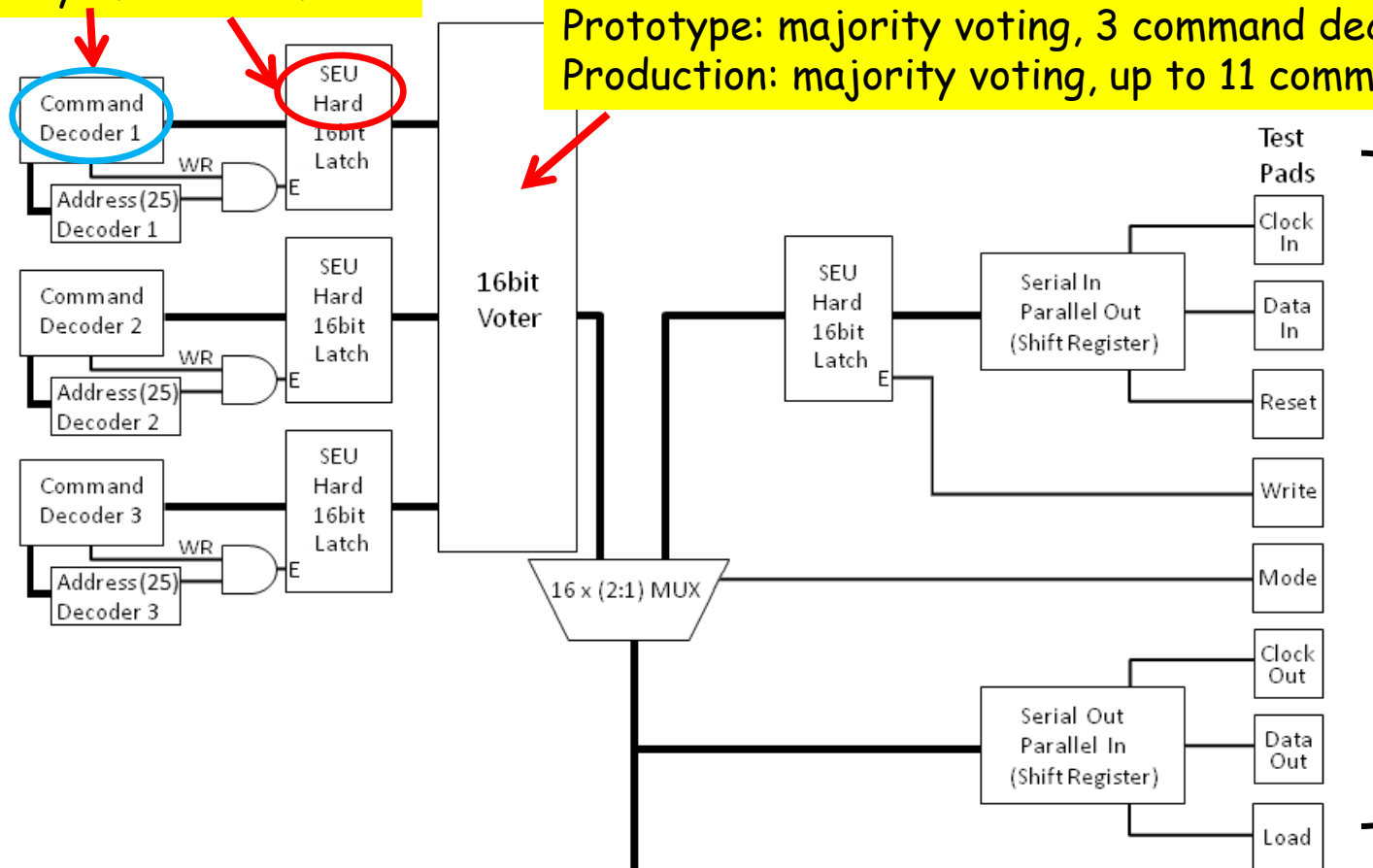Prototype: majority voting, 3 command decoders
 Production: majority voting, up to 11 command decoders



In prototype chip only

COMMAND WR (15)	STEER (14)	STEER VDC/DORIC (13)	SET DAC (12)	CH. SELECT (11:8)	DAC VALUE (7:0)
-----------------	------------	----------------------	--------------	-------------------	-----------------


Command Word



VCSEL Driver Section



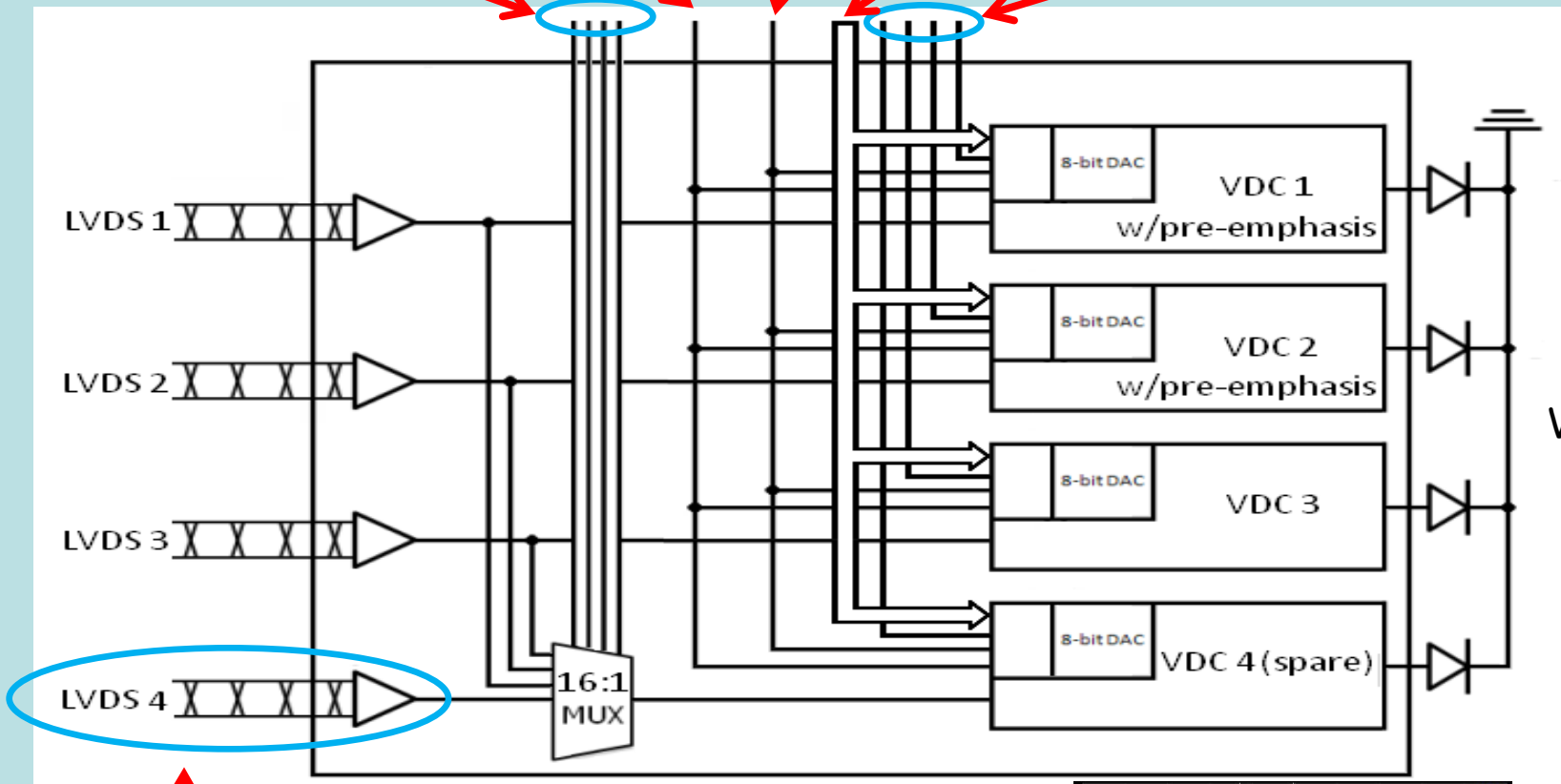Channel Select (3:0) Set DAC Command Write DAC Bits (7:0) Write Enable (3:0)



VCSEL

input added for prototype chip only.

main amplitude





Irradiation Results



2 chips were packaged for irradiation with 24 GeV/c protons at CERN in August 2010

Each chip contains 4 channels of drivers and receivers


Total dose: 1.7×10^{15} protons/cm²

Included purely electrical tests to avoid complications from degradation of optical components


Long cables limited testing to low speed

Observe little degradation of the devices

Test card

 

chip

 

PIN opto-pack
ULM 5 Gb/s





Single Event Upset Rate



SEU hardened latches or DAC could be upset by traversing charged particles

40 latches per 4-channel chip

SEU tracked by monitoring the amplitude of the VDC drive current

13 instances (errors) of a channel steered to a wrong channel in 71 hours for chip #1

Similar upset rate in chip #2

Estimate SEU rate:

$$\sigma = 3 \times 10^{-16} \text{ cm}^2$$

particle flux $\sim 3 \times 10^9 \text{ cm}^{-2}/\text{year}$ @ opto-link location

SEU rate $\sim 10^{-6}/\text{year}/\text{link}$



Summary Of 2010 Prototype Chip

Prototyped 4-channel VCSEL driver & PIN receiver/decoder:
Incorporated experience from current opto-links by adding:
 redundancy to bypass broken PIN or VCSEL channel
 individual VCSEL current control
 power-on reset to set VCSEL current to $\sim 10\text{mA}$ on power up

Results of tests:

VCSEL driver can operate up to $\sim 5\text{ Gb/s}$ with $\text{BER} < 5 \times 10^{-13}$
PIN receiver/decoder works even at low threshold
Irradiation with 24 GeV protons to $1.7 \times 10^{15}\text{ p/cm}^2$
 Very low SEU rate in latches $\sim 3 \times 10^{-7}/\text{year/link}$
 small decrease in VCSEL driver output current



2011 PIN Receiver Decoder Chip

Decodes 40 Mb/s bi-phase mark (BPM) signal

4 spare PIN receivers for redundancy

8 FE-I4 command decoders

Allows remote control by voting between commands received by the 8 FE-I4 command decoders


If one of the 8 inner PIN diodes fail

⇒ signal from one of the 4 redundant channel amplifier outputs can be steered to the digital portion of the failed channel

Majority voting of the command decoder values determines the command to be executed

Allows working control if only 2 PIN channels are alive

2011 PIN Receiver Decoder Chip

 

Submitted May 2011
size: 6.5 mm x 1.6 mm

600 μm x 900 μm
control logic

DLL + command decoder
+ LVDS driver

600 μm x 900 μm
voltage regulator
2.5 V \Leftrightarrow 1.5 V


Spare
PIN amplifiers

8 X
DORIC

Spare
PIN amplifiers



2011 PIN Receiver Decoder Chip

 



2011 VCSEL Driver Chip



Designed for 8 channel operation up to 5 Gb/s
4 spare VCSEL driver outputs

Receives serial data from PIN receiver/decoder
(command decoder vote) for configuration


If one of the 8 inner VCSELs fail

⇒ the data signal from the detector
can be steered to any of the spare VCSELs

8 bit DAC for remote control of
individual VCSEL current


Submitted May 2011

size: 1.5 mm x 4.5 mm

 



2011 VCSEL Driver Chip

 



Summary/Conclusions



Our 2010 4-channel driver/receiver chips with redundancy and other improvements work well

12-channel driver/receiver chips with redundancy submitted in May 2011

Will irradiate chips with 24 GeV protons in September 2011

Will Submit 4-channel driver/receiver compatible with high luminosity-LHC in 2012




Extra Slides





VCSEL Driver with Pre-Emphasis

 


Pre-emphasis working with tunable width and height



Recovered Clock/Data

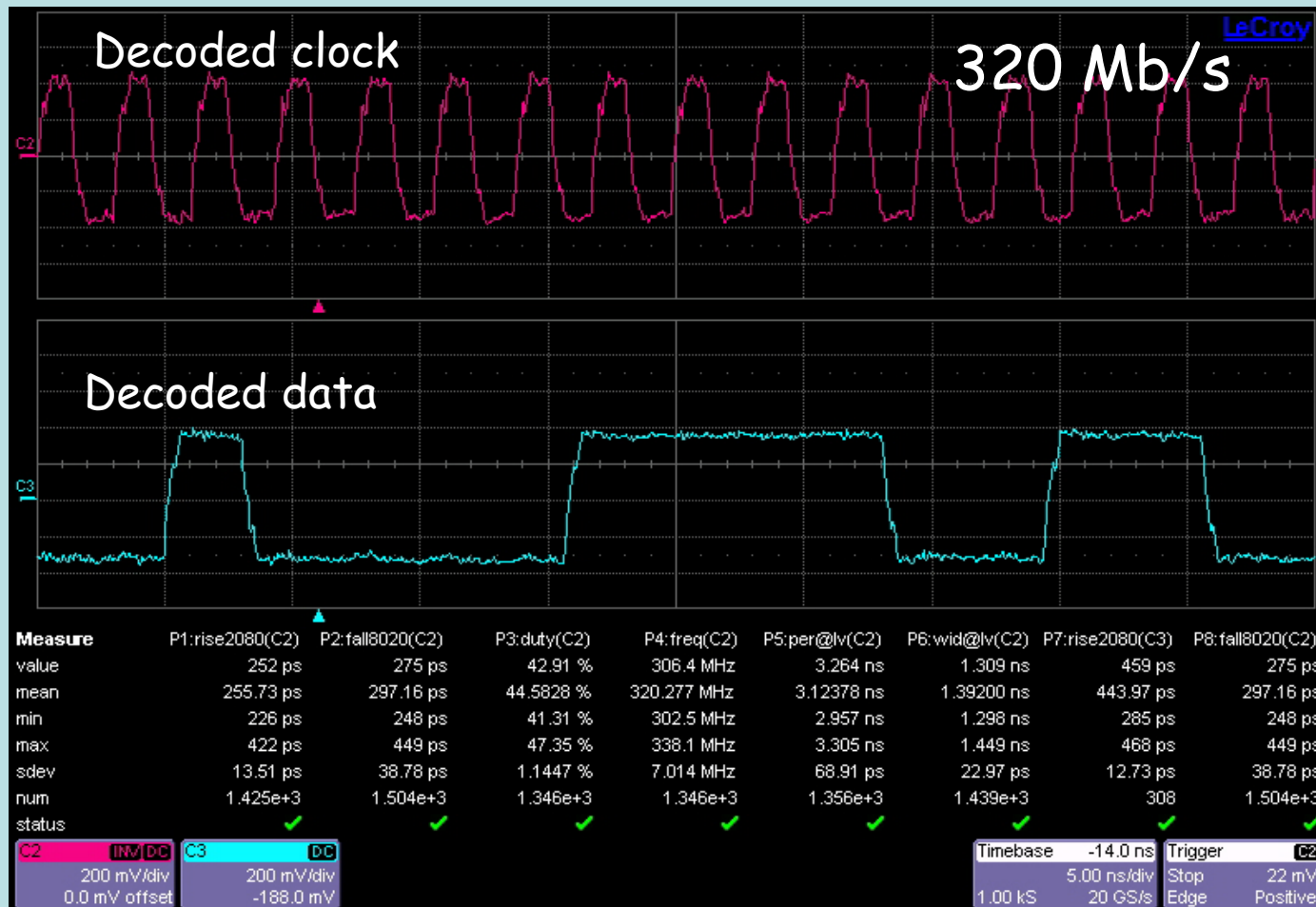Decoder recovers clock & data from bi-phase mark input stream





2010 VDC Results



Power-on reset circuit

In the present pixel detector an open control line disables 6 opto-links

Prototype chip has a power-on reset circuit

chips will power up with several mA of VCSEL current

Test port

can steer signal received to spare VDC/VCSEL

can set DAC to control individual VCSEL currents

All 4 channels run error free at 5 Gb/s

includes the spare with signal routed from the other inputs