


# Mixed-signal parameterized cells in general-purpose programming languages

Why chip design should be software-driven


Kennedy Caisley

18 March, 2024

# ■ Schematic and ■ Layout Design Tools

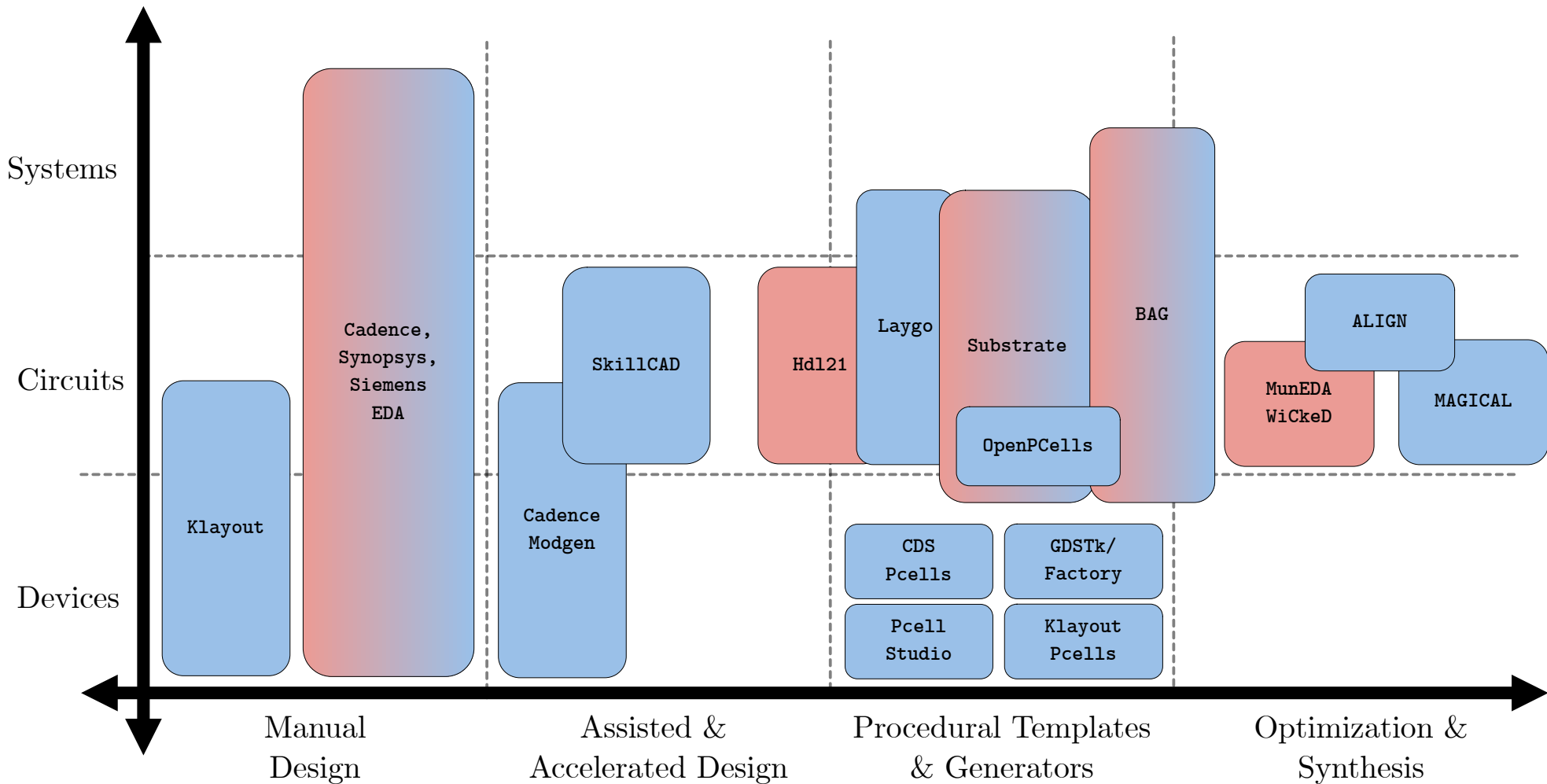

# ■ Schematic and ■ Layout Design Tools

 

# Let's start with schematics.


The image shows the Cadence Virtuoso Schematic Editor interface. The main window displays a schematic diagram of an ADC cascode opamp. The schematic includes several MOSFETs (M0, M1, M2, M3, M4) and current sources (V1, V2, V3, V4, V5). The output is labeled Vout. The schematic is connected to a power supply (vdd) and ground (gnd). The interface includes a menu bar (Launch, File, Edit, View, Create, Check, Options, Window, Help), a toolbar, and a workspace area. The workspace area shows the current schematic (ADC\_CASCADE\_OPAMP) and other open schematics (analog\_eq\_bias, tor\_actr). The left sidebar shows the Circuit Prospector with search filters (Category: Structures, Search for: MOS Curr, Within: All objects) and a Groups/Finders list. The right sidebar shows the Constraint Manager with a table of constraints.

Type (3)	Parameters
adc_cascade...	constraint
Cluster (4)	
Relative O...	R0
Alignment ...	top

Name	Constr_1
Owner	ether.adc_ca...
Enabled	true
Status	none
Notes	CP: Matched...
Orientations	R0

# What do schematics actually represent?

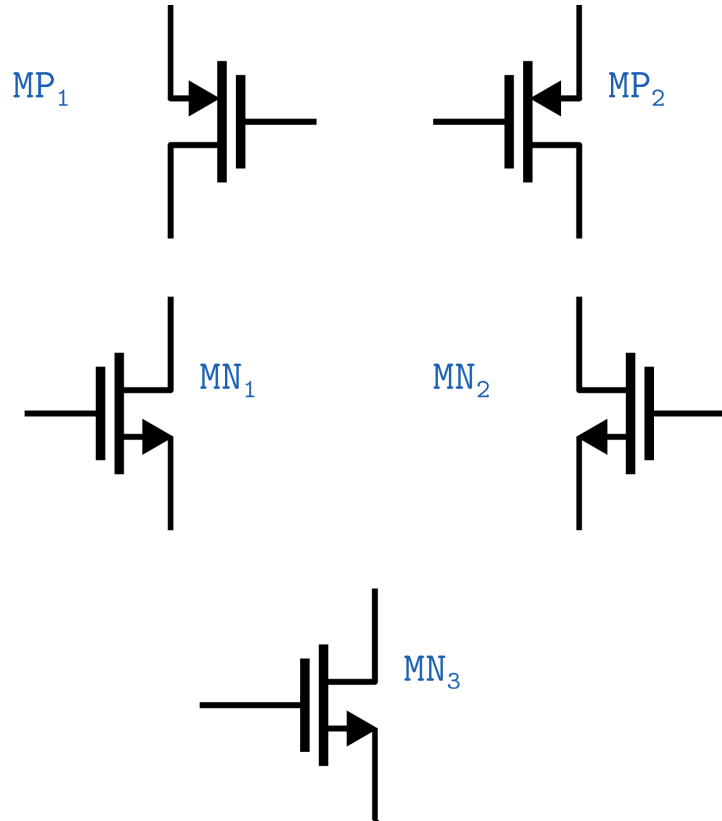

\* Amplifier netlist \*

MP1

MP2

MN1


MN2

MN3





# Some issues & observations

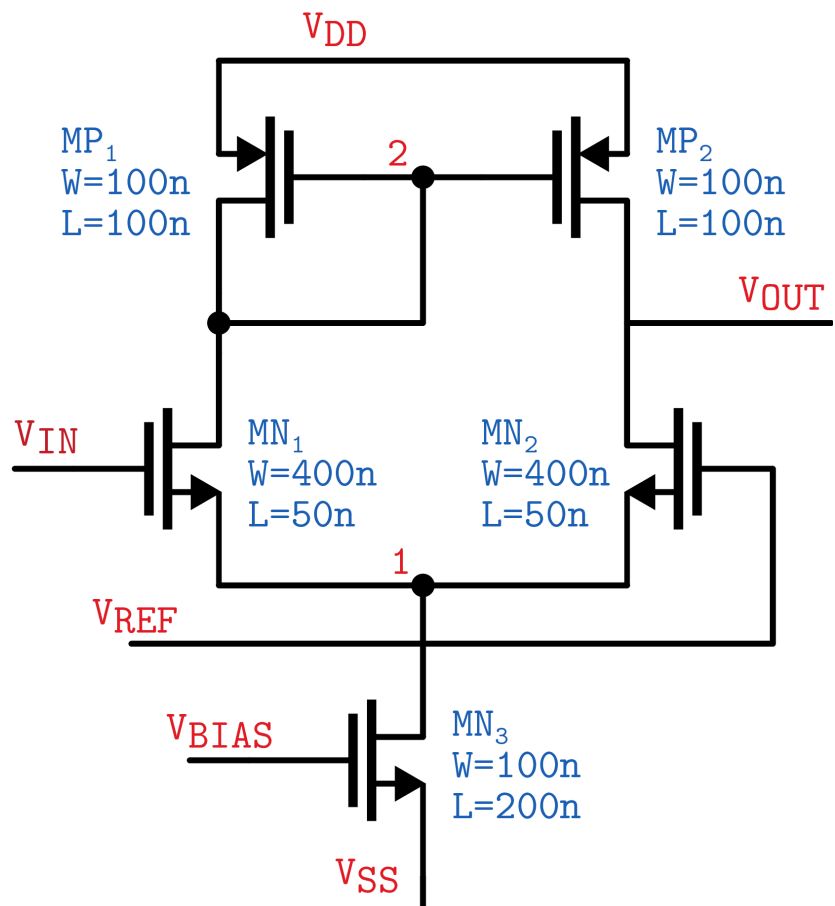

Structural info != performance. Must iterate & simulate

\* Amplifier netlist \*


```
MP1 2 2 vdd      w=100n l=100n
MP2 2 vout vdd   w=100n l=100n
MN1 vin 2 1      w=400n l=50n
MN2 vref vout 1  w=400n l=50n
MN3 vbias 1 vss  w=100n l=200n
```

Often a couple  
topologies to try


But sizing choice  
is enormous




# What if we express this in code?

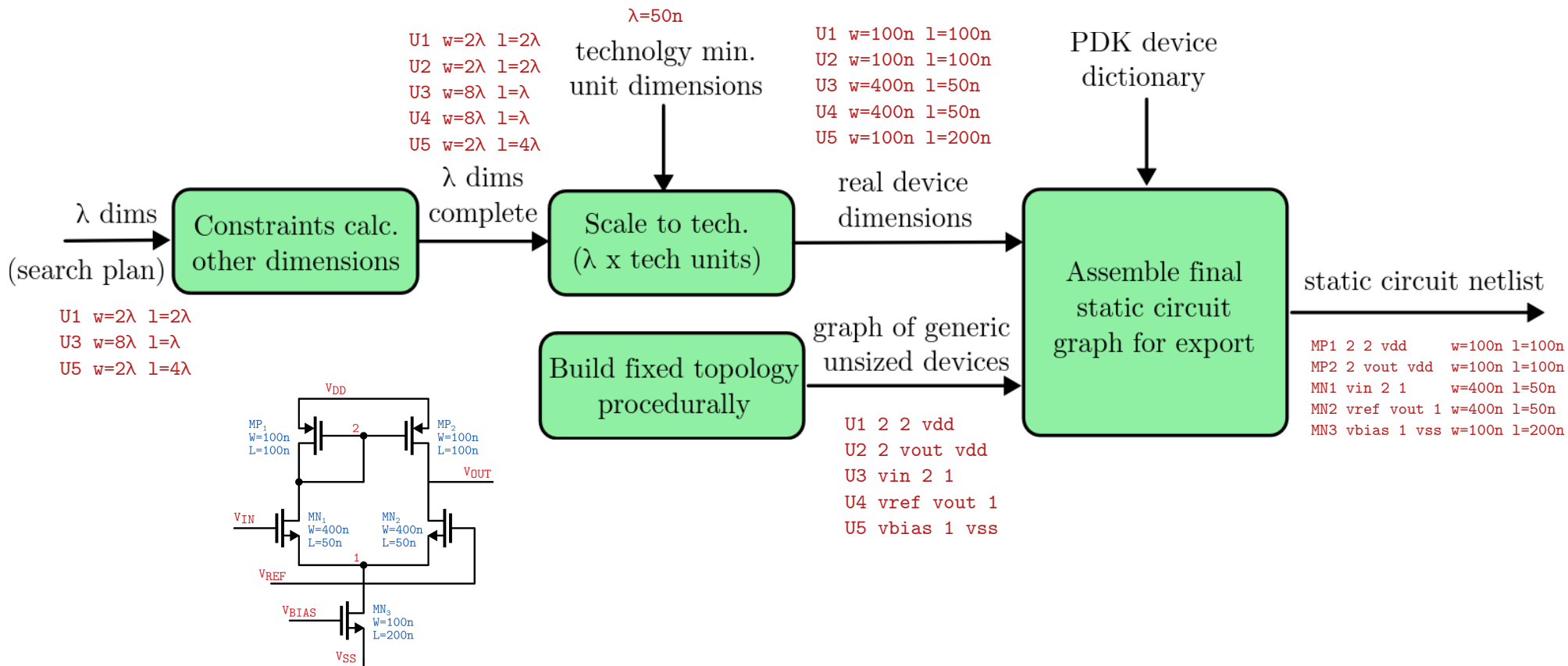

# Testbenches, Simulation, & Analysis

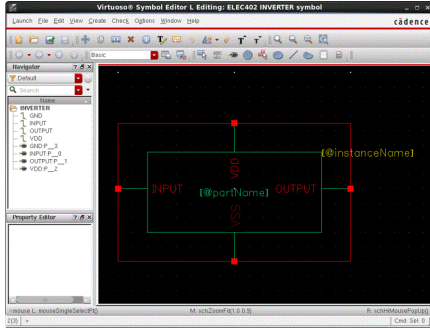


1. Create symbol

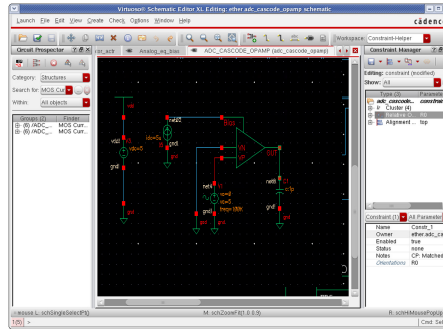

2. Instantiate DUT


3. Wrap with test sources/loads/mocks

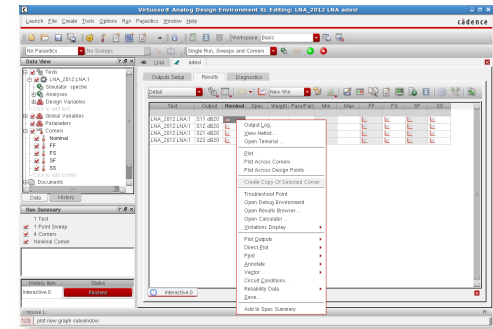


4. Simulation runs / options

5. Sweeps and variables

6. Test points

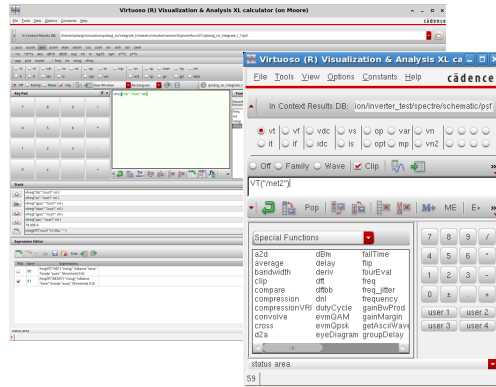


7. Post analysis of outputs

 


7. Visualization


# Testing with code

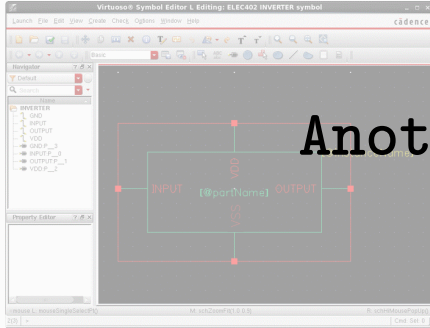

Another schematic generator

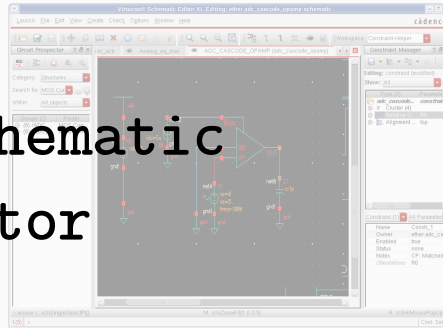

Unit test & asserts

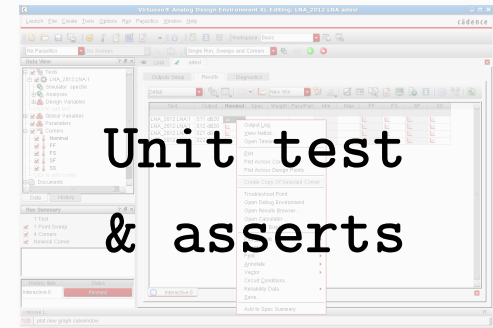

1. Create symbol


2. Instantiate DUT

3. Wrap with test sources/loads/mocks

4. Simulation runs / options


5. Sweeps and variables

6. Test points

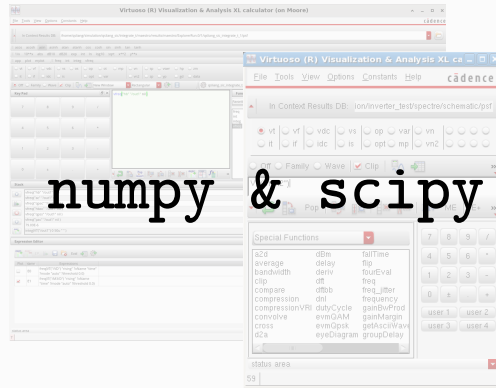


numpy & scipy


7. Post analysis of outputs

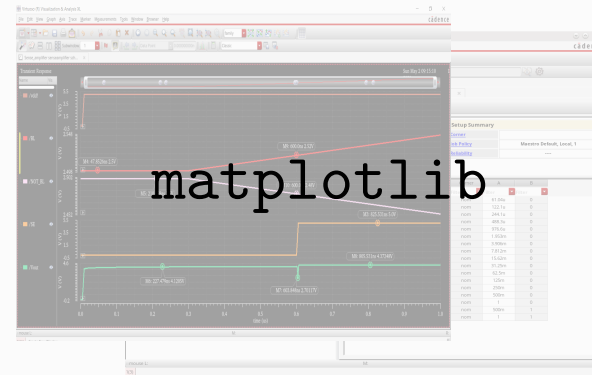

matplotlib

7. Visualization

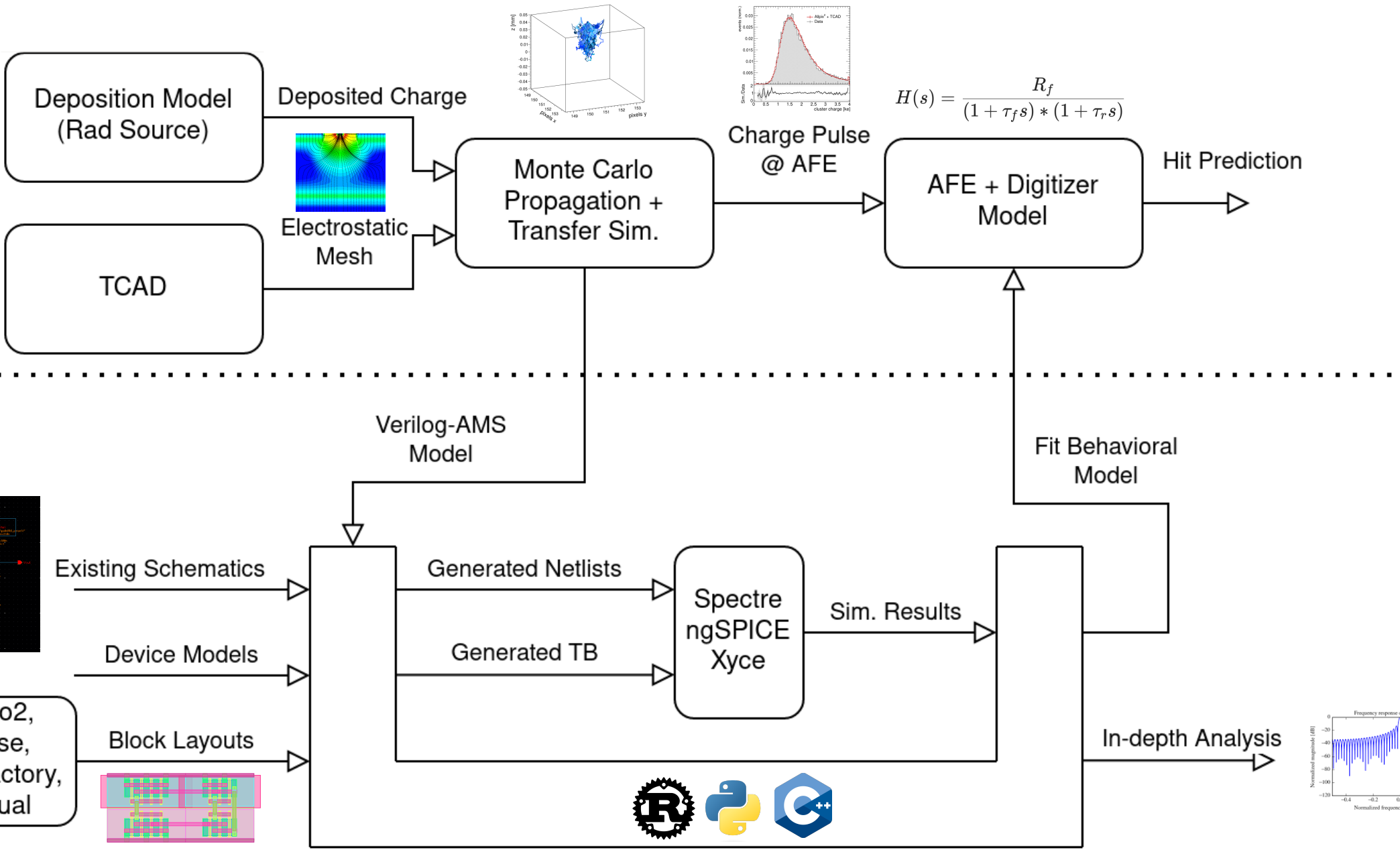

 

1  $\mu\text{m}$

180nm → 130nm → 65nm → 28nm

0.5x Reduced analog supply


2x Faster devices

2-3x device density



2x DRC rules, compact = better


2x cost → 8000€ / mm<sup>2</sup>

**“Correct by construction”**

 


# Procedural layout in code

 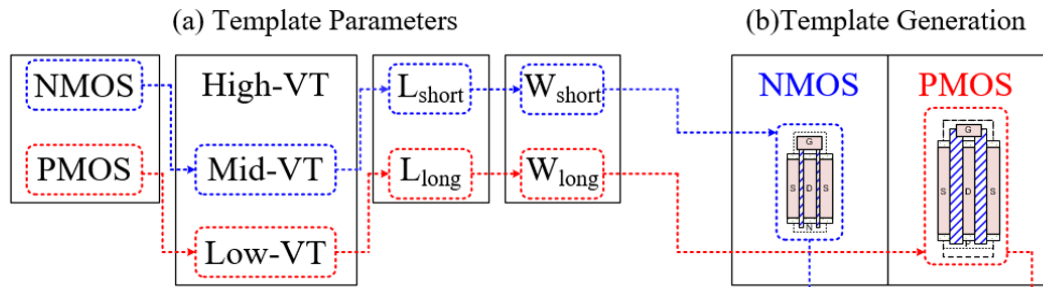

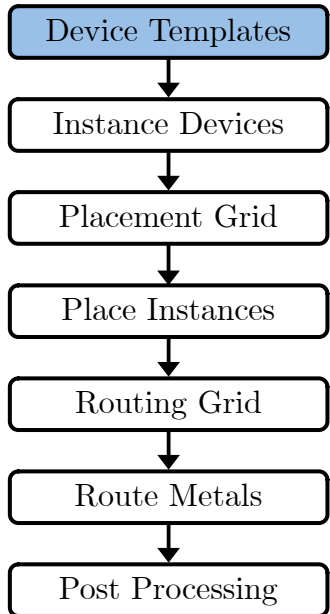


# Procedural layout in code

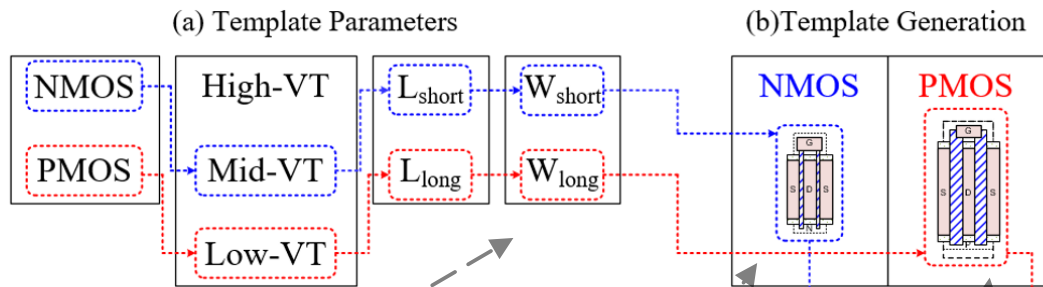


Limit unit device, as all should fit in a predefined area

Mimic PDK PCells

 
Similar approach for capacitors, resistors








 



# Procedural layout in code

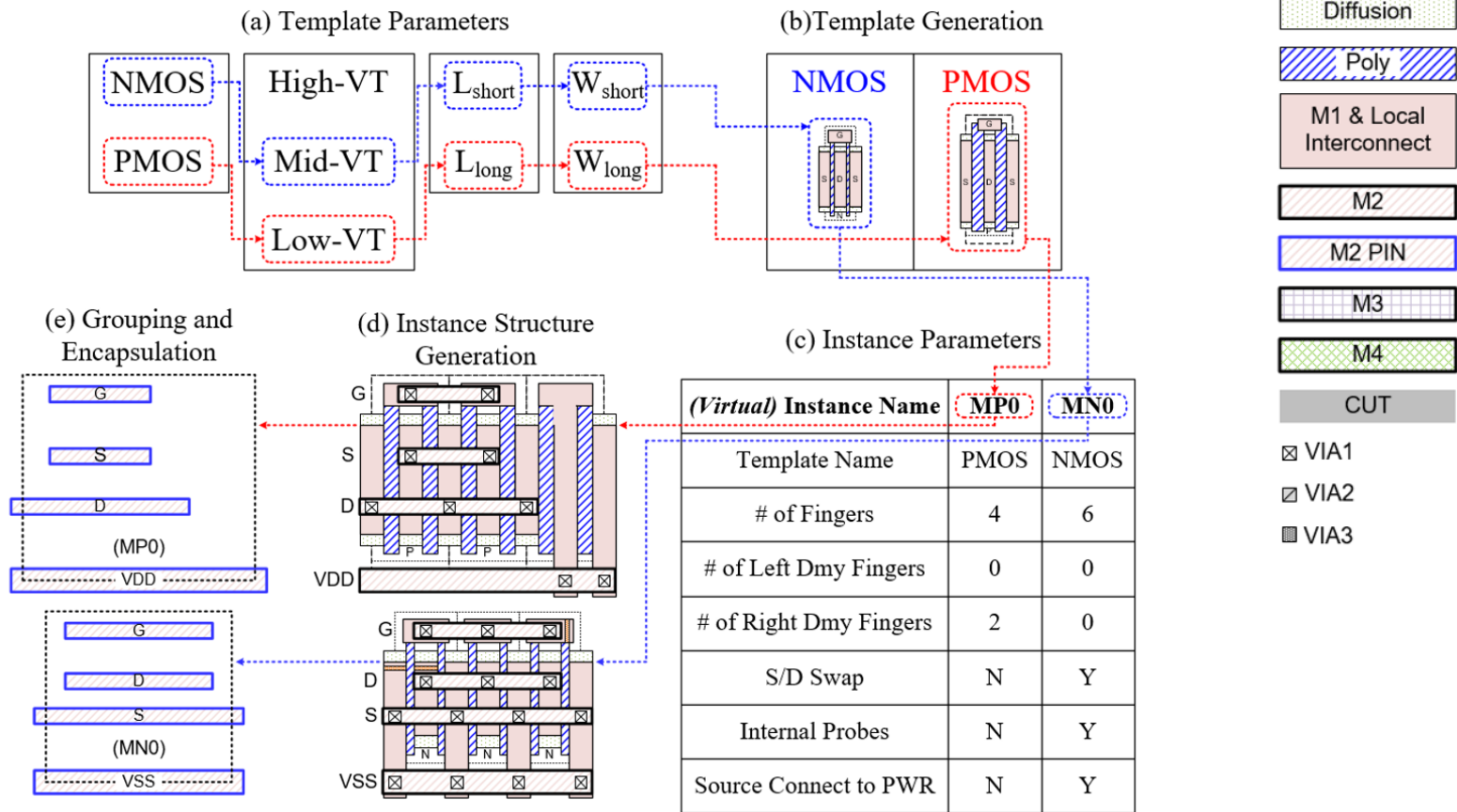

   


  (a) Generate virtual instances and encapsulate

Reminder: We divide large devices in netlist between multiple layout cells






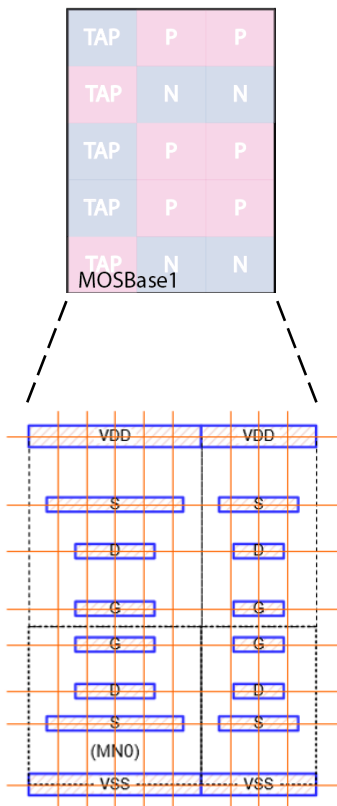
(a) Generate virtual instances and encapsulate





(b) Place instances and generate M1-M2 grid

(mask layers)

  


  

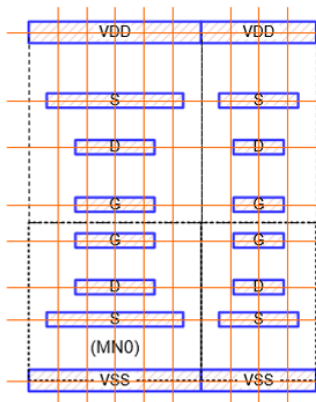 (a) Generate virtual instances and encapsulate



 (b) Place instances and generate M1-M2 grid



(c) Place M2 wires

(mask layers)

Well (N)

Implant (N or P)

Diffusion

Poly

M1 & Local Interconnect

M2

M2 PIN

M3



M4

CUT



⊠ VIA1

⊠ VIA2



■ VIA3

  

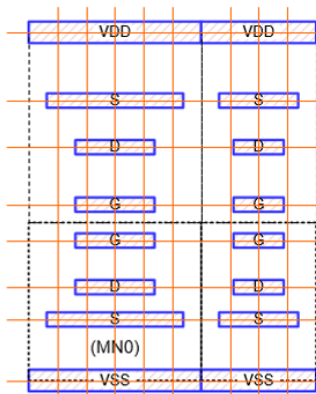
 
(a) Generate virtual instances and encapsulate



  (b) Place instances and generate M1-M2 grid



(c) Place M2 wires

  

(d) Generate M2-M3 grid and place M3 wires

(mask layers)

Well (N)

Implant (N or P)

Diffusion

Poly

M1 & Local Interconnect

M2

M2 PIN

M3



M4

CUT


⊠ VIA1

⊠ VIA2


■ VIA3

 
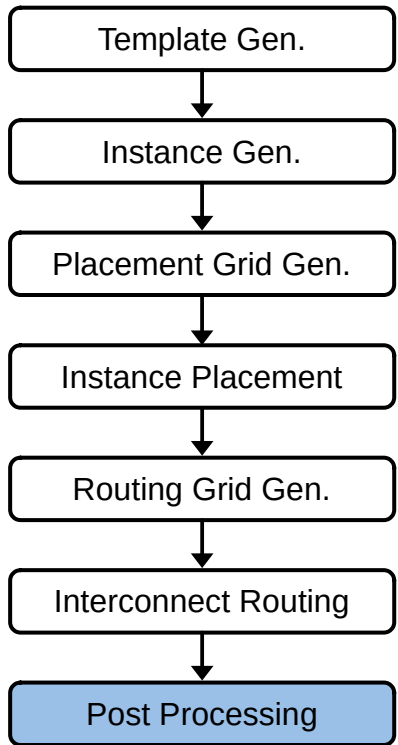


(a) Explicit device layout


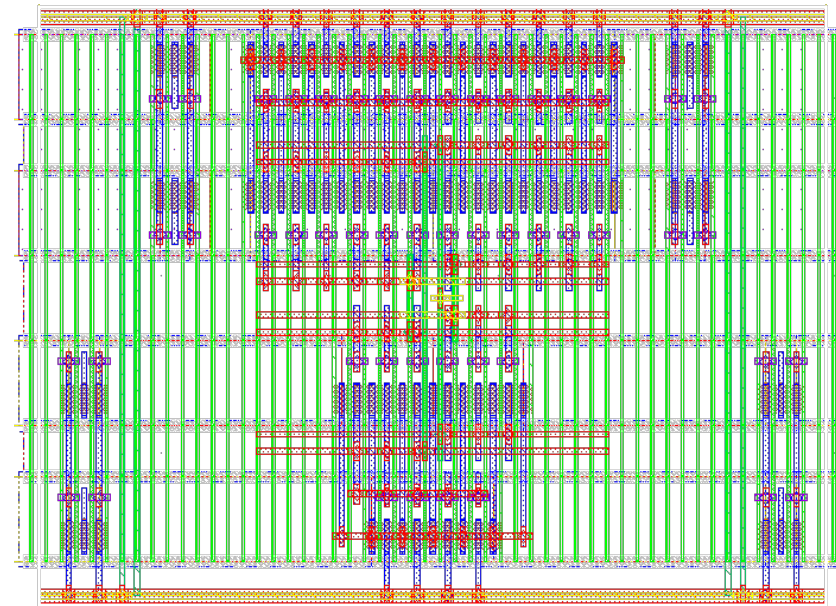


 (b) After post processing:  
dummy devices, poly fill/cut,  
guard rings, etc




 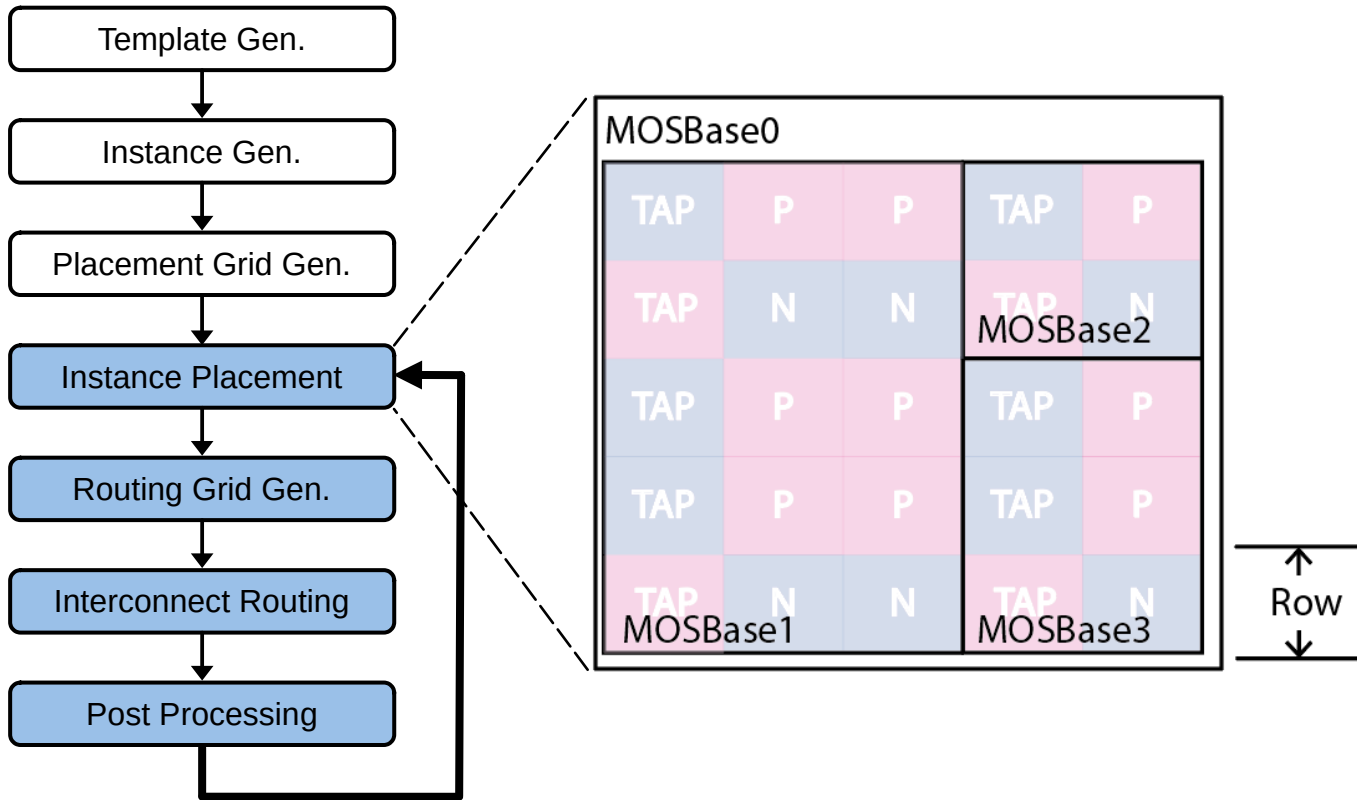

(a) Hierarchical layout w/ interconnect

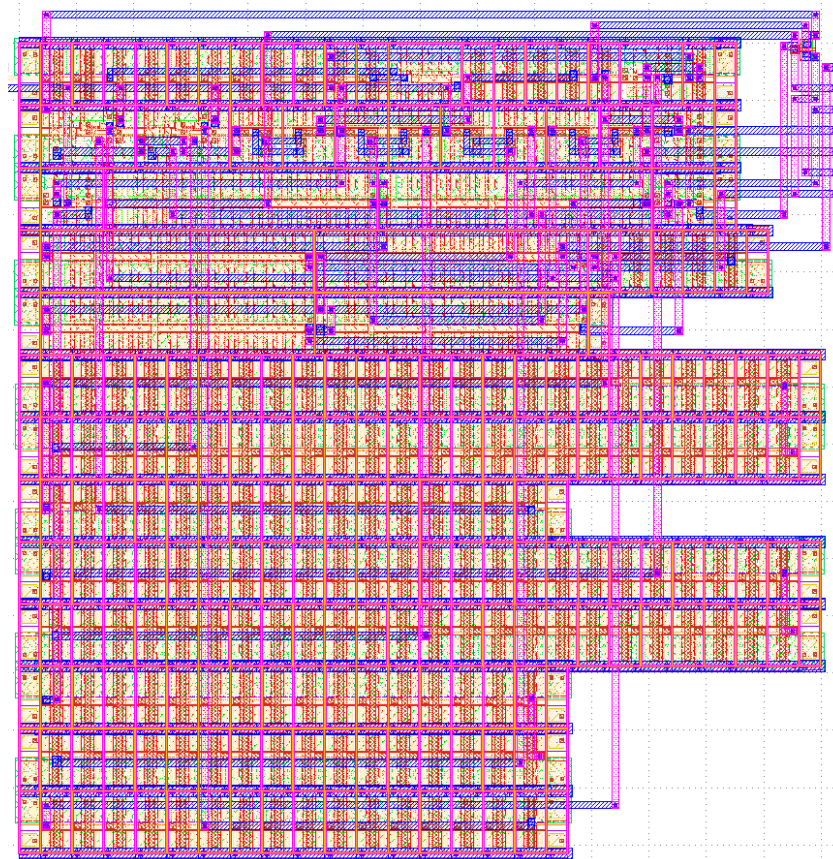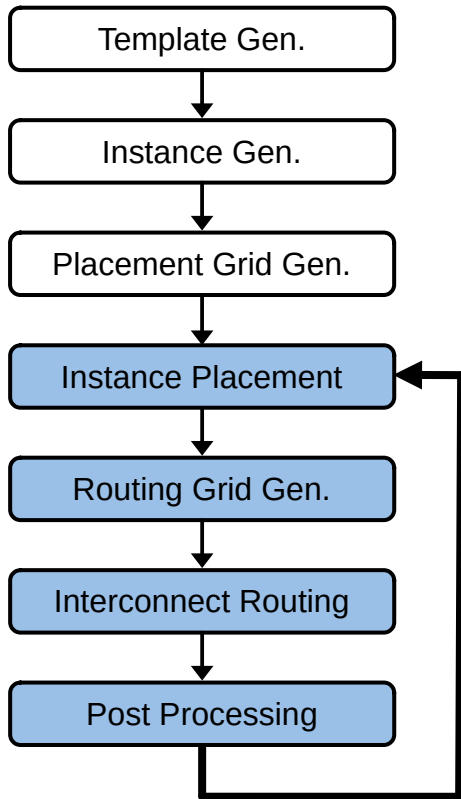


(a) Hierarchical layout w/ interconnect

 

(b) Jog interconnect to pins



 

\* StrongARM latch, produced from Substrate

```
.SUBCKT nmos_tile_w1250_l150_nf2 sd_0 sd_1 sd_2 g b
  Minst0 sd_0 g sd_1 b nshort l=0.150 mult=1 nf=1 w=1.250
  Minst1 sd_1 g sd_2 b nshort l=0.150 mult=1 nf=1 w=1.250
.ENDS nmos_tile_w1250_l150_nf2

.SUBCKT nmos_tile_w4000_l150_nf2 sd_0 sd_1 sd_2 g b
  Minst0 sd_0 g sd_1 b nshort l=0.150 mult=1 nf=1 w=4.000
  Minst1 sd_1 g sd_2 b nshort l=0.150 mult=1 nf=1 w=4.000
.ENDS nmos_tile_w4000_l150_nf2

.SUBCKT nmos_tile_w2000_l150_nf2 sd_0 sd_1 sd_2 g b
  Minst0 sd_0 g sd_1 b nshort l=0.150 mult=1 nf=1 w=2.000
  Minst1 sd_1 g sd_2 b nshort l=0.150 mult=1 nf=1 w=2.000
.ENDS nmos_tile_w2000_l150_nf2

.SUBCKT pmos_tile_w1000_l150_nf2 sd_0 sd_1 sd_2 g b
  Minst0 sd_0 g sd_1 b pshort l=0.150 mult=1 nf=1 w=1.000
  Minst1 sd_1 g sd_2 b pshort l=0.150 mult=1 nf=1 w=1.000
.ENDS pmos_tile_w1000_l150_nf2

.SUBCKT atoll_strong_arm_instance input_p input_n output_p output_n clock
vdd vss
  Xinst0 vss tail vss clock vss nmos_tile_w1250_l150_nf2
  Xinst1 vss tail vss clock vss nmos_tile_w1250_l150_nf2
  Xinst2 tail intn tail input_p vss nmos_tile_w4000_l150_nf2
  Xinst3 tail intp tail input_n vss nmos_tile_w4000_l150_nf2
  Xinst4 intn output_n intn output_p vss nmos_tile_w2000_l150_nf2
  Xinst5 intp output_p intp output_n vss nmos_tile_w2000_l150_nf2
  Xinst6 vdd output_n vdd output_p vdd pmos_tile_w1000_l150_nf2
  Xinst7 vdd output_p vdd output_n vdd pmos_tile_w1000_l150_nf2
  Xinst8 vdd output_n vdd clock vdd pmos_tile_w1000_l150_nf2
  Xinst9 vdd output_p vdd clock vdd pmos_tile_w1000_l150_nf2
  Xinst10 vdd intn vdd clock vdd pmos_tile_w1000_l150_nf2
  Xinst11 vdd intp vdd clock vdd pmos_tile_w1000_l150_nf2
.ENDS atoll_strong_arm_instance
```

# ■ Schematic and ■ Layout Design Tools

