

A 20-b accelerometer-based front-end for instrumentation

Enrico Sentieri – STMicroelectronics

Andrea Baschiroto – Univ. Milan-Bicocca

Microelectronics Users eXchange MUX-2011


CERN, June, 9th, 2011

Introduction

- **Introduction**
- **Design Objectives**
- **Noise Budget Partitioning**
- **Architecture**
- **ADC Architecture**

Sensor Accelerometers (1)

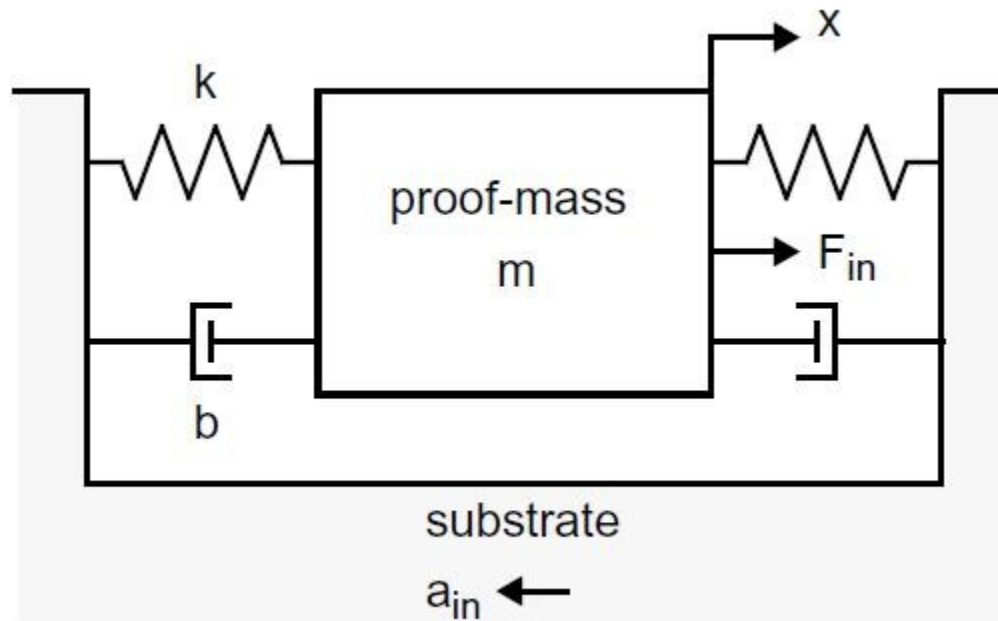
- Displacement accelerometers measure the displacement (x) of a suspended proof mass (m) in response to an input acceleration (a)



$$x = \frac{m}{k} \square a_{in}$$



Sensor Accelerometers (2)

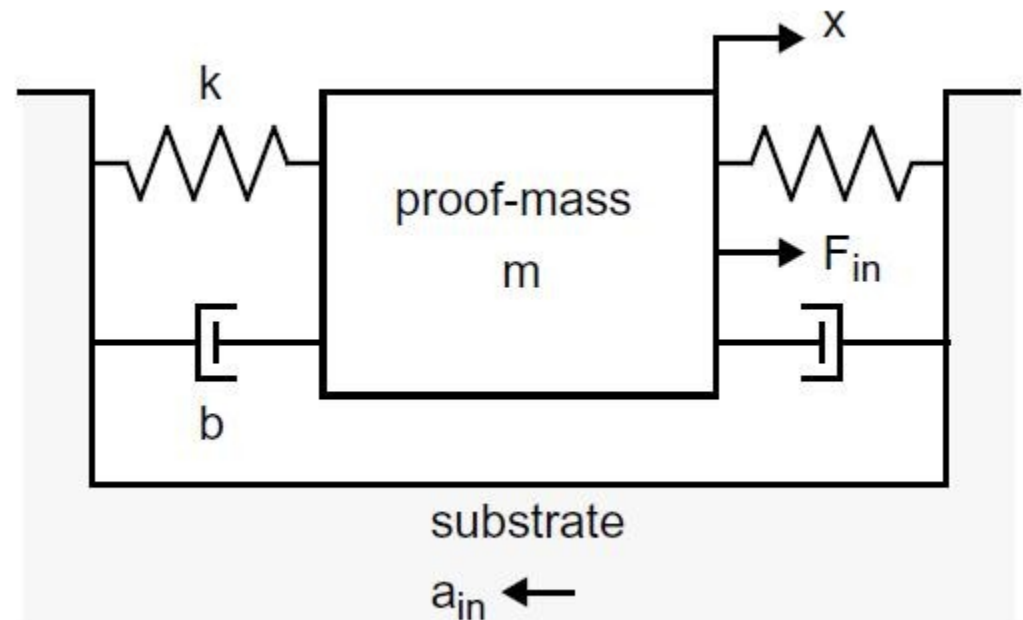- Displacement capacitive sensors are widely used in several systems
 - Accelerometers
 - Pressure sensors
 - Microphone
 - etc...



Sensor Accelerometer (3)

- Most popular technique to measure the proof mass displacement
 - → **Capacitive Position Sensing**
 - Different Sensor-Capacitive-Bridge topologies
 - Example:
 - Two nominally equal-sized capacitor are formed between the electrically conductive proof mass and stationary electrodes
 - When the substrate undergoes acceleration
 - → the proof mass displaces from the nominal position
 - → capacitive half-bridge unbalancement

 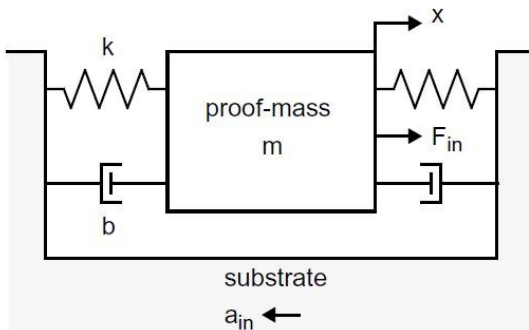


Sensor Accelerometer Interface (1)

- Capacitors sense AC signals
 - → AC modulation sources for capacitive sensing
 - The sensed signal is an Amplitude Modul. Signal
 - The acceleration signal modulates a HF carrier
- To extract the envelopment
 - → The sensed signal need to be demodulated or sampled
- Accelerometer sensitivity \approx modulation carrier amplitude

Sensor Accelerometer Interface (2)


- SC Architectures are very popular

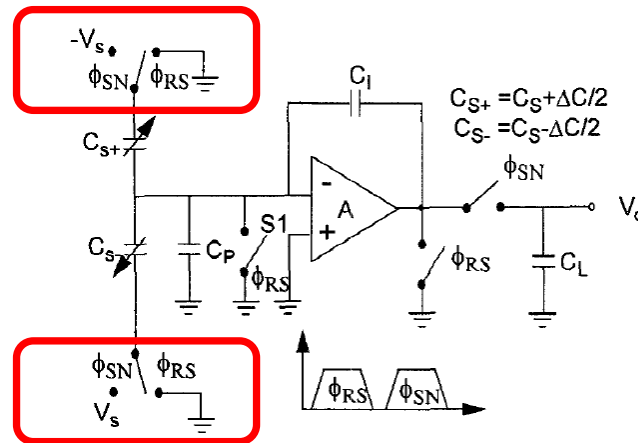

- MOS switches to connect the sensor and the circuit input.
 - The thermal noise of MOS switches (kT/C noise)
- SC circuits are sample data systems
 - It is not possible to insert an Anti-Alias filter between reading circuit and sensor
 - ➔ the input wide band noise is folded in base band
 - SC have much higher noise


Modulation/Demodulation

- Time Domain Signal Processing

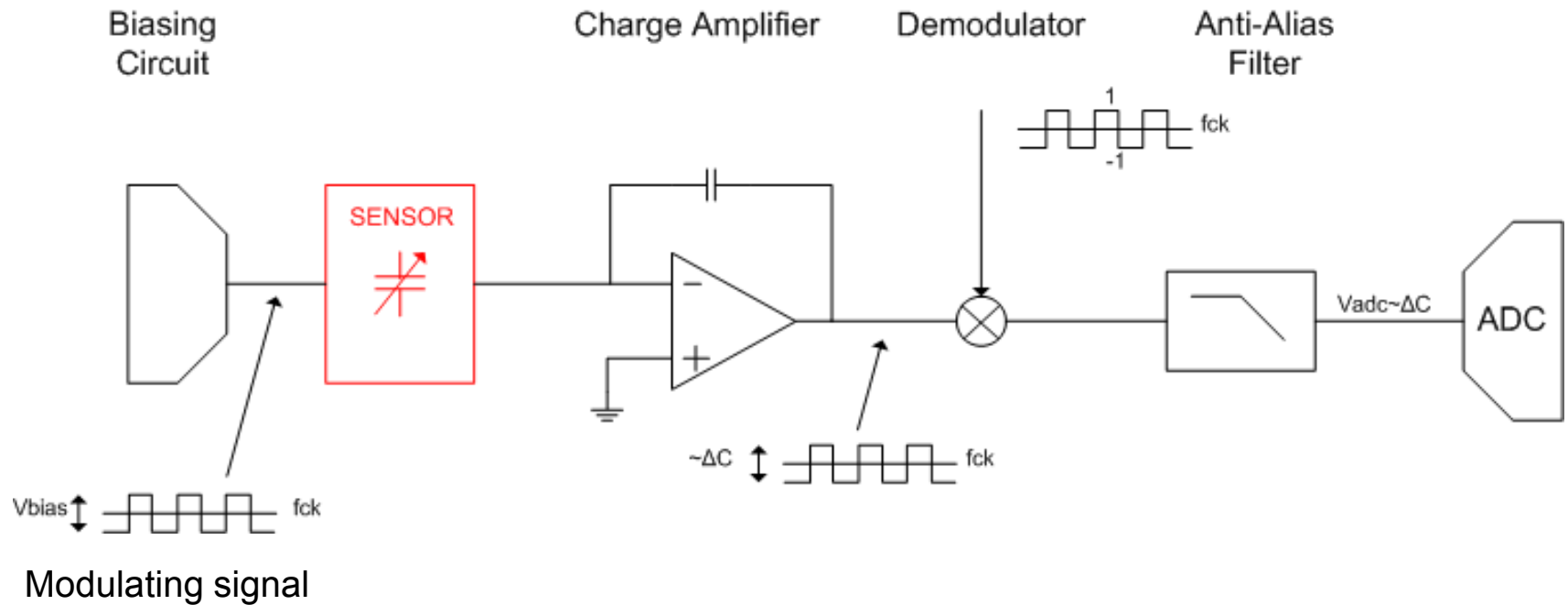

Modulation/Demodulation

- Frequency Domain Signal Processing

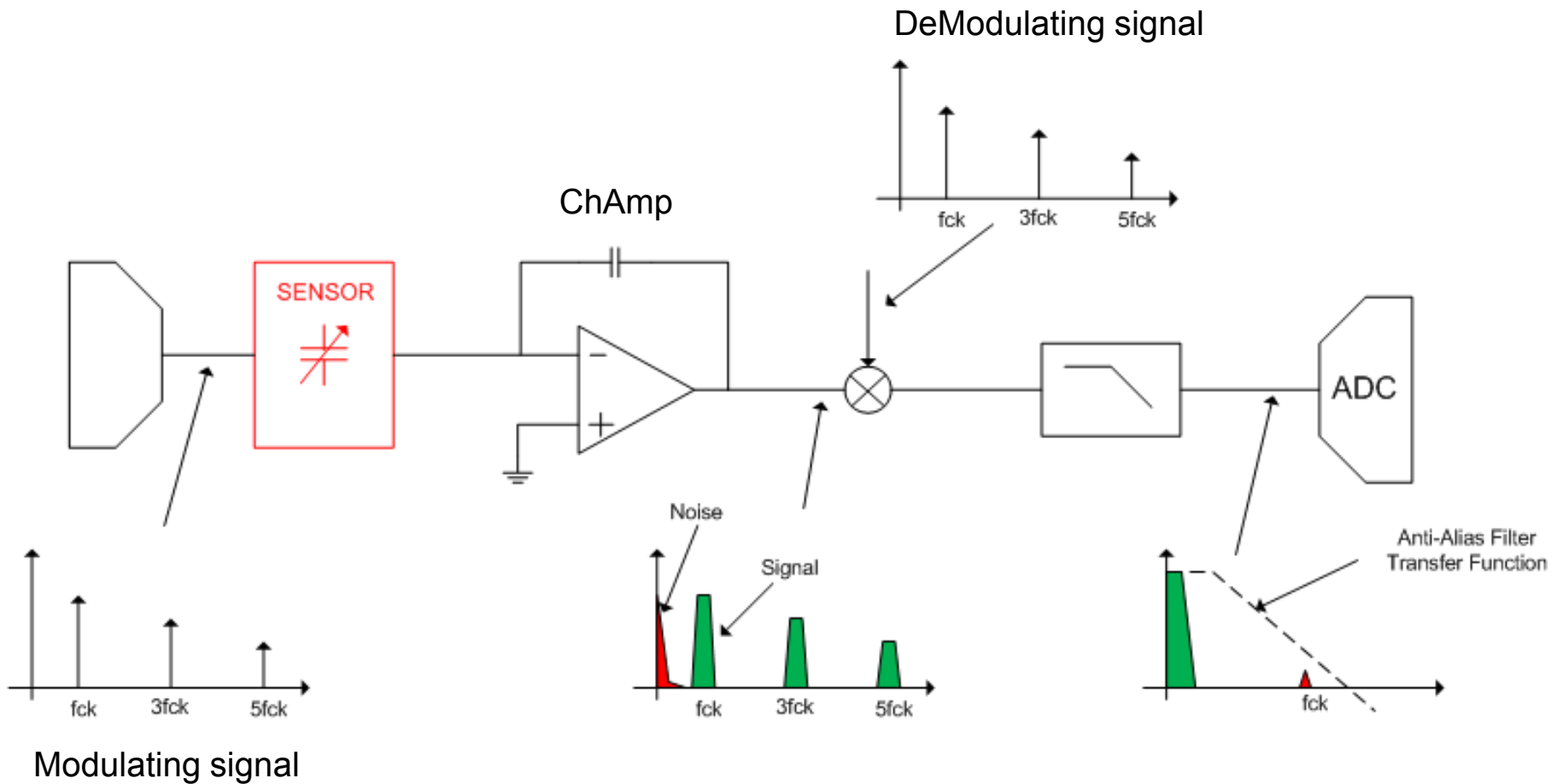

Gain Error due to Op-Amp band limited (1)


- Modulation → the acceleration is transposed to the odd harmonics frequencies of the Modulation signal

$$X_{2k+1} = \frac{4 \cdot V_0}{\pi} \cdot \frac{1}{2k+1}$$

- The ChAmp *transfer-function* shapes the modulated signal frequency spectrum
 - High-frequency component attenuation
 - → The Demodulated signal amplitude is affected by ChAmp Bandwidth
 - → Gain Error
 - Gain error depends on process and temperature variations


Gain Error due to opamp limited band (2)

Ideal Op-Amp (GBW=1GHz)

 

Gain Error due to opamp limited band (3)

Ideal Op-Amp (GBW=1MHz)

 

Mod/Dem-Freq vs. Power Consumption

- Higher Mod/Dem-Freq
 - 😊 In CMOS circuit, the electronics low frequency **flicker-noise** which often extends to low MHz
 - 😞 Larger opamp Gain-Bandwidth
 - → Higher Power Consumption
 - → trade-off between performances and power consumption
 - Typically the Mod/Dem-Freq (f_m) is from some tens of kHz to MHz
 - → $f_m = 100\text{kHz}$

Design Objectives

- ❑ Introduction
- ❑ **Design Objectives**
- ❑ Noise Budget Partitioning
- ❑ Architecture
- ❑ ADC Architecture


Design Objectives (1)

- Design a digitizing accelerometer interface that uses the full bandwidth and dynamic range of the sensor
 - → The Sensor Signal Full-Scale is $\pm 2G$
 - → The total equivalent acceleration noise $< 2.5\mu G$
 - sensor + electronic

$$SNR = 20 \log_{10} \left(\frac{2G}{\sqrt{2}} \frac{1}{2.5\mu G} \right) = 115dB$$


Design Objectives (2)

- Low power consumption
 - Architecture choice
 - → Open-Loop Capacitive sensor Interface
 - Interface Topology
 - → Charge Sensitive Amplifier with modulated input and synchronously demodulated output
- The capacitive bridge is driven (modulated) by a squared wave voltage
 - Gain error (due to Sensor and Integrated Circuit process variation) has to be compensated
- Bias Voltage Amplitude → 10b resolution programmable

 


Capacitive Sensor

 - The Capacitive sensor
 - → fully-differential
 - The bridge is driven by a differential signal **a** & **b**
 - With an acceleration
 - the capacitive bridge is unbalanced
 - a differential charge is injected in the pins **A** & **B**



Differential charge \approx acceleration

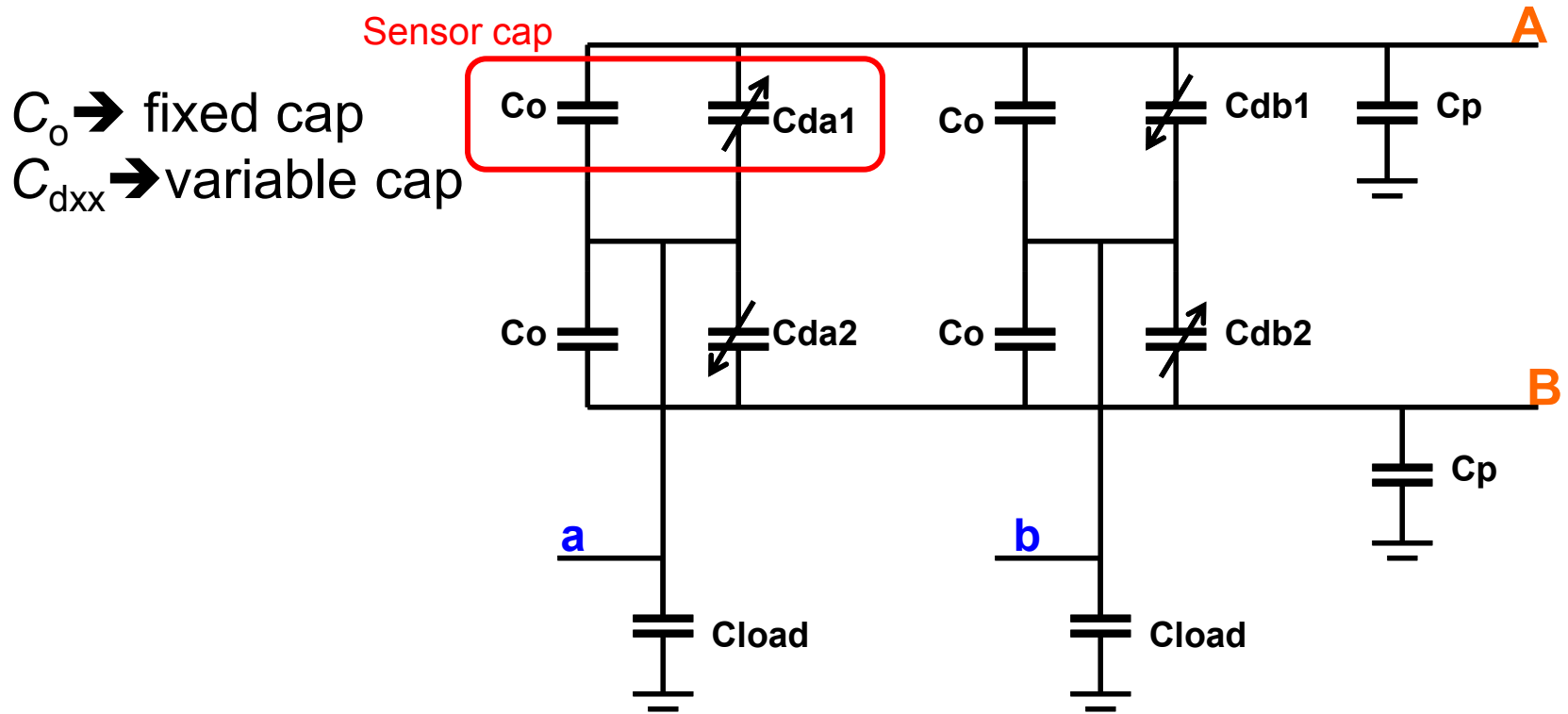Capacitive Sensor Equivalent electrical Model



a&b \rightarrow Modulating Sensor Pin

A&B \rightarrow Reading Sensor Pin


$$C_{da1} = C_{db2} = -C_{da2} = -C_{db1} = SF \cdot a$$

SF : Scale Factor [F/g]
a : acceleration [g]


Sensor Topologies:
 Jiangfeng Wu. "Sensing and Control Electronics for Low-Mass Low-Capacitance MEMS Accelerometers", Department of Electrical and Computer Engineering, Carnegie Mellon University, Spring 2002.

Capacitive Sensor Parameters

- Sensor Input and Interconnection Capacitance
 - $\rightarrow C_p = 12\text{pF}$
- $C_{\text{load}} = 20\text{pF}$
- Sensor cap
 - $C_o = 1\text{pF}$
- Scale Factor
 - $\rightarrow SF = 300\text{fF/G}$
- Sensor Dynamic Range
 - $\rightarrow \pm 2\text{G} \rightarrow S = 2\text{G}$
- Sensor Noise Density
 - $\rightarrow a_{\text{sn}} = 100\text{nG}/\sqrt{\text{Hz}}$
- Sensor Bandwidth
 - $\rightarrow BW = 300\text{Hz}$

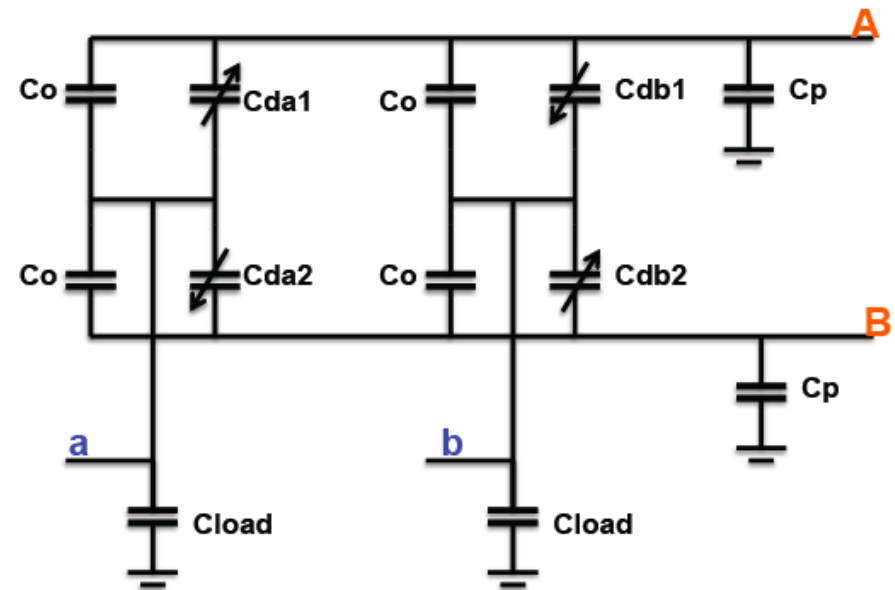

Ideal Sensor Accelerometer Interface

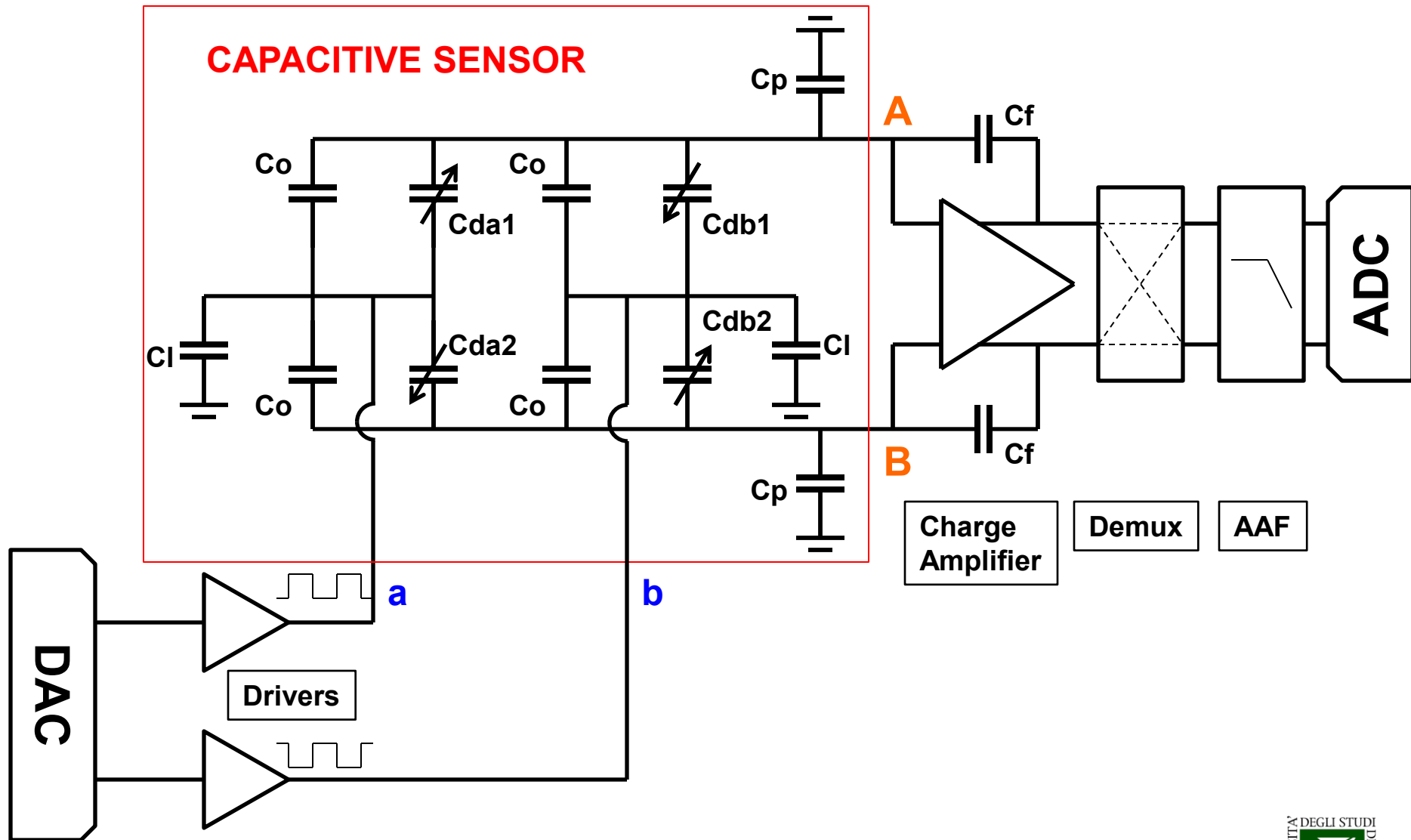

Technology Choice(1)

- The technology choice driven by:
 - Performance
 - Cost
 - Process Maturity
 - Analog Option Required

Technology Choice (2)

- Standard CMOS technology with double thick oxide
- A rough system analysis
 - → more than 90% device area is used for analog blocks
 - → No need to use technology with high level of integration density
 - → The technology choice is driven by analog requirement
- A Mature technology with two different thick oxide MOS has been selected:
 - 70Å (3.3V gate, 0.350µm minimum channel length)
 - 120Å (5.0V gate, 0.500µm minimum channel length)
 - The 5.0V MOS slower and noisier than 3.3V MOS
- Two power supply domains (5.0V & 3.3V) are available

Technology Choice (3)

- Resistors
 - Linear Resistor (Doped-Poly resistor)
 - Diffused Resistor
 - poor linearity
 - no flicker noise compared to the poly resistor
 - HIPO (High resistance poly) resistor
 - higher sheet resistance compared to poly resistor.
 - extra mask → higher cost
- Capacitor
 - High-linearity caps required for the Charge Amplifier feedback capacitor and ADC (Switched Capacitor) → Metal to metal capacitor is the best choice
 - MIM (Metal Insulator Metal)
 - Thin oxide → High density level
 - Extra Masks → Higher Cost
 - Fringed Capacitor
 - Lower density
 - No extra mask


Noise Budget Partitioning

- Introduction
- Design Objectives
- **Noise Budget Partitioning**
- Architecture
- ADC Architecture

Noise Budget Partitioning (1)

- Starting from high level specifications
 - → define the specification for each blocks of the system
 - → identify critical blocks
 - → roughly definition of a suitable architecture of each block

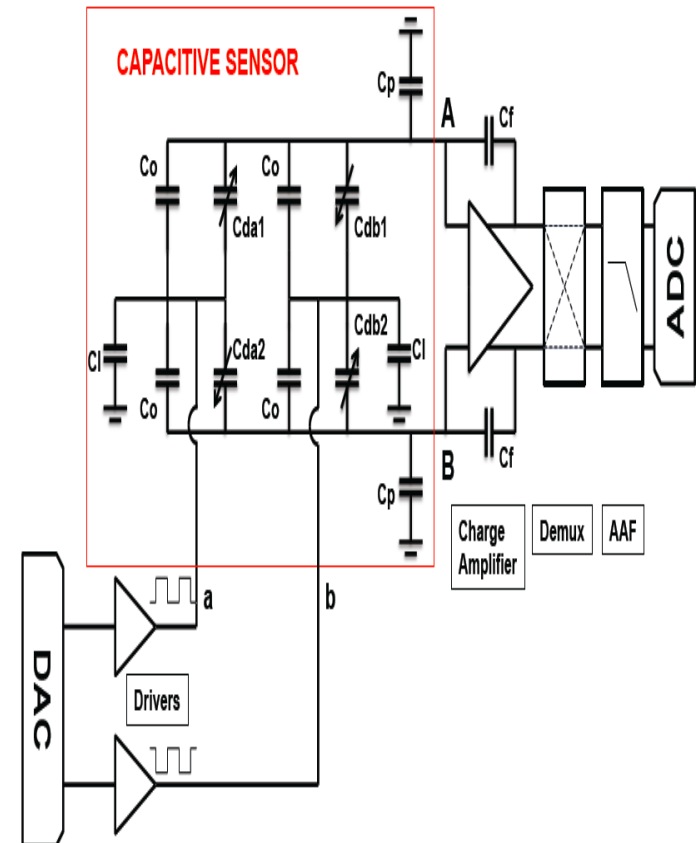- Simplifications
 - This preliminary analysis should be done not considering mod/dem effects



Noise Budget Partitioning (2)

- The **Noise Budget partitioning** is an iterative design process
- Some design specifications are defined based on preliminary analysis/assumptions
 - → the required performances for each block are evaluated
 - in case of any issue, the assumptions will be modified
- It's quite impossible, at the first run, to identify all the critical design parameter

Noise Budget Partitioning (3)

- Target: Total noise $\rightarrow a_{n_rms} = 2.5\mu\text{G}$
- Two different main Noise contributors:
 - **Sensor Noise** (Brownian Noise) $\rightarrow a_{sn_rms}$
 - **Electronic Noise** $\rightarrow a_{en_rms}$
 - Quantization Noise, Thermal Noise, & Flicker Noise

- **Sensor Noise** (a_{sn_rms}):


$$a_{sn_rms} = a_{sn} \square \sqrt{BW} = 100\text{nG}/\sqrt{\text{Hz}} \square \sqrt{300\text{Hz}} = 1.73 \mu\text{G}$$

- **Electronic Noise** \rightarrow Equivalent Acceleration noise is evaluated to match the design Objectives:

$$a_{en_rms} = \sqrt{a_{n_rms}^2 - a_{sn_rms}^2} = 1.81\mu\text{G}$$

Noise Budget Partitioning

- Assuming no-noise sensor

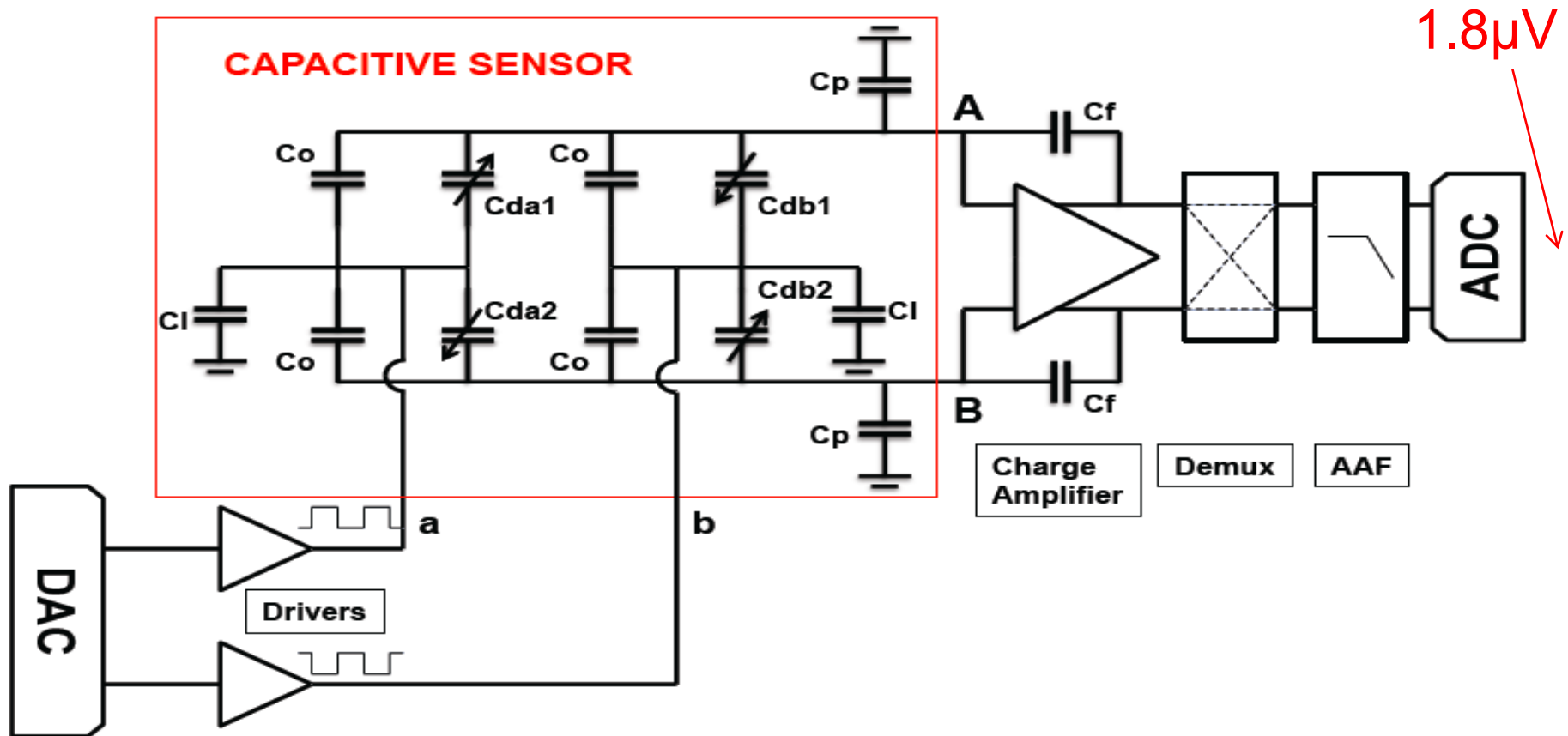

Noise Budget Partitioning (4)

- SNR due to the only electronic Noise evaluated at Sensor level:

$$SNR_e = 20 \log_{10} \left(\frac{S}{\sqrt{2}} \frac{1}{a_{en_rms}} \right) = 117.9dB$$

- → First design specification,
 - the SNR @ADC-output > 117.9dB
 - → ADC resolution has to be:

$$ENOB_{ADC} > \frac{SNR_e - 1.76}{6.02} = 19.3bit$$

ADC Performances (1)

- ADC resolution >19.3 bit
 - SC- $\Sigma\Delta$ Architecture
 - → the only one to satisfy this challenging design specifications.
 - Oversampled ADC architecture → Relaxed the Anti-Alias Filter requirements specification
- The small signal bandwidth
 - Critical opamp flicker-noise
 - → the ADC with *Correlated Double Sampling* or *Chopper Stabilization* technique

ADC Performances (2)

- Which Power Supply?
 - ADC under 5V supply domain
 - → higher reference voltage compared to 3.3V supply domain
 - → Sample capacitor reduction (less area) and/or reduce the Oversampling Ratio (smaller opamp bandwidth)

$$V_{\text{signal}} \propto V_{\text{ref}}$$

$$V_{\text{noise}} \propto \sqrt{\frac{K_b \square T}{C_s \square OR}}$$

V_{ref} : ADC reference Voltage

K_b : Boltzmann Constant


T: Temperature

C_s : Sampling Capacitor

OR: Oversampling Ratio

ADC Performances (3)

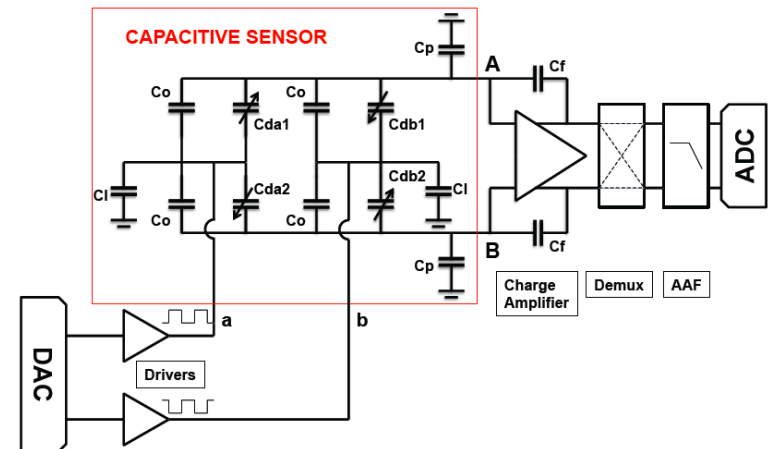- Which Power Supply?
 - 5.0V MOS have *higher 1/f noise* than 3.3V MOS
 - Increased oxide thickness → Increased trap number in the silicon oxide interface.
- If the ADC is designed under 5.0V domain
 - → The Charge-Amplifier to be designed under the same supply domain to use all the available ADC dynamic range



ADC Performances (4)

- Both solutions have some advantages (larger signal @5V) and some drawbacks (larger 1/f noise @5V)
- The best compromise performance vs. power consumption has been achieved supplying ***the ADC and Charge Amplifier at 3.3V***

ADC Performances (5)

Assumptions:

- ADC Differential Reference Voltage $\rightarrow 2.5V_{\text{peak}}$
 - Possible under 3.3V domain
- Maximum ADC Input signal $\rightarrow 2.0V_{\text{peak}}$
 - To avoid Modulator Saturation issue
 - ~2dB of margin
- ADC resolution required 20 bit

ADC Performances (6)

- Total Noise at ADC output

$$V_{n_{@ADCoutput}} = \frac{S_{in_ADC_{max}}}{\sqrt{2}} \square 10^{-\frac{SNR_e}{20}} = \frac{2}{\sqrt{2}} \square 10^{-\frac{117.9}{20}} = 1.8 \mu V$$

- ADC Noise

- Assuming dominant quantization noise

$$V_{n_{ADC}} = \frac{LSB}{\sqrt{12}} = \frac{V_{in_ADC_{max}}}{2^{(nbit-1)}} \square \frac{1}{\sqrt{12}} = \frac{2}{2^{19}} \square \frac{1}{\sqrt{12}} = 1.1 \mu V$$

Biasing and Reading Noise partitioning


$$V_{nBiasRead} = \sqrt{V_{n_@ADCout}^2 - V_{nADC}^2} = 1.42 \mu V$$

- The system is divided in to two different macro blocks:
 - Reading (Charge Amplifier and AAF)
 - Biasing (DAC and Driver)


	Noise Biasing/Noise Reading				
	3/1	2/1	1/1	1/2	1/3
Noise Biasing V_{nBias}	1.35 μV	1.27 μV	1 μV	0.63 μV	0.45 μV
Noise Reading V_{nRead}	0.45 μV	0.63 μV	1 μV	1.27 μV	1.35 μV

Noise Budget Partitioning

- Assuming no-noise sensor

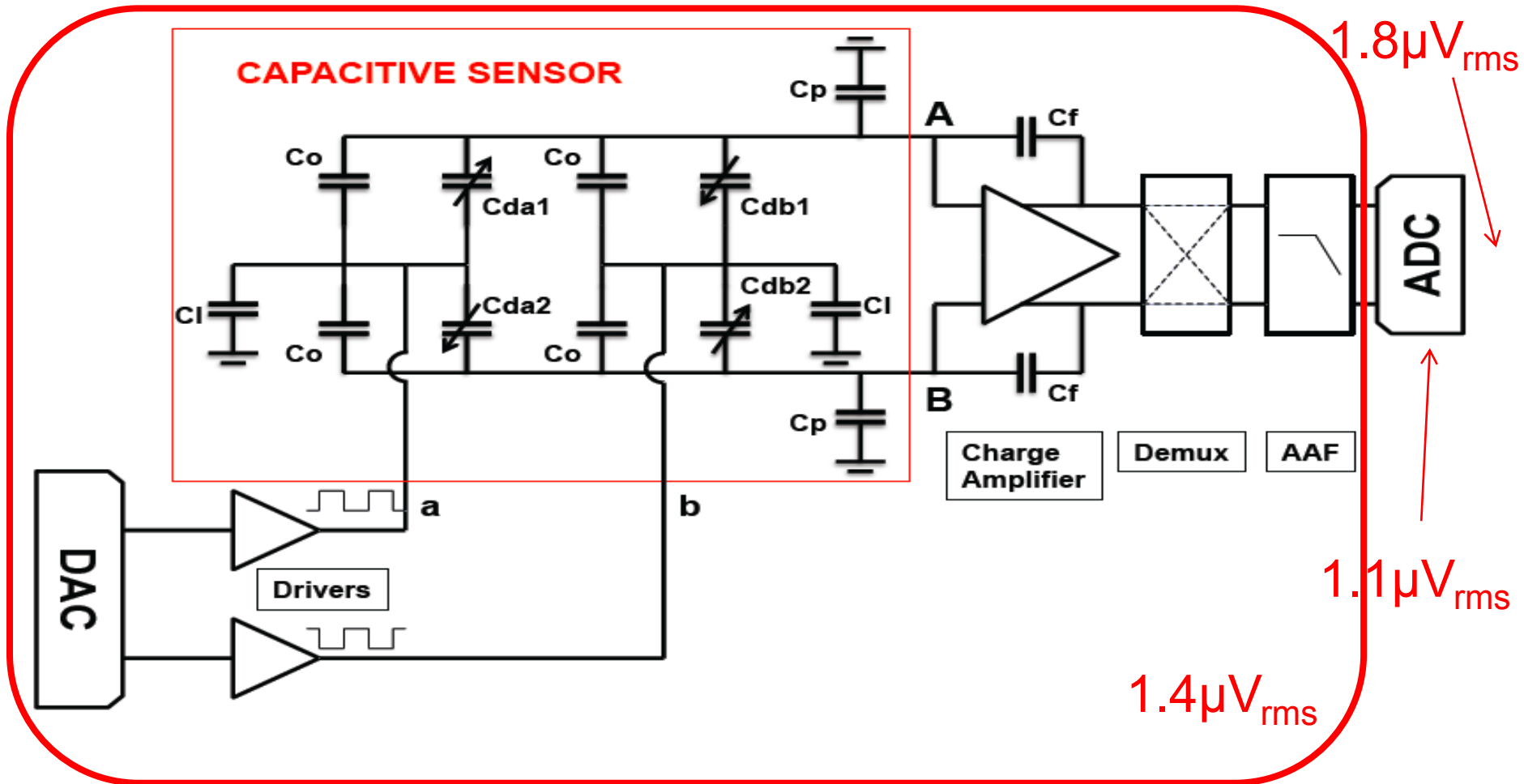

Sensor Transfer Function

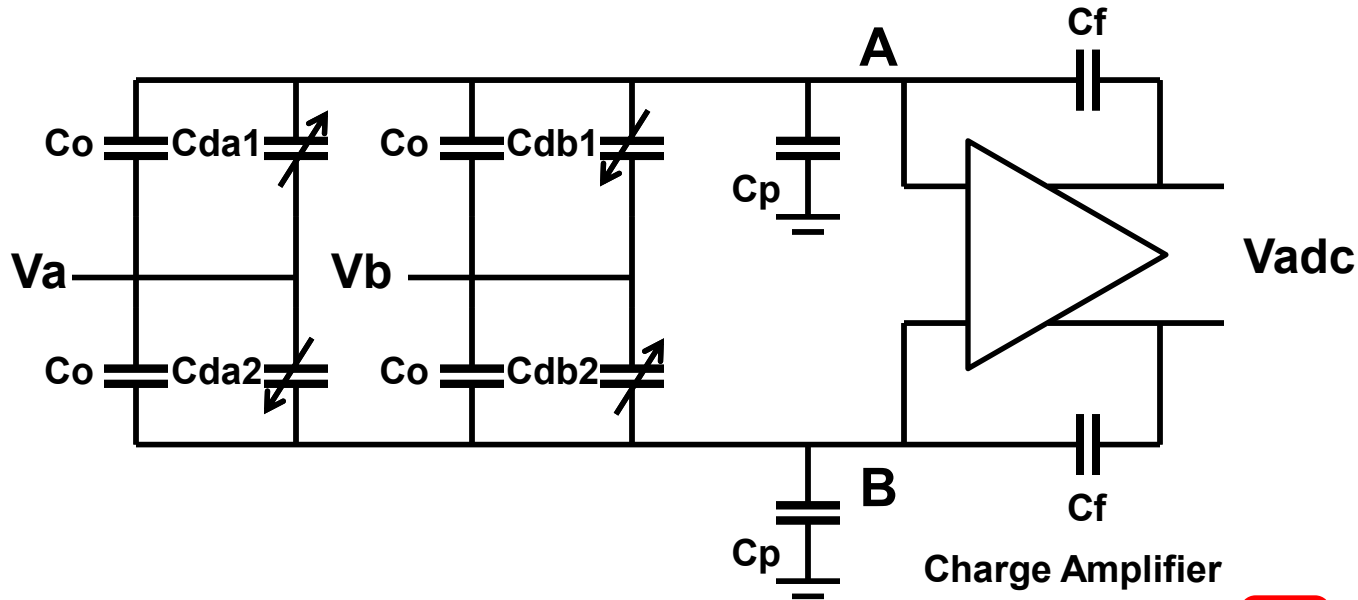


$$V_{s@ADCinput} = V_a \cdot \frac{C_{da1}}{C_f} + V_b \cdot \frac{C_{db1}}{C_f} - V_a \cdot \frac{C_{da2}}{C_f} - V_b \cdot \frac{C_{db2}}{C_f} = 2 \cdot \frac{C_d}{C_f} \cdot (V_a - V_b)$$

$$V_{s@ADCinput} = 2 \cdot \frac{SF \cdot a}{C_f} \cdot V_{bias}$$

V_{bias} is the differential Voltage applied to the sensor

$$\frac{V_{s@ADCinput}}{a} = 2 \cdot \frac{V_{bias}}{C_f} \cdot SF$$


Biassing Noise Gain

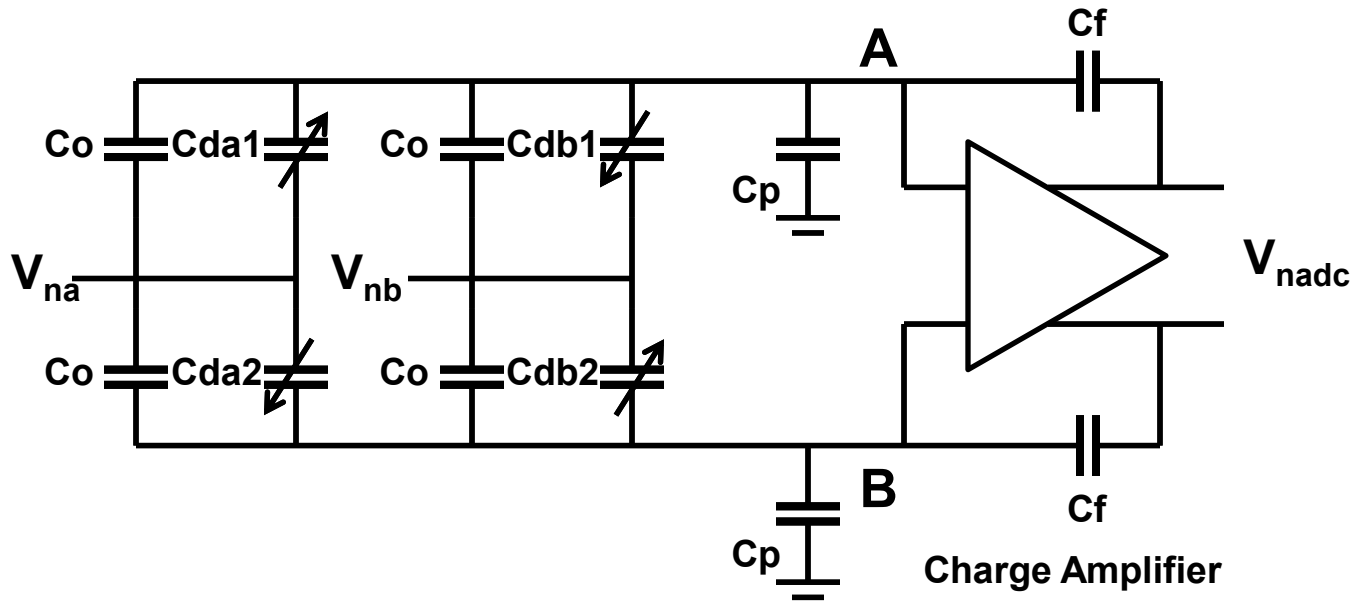

$$V_{na@ADCinput}^2 = V_{na}^2 \frac{2 C_d^2}{C_f^2} + V_{nb}^2 \frac{2 C_d^2}{C_f^2}$$

$$V_{na@ADCinput} = \frac{2 \cdot C_d}{C_f} \sqrt{V_{na}^2 + V_{nb}^2} = \frac{2 \cdot SF \cdot a}{C_f} \sqrt{V_{na}^2 + V_{nb}^2}$$

Charge Amplifier Noise Gain

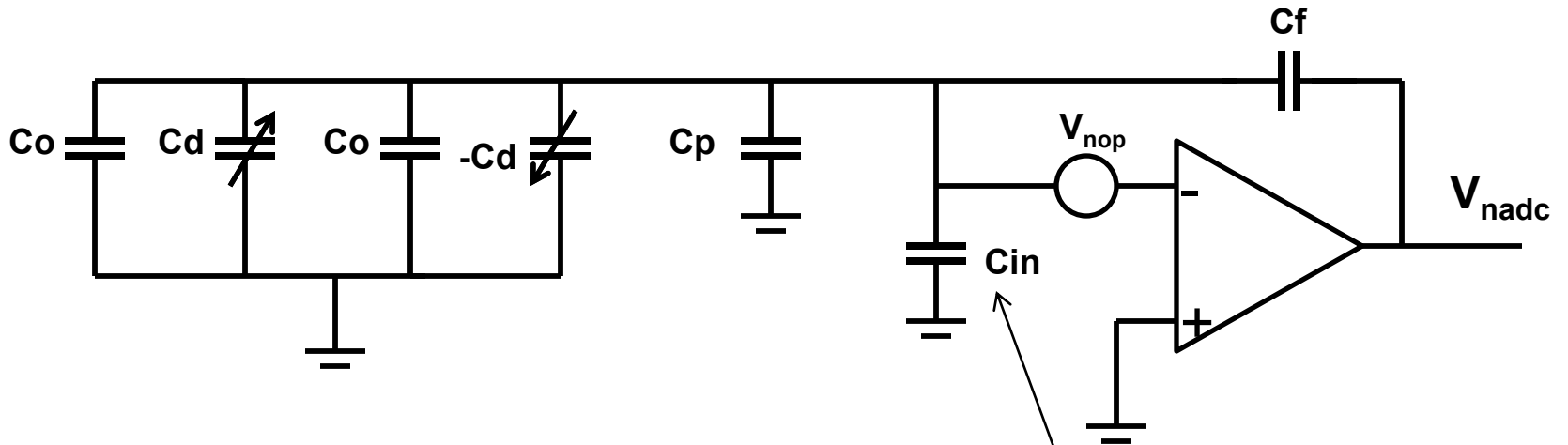

$$V_{nop@ADCinput} = V_{nop} \left[1 + \frac{2 \cdot C_o + C_p + C_{in}}{C_f} \right]$$

$$NG_{ChAmp} = 1 + \frac{2 \cdot C_o + C_p + C_{in}}{C_f}$$

$C_{in} \rightarrow$ Charge Amplifier Input Cap

Biasing Voltage (1)

$$\frac{V_{s@ADCInput}}{a} = 2 \cdot \frac{V_{bias}}{C_f} \cdot SF \quad NG_{ChAmp} = 1 + \frac{2 \cdot C_o + C_p + C_{in}}{C_f}$$

$$V_{nBias@ADCInput} = \frac{2 \cdot SF \cdot a}{C_f} \cdot \sqrt{V_{na}^2 + V_{nb}^2}$$

- To maximize the ADC input → two possibilities:
 - Increase the Bias Voltage
 - Decrease the ChAmp feedback cap (C_f)
 - → Increase the Charge Amplifier Gain
 - C_f ↓ → the (ChAmp & BiasCircuit) ADC input noise ↑
 - → No effect on the overall SNR

Biasing Voltage (2)

- To optimize SNR
 - $\rightarrow V_{\text{bias}}$ has to be maximized
 - \rightarrow The Sensor Drivers has to be realized under 5.0V Supply Domain
- Considering Supply Variation & Driver Output MOS headroom

$$\rightarrow V_{\text{bias}} = 4.5\text{V}$$

Charge Amplifier Feedback capacitor

- → $V_{bias} = 4.5V$
- The feedback cap (C_f) is evaluated to maximize ADC DR when the maximum acceleration (a_{max}) is applied to the sensor

$$V_{ADC} = 2 \cdot \frac{SF \cdot a}{C_f} \cdot V_{bias}$$

$$C_f = 2 \cdot SF \cdot a_{max} \cdot \frac{V_{bias}}{V_{ADCmax}} = 2 \cdot 300fF/G \cdot 2G \cdot \frac{4.5V}{2V} = 2.7pF$$

Biassing and Reading Noise partitioning (2)

- Read-out noise → Charge Amplifier noise

$$NG_{ChAmp} = 1 + \frac{2 \square C_o + C_p + C_{in}}{C_f} > 1 + \frac{2 \square C_o + C_p}{C_f} = 1 + \frac{2 + 12}{2.7} = 6.2$$

- The Charge Amplifier Input Noise is amplified

- Bias Noise Gain

$$NG_{Biasmax} = \frac{\Delta C_{max}}{C_f} = \frac{2 \times SF \times a_{max}}{C_f} = \frac{2 \times 300fF/G \times 2G}{2.7pF} = 0.44$$

- The Bias Input Noise is amplified

Biassing and Reading Noise partitioning (3)

- **Reading Noise** is more critical than **Biassing Noise** due to Charge Amplifier Noise Gain
 - Strategy: Increasing the Reading Noise Budget compared to the Biassing Noise Budget
 - 1/2 may be the best compromise to increase the reading Noise Budget
 - 1/3 small improvement for Reading and bigger worsening for the Biassing Noise Budget


	Noise Biassing/Noise Reading				
	3/1	2/1	1/1	1/2	1/3
Noise Biassing V_{nBias}	1.35 μ V	1.27 μ V	1 μ V	0.63 μ V	0.45 μ V
Noise Reading V_{nRead}	0.45 μ V	0.63 μ V	1 μ V	1.27 μ V	1.35 μ V

$$V_{nRead @ ADCInput} = 1.27\mu V$$

$$V_{nBias @ ADCInput} = 0.63\mu V \quad \square \quad V_{nBias @ DriverOutput} = \frac{0.63\mu V}{0.44} = 1.43\mu V$$

Noise Budget Partitioning

- Assuming no-noise sensor

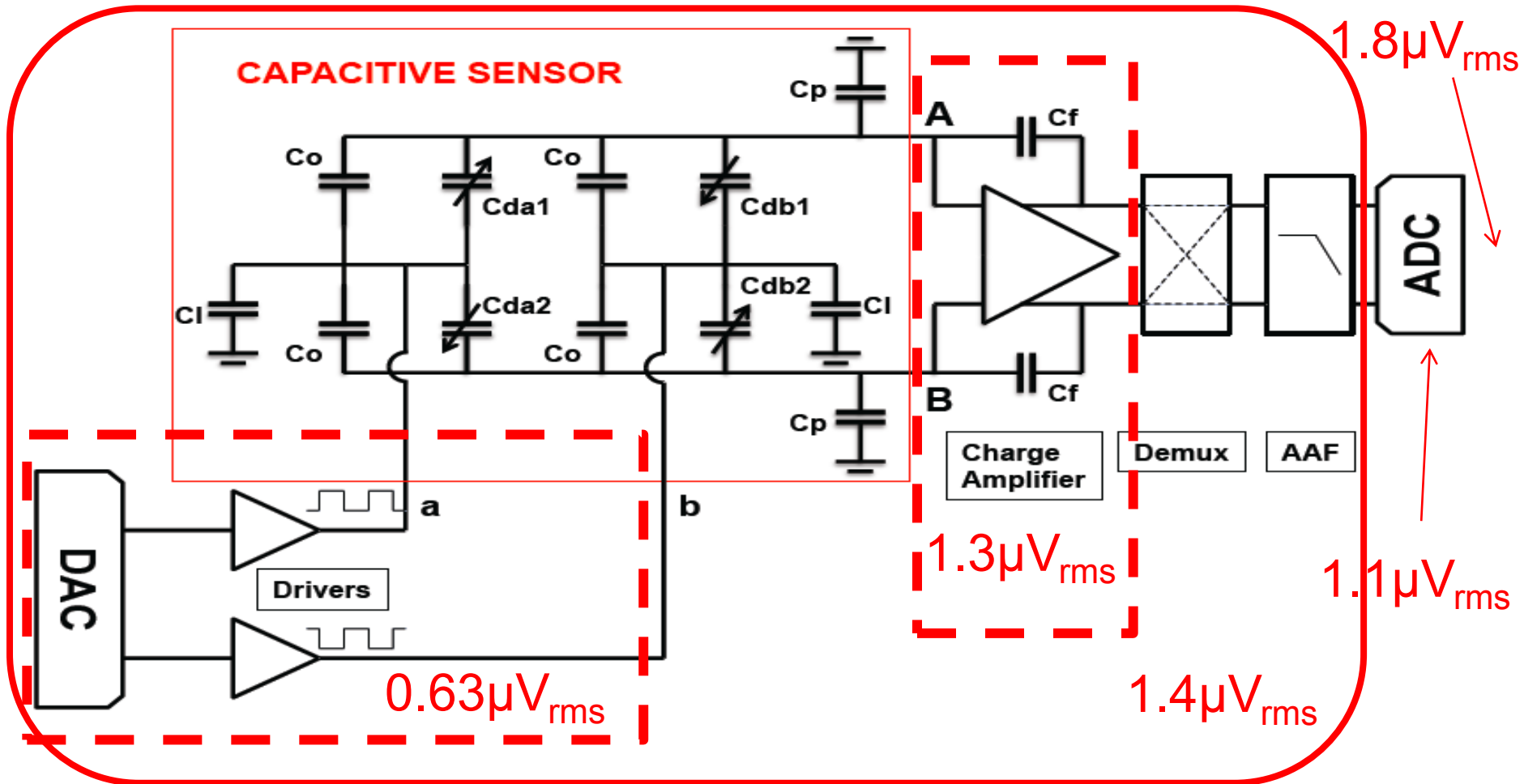

Noise Budget Partitioning Conclusion


- Starting from the high level system specifications
 - → a preliminary noise breakdown
- To descend the hierarchy, it is necessary to define the architecture of each block
 - → Next step → defining the circuits architecture and their noise budget
- It is mandatory to take into account the mod/dem effects

Architecture


- ❑ Introduction
- ❑ Design Objectives
- ❑ Noise Budget Partitioning
- ❑ **Architecture**
- ❑ ADC Architecture

Charge Amplifier

- Assuming no-noise sensor

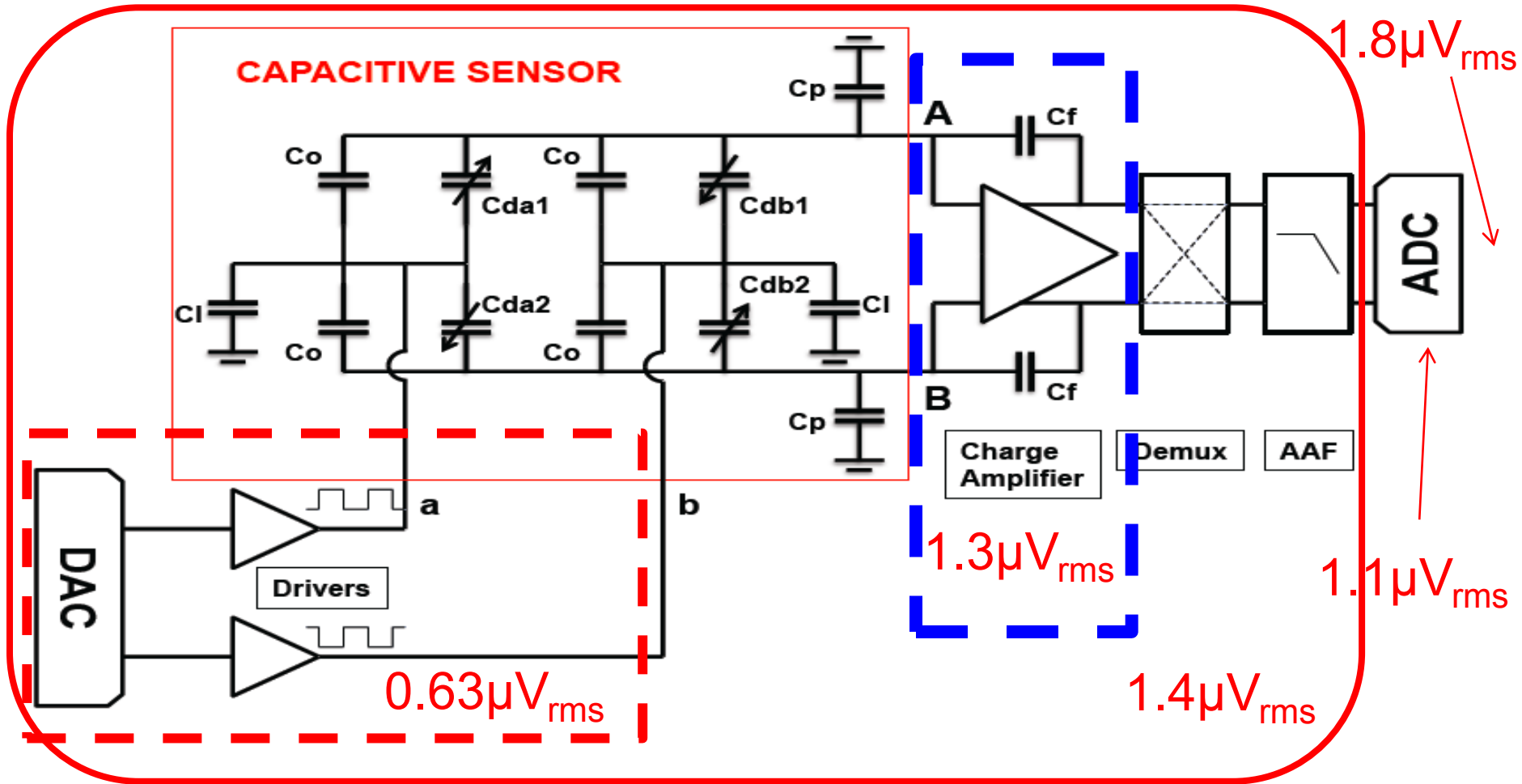



Charge Amplifier (1)

 

- Charge Amplifier needs a opamp input DC polarization

Charge Amplifier (2)
  
$$\frac{V_{ChAmp}}{V_s} = \frac{R_f \square C_s \square s}{1 + R_f \square C_f \square s}$$




- The Charge Amplifier Signal is Amplitude Modulated
 - Carrier frequency $\rightarrow f_m$
- To reduce the Charge Amplifier gain error
 - The pole frequency has to be lower than modulation frequency

Charge Amplifier (3)

$$V_n^2 = 4 \cdot k_b \cdot T \cdot R_f$$

$$V_{nChAmp} = \frac{V_n}{1 + C_f \cdot R_f \cdot s}$$
 
$$V_{nChAmp} @f=f_m = \sqrt{\frac{2 \cdot 4 \cdot k_b \cdot T \cdot R_f}{1 + (2 \cdot \pi \cdot f_m \cdot R_f \cdot C_f)^2}} \cdot \sqrt{\frac{2 \cdot k_b \cdot T}{R_f \cdot (\pi \cdot f_m \cdot C_f)^2}}$$



- $R_f \uparrow$ \rightarrow Output Noise density (due to R_f) \downarrow

Charge Amplifier (4)

- The noise spec $\rightarrow V_{nRead} = 1.27\mu V$
- Assumption:
 - R_f -Noise $\approx 1/3$ of the to Total Noise (negligible effect in the noise power budget)
- The ChAmp Output Noise density due to feedback resistor is:

$$\frac{1.27\mu V}{3 \sqrt{300}} = 24nV / \sqrt{Hz}$$

- Assumption: Modulation frequency $f_m = 100kHz$


$$R_f \approx \frac{2 \cdot k_b \cdot T}{V_{n_ChAmp@f=f_m}^2 \cdot (\pi \cdot f_m \cdot C_f)^2} = 20M\Omega$$

$$f_{pole} = \frac{1}{2 \cdot \pi \cdot R_f \cdot C_f} = 3kHz \ll f_m$$

Charge Amplifier (5)


- Large R_f 's
 - are difficult to be integrated in standard CMOS process
 - require large Area

 - Switched Capacitor
- MOS operating in triode
- Integrated Resistor



Charge Amplifier (6)


- Switched Capacitor capacitance sensing

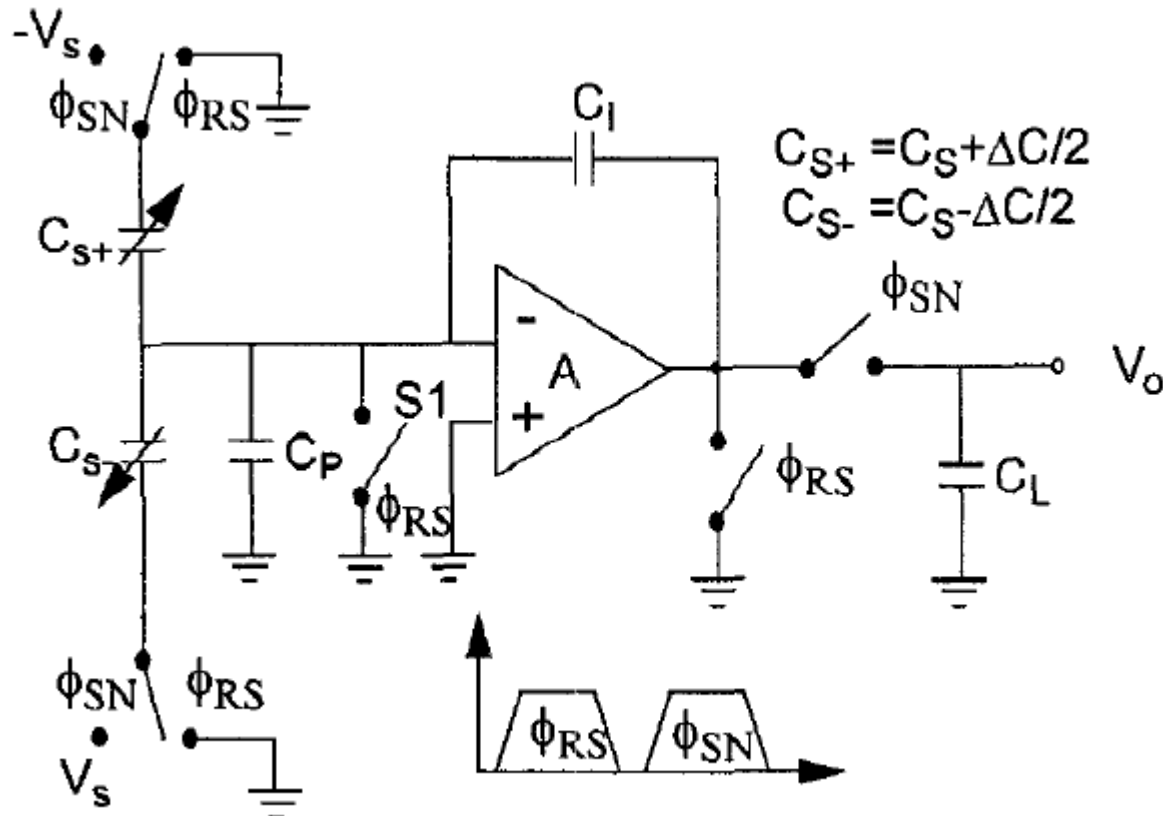

“Correlated Double Sampling in Capacitive Position Sensing Circuits for Micromachined Applications”
 Wongkomet, N.; Boser, B.E.;1998

Charge Amplifier (7)

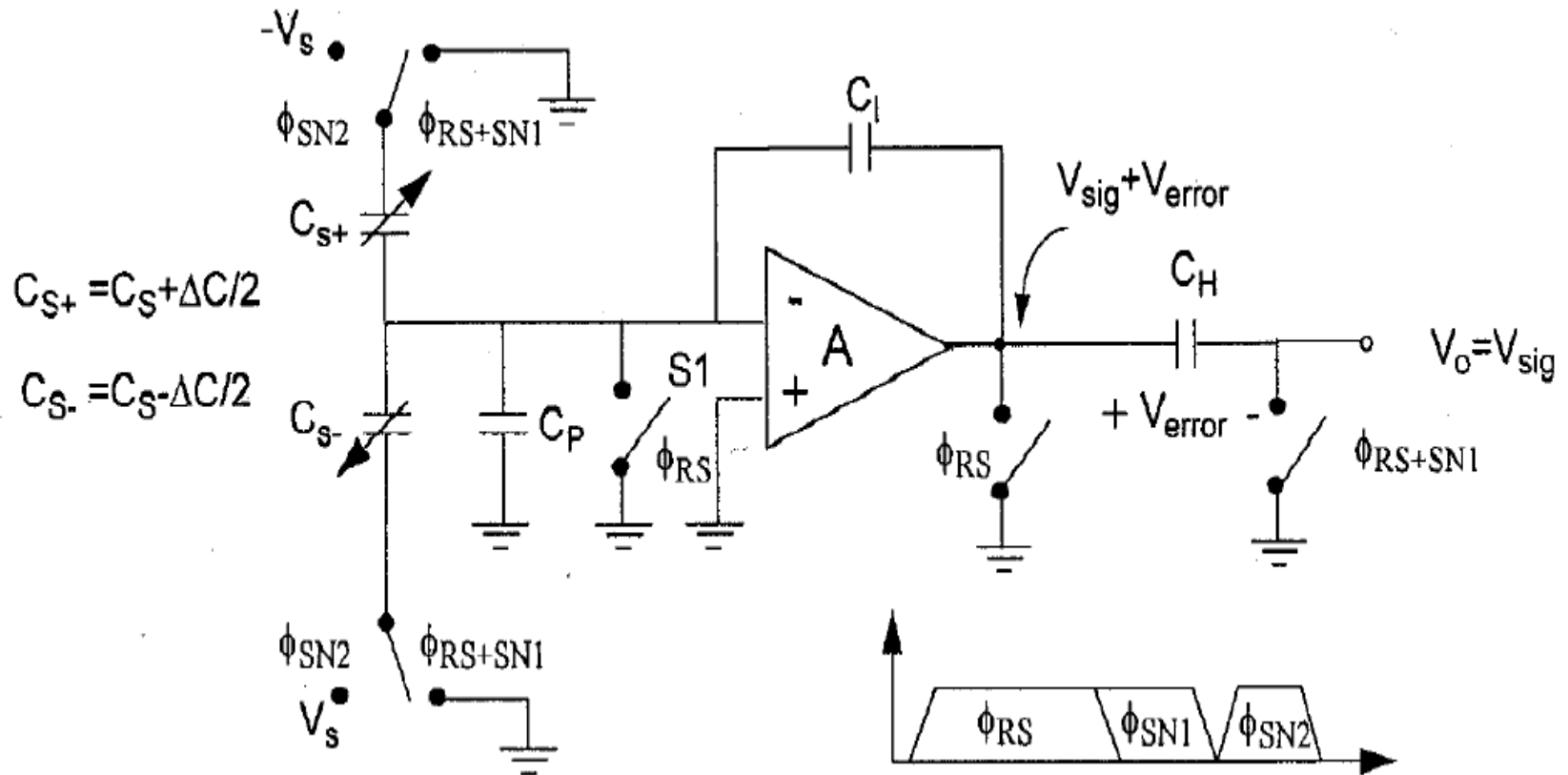
- Switched Capacitor capacitance sensing with CDS



“Correlated Double Sampling in Capacitive Position Sensing Circuits for Micromachined Applications”
 Wongkomet, N.; Boser, B.E.; 1998

Charge Amplifier (8)

- MOS operating in Triode region

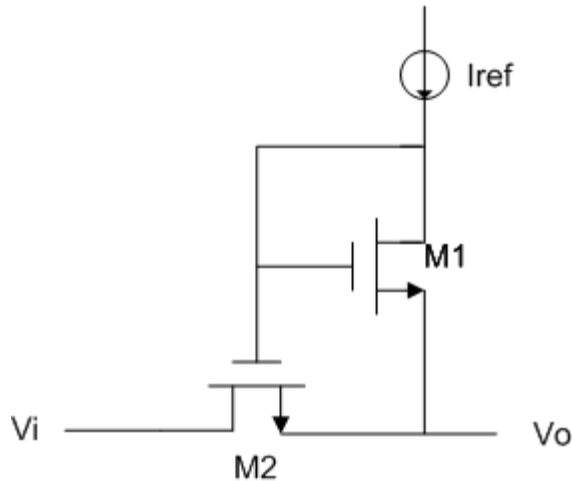

$$R = \frac{(W/L)_1}{(W/L)_2} \square N \square R_{ref}$$

"Single-Chip Surface Micromachined Integrated Gyroscope with 50°/h Allan Deviation"
J.A. green, S. J. Sherman, J.F. Chang and S.R. Lewis - 2002

- Good operation with small $(V_o - V_i)$ to keep M2 in triode
 - → Same ChAmp Input and Output
 - → This solution is mainly used when a pre-Amplifier is inserted after the Charge Amplifier

Charge Amplifier (9)

■ Integrated Resistor

- 😊 No Noise Folding
- 😊 Better Linearity/No dynamic limitation
- 😊 Better Noise Performance
- 😞 Huge Area increments

■ Roughly Area Estimation

- **Doped Poly Typical** $R_s(\Omega/\text{sq})=300 \rightarrow$ area for $2 \times 20\text{M}\Omega$ & $W=1\mu\text{m}$

$$A = \frac{2 \square 20\text{M}\Omega}{300} = 0.13\text{mm}^2$$

- **HIPO** $R_s(\Omega/\text{sq})=1000 \rightarrow$ area for $2 \times 20\text{M}\Omega$ & $W=1\mu\text{m}$

$$A = \frac{2 \square 20\text{M}\Omega}{1000} = 0.04\text{mm}^2$$

Charge Amplifier (10)


- Diffused Resistor have R_s higher or equal to HIPO resistor
 - 😊 Standard process (no extra mask)
 - 😞 Linearity Issue
 - 😞 Junction Leakage at the high Impedance Input of the Charge Amplifier

Charge Amplifier (11)

- The choice between **HIPO** and doped Poly depends on cost evaluation (mask/process vs. area)
- The real area used for the feedback resistor is higher than first roughly estimation
 - Distance between modules
 - Active area density


Charge Amplifier (12)

- ChAmp opamp
 - Output swing & Anti-Alias Filter Resistive Load
 - → Two-Stage topology
 - High current during the carrier rising/falling edge
 - → Class-AB output stage
 - Overall gain error reduction
 - → Closed-Loop gain-bandwidth $> 10 \times f_m$
 - ChAmp feedback factor $\approx 1/NG_{\text{ChAmp}} = 1/6$
 - Opamp noise is chopped
 - → Thermal noise dominates
 - → Thermal noise reduction
 - Large differential pairs and current generator MOS
 - → high parasitic capacitor
 - → stability Issue

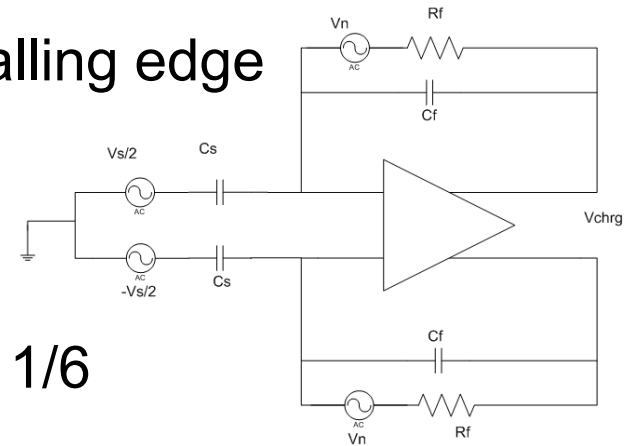

Charge Amplifier (13)

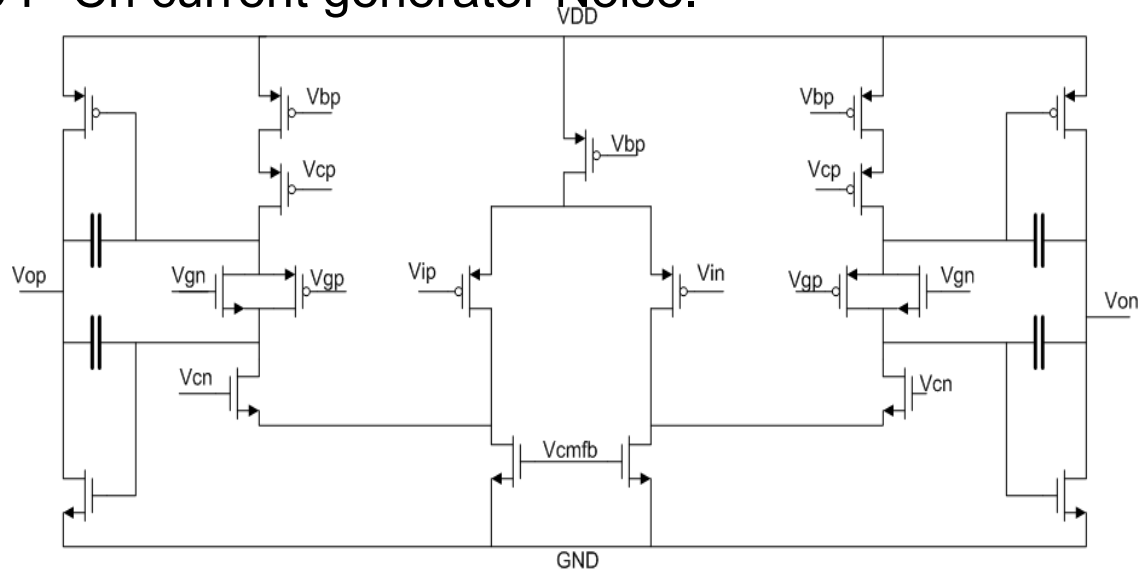- Usually LN → PMOS input differential pair (PMOS have lower 1/f noise than NMOS)
- Recent technologies have small difference between P-Ch and N-Ch flicker noise → Op-Amp with N-Ch differential pair can achieve better Noise performance
- The advantages of N-Ch differential pairs:
 - Higher g_m → Lower thermal noise
 - Higher rejection of the P-Ch current generator Noise.
- Opamp noise is chopped




Charge Amplifier (14)

- Low Noise circuits design
 - large transistor
 - → large channel width and MOS area
 - → thermal and 1/f noise reduction
- In case of capacitive sensing

$$NG_{ChAmp} = 1 + \frac{2 \square C_o + C_p + C_{in}}{C_f}$$

- Large Transistor
 - → Large gate capacitance
 - Increased Charge Amplifier Noise Gain

Charge Amplifier (15)

 

- For dominant thermal noise (chopper)
- Minimum noise for $C_{in} \leq C_{sensor} + C_{interconnect}$

$$NG_{ChAmp} = 1 + \frac{2 \square C_o + C_p}{C_f} = 6.2$$



$$\frac{V_{nRead@ADCInput}}{NG_{ChAmp} \square \sqrt{BW}} = \frac{1.27 \mu V}{6.2 \square \sqrt{300 Hz}} \square 11 nV / \sqrt{Hz}$$

Charge Amplifier (16)

- This rough result is useful only to understand the challenge of the Charge Amplifier opamp design
 - → $11\text{nV}/\sqrt{\text{Hz}}$ is an aggressive input noise target
- To reduce the noise
 - Sol1 → mod/dem frequency (f_m) increase
 - → $f_m >$ opamp flicker corner frequency
 - → higher power consumption (the Mod/Dem frequency effects all the circuits specifications)
 - Complexity in circuits Implementation
 - Sol2 → chopper opamp

Charge Amplifier (17)

 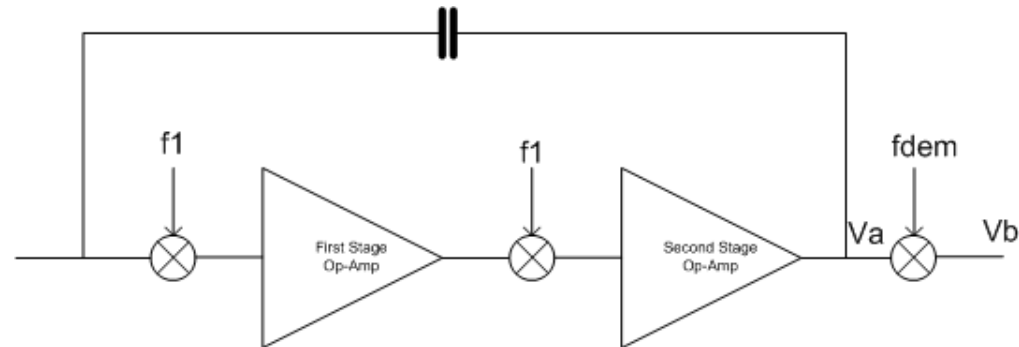
- The opamp $1/f$ noise is modulated by the Choppered square wave at frequency f_1 (Odd harmonics)
- The opamp modulated output signal is down converted by the demodulation clock (f_{dem})
- F_1 defined avoid that its odd harmonics are down converted in base band by the demodulation square wave
- Ex.: $f_1=1000\text{kHz}$ & $f_{dem}=100\text{kHz}$



$$X_{2k+1} = \frac{4 \cdot V_0}{\pi \cdot (2k+1)}$$

Charge Amplifier (18)

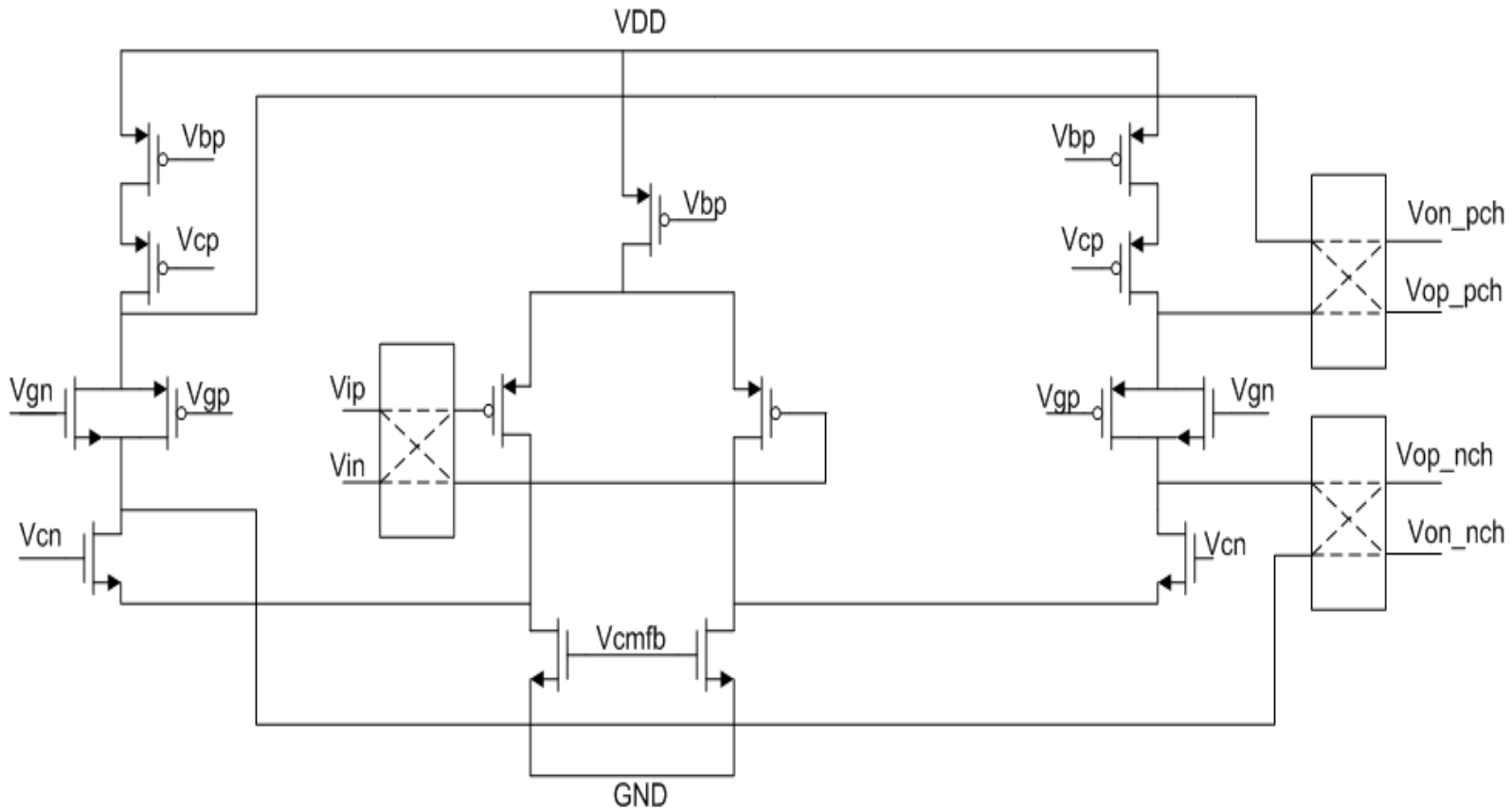First Stage of the Chopper Charge Amplifier Op-Amp




Charge Amplifier (19)

- Both solutions (Choppered and CT) have been designed and compared.
- CT solution performs the best results with the in term of:
 - Power consumption
 - Performances
 - Linearity
 - Development time
- Op-Amp specification:
 - GBW \approx 10MHz
 - Input referred Noise \approx 11nV/ $\sqrt{\text{Hz}}$
 - Current Consumption \approx 2.2mA \rightarrow 7.3mW@3.3V

Anti-Alias Filter (1)

 
- Large ADC Over Sampling Ratio
 - → One single pole Filter is enough to reduce the folding noise issue
- The Reading Block Noise budget is mainly used by the Charge Amplifier (High Complexity).
- If active solution is implemented the AAF Op-Amp needs Chopper Stabilization technique in order to remove the flicker Noise



- Passive Filter with external capacitor solution is widely used in very high performance standalone ADC.

Anti-Alias Filter (2)

 - The value of the AAF resistor is designed in order to have an attenuation of 0.4dB between the Dem. output and the ADC Input



$$F_s = 6\text{MHz}, C_s = 10\text{pF} \rightarrow R_{eq} = 17\text{M}\Omega$$

$$R_{aaf} = 800\Omega$$

Anti-Alias Filter (3)

- The AAF noise voltage:

$$V_{n_{R_{aaf}}} = \sqrt{4 \cdot k_b \cdot T \cdot R_{aaf} \cdot BW} = 65nV \quad \text{Negligible}$$

$$C_{\text{ext}} = 20nF \gg C_s$$

Cut-Off frequency: 10kHz < Modulation frequency

Attenuation at the ADC sampling frequency: -56dB


Anti-Alias Filter (4)

Passive Anti-Alias Filter solution

- 😊 Simple
- 😊 Less Risk compared with Active solution
- 😊 Noiseless
- 😊 No power consumption
- 😞 Requires external capacitors
- 😞 Gain Error

Bias Circuit


- Assuming no-noise sensor

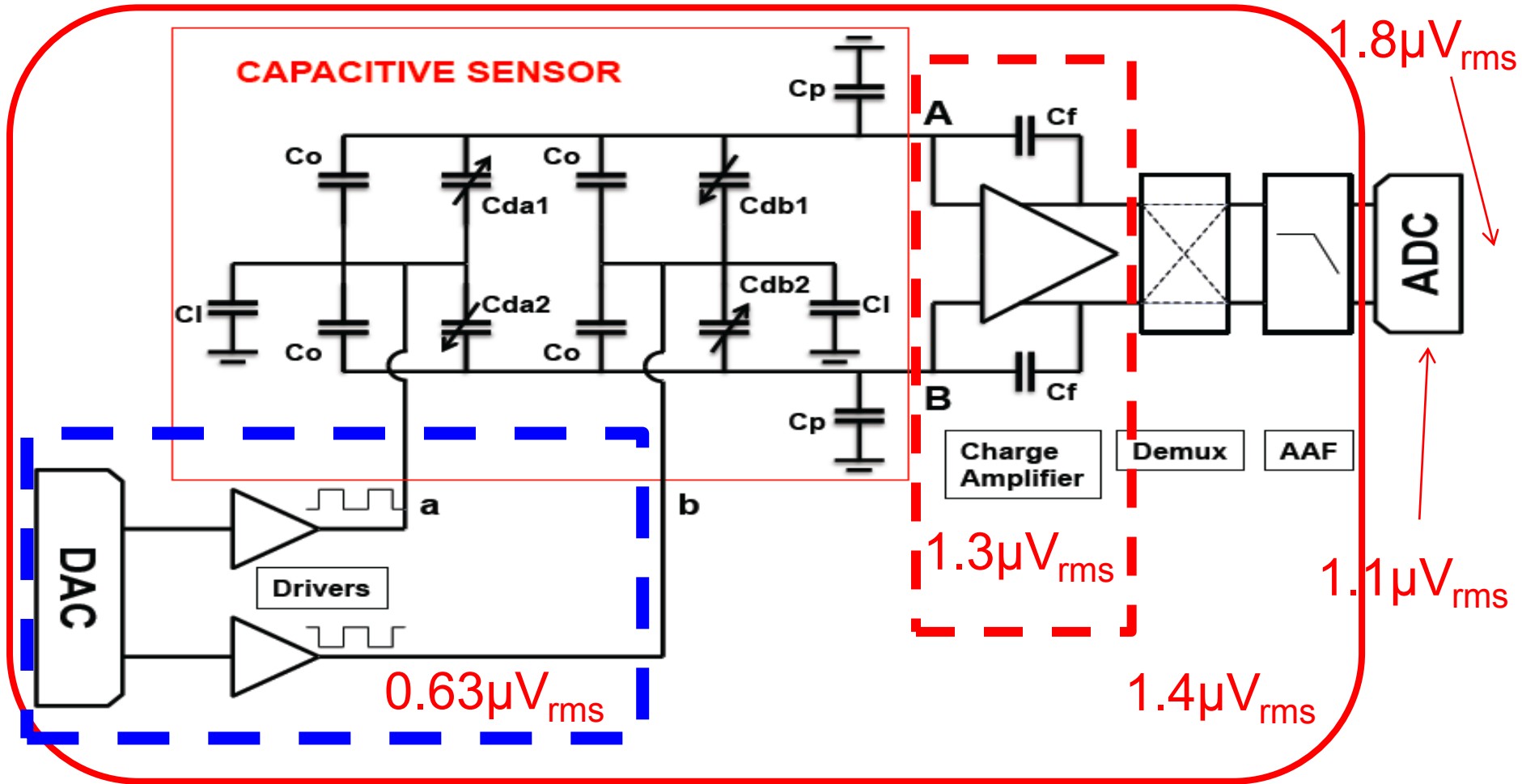

Bias Circuits


- Low Power/Low Noise Application → Reduce no. of circuits
- The Biasing circuit is divided in two blocks
 - DAC that is used to set the amplitude of the Carrier
 - Driver feeds the Sensor and Buffer the DAC output
 - High Impedance input Driver
- Two possible Implementations:
 - DAC dynamic Range 4.5V
 - Driver → Buffer
 - ☹ Rail-to-Rail Input Stage Op-Amp
 - DAC dynamic Range 2.5V (as ADC)
 - Driver → Non-Inverter gain configuration
 - ☹ The DAC and Driver Input Noises are amplified

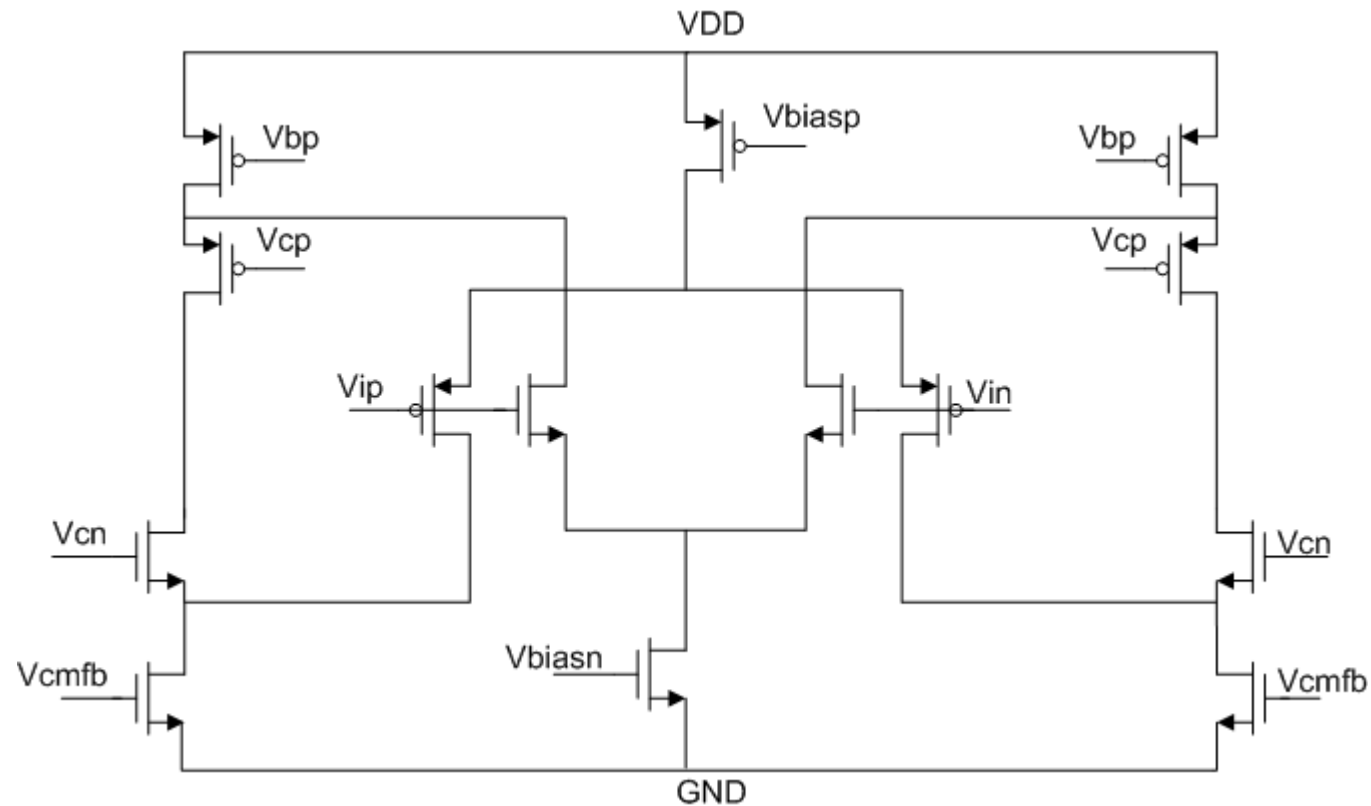Bias circuit / Rail-to-Rail Input Stage (1)



Bias circuit / Rail-to-Rail Input Stage (2)

 
- Rail-to-Rail Input stage critical point → distortion due to different offset of the P-ch and N-ch diff-pairs



- A squared wave is added to the carrier, its amplitude is equal to the difference between the N-ch and P-Ch differential pairs Offset.
- The carrier amplitude is effected by Offset Issue and it depends on DAC setting → equivalent to an INL issue


Bias circuit / Rail-to-Rail Input Stage (3)

 - INL problem reduced increasing the MOS sizes to be $<$ DAC INL
- Additional problem \rightarrow the diff-pair differential Flicker Noise is modulated
 - The power of the modulated Flicker Noise is equal to the sum of P-Ch and N-Ch differential pairs Flicker Noise power
 - The Driver Modulated Flicker Noise is demodulated in base band by the Demodulator and so it appears at ADC output



Bias circuit / Non Inverting Amplifier (1)


Fully Differential Difference Amplifier

 



- 😊 No extra Pole due to current generator
- 😊 Good CMRR
- 😞 More design Complexity
- 😞 Needs Common Mode Feedback Circuit

Bias circuit / Non-Inverting Amplifier (2)

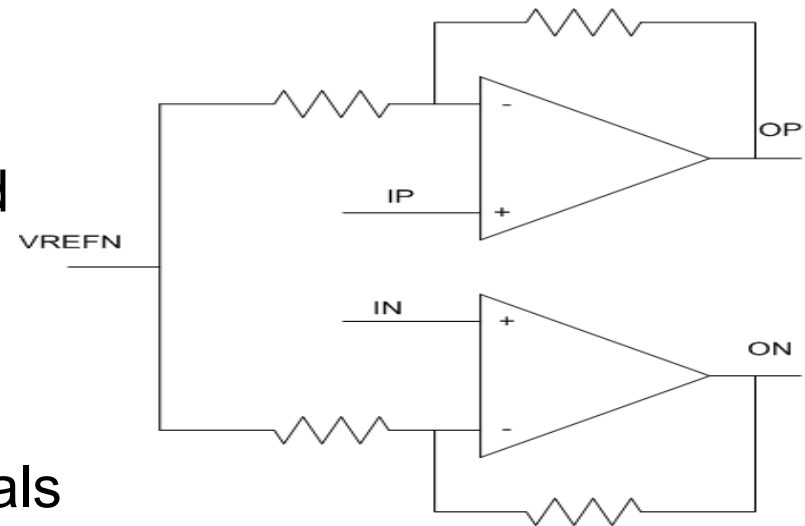- Single Ended opamp
 - 😊 Simple Architecture
 - 😊 Less power (No CMFB)
 - 😞 Extra pole due to differential to Single-Ended MOS diode
 - 😞 No Common Mode Rejection (the Common Mode and Differential signals are Amplified)





Bias circuit / DAC Architecture

 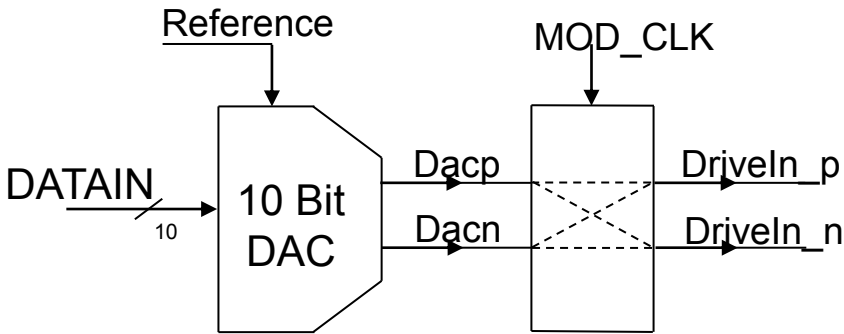

- Differential DAC inserted before the Modulator
 - 😊 Static DAC.
 - ☹️ DAC noise is not Choppered (Inserted before Modulator).
- Two possible topologies:
 - Current Steering


Resistive DAC Array (Poly Resistor)

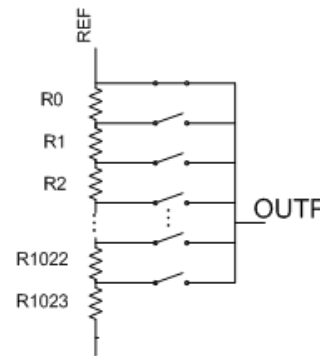 

- Poly Resistor Flicker Noise is lower than MOS flicker Noise


Rp1pp (p+poly res) Flicker/Thermal Noise evaluation (1)

- Flicker noise (pink noise) is present in polysilicon resistor with thermal noise.
 - It depends on **bias voltage**, **area** and **frequency** as shown below:
 - $V_n^2 \propto V_{bias}^2 / (W.L.f) \rightarrow$ flicker noise increases as bias voltage increases
- Ideal thermal noise for 1kΩ $\rightarrow \sqrt{[4 \cdot 1.38e-23 \cdot 300 \cdot 10^3]} = 4.07nV/\sqrt{Hz}$
- Total noise simulation graph of 1kΩ, Rp1pp resistor with 1uA ($\rightarrow \Delta V = 1mV$)

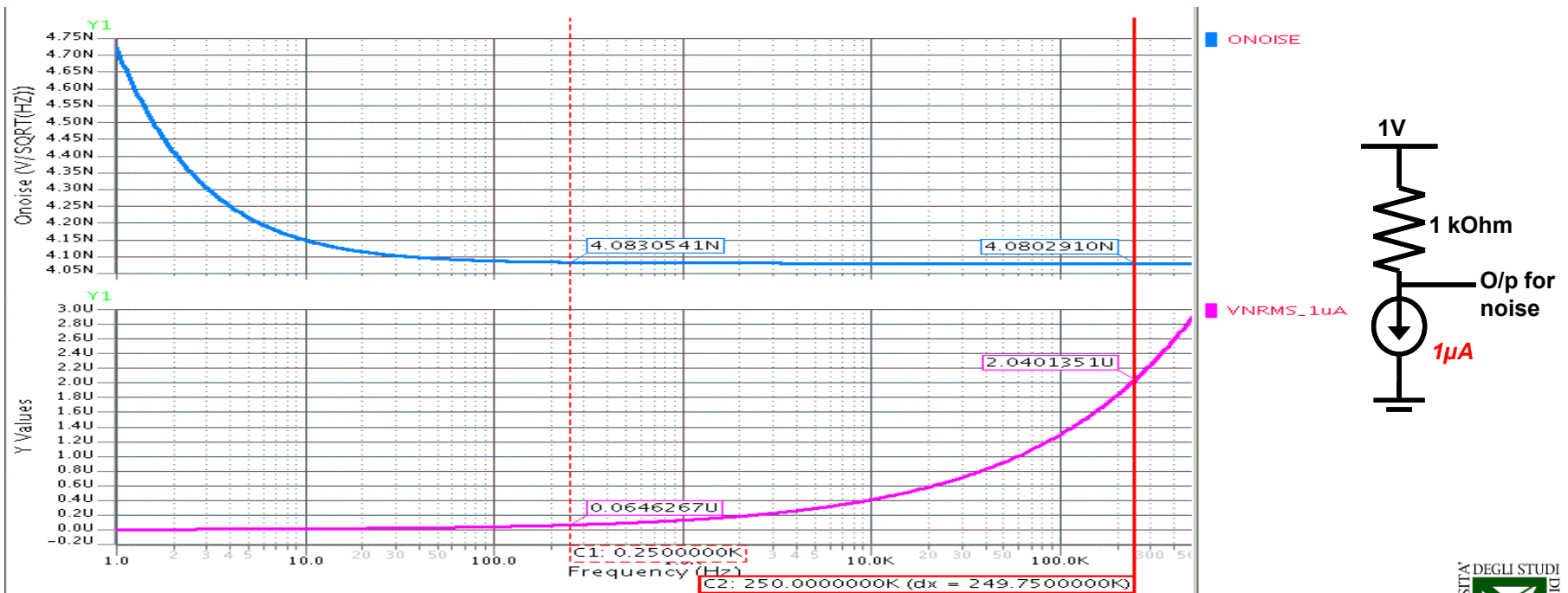


Rp1pp (p+poly res) Flicker/Thermal Noise evaluation (2)

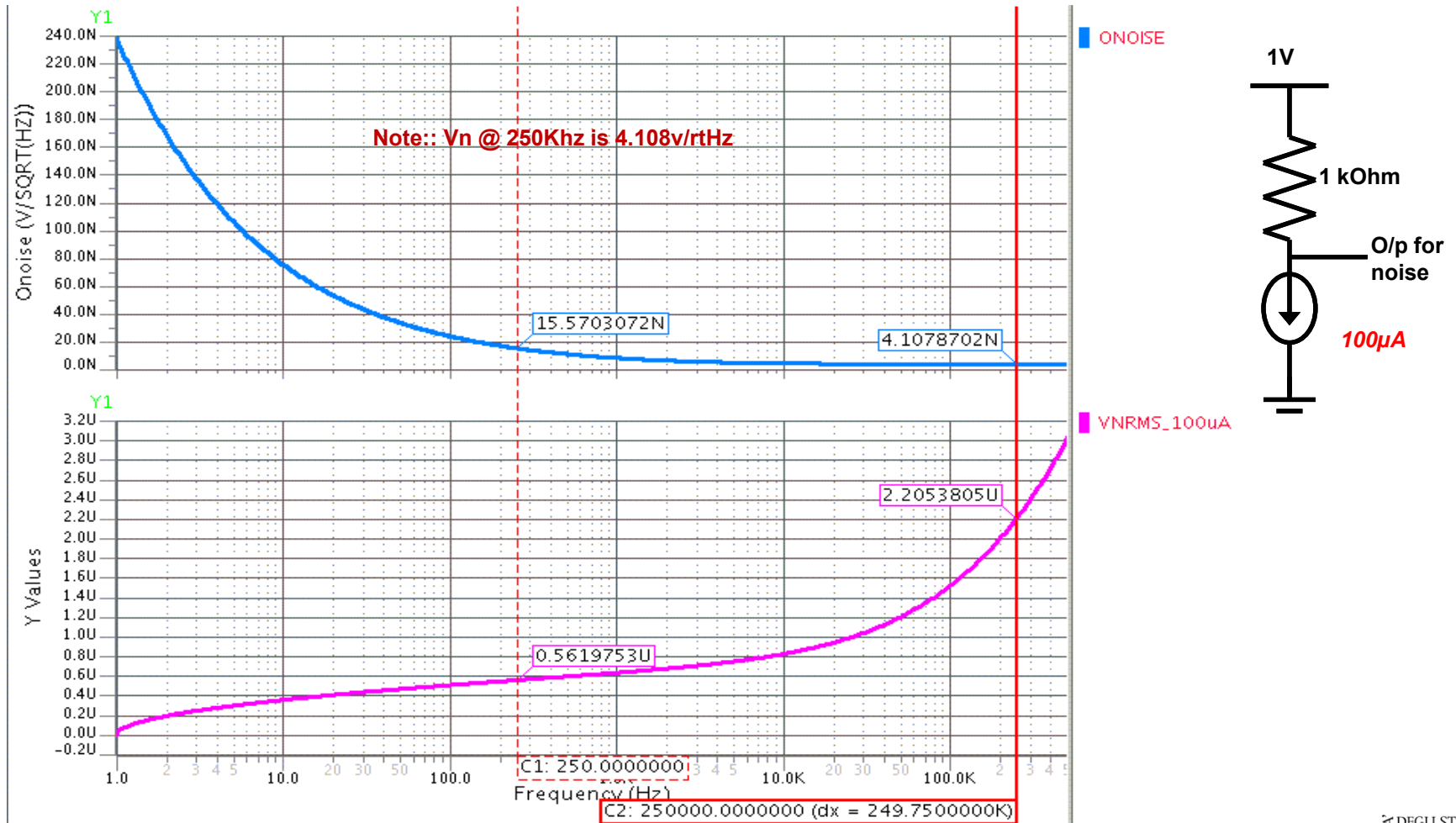- Total noise simulation of 1kΩ, Rp1pp resistor with 100uA (→ ΔV=0.1V)




MDAC Architecture

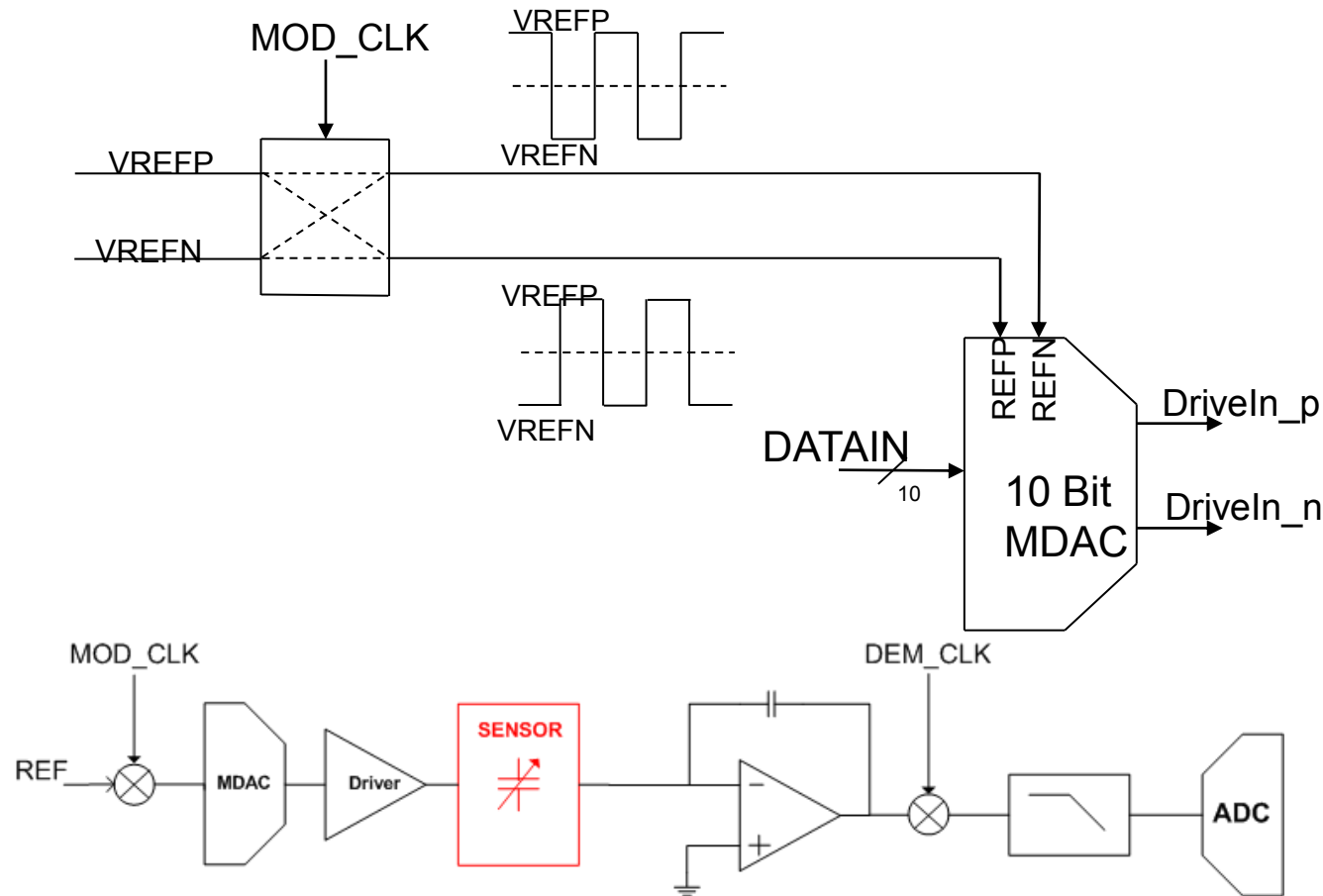- DAC Flicker Noise Reduction
 - ☹ Increase the dimension of the Resistor (Huge Impact on device area)
 - 😊 Move the Modulation before the DAC → MDAC Architecture




MDAC topology (1)

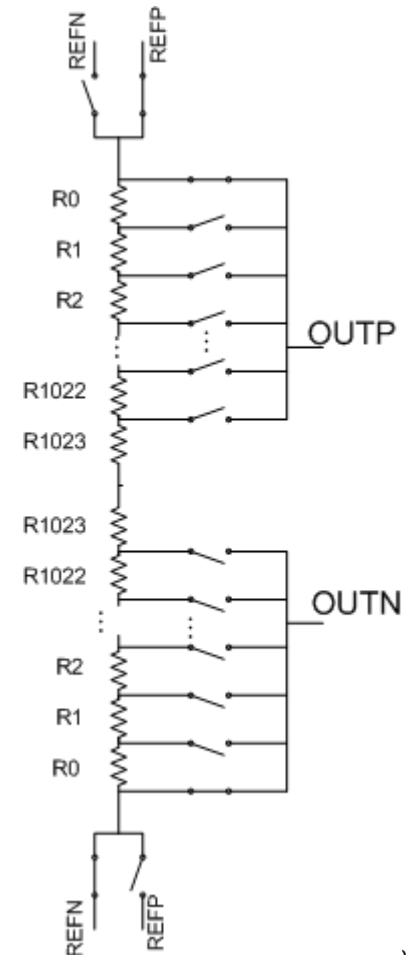- 10 Bit Differential MDAC Single Resistor String solution:
 - $2 \cdot 1024$ resistors
 - $2 \cdot 1024$ switches
- 😊 Good linearity
- 😞 Too Small value of the Resistor Module
- 😞 Huge Number of switches
 - Area
 - Parasitic Capacitor



MDAC topology (2)

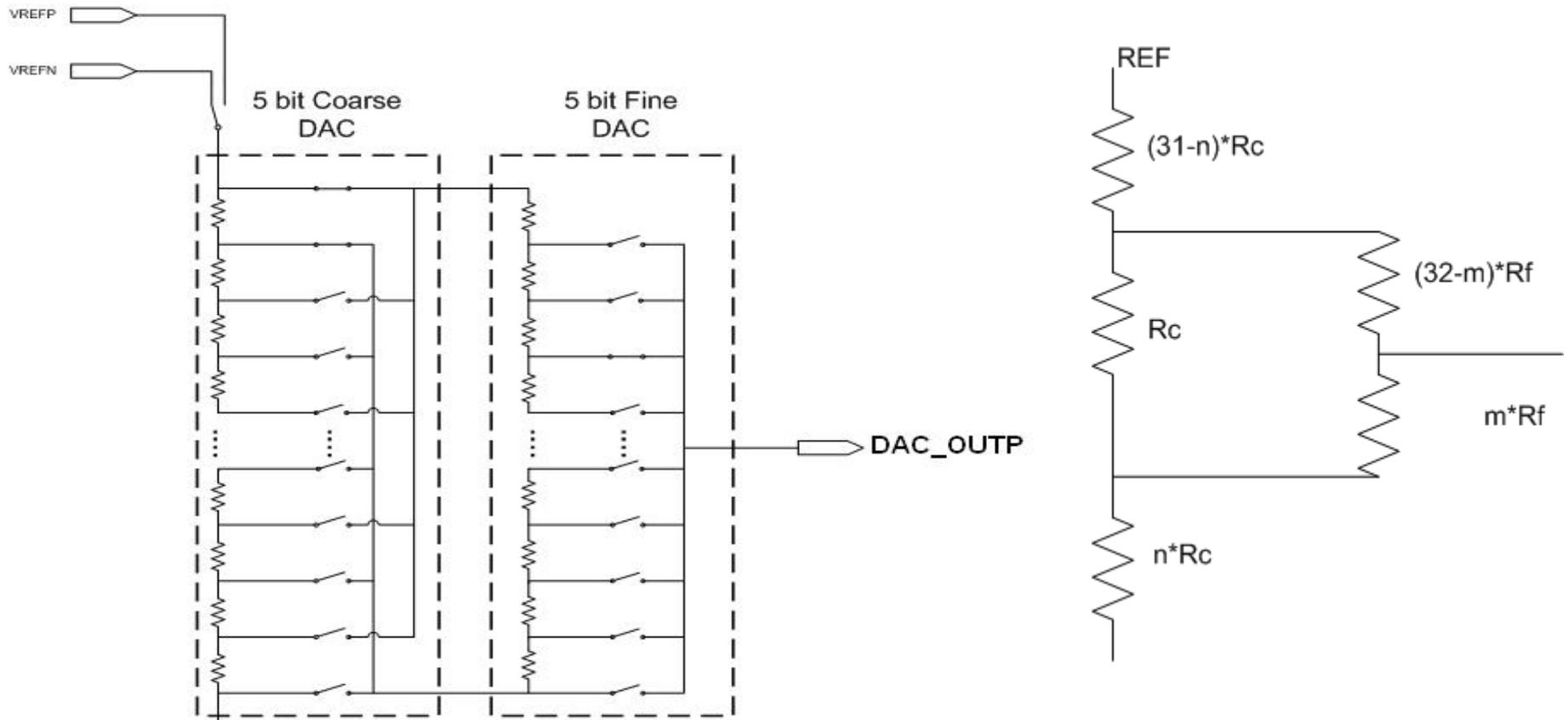
10 Bit Differential MDAC Double resistors
(Segmented)String Array




MDAC topology (3)

- 10 Bit Differential MDAC Double Resistor String Array solution:
 - 2*64 resistor
 - 2*64 switches

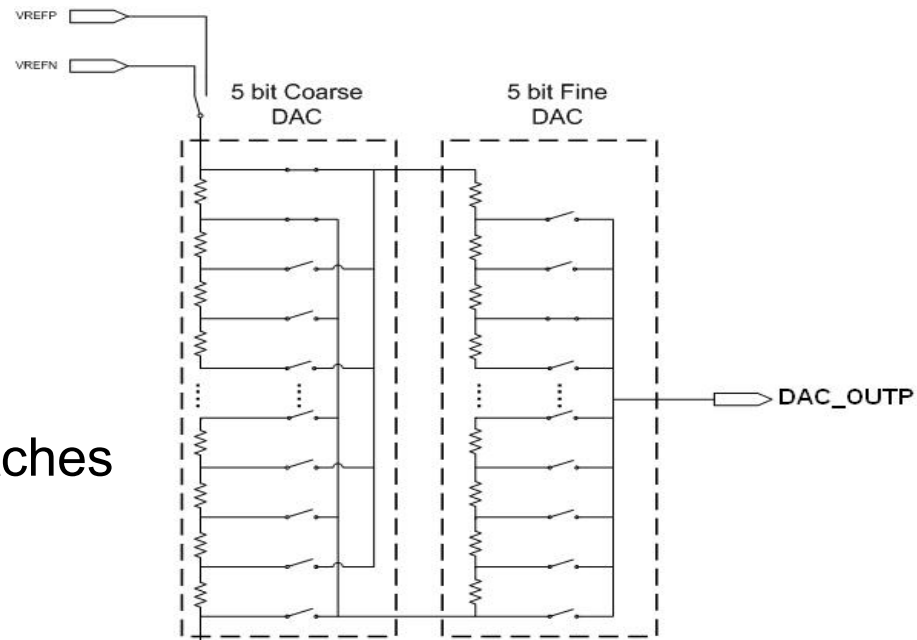
- ☹️ Worse linearity
- 😊 Bigger Resistor Module
- 😊 Reduced Number of switches



Driver Feedback resistor (1)

 

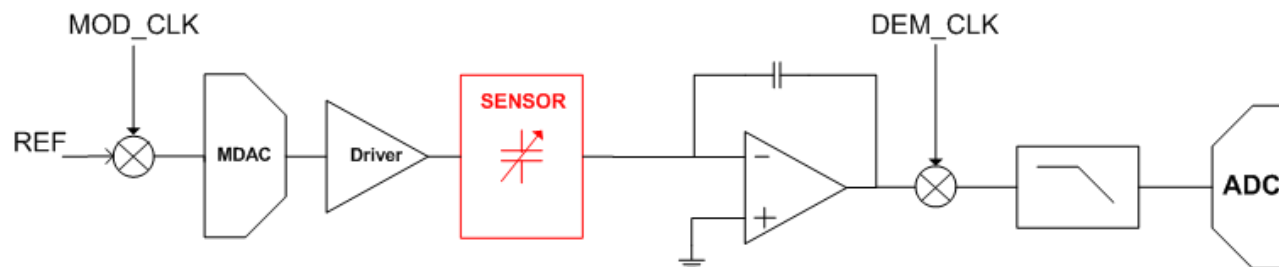- The squared wave current flowing in the feedback resistor modulates the flicker Noise of the P-Poly resistance
- The resistor flicker noise is folded in base band by the demodulator




Driver Feedback resistor (2)

Ideal Op-Amp
Ideal FeedBack resistor


Steady state Noise Analysis

Ideal Op-Amp
Poly Resistor

 
Periodic Steady-State Analysis `pss`: time = (0 s -> 10 us)



 
Periodic Steady-State Analysis `pss`: time = (0 s -> 10 us)



 Periodic Noise Analysis `pnoise`: freq = (1 Hz -> 150 kHz)



 Periodic Noise Analysis `pnoise`: freq = (1 Hz -> 150 kHz)




Driver Feedback resistor (3)

- Solutions
 - Increase the value of the feedback resistor
 - → maximum current reduction
 - → thermal noise increase
 - Increase the feedback resistor area
 - → flicker noise reduction
 - → parasitic capacitor increase
 - → stability issue and/or reduced closed loop bandwidth
 - Use Diffused resistor, with negligible flicker noise
 - → Linearity Issue

Driver Operational Amplifier (1)


- Output Dynamic range and Resistive feedback
 - → Two stage operational Amplifier
- Low power
 - → Class AB Output Stage
- Input Voltage Range [125mV-to-2.625V]
 - → P-Ch Input stage and supplied under 5V domain
- Output Voltage Range [125mV-to-4.625V]

Driver Operational Amplifier (2)

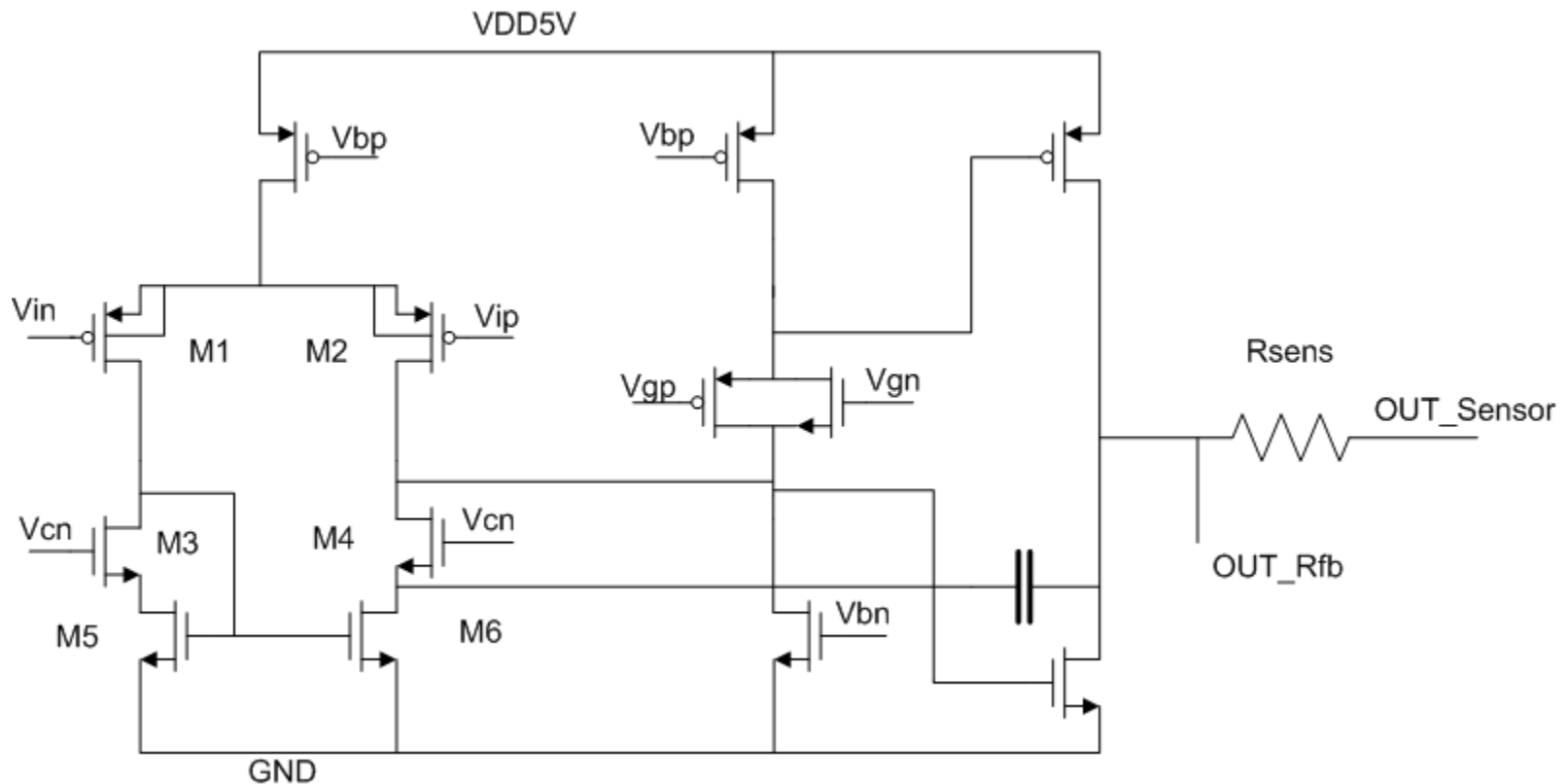


Driver Operational Amplifier (3)

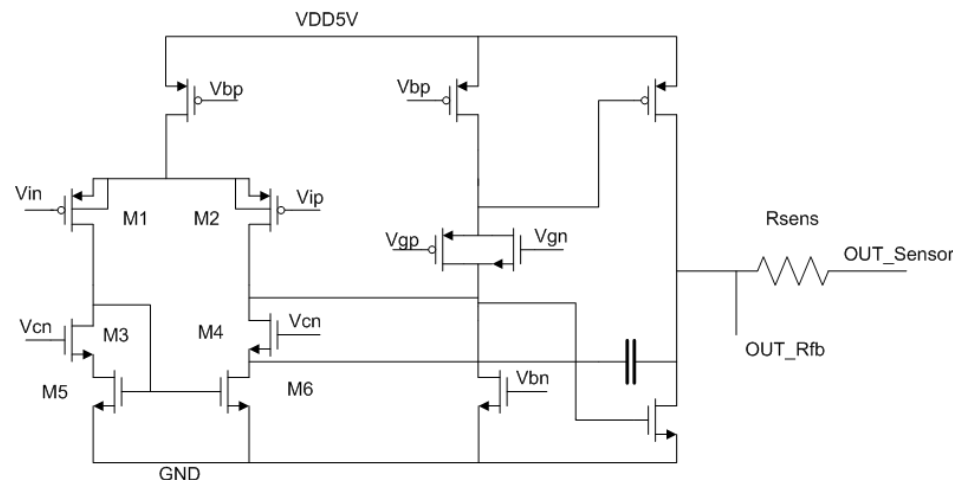- The Input Voltage Range is compatible with 3.3V MOS
 - 3VMOS better noise performance than 5VMOS
 - → (M1, M2, M3, M4, M5 and M6 are 3.3V MOS)
- Ahuja compensation
 - → move the output pole at higher frequency
- Output series resistor to Sensor Capacitive load adds a zero that help stability



Noise Budget Partitioning

- Assuming no-noise sensor

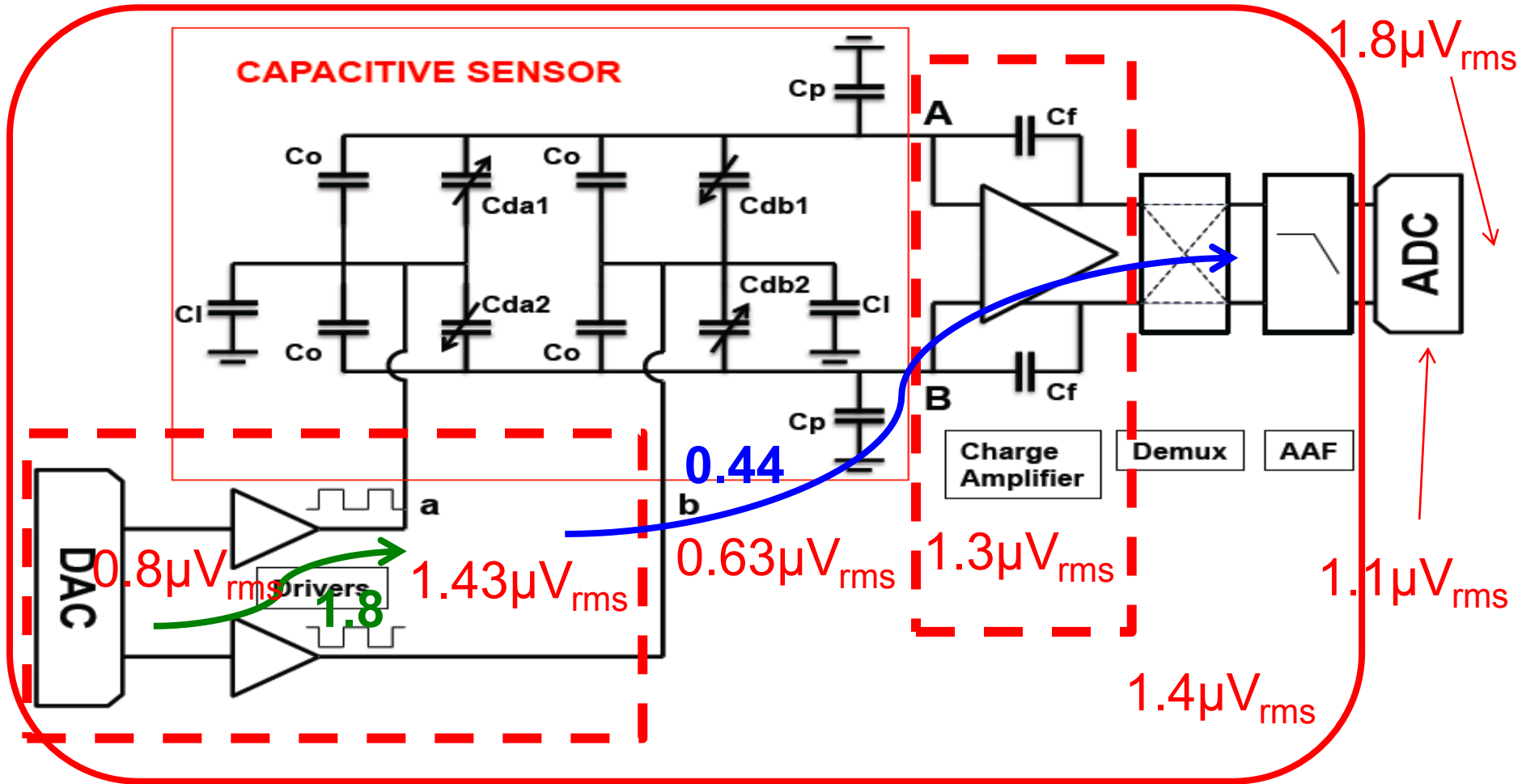

Biasing Circuit Design (1)

- Driver Gain $G_{\text{Driver}} = 4.5\text{V}/2.5\text{V} = 1.8$

$$V_{n\text{Bias@DriverOutput}} = \frac{0.63\mu\text{V}}{0.44} = 1.43 \mu\text{V}_{\text{rms}}$$

$$V_{n\text{Bias@DriverInput}} = \frac{V_{n\text{Bias@DriverOutput}}}{G_{\text{Driver}}} = \frac{1.43 \mu\text{V}_{\text{rms}}}{1.8} = 0.79 \mu\text{V}_{\text{rms}}$$

- The noise budget is equally divided between **MDAC** & **Drivers**

$$V_{n\text{MDAC}} = V_{n\text{Drivers}} = \frac{V_{n\text{Bias@DriverInput}}}{\sqrt{2}} = 0.56 \mu\text{V}_{\text{rms}}$$

- Two equal single-ended drivers are used

$$V_{n\text{Driver}} = \frac{V_{n\text{Drivers}}}{\sqrt{2}} = 0.4 \mu\text{V}_{\text{rms}}$$

Biasing Circuit Design (2)

- Driver Noise Contributors
 - Opamp
 - Feedback resistor
- The Driver Noise budget is equally divided between opamp and Feedback resistor contributors (No optimization)

$$Vn_{D_OP} = Vn_{D_RFB} = \frac{Vn_{Driver}}{\sqrt{2}} = \frac{0.4 \mu V}{\sqrt{2}} = 0.28 \mu V$$


Only thermal noise

$$\frac{Vn_{D_OP}}{\sqrt{BW}} = \frac{Vn_{D_RFB}}{\sqrt{BW}} = \frac{0.28 \mu V}{\sqrt{300}} = 16 nV / \sqrt{Hz}$$

$$\frac{Vn_{D_RFB}}{\sqrt{BW}} = \frac{4 k_b T R_2}{1 + \frac{R_2}{R_1}}$$


$$R_2 = 28 k\Omega \quad R_1 = 35 k\Omega$$

$$I_{fb}|_{max} = 70 \mu A$$

 

Biasing Circuit Design (3)

 - Opamp design is mainly driven by gain bandwidth requirement
 - GBW=4MHz
 - Input referred Noise density= 28nV/ $\sqrt{\text{Hz}}$
 - Driver Current Consumption =300uA
- Total Driver Current consumption
 - $I_{\text{tot}}=300\mu\text{A}+300\mu\text{A}+72\mu\text{A}=672\mu\text{A}$
 - $P_{\text{tot}}=3.4\text{mW}$




Biassing Circuit Design (4)

- DAC Noise three contributors:
 - Reference Voltage
 - Resistor Array
 - Switches


- The Noise Budget is equally divided between the three contributors
 - No optimization

- The single ended contributors are:

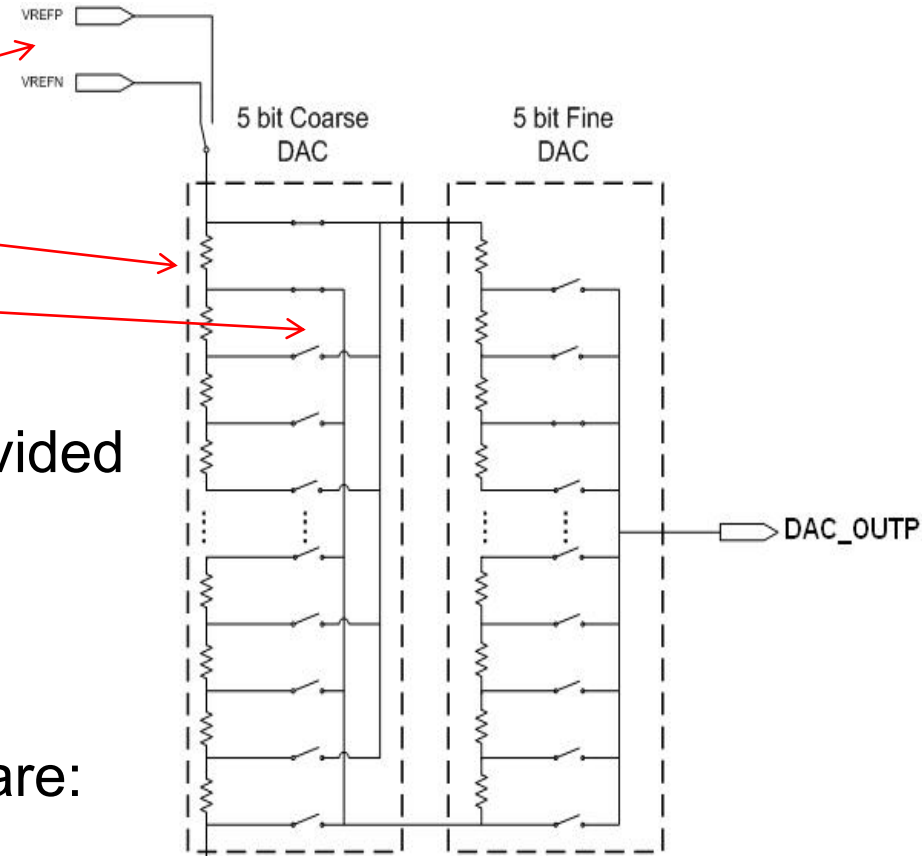


$$\frac{Vn_{MDAC}}{\sqrt{6}} = \frac{0.56 \mu V}{\sqrt{6}} = 0.22 \mu V \quad \square \quad 13nV/\sqrt{Hz}$$

Biasing Circuit Design (5)

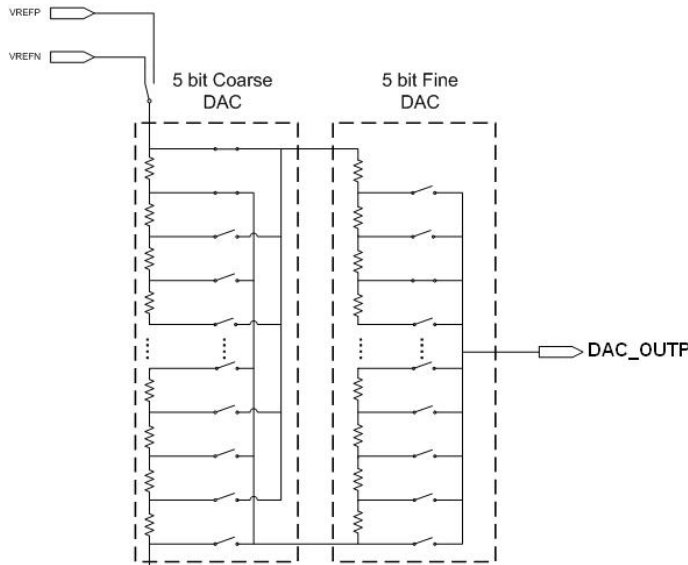

WC DAC Noise

 

- The relationship between Coarse and Fine resistor depends on DAC Linearity requirements

- Ex.: $R_f = 4 \cdot R_c$

$$\left(13nV / \sqrt{Hz}\right)^2 = 4 \times K_b \times T \times 8 \times (R_c + R_f)$$


$$R_c = 255\Omega$$

$$R_f = 1020\Omega$$

$$I_{DAC} = \frac{V_{ref}}{32 \times R_c \times 2} = 153\mu A$$

Biasing Circuit Design (6)

 
- Power consumption reduction
 - → two external caps filter the noise coming from V_{REF}
 - The DAC reference opamp is chopped
 - Static opamp
 - → Low power consumption ($<100\mu\text{A}$ per-buffers)




Power Consumption

	Current Consumption [μA]	Supply Voltage [V]	Power Consumption [mW]
Charge Amplifier	2200	3.3	7.3
Anti-Alias Filter	0	3.3	0
Drivers	672	5.0	3.4
Differential MDAC	353	3.3	1.16

Driver Noise vs. DAC Output Slope (1)

 


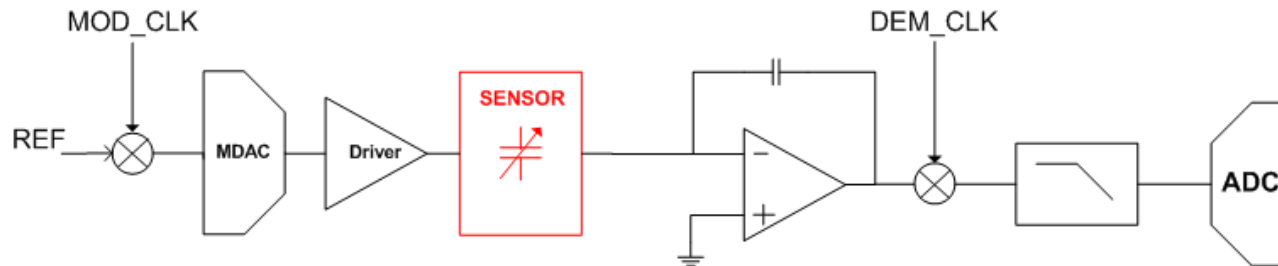- Output steps would have to be as more ideal as possible





Driver Noise vs. DAC Output Slope (2)

 - Tail current generator noise is modulated by the diff-pair unbalancement in slew-rate conditions
 - → Additional noise



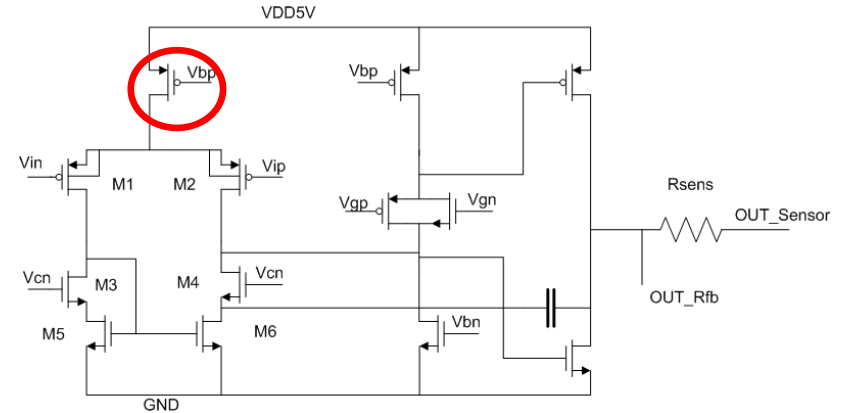 Periodic Steady-State Analysis `pss`: time = (0 s -> 20 us)



Driver Noise vs. DAC Output Slope (3)

- Tail current generator modulated noise reduction
 - Sol1 → Increase Op-Amp Gain Bandwidth
 - → Increase power consumption
 - Sol2 → Decrease DAC Output Signal Slope
 - → Increase Gain error (The effect is equivalent to reduce the Carrier Amplitude)
 - → To match the maximum ADC dynamic range the Charge Amplifier gain has to be increased
- Trade off GBW vs. Slope → Power vs. Noise

ADC Architecture

- ❑ Introduction
- ❑ Design Objectives
- ❑ Noise Budget Partitioning
- ❑ Architecture
- ❑ **ADC Architecture**

20b 250Hz ADC

- Sigma-Delta is the only possible 20b ADC solution
 - No matching requirement
 - Oversampling requirement (easy to be performed at small signal bandwidth)

20b 250Hz Sigma-Delta ADC

■ Overall Specs

- ADC Resolution: > 20 bit (SNR >123 dB)
- THD < -90 dB
- Bandwidth 1Hz-250Hz
- Output rate 500 Sps
- Anti Aliasing Filter External
- Supply Voltage 3.3V
- Area < 3.5 mm²

20b 250Hz Sigma-Delta ADC

- Noise Budget calculation
 - Reference Voltage: 2.5V
 - Input Amplitude: $4V_{pp}$ ($1.4V_{rms}$)

- For 125dB-SNR → Total Noise $\approx 700 \text{ fV}^2$

20b 250Hz Sigma-Delta ADC

- Noise Budget calculation
 - For 125dB-SNR → Total Noise ≈ 700 fV²
 - Noise Budget
 - Opamp Noise after chopper 150 fV²
 - kT/C Noise 250 fV²
 - $250 \text{ fV}^2 < kT/(C_s \cdot \text{OSR})$
 - Reference Noise 200 fV²
 - $Q_{\text{noise}} + \text{Other noise} < 50 \text{ fV}^2$
- → Equivalent SNR (considering only Q_{noise}) = 136 dB
 - → MATLAB SNR requirement > 136 dB

20b 250Hz Sigma-Delta ADC

- Sampling frequency choice

- Low sampling frequency

- Quantization noise

- Low OSR → low resolution

- high order

- Q_N is not the key limitation !!!

- Thermal noise

- Low OSR → large in-band noise

- For a given DR → Larger C_s → higher Power

$$N_{inband} = \frac{C_s}{OSR} = \frac{2 \cdot F_b}{F_s} \cdot \frac{kT}{C_s}$$

- High sampling frequency

- Smaller sampling period

- Larger opamp bandwidth spec → higher power


- Larger slew-rate → higher power

20b 250Hz Sigma-Delta ADC

- Sampling frequency choice
 - Trade-off choice
 - $\rightarrow \text{OSR} = 8.192$
 - $\rightarrow F_s = 250 \times 2 \times 8.192 = 4.096 \text{ MHz}$
 - $\rightarrow N_{\text{inband}}^2 = (kT/C_S)/\text{OSR}$
 - $\rightarrow C_S = kT / (N_{\text{inband}}^2 \cdot \text{OSR}) = 10 \text{ pF}$


20b 250Hz Sigma-Delta ADC – Topology Choice

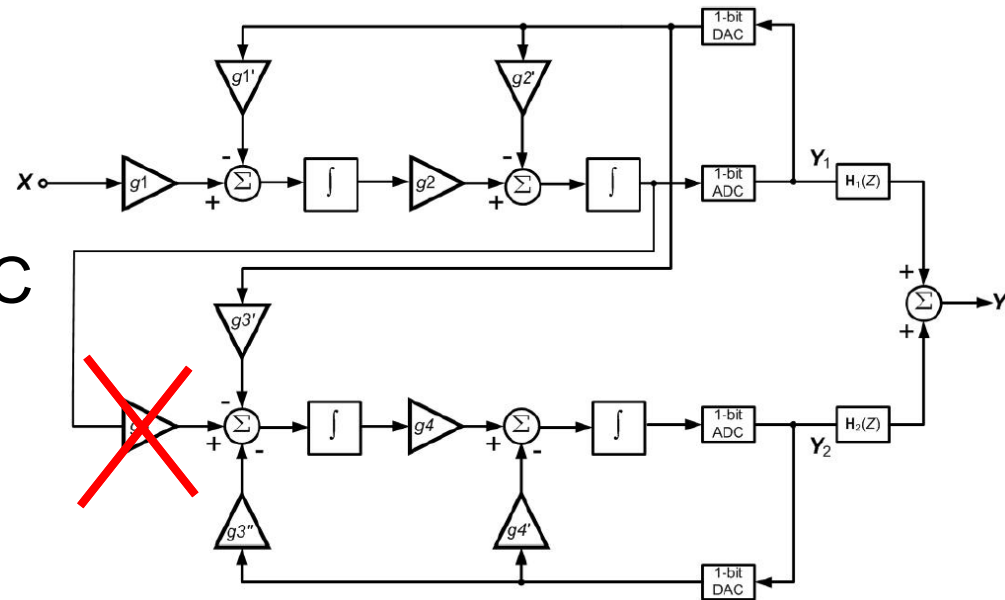- Single-bit 2+2-MASH
 - 😊 No DAC cap mismatch sensitivity
 - 😞 Cap mismatch sensitivity in the noise canceling network
 - 😞 Large Slew-rate requirements
 - 😊 Simple feedback DAC network
- Stability !!!



20b 250Hz Sigma-Delta ADC – Topology Choice

- 2nd-order FeedForward single-loop

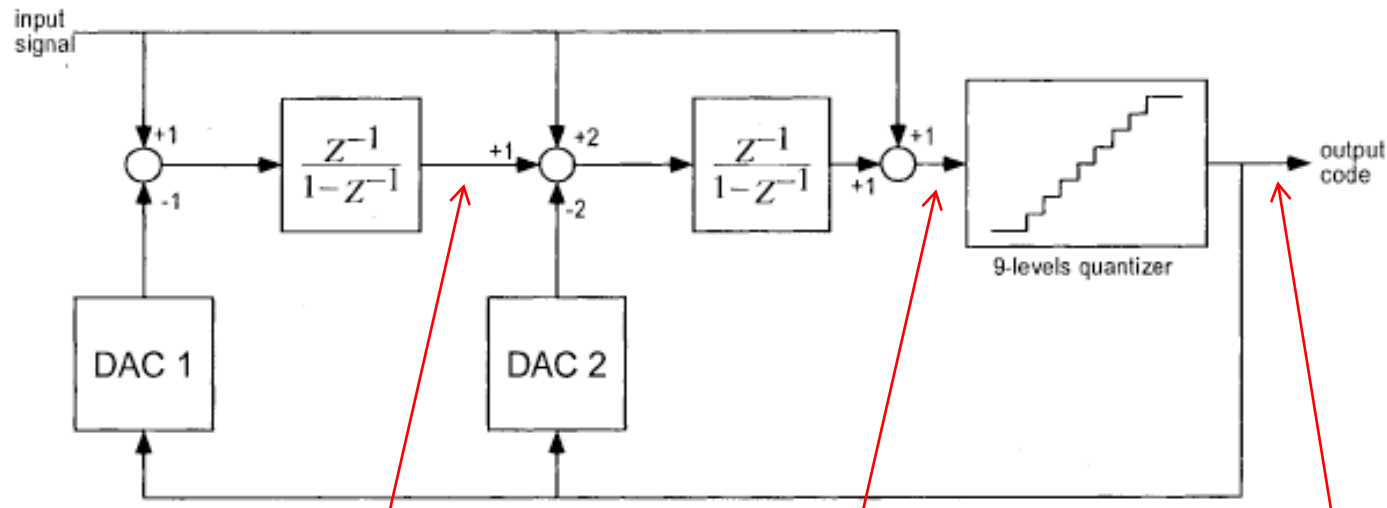


$$P = Q \cdot (-1 + z^{-1}) \cdot z^{-1} \quad R = Q \cdot (-2 + z^{-1}) \cdot z^{-1} \quad Y = X + Q \cdot (1 - z^{-1})^2$$

- No signal in P & R
 - Maximum opamp output swing → Quantizer LSB
 - Useful for multi-bit quantizer
 - Small integrator output swing

20b 250Hz Sigma-Delta ADC – Topology Choice

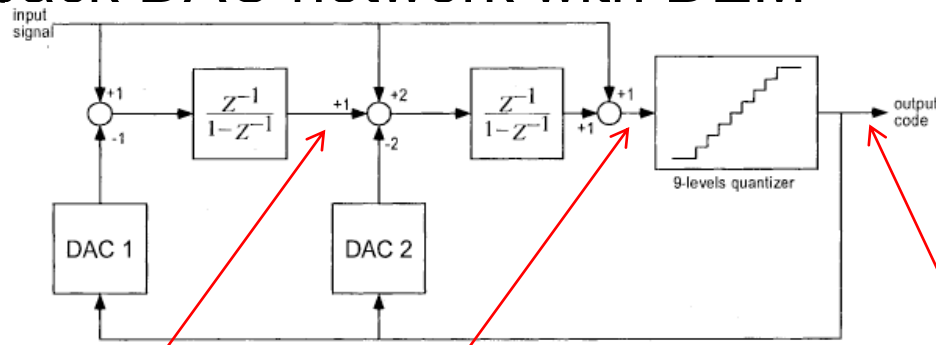- 3-bit 2nd-order FeedForward single-loop
 - ☹️ DAC cap mismatch sensitivity
 - 😊 No Cap mismatch sensitivity in the noise canceling network
 - 😊 No Finite opamp sensitivity in the noise canceling network
 - 😊 Reduced Slew-rate requirements
 - ☹️ Feedback DAC network with DEM



$$P = Q \cdot (-1 + z^{-1}) \cdot z^{-1}$$


$$R = Q \cdot (-2 + z^{-1}) \cdot z^{-1}$$

$$Y = X + Q \cdot (1 - z^{-1})^2$$

20b 250Hz Sigma-Delta ADC – Topology Choice

■ Silva's Topology ←←

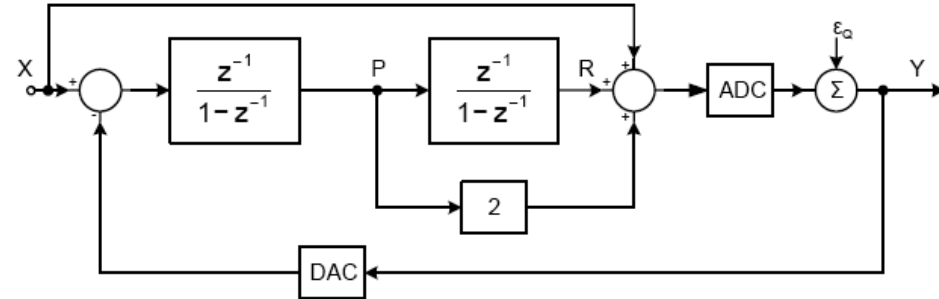
- 😊 Two input branches
 - Lower load for the previous stage
- 😊 Single DAC



$$P = Q \cdot (-1 + z^{-1}) \cdot z^{-1} \quad R = Q \cdot (-2 + z^{-1}) \cdot z^{-1} \quad Y = X + Q \cdot (1 - z^{-1})^2$$


■ Nys's Topology

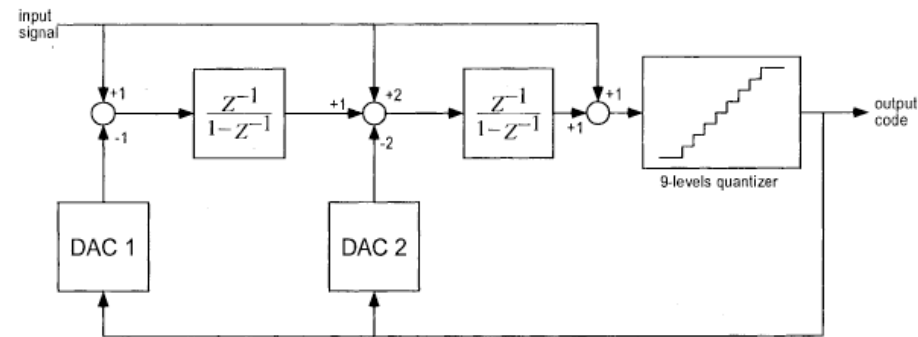- 😞 Three input branches
 - Higher load for the previous stage
- 😞 Two DACs





20b 250Hz Sigma-Delta ADC – Topology Choice

 - FF Topology
- Amplitude swing @ Integrator outputs
 - Output swing $< V_{FS}/2 \rightarrow$ relaxed opamp output swing
 - \rightarrow Low Power Consumption




20b 250Hz Sigma-Delta ADC – Topology Choice

  - FF Topology
- Integrator output step histogram
 - SR is still important




20b 250Hz Sigma-Delta ADC – Topology Choice

 - FFSDM → Stability & Recovery Test
 - Input overload signal
 - The structure recovers from overload
 - No reset circuit is need



20b 250Hz Sigma-Delta ADC – Topology Choice


- FFSDM – SC Implementation

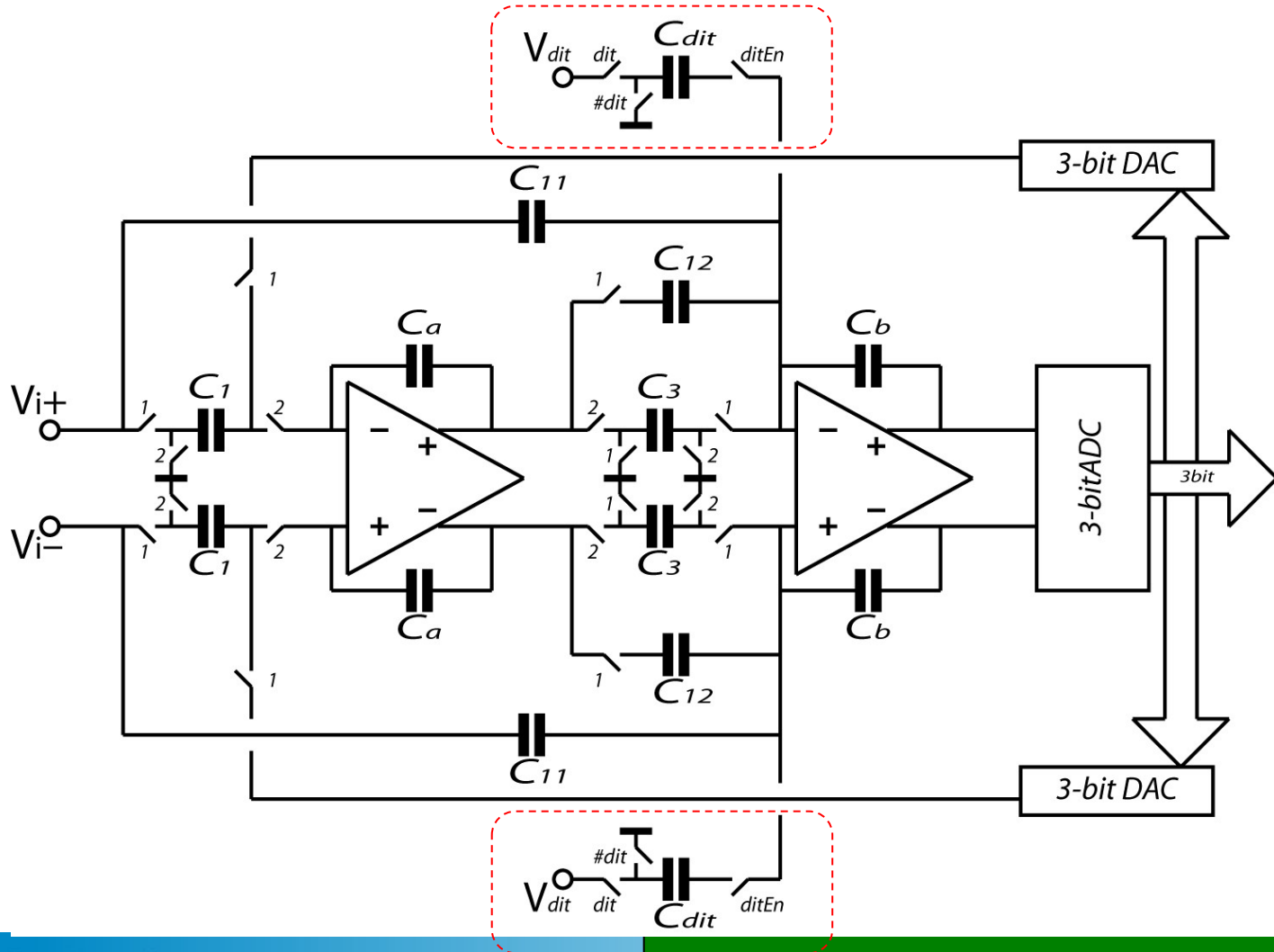

20b 250Hz Sigma-Delta ADC – Topology Choice

■ FFSDM → Architecture development

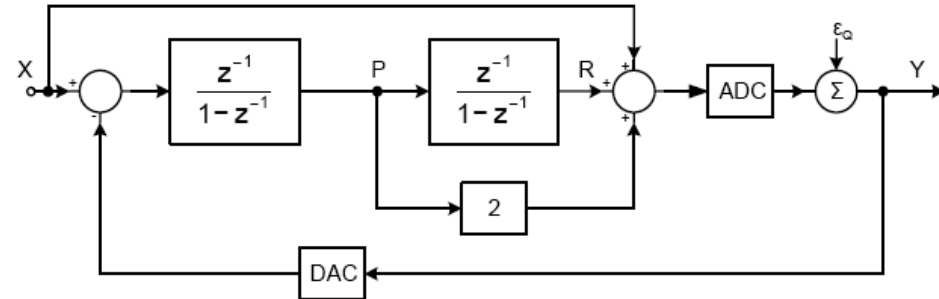- Q_{noise}
- DAC non-linearity (Cap mismatch)
- Instability / Recovery time
- Idle tones
- Quantizer V_{TH} Error
- FF Adder Gain Error




■ Circuit design development

- Opamp performance effects
 - Gain, Bandwidth, Slew-Rate
- Sampling Jitter
- Thermal noise


20b 250Hz Sigma-Delta ADC – Topology Choice

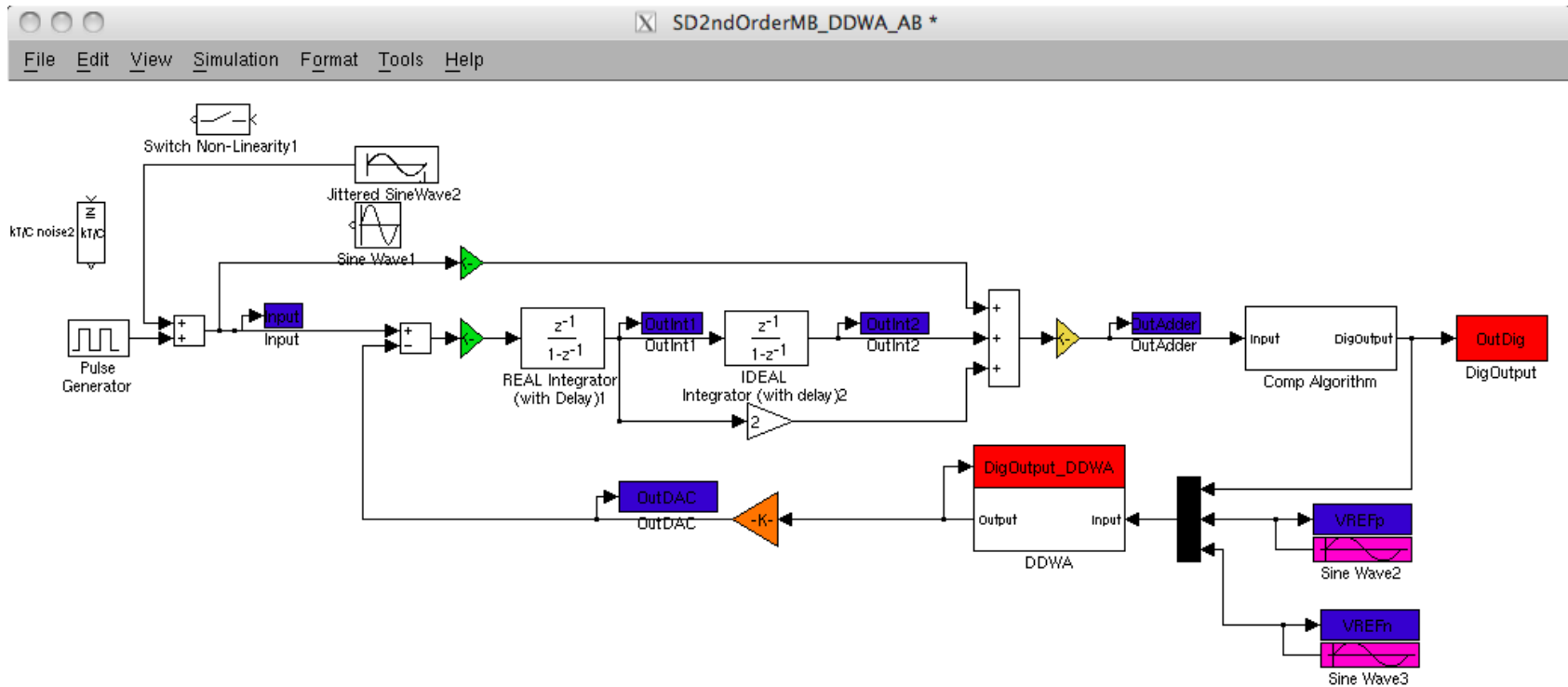- Simulink model
 - Transient effects (SR, QN, Jitter, mismatch)
 - Small signal effects (Thermal&1/f, Gain&Bandwidth)



20b 250Hz Sigma-Delta ADC – Topology Choice

 
- FFSDM - Real opamp performance
 - Gain = 50dB, UGB = 25MHz, SR = 40V/ μ s
 - Poor opamp gain requirement \rightarrow LowPowerCons



20b 250Hz Sigma-Delta ADC – Topology Choice


- FFSDM - Real opamp performance

 - SNR_{NoJitter}
- 192.71dB
- 168.08 dB
- 192.71 dB
- 192.71 dB
- 168.078dB




20b 250Hz Sigma-Delta ADC – Topology Choice

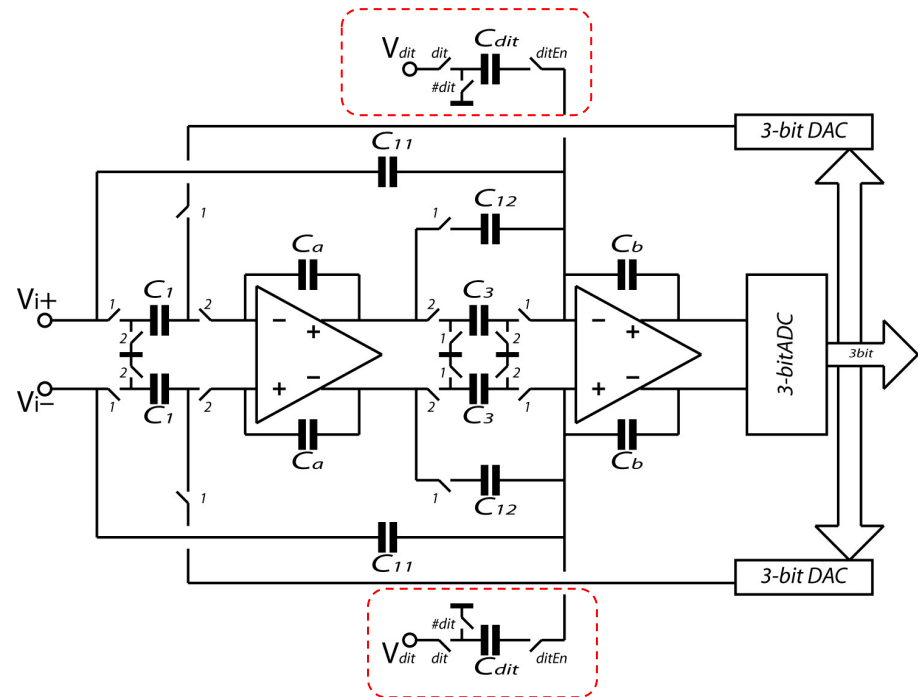- Dither Avoids Spurious_Tone generation at low signal-level
 - @ Low-Level Multibit ADC behaves like a single-bit ADC
- Dither is implemented with an SC branch
 - $C_{dit} = 1/10 C_b$
 - connected at the 2nd-opamp input
 - *dith* frequency = $F_s/4$
 - → input tones at $F_s/4$, i.e. far from the signal band
- can be disabled (dithEn signal)




20b 250Hz Sigma-Delta ADC – Implementation

 - Input noise reduction
 - The aggressive AAF reduces input noise bandwidth
 - It reduces settling time of the sampling operation
 - The final sampled value depends on charging starting point
 - → Sampling error depends on signal amplitude
 - THD




20b 250Hz Sigma-Delta ADC – Implementation

 - Input noise reduction - Solution
 - The sampling capacitor is reset at the beginning of the sampling phase
 - The signal-dependent error is canceled




20b 250Hz Sigma-Delta ADC – Implementation

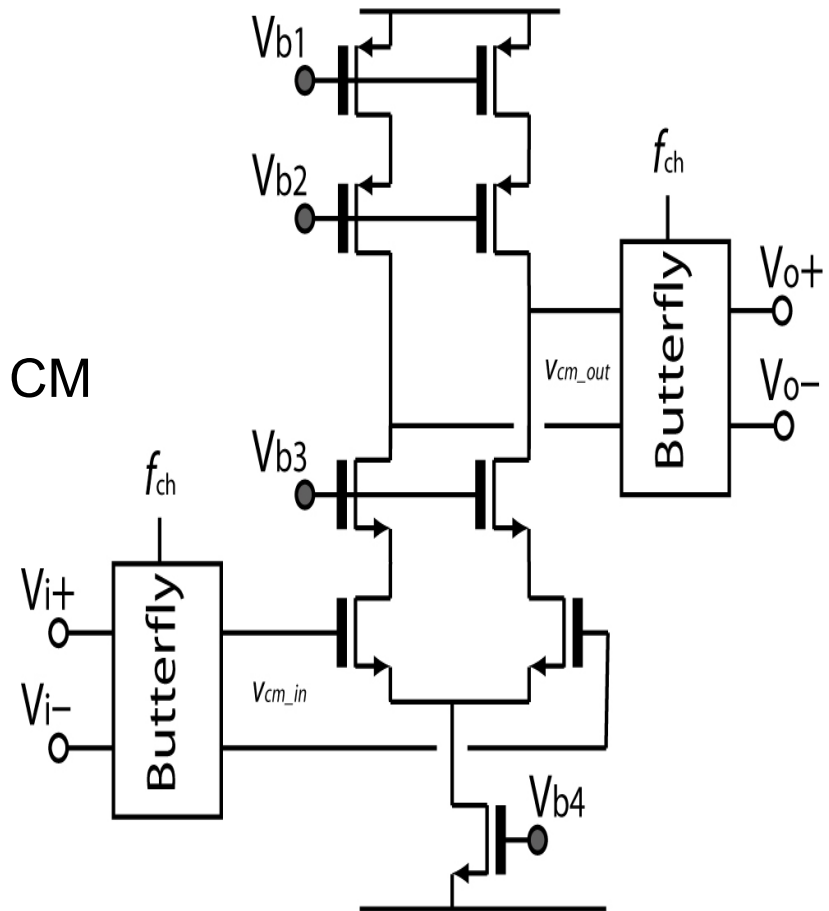- 1st-opamp design
 - 1/f Noise → Chopper
 - FFSDM
 - → Reduce swing
 - → Telescopic cascode
 - Different input.vs.output CM compensated in the SC structure




20b 250Hz Sigma-Delta ADC – Implementation

 - Chopper concept
 - Chopper frequency choice: Trade-off motivation
 - Low chopping frequency → Larger in-band noise folding
 - High chopping frequency → Large-&-frequent opamp output steps
- Chopper frequency choice → $F_s/8$




20b 250Hz Sigma-Delta ADC – Implementation

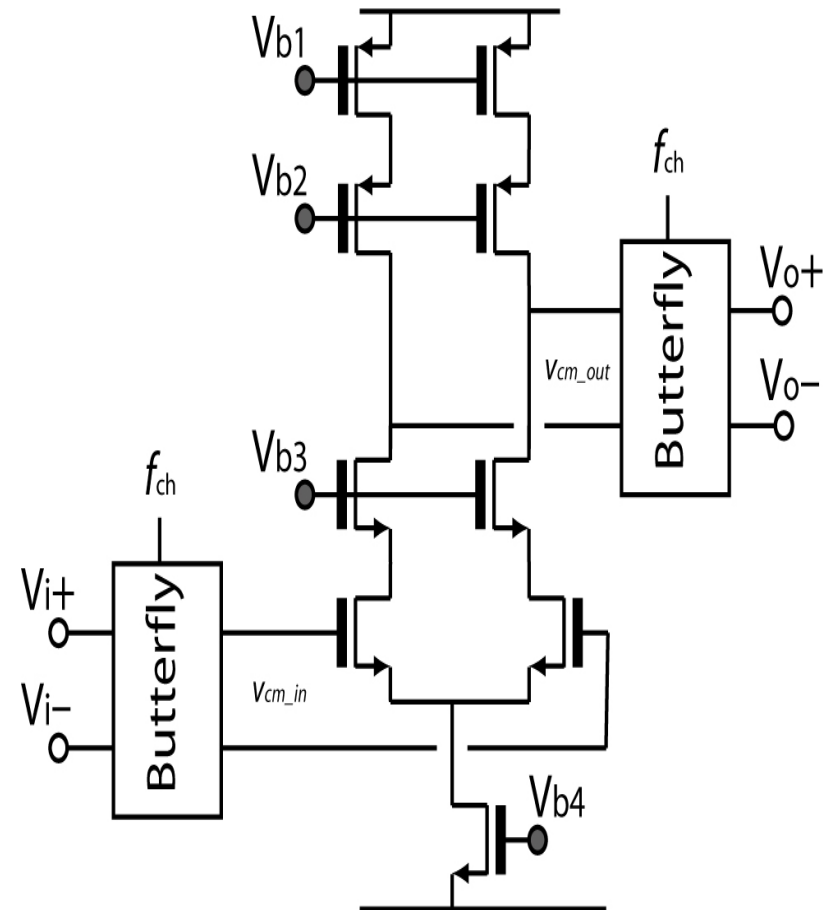- Chopper concept
 - In a two-stage opamp only the 1st-stage is chopped
 - Negligible 2nd-stage 1/f noise
 - Smaller 1st-stage output swing
 - In a single-stage opamp
 - → The full opamp is chopped
 - → Significant output swing
 - !!! BUT in FF-SDM
 - → small 1st-opamp output swing
 - → Chopper is not critical



20b 250Hz Sigma-Delta ADC – Implementation

 - Chopper Transient evolution
 - Output1 → pink line
 - Output2 → Green line




DC-gain	93dB
UGB	35MHz
Settling time (closed loop configuration)	< 120ns
Chopper frequency	Fs/8
Current consumption	390μA

20b 250Hz Sigma-Delta ADC – Implementation

- Multibit ADC
- ADC Threshold voltage generation
 - Passive SC solution in the comparator (single-ended version)
- Charge balance
 
$$V_c(2) = V_{in} - \frac{C_p}{C_p + C_m} \Delta V_R$$




- $V_{TH} = 7 \rightarrow C_p = 7 \cdot C \ \& \ C_m = 1 \cdot C$
- $V_{TH} = 5 \rightarrow C_p = 5 \cdot C \ \& \ C_m = 3 \cdot C$
- $V_{TH} = 3 \rightarrow C_p = 3 \cdot C \ \& \ C_m = 7 \cdot C$

$$V_c(2) = V_{in} - \frac{C_p \Delta V_{R+} + C_m \Delta V_{R-}}{C_p + C_m} = V_{in} - \frac{C_p - C_m}{C_p + C_m} \Delta V_{R+}$$


20b 250Hz Sigma-Delta ADC – Implementation

 - Multibit ADC
- Fully-differential scheme




20b 250Hz Sigma-Delta ADC – Implementation

 - Multibit ADC
- Fully-differential scheme




20b 250Hz Sigma-Delta ADC – Implementation

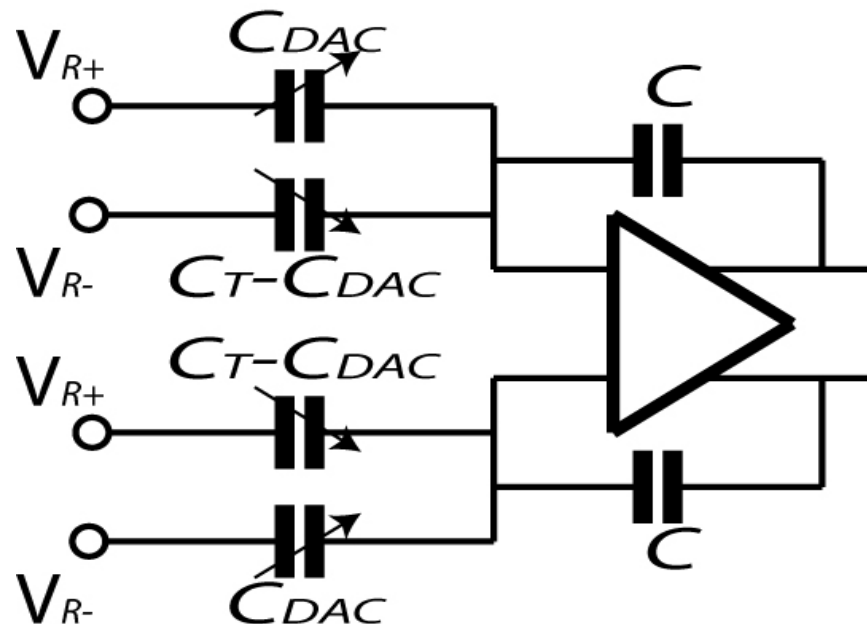- Multibit DAC
- Fixed total opamp input capacitance
 - Independent on the input data
- Fixed total load for V_{R+} & V_{R-}
 - Independent on the input data




20b 250Hz Sigma-Delta ADC – Implementation

- Multibit DAC: 3bit operation example

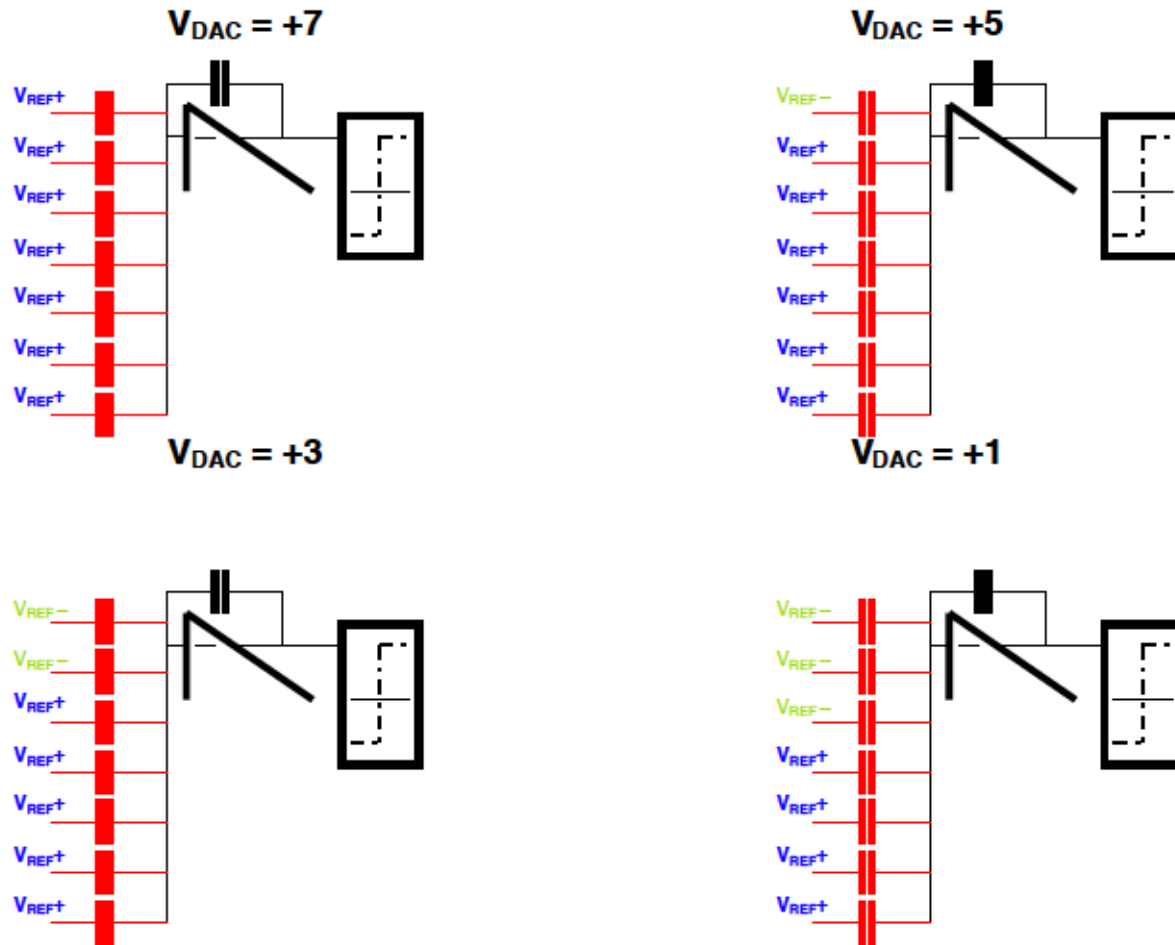


20b 250Hz Sigma-Delta ADC – Implementation

- Multibit DAC: 3bit operation example

 


20b 250Hz Sigma-Delta ADC – Simulation

- $A_{in} = -4\text{dB}_{FS}$, Dither=NO

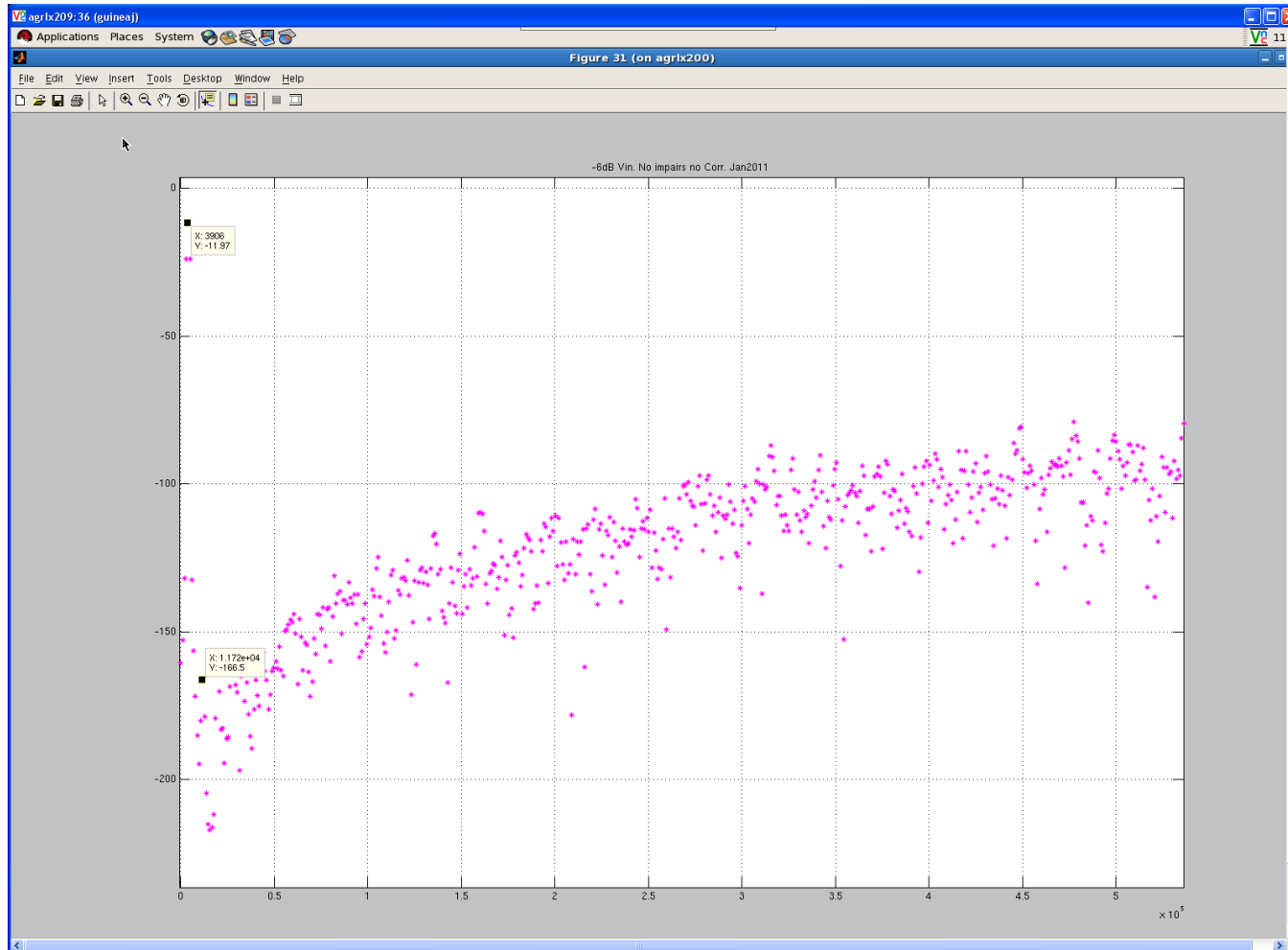

20b 250Hz Sigma-Delta ADC – Simulation

 - $A_{in} = -4\text{dB}_{FS}$, Dither= **YES**



Overall System Power Consumption

	Current Consumption [μA]	Supply Voltage [V]	Power Consumption [mW]
Charge Amplifier	2200	3.3	7.3
Anti-Alias Filter	0	3.3	0
Drivers	672	5.0	3.4
Differential MDAC	353	3.3	1.16
ADC	890	3.3	3