



Introduction to Field Programmable Gate Arrays

Hannes Sakulin
CERN / EP-CMD



International School of
Trigger and Data Acquisition 2024

USTC Hefei, China, 20 June 2024

What is a **F**ield **P**rogrammable **G**ate **A**rray ?

... a quick answer for the impatient

- An FPGA is an integrated circuit
 - Mostly digital electronics
- An FPGA is programmable in the in the field (=outside the factory), hence the name “field programmable”
 - Circuit design is specified with a hardware description language or schematics
 - Tools compute a programming file for the FPGA (bitstream)
 - The FPGA is configured with the design (gateware / firmware)
 - Your electronic circuit is ready to use

With an FPGA you can build electronic circuits ...
... without using a bread board or soldering iron
... without plugging together NIM modules
... without having a chip produced at a factory



Outline

- Quick look at digital electronics
- FPGAs and their features
- Programming techniques
- Design flow
- Example Applications in the Trigger and DAQ domain

The basic elements of digital electronics

The building blocks: logic gates

AND gate



Truth table

INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

C equivalent

`q = a && b;`

OR gate



INPUT		OUTPUT
A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

`q = a || b;`

Exclusive OR gate
XOR gate




INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

`q = a != b;`

⋮

Combinatorial logic (asynchronous)

 

Outputs are determined by Inputs, only


Example: Full adder with carry-in, carry-out

A	B	C _{in}	S	C _{out}
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

Combinatorial logic may be implemented using Look-Up Tables (LUTs)

LUT = small memory

(Synchronous) sequential logic

 


Outputs are determined by Inputs and their history (Sequence)
The logic has an internal state

Example: 2-bit binary counter

https://www.zepedia.com/read.php?b=9&c=32&d_flip-flop_based_implementation_digital_logic_design


Element that keeps the state: Flip-flop

 

D Flip-flop (D=data, delay) :
samples the data at the rising (or falling) edge of the clock

The output will be equal to the last sampled input until the next rising (or falling) clock edge

(Synchronous) sequential logic

 

Outputs are determined by Inputs and their history (Sequence)
The logic has an internal state

Example: 2-bit binary counter

https://www.zeepeedia.com/read.php?b=9&c=32&d_flip-flop_based_implementation_digital_logic_design


	Flip-flop 1			Flip-flop 2			
time	D	Q	Q'	D= $Q_0 \text{ xor } Q_1$	Q	Q ₁	Q ₀
Before clock edge 1	1	0	1	0	0	0	0
after clock edge 1	0	1	0	1	0	0	1
after clock edge 2	1	0	1	1	1	1	0
after clock edge 3	0	1	0	0	1	1	1
after clock edge 4	1	0	1	0	0	0	0

Synchronous sequential logic

LUT

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

+

 

=

Signal processor

Trigger logic

Data compression logic

Network Interface Card

Neural net classifier




⋮

Using Look-Up-Tables and Flip-Flops
any kind of digital electronics may be implemented

Of course electronics design is an art in itself ...

What is inside an FPGA?


Basic elements of an FPGA

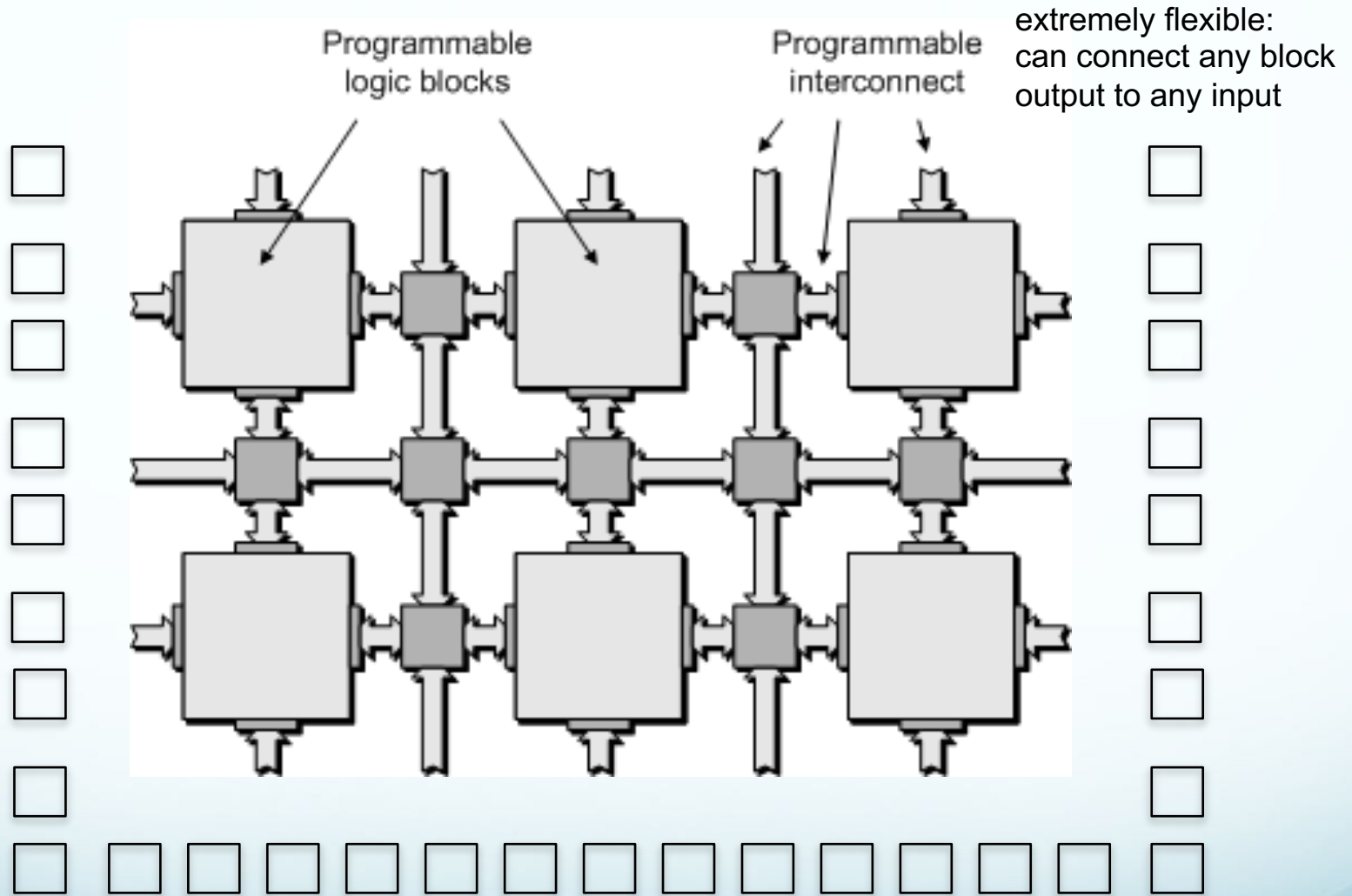


Fine-grained: 10.000's
up to millions of logic blocks

Programmable Input / Output pins

LUT-based Fabrics

 


Typical LUT-based Logic Cell

 

Xilinx: logic cell,
Altera: logic element

- LUT may implement any function of the inputs
- Flip-Flop registers the LUT output
- May use only the LUT or only the Flip-flop
- LUT may alternatively be configured a shift register
- Additional elements (not shown): fast carry logic

General-Purpose Input/Output (GPIO)

 

Today: Up to >1000 user I/O pins

Input and / or output

Voltages from (1.0), 1.2 .. 3.3 V

Many IO standards

Single-ended: LVTTL, LVCMOS, ...

Differential pairs: LVDS, ...

A toy example


Toy example: trigger on energy cluster

1	2	3
4	5	6
7	8	9

Say, we have a 3x3 pixel detector

Each pixel can measure deposited energy with 2 bit resolution

 Trigger condition: the sum of energies deposited in a 2x2 pixel area exceeds 5 counts.



Toy example: VHDL code

1	2	3
4	5	6
7	8	9

We describe the trigger logic in the VHDL(*) hardware description language:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package types is
  type t_energy_array is array (1 to 9) of std_logic_vector (1 downto 0);
end types;
```


types.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.types.all;

entity top is
  Port ( energies : in t_energy_array;
        accept : out STD_LOGIC);
end top;

architecture Behavioral of top is
begin
  -- check only the top left 2x2 cluster
  accept <= '1' when (( '0' & (UNSIGNED('0' & energies(1)) + UNSIGNED('0' & energies(2)))) +
                    ( '0' & (UNSIGNED('0' & energies(4)) + UNSIGNED('0' & energies(5)))) > 5 else '0';
end Behavioral;
```

top.vhd

 

accept

(*) Very High-Speed Integrated Circuit Hardware Description Language


Toy example: constraints

1	2	3
4	5	6
7	8	9

We define which FPGA pins our signals are connected to:

```
set_property PACKAGE_PIN G13 [get_ports {energies[1][0]}]
set_property PACKAGE_PIN B11 [get_ports {energies[1][1]}]
set_property PACKAGE_PIN A11 [get_ports {energies[2][0]}]
set_property PACKAGE_PIN D12 [get_ports {energies[2][1]}]
set_property PACKAGE_PIN D13 [get_ports {energies[3][0]}]
set_property PACKAGE_PIN B18 [get_ports {energies[3][1]}]
set_property PACKAGE_PIN A18 [get_ports {energies[4][0]}]
set_property PACKAGE_PIN K16 [get_ports {energies[4][1]}]
set_property PACKAGE_PIN D4 [get_ports accept]
```

```
set_property PACKAGE_PIN E15 [get_ports {energies[5][0]}]
set_property PACKAGE_PIN E16 [get_ports {energies[5][1]}]
set_property PACKAGE_PIN D15 [get_ports {energies[6][0]}]
set_property PACKAGE_PIN C15 [get_ports {energies[6][1]}]
set_property PACKAGE_PIN J18 [get_ports {energies[7][0]}]
set_property PACKAGE_PIN J17 [get_ports {energies[7][1]}]
set_property PACKAGE_PIN K15 [get_ports {energies[8][0]}]
set_property PACKAGE_PIN J15 [get_ports {energies[8][1]}]
set_property PACKAGE_PIN U12 [get_ports {energies[9][0]}]
set_property PACKAGE_PIN V12 [get_ports {energies[9][1]}]
```

 

accept



Toy example: timing and floorplan

1	2	3
4	5	6
7	8	9

We let the design tool compute the configuration for our FPGA ...
... some minutes later we get the the utilization report

Name	^ 1	Slice LUTs (20800)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (210)
top		2	1	2	9


... and can look at the floor plan

  

accept

Toy example: floorplan

1	2	3
4	5	6
7	8	9



 


Toy example: floorplan

1	2	3
4	5	6
7	8	9



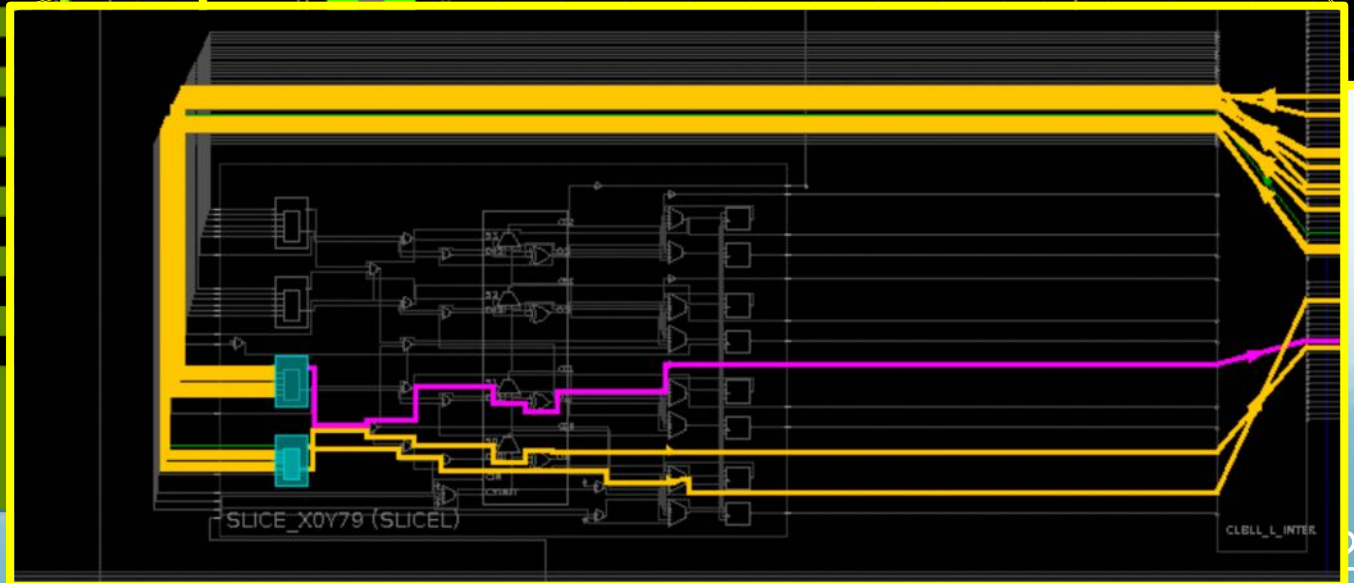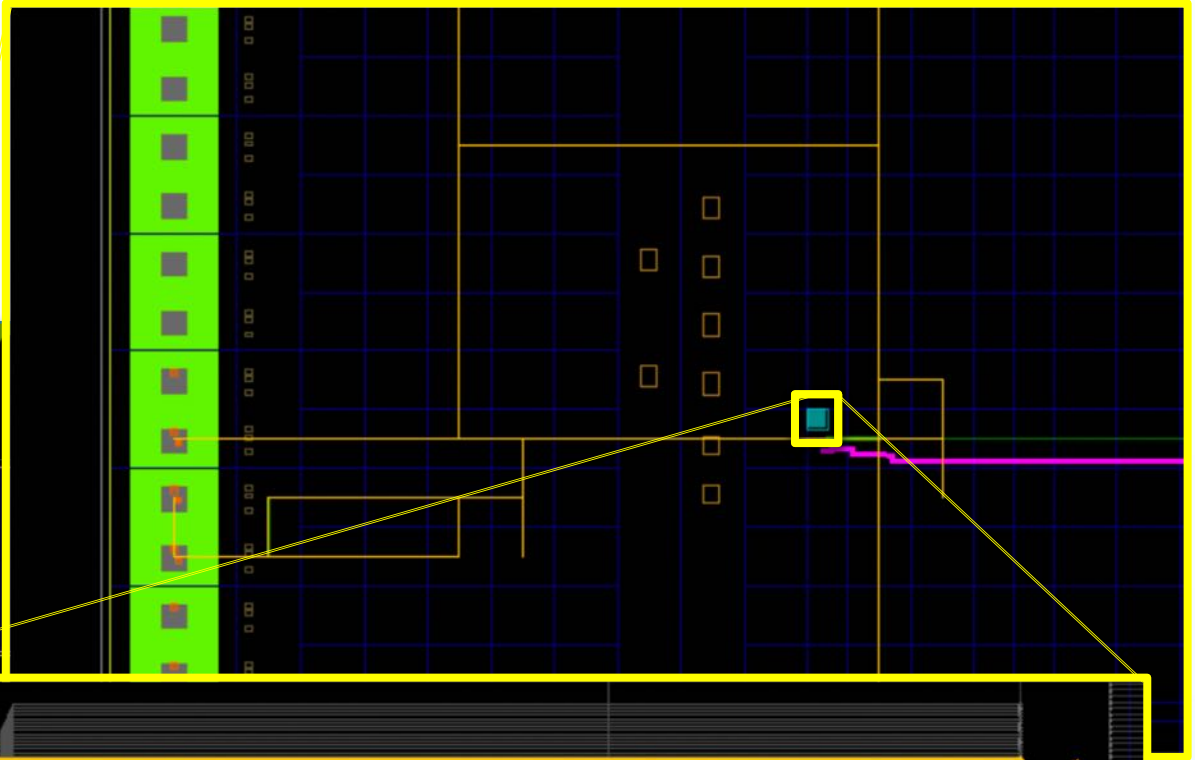
 
- e₁ — 2//
- e₂ — 2//
- e₃ — 2//
- e₄ — 2//
- e₅ — 2//
- e₆ — 2//
- e₇ — 2//
- e₈ — 2//
- e₉ — 2//



Toy example: Register Transfer Level (RTL) design

1	2	3
4	5	6
7	8	9

  The design tool can also display the schematics of the circuit:



Toy example: Full example, 4 possible clusters

1	2	3
4	5	6
7	8	9

Let's do the full example:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use work.types.all;

entity top is
  Port ( energies : in t_energy_array;
        accept : out STD_LOGIC);
end top;


architecture Behavioral of top is
  function check_cluster_energy (energies : t_energy_array;
                                i1, i2, i3, i4 : integer) return boolean is
    variable sum1, sum2 : unsigned(2 downto 0);
  begin
    sum1 := UNSIGNED('0' & energies(i1)) + UNSIGNED('0' & energies(i2));
    sum2 := UNSIGNED('0' & energies(i3)) + UNSIGNED('0' & energies(i4));
    return (('0' & sum1) + ('0' & sum2)) > 5;
  end check_cluster_energy;
begin
  accept <= '1' when check_cluster_energy(energies, 1,2,4,5)
    or check_cluster_energy(energies, 4,5,7,8)
    or check_cluster_energy(energies, 2,3,5,6)
    or check_cluster_energy(energies, 5,6,8,9)
  else '0';
end Behavioral;
```

check all 4 possible
2x2 regions

top.vhd

accept

e1
e2
e3
e4
e5
e6
e7
e8
e9

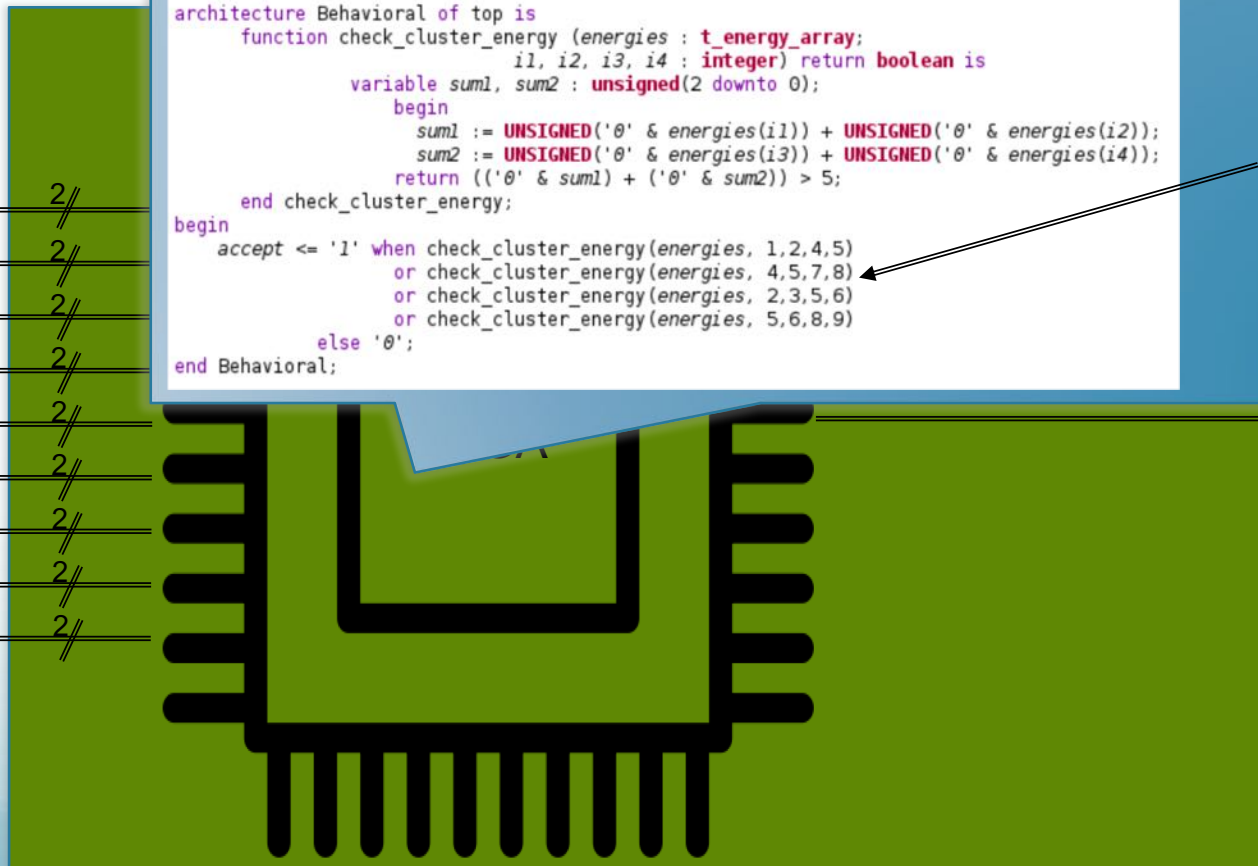



Toy example: resource usage and floorplan



We let the design tool compute the configuration for our FPGA

Name ^ 1	Slice LUTs (20800)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (210)
N top	10	4	10	19

utilization report

  




Toy example: floorplan



We let the design tool compute the configuration for our FPGA


Name ^ 1	Slice LUTs (20800)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (210)
N top	10	4	10	19

utilization report

   


Toy example: RTL design

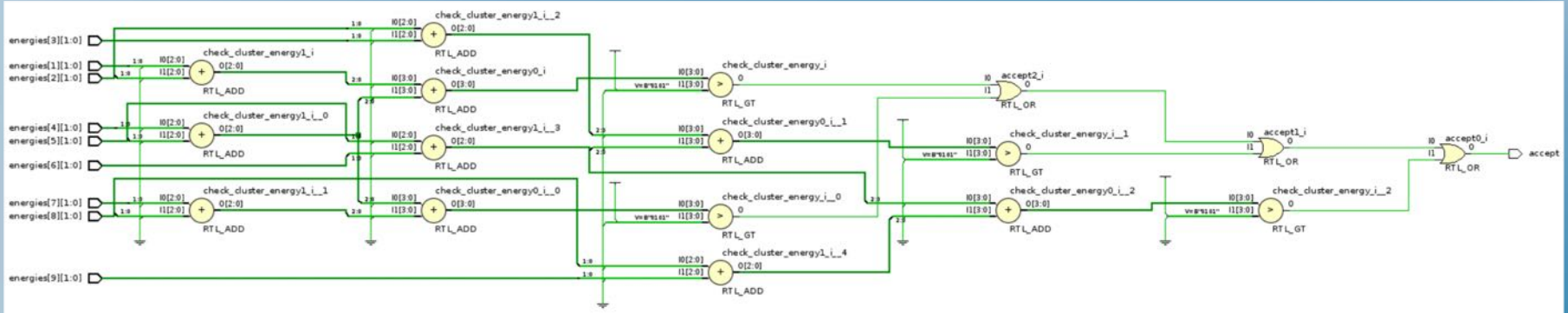Again, we can look at the generated schematics:



 If we look closely, we can see that adders that are shared between adjacent 2x2 areas, are only implemented once.




Toy example: Timing

1	2	3
4	5	6
7	8	9

Timing: In this example asynchronous design using a Xilinx Artix 7
(note that asynchronous designs are not how we typically use FPGAs)

Input-to-output delay: ~ 10 ns

 


Toy example: Timing

1	2	3
4	5	6
7	8	9

Timing: In this example asynchronous design using a Xilinx Artix 7 (note that asynchronous designs are not how we typically use FPGAs)


Input-to-output delay: ~ 10 ns

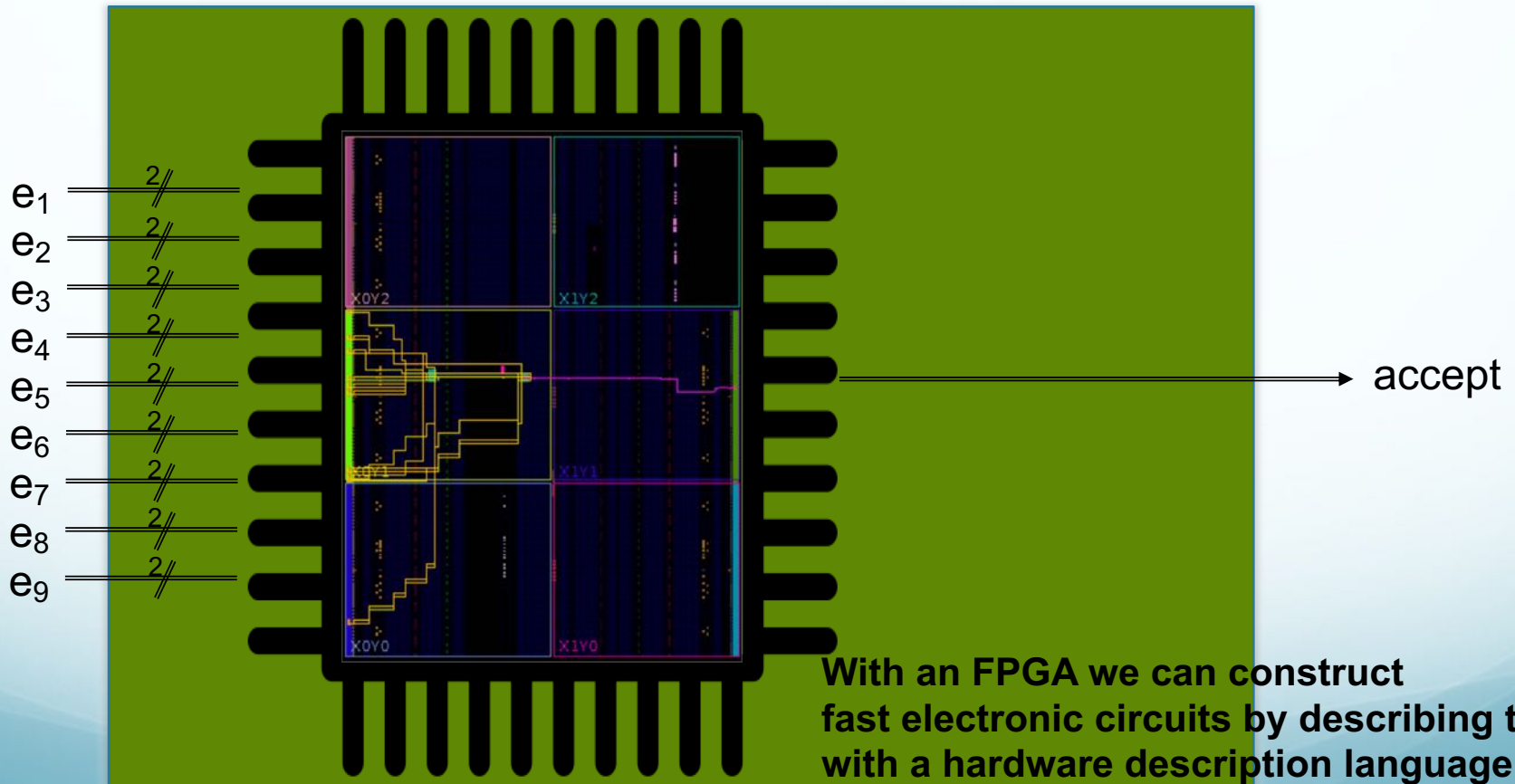

With an FPGA we can construct fast electronic circuits by describing them with a hardware description language.

Doing the same with a microcontroller

1	2	3
4	5	6
7	8	9

 


Doing the same with a microcontroller

1	2	3
4	5	6
7	8	9



e₁
e₂
e₃
e₄
e₅
e₆
e₇
e₈
e₉

 

We write code that is executed by a processor

```
const int PINS_E_LOW[] = { 2, 4, 6, 8, 10, 22, 26, 30, 34 };
const int PINS_E_HIGH[] = { 3, 5, 7, 9, 11, 24, 28, 32, 36 };
const int PIN_ACCEPT = 13;

void setup() {
  for (int i=0;i<9;++i) {
    pinMode(PINS_E_LOW[i], INPUT);
    pinMode(PINS_E_HIGH[i], INPUT);
  }
  pinMode(PIN_ACCEPT, OUTPUT);
}

void loop() {
  unsigned int e[9];
  for (int i=0;i<9;++i) {
    e[i] = digitalRead(PINS_E_LOW[i]) < HIGH ? 1 : 0
          + (digitalRead(PINS_E_HIGH[i]) < HIGH ? 1 : 0) << 1;
  }

  if ( (e[0]+e[1]+e[3]+e[4] > 5) ||
        (e[3]+e[4]+e[6]+e[7] > 5) ||
        (e[1]+e[2]+e[4]+e[5] > 5) ||
        (e[4]+e[5]+e[7]+e[8] > 5) )
    digitalWrite(PIN_ACCEPT, HIGH);
  else
    digitalWrite(PIN_ACCEPT, LOW);
}
```

Probably about ~50-100 instructions at 20 MHz

Input to output delay: 2-5 μs

accept

Microcontroller vs FPGA




	μC / CPU	FPGA
Principle of operation	Source code is translated to machine instructions and executed by CPU	Hardware Description Language is translated to configuration of FPGA, defining an electronic circuit
Processing time	Microseconds	10's of nanoseconds

A closer look at FPGAs

Additional elements in an FPGA


- Besides logic cells and interconnect (distributed logic) we have additional elements in an FPGA:
 - Either to provide functions that cannot be implemented with distributed logic (because the logic would be too slow)
 - Clock resources, clock Managers
 - Gigabit transceivers
 - ...
 - Or to provide functionality that could also be implemented with distributed logic, but is more efficiently(*) implemented as a hard macro (in silicon)
 - Multipliers, DSPs
 - RAM
 - Processors

Clock Trees

 


Typical FPGA designs use one or multiple clocks
Clock trees guarantee that the clock arrives at the same time at all flip-flops
Typical fabric clock 10's to 100's of MHz up to ~ 1 GHz

Clock Managers

 


Our toy example with clock

Adding a clock and flip-flops

 


We transform our design into a pipeline with 3 processing stages

Adding a clock and flip-flops

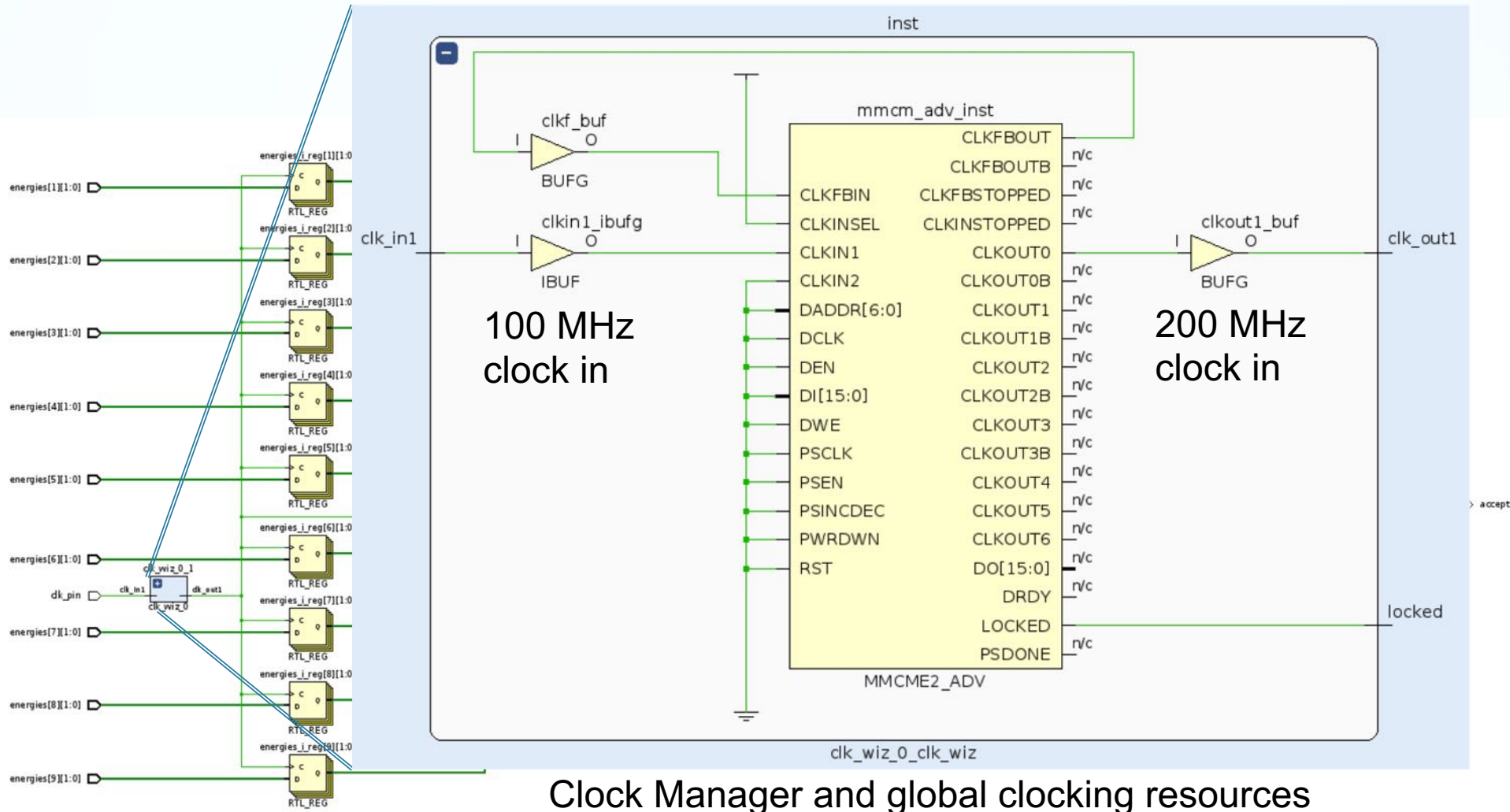


Clock Manager and global clocking resources

Adding a clock and flip-flops

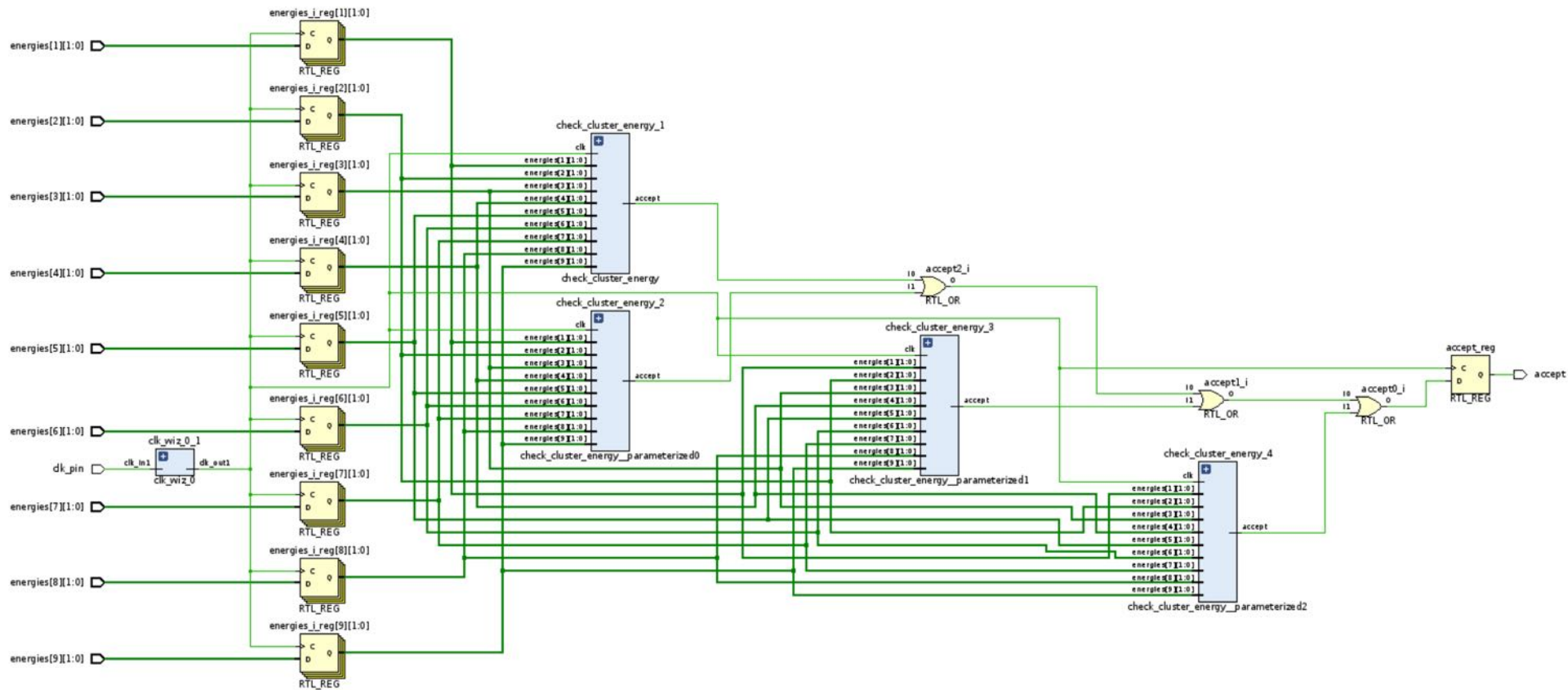

We transform our design into a pipeline with 3 processing stages


Adding a clock and flip-flops

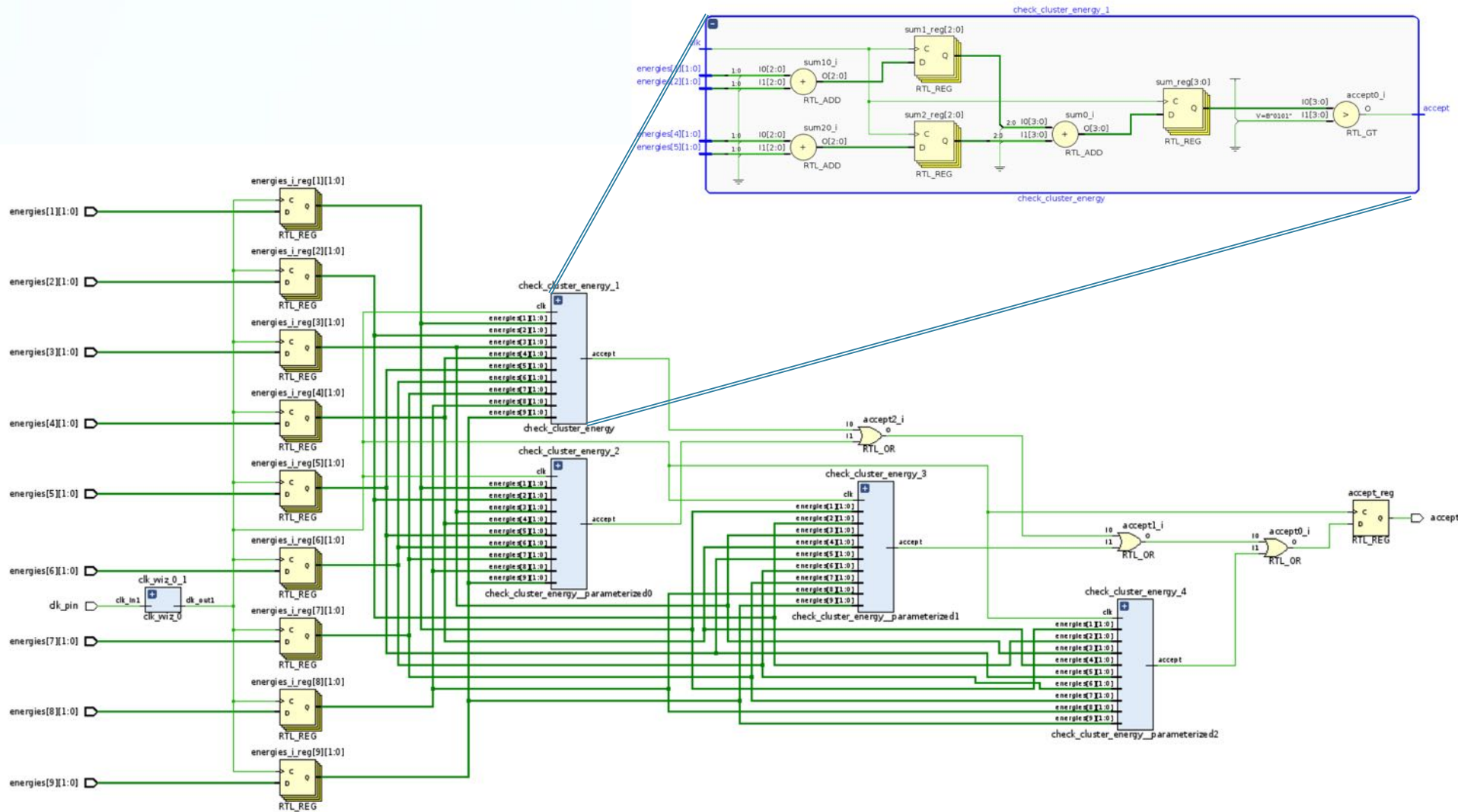


We transform our design into a pipeline with 3 processing stages

Resource usage & floorplan



Name	^1	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (210)	ILOGIC (210)	OLOGIC (210)	BUFGCTRL (32)	MMCME2_ADV (5)
▼ N top		27	30	10	27	20	18	1	2	1
▶ check_cluster_energy_1 (check_cluster_energy)		9	9	5	9	0	0	0	0	0
▶ check_cluster_energy_2 (check_cluster_energy__parameterized0)		5	6	2	5	0	0	0	0	0
▶ check_cluster_energy_3 (check_cluster_energy__parameterized1)		8	9	3	8	0	0	0	0	0
▶ check_cluster_energy_4 (check_cluster_energy__parameterized2)		5	6	2	5	0	0	0	0	0
> ▶ clk_wiz_0_1 (clk_wiz_0)		0	0	0	0	0	0	0	2	1

 


Floorplan: clock resources

 


4. Global Clock lines

  

1. Clock capable input pin

 

2. Clock manager






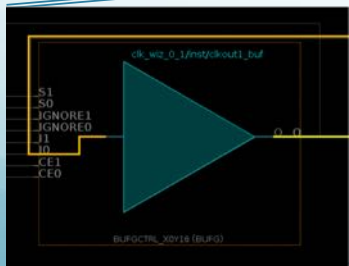


3. Global Clock buffer

Floorplan: flip-flops

1. Input flip-flop near pad

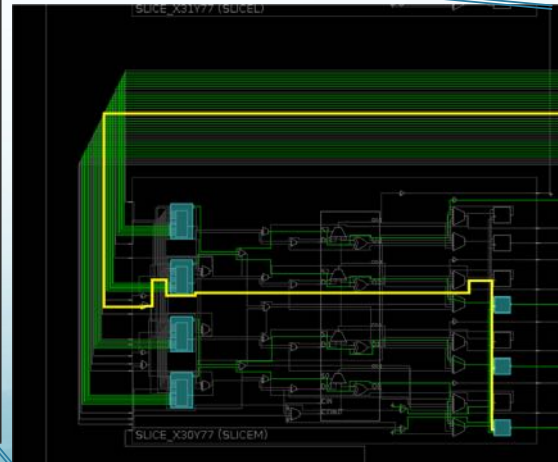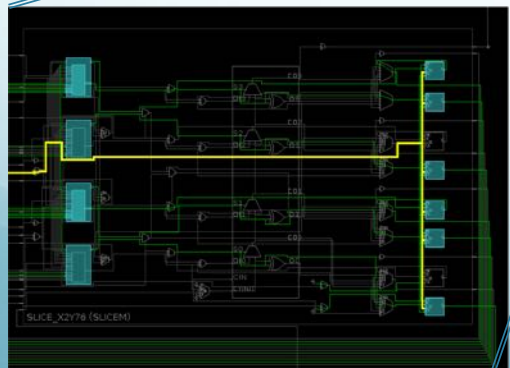    4. Output flip-flops near pad after comparator stage



2. Flip-flops after first adder stage

3. Flip-flops after second adder stage

VHDL code

3) Instantiate cluster energy check module

```
entity top is
  Port ( energies : in t_energy_array;
        accept : out STD_LOGIC;
        clk_pin : in std_logic);
end top;

architecture Behavioral of top is

  component clk_wiz_0 is
    port (
      clk_out1 : out STD_LOGIC;
      locked   : out STD_LOGIC;
      clk_in1  : in  STD_LOGIC);
  end component clk_wiz_0;

  component check_cluster_energy is
    generic (
      i1, i2, i3, i4 : integer);
    port (
      energies : in  t_energy_array;
      accept   : out STD_LOGIC;
      clk      : in  std_logic);
  end component check_cluster_energy;

  signal clk, locked : std_logic;
  signal energies_i : t_energy_array;
  signal accept1, accept2, accept3, accept4 : std_logic;
begin
```

```
clk_wiz_0_1: entity work.clk_wiz_0
  port map (
    clk_out1 => clk,
    locked   => locked,
    clk_in1  => clk_pin);
```

```
reg_inputs: process (clk) is
begin
  if rising_edge(clk) then
    energies_i <= energies;
  end if;
end process reg_inputs;
```

```
check_cluster_energy_1: entity work.check_cluster_energy
  generic map (
    i1 => 1,
    i2 => 2,
    i3 => 4,
    i4 => 5)
  port map (
    energies => energies_i,
    accept   => accept1,
    clk      => clk);

check_cluster_energy_2: entity work.check_cluster_energy...
check_cluster_energy_3: entity work.check_cluster_energy...
check_cluster_energy_4: entity work.check_cluster_energy...

reg_output: process (clk) is
begin
  if rising_edge(clk) then
    accept <= accept1 or accept2 or accept3 or accept4;
  end if;
end process reg_output;

end Behavioral;
```

1) Instantiate clocking logic

- Customized firmware block produced by FPGA design tool
- Also called IP (Intellectual Property) Core

2) Clocked process: register inputs

4) Clocked process: register OR of Cluster checks

VHDL code – cluster energy check

```
entity check_cluster_energy is
  generic (i1, i2, i3, i4: integer);
  port (energies : in t_energy_array;
        accept : out STD_LOGIC;
        clk : in std_logic);
end entity check_cluster_energy;

architecture Behavioral of check_cluster_energy is

  signal sum1, sum2 : UNSIGNED(2 downto 0);
  signal sum : UNSIGNED(3 downto 0);
begin -- architecture Behavioral

p1: process (clk) is
  begin -- process p1
    if clk'event and clk = '1' then -- rising clock edge
      sum1 <= UNSIGNED('0' & energies(i1)) + UNSIGNED('0' & energies(i2));
      sum2 <= UNSIGNED('0' & energies(i3)) + UNSIGNED('0' & energies(i4));
      sum <= UNSIGNED('0' & sum1) + UNSIGNED('0' & sum2);
    end if;
  end process p1;

  accept <= '1' when sum > 5 else '0';
end architecture Behavioral;
```

Inside clocked process:
<= assignment creates flip-flop

Outside process: asynchronous logic

Constraints

```
set_property PACKAGE_PIN V12 [get_ports {energies[9][1]}]
```

Assign clock pin

```
set_property PACKAGE_PIN E3 [get_ports clk_pin]
```


Use input/output flip-flops

```
set_property IOB true [get_ports {energies[1][0]}]
set_property IOB true [get_ports {energies[1][1]}]
set_property IOB true [get_ports {energies[2][0]}]
set_property IOB true [get_ports {energies[2][1]}]
set_property IOB true [get_ports {energies[3][0]}]
set_property IOB true [get_ports {energies[3][1]}]
set_property IOB true [get_ports {energies[4][0]}]
set_property IOB true [get_ports {energies[4][1]}]
```

```
set_property IOB true [get_ports {energies[5][0]}]
set_property IOB true [get_ports {energies[5][1]}]
set_property IOB true [get_ports {energies[6][0]}]
set_property IOB true [get_ports {energies[6][1]}]
set_property IOB true [get_ports {energies[7][0]}]
set_property IOB true [get_ports {energies[7][1]}]
set_property IOB true [get_ports {energies[8][0]}]
set_property IOB true [get_ports {energies[8][1]}]
set_property IOB true [get_ports {energies[9][0]}]
set_property IOB true [get_ports {energies[9][1]}]
```

```
set_property IOB true [get_ports accept]
```

Timing

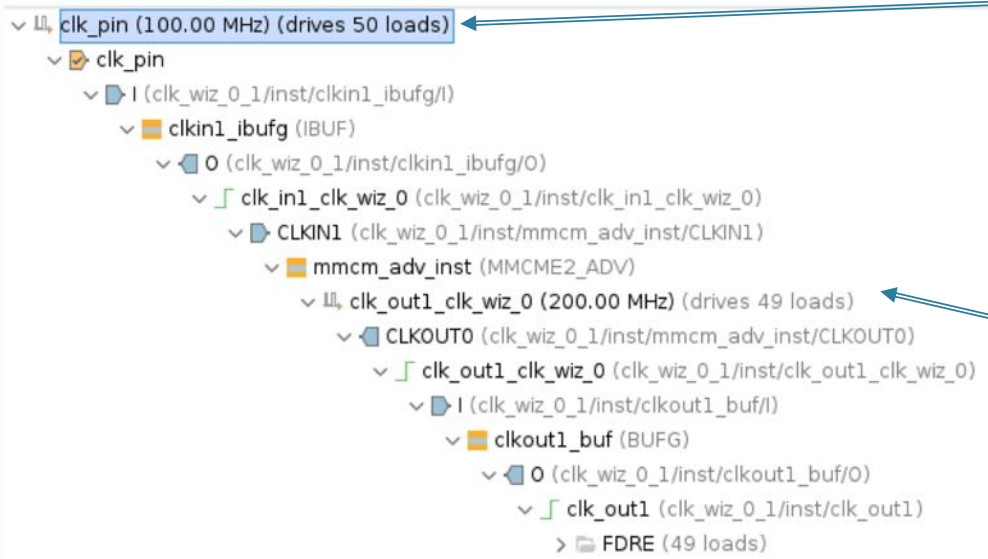

100 MHz clock at pin

200 MHz internal clock
(we set this as a
parameter to the clock
manager)


**Design can check for clusters at 200 MHz (every 5 ns),
but needs 4 clock cycles (20 ns) to compute the trigger decision**

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 0.478 ns	Worst Hold Slack (WHS): 0.392 ns	Worst Pulse Width Slack (WPWS): 2.000 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 31	Total Number of Endpoints: 31	Total Number of Endpoints: 55

All user specified timing constraints are met.

Other elements in FPGAs


Embedded RAM blocks

 


Can be used in many ways:
Look-up of mathematical function
Buffer memory
...

Today: Up to ~500 Mbit of RAM⁴⁹

Embedded Multipliers & DSPs

 


Digital Signal Processor (DSP)

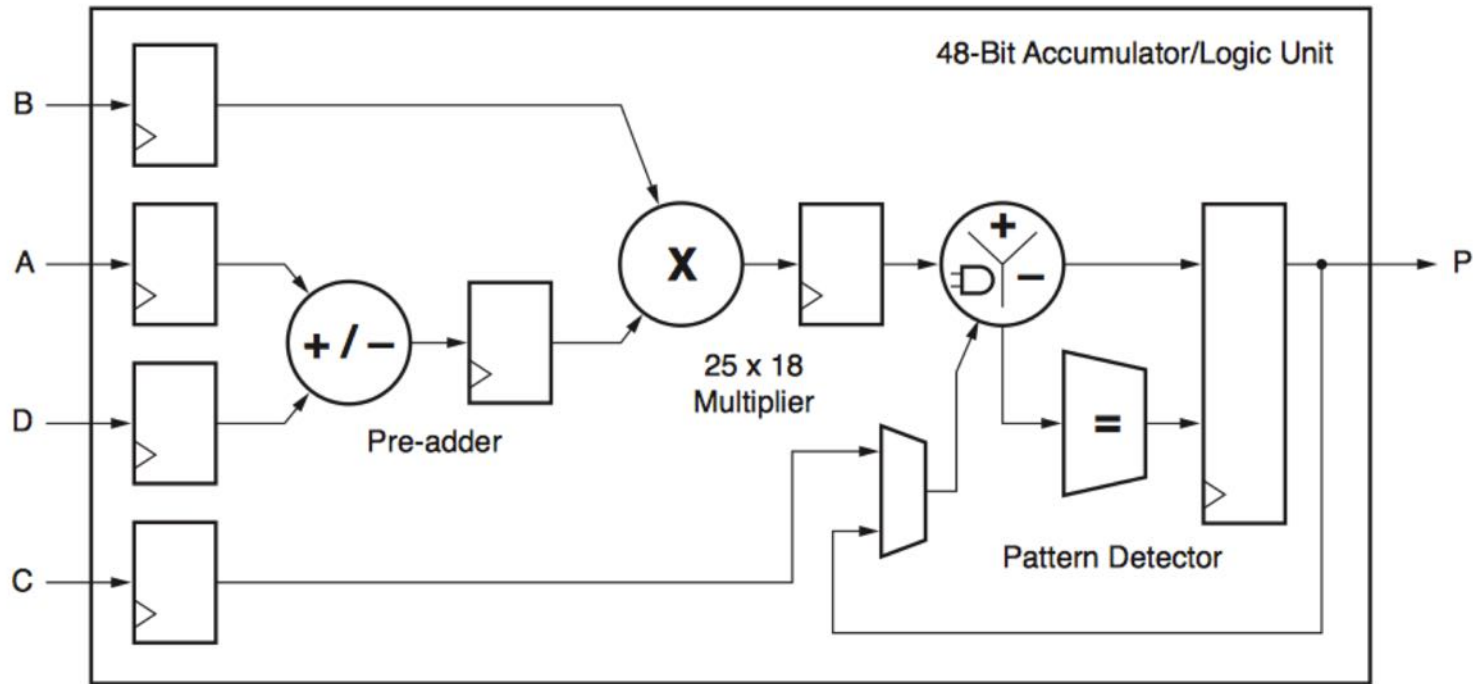

DSP block (Xilinx 7-series)
Up to several 1000 per chip


Soft and Hard Processor Cores

 - Soft core
 - Design implemented with the programmable resources (logic cells) in the chip
- Hard core
 - Processor core that is available in addition to the programmable resources
 - E.g.: Power PC, ARM




High-Speed Serial Interconnect

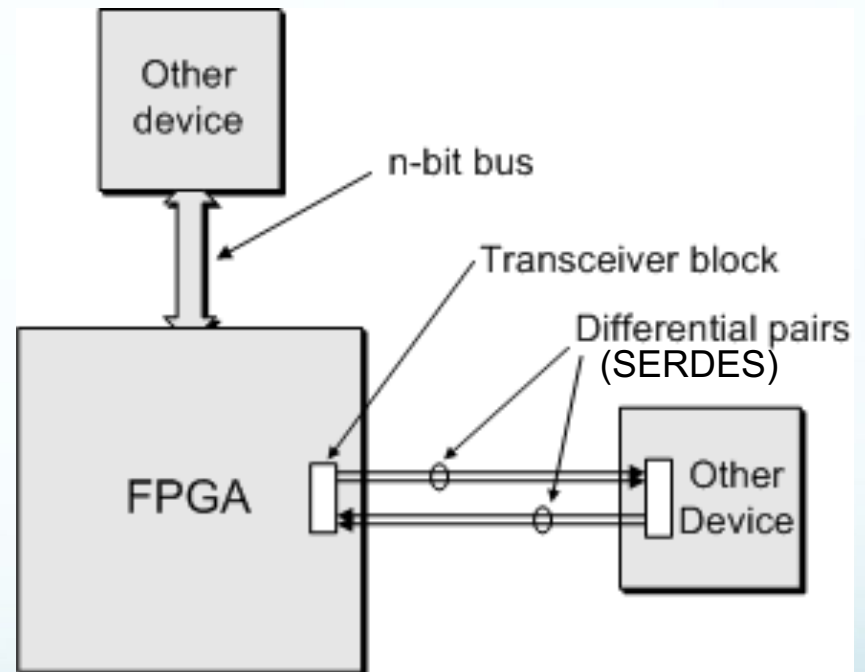- Using differential pairs
- Standard I/O pins limited to about 1 Gbit/s
- Latest serial transceivers: typically 25 Gb/s
 - up to 112 Gb/s with Pulse Amplitude Modulation (PAM)
- FPGAs with multi-Tbit/s IO bandwidth



Components in a modern FPGA

 

- Logic block
- SRAM block
- Multiplier
- DSP block
- PLL
- Clock Manager
- I/O Bank
- SERDES block

Programming techniques

Fusible Links (not used in FPGAs)





Unprogrammed link




Programmed link

Antifuse Technology

  

EPRM Technology


Erasable Programmable Read Only Memory

 

Intel, 1971

EEPROM and FLASH Technology

 Electrically Erasable Programmable Read Only Memory




EEPROM: erasable word by word

FLASH: erasable by block or by device

Erasure by "Fowler-Nordheim" Tunneling


SRAM-Based Devices

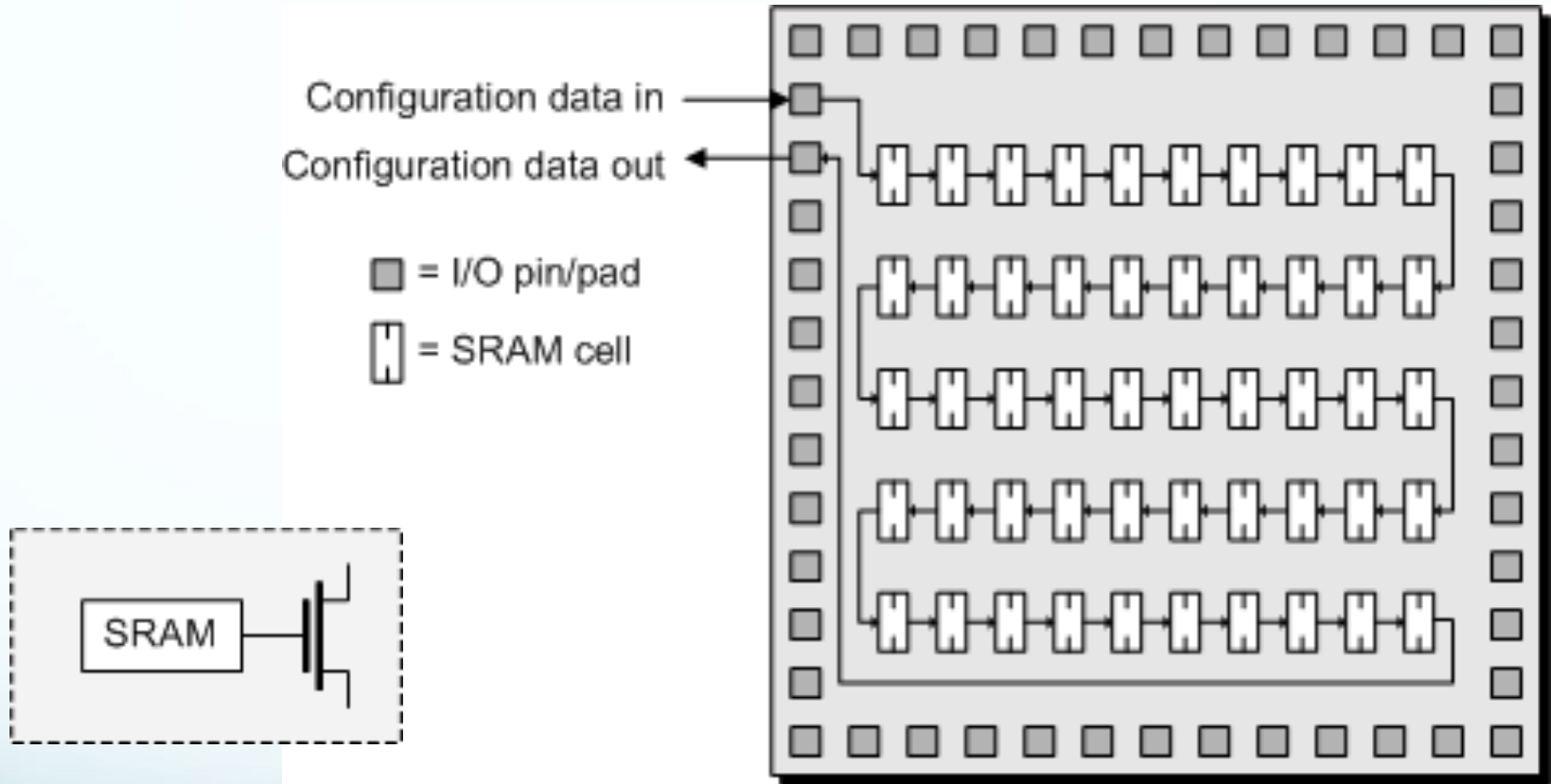


Multi-transistor SRAM cell

Programming a 3-bit wide LUT

 


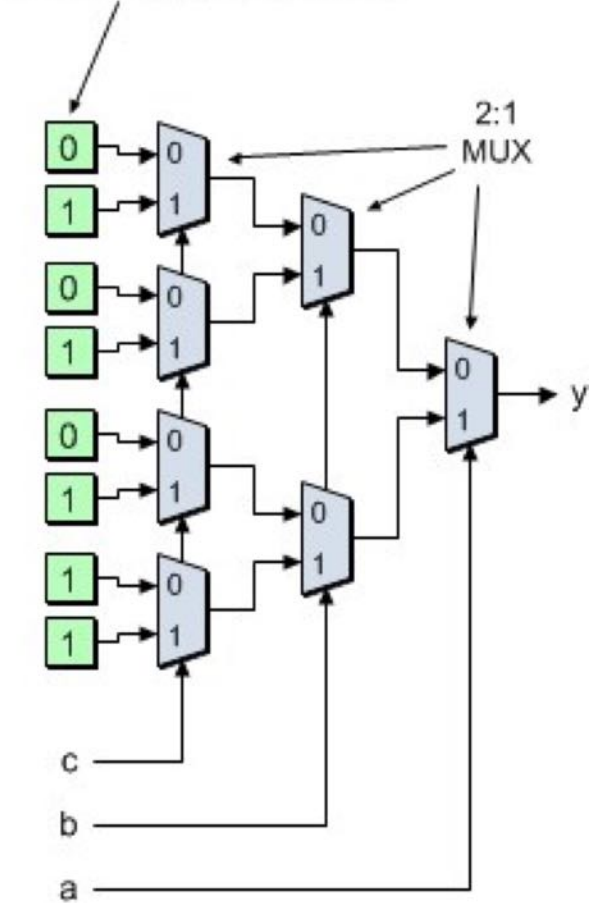

Hard-wired 0s and 1s
(Antifuse technology)



SRAM cells
(SRAM-based technology)

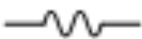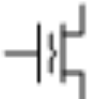

Summary of Technologies

Technology	Symbol	Predominantly associated with ...
Fusible-link		SPLDs
Antifuse		FPGAs
EPROM		SPLDs and CPLDs
E ² PROM/ FLASH		SPLDs, CPLDs, and FPGAs
SRAM		FPGAs (some CPLDs)

← Rad-tolerant secure

← Rad-tolerant (e.g. Alice)

← Used in most FPGAs

Major Manufacturers

- AMD Xilinx (formerly Xilinx)
 - First company to produce FPGAs in 1985
 - About 55% market share, today
 - SRAM based CMOS devices
- Intel FPGA (formerly Altera)
 - About 35% market share
 - SRAM based CMOS devices
- Microchip (Microsemi, Actel)
 - Anti-fuse FPGAs
 - Flash based FPGAs
 - Mixed Signal
- Lattice Semiconductor
 - SRAM based with integrated Flash PROM
 - low power



Bought by AMD in 2022




Altera bought by Intel in 2015



Trends

Ever-decreasing feature size

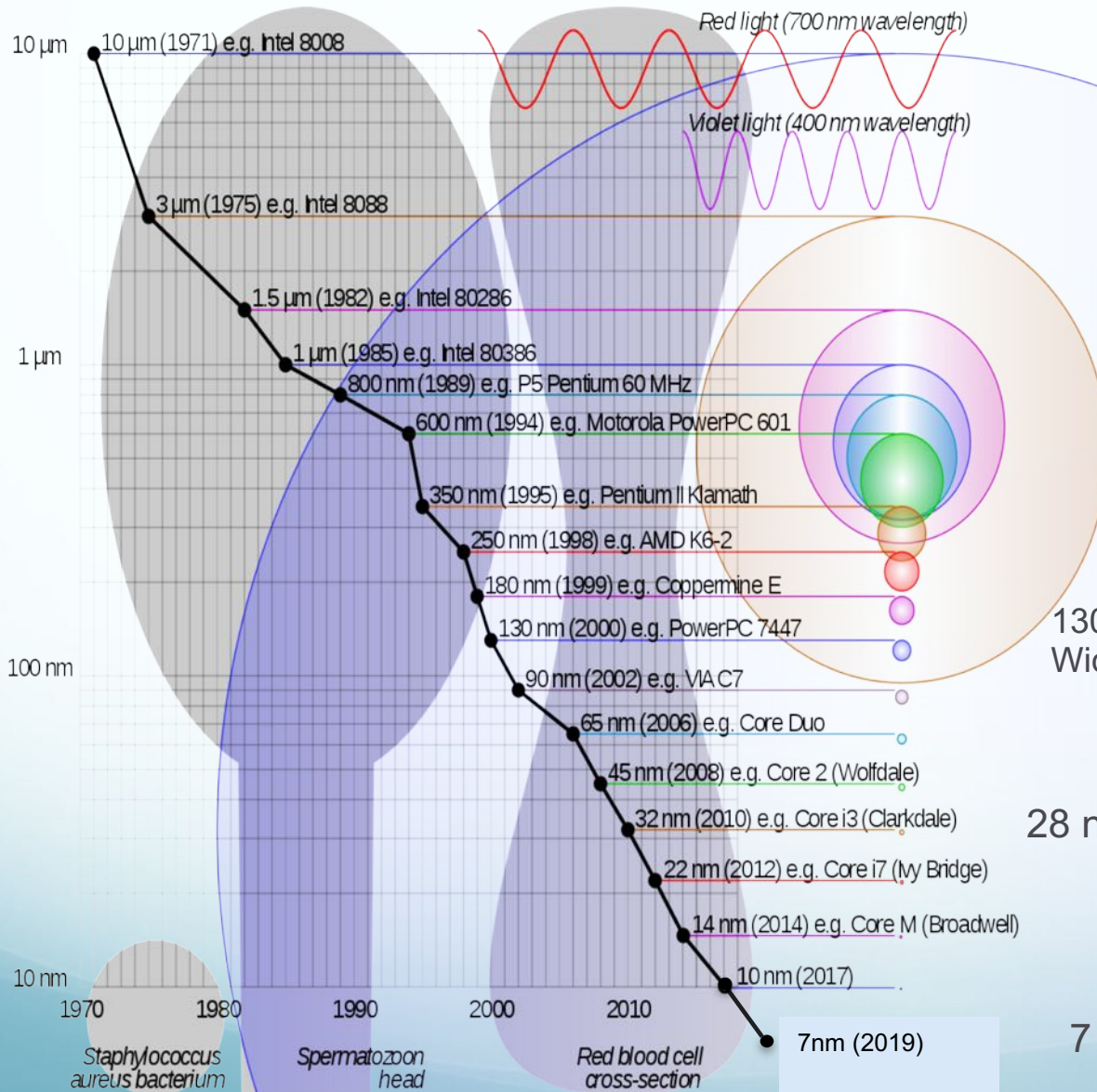

- Higher capacity
- Higher speed
- Lower power consumption

130 nm Xilinx Virtex-2
Widely used at LHC startup

28 nm Xilinx Virtex-7 / Altera Stratix V
16 nm Xilinx UltraScale +
14 nm Intel Stratix 10

7 nm Xilinx Versal ACAP(*)


Technology nodes < 28 nm are commercial names and do not represent any geometry of transistors.

(*) Adaptive Compute Acceleration Platform

Trends

- Speed of logic keeps increasing
- Look-up-tables with more inputs (5 or 6)
- Speed of serial links increasing (multiple Gb/s)
- More integrated memory
 - Integrated High Bandwidth Memory (HBM) in-package
 - 10x faster than DDR4 (Xilinx: up to 8 GB, Intel: up to 16GB)
- More and more hard macro cores on the FPGA
 - PCI Express
 - Gen2: 5 Gb/s per lane
 - Gen3: 8 Gb/s per lane (typically up to 16 lanes)
 - Gen4: 16 Gb/s per lane
 - 10 Gb/s, 40 Gb/s, 100 Gb/s Ethernet, 150 Gb/s Interlaken
- Sophisticated soft macros
 - CPUs
 - Gb/s MACs
 - Memory interfaces (DDR2/3/4)
- Processor-centric architectures – see next slide

System-On-a-Chip (SoC) FPGAs

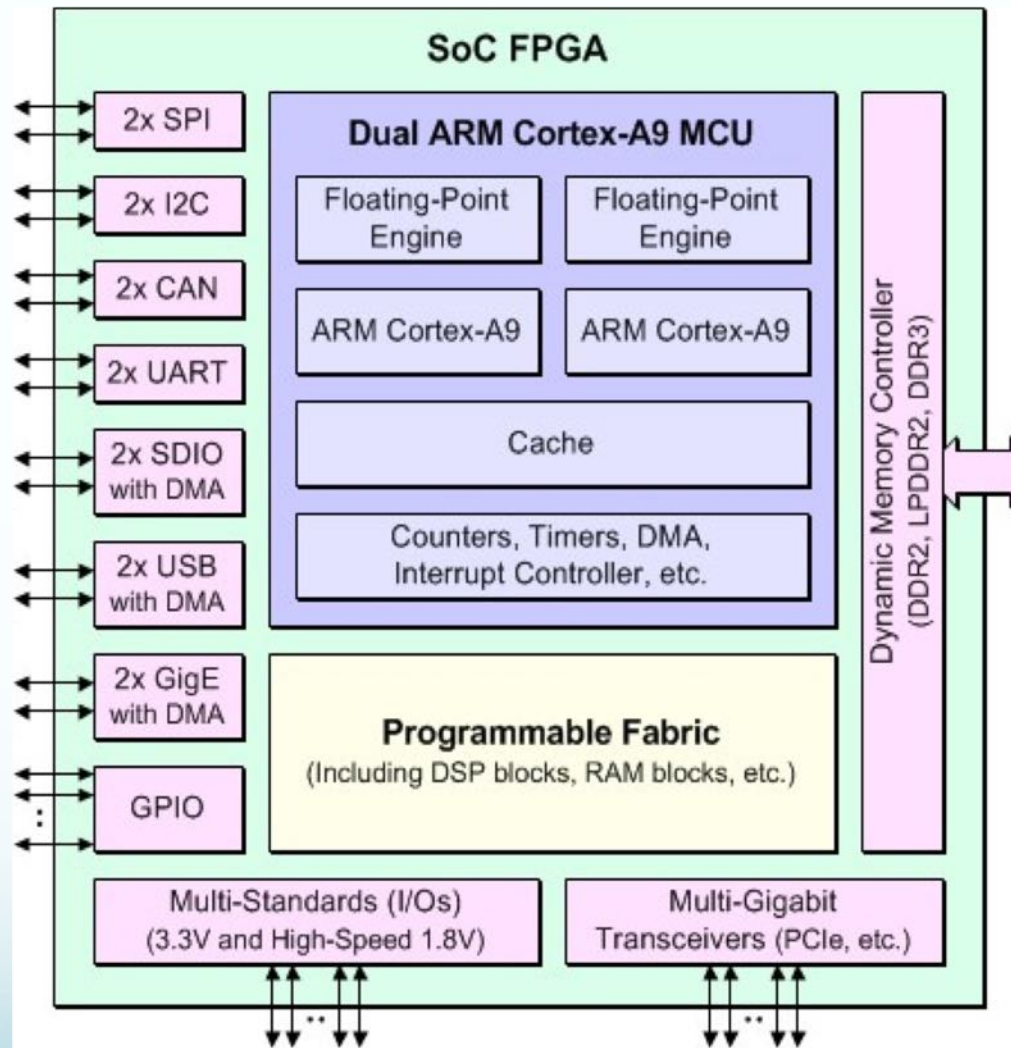


Xilinx Zynq

Intel Stratix 10 SoC

CPU(s) + Peripherals + FPGA in one package

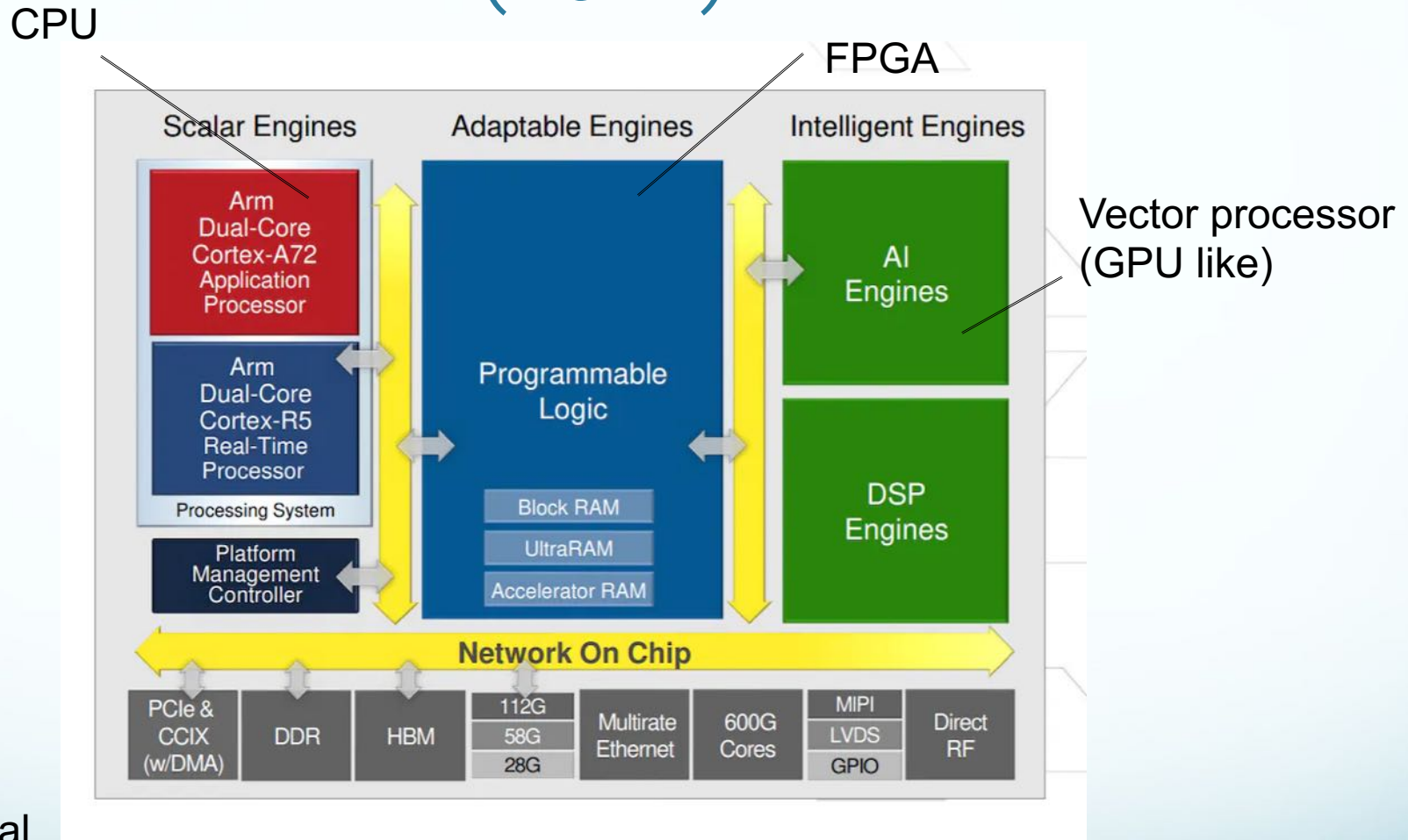Adaptive Compute Acceleration Platform (ACAP)



Xilinx Versal

<https://www.electronicdesign.com/markets/automation/video/21234012/electronic-design-versal-card-streamlines-acap-fpga-ai-development>

CPU(s) + Peripherals + FPGA + AI (Adaptable Intelligence) Engines in one package

FPGA – ASIC comparison


FPGA

- A chip (the FPGA) is configured to represent a digital circuit
- May be reprogrammed in the field (gateway upgrade)
 - New features
 - Bug fixes
- Rapid development cycle (minutes / hours)
- Only digital designs are possible
- Low development cost
 - You can get started with a development board (< \$100) and free software
- High-end FPGAs rather expensive



ASIC(*)

- A chip is produced in a foundry for a specific purpose
- Design cannot be changed once it is produced
- Long development cycle (weeks / months)
- Analog designs possible
- Higher performance
 - Speed, Area, Power
- Better radiation hardness
- Extremely high development cost
 - ASICs are produced at a semiconductor fabrication facility ("fab") according to your design
- Lower cost per device compared to FPGA, when large quantities are needed

 


(*) Application Specific Integrated Circuit

FPGA design flow

Design entry

Schematics

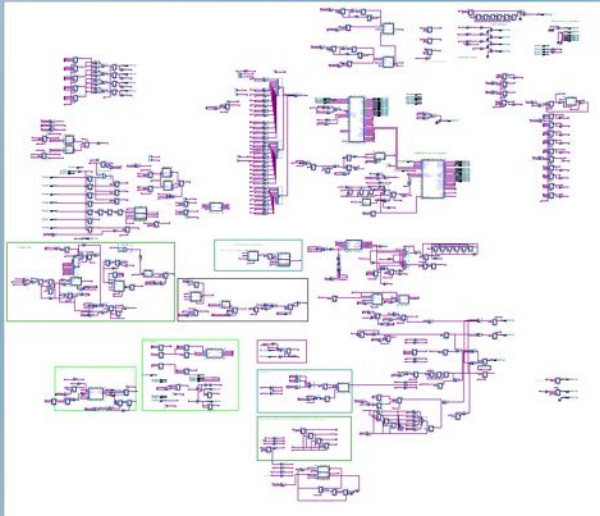

- Graphical overview
- Can draw entire design
- Use pre-defined blocks

rarely used today

Hardware description language VHDL, Verilog

```
entity DelayLine is
    generic (
        n_halfcycles : integer := 2);
    port (
        x           : in std_logic_vector;
        x_delayed  : out std_logic_vector;
        clk         : in std_logic);
end entity DelayLine;
```

- Can generate blocks using loops
- Can synthesize algorithms
- Independent of design tool
- May use tools used in SW development (SVN, git ...)

Hardware Description Language

- Looks similar to a programming language
 - BUT be aware of the difference
 - Programming language => translated into machine instructions that are executed by a CPU
 - HDL => translated into gateware (logic gates & flip-flops)
- Common HDLs
 - VHDL
 - Verilog
 - AHDL (Altera specific)
- Newer trends
 - C-like languages (handle-C, System C)
 - Labview
 - High Level Synthesis (HLS) from C/C++

Example: VHDL

architecture behavioral of VMEReg is

```
signal vme_en_i    : std_logic;
signal Q          : std_logic_vector(15 downto 0);
```

```
begin -- behavioral
```

```
vme_addr_decode : process (vme_addr, vme_en) is
  variable my_addr_vec : std_logic_vector(vme_addr'high downto 0);
  variable selected    : boolean;
begin -- process vme_addr_decode
  my_addr_vec := std_logic_vector( TO_UNSIGNED ( my_vme_base_address, vme_addr'high+1 ) );
  selected    := my_addr_vec(vme_addr'high downto 1) = vme_addr(vme_addr'high downto 1);
  vme_en_i <= '0' ;
  if selected then
    vme_en_i <= vme_en;
  end if;
end process vme_addr_decode;
```

Asynchronous logic
All signals in sensitivity list

```
reg: process (vme_clk, reset) is
begin -- process reg
  if reset = '1' then
    Q <= init_val;
    vme_en_out <= '0';
  elsif vme_clk'event and vme_clk = '1' then -- rising clock edge
    vme_en_out <= vme_en_i;
    if vme_en_i = '1' and vme_wr = '1' then
      Q <= vme_data;
    end if;
  end if;
end process reg;
```

Synchronous logic
Only clock (and reset) in sensitivity list


```
data <= Q;
vme_data_out <= Q;
```

```
end behavioral;
```

- Looks like a programming language
- All statements executed in parallel, except inside processes

Schematics & HDL combined


Graphical State Diagram

 


Textual HDL

```
When clock rises  
if (s == 0)  
  then y = (a & b) | c;  
  else y = c & !(d ^ e);
```


Top-level
block-level
schematic

 


Graphical Flowchart

 

Block-level schematic

 

Design flow

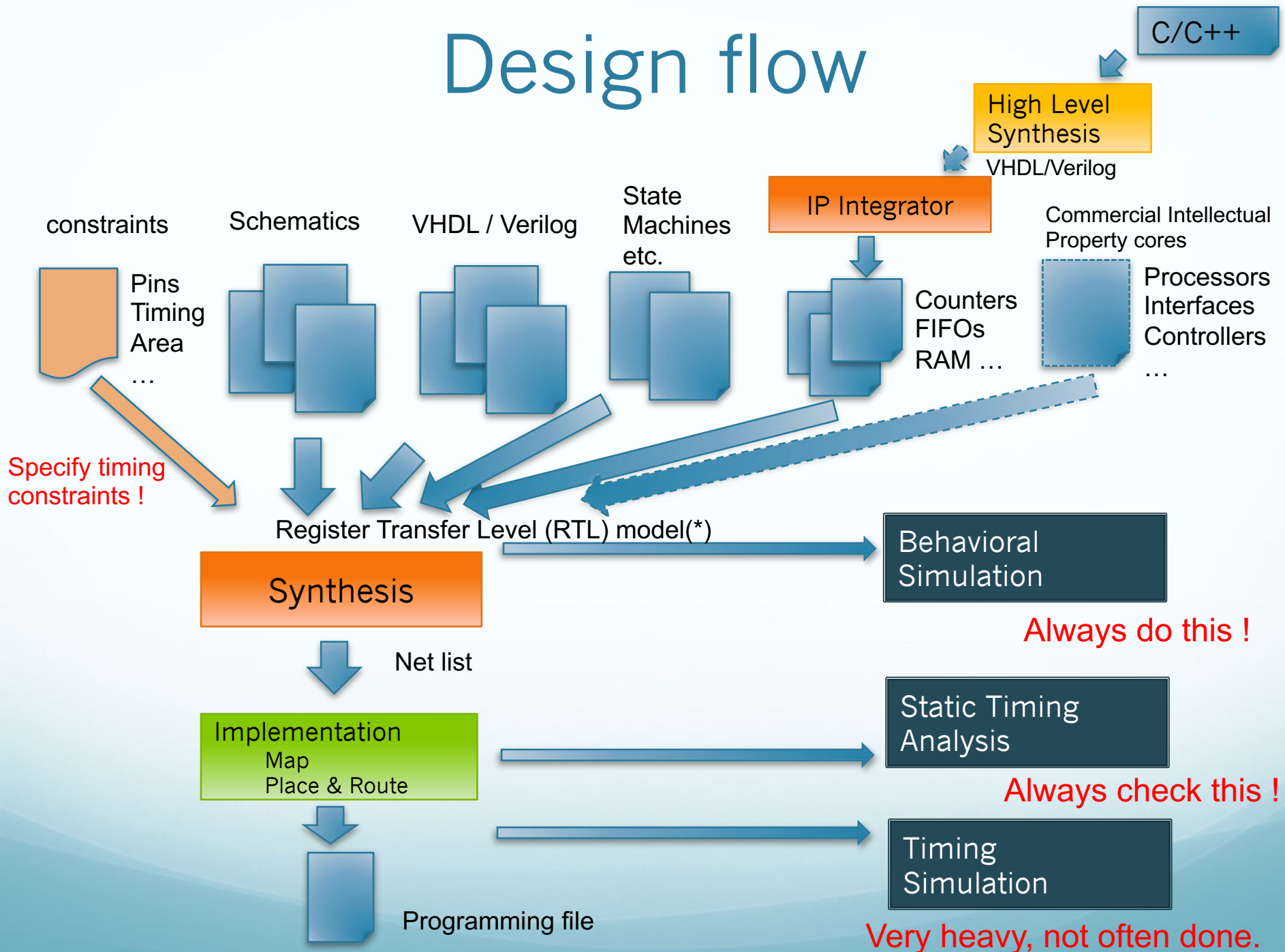

C/C++

High Level Synthesis

VHDL/Verilog

IP Integrator

Commercial Intellectual Property cores

Processors
Interfaces
Controllers
...

Counters
FIFOs
RAM ...

State Machines
etc.

VHDL / Verilog

Schematics

constraints
Pins
Timing Area
...

Specify timing constraints !

Register Transfer Level (RTL) model(*)

Synthesis

Behavioral Simulation

Always do this !

Net list

Implementation
Map
Place & Route

Static Timing Analysis

Always check this !



Programming file

Timing Simulation



Very heavy, not often done.

(*) asynchronous logic + registers (=flip-flops)

Floorplan

  


Manual Floor planning

  


- For large designs, manual floor planning may be necessary

Routing congestion
Xilinx Virtex 7 (Vivado)

Simulation

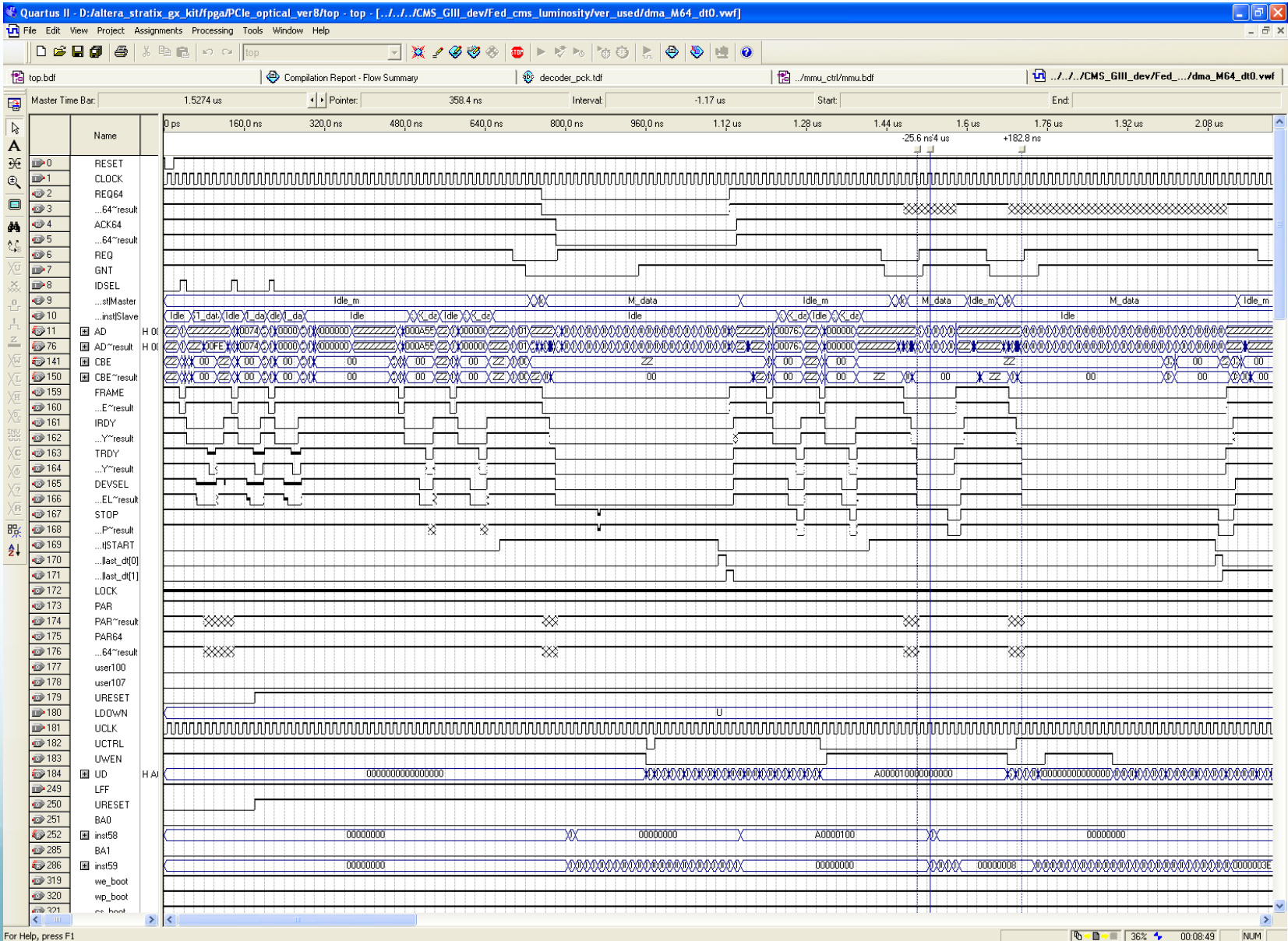


Embedded Logic Analyzers

 

A great tool for debugging your design

FPGA applications in the Trigger & DAQ domain

First-Level Trigger at Collider

 

Timing: beam crossings

LHC: 25 ns





detector

Coarse grain data

Full data
(fine grain)

Delay
FIFO

  

Fixed Latency
(= processing time
of the first
level trigger)

N beam crossings


Trigger decision YES / NO
(for every beam crossing)

De-
randomizer
FIFO




Latency should be short
In order to limit the length
of the delay FIFOS

Pipelined Logic

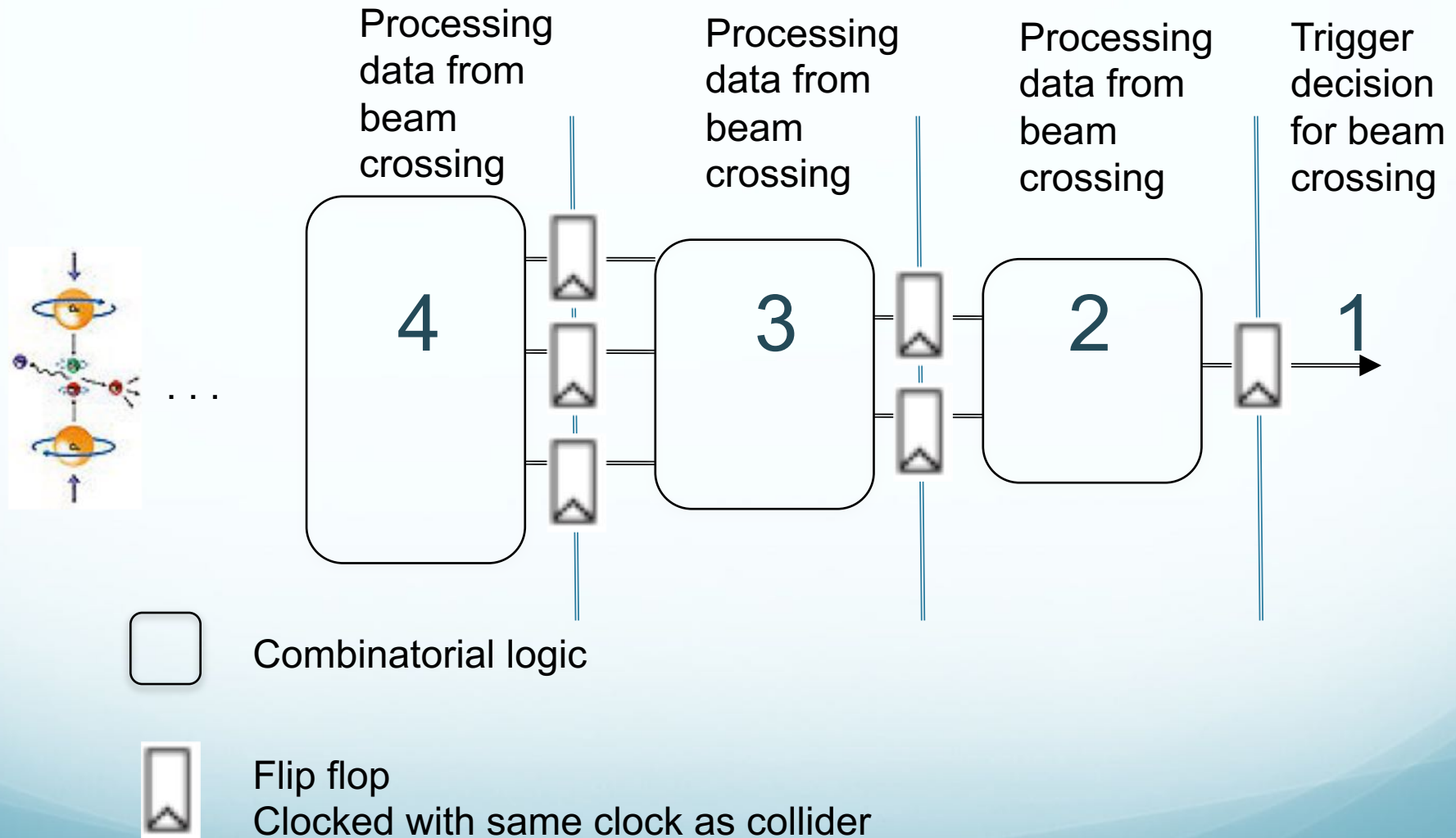

Pipelined Logic – a clock cycle later

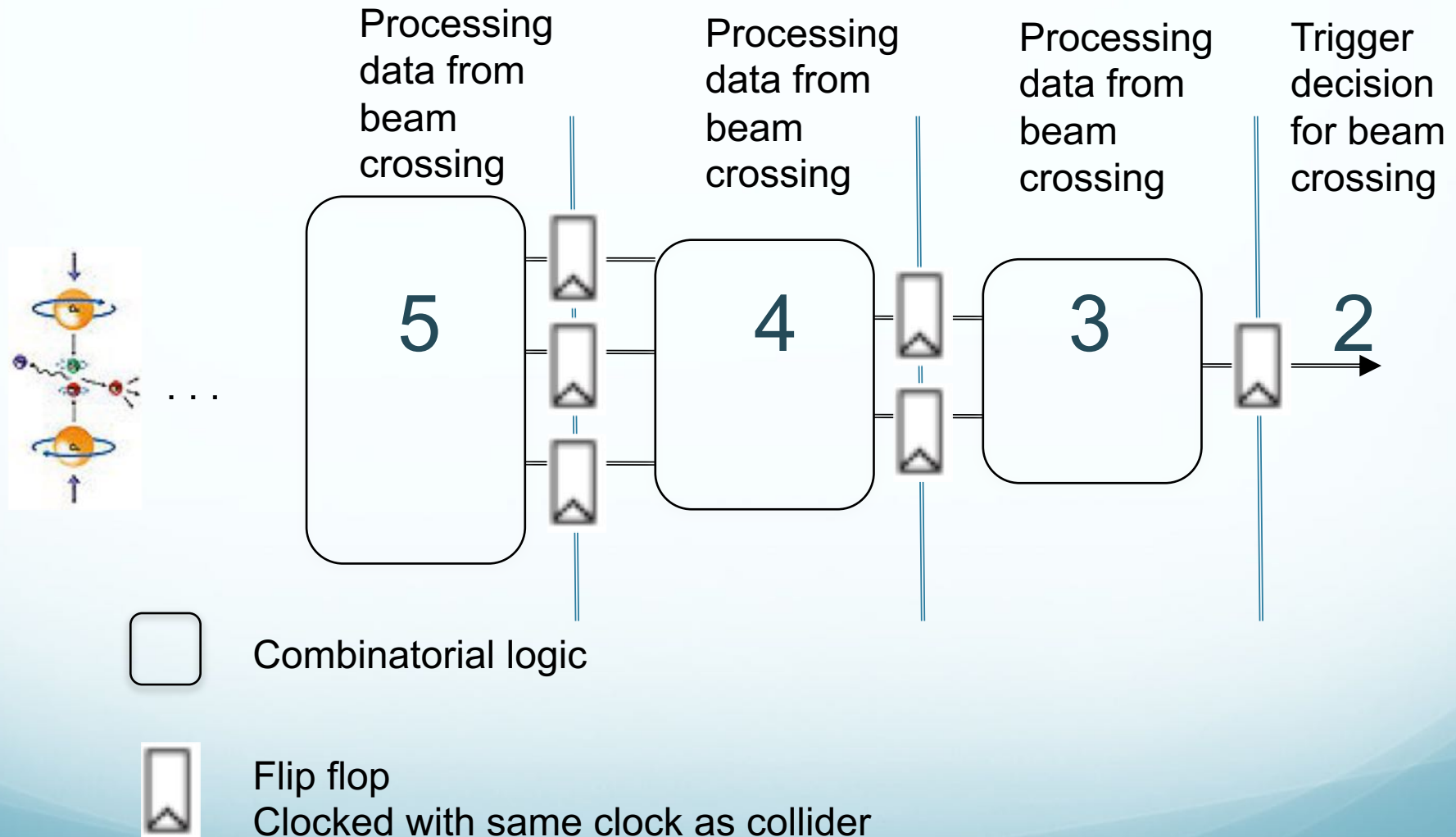

Why are FPGAs ideal for First-Level Triggers ?

- They are fast
 - Much faster than discrete electronics (shorter connections)
- Many inputs
 - Data from many parts of the detector has to be combined
- All operations are performed in parallel
 - Can build pipelined logic
- They can be re-programmed
 - Trigger algorithms can be optimized




Low latency

High performance

Trigger algorithms implemented in FPGAs

- Trigger
 - Peak finding
 - Pattern Recognition
 - Track Finding
 - Clustering / Energy summing
 - Topological Algorithms (invariant mass)
 - Vertex Finding
 - Particle flow (reconstruction jets, etc. from individual particle tracks)
 - Inference with Neural Networks
 - Many more ...
- Trigger Control system
 - Fast (busy) signal merging & monitoring
 - Generation of random triggers
 - Generation of calibration sequences
 - Automatic recovery sequences
 - Monitoring (dead times, rates, ...)

Neural Networks in Trigger

 


By Glosser.ca - Own work, Derivative of File:Artificial neural network.svg, CC BY-SA 3.0, <https://commons.wikimedia.org/w/index.php?curid=24913461>

- Principle
 - Node is assigned a value based on the weighted sum of nodes in the previous layer
 - Maps well to DSP resources in FPGA (multiplier + adder)
- Applications:
 - Jet classification
 - Assignment of transverse momentum based on many measurements
 - Topological trigger
 - ...
- Tools
 - Many commercial tools
 - hls4ml (optimized for latency)
 - Firmware generation from high-level model using Vivado HLS




CMS Global Muon Trigger

 


- VME card (9U)
 - Input: ~ 1000 bits @ 40 and 80 MHz
 - Output: ~ 50 bits @ 80MHz
 - Processing time: 250 ns
 - Pipelined logic
one new result every 25 ns
 - 10 Xilinx Virtex-II FPGAs
 - up to 500 user I/Os per chip
 - Up to 25000 LUTs per chip used
 - Up to 96 x 18kbit RAM used
 - In use in the CMS trigger 2008-2015
- The CMS Global Muon trigger received 16 muon candidates from the three muon systems of CMS
 - It merged different measurements for the same muon and found the best 4 over-all muon candidates

CMS Global Muon Trigger main FPGA

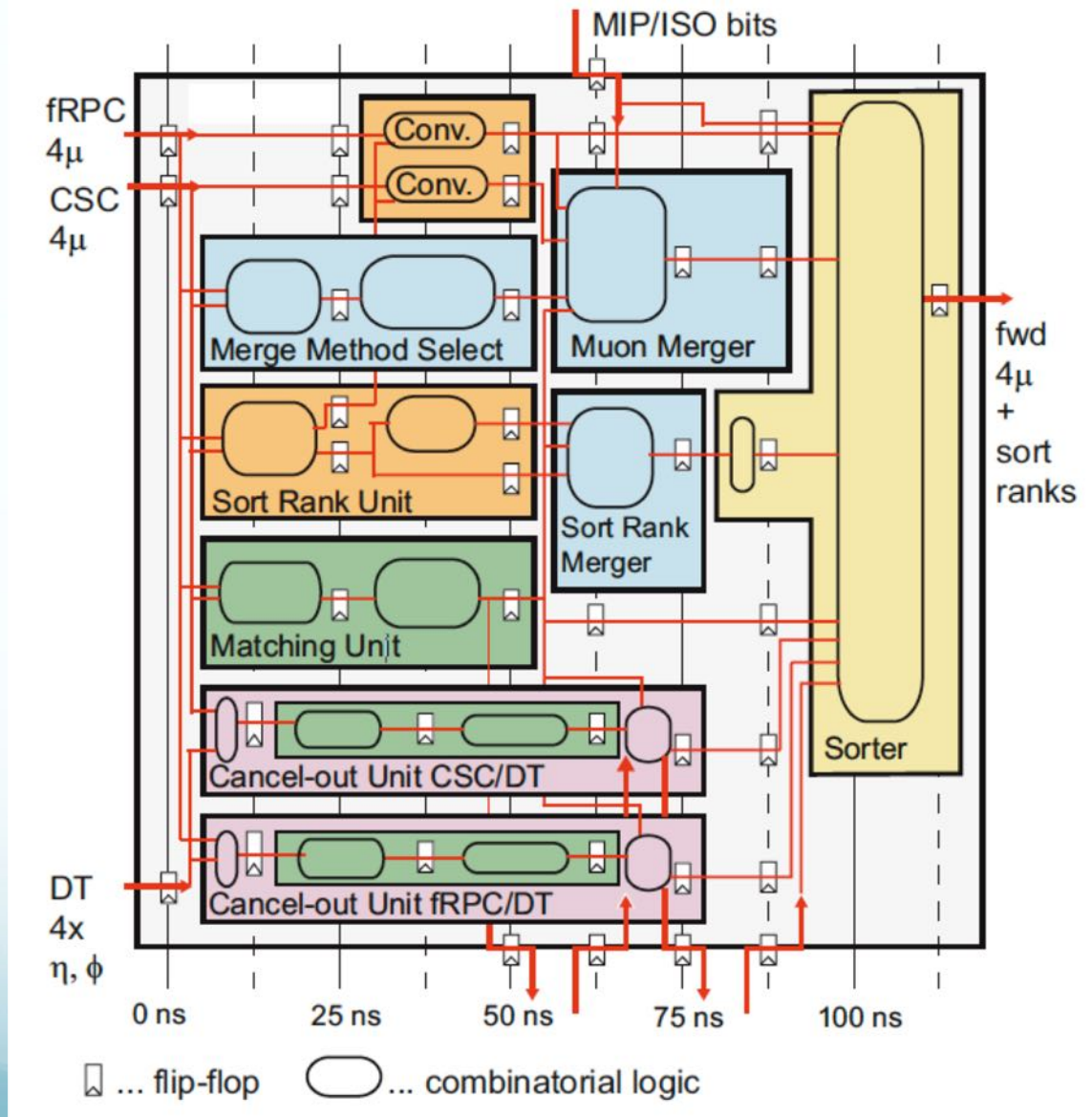

 μ TCA board for Run 2&3 CMS trigger based on Virtex 7



MP7, Imperial College



Virtex 7 with 690k logic cells
80 x 10 Gb/s transceivers bi-directional
72 of them as optical links on front panel
0.75 + 0.75 Tb/s
Being used in the CMS trigger since 2015

Input/output:
up to 14k bits per 40 MHz clock

Same board used for different functions
(different gateway)
Separation of framework + algorithm fw

CMS ATCA Trigger boards for HL-LHC (2029+)

120 x
25 Gb/s

  

Serenity, UK

APX, US


- Few types of generic boards, ATCA standard
- Xilinx Virtex/Kintex Ultrascale+ FPGAs (> 3 million logic cells / FPGA)
- 25-28 Gb/s optical links
- SoC FPGAs used for board control (on some boards)
- Advanced firmware algorithms
 - Vertex finding
 - Particle flow
 - Neural network classifiers

FPGAs in Data Acquisition

- Frontend Electronics
 - Pedestal subtraction
 - Zero suppression
 - Compression
 - Buffering ...
- Custom data links
 - E.g. SLINK-64 over copper
 - Several serial LVDS links in parallel
 - Up to 400 MB/s
 - SLINK/SLINK-express over optical
- Interface from custom hardware to commercial electronics
 - PCI/PCIe, VME bus, Myrinet, 10/40/100 Gb/s Ethernet etc.

C-RORC (Alice) / Robin NP (ATLAS) for Run-2

Xilinx Virtex-6 FPGA

 


Commercial PCIe link out (DMA to host memory)

CMS Front-end Readout Link (Run-1)


- SLINK Sender Mezzanine Card: 400 MB / s
 - 1 FPGA (Altera)
 - CRC check
 - Automatic link test

Commercial Myrinet Network Interface Card on internal PCI bus

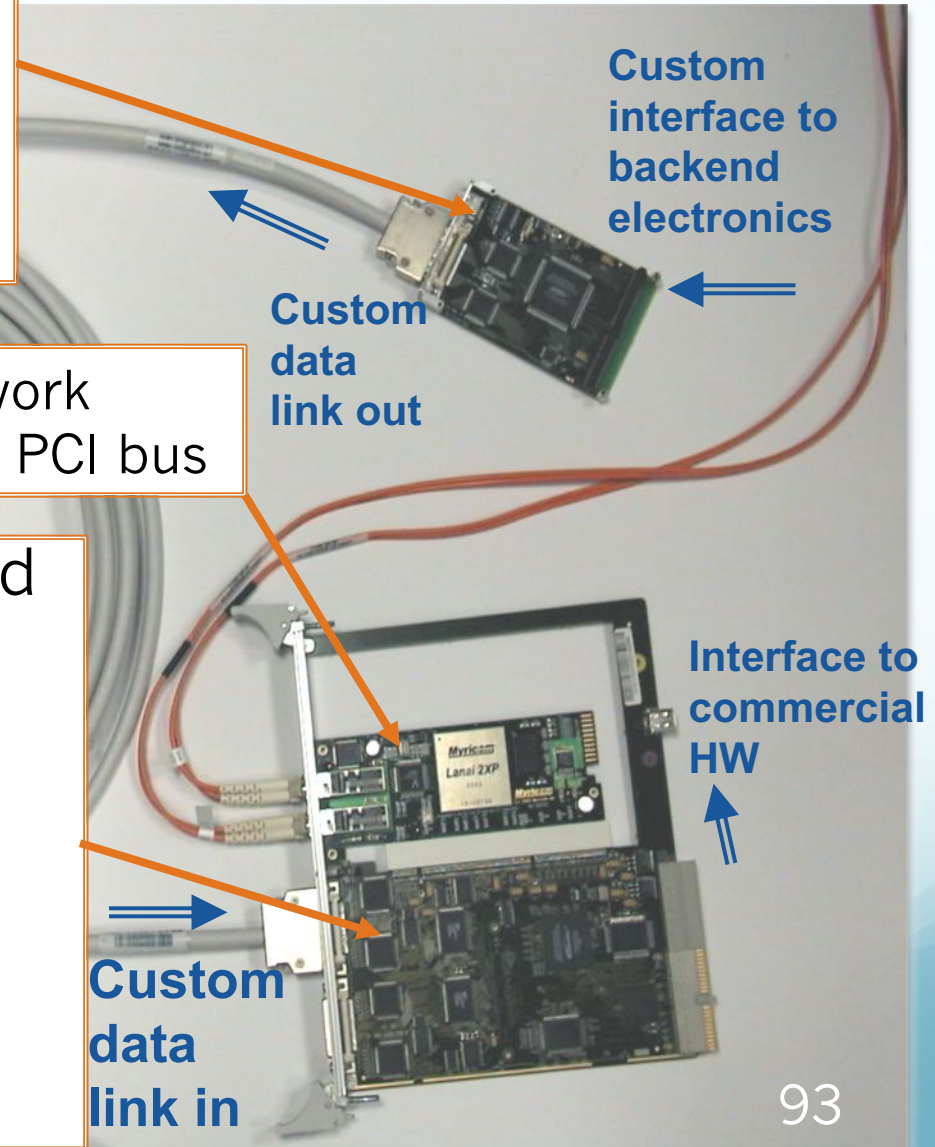- Front-end Readout Link Card
 - 1 main FPGA (Altera)
 - 1 FPGA as PCI interface
 - Custom Compact PCI card
 - Receives 1 or 2 SLINK64
 - 2nd CRC check
 - Monitoring, Histogramming
 - Event spy



 CMS Readout Link for Run-2&3 in use since 2015



10 Gb/s TCP/IP

Myrinet NIC replaced by custom-built card ("FEROL")

Cost effective solution (need many boards)
Rather inexpensive FPGA + commercial chip to combine 3 Gb/s links to 10 Gb/s

SLINK-64 input
LVDS / copper

FEROL (Front End Readout Optical Link)

Input: 1x or 2x SLINK (copper)
1x or 2x 5Gb/s optical
1x 10Gb/s optical

Output: 10 Gb/s Ethernet optical
TCP/IP sender in FPGA

CMS Readout Link for Run-2&3 in use since 2015

Commercial data link out

10 Gb/s TCP/IP


10 Gb/s SLINK Express

5 Gb/s SLINK Express

5 Gb/s SLINK Express

Custom data link in

SLINK-64 input
LVDS / copper

 

FEROL (Front End Readout Optical Link)

Input: 1x or 2x SLINK (copper)
1x or 2x 5Gb/s optical
1x 10Gb/s optical

Output: 10 Gb/s Ethernet optical
TCP/IP sender in FPGA

PCIe40 – LHCb and ALICE Run-3


Custom data link in



Clock, control



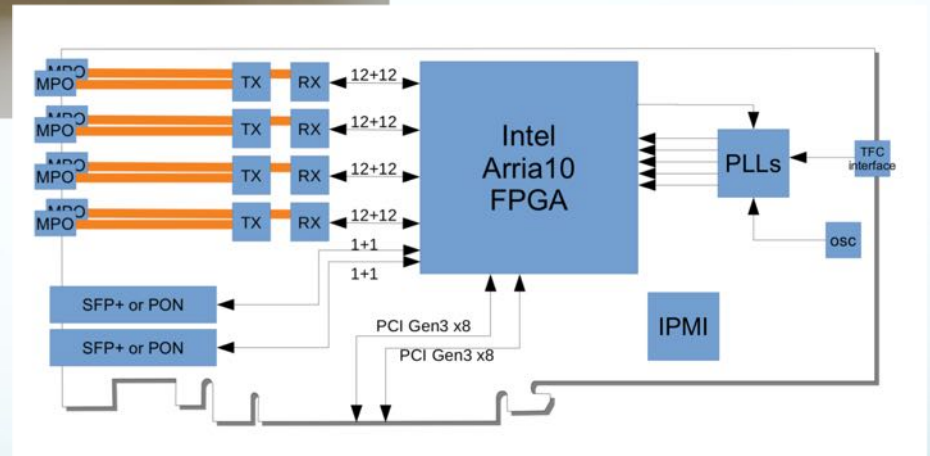Direct Memory Access transfer to host memory



- 48 bidirectional links running at up to 10 Gbits/s each (minipods)
- 2 bidirectional links running at up to 10 Gbits/s devoted to time distribution (can use SFP+ or 10G PON devices)
- Sustained 112 Gbits/s interface with CPU through PCIe

CMS DTH (DAQ and Timing Hub) for HL-LHC (2029+)

Custom data link in



Commercial data link (TCP/IP) out



Clock & control uplink



Main board



Rear transition module

Zynq SoC FPGA for control

DTH prototype 2

Clock & control distribution via backplane

- **ATCA** board using Xilinx Virtex Ultrascale + FPGAs
- One or two DAQ units per board
 - Up to 24 inputs at 25 Gb/s
 - **5x 100 Gb/s** Ethernet to commercial network
 - TCP/IP in FPGA
- Board contains switch for control network



FPGAs in other domains

- Machine Learning Inferencing
- Automotive Driver Assist (Image Processing)
- 5G Wireless
- Medical imaging
- Speech recognition
- Cryptography
- Bioinformatics (Genome sequencing)
- Aerospace / Defense
- (Bitcoin mining)
- ASIC Prototyping
- Compute accelerators
 - Accelerator cards




- Server processors w. FPGA
- Financial
- Video transcoding
- ...

Lab Session 5: Programming an FPGA

 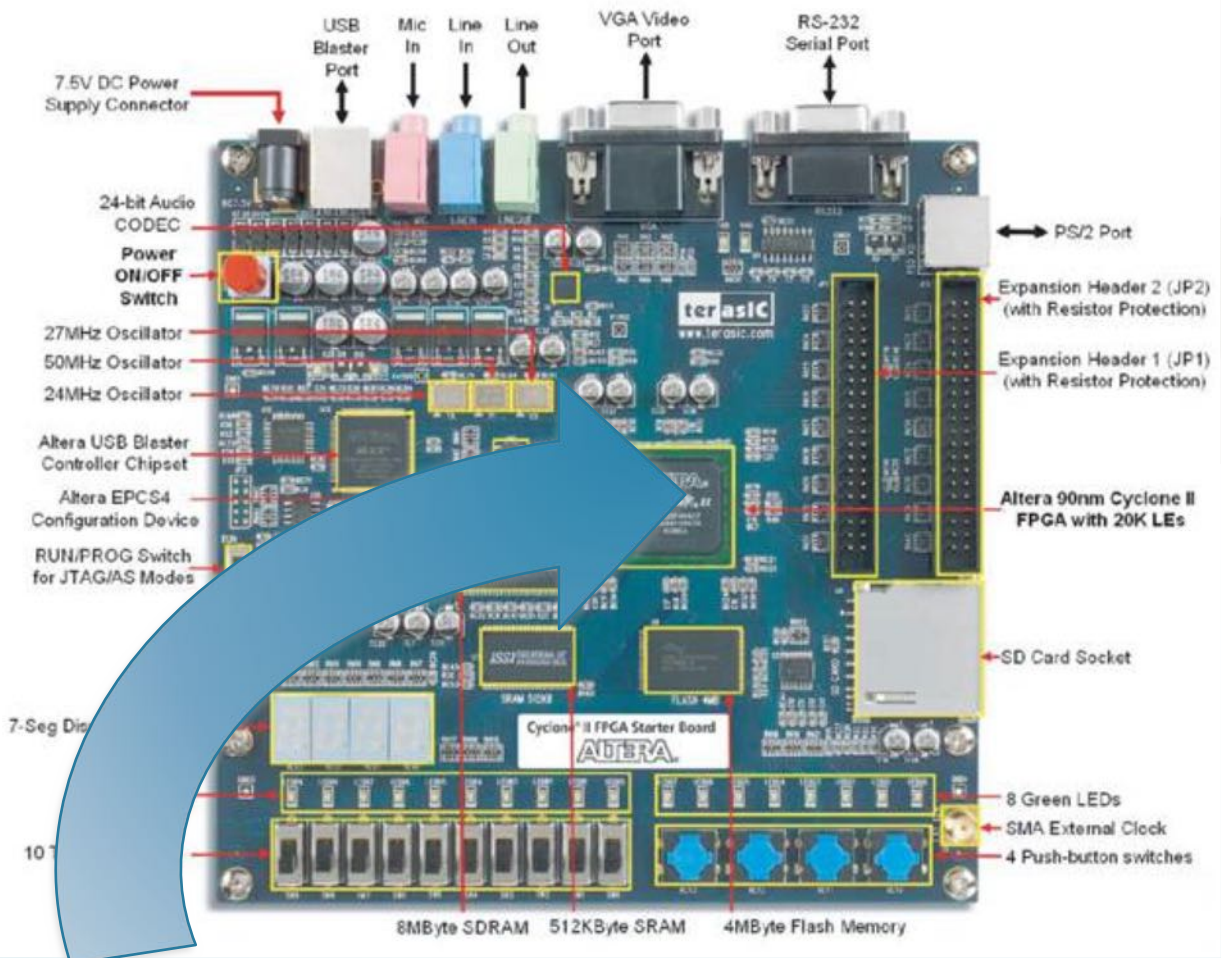

You are going to design the digital electronics inside this FPGA !

Lab Session 13: System-on-a-chip FPGA

 

PYNQ-Z2 board
Xilinx Zynq w. dual-core ARM

Design the digital electronics and software in this SoC FPGA!

Thank you

Acknowledgement

- Parts of this lecture are based on material by Clive Maxfield, author of several books on FPGAs. Many thanks for his kind permission to use his material!

Re-use

- Re-use of the material is permitted only with the written authorization of both Hannes Sakulin (Hannes.Sakulin@cern.ch) and Clive Maxfield.

Reference Material

Top-of-the-line Xilinx devices

Device Name	VU3P	VU5P	VU7P	VU9P	VU11P	VU13P	VU27P	VU29P	VU31P	VU33P	VU35P	VU37P	
System Logic Cells (K)	862	1,314	1,724	2,586	2,835	3,780	2,835	3,780	962	962	1,907	2,852	
CLB Flip-Flops (K)	788	1,201	1,576	2,364	2,592	3,456	2,592	3,456	879	879	1,743	2,607	
CLB LUTs (K)	394	601	788	1,182	1,296	1,728	1,296	1,728	440	440	872	1,304	
Max. Dist. RAM (Mb)	12.0	18.3	24.1	36.1	36.2	48.3	36.2	48.3	12.5	12.5	24.6	36.7	
Total Block RAM (Mb)	25.3	36.0	50.6	75.9	70.9	94.5	70.9	94.5	23.6	23.6	47.3	70.9	
UltraRAM (Mb)	90.0	132.2	180.0	270.0	270.0	360.0	270.0	360.0	90.0	90.0	180.0	270.0	
HBM DRAM (GB)	–	–	–	–	–	–	–	–	4	8	8	8	
HBM AXI Interfaces	–	–	–	–	–	–	–	–	32	32	32	32	
Clock Mgmt Tiles (CMTs)	10	20	20	30	12	16	16	16	4	4	8	12	
DSP Slices	2,280	3,474	4,560	6,840	9,216	12,288	9,216	12,288	2,880	2,880	5,952	9,024	
Peak INT8 DSP (TOP/s)	7.1	10.8	14.2	21.3	28.7	38.3	28.7	38.3	8.9	8.9	18.6	28.1	
PCIe® Gen3 x16	2	4	4	6	3	4	1	1	0	0	1	2	
PCIe Gen3 x16/Gen4 x8 / CCIX ⁽¹⁾	–	–	–	–	–	–	–	–	4	4	4	4	
150G Interlaken	3	4	6	9	6	8	6	8	0	0	2	4	
100G Ethernet w/ KR4 RS-FEC	3	4	6	9	9	12	11	15	2	2	5	8	
Max. Single-Ended HP I/Os	520	832	832	832	624	832	520	676	208	208	416	624	
GTY 32.75Gb/s Transceivers	40	80	80	120	96	128	32	32	32	32	64	96	
GTM 58Gb/s PAM4 Transceivers							32	48					
100G / 50G KP4 FEC							16 / 32	24 / 48					
Extended ⁽²⁾	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3	-1 -2 -2L -3
Industrial	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	-1 -2	–	–	–	–	
Footprint ^(3,4,5)	Dim. (mm)	HP I/O, GTY					HP I/O, GTY, GTM		HP I/O, GTY				
Footprint compatible with 20nm UltraScale Devices with same footprint identifier	C1517	40x40	520, 40										
	F1924 ⁽⁶⁾	45x45				624, 64							
	A2104	47.5x47.5		832, 52	832, 52	832, 52							
		52.5x52.5 ⁽⁷⁾					832, 52						
	B2104	47.5x47.5		702, 76	702, 76	702, 76	572, 76						
		52.5x52.5 ⁽⁷⁾					702, 76						
	C2104	47.5x47.5		416, 80	416, 80	416, 104	416, 96						
		52.5x52.5 ⁽⁷⁾					416, 104						
	D2104	47.5x47.5				676, 76	572, 76						
		52.5x52.5 ⁽⁷⁾					676, 76	676, 16, 30	676, 16, 30				
	A2577	52.5x52.5			448, 120	448, 96	448, 128	448, 32, 48	448, 32, 48				
	H1924	45x45								208, 32			
H2104	47.5x47.5									208, 32	416, 64		
H2892	55x55										416, 64	624, 96	



INTEL® STRATIX® 10 GX/SX PRODUCT TABLE

PRODUCT LINE	GX 400 SX 400	GX 650 SX 650	GX 850 SX 850	GX 1100 SX 1100	GX 1650 SX 1650	GX 2100 SX 2100	GX 2500 SX 2500	GX 2800 SX 2800	GX 4500 SX 4500	GX 5500 SX 5500
Logic elements (LEs) ¹	378,000	612,000	841,000	1,092,000	1,624,000	2,005,000	2,422,000	2,753,000	4,463,000	5,510,000
Adaptive logic modules (ALMs)	128,160	207,360	284,960	370,080	550,540	679,680	821,150	933,120	1,512,820	1,867,680
ALM registers	512,640	829,440	1,139,840	1,480,320	2,202,160	2,718,720	3,284,600	3,732,480	6,051,280	7,470,720
Hyper-Registers from Intel® HyperFlex™ FPGA architecture	Millions of Hyper-Registers distributed throughout the monolithic FPGA fabric									
Programmable clock trees synthesizable	Hundreds of synthesizable clock trees									
M20K memory blocks	1,537	2,489	3,477	4,401	5,851	6,501	9,963	11,721	7,033	7,033
M20K memory size (Mb)	30	49	68	86	114	127	195	229	137	137
MLAB memory size (Mb)	2	3	4	6	8	11	13	15	23	29
Variable-precision digital signal processing (DSP) blocks	648	1,152	2,016	2,520	3,145	3,744	5,011	5,760	1,980	1,980
18 x 19 multipliers	1,296	2,304	4,032	5,040	6,290	7,488	10,022	11,520	3,960	3,960
Peak fixed-point performance (TMACS) ²	2.6	4.6	8.1	10.1	12.6	15.0	20.0	23.0	7.9	7.9
Peak floating-point performance (TFLOPS) ³	1.0	1.8	3.2	4.0	5.0	6.0	8.0	9.2	3.2	3.2
Secure device manager	AES-256/SHA-256 bitstream encryption/authentication, physically unclonable function (PUF), ECDSA 256/384 boot code authentication, side channel attack protection									
Hard processor system ⁴	Quad-core 64 bit ARM® Cortex®-A53 up to 1.5 GHz with 32 KB I/D cache, NEON® coprocessor, 1 MB L2 cache, direct memory access (DMA), system memory management unit, cache coherency unit, hard memory controllers, USB 2.0 x2, 1G EMAC x3, UART x2, SPI x4, I ² C x5, general-purpose timers x7, watchdog timer x4									
Maximum user I/O pins	392	400	736	736	704	704	1160	1160	1640	1640
Maximum LVDS pairs 1.6 Gbps (RX or TX)	192	192	360	360	336	336	576	576	816	816
Total full duplex transceiver count	24	48	48	48	96	96	96	96	24	24
GXT full duplex transceiver count (up to 30 Gbps)	16	32	32	32	64	64	64	64	16	16
GX full duplex transceiver count (up to 17.4 Gbps)	8	16	16	16	32	32	32	32	8	8
PCI Express® (PCIe®) hard intellectual property (IP) blocks (Gen3 x16)	1	2	2	2	4	4	4	4	1	1
Memory devices supported	DDR4, DDR3, DDR2, DDR, QDR II, QDR II+, RLDRAM II, RLDRAM 3, HMC, MoSys									
Package Options and I/O Pins: General-Purpose I/O (GPIO) Count, High-Voltage I/O Count, LVDS Pairs, and Transceiver Count ⁵										
F1152 pin (35 mm x 35 mm, 1.0 mm pitch)	392,8,192,24	392,8,192,24	-	-	-	-	-	-	-	-
F1760 pin (42.5 mm x 42.5 mm, 1.0 mm pitch)	-	400,16,192,48	-	-	-	-	-	-	-	-
F1760 pin (42.5 mm x 42.5 mm, 1.0 mm pitch)	-	-	688,16,336,48	688,16,336,48	688,16,336,48	688,16,336,48	688,16,336,48	688,16,336,48	-	-
F2112 pin (47.5 mm x 47.5 mm, 1.0 mm pitch)	-	-	736,16,360,48	736,16,360,48	-	-	-	-	-	-
F2397 pin (50 mm x 50 mm, 1.0 mm pitch)	-	-	-	-	704,32,336,96	704,32,336,96	704,32,336,96	704,32,336,96	-	-
F2912 pin (55 mm x 55 mm, 1.0 mm pitch)	-	-	-	-	-	-	1160,8,576,24	1160,8,576,24	1640,8,816,24	1640,8,816,24



INTEL® STRATIX® 10 TX PRODUCT TABLE


PRODUCT LINE		TX 1650		TX 2100		TX 2500			TX 2800		
Resources	Logic elements (LEs) ¹	1,679,000		2,073,000		2,422,000			2,753,000		
	Adaptive logic modules (ALMs)	569,200		702,720		821,150			933,120		
	ALM registers	2,276,800		2,810,880		3,284,600			3,732,480		
	Hyper-Registers from Intel® Hyperflex™ FPGA architecture	Millions of Hyper-Registers distributed throughout the monolithic FPGA fabric									
	Programmable clock trees synthesizable	Hundreds of synthesizable clock trees									
	eSRAM memory blocks	2		2		-			-		
	eSRAM memory size (Mb)	90		90		-			-		
	M20K memory blocks	6,162		6,847		9,963			11,721		
	M20K memory size (Mb)	120		134		195			229		
	MLAB memory size (Mb)	9		11		13			15		
	Variable-precision digital signal processing (DSP) blocks	3,326		3,960		5,011			5,760		
	18 x 19 multipliers	6,652		7,920		10,022			11,520		
	Peak fixed-point performance (TMACS) ²	13.3		15.8		20.0			23.0		
Peak floating-point performance (TFLOPS) ³	5.3		6.3		8.0			9.2			
I/O and Architectural Features	Secure device manager	AES-256/SHA-256 bitstream encryption/authentication, physically unclonable function (PUF), ECDSA 256/384 boot code authentication, side channel attack protection									
	Hard processor system	Quad-core 64-bit ARM® Cortex®-A53 up to 1.5 GHz with 32KB I/D cache, NEON® coprocessor, 1 MB L2 Cache, direct memory access (DMA), system memory management unit, cache coherency unit, hard memory controllers, USB 2.0 x2, 1G EMAC x3, UART x2, SPI x4, I²C x5, general purpose timers x7, watchdog timer x4									
		-		-		Yes			Yes		
	Maximum user I/O pins	544	440	544	440	544	440	296	544	440	296
	Maximum LVDS pairs 1.6 Gbps (RX or TX)	264	216	264	216	264	216	144	264	216	144
	Total full duplex transceiver count	72	96	72	96	72	96	144	72	96	144
	GXE transceiver count - PAM-4 (up to 58 Gbps) or NRZ (up to 30 Gbps)	12 PAM-4 24 NRZ	36 PAM-4 72 NRZ	12 PAM-4 24 NRZ	36 PAM-4 72 NRZ	12 PAM-4 24 NRZ	36 PAM-4 72 NRZ	60 PAM-4 120 NRZ	12 PAM-4 24 NRZ	36 PAM-4 72 NRZ	60 PAM-4 120 NRZ
	GXT transceiver count - NRZ (up to 28.3 Gbps)	32	16	32	16	32	16	16	32	16	16
	GX transceiver count - NRZ (up to 17.4 Gbps)	16	8	16	8	16	8	8	16	8	8
	PCI Express* (PCIe*) hard intellectual property (IP) blocks (Gen3 x16)	2	1	2	1	2	1	1	2	1	1
	100G Ethernet MAC (no FEC) hard IP blocks	2	1	2	1	2	1	1	2	1	1
	100G Ethernet MAC + FEC hard IP blocks	4	12	4	12	4	12	20	4	12	20
	Memory devices supported	DDR4, DDR3, DDR2, DDR, QDR II, QDR II+, RDRAM II, RDRAM 3, HMC, MoSys									
Package Options and I/O Pins: General-Purpose I/O (GPIO) Count, High-Voltage I/O count, LVDS pairs, GXE (E-Tile) Transceiver Count, and GXT+GX (H-Tile) Transceiver Count ⁴											
F2112 pin (47.5 mm x 47.5 mm, 1.0 mm pitch)	544,16,264,24,48		544,16,264,24,48		544,16,264,24,48			544,16,264,24,48			
F2397 pin (50 mm x 50 mm, 1.0 mm pitch)	440,8,216,72,24		440,8,216,72,24		440,8,216,72,24			440,8,216,72,24			
F2912 pin (55 mm x 55 mm, 1.0 mm pitch)	-		-		296,8,144,120,24			296,8,144,120,24			



INTEL® STRATIX® 10 MX (DRAM SYSTEM-IN-PACKAGE) PRODUCT TABLE


PRODUCT LINE		MX 1100	MX 1650	MX 1650	MX 1650	MX 2100	MX 2100	MX 2100	MX 2100	
Resources	Logic elements (LEs) ¹	1,092,000	1,679,000	1,679,000	1,679,000	2,073,000	2,073,000	2,073,000	2,073,000	
	Adaptive logic modules (ALMs)	370,080	569,200	569,200	569,200	702,720	702,720	702,720	702,720	
	ALM registers	1,480,320	2,276,800	2,276,800	2,276,800	2,810,880	2,810,880	2,810,880	2,810,880	
	Hyper-Registers from Intel® Hyperflex™ FPGA architecture	Millions of Hyper-Registers distributed throughout the monolithic FPGA fabric								
	Programmable clock trees synthesizable	Hundreds of synthesizable clock trees								
	HBM2 high-bandwidth DRAM memory (GBytes)	3.25	8	16	8	8	8	16	8	
	eSRAM memory blocks	1	2	2	2	2	2	2	2	
	eSRAM memory size (Mb)	45	90	90	90	90	90	90	90	
	M20K memory blocks	4,401	6,162	6,162	6,162	6,847	6,847	6,847	6,847	
	M20K memory size (Mb)	86	120	120	120	134	134	134	134	
	MLAB memory size (Mb)	6	9	9	9	11	11	11	11	
	Variable-precision digital signal processing (DSP) blocks	2,520	3,326	3,326	3,326	3,960	3,960	3,960	3,960	
	18 x 19 multipliers	5,040	6,652	6,652	6,652	7,920	7,920	7,920	7,920	
	Peak fixed-point performance (TMACS) ²	10.1	13.3	13.3	13.3	15.8	15.8	15.8	15.8	
Peak floating-point performance (TFLOPS) ³	4.0	5.3	5.3	5.3	6.3	6.3	6.3	6.3		
Secure device manager	AES-256/SHA-256 bitstream encryption/authentication, physically unclonable function (PUF), ECDSA 256/384 boot code authentication, side channel attack protection									
Hard processor system	Quad-core 64 bit ARM® Cortex®-A53 up to 1.5 GHz with 32 KB I/D cache, NEON® coprocessor, 1 MB L2 cache, direct memory access (DMA), system memory management unit, cache coherency unit, hard memory controllers, USB 2.0 x2, 1G EMAC x3, UART x2, serial peripheral interface (SPI) x4, I ² C x5, general-purpose timers x7, watchdog timer x4									
	Yes	-	-	-	-	-	-	-	-	
Maximum user I/O pins	448	656	656	584	640	656	656	584		
LVDS pairs 1.6 Gbps (RX or TX)	216	312	312	288	312	312	312	288		
Total full duplex transceiver count	48	96	96	96	48	96	96	96		
GXE transceiver count - PAM4 (up to 58 Gbps) or NRZ (up to 30 Gbps)	0	0	0	72	0	0	0	72		
GXT transceiver count - NRZ (up to 28.3 Gbps)	32	64	64	16	32	64	64	16		
GX transceiver count - NRZ (up to 17.4 Gbps)	16	32	32	8	16	32	32	8		
PCI Express® (PCIe®) hard intellectual property (IP) blocks (Gen3 x16)	2	4	4	1	2	4	4	1		
100G Ethernet MAC (no FEC) hard IP blocks	2	4	4	1	2	4	4	1		
100G Ethernet MAC + FEC hard IP blocks	0	0	0	12	0	0	0	12		
Memory devices supported	DDR4, DDR3, DDR2, DDR, QDR II, QDR II+, RLDRAM II, RLDRAM 3, HMC, MoSys									
Package Options and I/O Pins: General-Purpose I/O (GPIO) Count, High-Voltage I/O Count, LVDS Pairs, and Transceiver Count ^{4,5}										
F1760 pin (42.5 mm x 42.5 mm, 1.0 mm pitch)	448,16,216,48	-	-	-	-	-	-	-	-	
F2597 pin (52.5 mm x 52.5 mm, 1.0mm pitch)	-	656, 32, 312, 96	656, 32, 312, 96	-	640, 16, 312, 48	656, 32, 312, 96	656, 32, 312, 96	-	-	
F2912 pin (55 mm x 55 mm, 1.0 mm pitch)	-	-	-	584, 8, 288, 96	-	-	-	584, 8, 288, 96	-	

FPGA count in CMS trigger for HL-LHC

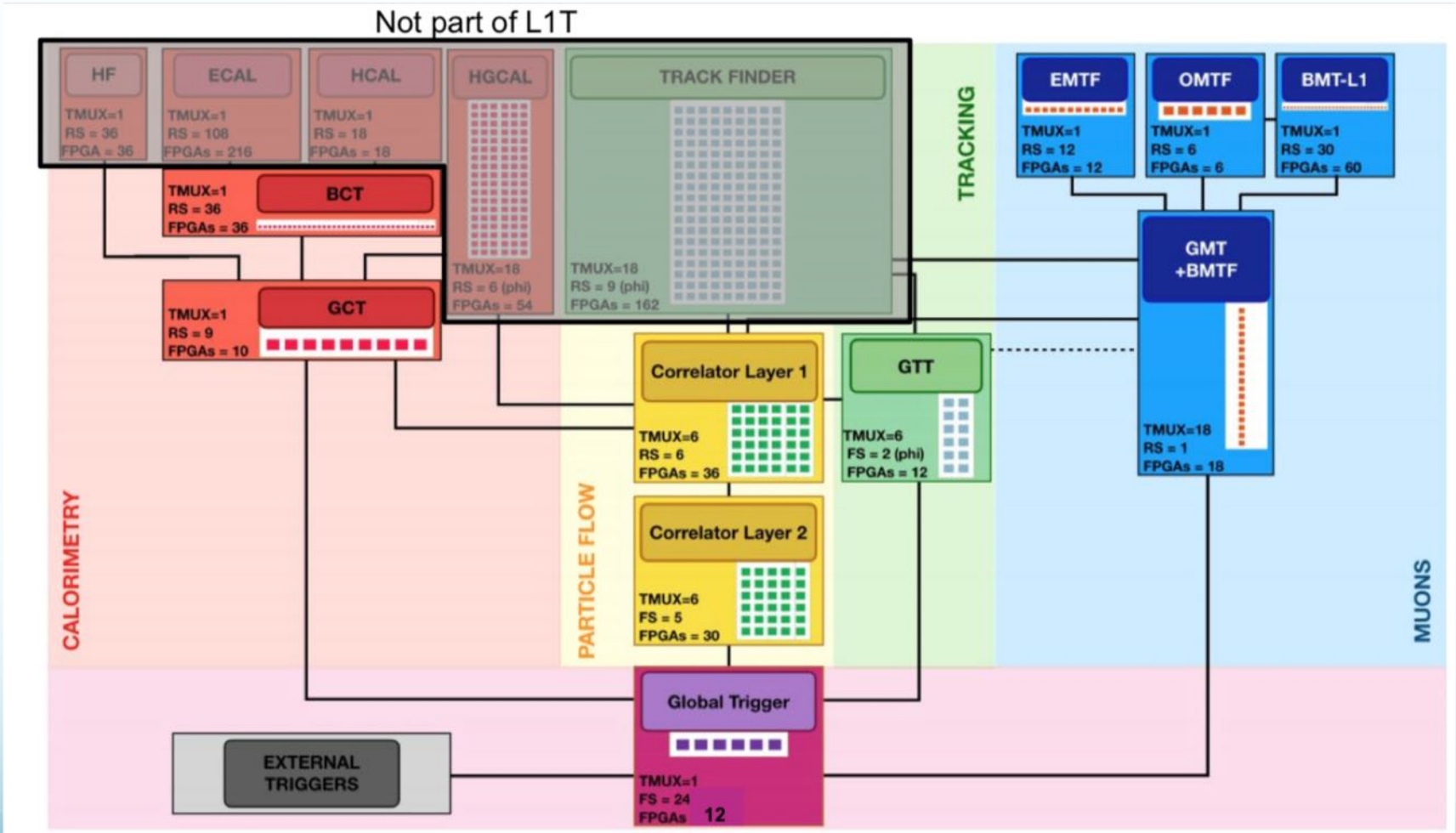



History

Long long time ago ...

 

Simple Programmable Logic Devices (sPLDs)

a) Programmable Read Only Memory (PROMs)

  


Late 60's

Unprogrammed PROM (Fixed AND Array, Programmable OR Array)

Simple Programmable Logic Devices (sPLDs)

b) Programmable Logic Arrays (PLAs)


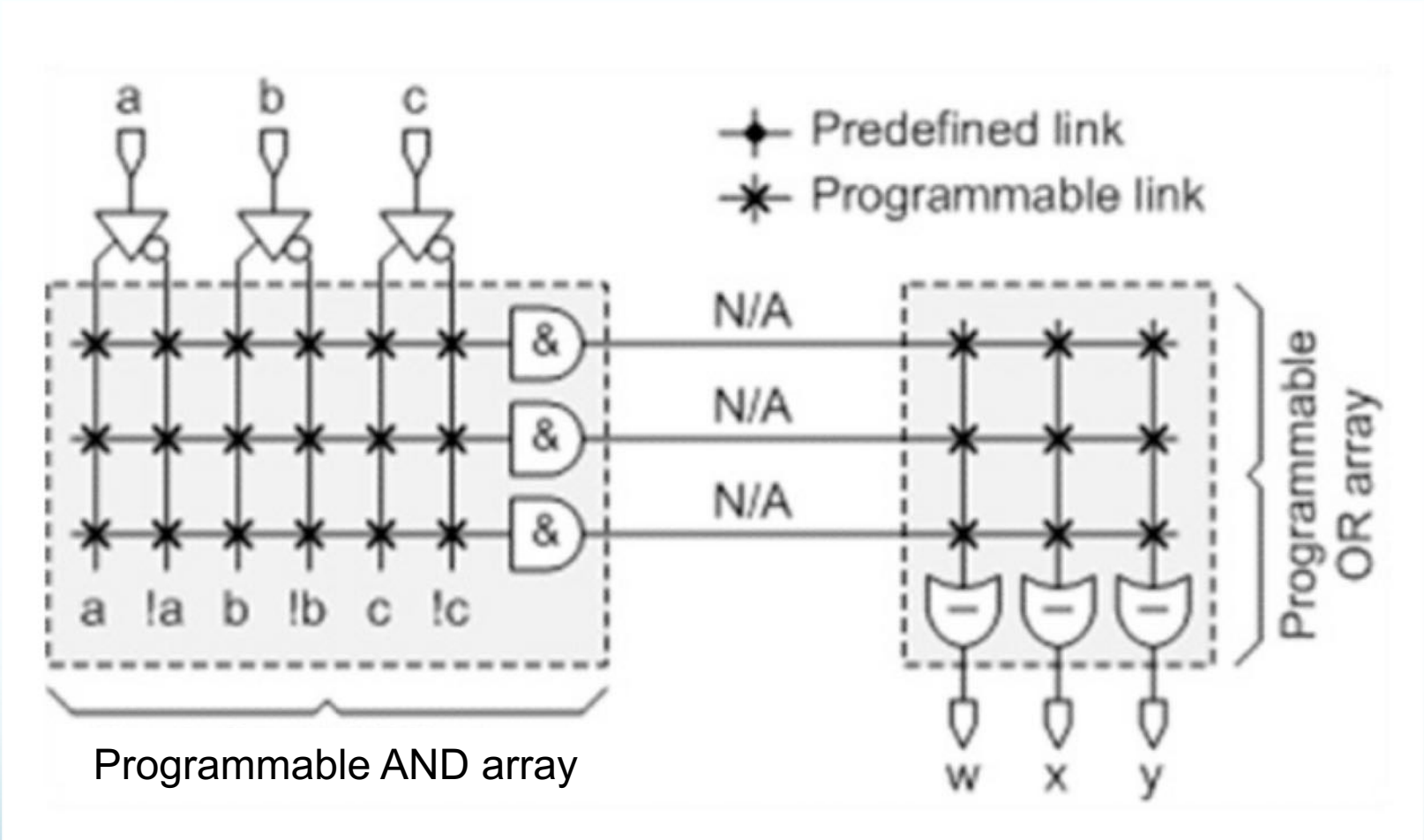


Unprogrammed PLA (Programmable AND and OR Arrays)

Most flexible
but slower


Simple Programmable Logic Devices (sPLDs)

c) Programmable Array Logic (PAL)

 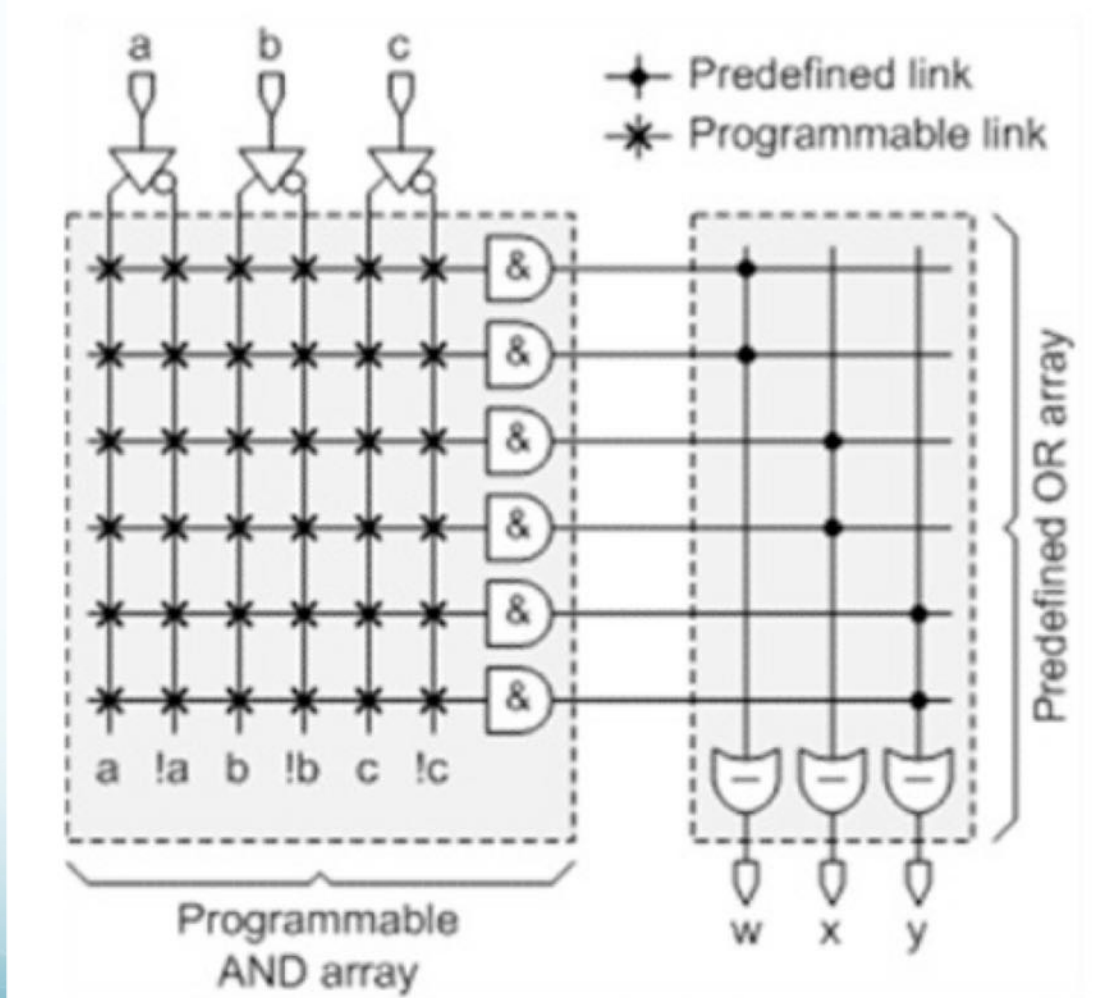


Unprogrammed PAL (Programmable AND Array, Fixed OR Array)

Complex PLDs (CPLDs)

 


Coarse grained
100's of blocks, restrictive structure
(EE)PROM based

FPGAs ...

 


Timing

Design Considerations (SRAM Config.)

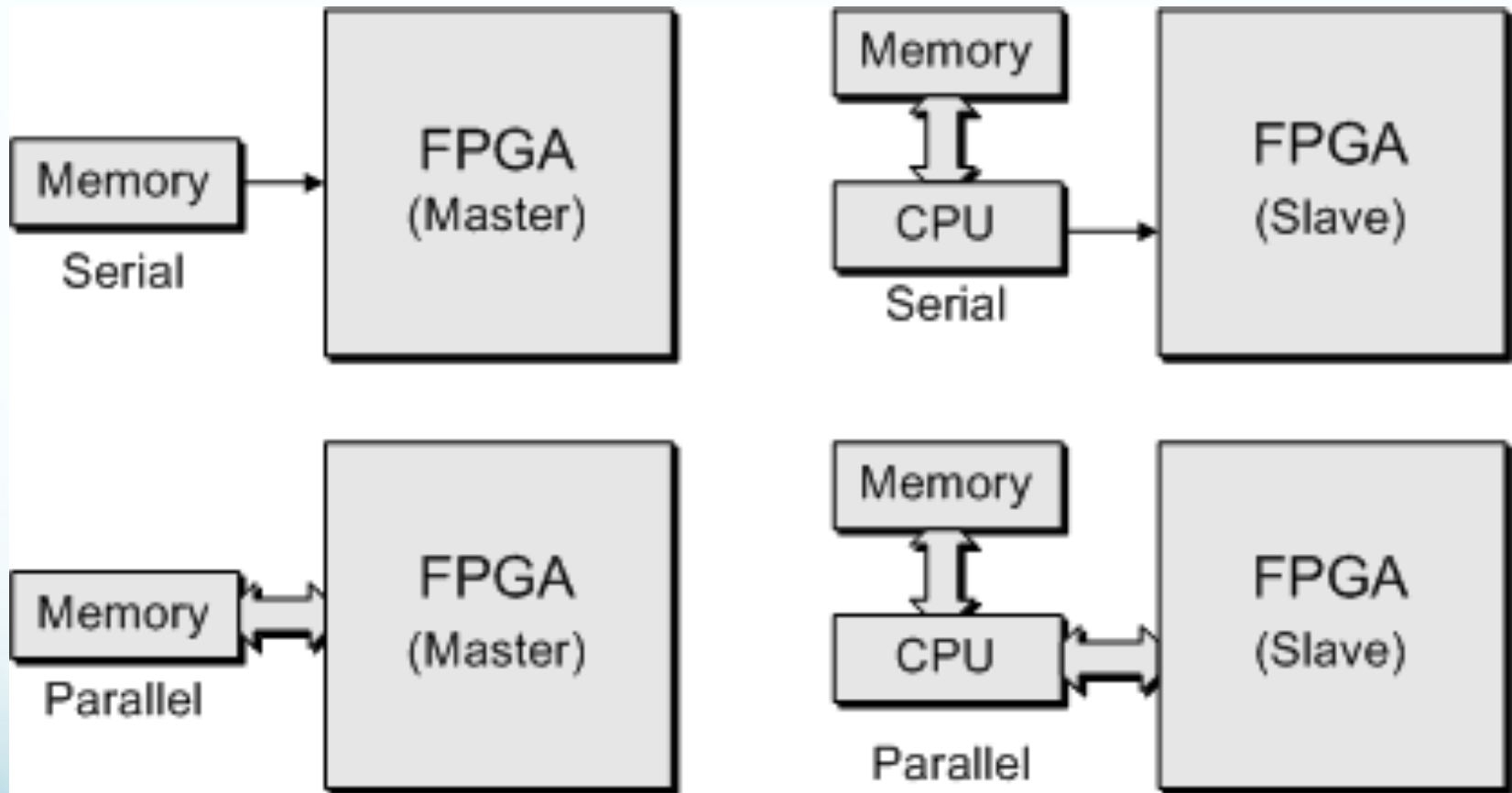


Configuration at power-up

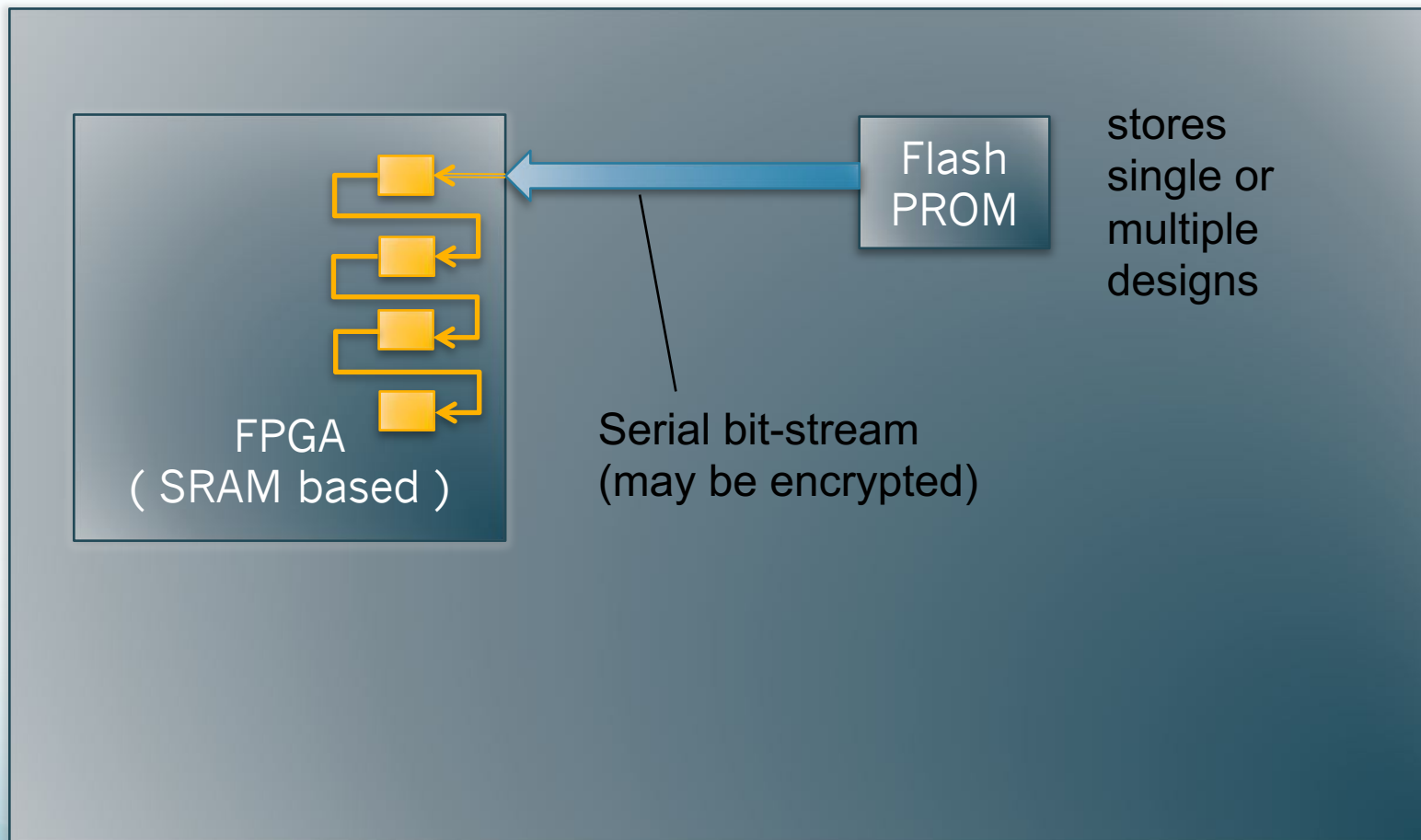


Typical FPGA configuration time: milliseconds

Programming via JTAG

Joint Test Action Group

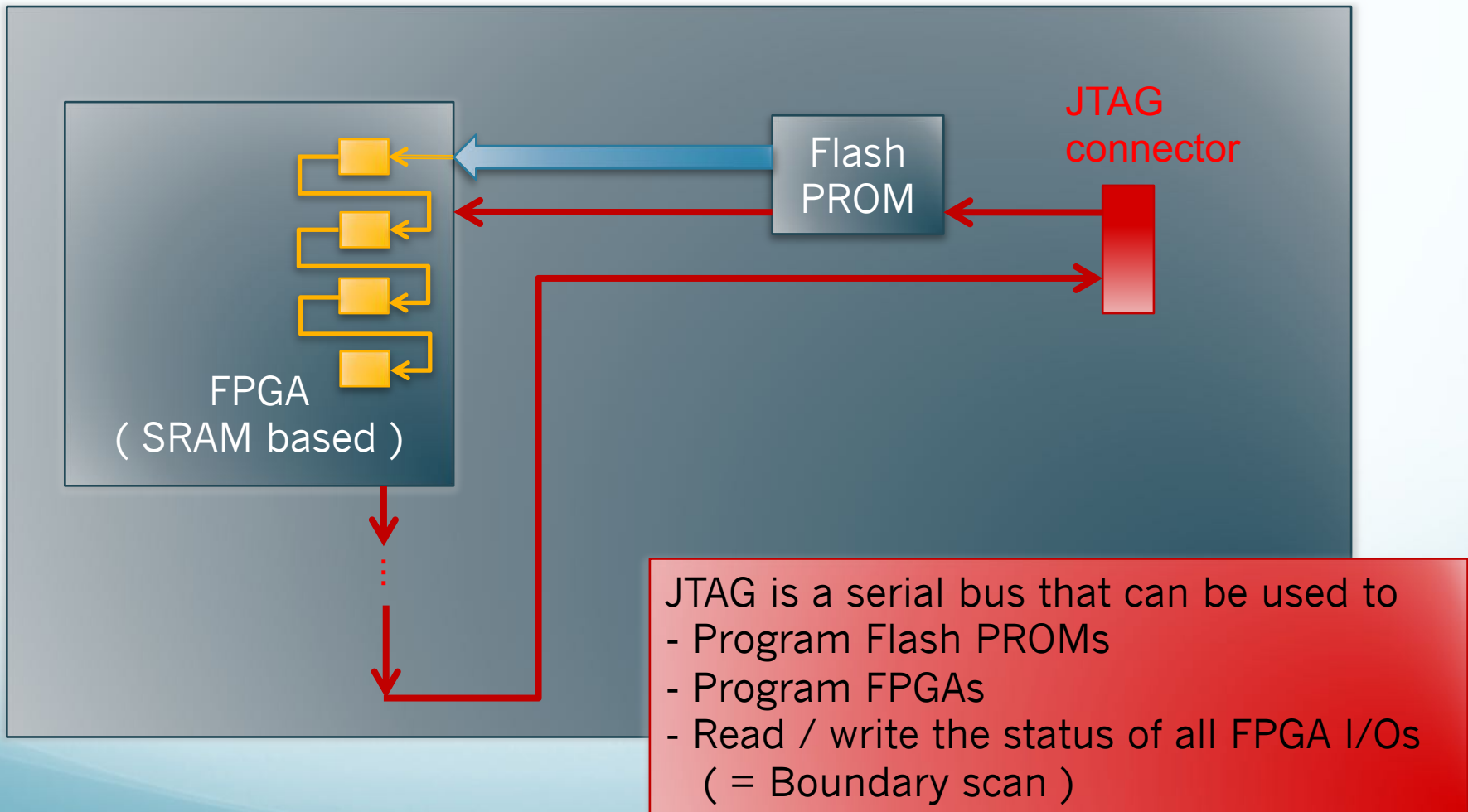

Remote programming

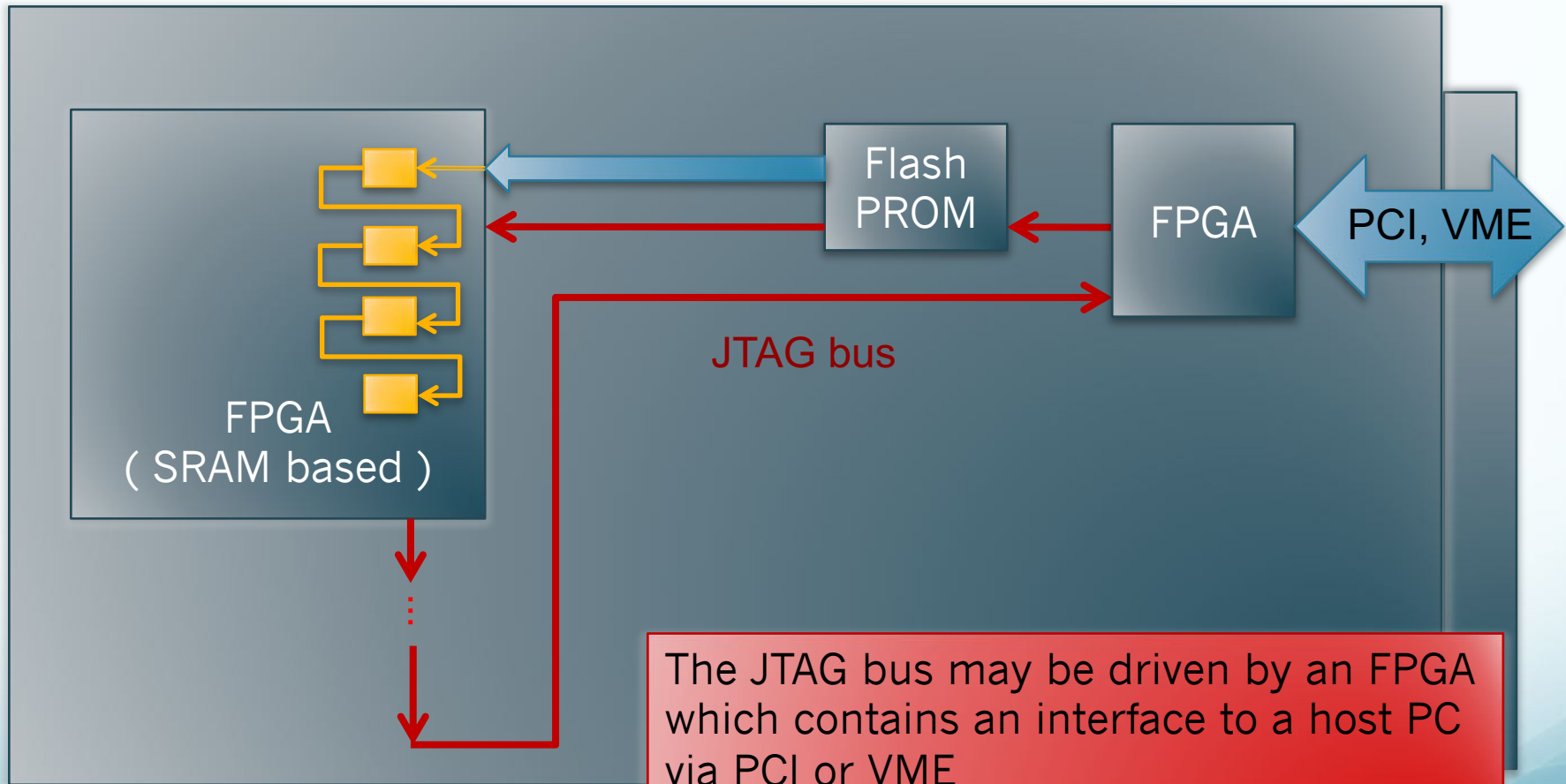


The JTAG bus may be driven by an FPGA which contains an interface to a host PC via PCI or VME

gateway can then be updated remotely


Timing

Timing

- Timing in FPGA design is critical

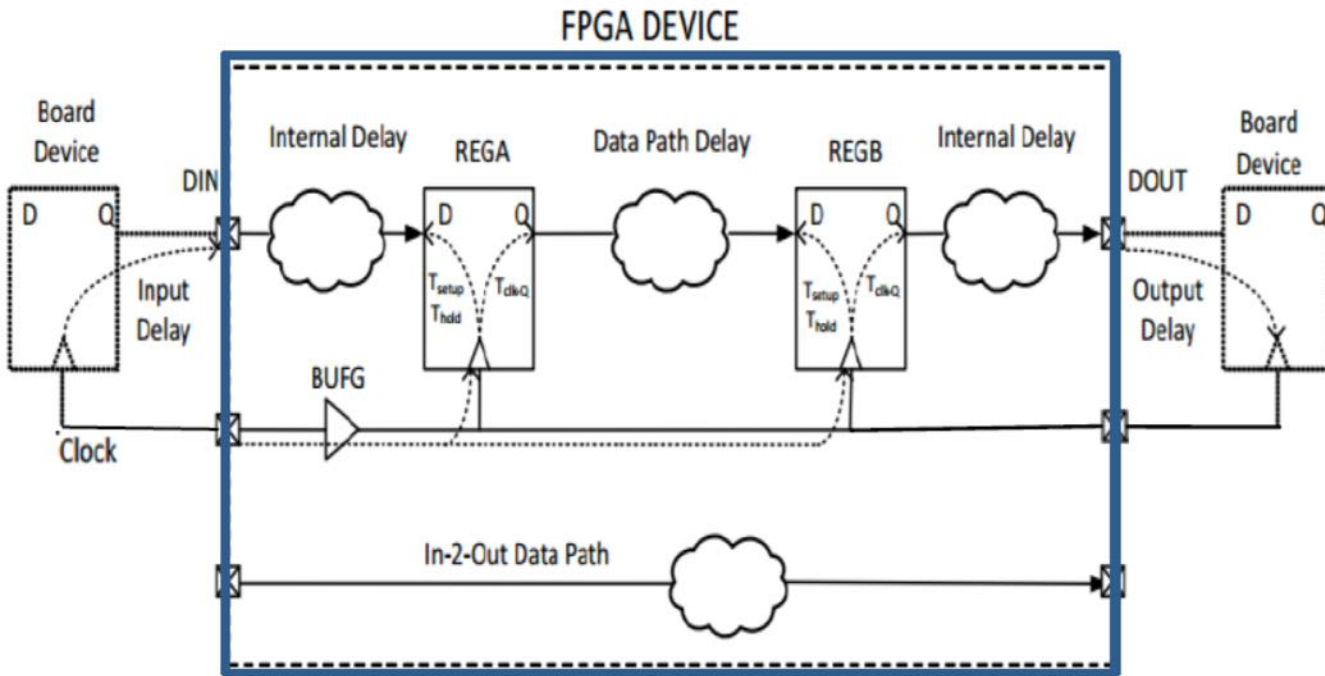


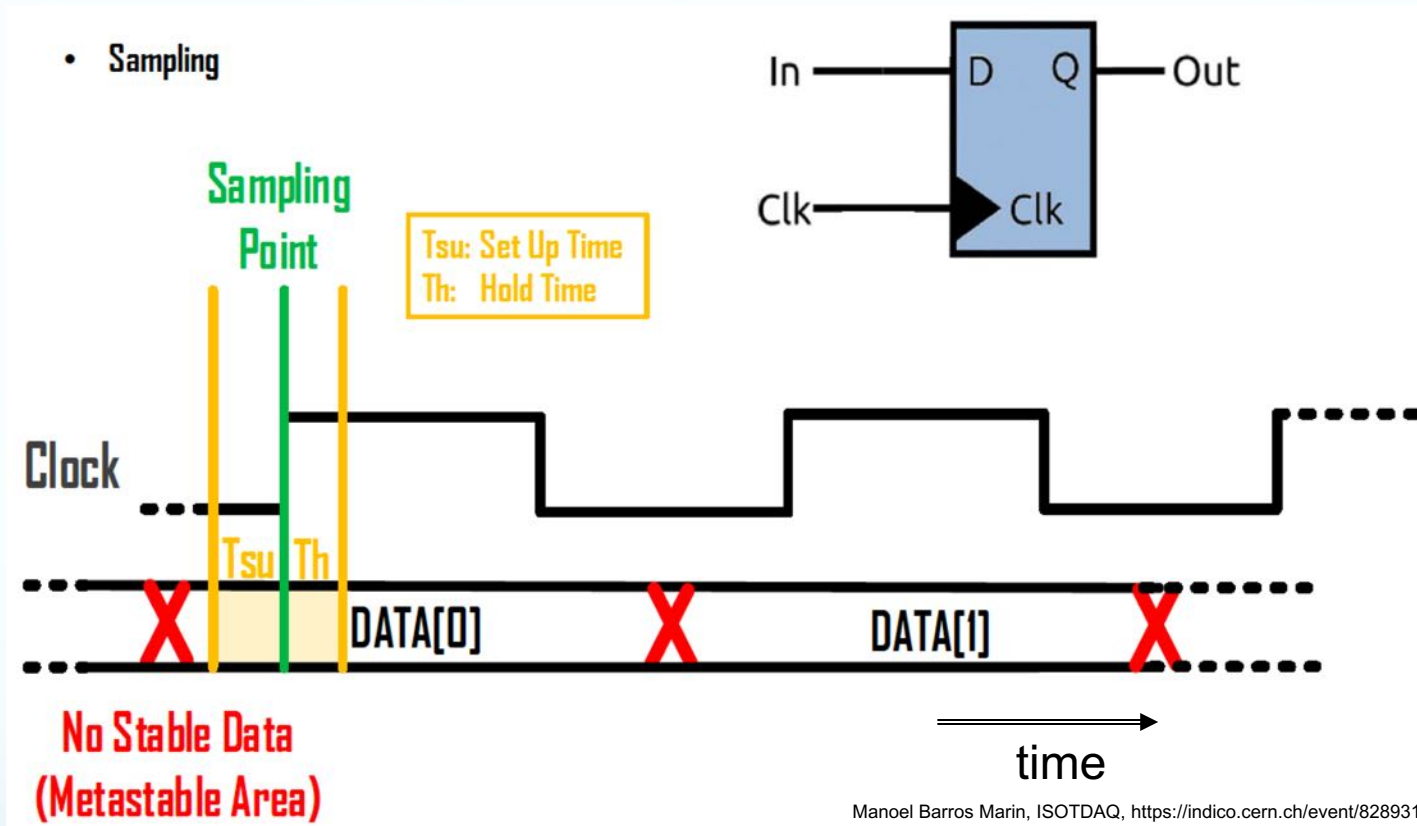
Data paths must respect setup and hold times



- **Setup time** is the amount of **time** required for the input to a Flip-Flop to be stable before a clock edge. **Hold time** is similar to **setup time**, but it deals with events after a clock edge occurs.

Timing

- Timing in FPGA design is critical

 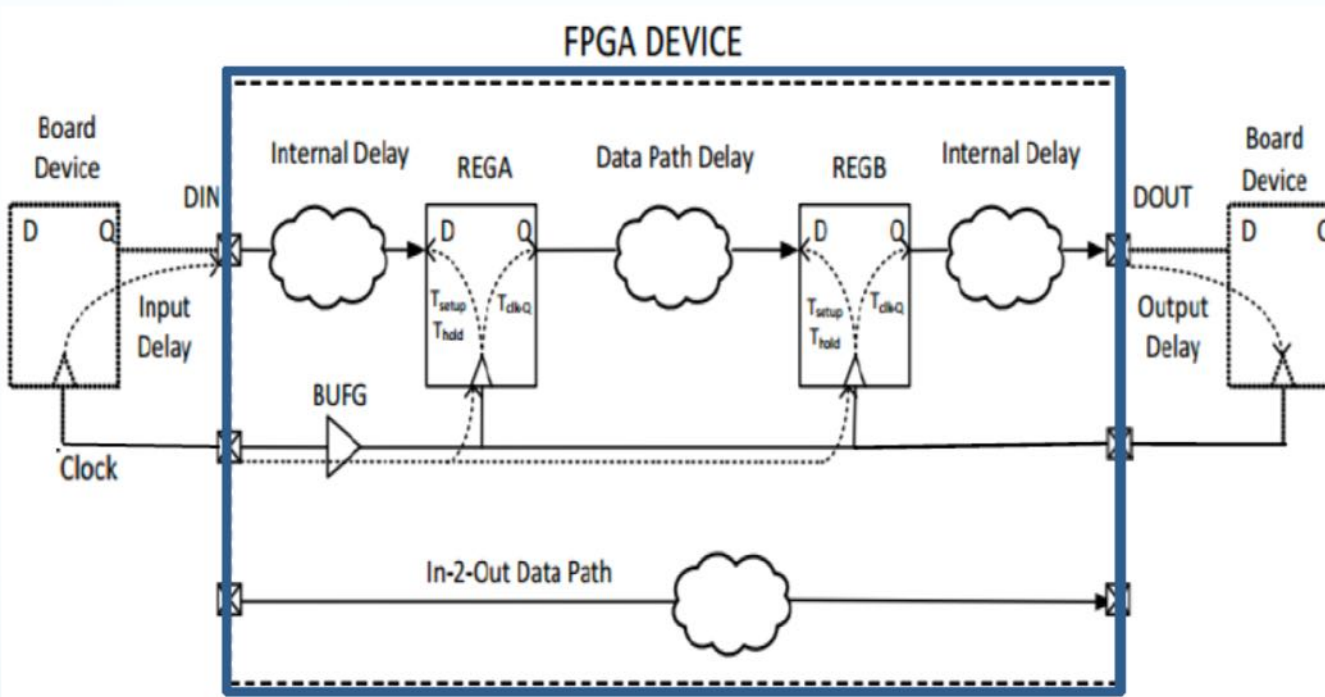


Synthesized RTL (Netlist) is implemented into FPGA

Manoel Barros Marin, ISOTDAQ, <https://indico.cern.ch/event/828931/>

Timing

- Timing in FPGA design is critical

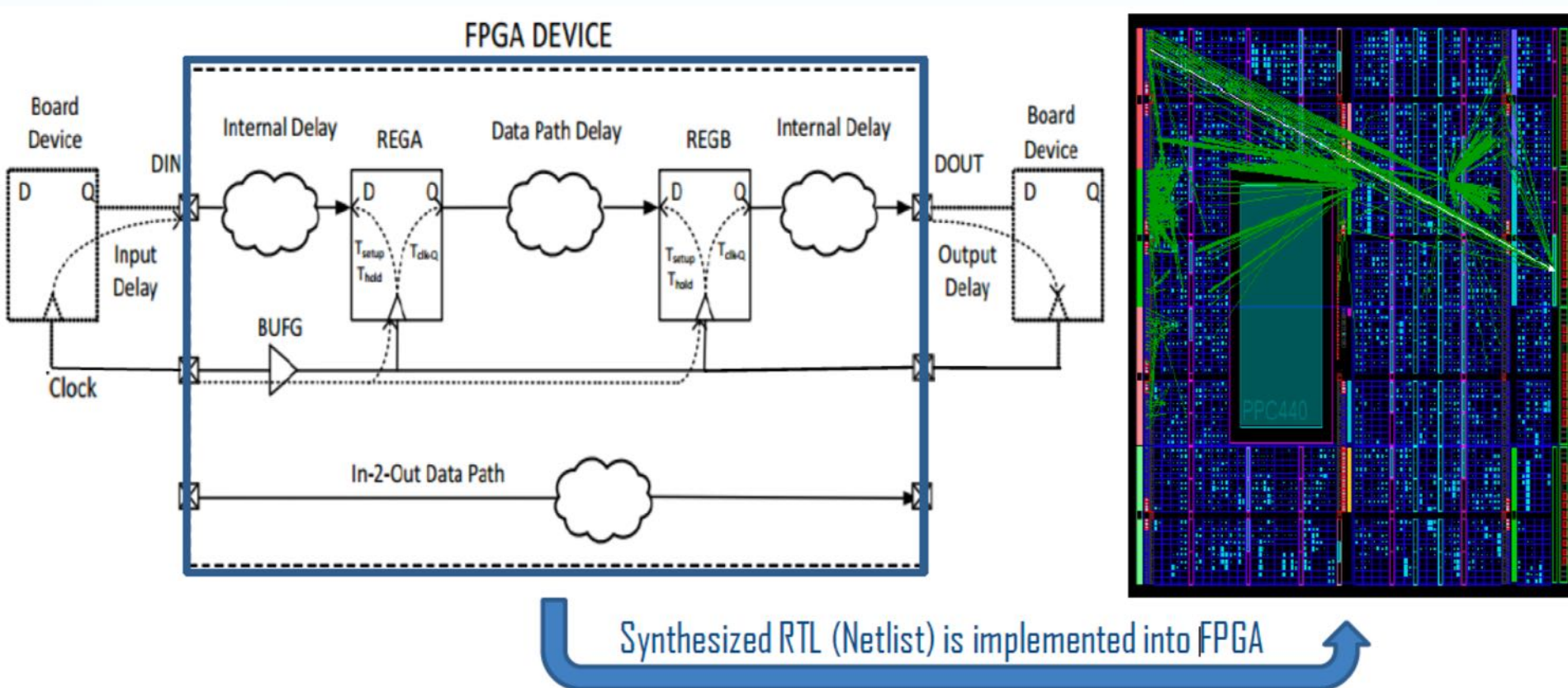


- If signals do not arrive at destination on time
 - Catastrophic consequences

Timing


- Always use dedicated clock networks to distribute clocks
 - Assures that clock is seen at all FFs at same time
 - Other clocking resources
 - Clock capable pins
 - Clock buffers
 - Clock Multiplexers
 - Phase Locked Loops
 - Digital Clock Managers



- Do not gate or derive clocks

 

Meeting timing closure

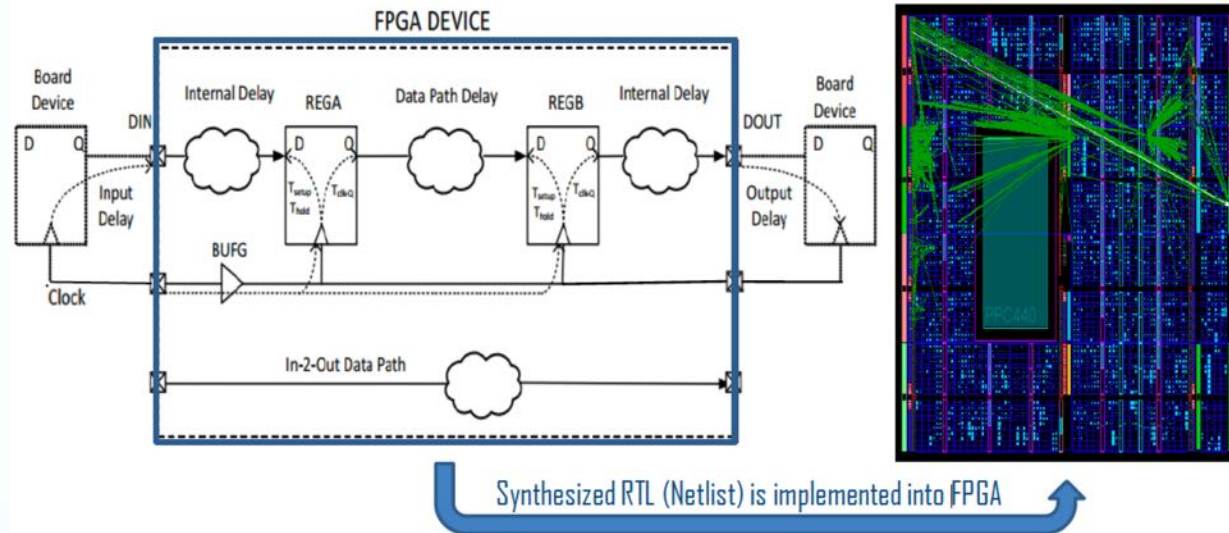

- Place & route step will try to position registers (flip-flops) and logic so that data path delays respect setup and hold times
- Options to meet timing
 - Instruct Place & route to use higher effort level
 - Add register stages & reduce amount of logic in data path (increases latency)
 - Choose location of inputs and outputs (at board design, or through optical patch panel)
 - Placement (area) constraints (give hints to the place & route step)
- Good practice
 - Whenever possible use I/O flip-flops (i.e FFs inside input/output cells)
 - Ensures timing with respect to external components is respected