

Digital design with VHDL

Lecture week on next generation particle detectors
10th – 14th June 2024, Bergen Norway

Johan Alme (johan.alme@uib.no)



ITS2 Readout

Specifications – ITS Readout Electronics is organized in Readout Units (RU)

The ITS front-end electronics are divided into **192** modular **Readout Units**, each connected to one ITS stave, and optically interfaced with both the Common Readout Unit (CRU) and the Central Trigger Processor (CTP).



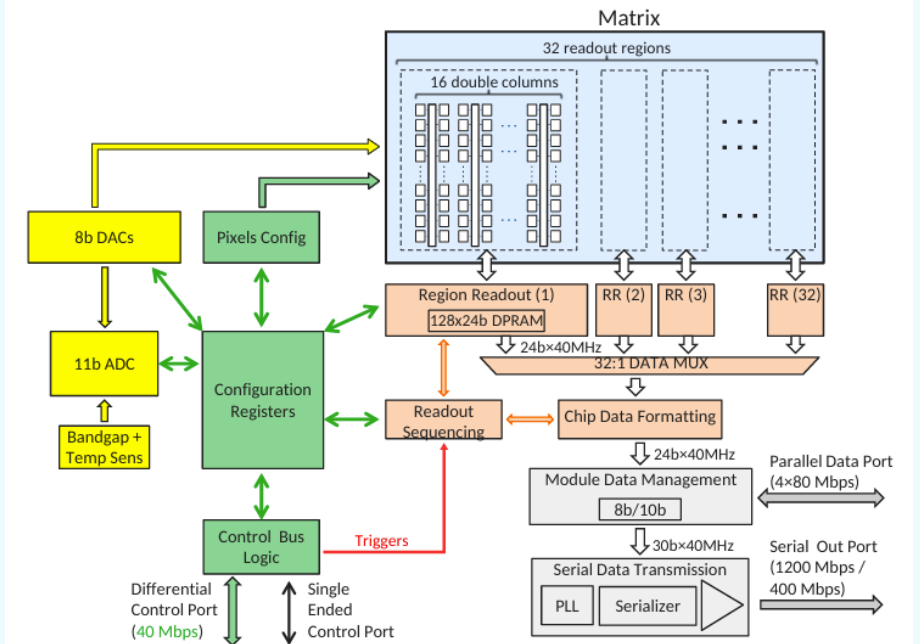


Figure 2.1: ALPIDE chip block diagram.


ALPIDEmanual_v0_3.pdf

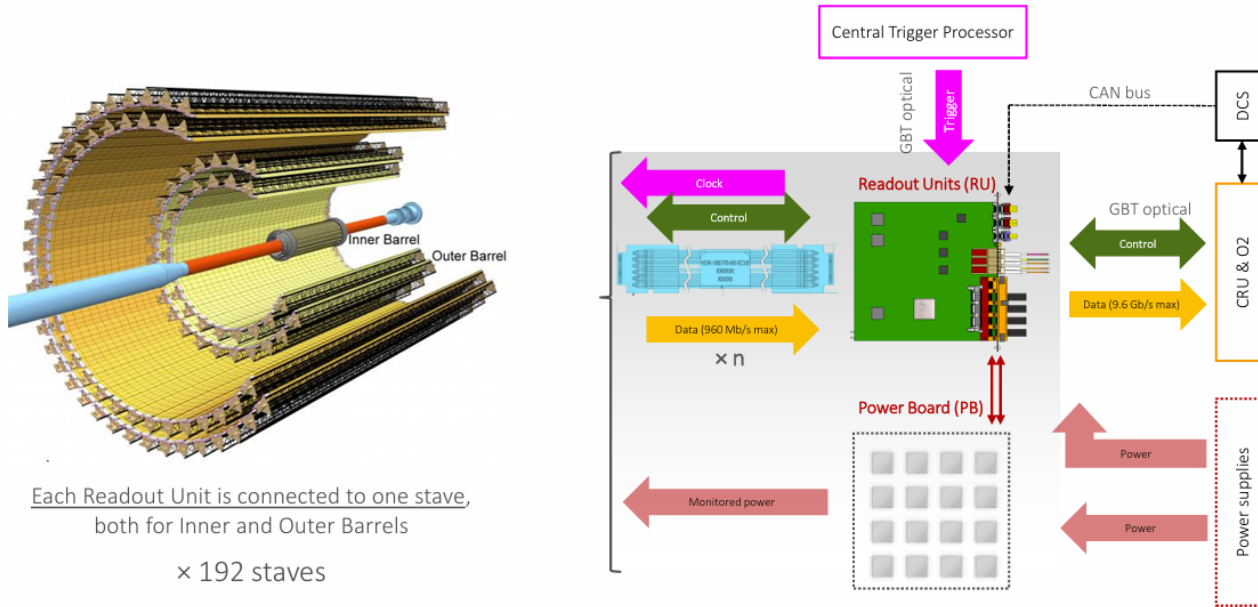

ITS3 Readout

 

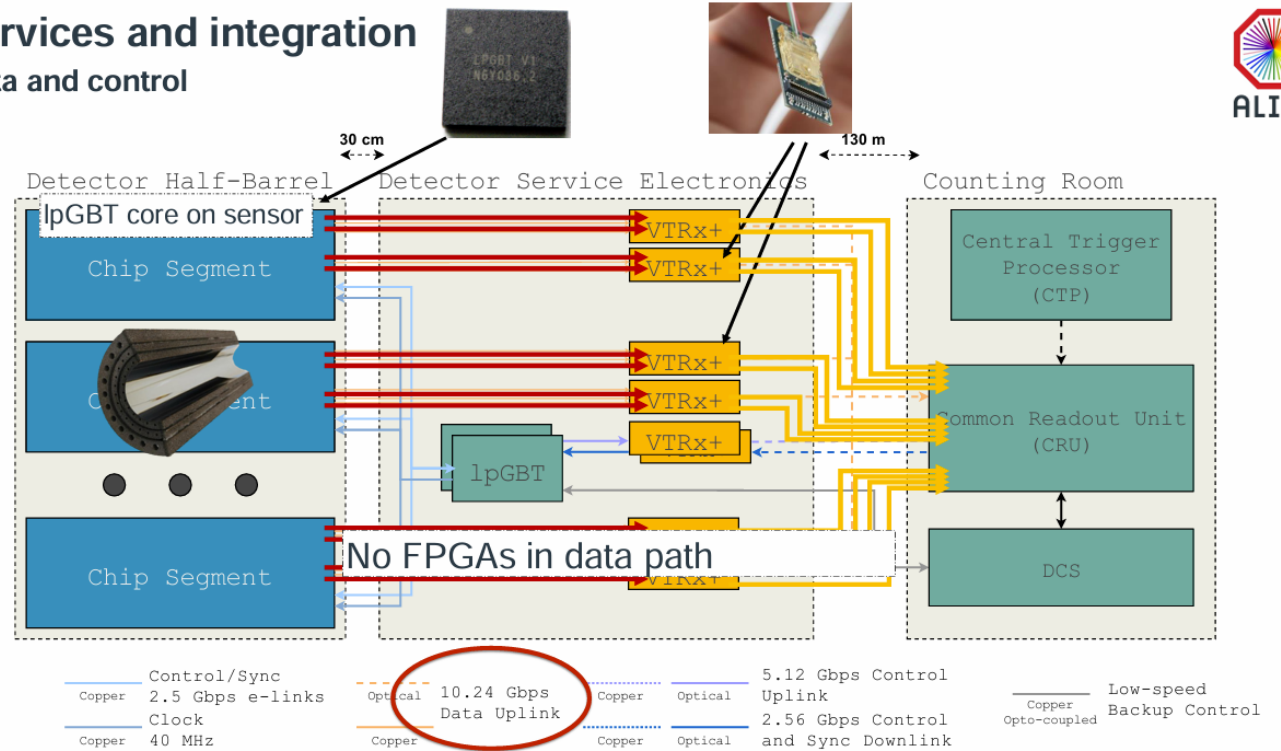Services and integration Data and control




October 5th 2023

TWEPP23: ALICE ITS3: a bent stitched MAPS-based vertex detector - Speaker: O. Groetvik


15




FPGAs Field Programmable Gate Arrays

 




FPGAs Field Programmable Gate Arrays

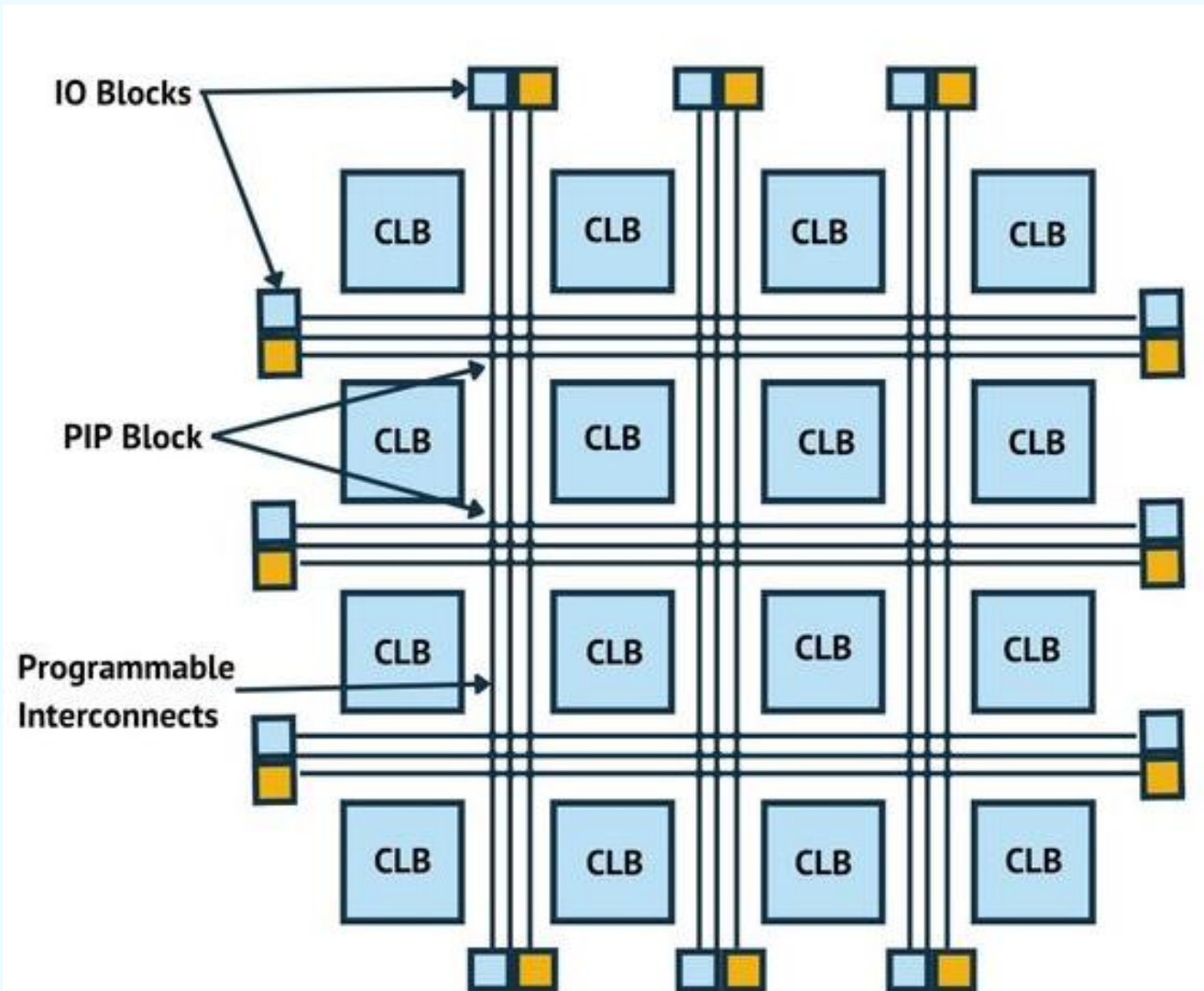

FPGAs Field Programmable Gate Arrays

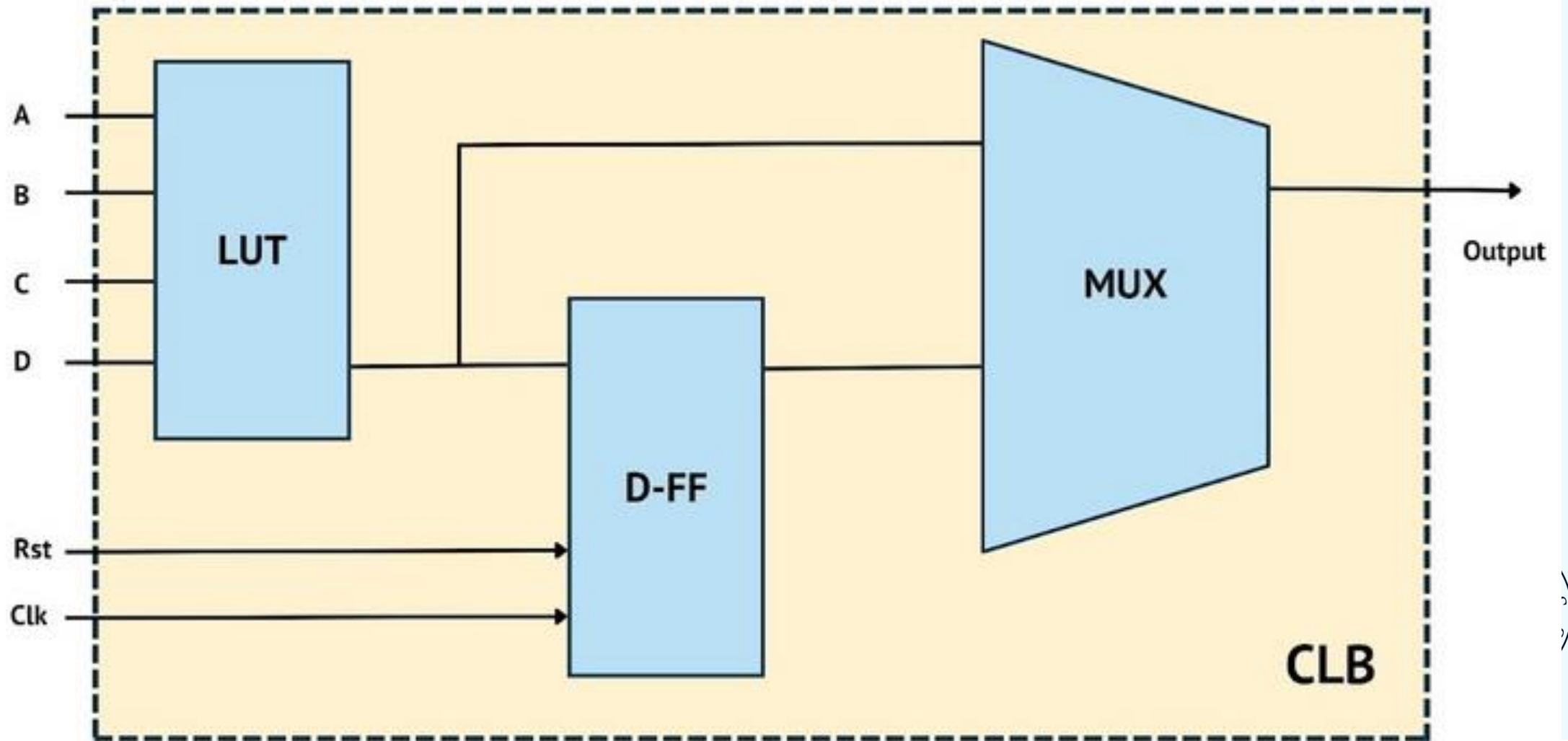

FPGAs Field Programmable Gate Arrays

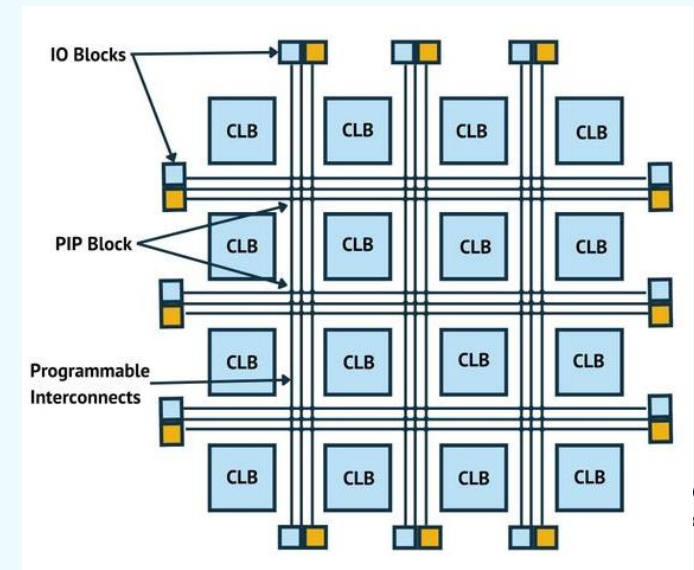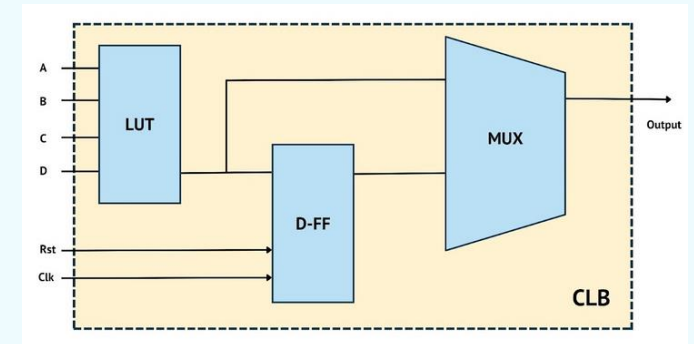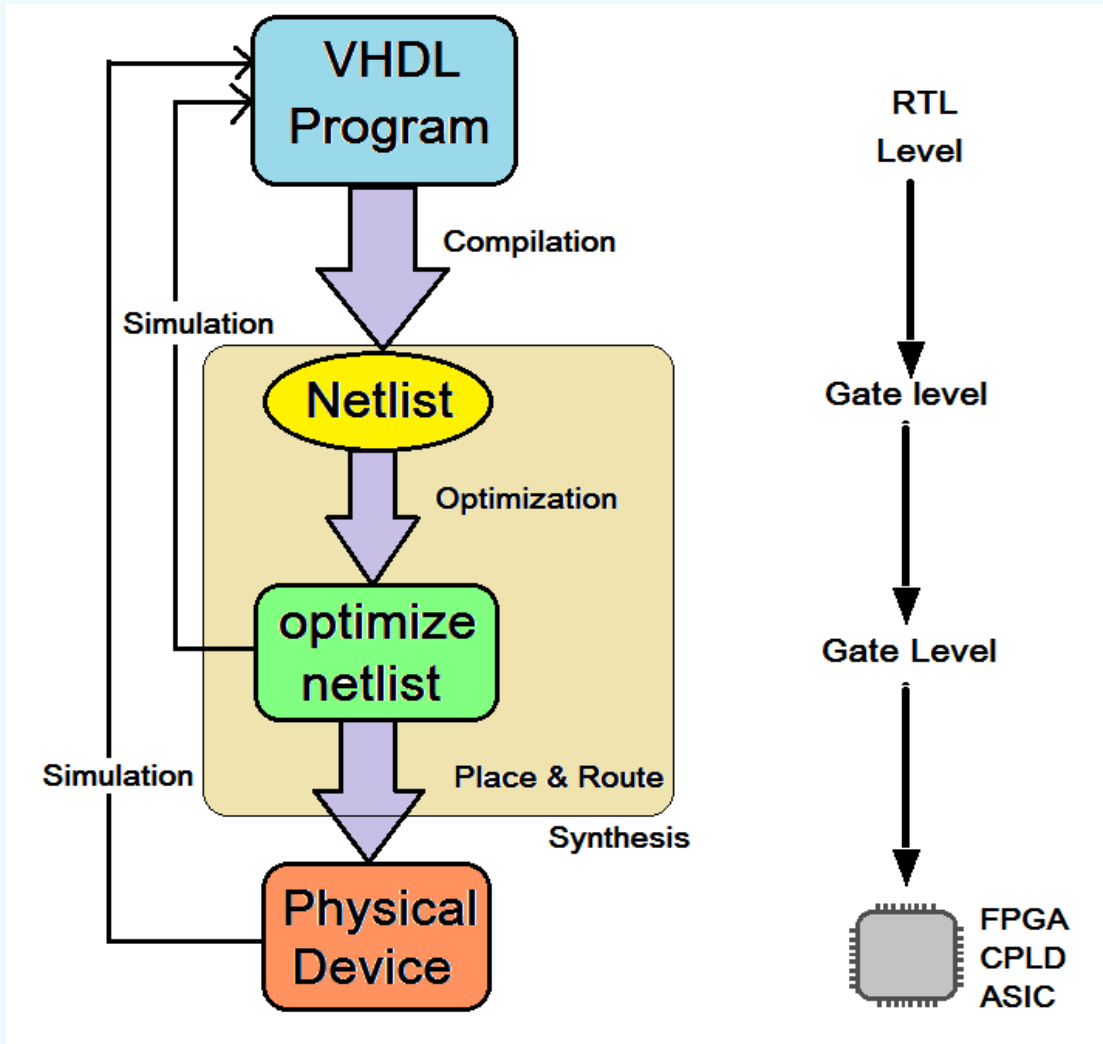


Default VHDL model

Libraries &
Packages headers


Interface definition
(input and outputs)

Functional/behavioural
implementation

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
USE ieee.std_logic_unsigned.ALL;  
  
entity L1_line_decoder is  
port(  
    clk           : in  std_logic;  
    reset_n      : in  std_logic;  
    L1Accept     : in  std_logic;  
    L0_support   : in  std_logic;  
    L0           : out std_logic;  
    L1a         : out std_logic);  
end L1_line_decoder;  
  
architecture behave of L1_line_decoder is  
    signal shiftreg : std_logic_vector(2 downto 0);  
begin  
  
    p_gen_triggers : process(clk, reset_n)  
    begin  
        if (reset_n = '0') then  
            L0 <= '0';  
            L1a <= '0';  
        elsif rising_edge(clk) then  
            L0 <= '0';  
            L1a <= '0';  
            if (L0_support = '0') then --old version of software  
                if (shiftreg = "010") then  
                    L1a <= '1';  
                end if;  
            else  
                if (shiftreg = "010") then  
                    L0 <= '1';  
                end if;  
                if (shiftreg = "011") then  
                    L1a <= '1';  
                end if;  
            end if;  
        end process p_gen_triggers;  
  
    p_shiftreg : process(clk)  
    begin  
        if falling_edge(clk) then  
            shiftreg(0) <= L1Accept;  
            shiftreg(2 downto 1) <= shiftreg(1 downto 0);  
        end if;  
    end process p_shiftreg;  
end behave;
```

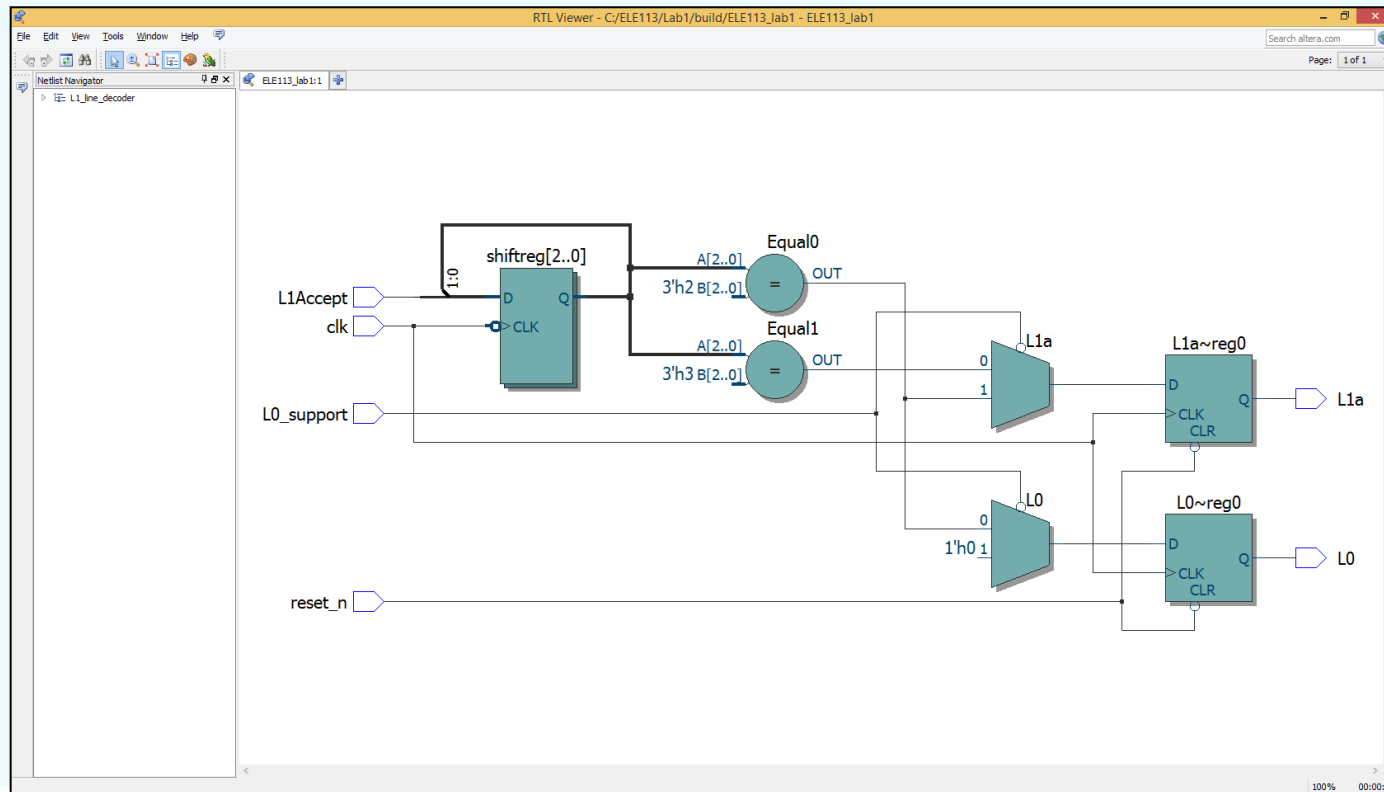

Concurrency

 

- THINK HARDWARE:
 - In real life the value @ **E** is always the result of **B and C**
 - Whenever **B** and/or **C** changes – **E** will change accordingly!
 - Similarly the value @ **D** changes when **A** and/or **B** changes
 - It might happen that the value @ **D** and @ **E** changes at the same time → *Concurrency*
- The following assignment statements are *concurrent* – they can be written in *any order*

```
D <= A NOR B;  
E <= B AND C;  
Q <= D OR E;
```

==


```
Q <= D OR E;  
D <= A NOR B;  
E <= B AND C;
```

==

```
Q <= (A NOR B) OR (B AND C);
```




 Digital design – Register Transfer Level (RTL)




Typical VHDL constructs (1): D flip-flop
 
```
d_ff : process(clk)
begin
    if rising_edge(clk) then
        q <= data;
    end if;
end process d_ff;
```




Typical VHDL constructs (2): D flip-flop with asynchronous reset
 
```
d_ff : process(clk, reset)
begin
  if (reset = '0') then
    q <= '0';
  elsif rising_edge(clk) then
    q <= data;
  end if;
end process d_ff;
```




Typical VHDL constructs (3): D flip-flop with synchronous reset
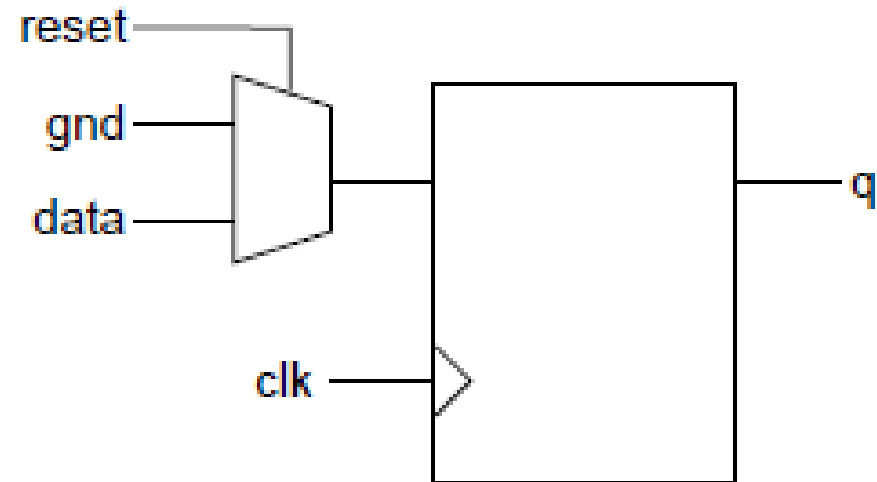
```
d_ff : process(clk)
begin
  if rising_edge(clk) then
    if (reset = '0') then
      q <= '0';
    else
      q <= data;
    end if;
  end if;
end process d_ff;
```




Typical VHDL constructs (4): Priority encoder
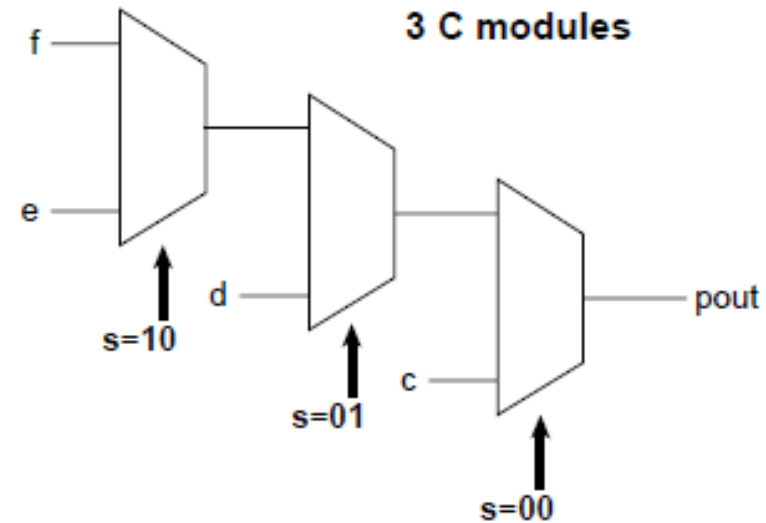
```
priority_encoder: process (a, c, d, e, f)
begin
  if (s = "00") then
    pout <= c;
  elsif (s = "01") then
    pout <= d;
  else
    pout <= f;
  end if;
end process priority_encoder;
```




Typical VHDL constructs (5): Multiplexer
 
```
mux : process(s, c, d, e, f)
begin
  case s is
    when "00" => mux_out <= c;
    when "01" => mux_out <= d;
    when "10" => mux_out <= e;
    when others => mux_out <= f;
  end case;
end process mux;
```



VHDL for design... and VERIFICATION

- A verification specification is always needed, but
 - The verification spec. should not be too extensive/detailed
 - Required details could be added in a later spec. iteration
- A separate verification specification document is normally not needed
- Turn the verification spec into testcases
- We will use a simplistic verification model here. Various complex testbench models exist
 - UVVM
 - UVM
 - COCOTB ...

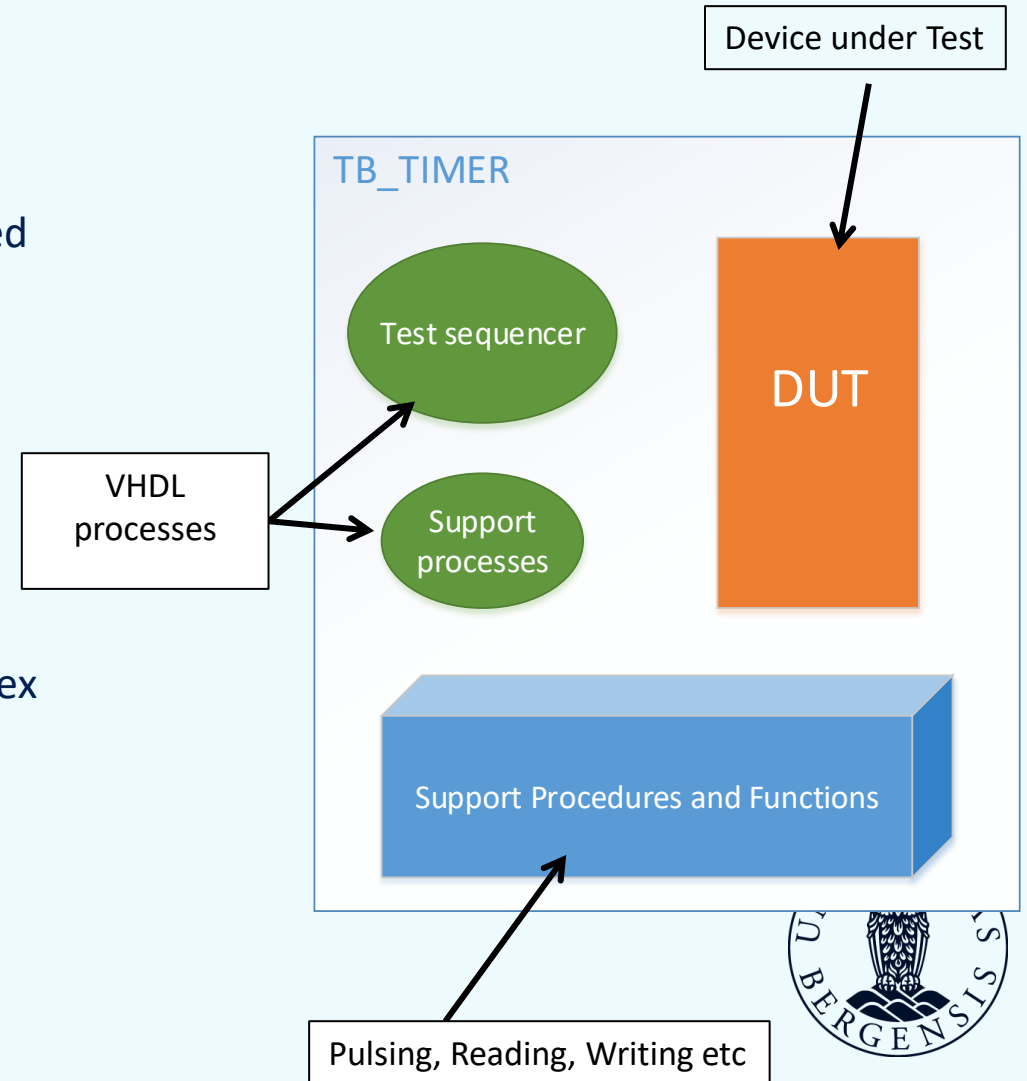

Sources

- This assignment:

https://universityofbergen-my.sharepoint.com/:f:/g/personal/johan_alme_uib_n_o/EklesnHWAXtPivKrNOX7fFkBO8xOUjZeSWtmw0Awt_R2Aw?e=IOuxGv

Password: IRTG2024

- FYS4220 (UiO): <https://fys4220.github.io/>

