

# Analog FE: ASIC

Upgrade of the front end electronics of the  
LHCb calorimeter


D. Gascón, E. Picatoste, C. Abellan, F. Machefert, J. Lefrançois, O. Duarte

**ICC-UB, URL, LAL**




- I. Introduction
- II. Input stage
- III. Channel architecture
- IV. Technology

# I. Introduction: current ECAL/HCAL FE

LAL-Orsay

 

- Pulse shaping in 25 ns
- Residue < 1% after 25 ns
- Integrator plateau : 4 ns
- Linearity < 0.5%
- Rise time ~ 5 ns

   


**BiCMOS 0.8um Integrated Circuit  
4 Channels per chip**

# I. Introduction: motivation and task sharing

- **PM current has to be reduced**
  - Otherwise PMT would die rapidly (require a factor  $\sim 5$ )
  - FE electronics gain has to be increased correspondingly
  - FE noise should not be increased in the operation !
- **New front end board is required:**
  - Low noise analog electronics
  - GBT for data transmission @ 40MHz
    - *Digital development @ LAL (Frédéric's talk)*
- **For 12 bit DR, input referred noise:**
  - Voltage amplifier:  $< 1 \text{ nV}/\sqrt{\text{Hz}}$
  - Current amplifier:  $< 10 \text{ pA}/\sqrt{\text{Hz}}$
  - Active cooled termination required:
    - *ASIC development @ UB (Edu's and this talks)*
- **But 2/3 of the signal are lost by clipping:**
  - Alternative solution: remove clipping at the PM base (detector)
  - Perform clipping after amplification in FE
  - Alternative analog COTS + delay line solution
    - *COTS development @ URL (Carlos' talk)*

See talk noise in June 2009 meeting:

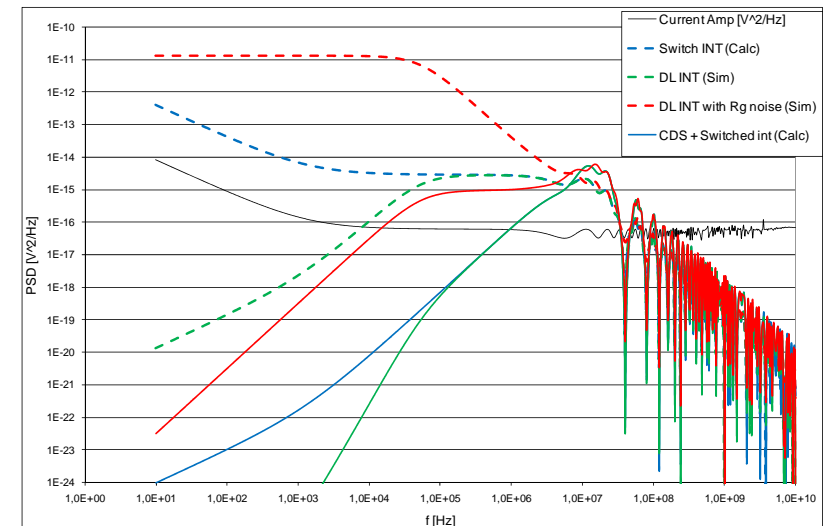
<http://indico.cern.ch/materialDisplay.py?contribId=1&sessionId=0&materialId=slides&confId=59892>



This talk considers single ended implementation, results should be scaled by  $\sqrt{2}$

# I. Introduction: requirements

- Requirements (LOI):

|                           | Value   | Comments   |
|---------------------------|---|--|
| Energy range              | 0-10 GeV/c (ECAL)<br>Transverse energy                    | 1-3 Kphe / GeV<br>Total energy   |
| Calibration               | 4 fC / 2.5 MeV / ADC cnt                                  | 4 fC input of FE card: assuming 25 $\Omega$ clipping at PMT base<br>12 fC / ADC count if no clipping               |
| Dynamic range             | 4096-256=3840 cnts :12 bit                                | Enough? New physic req.? Pedestal variation? Should be enough  |
| Noise                     | $\ll 1$ ADC cnt or ENC $< 5$ -6 fC                        | $< 0.7$ nV/ $\sqrt{\text{Hz}}$  |
| Termination               | 50 $\pm$ 5 $\Omega$                                       | Passive vs. active   |
| AC coupling               | Needed  | Low freq. (pick-up) noise  |
| Baseline shift Prevention | Dynamic pedestal subtraction (also needed for LF pick-up) | How to compute baseline?<br>Number of samples needed?  |
| Max. peak current         | 4-5 mA over 25 $\Omega$<br>1.5 mA at FE input if clipping | 50 pC in charge  |
| Spill-over correction     | Clipping  | Residue level: 2 % $\pm$ 1 % ?   |
| Spill-over noise          | $\ll$ ADC cnt   | Relevant after clipping?   |
| Linearity                 | $< 1\%$   |  |
| Crosstalk                 | $< 0.5\%$   |  |
| Timing                    | Individual (per channel)                                  | PMT dependent  |

See talk about noise in June 2009 meeting:

<http://indico.cern.ch/materialDisplay.py?contribId=1&sessionId=0&materialId=slides&confId=59892>

This talk considers single ended implementation, results should be scaled by  $\text{xsqrt}(2)$

## II. Input stage: active line termination

- **Electronically cooled termination required:**

- 50 Ohm resistor noise is too high
- e. g. ATLAS LAr (discrete component)

- **Common gate with double voltage feedback**

- Inner loop to reduce input impedance preserving linearity and with low noise
- Outer loop to control the input impedance accurately

$$Z_i \approx \frac{1/g_{m1}}{G} + R_{C1} \frac{R_1}{R_1 + R_2}$$


- Transimpedance gain is given by  $R_{C1}$

- Noise is  $< 0.5 \text{ nV}/\sqrt{\text{Hz}}$

- Small value for  $R_1$  and  $R_2$
- Large  $g_{m1}$  and  $g_{m2}$

- **Need ASIC for LHCb**

- 32 ch / board: room and complexity

 

## II. Input stage : LAPAS chip for ATLAS LAr upgrade


- TWEPP 09

### LAPAS: A SiGe Front End Prototype for the Upgraded ATLAS LAr Calorimeter

Mitch Newcomer

On Behalf of the ATLAS LAr Calorimeter Group\*

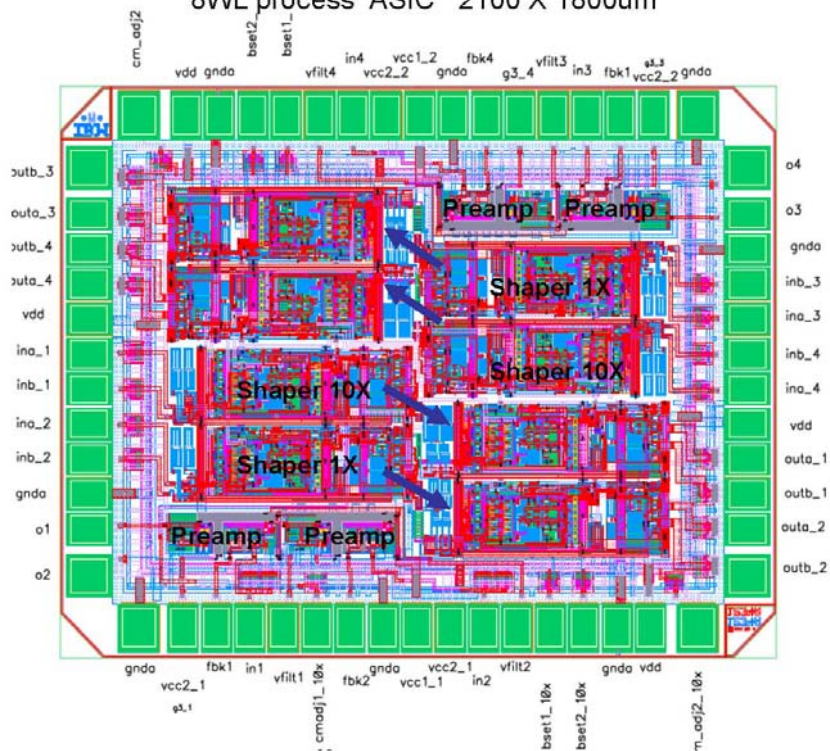**LAPAS: Liquid Argon PreAmplifier Shaper**  
8WL process ASIC 2100 X 1800um



*Special Acknowledgment of the significant contributions of Emerson Vernon, Sergio Rescia (BNL) and Nandor Dressnandt (Penn) to this work.*


## II. Input stage: LAPAS chip for ATLAS LAr upgrade

### • Technology:

- IBM 8WL SiGe BiCMOS
- 130 nm CMOS (CERN's techno)
- Radiation tolerance:
  - FEE Rad Tolerance TID~ 300Krad,
  - Neutron Fluence  $\sim 10^{13}$  n/cm<sup>2</sup>
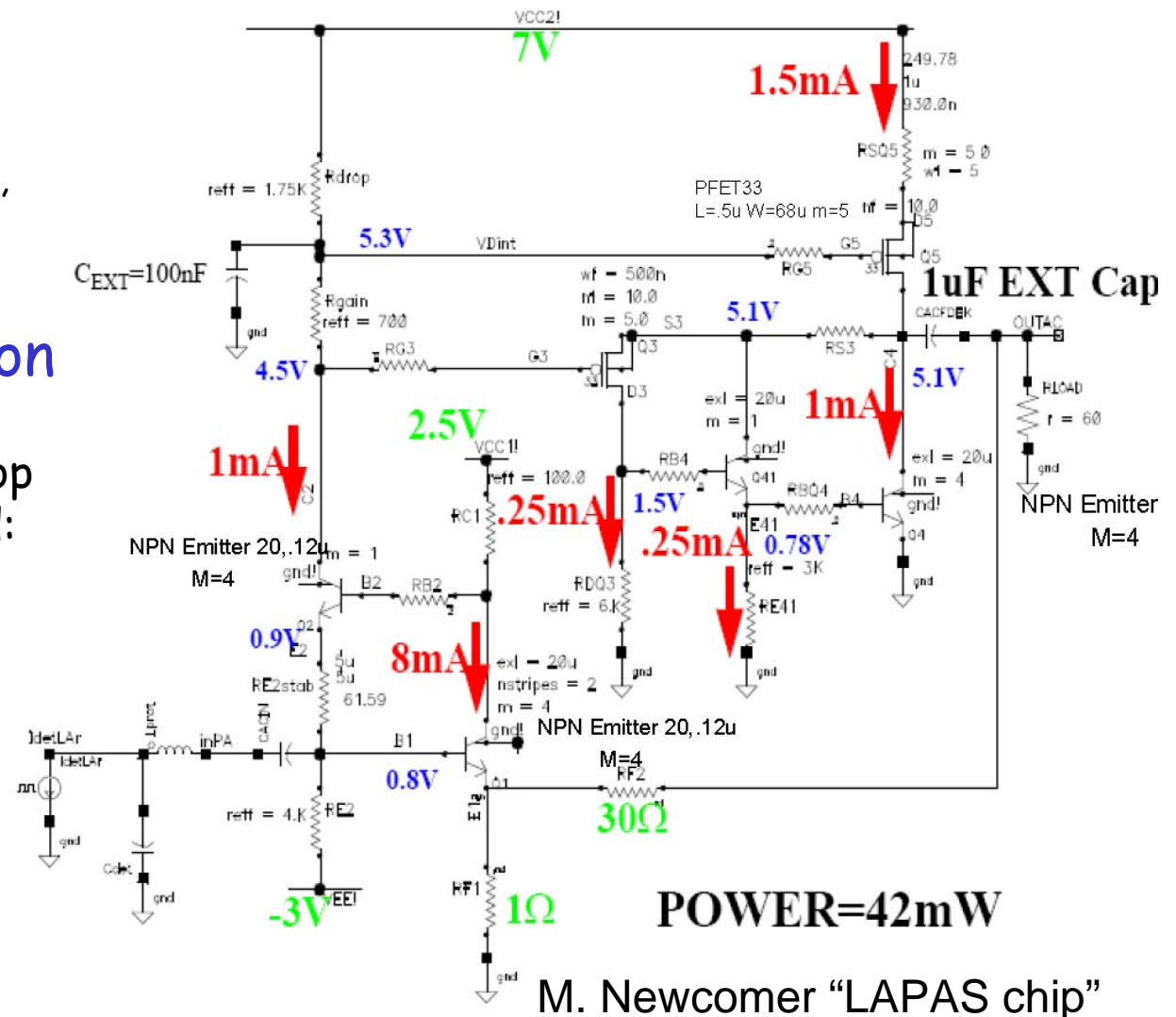
### • Circuit is "direct" translation

- Need external 1 uF AC coupling capacitor for outer feedback loop
- Three pads per channel required:
  - Input
  - Two for AC coupling capacitor
- Voltage output





## II. Input stage: current output / current feedback

### • Current mode feedback:

- Inner loop: lower input impedance
  - Current feedback (gain): mirror: K
- Outer loop: control input impedance
  - Current feedback: mirror: m

### • Current gain: m

### • Input impedance

$$Z_i \approx \frac{1/g_{m1} + R_e}{1 + K} + \frac{K}{1 + K} m R_f$$

### • Current mode feedback used


- Optical communications
- SiPM readout

### • Low voltage

- Only 1 V<sub>be</sub> for the super common base input stage
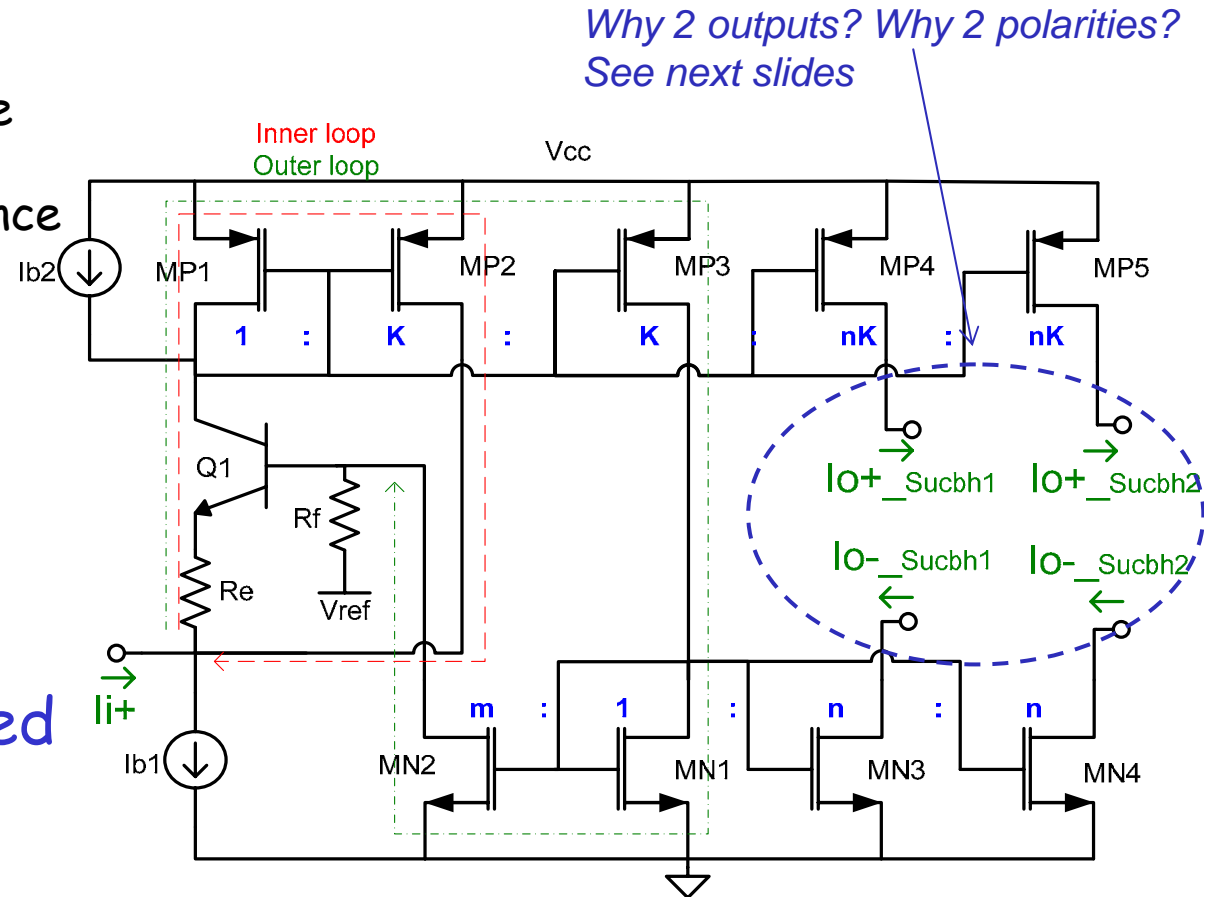
### • Better in terms of ESD:

- No input pad connected to any transistor gate or base



**POWER < 10 mW**

### III. Channel architecture

*Very difficult to integrate HQ analog delay lines*



*2 switched alternated paths as in PS/SPD*




*Switching noise !*




*Fully differential ASAP*

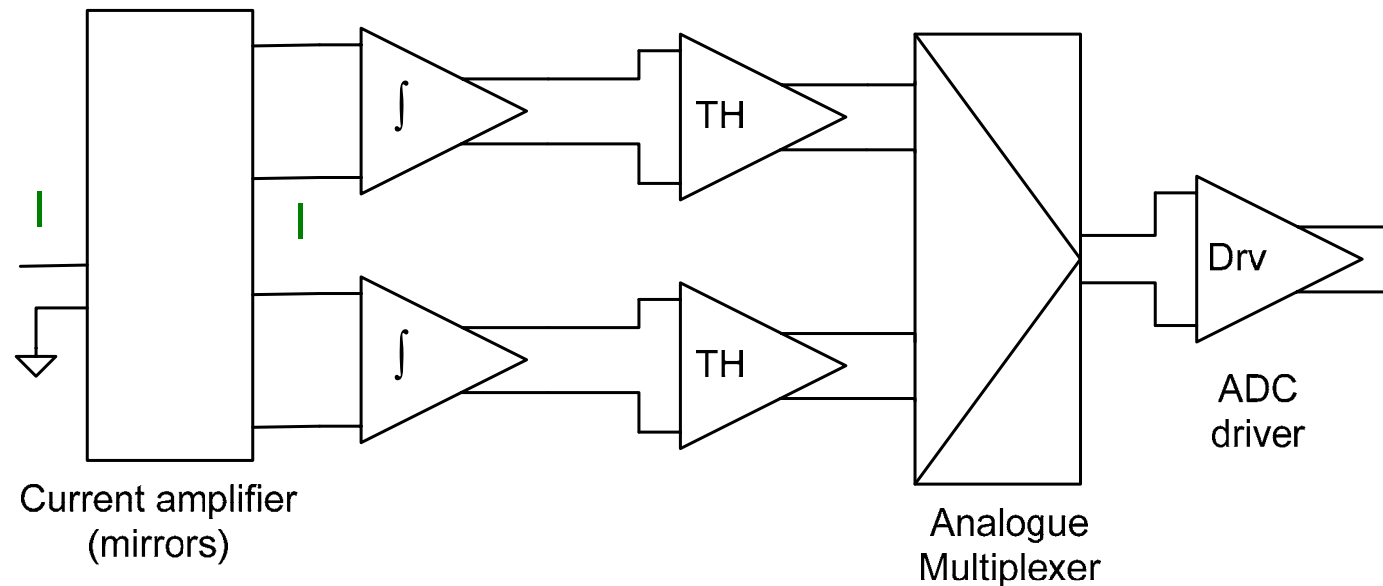- Current mode amplifier
- Switched integrator
  - Fully differential Op Amp
- Track and hold
  - 12 bit: flip-around architecture
- Analogue multiplexer
- ADC driver
  - To match ADC input impedance


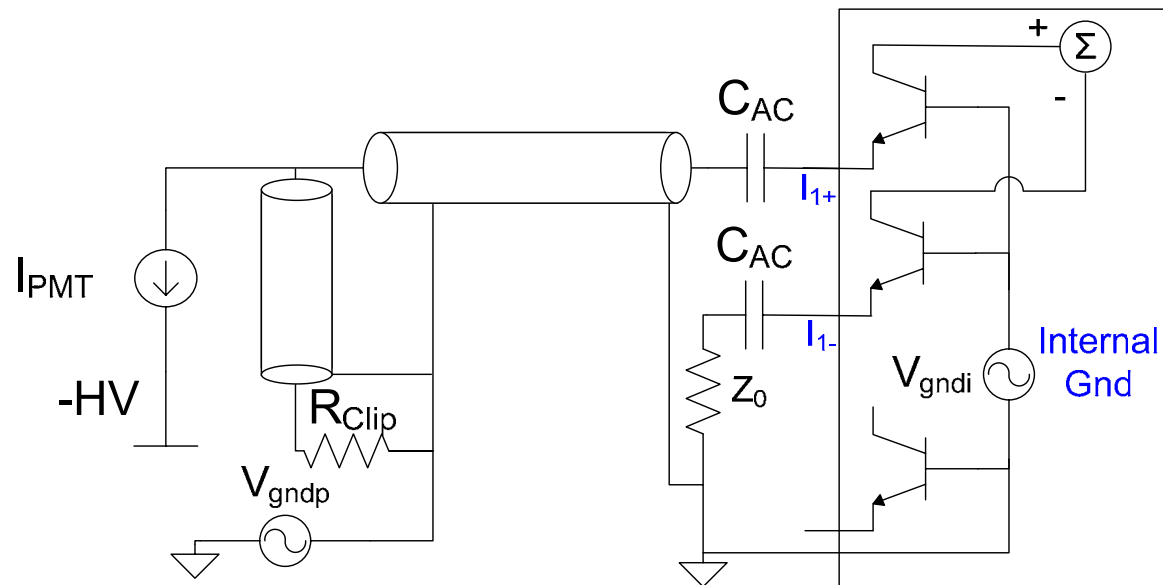
### III. Channel architecture: pseudo-differential input

- Pseudo-differential input attenuates ground (and CM) noise in FE:
  - Mitigates  $V_{\text{gndi}}$  (conducted) noise (attenuation depends on matching)
  - Symmetrical chip/PCB layout also mitigates capacitive coupling (xtalk, pick-up)




- Drawback: uncorrelated HF noise  $\times \sqrt{2}$ 
  - Predictable and stable effect
- Current mode preamplifier makes easier pseudo differential input:
  - Current: 2 pads per channel
  - Voltage (external component): 6 pads per channel
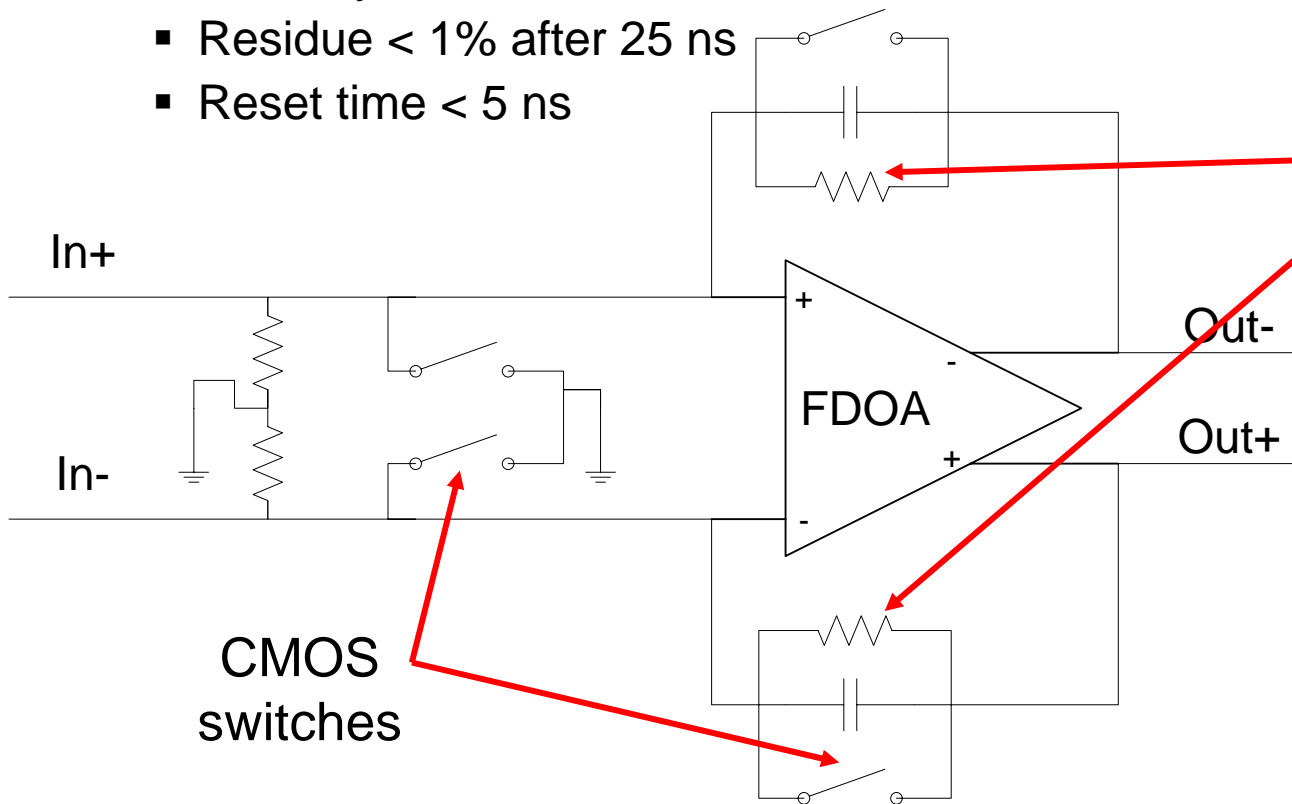
### III. Channel architecture


- Switched integrator

- Integrator plateau : 4 ns
- Linearity < 1%
- Residue < 1% after 25 ns
- Reset time < 5 ns




- $R_f$  to improve plateau

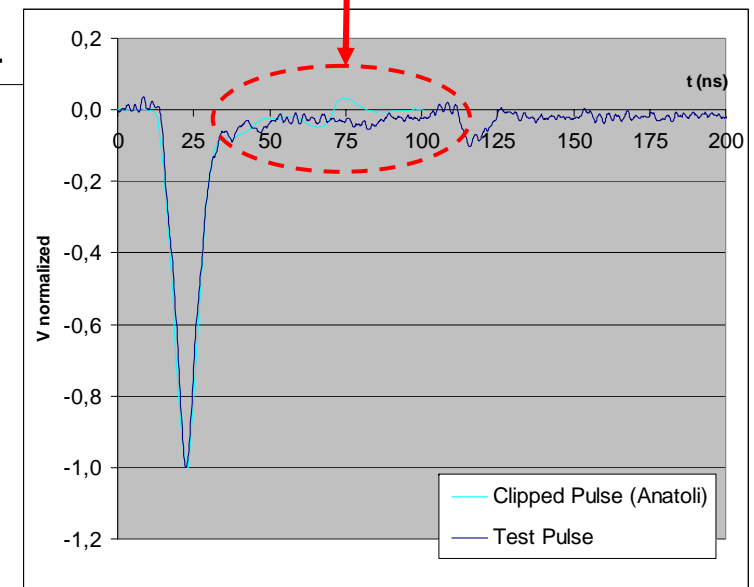- 100 ns time constant
- Cancel slow component of the clipped signal (remanent)


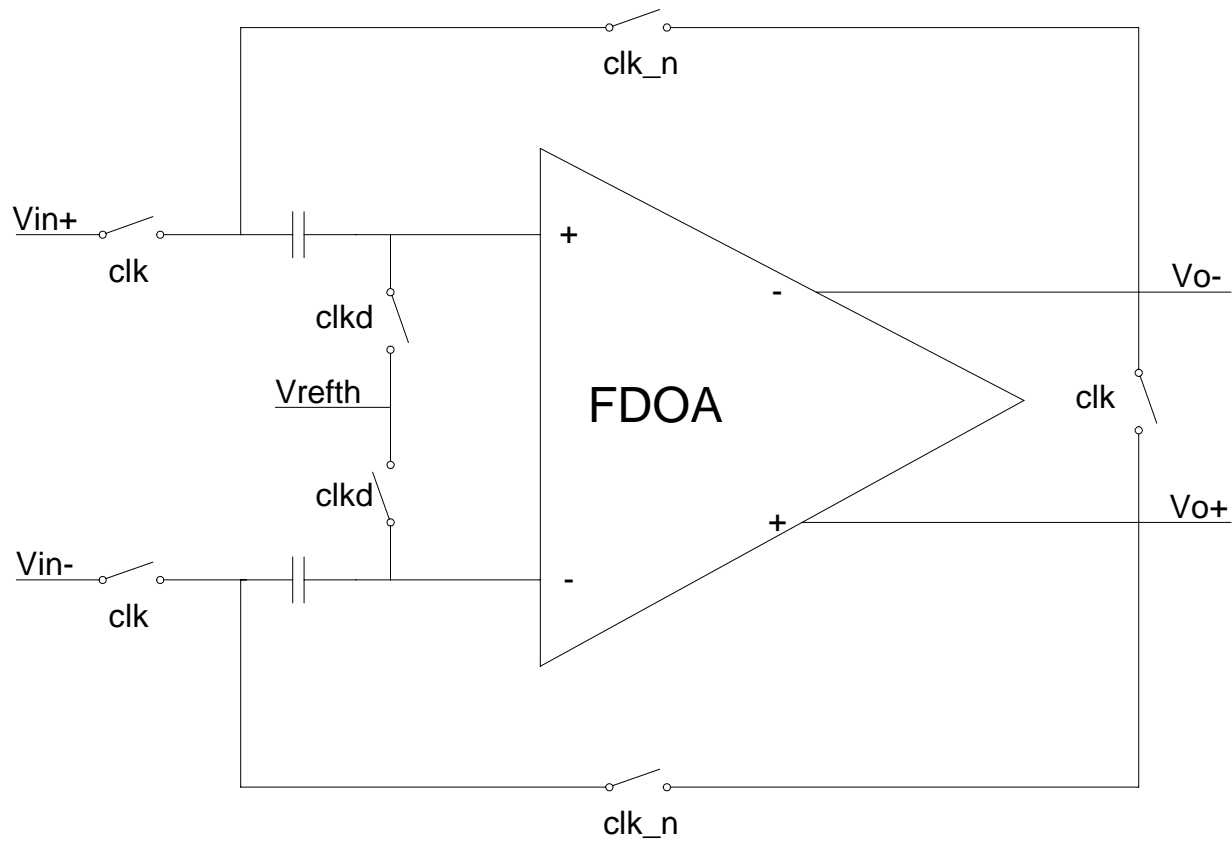
### III. Channel architecture


- Track and hold
  - 12 bit: flip-around architecture



### III. Channel architecture

- Fully differential Op Amp
  - Folded cascode + Miller stage with CMFB

| FDOA specifications |              |
|---------------------|--------------|
| Parameter           | Value        |
| Gain bandwidth      | 500 MHz      |
| Phase margin        | > 65°        |
| Slew rate           | > 0.5 V/ns   |
| $V_{CM}$            | 1.2 to 1.8 V |

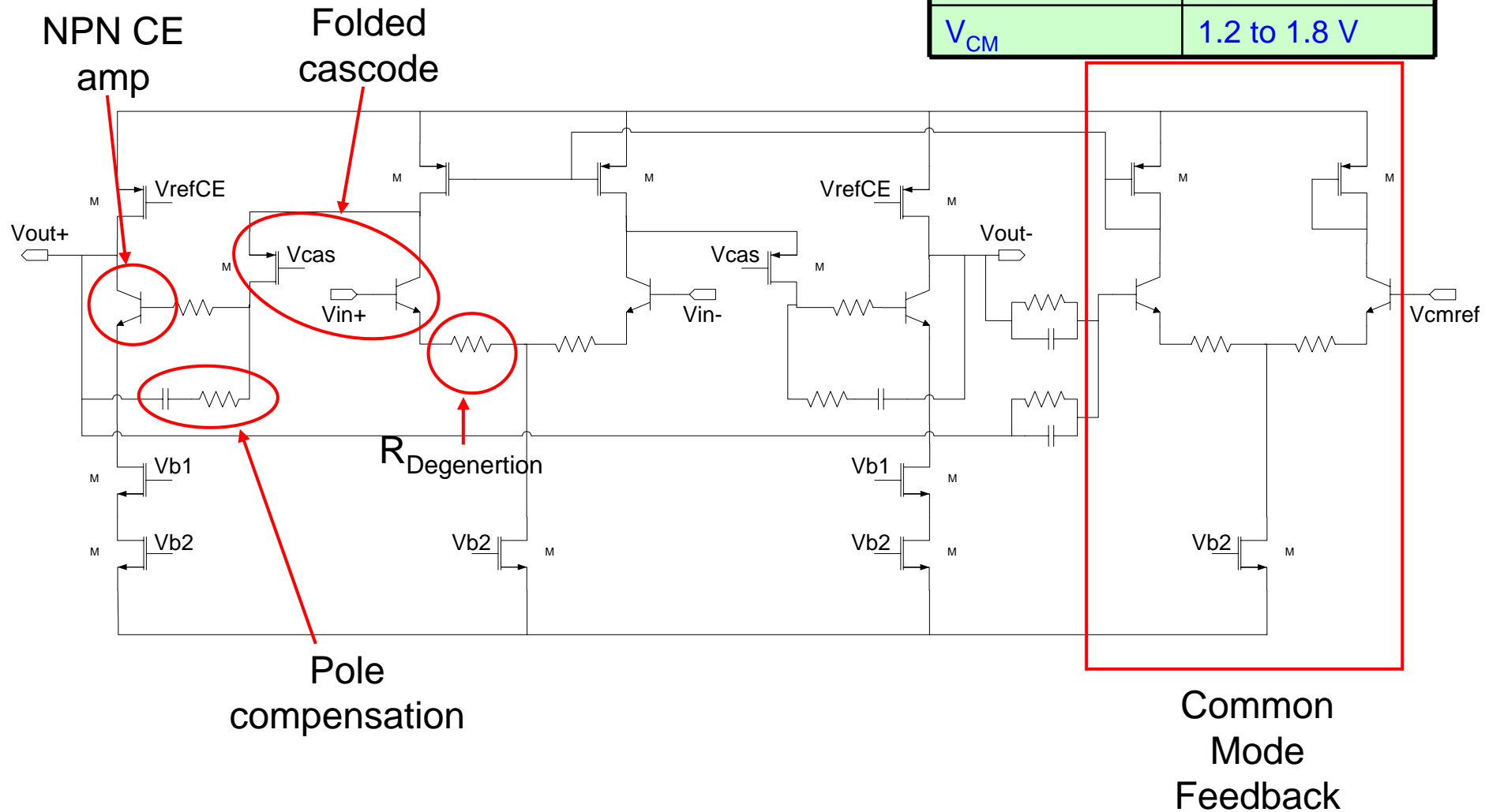

Common  
Mode  
Feedback

## IV. Technology: choice of technology

- **SiGe BiCMOS is preferred:**

- SiGe HBTs have higher  $gm/I_{bias}$  than MOS: less noise, less  $Z_i$  variation
- SiGe HBTs have higher  $f_t$  (>50 GHz): easier to design high GBW amplifiers

- **Several technologies available:**

- IBM
- IHP
- AMS BiCMOS 0.35  $\mu m$

|                                    | IBM          | IHP          | AMS          |
|------------------------------------|--------------|--------------|--------------|
| HBT $f_t$                          | > 100 GHz    | 190 GHz      | 60 GHz       |
| CMOS                               | 0.13 $\mu m$ | 0.13 $\mu m$ | 0.35 $\mu m$ |
| Proto Cost<br>[€/mm <sup>2</sup> ] | > 3 K        | > 3 K        | 1 K          |

- **AMS is preferred**

- Factor 2 or 3 cheaper
- Too deep submicron CMOS not required / not wanted:
  - Few channels per chip (4 ?)
  - Smaller supply voltage
  - Worst matching
- Radiation hardness seems to be high enough (to be checked)

## IV. Technology: radiation tolerance

- Requirements:

- Dose in 5 years (TID): 10-20 krad
- Neutron fluence?

- AMS SiGe BiCMOS 0.35 um should be ok:

- Omega studies about ILC calorimeters...
- ATLAS: CNM studies: <http://cdsweb.cern.ch/record/1214435/files/ATL-LARG-SLIDE-2009-337.pdf>
- **CMS: Technology adopted for HCAL upgrade (QIE10 chip)**
  - Total radiation dose = 10 krad = 100 Gy
  - Neutron fluence =  $10^{13}/\text{cm}^2$
  - Charged hadron fluence =  $2 \times 10^{10}/\text{cm}^2$

*Possible to share efforts on rad qualification? Engineering run? Cost...*

- Radiation tolerance should be taken into account at design:

- Cumulative effects:
  - Use feedback (global or local): minimal impact of beta degradation
  - Not rely on absolute value of components, use ratios but
- Transient events:
  - Guard rings for CMOS and substrate contacts: avoid SEL
  - Majority triple voting: SEU hardened logic (if any)



## V. Status and plans


### • Prototyped in AMS :

- Low noise current amplifier:
- Basic schemes
- Integrator:
  - High GBW fully differential OpAmp
- Track and hold
- Clock generation

### • Channel will be final with:

- Analogue multiplexer
- ADC driver
- Tuneability on gain, input impedance and integration plateau
  - To compensate process variations
  - To cover different operation conditions

*See Edu's talk*

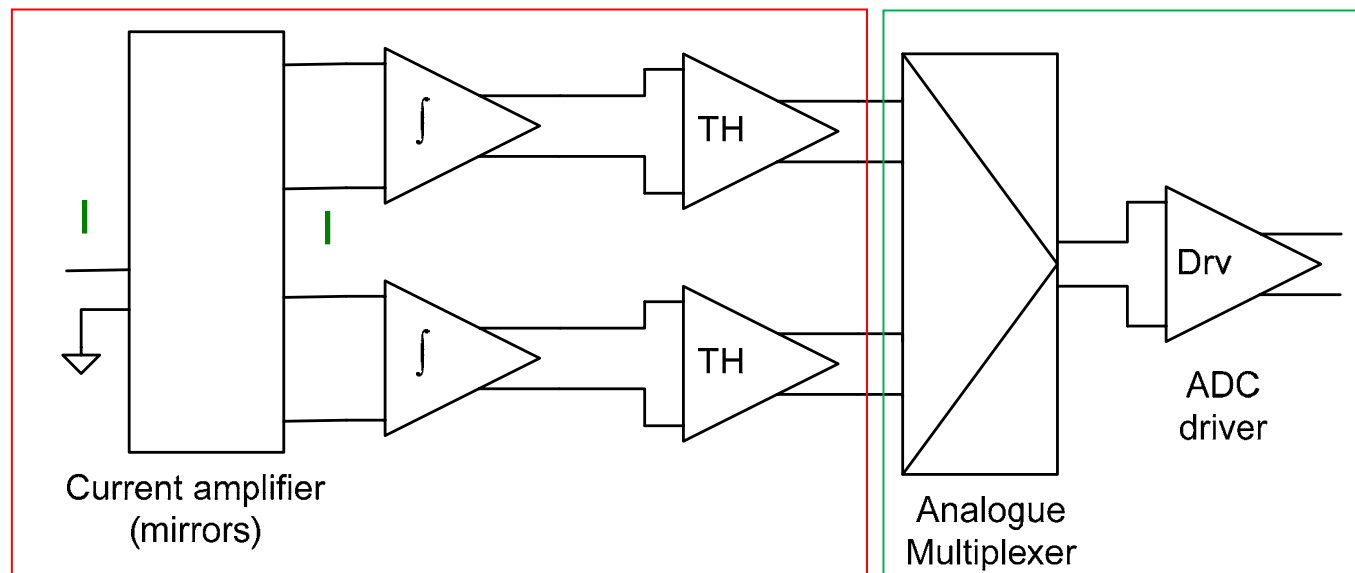




BACK-UP

# I. Introduction: voltage output versus current output

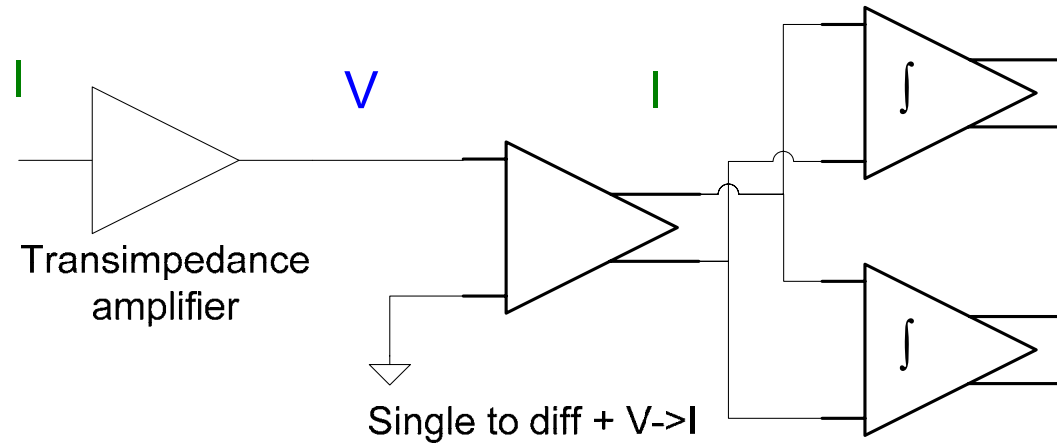
## • Voltage output:

- Pros:
  - Tested
- Cons:
  - I (PMT)  $\rightarrow$  V and V  $\rightarrow$  I (integrate)
  - Larger supply voltage required
  - External components
  - 2 additional pads per channel


 
## • Current output ("à la PS")

- Pros:
  - "Natural" current processing
  - Lower supply voltage
  - All low impedance nodes:
    - Pickup rejection
  - No external components
  - No extra pad
- Cons:
  - Trade-off in current mirrors: linearity vs bandwidth



## II. Preamplifier: current output / mixed feedback

- **Mixed mode feedback:**

- Inner loop: lower input impedance
  - Voltage feedback (gain): Q2 and Rc
- Outer loop: control input impedance
  - Current feedback: mirrors and Rf

- Variation of LAr preamplifier


- Current gain: m

- Input impedance


$$Z_i \approx \frac{1/g_{m1} + R_e}{g_{m2} R_c} + m R_f$$

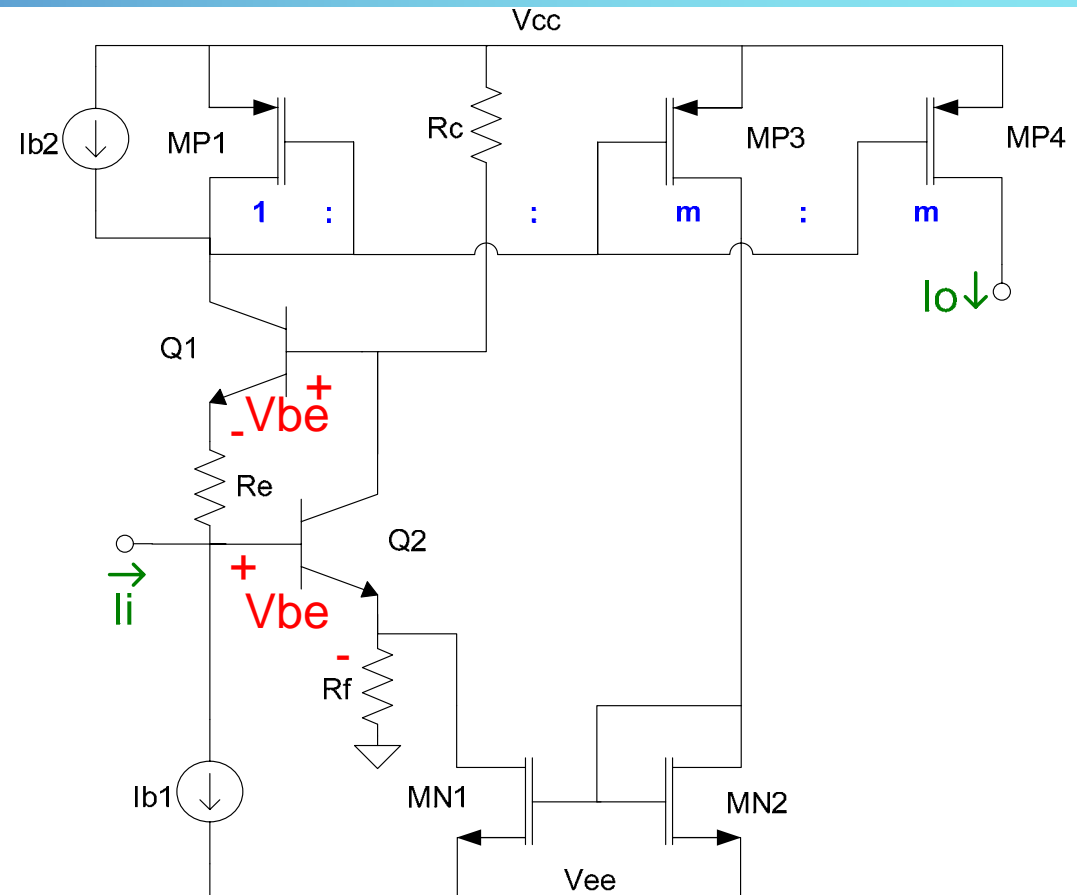- **Problem:**


- Voltage feedback for the super common base needs 2 Vbe (about 1.5 V !)
- Small room for current mirrors with 3.3 V
  - Need cascode current mirrors
  - 5 V MOS available: but poor HF performance


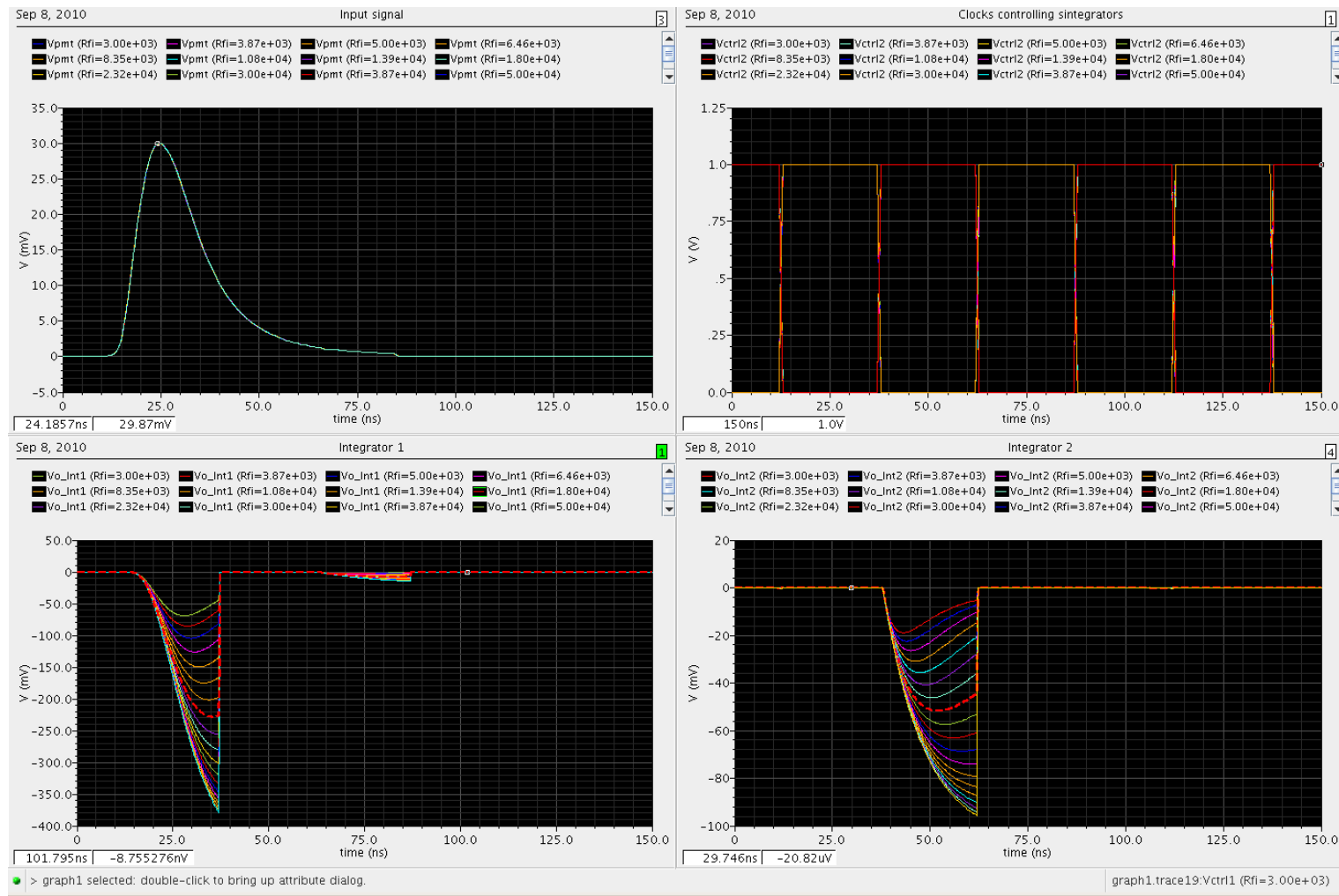
# • Possible alternative to delay line clipping or gaussian shaping



 - Possible alternative to delay line clipping or gaussian shaping



## IV. Technology issues: effect of process variations

- Input impedance is the key point
- Two types of parameter variation simulated
  - Mismatch between closely placed devices (local variation component to component)
    - No problem: 1 % level
  - Process variation (lot to lot):
    - Problem: 10-30 % level !! (uniform distribution)
      - Pessimistic: experience tell that usually production parameters are close to the typical mean values
- In principle process variation affects whole production (1 run)
  - Could be compensated with an external resistor in series / parallel with the input
- Variation wafer-to-wafer or among distant chips in the same wafer:
  - Can not be simulated
  - Higher than mismatch and lower than process variation
  - According to previous experience: 2-3 % sigma: BUT NO WARRANTY
- Should we foresee a way to compensate it?
  - Group (2-3) chips and:
    - Different pcb (2 - 3 different external resistor values)
    - Tune a circuit parameter
  - Automatic tuning

## IV. Technology issues: effect of process variations

### • Input impedance controllable by:

- Tune feedback resistor  $R_f$ 
  - Difficult: small value ( $R_{on}$  of the switch)
- Tune second feedback current
  - Binary weighted ladder (3 bits?): simple

### • How control current ladder control?

- Group ASICs a fix the value, set by:
  - External jumper
  - Slow control: dig interface required
- Automatic tuning
  - Reference voltage
    - Reference currents: external or band gap
    - External resistor
  - Wilkinson or SAR ADC style logic

