



Progress on ICECAL prototypes and chip tests

Upgrade of the front end electronics of the LHCb
calorimeter

D. Gascón, E. Picatoste, A. Sanuy


Universitat de Barcelona
Institut de Ciències del Cosmos ICC-UB

Calorimeter upgrade meeting – CERN – July 22nd 2011

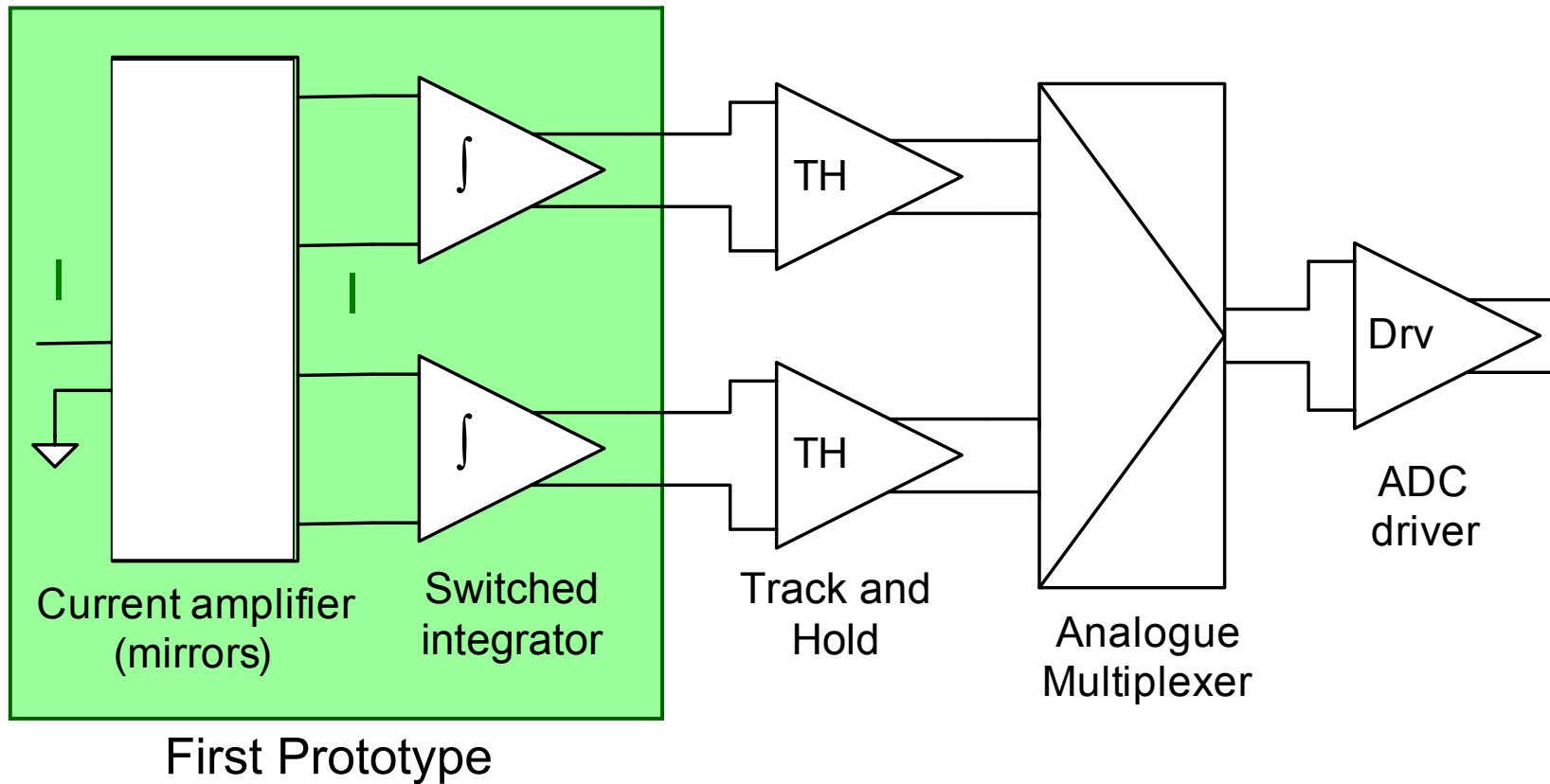1. First prototype
 - i. Key tests
 - ii. Test set-up
 - iii. Offset
 - iv. Noise
 - v. Input impedance
 - vi. Linearity
 - vii. Flatness: clock jitter vs input signal
 - viii. Characterization of preamp
2. Second prototype
 - i. What is new
 - ii. Flatness: clock jitter vs input signal
3. Summary

First prototype

- ECAL analogue FE IC: channel architecture




First prototype

- ICECAL chip

SiGe BiCMOS 0.35um
AMS 2 mm²
Submitted: June 7th 2010

Current preamp

Integrators

 


First prototype

- ICECAL chip

SiGe BiCMOS 0.35um
AMS 2 mm²
Received: October 2010
12 chips

Current preamp


Integrators

 


Key tests on the first prototype

- The purpose of this prototype is to test key points of a novel circuit idea:
 - Input impedance control by current feedback
 - Low noise performance
 - Dynamic range:
 - Linearity
- Also, to test critical aspects of a switched solution:
 - Offset between subchannels
 - Noise
 - “Flatness” of the integrator output
 - Effect of the clock jitter versus signal

Test set-up

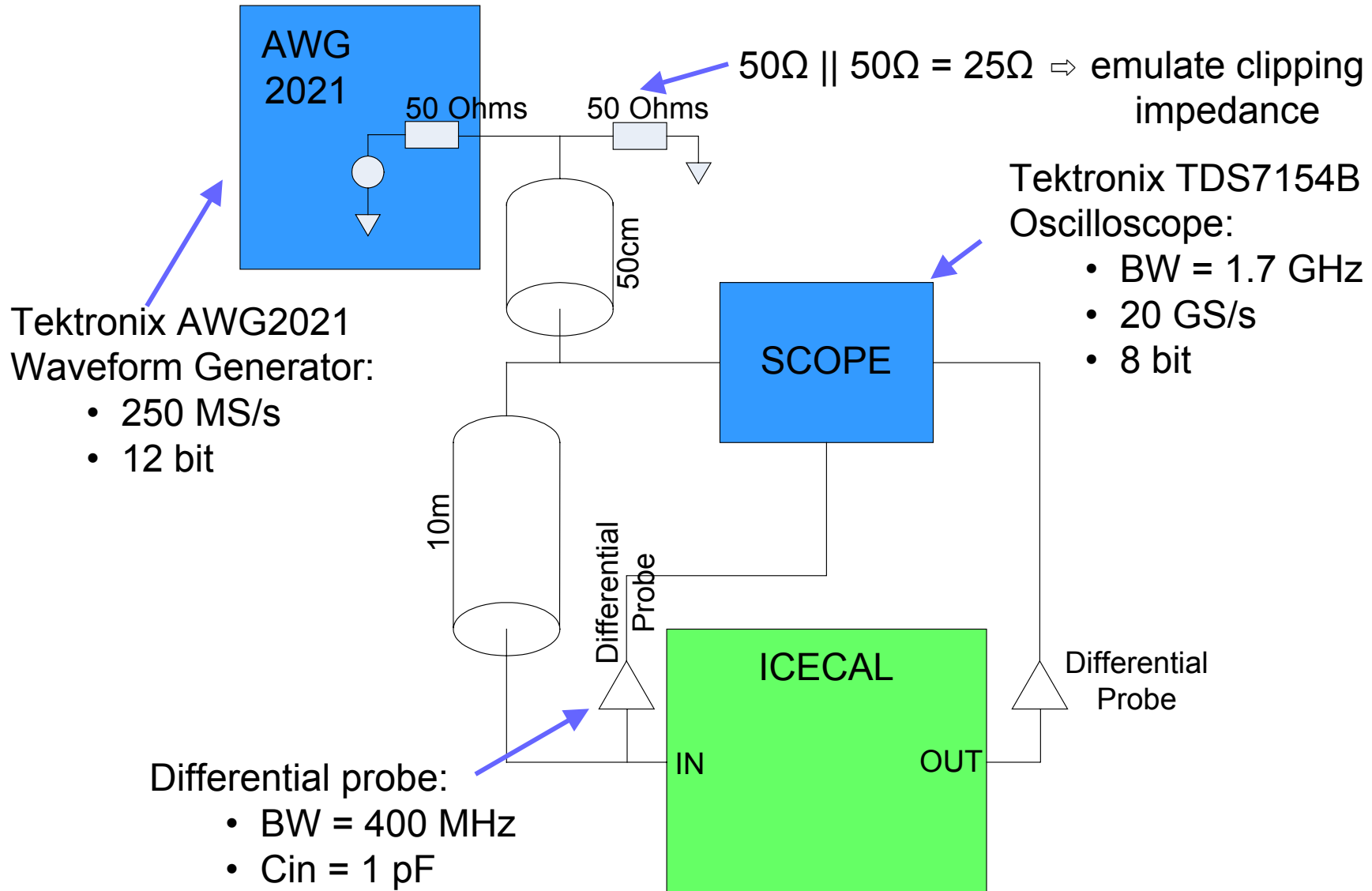


Test set-up: linearity

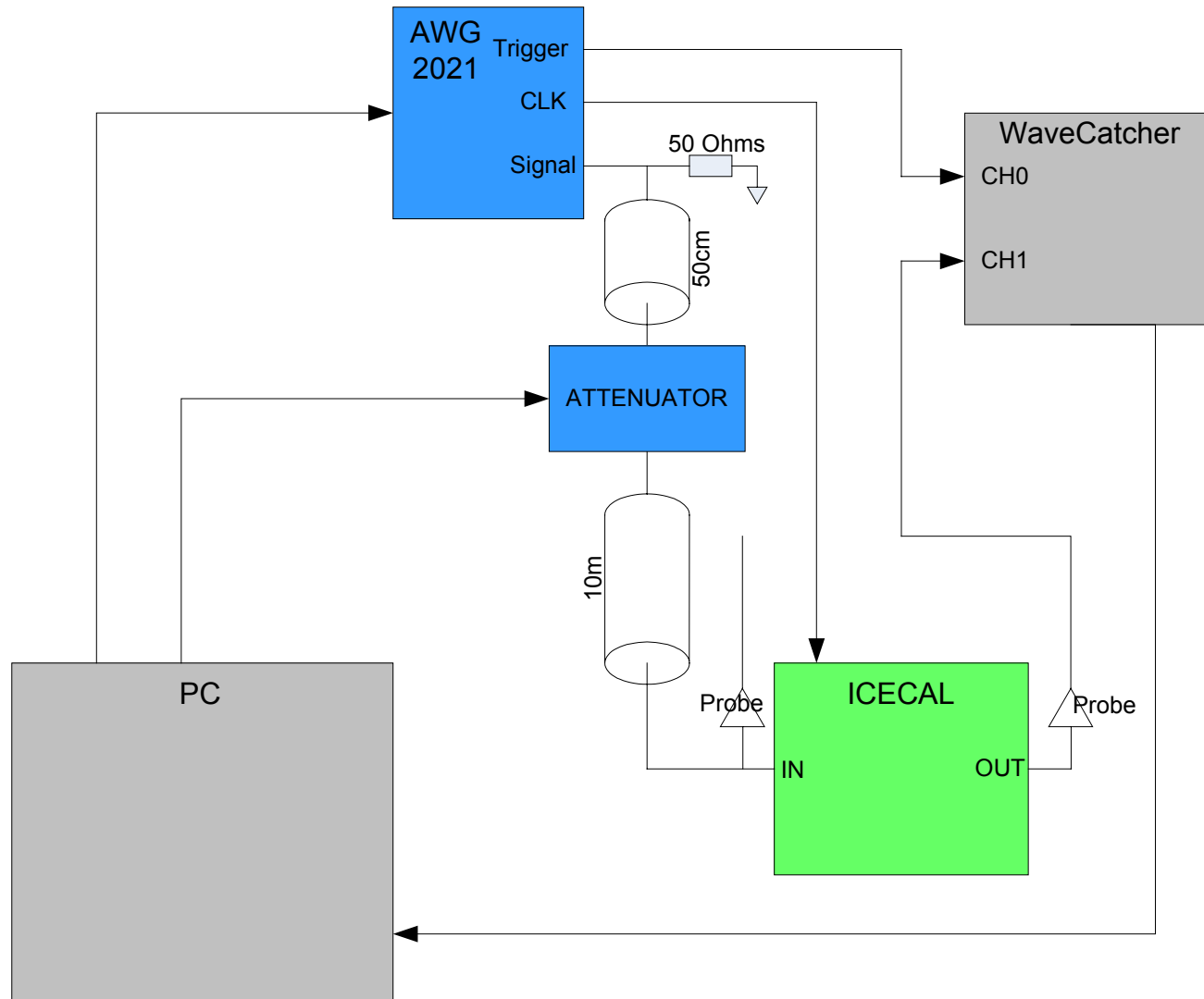

- **Attenuator:**
 - Better linearity than AWG (<1%)
 - No need for timing corrections
- **WaveCatcher:**
 - Better linearity than oscilloscope
- **PC:**
 - Automated system


Test set-up

 

22nd July 2011

LHCb Upgrade

First Prototype: Offset

 


Offset measurement:

Preamp current offset is integrated
=> Offset at output


5 % of dynamics

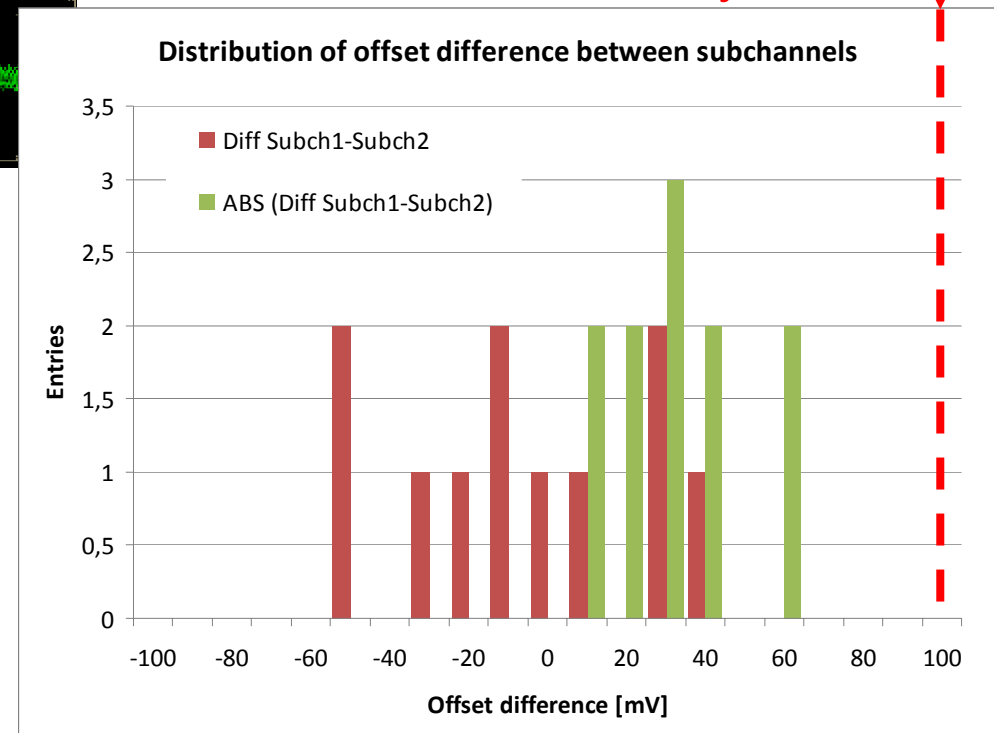- With AC coupling between ICECAL and ADC what really matters is the difference between the offset of the 2 subchannels
- Well below the 5 % of the full scale range (2 V)





Noise: simulation

- Transient noise analysis

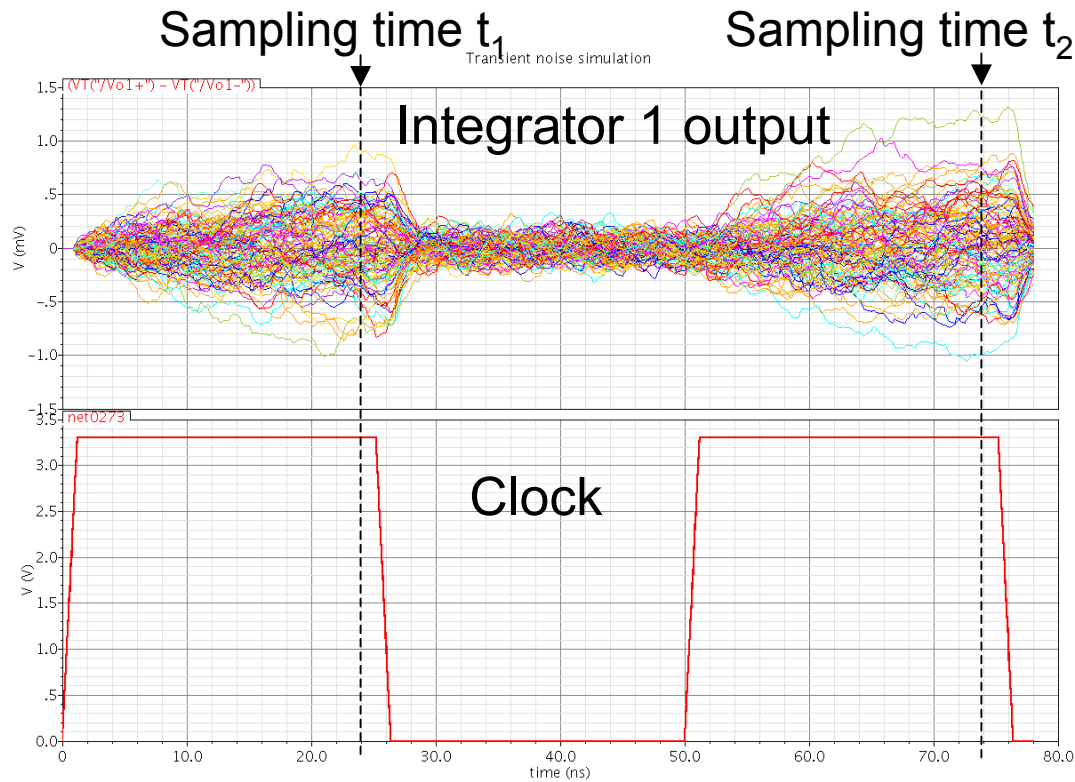


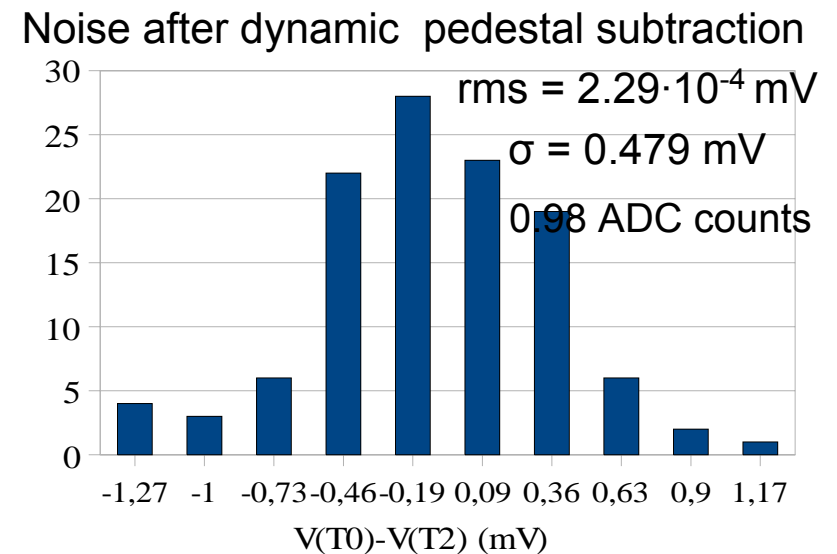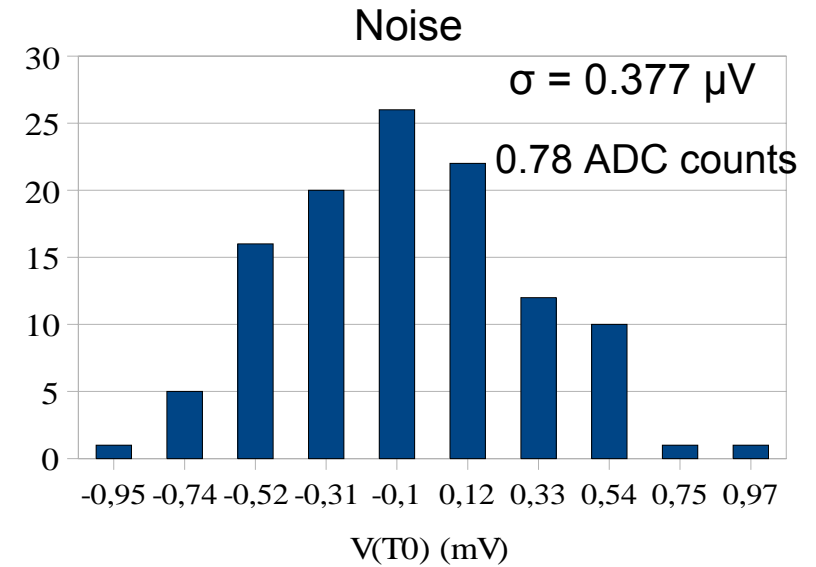- Correlated sampling: distribution of $V(t_1) - V(t_2)$ to remove LF noise




Noise

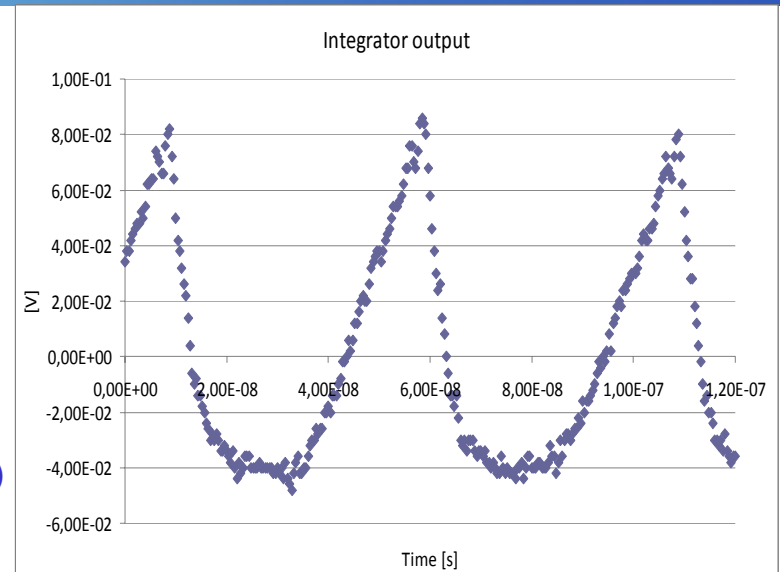
- The noise:
 - Generate a histogram of the voltage value by the end of the cycle (from 100 waveforms).
 - Gaussian fit => standard deviation
- Correlated Double Sampling (CDS) ↔ dynamic pedestal subtraction:
 - LF pick-up noise at measurements (chip connection/socket)
 - without CDS: 1.8 ADC counts
 - with CDS: 1.2 ADC counts (≈1 ADC count from simulations)



 
Output fluctuation at different sampling times



 Output fluctuation sampled with dynamic pedestal subtraction



Input impedance





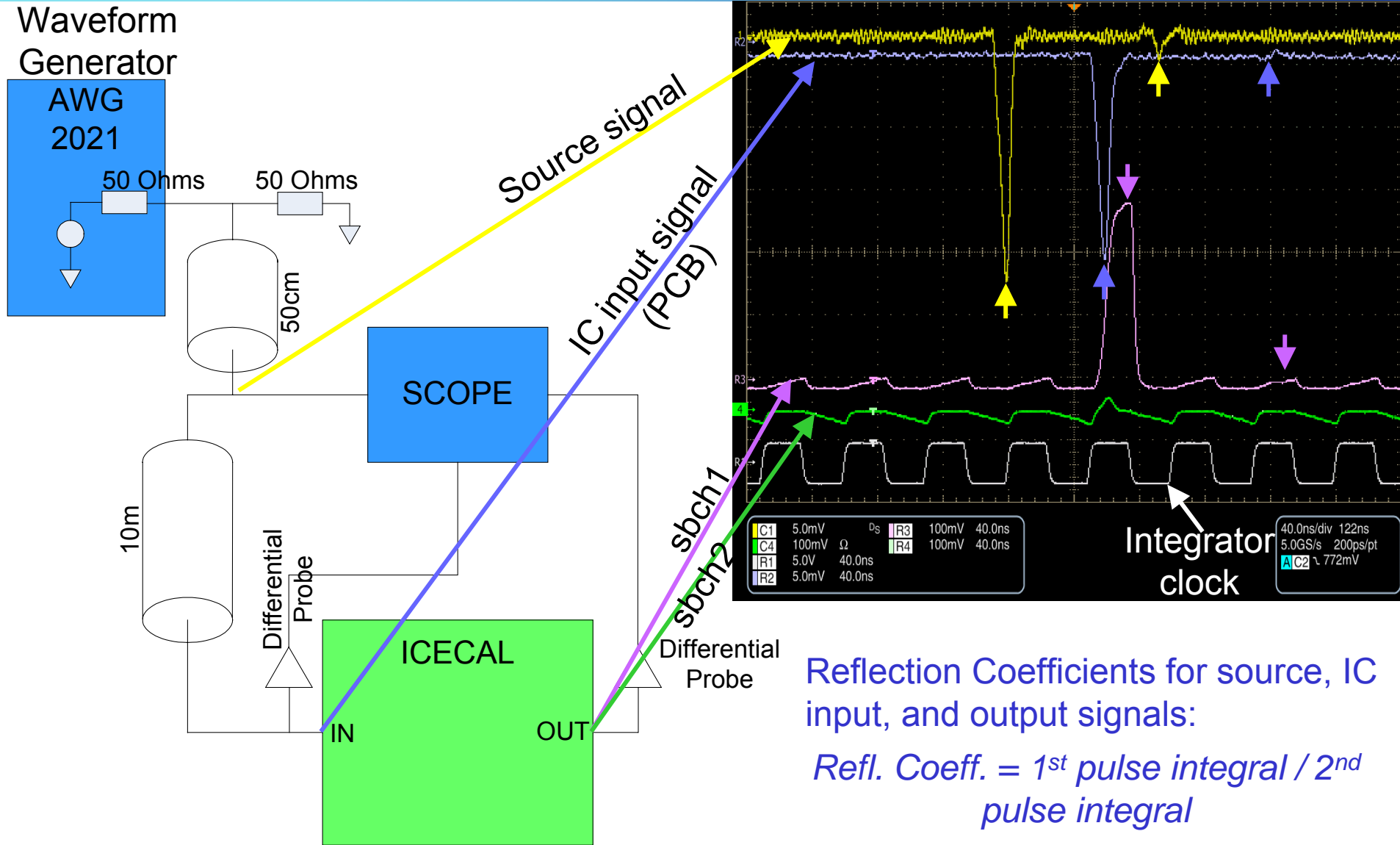


Reflection Coefficients for source, IC input, and output signals:

$$\text{Refl. Coeff.} = \frac{1^{\text{st}} \text{ pulse integral}}{2^{\text{nd}} \text{ pulse integral}}$$

Input impedance

Waveform Generator

     


Source signal

IC input signal (PCB)


sbch1

sbch2



Differential Probe

 


Input impedance

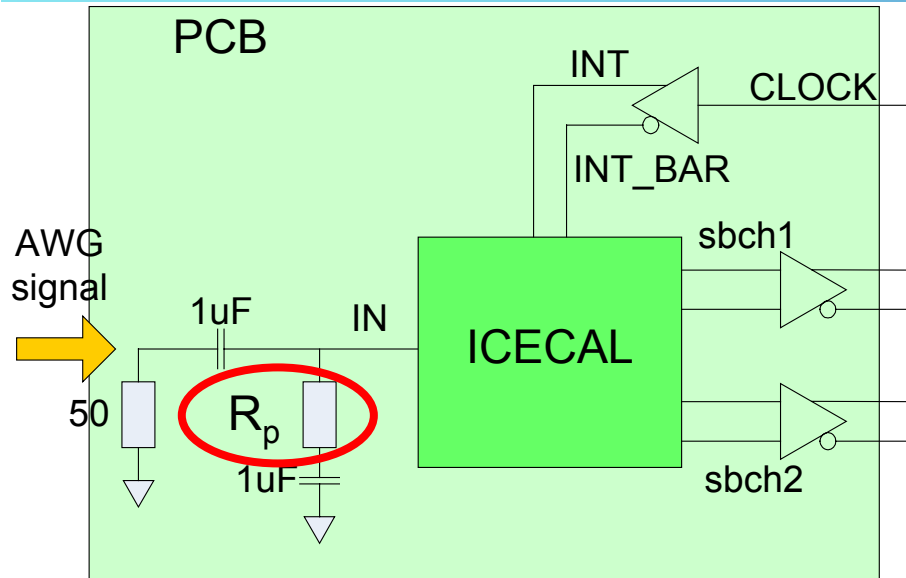

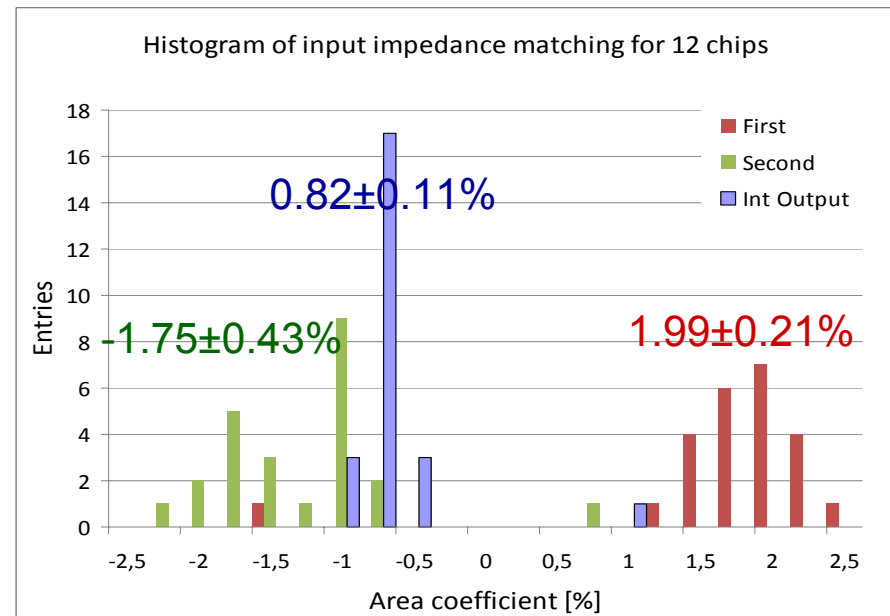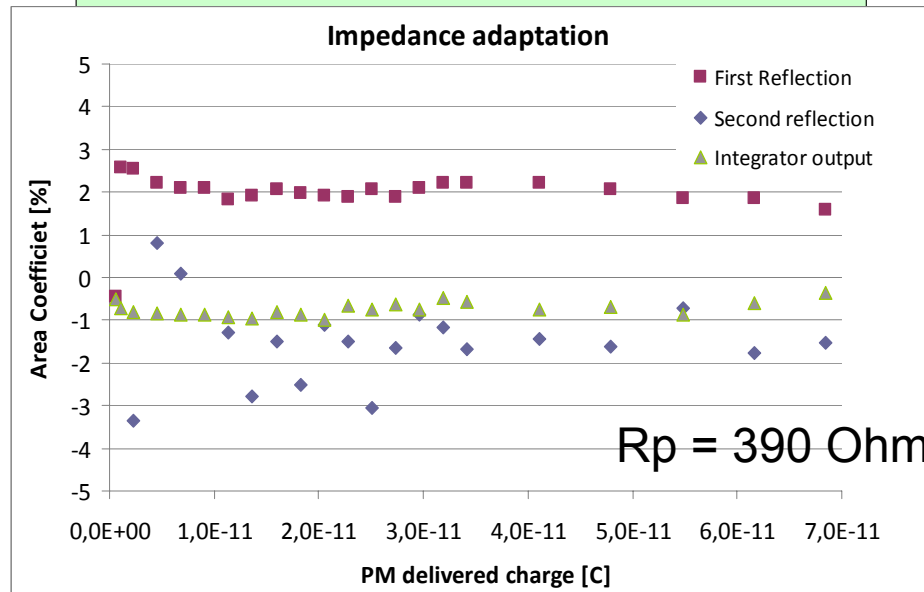- PCB input circuit with AC coupling with R_p :
 - Z_{in} a little higher than 50Ω
 - R_p used to fine tune Z_{in}
 - Optimal R_p is between 360 and 390Ω
- Dynamic variation of input impedance is $\ll 1\%$ for full dynamic (50 pC)
- Measurement error for second reflection is quite high for low amplitudes (diff probe noise)
- Low Refl. Coef. dispersion $< 0.5\%$




Linearity

 


- Relative linearity error $< 1\%$ for the full range (2V)
- Error is large for very low amplitude values
- Attenuator and WaveCatcher offer better linearity but the differential probe may need calibration

Plateau at the integrator output

 
- Due to clock jitter, the signal at the output must be stable (<1%) for 4 ns.
- Input signal AWG generated similar to clipped.
- Method:
 - Delay clock signal in 1ns increments
 - Use LEMO cable



 - The output variation is smaller than 1% for about 3 ns delay variation
 - Consistent for different signal amplitudes
- Can be improved using a resistor in parallel to the integrator capacitor (ICECAL2)




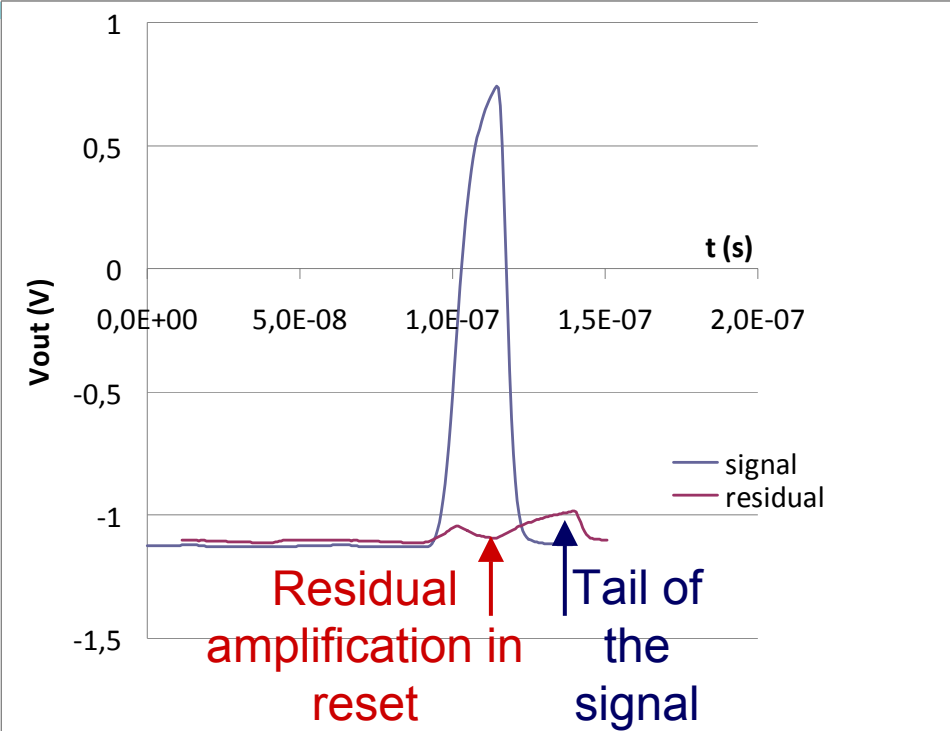Residual Amplification (switch ON resistance)




- The residual amplification in reset is 2% of the main signal
- Effect of the tail of the signal:
 - Caused by the signal tail; due to not perfect clipping
 - Measured 12% of the main signal

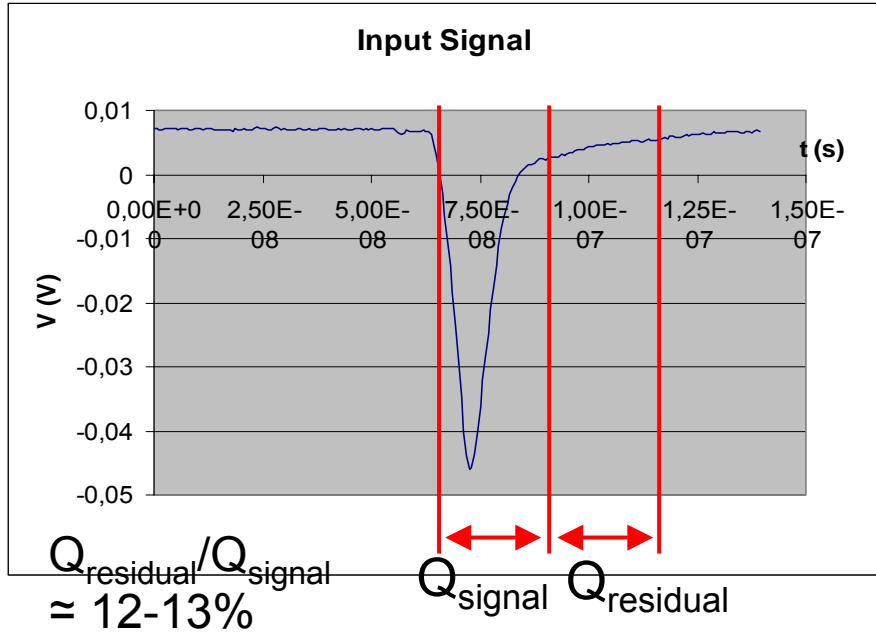- Measure at 2 points after cycle with main signal:
 - Just after reset period (beginning of integration period)
 - End of integration period (effects of the tail of the signal)
 - Clipping is not perfect
 - => small signal tail



Second Prototype

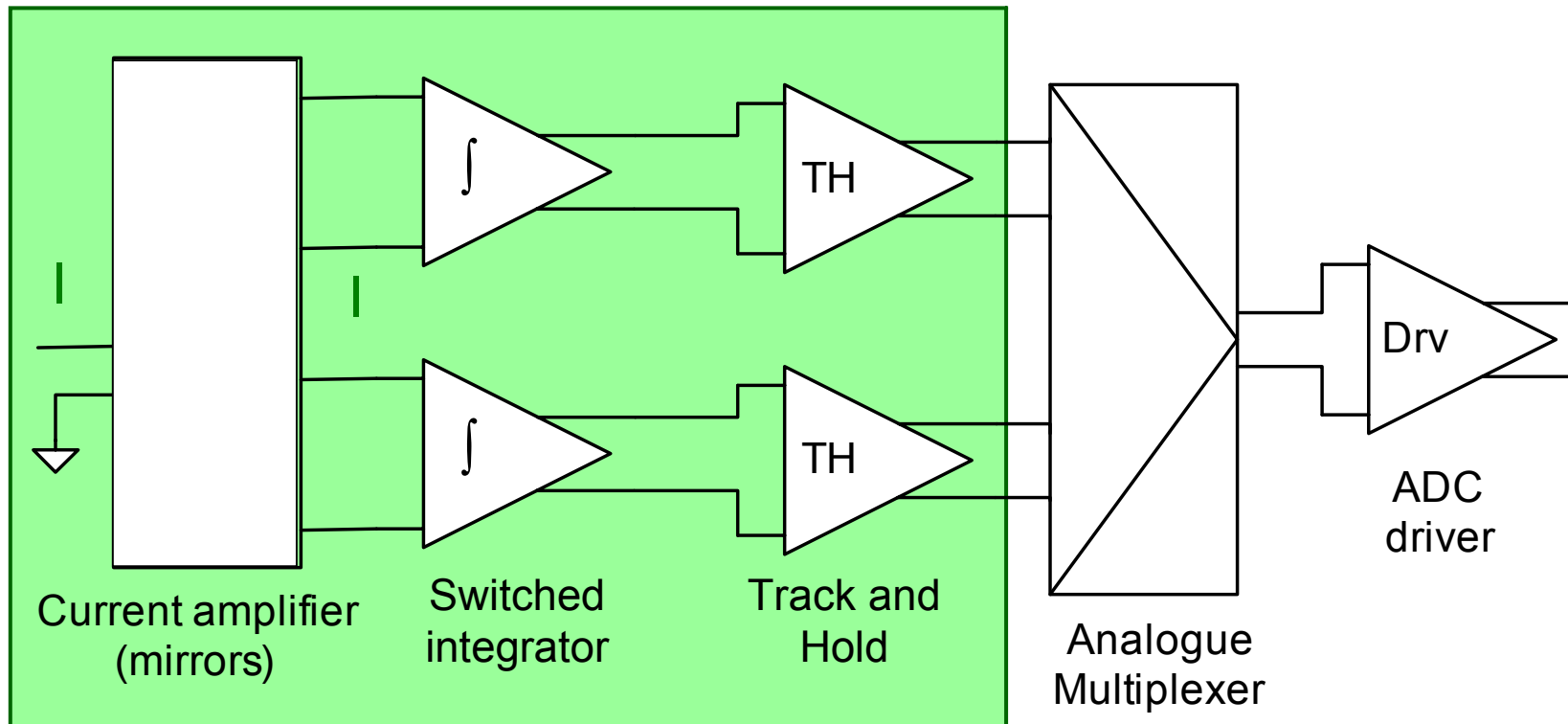ECAL analogue FE IC: channel architecture



Second Prototype:
ICECAL2


Second Prototype

ICECAL2 chip

SiGe BiCMOS 0.35um
 AMS 2 mm²
 Submitted: June 6th 2011


Current preamp

Integrators

 

Track-and-Hold

Second Prototype

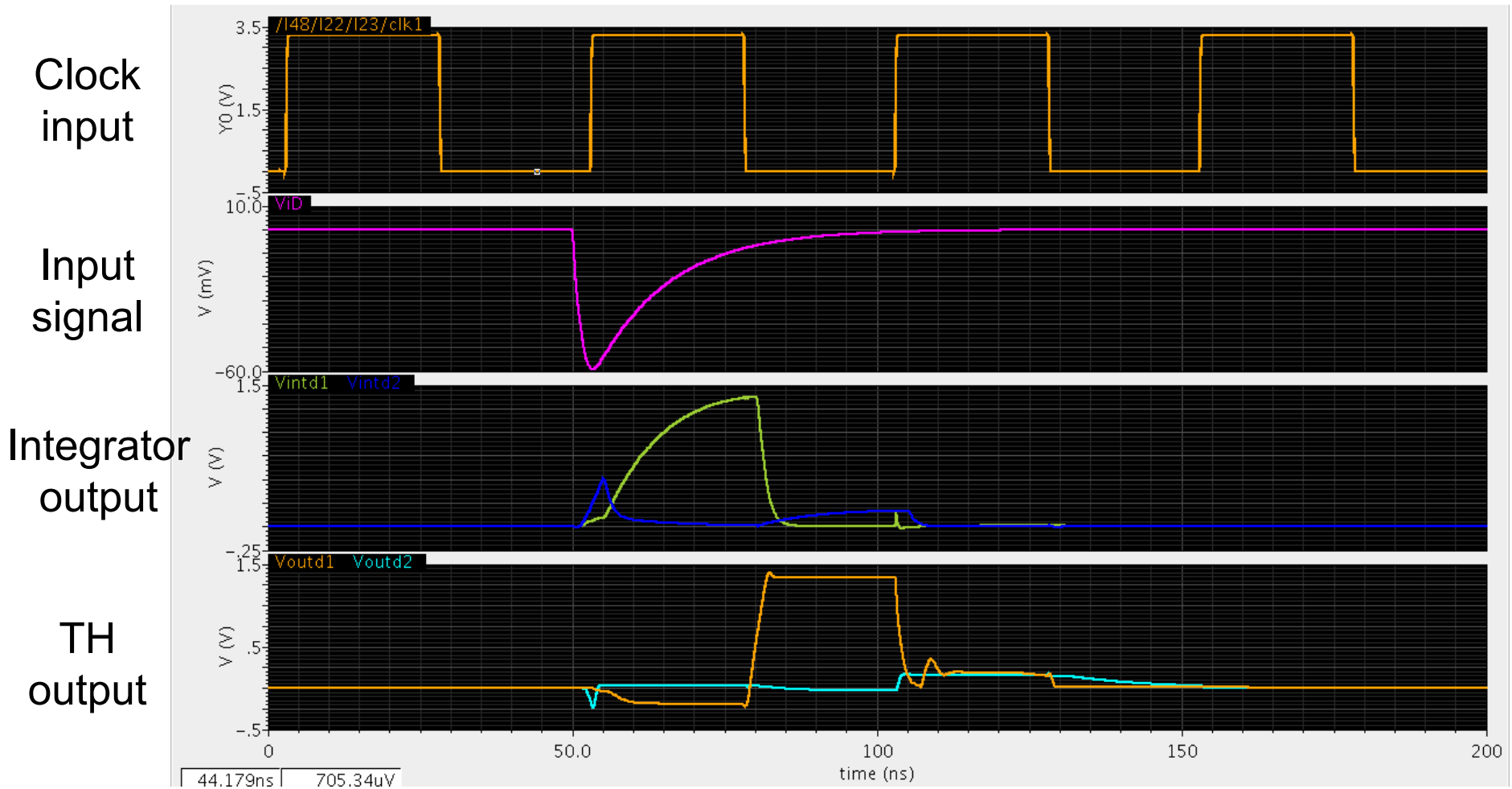

Summary

- Measurements of the first prototype of the input stage (preamp+integrator) are about finished
 - Principle is ok
 - Good results with 12 chips statistics
 - Need to study the effect of bias (op. point) variation
- A second prototype was submitted in June
 - It includes: preamp + integrator + track-and-hold
 - Added a feedback resistor to improve the integrator output stability
- We are preparing a new set-up: AUTOMATIZED IN CAT
 - Analog mezzanine including ICECAL+ADC
 - Calibrated and programmable attenuators
 - 12 bit 500 MHz (3 GS/s) DAQ: WaveCatcher


Back-up:



Test set-up



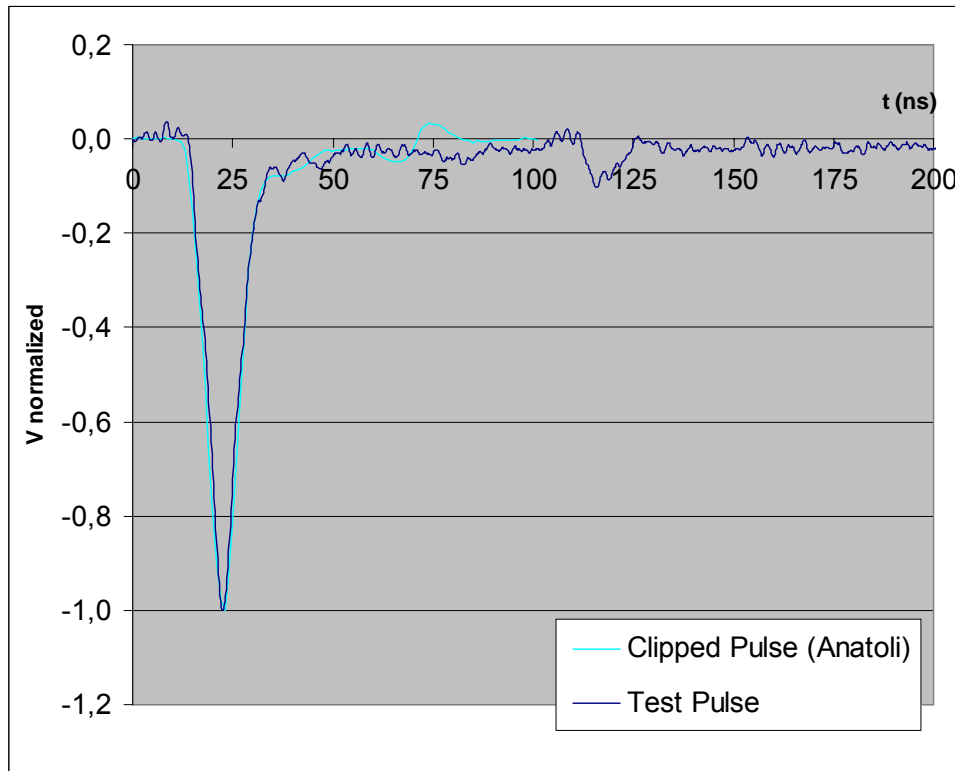Waveform Generator signal vs. Measured clipped signal (Anatoli)



Fast pulse (no tail) to measure reflections

