

ASIC design challenges

with a focus on precise timing

Gianni Mazza

INFN sez. di Torino


mazza@to.infn.it

June 19th 2024

Basic techniques for timing measurements


- Single sampling
 - Simpler system
 - Lower power
 - Lower data throughput
 - Requires time walk compensation
 - Requires pile-up management
- Multiple sampling
 - Digital post-processing
 - Provides both time and charge informations
 - Possibility to remove common noise
 - Requires high performance ADC

Timing systems: single sample

 

- The sensor signal is usually amplified and shaped
- A comparator generates a digital pulse
- The threshold crossing time is captured and digitized by a TDC
- TDC can be embedded on the front-end chip or external
- **Timing is derived from a single sample**

Time jitter - single sampling

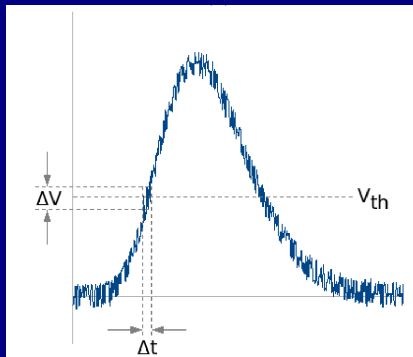


- The front-end rise time should be matched to the sensor collection time

$$\sigma_T = \frac{\sigma_V}{\frac{\Delta V(t)}{\Delta t}}$$
$$\frac{\Delta V(t)}{\Delta t} \approx \frac{V}{t_r} \rightarrow \sigma_T = \frac{t_r}{SNR}$$
$$t_r \propto \frac{1}{BW}, SNR \propto \frac{1}{\sqrt{BW}}$$
$$\sigma_T \propto \frac{1}{\sqrt{BW}}$$

$$t_r = 1 \text{ ns}, SNR = 10 \rightarrow \sigma_T = 100 \text{ ps}$$
$$t_r = 40 \text{ ns}, SNR = 20 \rightarrow \sigma_T = 2 \text{ ns}$$

Time walk


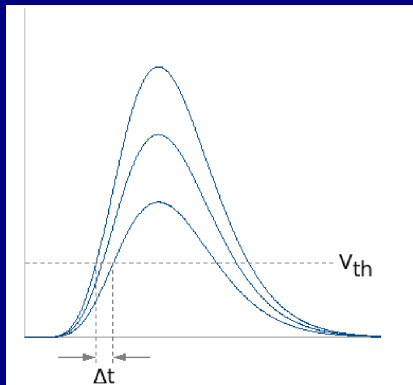


$$\Delta T = \tau_P \ln\left(\frac{2k}{2k-1}\right)$$

$$k = \frac{V_P}{V_{Pmin}}$$

- Pulses of same shape and different amplitude crosses the threshold at different times
- Large variations if SNR is low
- Even worse if also the signal shape changes
- Time walk introduces an error in time measurement
- Correction techniques :
 - Amplitude correction
 - Zero crossing comparator
 - Constant fraction discriminator

Simplest TDC : digital counter

 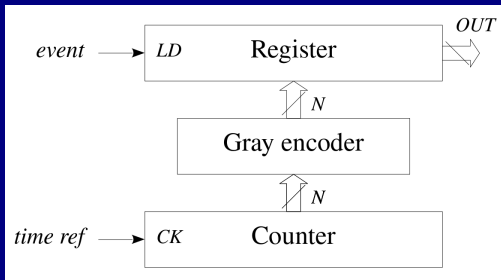


- Free running counter
- Upon hit arrival, the counter state is stored in a register
- **Gray-coded** counter if the hit is not synchronized with the clock
- Easy to extend to multiple channel - *caveat : power consumption*
- Time precision is limited by the clock period

$$\sigma_{TDC} = \frac{T_{CK}}{\sqrt{12}}$$


- *e.g. 1 ns resolution (i.e. 290 ps r.m.s.) requires a 1 GHz clock*

How to improve the resolution beyond the clock period

- Counter-based TDC ok for resolutions down to few ns, an additional circuit is required to measure the time elapsing between the event and the next clock transition
- Techniques to move into the ps resolution :
 - PLL, DLL
 - Closed loop system
 - Clock cleaning, clock multiplication (PLL)
 - Long delay chains (DLL)
 - Complex, high power
 - TAC
 - Simple, high time resolution
 - Dead time
 - Vernier line
 - High time resolution
 - Based on gate delays (PVT variations)
 - Long delay chains
 - Interpolation, RC delays

 

Timing systems: multiple samples

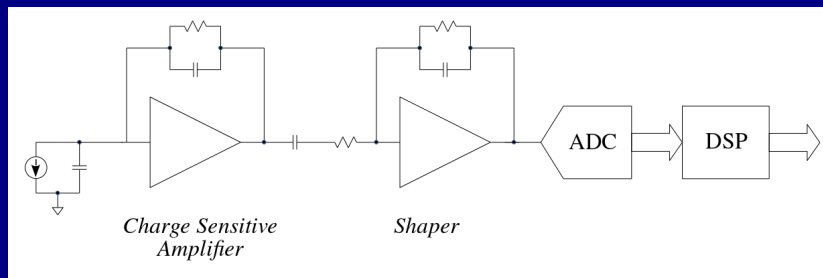


- The sensor signal is usually amplified and shaped
- The full waveform is sampled and digitized at high speed
- A high performance ADC is required
- In many systems, sampling and digitization are decoupled
- Timing is extracted with DSP algorithms from the digitized waveform samples
- **Timing is derived from multiple samples**

Choice of the sampling rate

- f_S : in principle the higher the better
 - *but increases cost, power consumption and data throughput*
- Shannon's theorem : $f_S > 2 \cdot f_{MAX}$
 - Mandatory for digital filtering
 - f_{MAX} is much higher than the -3 dB bandwidth
 - Not easy to calculate f_{MAX} from the pulse basic parameters ($t_r, t_f, FWHM$)
 - Anti aliasing filters
- Oscilloscope manufacturer rule of thumb : $f_S > 5 \cdot f_{MAX}$
- To emulate "analogue-like" timing algorithms, a minimum of 3 samples on the trailing edge are required. More samples allow the use of simpler algorithms
- If $f_S \gg 2 \cdot f_{MAX}$, the extra samples can be used to decrease the quantization noise (**oversampling**)


Comparison between ADC architectures

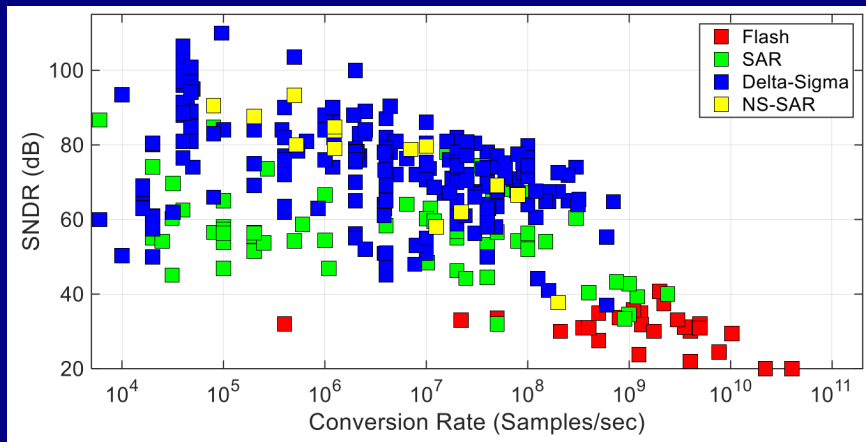

$$SNDR = 6.02 \times N + 1.78$$

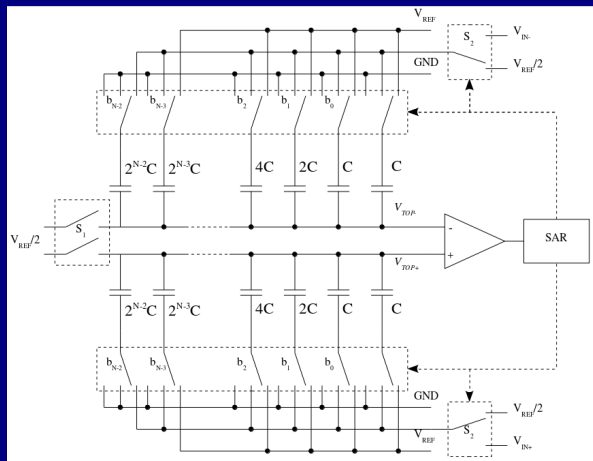B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]

Successive approximation ADCs with capacitive DAC



- Resolutions : 8-14 bits, sampling frequency : few hundreds MS/s
- Calibration required for $N > 10$ bits
- Conversion in N -clock cycles (+sampling time). Often requires a PLL


Multiple sampling : possible architectures

- Continuous DAQ


- All the data are acquired at the sampling rate
- The result is obtained after a fixed latency
- Require a continuously sampling ADC
- 12 bits, 1 GS/s \rightarrow 12 Gb/s per channel

- Zone of Interest DAQ

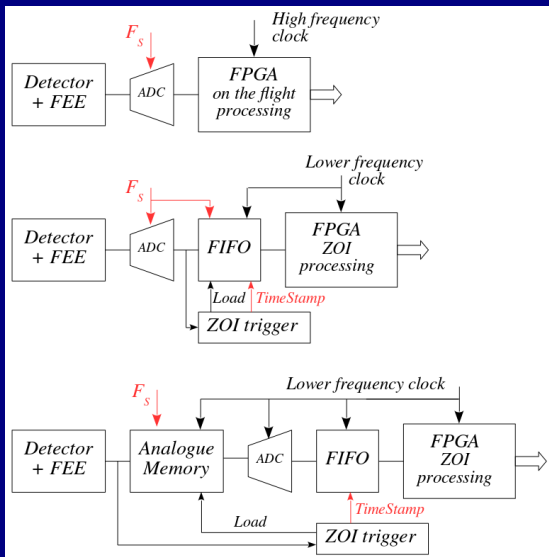- Require a trigger logic
- Strong data rate reduction
- No fixed latency
- No full rate ADC if an analogue memory is used.



Maximum ENOB vs input frequency

 

$$SNR_{ideal} = 20 \log_{10} \left[\frac{1}{2\pi f_{sig} t_j} \right]$$

$$SNR_{bits} = [6.02N + 1.76]$$

f_{sig} : signal maximum frequency


t_j : r.m.s. jitter

N : number of bits

Note :



- f_{sig} is the **signal** (not the **sampling**) frequency
- ENOB always smaller than ADC resolution (includes errors and non-linearity)

Design example : VMM3

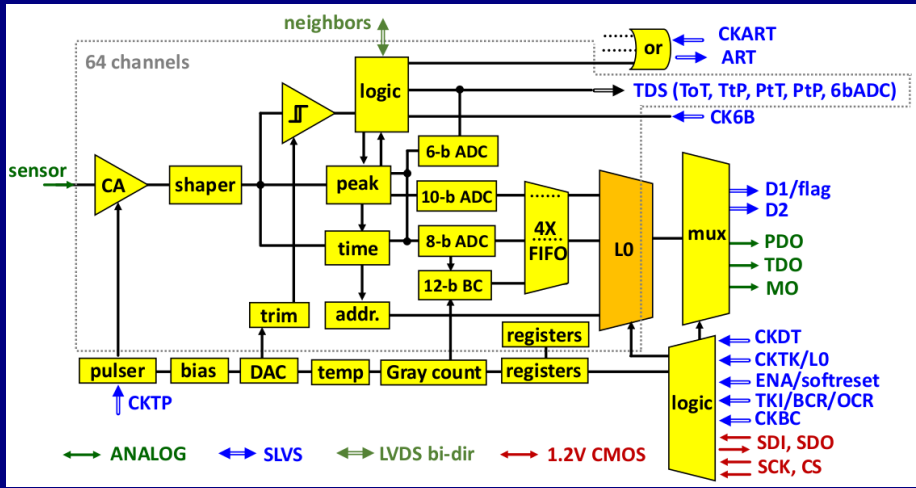

G. De Geronimo, *Prospects for VMM4*, RD51 Collaboration Meeting, Dec. 4-8 2023


Design example : HGCROC/HKROC

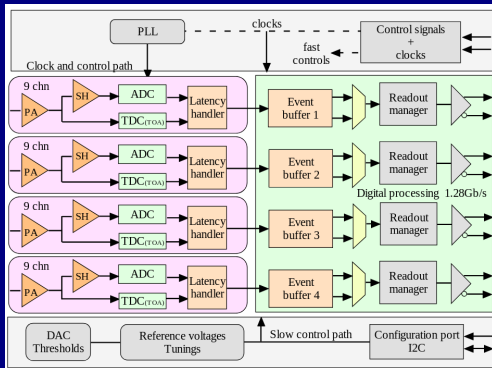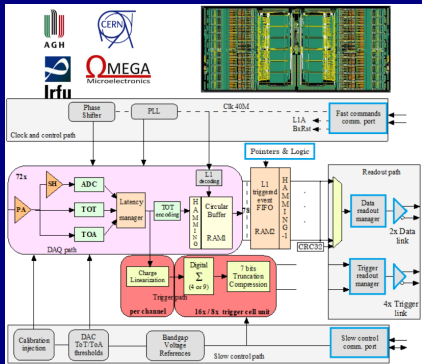


- ADC : 40 MS/s 10 bit (AGH Krakow), ToT to extend dynamic range
- Peak waveform sampling

C. De La Taille, ASICs for 5D calorimetry at Ω , 16th Pisa meeting May 27-31 2024

Design example : LiTE-DTU

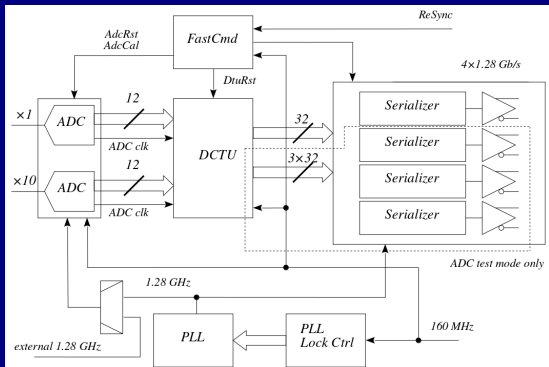

 - Two 12 bits, 160 MS/s ADCs (designed by Renesas)
- Clock multiplication PLL (from LpGBT)
- Technology : CMOS 65 nm




- Data Compression and Transmission Unit
- Fast command and lock control units
- 1.28 Gb/s serializers

Conclusions

- Time measurements : two main architectures
 - Single sample
 - Waveform sampler
- Single sample
 - Relative simple system
 - Time-walk correction required
 - Pile-up events can be difficult to detect
 - Key element : TDC
- Waveform sampler
 - Better signal reconstruction
 - Higher complexity and power requirements
 - High data rate
 - Key element : ADC
- Slow event rate allows for less demanding architectures

Backup slides

Extension with Time Interleaving

 


$$SNDR = 6.02 \times N + 1.78$$


B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]

PLL and DLL

PLL

 

DLL

 


PLL

- Can improve clock jitter
- Key element is the VCO

DLL

- Does not improve clock jitter
- Long delay lines
- Simpler to design

Time interleaved converters

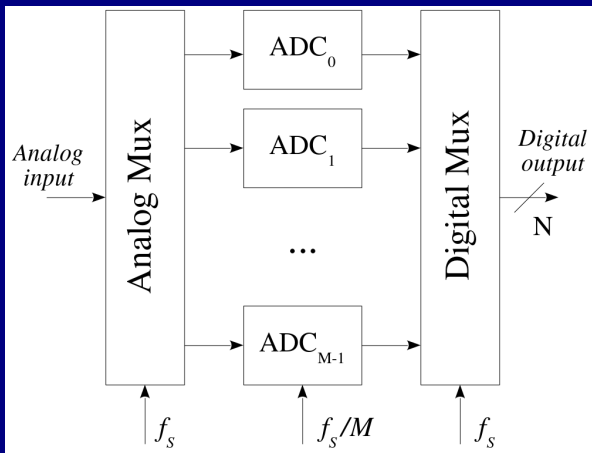

- Widely used in DSO
- Analog mux performances critical
- ADC intercalibration required