

# Some ideas about a FE for a SciFi tracker based on SiPM

A. Comerma, D. Gascón

**Universitat de Barcelona**

Institut de Ciències del Cosmos ICC-UB

- I. Introduction
- II. Measurements with SiPM + CTA preamplifier
- III. Simulations with a FE designed for PET
- IV. Simulations with ICECAL FE stage (LHCb Calo upgrade)
- V. Discussion

# I. Introduction

---

- Two basic approaches for the input stage:
  - Charge sensitive amplifier
  - (Super) common base/gate stages
- Our developments are focused on the later: speed and power ! :
  - SiGe AMS 0.35 um BiCMOS technology
  - But no serious problem to adapt to CMOS for this application
- We will present an overview of our developments related to SiPM readout:
  - Preamplifier for CTA project (tested)
  - FE stage for PET application (simulation)
  - Version (simulation) of the ICECAL chip (tested)
- Signal processing ?
  - Peak detector
  - Integration
  - ToT
- Measurements and simulations using SiPM model will be shown

## II. Measurements with SiPM + CTA preamplifier

### • Basic circuit:

- Super common base input
- Cascode current mirror with CB feedback
- Fully differential transimpedance amplifier

### • Performances


- $BW > 500$  MHz
- Low  $Z_i < 10$  Ohm up to  $> 500$  MHz
- Low noise ( $i_n = 10$  pA/sqrt(Hz))
- Differential: optimal CMRR and PSRR

### • But the current mirror can not stand a 1000 phe pulse

- Saturation at 500 to 1000 phe


### • Not enough for 16 bit...

### Simplified schematic


 

 
## II. Measurements with SiPM + CTA preamplifier

- Previous circuit is modified to split the input current by a novel technique:
  - Current is divided in the common stage
  - Different current mirrors for high and low gain
    - Each can be optimized for BW / linearity
  - Dedicated saturation control circuit is added to the HG mirror
    - Current division remains operational even if HG mirror saturates
    - Saturation threshold of HG mirror can be controlled
  - Range: > 6000 phe
    - True delta pulse with 500 MHz BW
    - No arrival time effect considered
  - Patent pending (cur. splitting has other possible applications)




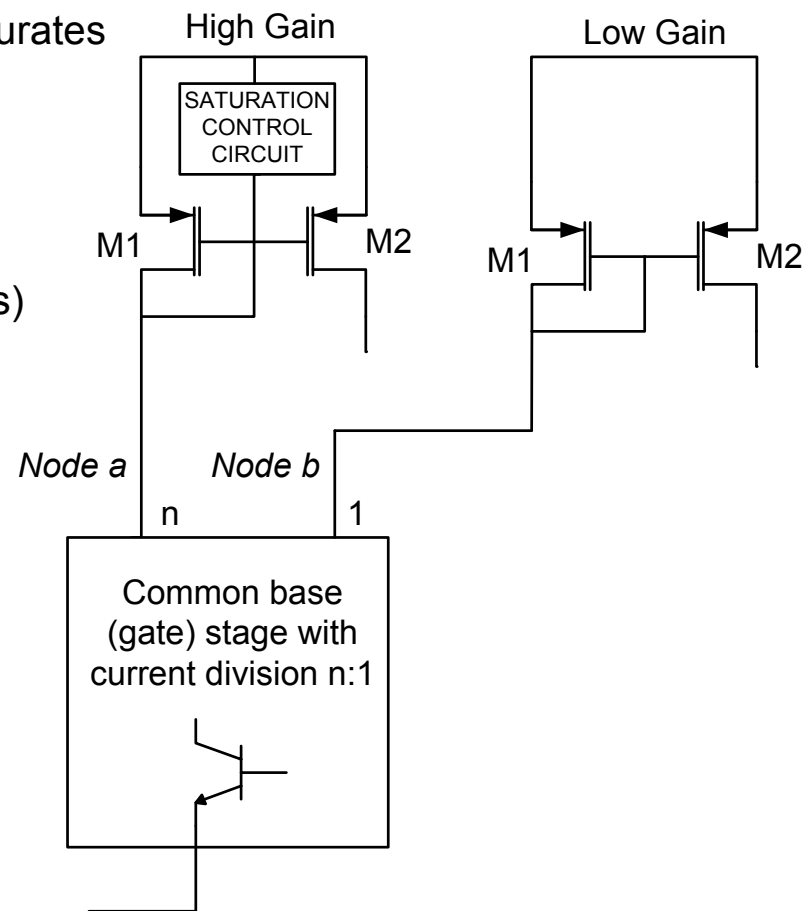
 
**PACTA chip**  
 SiGe BiCMOS 0.35um  
 AMS 2 mm<sup>2</sup>  
 QFN32 package



## II. Measurements with SiPM + CTA preamplifier

 
 
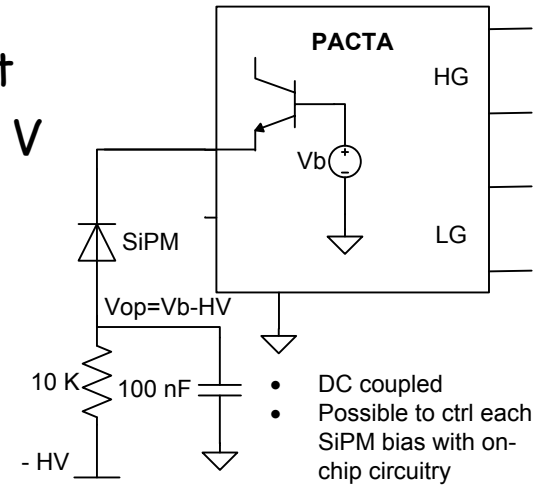
### • Preliminary tests with SiPM

- Low  $Z_{in}$  current mode circuit are well suited for SiPM readout
- We just took an available MPPC (S10931-050P), operated at 1 V overvoltage
- Recovery time seems to be dominated by internal SiPM time constant
  - $R_q(C_q+C_d) = 18$  ns, with  $(C_q+C_d)$  about 90 fF and  $R_q$  about 200K
  - PACTA  $Z_i$  related time constant is below 1 ns ( $15$  Ohm  $\times$  40 pF)



   
## II. Measurements with SiPM + CTA preamplifier

- Preliminary tests with SiPM
  - Bi-gain is also working


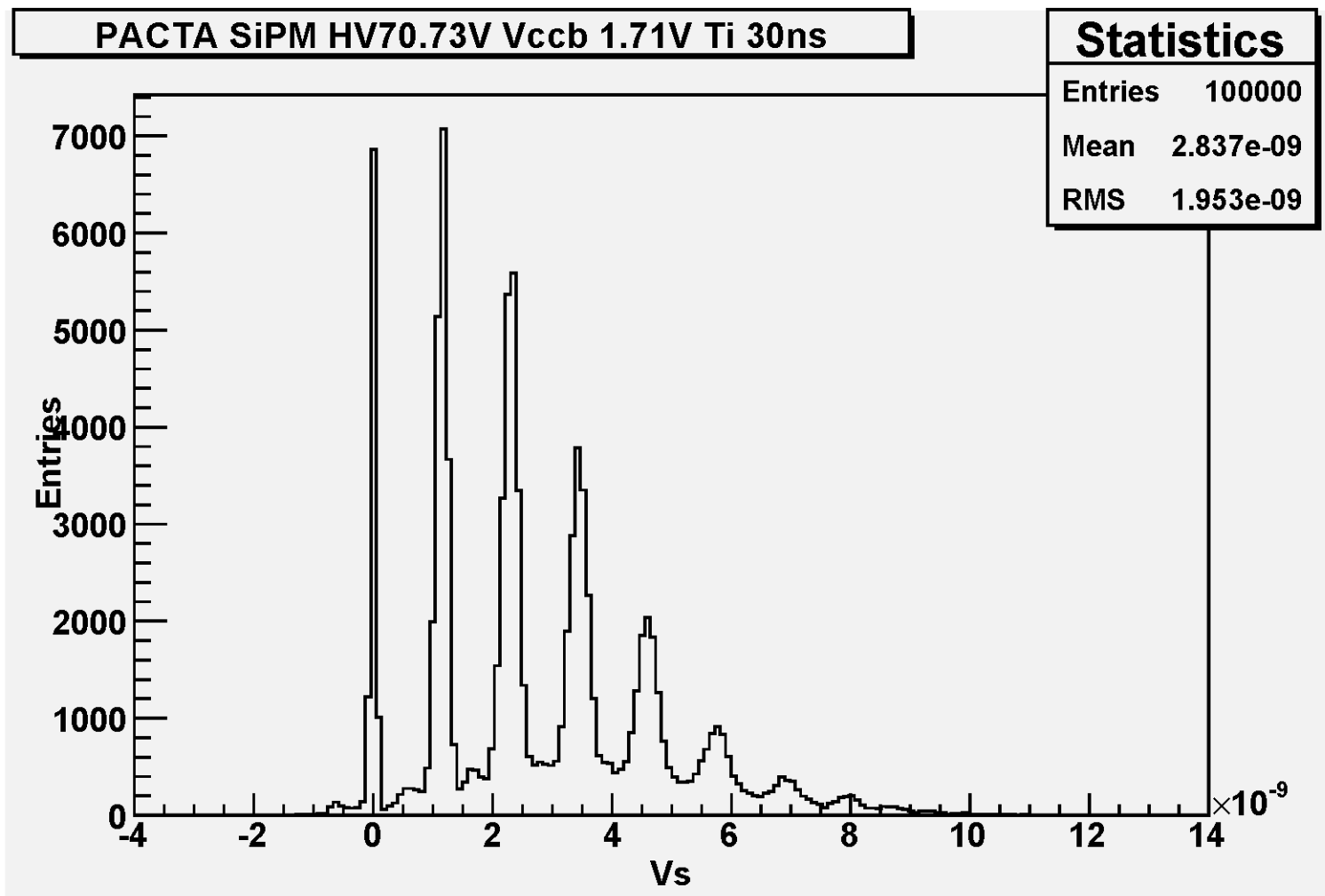
## II. Measurements with SiPM + CTA preamplifier

- Preliminary tests with SiPM
  - Charge spectrum






### III. Simulations with a FE designed for PET

- PACTA preamplifier could perform well as a VFE but some drawbacks:
  - Current division seems not necessary in this application, could be removed.
  - Limited voltage swing for SiPM adjustment:
    - Major problem
    - Related to common emitter amplifier feedback to decrease  $Z_i$
- Alternative feedback techniques:
  - FE for PET applications: OpAmp with input negative rail swing capability
  - ICECAL chip (LHCb calo upgrade): current mode feedback
    - Also used in BASIC chip for PET applications
- FE for PET applications
  - High gain with fast leading edge current discriminator
  - Low gain with TIA (on the long term, integrator)
  - Input impedance is 20 Ohm
  - Input ref. noise is 2-3  $\mu\text{A rms}$
  - Max. signal is  $> 9 \text{ mA peak}$
  - Power consumption about 5 mW / ch
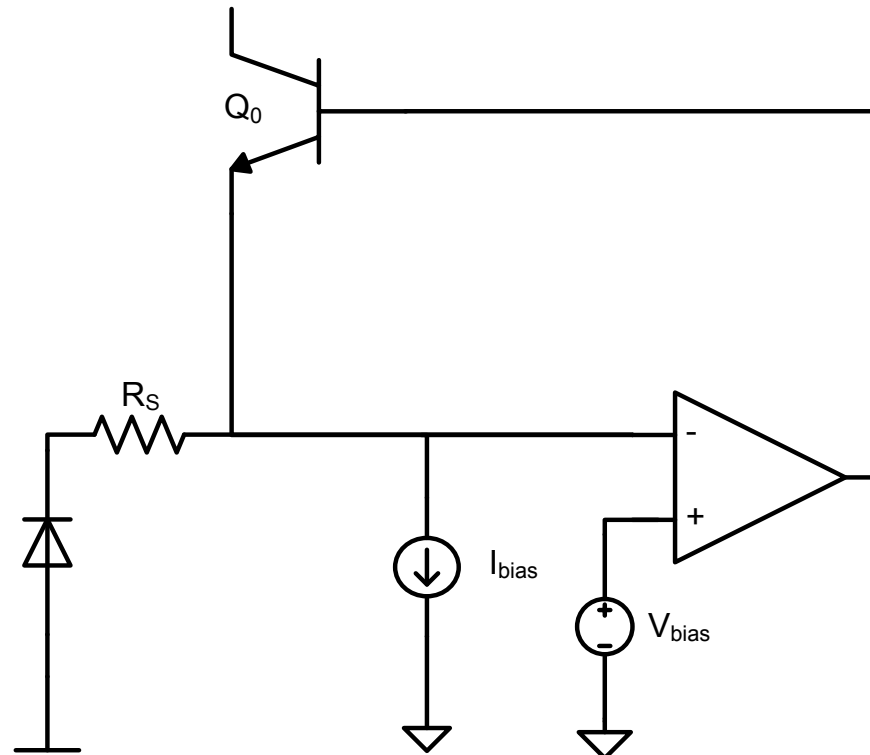
### III. Simulations with a FE designed for PET

- Simplified schematic of the input stage:


- OpAmp with input negative rail swing capability to decrease  $Z_i$  and control SiPM cathode
- Input impedance is about 20 Ohm
- SiPM cathode voltage can be tuned: 0 - 1 V


 
### III. Simulations with a FE designed for PET


- Transient response for 1 to 30 fired cells

*SiPM model adjusted to fit Guido's measurements*




### III. Simulations with a FE designed for PET

- Peak or integral measurements are ok

 
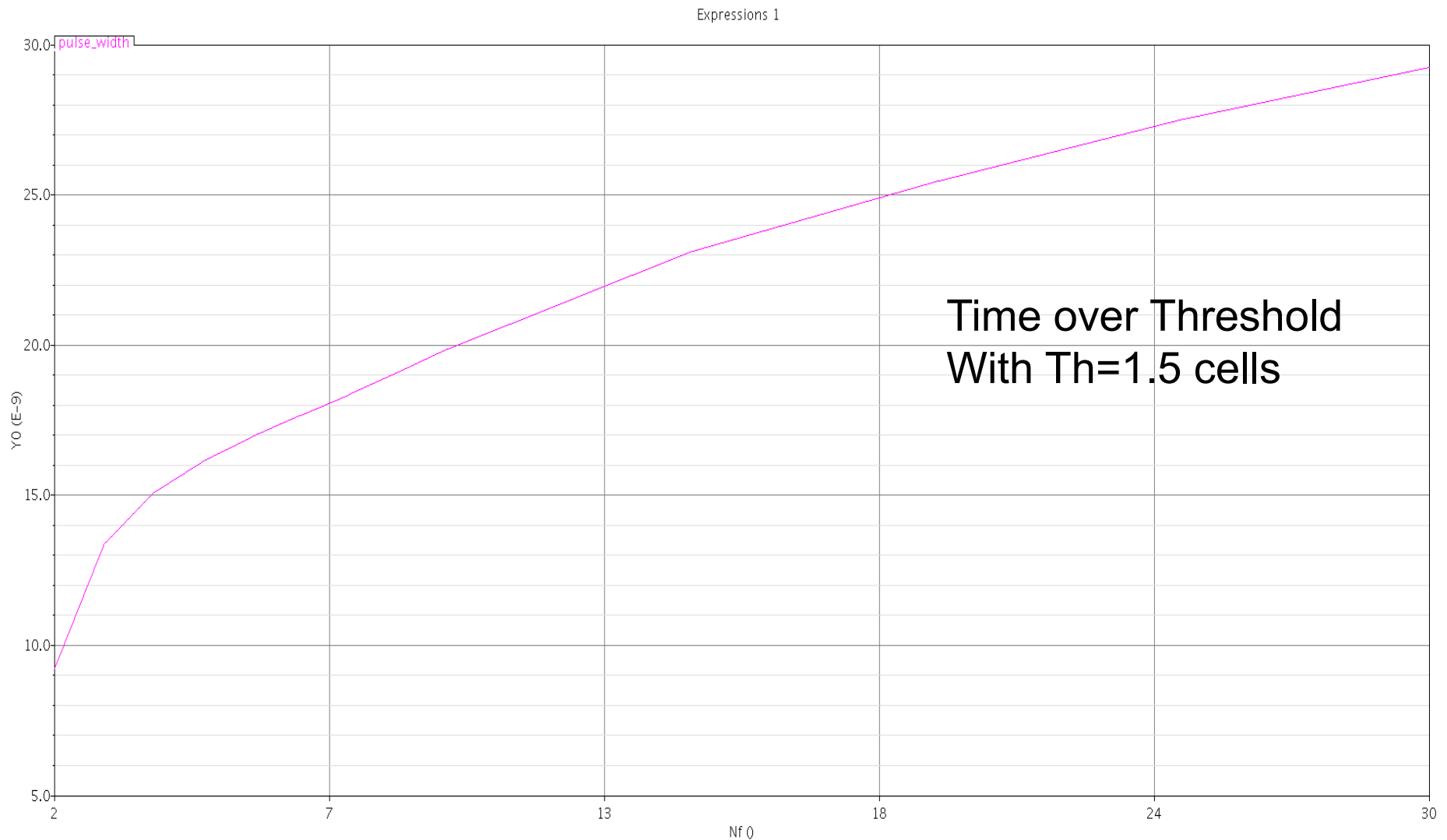
### III. Simulations with a FE designed for PET

- Is ToT feasible? What resolution (clock) is needed?



### III. Simulations with ICECAL FE stage (LHCb Calo upgrade)

- **Current mode feedback:**
  - Inner loop: lower input impedance
    - Current feedback (gain): mirror: K
  - Outer loop: control input impedance
    - Current feedback: mirror: m

- **Current gain: m**

- **Input impedance**


$$Z_i \approx \frac{1/\sigma + R_e}{1 + K} + \frac{K}{1 + K} m R_f$$

- **Current mode feedback used**

- Optical communications
- SiPM readout

- **For SciFi just remove outer loop**

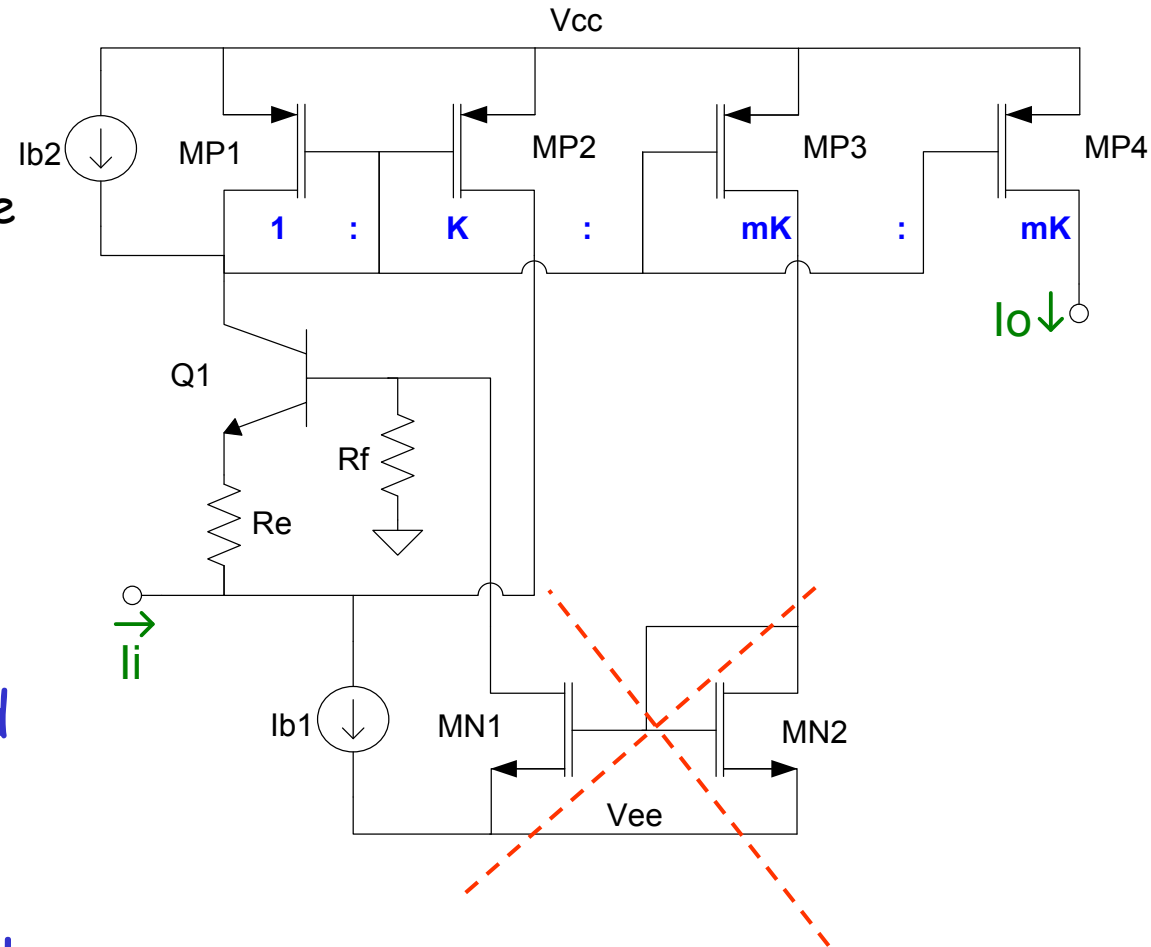
- SiPM cathode can be tuned from 0 to 1 V
  - Base of Q1
- Input impedance < 20 ohm



**POWER 5 mW**

### III. Simulations with ICECAL FE stage (LHCb Calo upgrade)


- Transient simulation (1 to 30 cells)

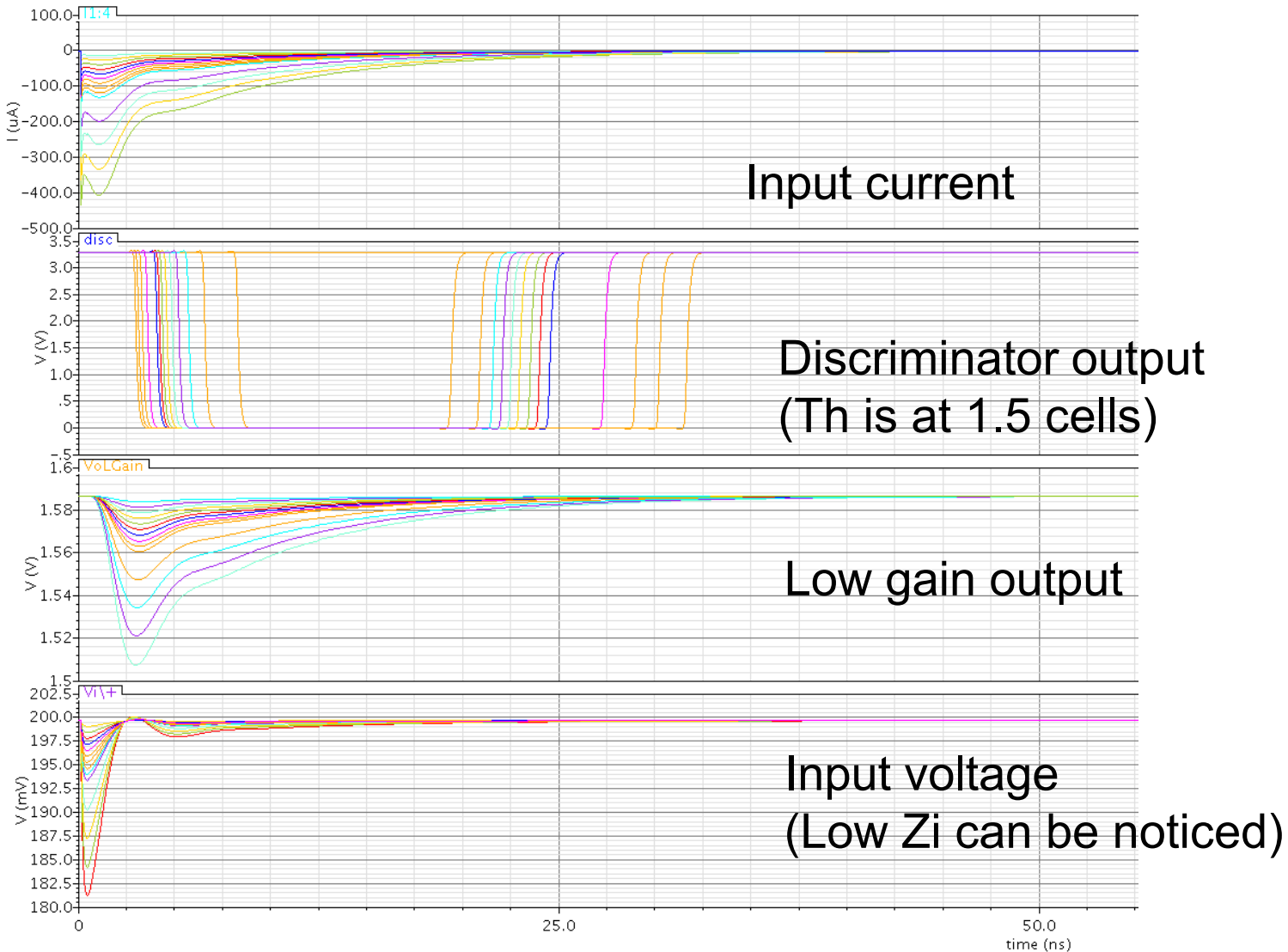

### III. Simulations with ICECAL FE stage (LHCb Calo upgrade)

- Peak or integral measurements are ok as well


Expressions 2

 



### III. Simulations with a FE designed for PET

- Similar results for ToT

 

## IV. Discussion

---

- Current mode input stage seems a good choice
  - Low input impedance and fast: minimize pile-up
  - As long as 5 mW/ch is ok
- Signal processing
  - With peak detection / integration problem is pushed to ADC
  - Is ToT feasible?
    - Detector simulation
    - Resolution needed? TDC implementation
- ADC, possible solutions:
  - Maybe multiplexed SAR 5bits ADC
  - Low power current mode cyclic ADCs
  - See next slides

# Feasibility

## Fast SAR ADCs

	ADC Flash				
	Choi	Deguchi	Yoo	Verbruggen	Paulus
Precision	6 bit	6 bit	6 bit	5 bit	6 bit
Echantillonnage	5 GS/s	3.5 GS/s	1 GS/s	1.75 GS/s	4GS/s
Technologie	65 nm	90 nm	250 nm	90nm	130 nm
Année	2008	2007	2001	2008	2004
Tension alimentation	1.3 V	0.9 V	2.5 V	1 V	1.5 V
Consommation	320 mW	98 mW	67 mW	7.6 mW	990 mW


	ADC SAR			
	Draxelmayr	Chen	Ginsburg	Liu
Precision	6 bit	6 bit	5 bit	10 bit
Echantillonnage	600 MS/s	600 MS/s	500 MS/s	50 MS/s
Technologie	90 nm	130 nm	180 nm	130 nm
Année	2004	2006	2005	2009
Tension alimentation	1.2 V	1.2 V	1.2 V / 1.8 V	1.2 V
Consommation	10 mW	5.3 mW	7.8 mW	0.92 mW

### Target specification:

- BW = 500 MHz
- SR = 2 GS/s
- 6 bit ; ENOB  $\geq 5$  at 500 MHz
 
### Promising state of the art

- Existing architectures in this range
- Some are power-efficient
- Development required to fit the specif.



B.E. Jonsson 2010, IEEE

## IV. Discussion

### • Current mode cyclic ADC:

- DCD chip (DEPFET readout): 180 nm CMOS
- ADC core is 40  $\mu\text{m}$  x 55  $\mu\text{m}$  and 1 mW
- Conversion time for 8 bits: 160 ns (fast version): 20 ns/bit
- To be improved for 5 bits @ 40 MHz, unless analogue sparsification is used

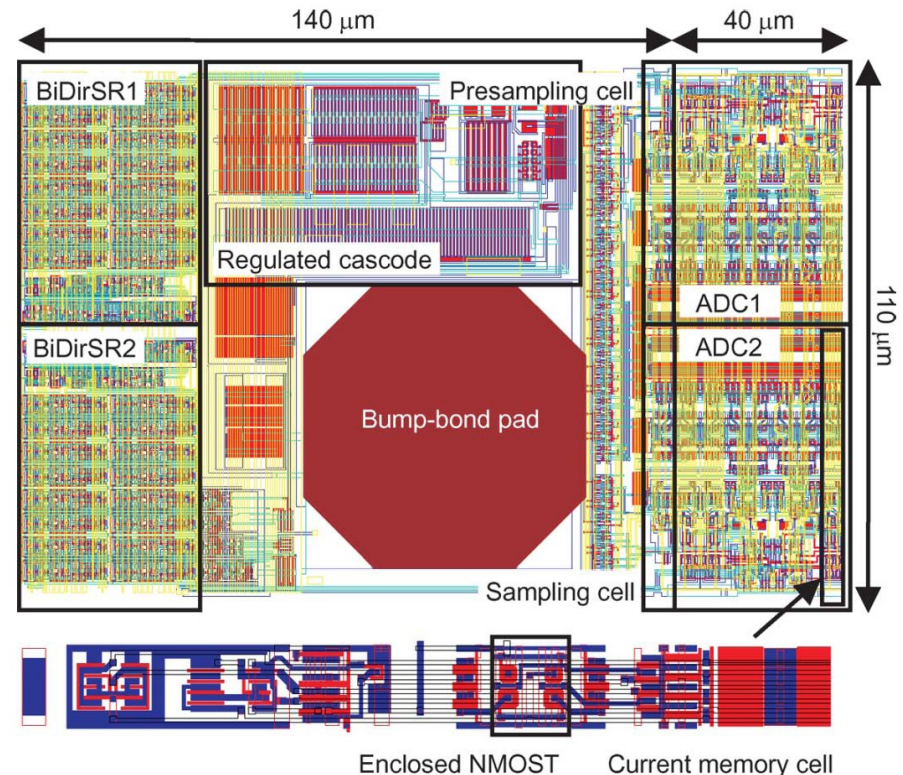
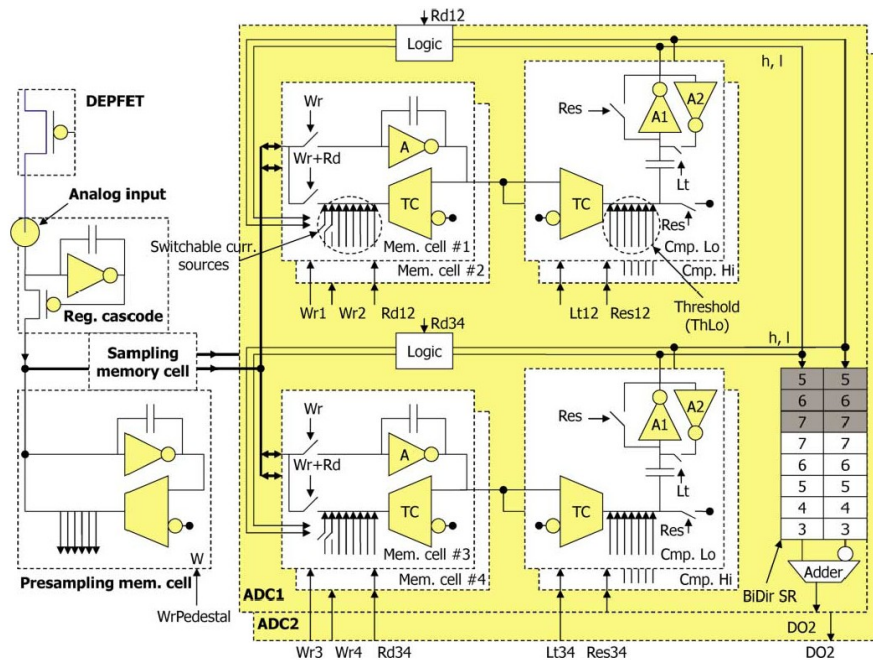


Fig. 2. Block diagram of the DCD channel. The channel consists of a signal receiver (regulated cascode), two current-mode ADCs and two additional sampling cells that allow double sampling. One DEPFET transistor is also shown.