


RF Engineering

Exercises with Dellsperger Smith


Christine Völlinger & Manfred Wendt – CERN

Impedance Matching

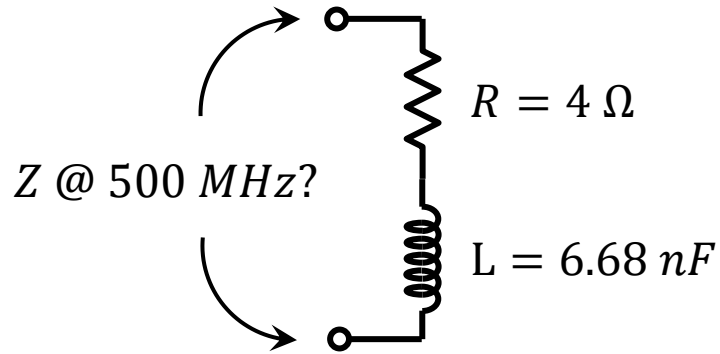- Example of a simple impedance matching for a single frequency



$$Z = R + j\omega L = (4 + j21) \Omega$$

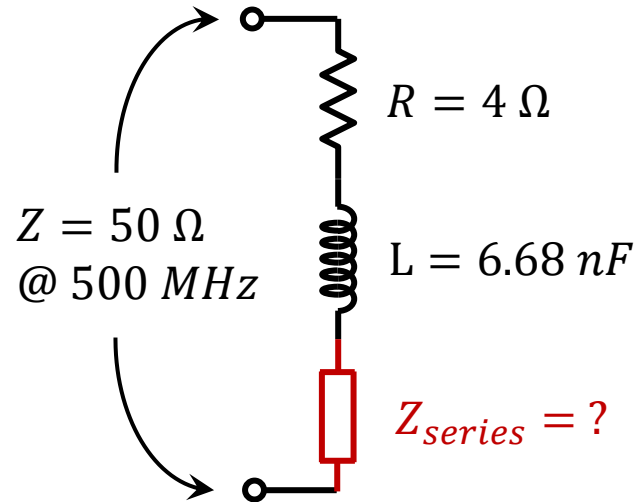


$$Z = R + j\omega L + Z_{series} = 50 \Omega$$

$$Z_{series} = R_{series} + jX_{series} = 50 - (4 + j21) \Omega$$

$$\Rightarrow R_{series} = 46 \Omega$$
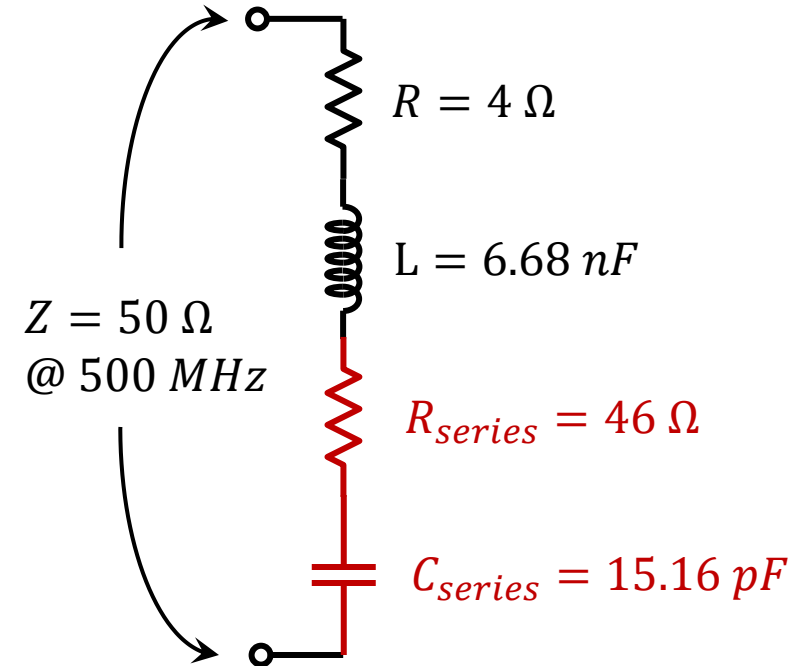
$$X_{series} = 21 \Omega = \frac{1}{\omega C_{series}} \Rightarrow C_{series} = 15.16 \text{ pF}$$



Matching Network Exercises with “Smith V4.1” (1)

- Download the freeware tool “Smith V4.1” by *Fritz Dellsperger* from <https://www.fritz.dellsperger.net/smith.html>
 - Requires a MS-Windows compatible computer
- 1. Use R , L and C elements in series to match the impedances at 500 MHz to $Z_0 = 50\ \Omega$. Use only two components for each matching circuit.
 - You should enter Z_L as the first data point in the smith chart by clicking on the “Mouse” or “Keyboard” buttons at the top. You may have to switch from “polar” to “cartesian” coordinates. Then design your matching circuit from there.
 - You will only need the Z -plane for this exercise; the Y -plane can be turned off in the program “Settings”.

Z_L	C Series	L Series	R Series
$Z = (50 + j25)\ \Omega$			
$Z = (50 - j25)\ \Omega$			
$Z = (4 + j21)\ \Omega$			
$Z = (20 - j50)\ \Omega$			

Matching Network Exercises with “Smith V4.1” (2)

2. Use R , L and C elements in parallel to match the impedances at 500 MHz to $Z_0 = 50 \Omega$. Use only two components for each matching circuit.
- Hint: You will only need the Y -plane for this exercise
 - Another hint: Make use of “Undo” if something goes wrong or restart the program.

Z_L	C Shunt	L Shunt	R Shunt
$Z = (50 + j25) \Omega$			
$Z = (50 - j25) \Omega$			
$Z = (4 + j21) \Omega$			
$Z = (20 - j50) \Omega$			

Matching Network Exercises with “Smith V4.1” (3)

3. Match the impedances at 500 MHz to $Z_0 = 50 \Omega$. Use only two reactive components (in series or parallel) to create a lossless matching circuit.

– Multiple solution are possible!

Z_L	C Series	L Series	C Shunt	L Shunt
$Z = (32 - j66) \Omega$				
$Z = (13 - j9) \Omega$				
$Z = (37 + j34) \Omega$				
$Z = (78 + j78) \Omega$				

4. The input impedance $Z_L = (17 - j18) \Omega$ of an amplifier shall be matched to $Z_0 = 50 \Omega$ at 500 MHz. Use only two coaxial lines with characteristic impedances of 50 Ω and 25 Ω in a series configuration.

What is the electrical length of the two lines?

– Multiple solutions are possible!