

# **RF Engineering**

# **Scattering (S)-Parameters**

*Christine Völlinger & Manfred Wendt – CERN*


- **A brief recap on electrical networks**
  - A simplified way to describe electrical, electronics and RF circuits
  - Electrical network composed out of lumped and distributed elements
  - Two-port RC-filter example using admittance (Y) parameters
- **Introduction to scattering (S) parameters**
  - General concept of incident / reflected waves scattered at the ports of an RF network
  - Reference impedance  $Z_0$
  - 1-port and 2-port S-parameters
  - Properties of the S-matrix: reciprocity, symmetry, losses
  - A few S-matrix examples for RF networks with 1-, 2-, 3-, and 4-ports
  - S-parameters in practice: the SnP Touchstone file format
  - Cascading (“chaining”) 2-port S-matrices
  - General  $n$ -port networks

Please note the references  
to the JUAS proceedings!

- The electromagnetic behavior of RF circuits and systems, like any other electrical / electronics circuit or system can be described by Maxwell's equations

$$\nabla \cdot \mathbf{E} = \frac{\rho}{\epsilon}, \quad \nabla \times \mathbf{B} - \frac{\partial \mathbf{E}}{c^2 \partial t} = \mu \mathbf{J}, \quad \nabla \times \mathbf{E} + \frac{\partial \mathbf{B}}{\partial t} = 0, \quad \nabla \cdot \mathbf{B} = 0$$

- These equations need to be solved, taking all the boundaries and materials into account
- **However, this is far too complicated and inconvenient for most practical situations!**
  - **simplified electrical network description based on approximative lumped or distributed elements**
    - With given characteristics and values of each circuit element represented by a symbol in an electrical network, following the laws of *Ohm* and *Kirchhoff*. Here some examples:

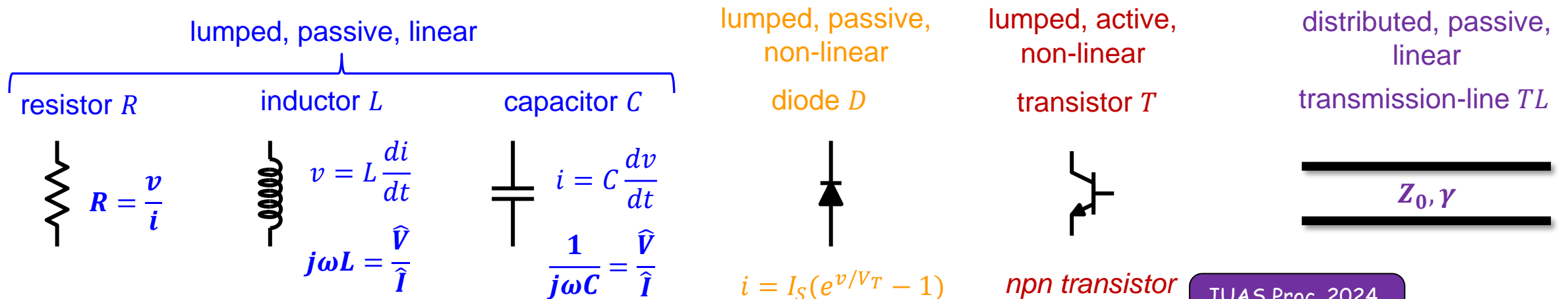

- Complex electrical, electronics and RF systems are divided into functional blocks, i.e., **networks, with  $n$ -ports**, each port has two terminals
  - The two-port network is most popular, typical examples for two-port networks are filters, attenuators, amplifiers, etc.




### Y- parameters

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 & Y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0} & Y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 & Y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0} & Y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0} \end{aligned}$$

$I_1, I_2$ : dependent  
 $V_1, V_2$ : independent

- The characteristic behavior of the  $n$ -port network is defined by a set of  $2n$  parameters, linked to their ports.
  - A two-port network has four parameters as port voltages ( $V_1, V_2$ ) and port currents ( $I_1, I_2$ ), two are independent, the other two are dependent parameters.
  - Various combinations of dependent and independent port voltages and currents exist, accordingly various  $n \times n$  matrix definitions for linear  $n$ -port networks exist, known as  $Y$ -,  $Z$ -,  $h$ - and  $g$ - parameters.

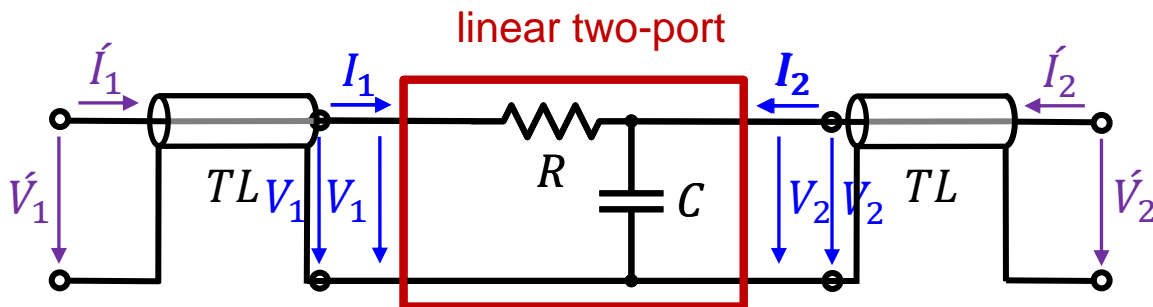- It is more convenient to express the parameters for **linear networks in the frequency domain**
  - Avoids solving differential equations! Example: Simple RC two-port network
    - Only for time-invariant and linear networks!



Y- parameters:

$$Y = \frac{1}{R} \begin{bmatrix} 1 & -1 \\ -1 & 1 + j\omega RC \end{bmatrix}$$

Z- parameters:

$$Z = \frac{1}{j\omega C} \begin{bmatrix} 1 + j\omega RC & 1 \\ 1 & 1 \end{bmatrix}$$

- **Voltage/current-based network parameters fail at high frequencies!**
  - Now voltages and currents are a **function of frequency (or time) AND space (location):  $V(\omega, z), I(\omega, z)$** 
    - Originating from time/space varying EM-fields
  - Example: RC two-port network embedded between transmission-lines
    - While it is still possible to solve the network problem, it becomes complicated and cumbersome based on  $V$  and  $I$
  - The circuit may become unstable or might be damaged, when operating on a short or open end for characterizing the network parameters
  - Due to parasitic effects, a reliable measurement of  $V$  and  $I$  becomes almost impossible.
- **Resolution: RF scattering parameters based on power-waves for linear networks which include distributed elements**
  - The magnitude of a traveling wave is independent of the location  $z$  in a lossless transmission-line

JUAS Proc. 2024  
II.2.7.1, p. 830

- **Analogy to optical waves**
  - **Light falls on a car window**
    - Some parts of the incident light is reflected (you see the mirror image)
    - Other parts of the light is transmitted through the window (you can still see objects inside the car)
  - **Optical reflection and transmission coefficients of the window glass define the ratio between reflected and transmitted light.**
- **Similar in RF networks:**  
**The scattering (S)-parameters of an  $n$ -port RF network (DUT) is characterized by incident and reflected / transmitted (power) waves.**



- for an arbitrary  $n$ -port microwave or RF network are defined by a set of normalized complex voltage waves:

incident wave at port  $i$ :


$$a_i = \frac{V_i + Z_i I_i}{2\sqrt{\Re\{Z_i\}}} = \frac{V_i^{inc}}{\sqrt{\Re\{Z_i\}}}$$

reflected wave at port  $i$ :

$$b_i = \frac{V_i - Z_i^* I_i}{2\sqrt{\Re\{Z_i\}}} = \frac{V_i^{refl}}{\sqrt{\Re\{Z_i\}}}$$

$Z_i^*$ :  
conjugate  
complex

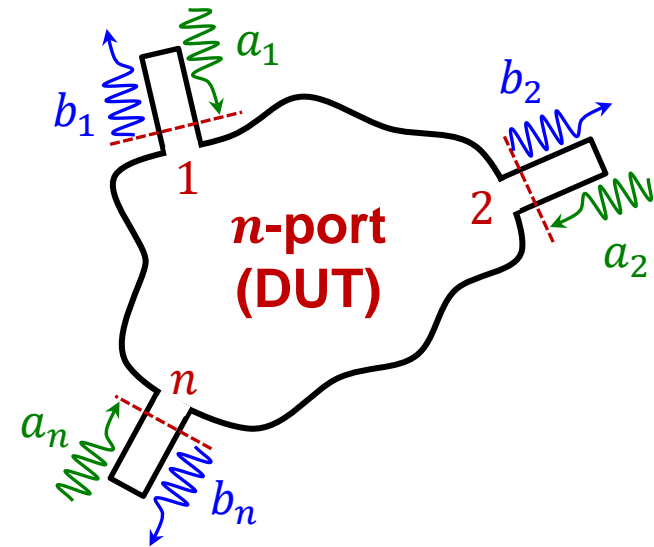
- as **incident**  $a_i$  and **reflected / transmitted**  $b_i$  **power waves** at the  $i^{th}$  port of the network, defined by the terminal voltage  $V_i$  and current  $I_i$ , and an arbitrary **reference impedance**  $Z_i$ 
  - Please note the complex notation implies linear, time-invariant networks describe in the frequency-domain



- Today, for most practical cases the **RF network**, also called “**device under test**” (DUT) is characterized by a **vector network analyzer (VNA)**, connected with coaxial cables (transmission-lines) with a **characteristic impedance of  $Z_0 = 50 \Omega$**  to the ports.
  - Usually the S-parameters are defined for a port reference impedance:  $Z_i = Z_0 = 50 \Omega$
  - Some VNAs with a physical reference impedance of  $Z_0 = 50 \Omega$  allow a mathematical port impedance conversion to adapt to a port reference impedance  $Z_i \neq 50 \Omega$



- **Electrical / electronics networks**
  - 1 ...  $n$ -port electronics circuits
  - Defined by **voltages**  $V_i(\omega)$  or  $v_i(t)$  and **currents**  $I_i(\omega)$  or  $i_i(t)$  at the port terminals
  - Characterized by circuit matrices, e.g.,  $Z$ ,  $Y$ ,  $h$ , etc.
- **RF / microwave networks**
  - 1 ...  $n$ -port RF DUT circuit or subsystem, e.g., filter, amplifier, transmission-line, hybrid, circulator, resonator, etc., which may include distributed elements
  - Defined by **incident**  $a_i(\omega)$  and **reflected / transmitted waves**  $b_i(\omega)$  at a **reference plane  $s$  (physical position)** at the ports.
  - Characterized by a scattering parameter (S-parameter) matrix of the reflected and transmitted power waves, typically as a function of the frequency  $f = 2\pi/\omega$
  - Normalized to a **reference impedance** of typically  $Z_0 = 50 \Omega$

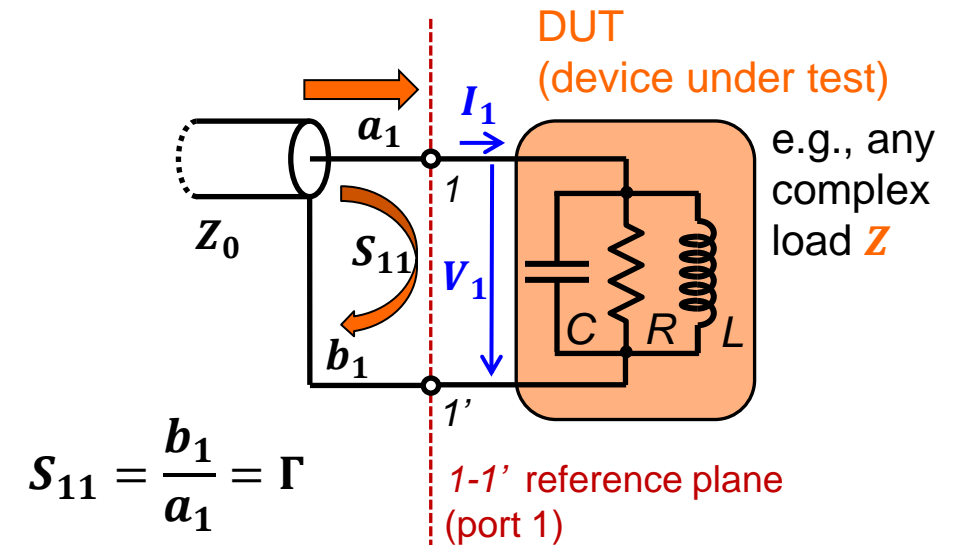


### 1-port RF network (DUT) example

- S-Parameters allow to characterize the DUT with the measurement equipment located at some physical distance
- All high frequency effects of distributed elements are included with respect to the reference plane



# S-Parameters – 2-port (1)

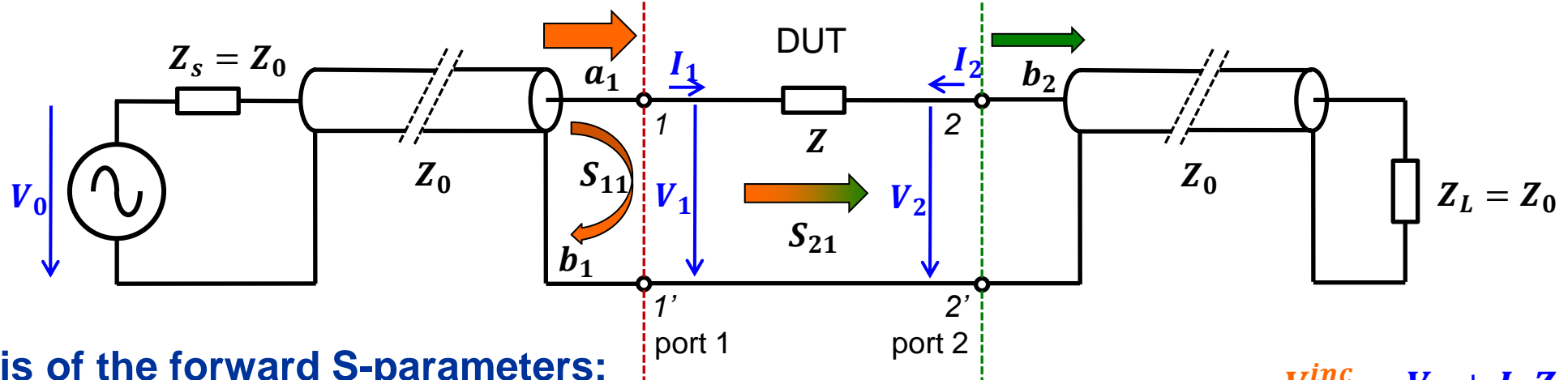

• Analysis of the forward S-parameters:

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \equiv \text{input reflection coefficient}$$

$(Z_L = Z_0 \Rightarrow a_2 = 0)$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \equiv \text{forward transmission gain}$$

- 3 +port networks still can be fully characterized with a 2-port VNA, but always remember:
- **ALWAYS: Terminated unused ports in their characteristic impedance!**


- Independent parameters:

$$a_1 = \frac{V_1^{inc}}{\sqrt{Z_0}} = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}}$$

- Dependent parameters:

$$b_1 = \frac{V_1^{refl}}{\sqrt{Z_0}} = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}}$$
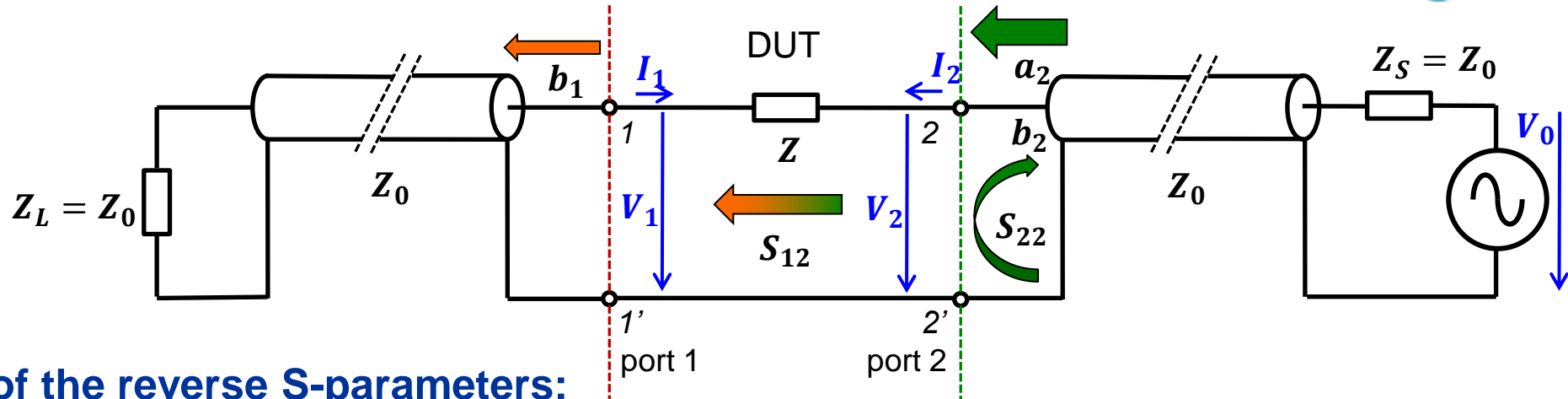
$$b_2 = \frac{V_2^{refl}}{\sqrt{Z_0}} = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}}$$



• Analysis of the reverse S-parameters:

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \equiv \text{output reflection coefficient}$$

$(Z_L = Z_0 \Rightarrow a_1 = 0)$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \equiv \text{reverse transmission gain}$$

- Examples of 2-ports DUT: filters, amplifiers, attenuators, transmission-lines (cables), etc.
- **ALL ports ALWAYS need to be terminated in their characteristic impedance!**

– Independent parameters:

– Dependent parameters:

$$a_2 = \frac{V_2^{inc}}{\sqrt{Z_0}} = \frac{V_2 + I_2 Z_0}{2\sqrt{Z_0}}$$

$$b_1 = \frac{V_1^{refl}}{\sqrt{Z_0}} = \frac{V_1 - I_1 Z_0}{2\sqrt{Z_0}}$$

$$b_2 = \frac{V_2^{refl}}{\sqrt{Z_0}} = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}}$$

# S-Parameters – 2-port (3)

- Linear equations for a 2-port network (DUT):

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

– with:

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

≡ input reflection coefficient

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

≡ output reflection coefficient

impedance  
measurements


$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

≡ forward transmission (insertion) gain

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

≡ reverse transmission (insertion) gain

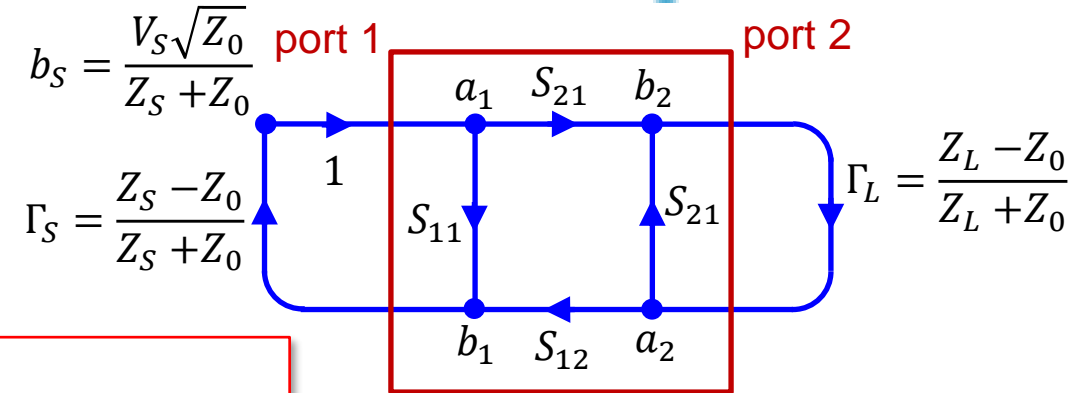transmission  
(insertion)  
measurements



signal flow graph (SFG)  
of a 2-port network

- port1:  $V_S$  with  $Z_S \neq Z_0$
- port 2:  $Z_L \neq Z_0$

- Reflection coefficient and impedance at the  $i^{\text{th}}$ -port of a RF network (DUT):

$$S_{ii} = \frac{b_i}{a_i} = \frac{\frac{V_i}{I_i} - Z_0}{\frac{V_i}{I_i} + Z_0} = \frac{Z_i - Z_0}{Z_i + Z_0} = \Gamma_i$$

$$Z_i = Z_0 \frac{1 + S_{ii}}{1 - S_{ii}} \text{ with } Z_i = \frac{V_i}{I_i} \text{ being the input impedance at the } i^{\text{th}} \text{ port}$$

- Power reflection and transmission for a  $n$ -port network (DUT):

$$|S_{ii}|^2 = \frac{\text{power reflected from port } i}{\text{power incident on port } i}$$

$$|S_{ij}|^2 = \text{transmitted power between ports } i \text{ and } j$$

with all ports terminated in their characteristic impedance  $Z_0$   
and  $Z_s = Z_0$

Here the US notation is used, where power =  $|a_i|^2$ .  
European notation (often):  
power =  $|a_1|^2/2$   
These conventions have no impact on the S-parameters, they are only relevant for absolute power calculations

- Waves traveling towards the  $n$ -port:  $(a) = (a_1, a_2, a_2, \dots a_n)$
- Waves traveling away from the  $n$ -port:  $(b) = (b_1, b_2, b_2, \dots b_n)$
- The relation between  $a_i$  and  $b_i$  ( $i = 1 \dots n$ ) can be written as a system of  $n$  linear equations  
( $a_i$  = the independent variable,  $b_i$  = the dependent variable)

one-port	$b_1 = S_{11}a_1$	$+ S_{12}a_2$	$+ S_{13}a_3$	$+ S_{14}a_4$	$+ \dots$
two-port	$b_2 = S_{21}a_1$	$+ S_{22}a_2$	$+ S_{23}a_3$	$+ S_{24}a_4$	$+ \dots$
three-port	$b_3 = S_{31}a_1$	$+ S_{32}a_2$	$+ S_{33}a_3$	$+ S_{34}a_4$	$+ \dots$
four-port	$b_4 = S_{41}a_1$	$+ S_{42}a_2$	$+ S_{43}a_3$	$+ S_{44}a_4$	$+ \dots$

– in compact matrix form follows

$$(b) = (S)(a)$$

## 1. Select all correct answers


- Y- and Z-parameters of electrical networks require a reference impedance  $Z_0$
- Scattering parameters of RF networks are based on normalized, complex power waves incident and reflected / transmitted at their ports
- DUT stands for “Device Under Test”, as acronym for the RF network to be characterized
- S-parameters are only defined for a reference impedance of  $Z_0 = 50\Omega$ .
- Unused ports in a S-parameter measurement setup always need to be terminated in their characteristic port impedance

- **A port of the network is matched if:**  $S_{ii} = 0$ 
  - i.e., no reflections!
- **A  $n$ -port is reciprocal if:**  $(S)^T = (S) \Rightarrow S_{ij} = S_{ji} \quad \forall i, j$   $(S)^T$ : transpose Matrix symmetry
  - **Most passive components are reciprocal, e.g., resistor, capacitor, inductor, transformer, etc.**
    - But not components with inhomogeneous material properties, e.g., magnetized ferrites, plasma, etc.
  - **Active components, like amplifiers are non-reciprocal**
- **A  $n$ -port is symmetric if:**  $S_{ij} = S_{ji} \wedge S_{ii} = S_{jj}$  Matrix symmetry and electrical symmetry
  - It **needs to be reciprocal**, and input and output reflection coefficient need to be equal.
- **A  $n$ -port is passive and lossless if the matrix  $(S)$  is unitary:**  $(S)^\dagger (S) = (S)^T (S)^* = (I)$   $(S)^\dagger = (S^*)^T$ : conjugate transpose (*Hermitian*)  
 $(I)$ : identity matrix
  - **Example: passive, lossless 2-port:**

$$(S^*)^T (S) = \begin{pmatrix} S_{11}^* & S_{21}^* \\ S_{12}^* & S_{22}^* \end{pmatrix} \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} \Rightarrow \begin{aligned} \angle S_{11} - \angle S_{12} &= \angle S_{21} - \angle S_{22} - \pi \\ |S_{11}| &= |S_{22}|, \quad |S_{12}| = |S_{21}| \\ |S_{11}| &= \sqrt{1 - |S_{12}|^2} \end{aligned}$$



**π-network**

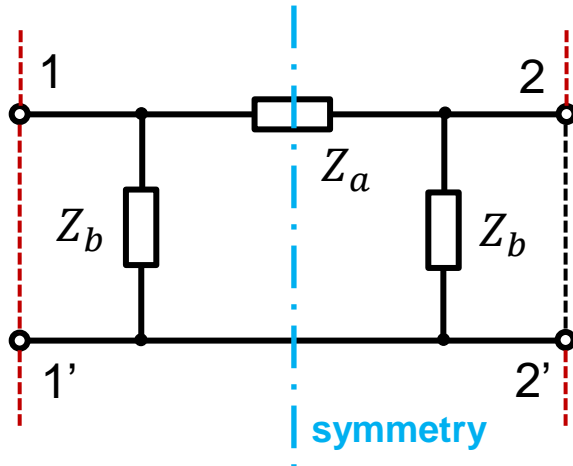


$$(S_\pi) = \frac{1}{\Delta} \begin{pmatrix} Z_a Z_b^2 - Z_0^2 (Z_a + 2Z_b) & 2Z_0 Z_b^2 \\ 2Z_0 Z_b^2 & Z_a Z_b^2 - Z_0^2 (Z_a + 2Z_b) \end{pmatrix}$$

with:  $\Delta = (Z_a + Z_b)[Z_a Z_b + Z_0(Z_a + 2Z_b)]$

$S_{12} = S_{21} \wedge S_{11} = S_{22} \Rightarrow$  reciprocal and symmetric

**voltage-divider network**

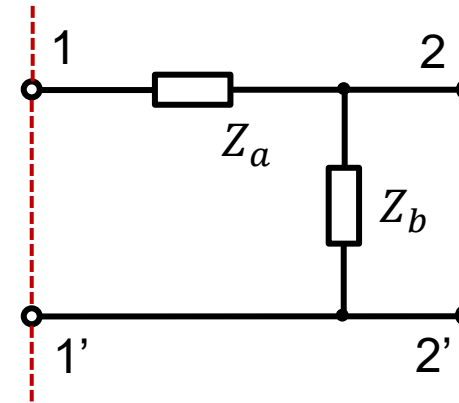


$$(S_{div}) = \frac{1}{\Delta} \begin{pmatrix} Z_a Z_b - Z_0(Z_0 - Z_a) & 2Z_0 Z_b \\ 2Z_0 Z_b & Z_a Z_b - Z_0(Z_0 + Z_a) \end{pmatrix}$$

with:  $\Delta = Z_0(Z_0 + Z_a) + Z_b(2Z_0 + Z_a)$

$S_{12} = S_{21} \wedge S_{11} \neq S_{22} \Rightarrow$  reciprocal, but not symmetric

- Without prof: The S-matrix is always reciprocal for symmetric networks.

## 2-port series-network

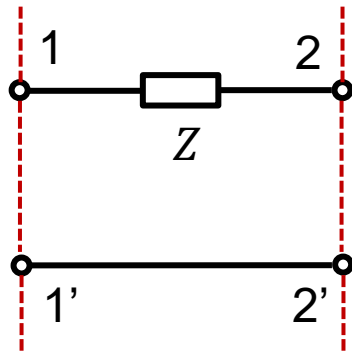


$$(S) = \frac{1}{2Z_0 + Z} \begin{pmatrix} Z & 2Z_0 \\ 2Z_0 & Z \end{pmatrix}$$

$$S_{11} = S_{22} \wedge S_{12} = S_{21}$$

$Z = j\omega L = j10$	$Z = R = 10$
$ S_{11}  = \sqrt{1 -  S_{12} ^2}$	
$\frac{1}{\sqrt{101}} = \sqrt{1 - \left(\frac{10}{\sqrt{101}}\right)^2}$	$\frac{1}{11} \neq \sqrt{1 - \left(\frac{10}{11}\right)^2}$
$\angle S_{11} - \angle S_{12} = \angle S_{21} - \angle S_{22} - \pi$	
$\tan^{-1}(10) + \tan^{-1}\frac{1}{10} = -\tan^{-1}\frac{1}{10} - \tan^{-1}(10) - \pi$	$0 - 0 \neq 0 - 0 - \pi$
$\Rightarrow$ <b>lossless</b>	$\Rightarrow$ <b>lossy</b>

Prompts		Possible Answers
A. matched		1. $S_{ii} = S_{ij}$
B. symmetric		2. $(S^*)^T(S) = (I)$
C. reciprocal		3. $S_{ij} = S_{ji} \wedge S_{ii} = S_{jj}$
D. passive and lossless		4. $S_{ii} = 0$
		5. $\Gamma = +j$
		6. $S_{ij} = S_{ji}$

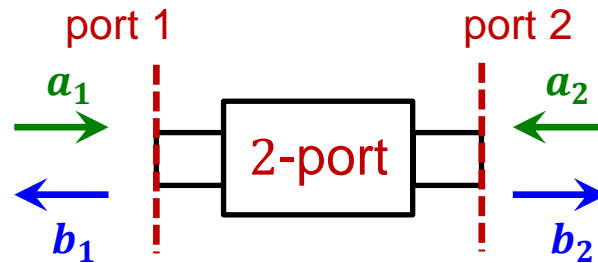

### 3. Mark all correct answers for the S-parameters of a 2-port RF network

- $a_1$  and  $b_1$  are independent parameters
- $S_{11}$  is the input reflection coefficient
- $a_1$  and  $a_2$  are the incident waves at port 1 and port 2, respectively.
- $b_1$  and  $b_2$  are the transmitted waves between port 1 and port 2, and vice versa.
- $S_{21}$  and  $S_{12}$  are the forward and reverse transmission gains.
- To characterize the S-parameters at port 2, port 1 needs to be terminated in its characteristic port impedance.

- **Examples for 1-port S-matrices are any simple, passive (complex) impedances  $Z$** 
  - Any R, L, C, RL, RC, LC and RLC circuit or any combinations of those elements leading to a single port network, which of course also may include distributed (transmission-line) elements
  - “Special” cases are:
    - $Z = Z_0 \Rightarrow S_{11} = 0$  (matched, ideal termination)
    - $Z = 0 \Rightarrow S_{11} = -1$  (ideal short)
    - $Z = \infty \Rightarrow S_{11} = +1$  (ideal open)
  - If  $|S_{11}| > 1$  an active element is involved, e.g., a reflection amplifier
- **Strictly speaking, a simple RF resonator, e.g., a “pill-box” cavity, is a 3-port**
  - One coaxial or waveguide port as RF power coupler, plus two beam (waveguide) ports.
- **However, for many practical cases it can be treated as 1-port**
  - The mode of interest, e.g., TM<sub>010</sub>, is trapped with no or negligible fields contribution near the beam-ports
  - We consider only a single coupler to characterize, e.g., the TM<sub>010</sub> mode in terms of a 1-port S-parameter measurement
    - Typically applying an RLC-parallel equivalent circuit

$$(S) = S_{11} = \Gamma$$

- **Ideal (matched:  $Z = Z_0$ ) transmission-line of length  $\ell$**


$$(S) = \begin{pmatrix} 0 & e^{-\gamma\ell} \\ e^{-\gamma\ell} & 0 \end{pmatrix}$$

$\gamma = \alpha + j\beta$ : propagation constant  
 $\alpha$ : attenuation constant in [Np/m]  
 $\beta = 2\pi/\lambda$ : phase constant [rad/m]

– For a lossless transmission-line:  $\alpha = 0 \Rightarrow |S_{21}| = |S_{12}| = 1$

– For a lossless line of length  $\ell = \lambda/4$ :  $(S) = \begin{pmatrix} 0 & -j \\ -j & 0 \end{pmatrix}$

signal flow graph (SFG):

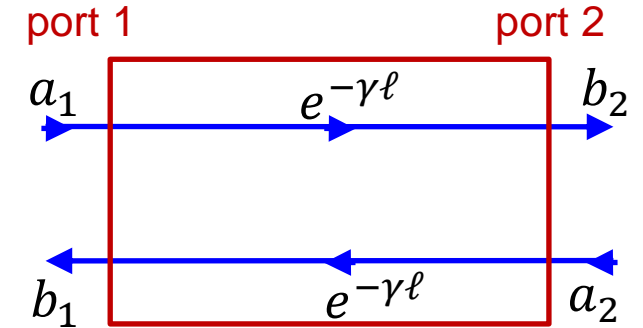

- **Ideal attenuator**


$$(S) = \begin{pmatrix} 0 & k \\ k & 0 \end{pmatrix}$$

$k = V_2/V_1 = 10^{-(\Delta dB/20)}$ : attenuation  $k < 1, k \in \mathbb{R}$   
 $\Delta dB = 20 \log_{10} V_1/V_2$ : attenuation in dB  
 $\alpha = -\ln k$ : attenuation in neper

T-attenuator:

$$R_A = \frac{1-k}{1+k} Z_0$$


$$R_B = \frac{2k}{1-k^2} Z_0$$

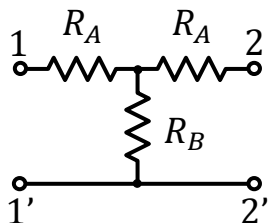


$\pi$ -attenuator:

$$R_1 = \frac{1-k}{1+k} Z_0$$

$$R_2 = \frac{1-k^2}{2k} Z_0$$

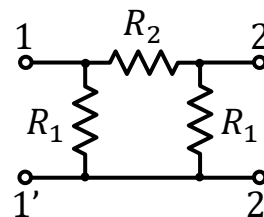

SFG example: 3 dB attenuator

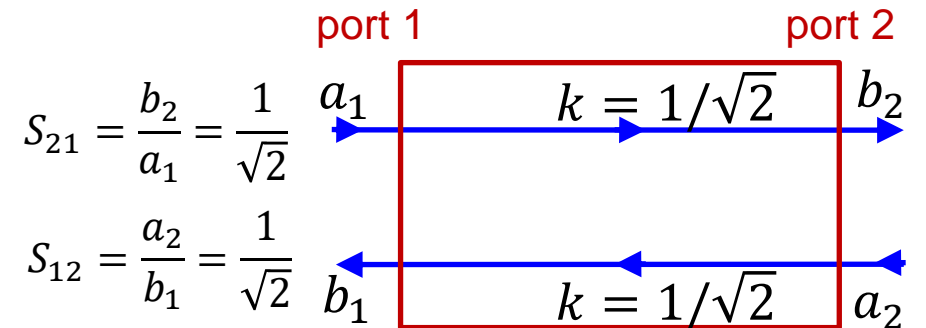


$$S_{21} = \frac{b_2}{a_1} = \frac{1}{\sqrt{2}}$$

$$S_{12} = \frac{a_2}{b_1} = \frac{1}{\sqrt{2}}$$

- **Ideal amplifier (gain stage)**

$$(S) = \begin{pmatrix} 0 & 0 \\ G_V & 0 \end{pmatrix}$$

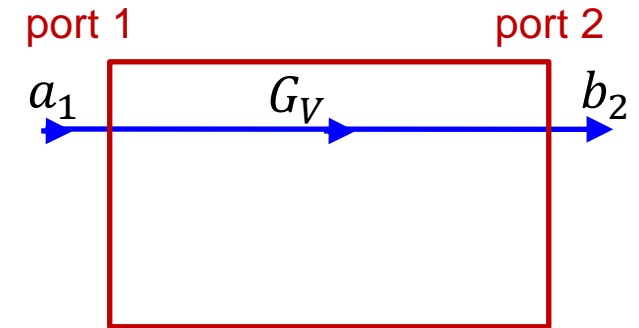
$G_V = V_{out}/V_{in} = 10^{g/20}$ : voltage gain  $G_V > 1$   
 $g = 20 \log_{10} V_{out}/V_{in}$ : voltage gain in dB



- **Low-noise RF transistor**

$$(S) = \begin{pmatrix} 0.78e^{j158^\circ} & 0.08e^{-j24^\circ} \\ 3.43e^{j42^\circ} & 0.3e^{-j159^\circ} \end{pmatrix}$$

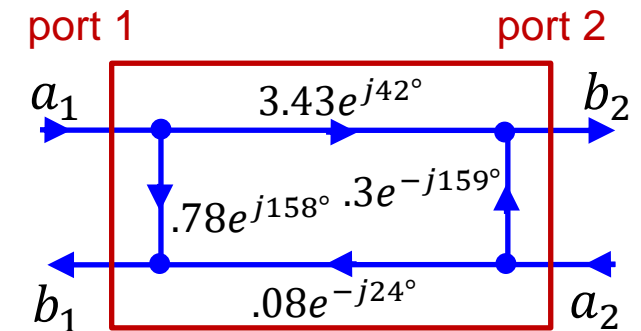Datasheet Avago VMMK-1218:  
 $f = 10 \text{ GHz}$ ,  $Z_0 = 50 \Omega$ ,  $T_A = 25^\circ\text{C}$ ,  
 $V_{ds} = 2\text{V}$ ,  $I_{ds} = 20\text{mA}$



- Avago VMMK-1218
- E-pHEMT GaAs FET

- The S-parameters are different at other frequencies and operational conditions
- The transistor requires impedance matching networks at in- and output



- 3-port resistive power divider


$$(S) = \frac{1}{2} \begin{pmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{pmatrix}$$

$$b_1 = \frac{1}{2}(a_2 + a_3)$$

$$b_2 = \frac{1}{2}(a_1 + a_3)$$

$$b_3 = \frac{1}{2}(a_1 + a_2)$$

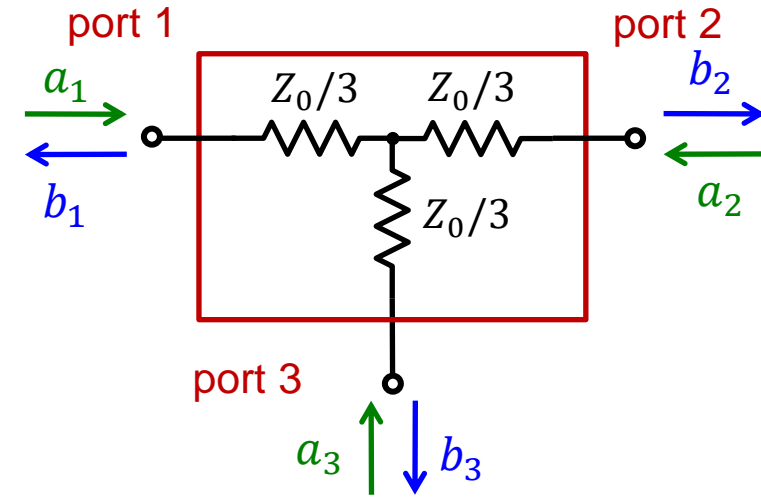– The transfer-loss between *ij*-ports is 6 dB.



- Ideal circulator


$$(S) = \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix}$$

$$b_1 = a_3$$

$$b_2 = a_1$$

$$b_3 = a_2$$

– Matched, but not reciprocal

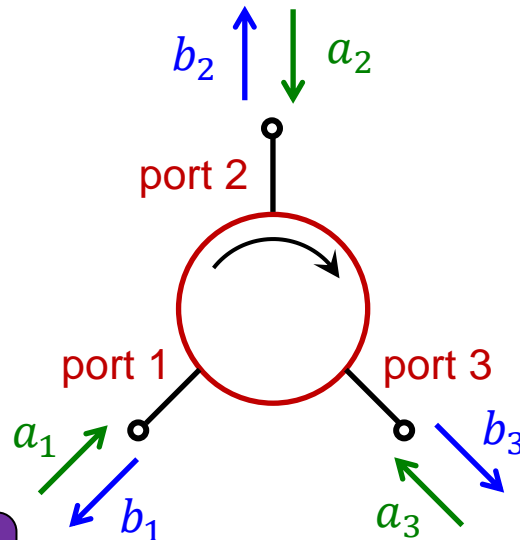


- Isolator, based on the circulator

– Terminating, e.g., port 3 internally results in a 2-port, called **isolator**

$$(S) = \begin{pmatrix} 0 & 0 \\ 1 & 0 \end{pmatrix}$$

$$b_2 = a_1$$


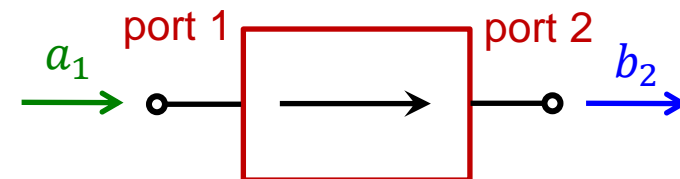


- Ideal directional coupler

$$(S) = \begin{pmatrix} 0 & \tau & \kappa & 0 \\ \tau & 0 & 0 & \kappa \\ \kappa & 0 & 0 & \tau \\ 0 & \kappa & \tau & 0 \end{pmatrix}$$

$\tau$ : transmission coefficient  
 $\kappa$ : coupling coefficient

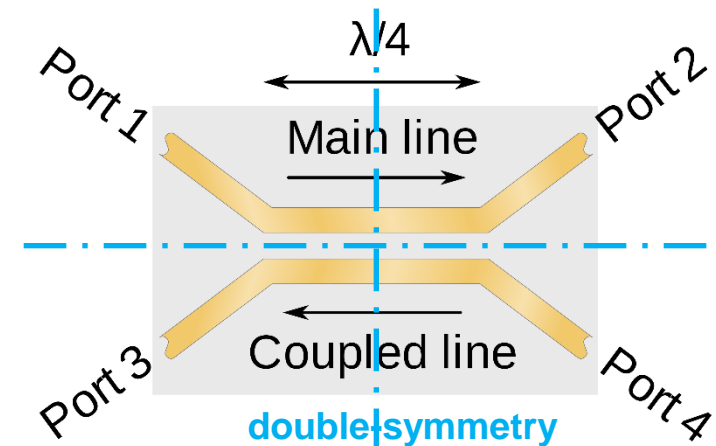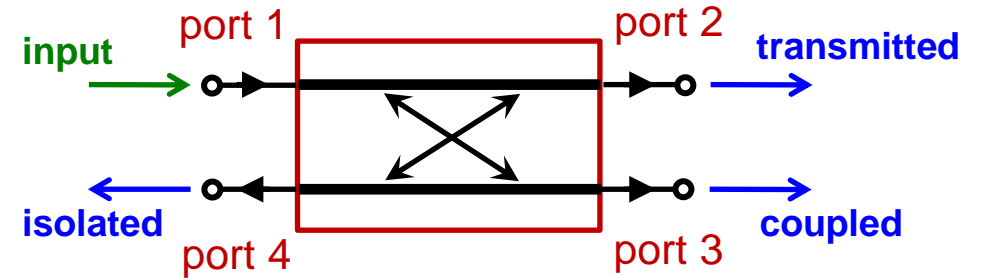- Matched, symmetric, infinite isolation
- Distinguishes between forward and reflected signal power on the main line port 1-2
  - Forward power at coupled port 3
  - Reflected power at coupled port 4



[https://en.wikipedia.org/wiki/Power\\_dividers\\_and\\_directional\\_couplers](https://en.wikipedia.org/wiki/Power_dividers_and_directional_couplers)

- **Ideal, lossless TEM directional coupler**

- The coupled port 3 is in-phase with the input port 1
- The main line output port 2 is in quadrature phase ( $\pi/2$  phase delay) with the input port 1

$$(S) = \begin{pmatrix} 0 & -jt & k & 0 \\ -jt & 0 & 0 & k \\ k & 0 & 0 & -jt \\ 0 & k & -jt & 0 \end{pmatrix}$$

**Lossless conditions:**

$$(S)^\dagger(S) = (I) \Rightarrow \sum_{k=1}^N S_{ki}S_{kj}^* = 0 \quad \forall i \neq j \quad \wedge \quad \sum_{k=1}^N S_{ki}S_{ki}^* = \sum_{k=1}^N |S_{ki}|^2 = 1$$

$$\sum_{k=1}^N |S_{ki}|^2 = 1 \Rightarrow k^2 + t^2 = 1 \Rightarrow t = \sqrt{1 - k^2}$$

- **Lossless TEM direction coupler:**

$$(S) = \begin{pmatrix} 0 & -j\sqrt{1 - k^2} & k & 0 \\ -j\sqrt{1 - k^2} & 0 & 0 & k \\ k & 0 & 0 & -j\sqrt{1 - k^2} \\ 0 & k & -j\sqrt{1 - k^2} & 0 \end{pmatrix}$$

- In practice, **S-parameters are a function of the frequency:  $S(f)$** 
  - Some instruments or applications can also provide time-domain S-parameters
- In most real-world practical situations, S-parameters are acquired by a measurement, e.g., characterization of a RF component or sub-system by a VNA.
  - By characterizing the DUT over a range of frequencies,  $f_{min} < f < f_{max}$  in steps of  $\Delta f$
- Also, numerical RF analysis tools (Qucs, ADS, Microwave Office, etc.) generate S-parameters through linear RF circuit / systems simulations.
  - Numerical EM software tools (CST, HFSS, etc.) and PCB tools (Cadence Allegro) can also generate S-parameters
- Both application types, VNA measurements and RF/EM simulation software exchange S-parameters on a file basis
  - The *SnP Touchstone* ASCII file format is de-facto the industry standard for S-parameters
  - Example *Touchstone s2p* file:

```

!Keysight Technologies,P5024A,MY58100247,A.15.20.07
!Date: Wednesday, October 06, 2021 16:19:17
!Correction: S11(C 2-Port )
!S21(C 2-Port )
!S12(C 2-Port )
!S22(C 2-Port )
!S2P File: Measurements: S11, S21, S12, S22:
# Hz S dB R 50 # format
2000000000 -2.5430779 -88.497566 -18.274168 38.763039 -18.26178 38.742687 -2.4251425 -85.792152
2000100000 -2.5365531 -88.473915 -18.266272 38.606499 -18.269154 38.716461 -2.4215624 -85.861908
2000200000 -2.5314419 -88.471634 -18.280306 38.559021 -18.258684 38.624985 -2.4253747 -85.806236
2000300000 -2.5216722 -88.617905 -18.269596 38.352692 -18.266785 38.342678 -2.4210978 -85.8368
2000400000 -2.5178108 -88.521271 -18.257862 38.298622 -18.275055 38.266792 -2.4244151 -85.914787
2000500000 -2.5327342 -88.484985 -18.263821 38.31945 -18.27046 38.20409 -2.4263382 -85.85775
2000600000 -2.5191193 -88.462044 -18.262426 38.195797 -18.246525 38.250874 -2.3989511 -85.885635
2000700000 -2.5219827 -88.44445 -18.253748 38.216946 -18.245417 38.138355 -2.4155877 -85.859711
2000800000 -2.5198817 -88.588783 -18.255999 37.902744 -18.257757 38.035915 -2.415241 -85.887199
2000900000 -2.5370498 -88.496101 -18.256392 38.004234 -18.258446 37.872906 -2.4170656 -85.854294
2001000000 -2.5363033 -88.544846 -18.252661 37.830475 -18.259445 37.925297 -2.4102871 -85.901245
2001100000 -2.5417418 -88.47406 -18.270754 37.731613 -18.252403 37.74762 -2.4158244 -85.822517
  
```

2-port VNA file

Touchstone v1.1 example file  
 • v2.0 is different, file ext. \*.ts


frequency  $f$   $|S_{11}|$ [dB]  $\angle S_{11}$ [deg]

- The file name extension specifies the number  $n$  of ports
  - Attention: NOT equal to the number of columns! The carriage return (CR) is different between s1p, s2p and s3p, s4p files!
- The comment header (!) includes general information, e.g., type of instrument, measurement time, etc.
- The format line (#) defines the format (mag[dB]/angle[deg], mag/angle, real/imag), stimulus units and the reference impedance
- The column delimiter varies, e.g., space, comma, semicolon, etc.
  - Column order in the example file:  $f\_Hz$   $S11\_dB$   $S11\_deg$   $S21\_dB$   $S21\_deg$   $S12\_dB$   $S12\_deg$   $S22\_dB$   $S22\_deg$

JUAS Proc. 2024  
II.2.7.8, p. 849

- Cascading e.g., 2-port S-parameter networks is important to characterize a larger RF system.
  - Solution: Scattering transfer (T) parameters, which directly relates the waves at input and output
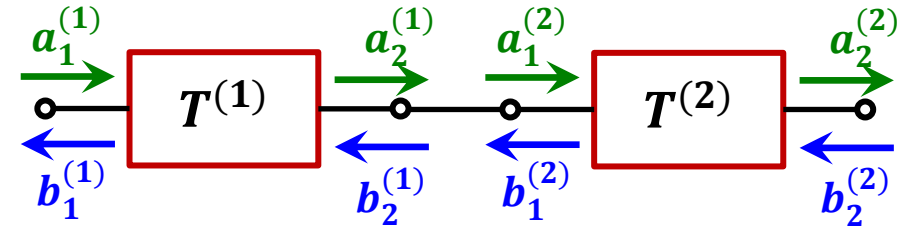
$$(T) = \begin{pmatrix} T_{11} & T_{12} \\ T_{12} & T_{22} \end{pmatrix} \Rightarrow \begin{aligned} b_1 &= T_{11}a_2 + T_{12}b_2 \\ a_1 &= T_{21}a_2 + T_{22}b_2 \end{aligned}$$



- T-parameters enable cascaded 2-port networks by simply multiplying their matrices:

$$(T) = (T^{(1)})(T^{(2)}) \dots (T^{(N)})$$

- Relation between 2-port **T-parameters** and **S-parameters**:

$$(T) = \frac{1}{S_{21}} \begin{pmatrix} -\det(S) & S_{11} \\ -S_{22} & 1 \end{pmatrix}$$


with:  $\det(S) = S_{11}S_{22} - S_{12}S_{21}$

$$(S) = \frac{1}{T_{22}} \begin{pmatrix} T_{12} & \det(T) \\ 1 & -T_{21} \end{pmatrix}$$

with:  $\det(T) = T_{11}T_{22} - T_{12}T_{21}$

- Also called “chain” parameters, used for cascading networks based on V and I
  - Useful for chaining a mix of lumped elements and transmission-lines
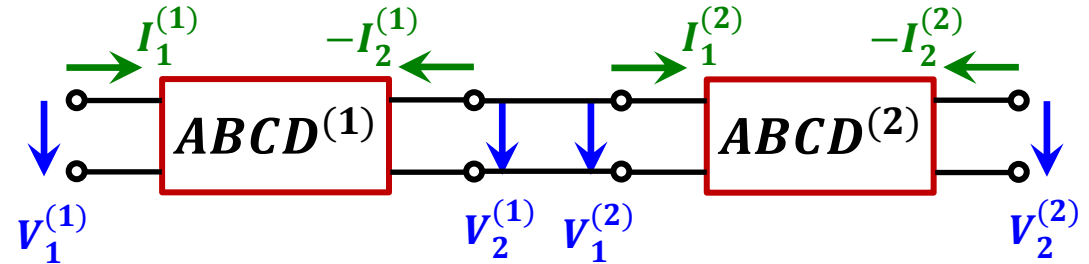
$$(ABCD) = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \Rightarrow \begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$



- Chaining 2-port ABCD-parameter networks:

$$(ABCD) = (ABCD^{(1)})(ABCD^{(2)}) \dots (ABCD^{(N)})$$

Please try to follow  
Example II.2.7.3  
JUAS Proc. 2024  
II.2.7.10, p. 852/853

- Relation between 2-port **ABCD-parameters**


$$(T) = \frac{1}{2S_{21}} \begin{pmatrix} (1 + S_{11})(1 - S_{22}) + S_{12}S_{21} & [(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}]Z_0 \\ [(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}]/Z_0 & (1 - S_{11})(1 + S_{22}) + S_{12}S_{21} \end{pmatrix}$$

and **S-parameters**:


$$(S) = \frac{1}{A + B/Z_0 + CZ_0 + D} \begin{pmatrix} A + B/Z_0 - CZ_0 - D & 2(AD - BC) \\ -A + B/Z_0 - CZ_0 + D & -A + B/Z_0 - CZ_0 + D \end{pmatrix}$$



- A general  $n$ -port may include ports of different technologies, i.e., waveguides, as well as TEM transmission-lines, such as coaxial lines, microstrip lines etc.
  - In the frequency range of interest different modes may propagate at each physical port, e.g., several waveguide modes in a rectangular waveguide and/or higher order modes in a coaxial line..
  - Each EM-mode must then be represented by a distinct modal port.
    - This is very important in EM-simulation to ensure the absorption of the energy for all modes!
  - The number of modal ports needed generally, increases with frequency, as more waveguide modes can propagate.

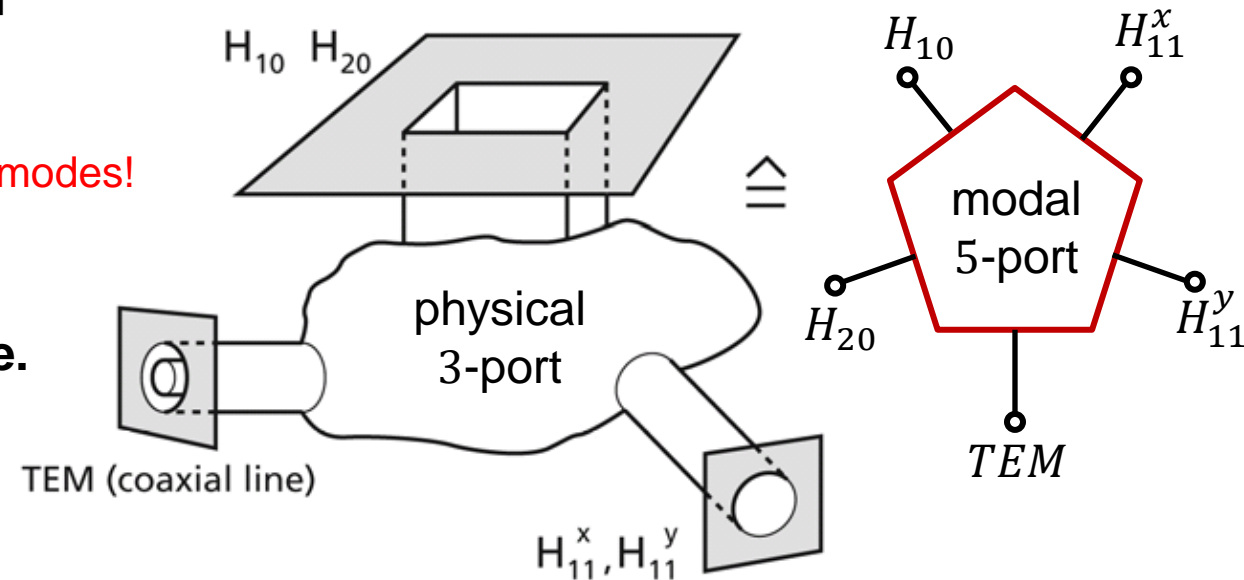

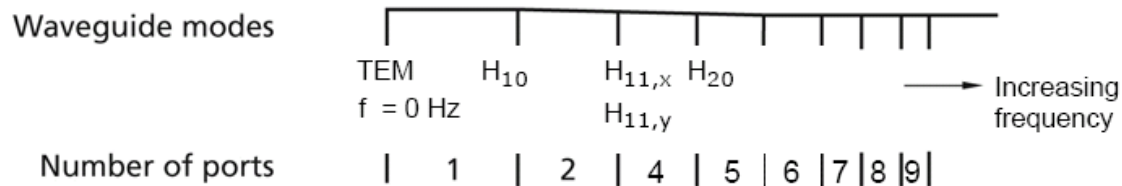$H_{11}^x, H_{11}^y$ :  $x, y$ -polarization of the  $E_{11}$  circular mode



- The scattering (S) parameters are based on incident and reflected normalized complex voltage waves (power waves), defined at the ports of a RF network.
- S-Parameters are used to characterize a linear, time-invariant RF component, circuit or sub-system as function of frequency under realistic operational conditions
  - The S-parameters are given in a matrix notation, and have complex values
- The characteristic of the S-matrix may provide additional details about the network, such as reciprocity, symmetry, losses.
- Typically, the S-parameters matrix of a RF network is acquired by measurement characterization with a vector network analyzer (VNA), or by a numerical analysis, e.g., circuit analysis or electromagnetic simulation software
- The S-parameter matrices of a set of networks can be converted to transfer (T) parameter matrices to enable a simple cascading of those networks
- The number of logical, modal ports might be higher than the number of physical ports for a general RF network utilizing various transmission-line technologies.


# Backup Slides

- Its simplest form is for a passive **1-port network**:

$$(S) = S_{11} \Rightarrow b_1 = S_{11}a_1$$

- with the reflection coefficient:

$$\Gamma = S_{11} = \frac{b_1}{a_1}$$

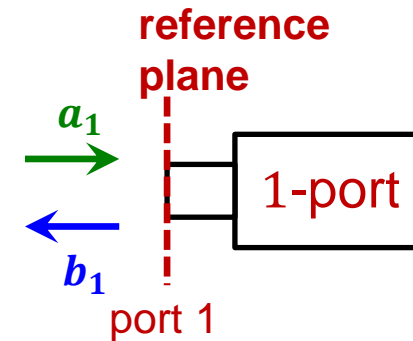


- Most popular is the **2-port network**:


$$(S) = \begin{pmatrix} S_{11} & S_{12} \\ S_{12} & S_{22} \end{pmatrix} \Rightarrow \begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 \end{aligned}$$

- An unmatched load, present at port 2 with a reflection coefficient  $\Gamma_{load}$  transfers to the input port as:
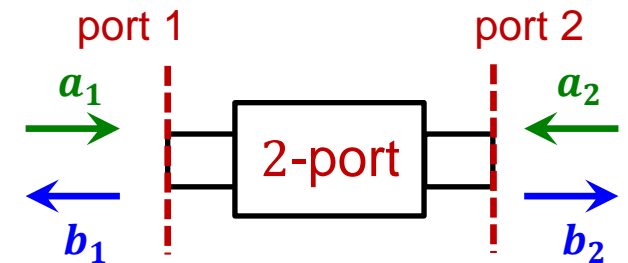
$$\Gamma_{in} = S_{11} + \frac{S_{21}\Gamma_{load}S_{12}}{1 - S_{22}\Gamma_{load}}$$



## 2-port series-network

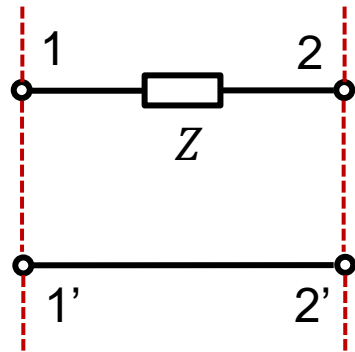

$$(S) = \frac{1}{2Z_0 + Z} \begin{pmatrix} Z & 2Z_0 \\ 2Z_0 & Z \end{pmatrix}$$

$$S_{11} = S_{22} \wedge S_{12} = S_{21}$$

$$Z = j\omega L = j10$$

$$Z = R = 10$$

$$|S_{11}| = \sqrt{1 - |S_{12}|^2}$$

$$\frac{1}{\sqrt{101}} = \sqrt{1 - \left(\frac{10}{\sqrt{101}}\right)^2}$$

$$\frac{1}{11} \neq \sqrt{1 - \left(\frac{10}{11}\right)^2}$$

$$\angle S_{11} - \angle S_{12} = \angle S_{21} - \angle S_{22} - \pi$$

$$\tan^{-1}(10) + \tan^{-1}\frac{1}{10} = -\tan^{-1}\frac{1}{10} - \tan^{-1}(10) - \pi$$

$$0 - 0 \neq 0 - 0 - \pi$$

⇒ **lossless**

⇒ **lossy**

## 4-port ideal directional coupler


$$(S) = \frac{1}{2} \begin{pmatrix} 0 & \sqrt{3} & j & 0 \\ \sqrt{3} & 0 & 0 & j \\ j & 0 & 0 & \sqrt{3} \\ 0 & j & \sqrt{3} & 0 \end{pmatrix}$$

- It is evident, this ideal 4-port coupler is symmetric and reciprocal

$$S_{ij} = S_{ji} \wedge S_{ii} = S_{jj}$$

- It also is matched:  $S_{ii} = 0$
- But is it lossless or lossy?

## 2-port series-network

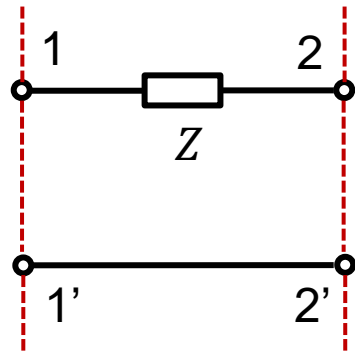

$$(S_{ser}) = \frac{1}{2Z_0 + Z} \begin{pmatrix} Z & 2Z_0 \\ 2Z_0 & Z \end{pmatrix}$$

$$S_{11} = S_{22} \wedge S_{12} = S_{21}$$

$$Z = j\omega L = j10$$

$$Z = R = 10$$

$$|S_{11}| = \sqrt{1 - |S_{12}|^2}$$

$$\frac{1}{\sqrt{101}} = \sqrt{1 - \left(\frac{10}{\sqrt{101}}\right)^2}$$

$$\frac{1}{11} \neq \sqrt{1 - \left(\frac{10}{11}\right)^2}$$

$$\angle S_{11} - \angle S_{12} = \angle S_{21} - \angle S_{22} - \pi$$

$$\tan^{-1}(10) + \tan^{-1}\frac{1}{10} = -\tan^{-1}\frac{1}{10} - \tan^{-1}(10) - \pi$$

$$0 - 0 \neq 0 - 0 - \pi$$

⇒ lossless

⇒ lossy

## 4-port ideal directional coupler

$$(S_{dc}) = \frac{1}{2} \begin{pmatrix} 0 & \sqrt{3} & j & 0 \\ \sqrt{3} & 0 & 0 & j \\ j & 0 & 0 & \sqrt{3} \\ 0 & j & \sqrt{3} & 0 \end{pmatrix}$$

$$(S)^\dagger(S) = (I) \Rightarrow \sum_{k=1}^N S_{ki}S_{ki}^* = 1 \wedge \sum_{k=1}^N S_{ki}S_{kj}^* = 0 \forall i \neq j$$

- Multiply matrix columns by itself with the conjugate complex  
– and test for = 1


$$S_{11}S_{11}^* + S_{21}S_{21}^* + S_{31}S_{31}^* + S_{41}S_{41}^* = (0 \cdot 0 + \sqrt{3} \cdot \sqrt{3} + j \cdot (-j) + 0 \cdot 0)/2^2 = 1$$

$$S_{12}S_{12}^* + S_{22}S_{22}^* + S_{32}S_{32}^* + S_{42}S_{42}^* = (\sqrt{3} \cdot \sqrt{3} + 0 \cdot 0 + 0 \cdot 0 + j \cdot (-j))/2^2 = 1$$

$$S_{13}S_{13}^* + S_{23}S_{23}^* + S_{33}S_{33}^* + S_{43}S_{43}^* = (j \cdot (-j) + 0 \cdot 0 + 0 \cdot 0 + \sqrt{3} \cdot \sqrt{3})/2^2 = 1$$

$$S_{14}S_{14}^* + S_{24}S_{24}^* + S_{34}S_{34}^* + S_{44}S_{44}^* = (0 \cdot 0 + j \cdot (-j) + \sqrt{3} \cdot \sqrt{3} + 0 \cdot 0)/2^2 = 1$$

## 2-port series-network

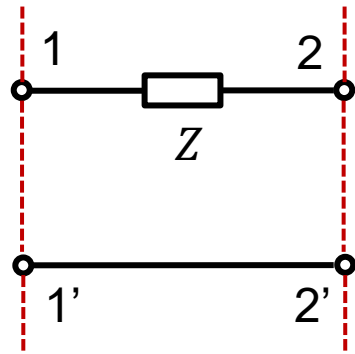

$$(S_{ser}) = \frac{1}{2Z_0 + Z} \begin{pmatrix} Z & 2Z_0 \\ 2Z_0 & Z \end{pmatrix}$$

$$S_{11} = S_{22} \wedge S_{12} = S_{21}$$

$$Z = j\omega L = j10$$

$$Z = R = 10$$

$$|S_{11}| = \sqrt{1 - |S_{12}|^2}$$

$$\frac{1}{\sqrt{101}} = \sqrt{1 - \left(\frac{10}{\sqrt{101}}\right)^2}$$

$$\frac{1}{11} \neq \sqrt{1 - \left(\frac{10}{11}\right)^2}$$

$$\angle S_{11} - \angle S_{12} = \angle S_{21} - \angle S_{22} - \pi$$

$$\tan^{-1}(10) + \tan^{-1}\frac{1}{10} = -\tan^{-1}\frac{1}{10} - \tan^{-1}(10) - \pi$$

$$0 - 0 \neq 0 - 0 - \pi$$

⇒ **lossless**

⇒ **lossy**

## 4-port ideal directional coupler

$$(S_{dc}) = \frac{1}{2} \begin{pmatrix} 0 & \sqrt{3} & j & 0 \\ \sqrt{3} & 0 & 0 & j \\ j & 0 & 0 & \sqrt{3} \\ 0 & j & \sqrt{3} & 0 \end{pmatrix}$$

$$(S)^\dagger(S) = (I) \Rightarrow \sum_{k=1}^N S_{ki}S_{ki}^* = 1 \wedge \sum_{k=1}^N S_{ki}S_{kj}^* = 0 \forall i \neq j$$

- **Multiply all different matrix columns with the conjugate complex**
  - and test for = 0

$$S_{11}S_{12}^* + S_{21}S_{22}^* + S_{31}S_{32}^* + S_{41}S_{42}^* = (0 \cdot \sqrt{3} + \sqrt{3} \cdot 0 + j \cdot 0 + 0 \cdot (-j))/2^2 = 0$$

$$S_{11}S_{13}^* + S_{21}S_{23}^* + S_{31}S_{33}^* + S_{41}S_{43}^* = (0 \cdot (-j) + \sqrt{3} \cdot 0 + j \cdot 0 + 0 \cdot \sqrt{3})/2^2 = 0$$

$$S_{11}S_{14}^* + S_{21}S_{24}^* + S_{31}S_{34}^* + S_{41}S_{44}^* = (0 \cdot 0 + \sqrt{3} \cdot (-j) + j \cdot \sqrt{3} + 0 \cdot 0)/2^2 = 0$$

$$S_{12}S_{13}^* + S_{22}S_{23}^* + S_{32}S_{33}^* + S_{42}S_{43}^* = (\sqrt{3} \cdot (-j) + 0 \cdot 0 + 0 \cdot 0 + j \cdot \sqrt{3})/2^2 = 0$$

$$S_{12}S_{14}^* + S_{22}S_{24}^* + S_{32}S_{34}^* + S_{42}S_{44}^* = (\sqrt{3} \cdot 0 + 0 \cdot (-j) + 0 \cdot \sqrt{3} + j \cdot 0)/2^2 = 0$$

$$S_{13}S_{14}^* + S_{23}S_{24}^* + S_{33}S_{34}^* + S_{43}S_{44}^* = (j \cdot 0 + 0 \cdot (-j) + 0 \cdot \sqrt{3} + \sqrt{3} \cdot 0)/2^2 = 0$$