

# **RF Engineering**

## **Introduction to the *Smith* Chart**

***Christine Völlinger & Manfred Wendt – CERN***

- **Signals and reflections on transmission-lines**
  - Reflections effects of pulse signals on transmission-lines due to characteristic-termination impedance mismatch
  - Standing waves on transmission-lines for continuous wave (CW) sinusoidal signals, definition of the reflection coefficient
  - Relation between reflection coefficient, standing wave ration and return loss
- **The *Smith* chart**
  - Refresher: Visualization of a complex impedance in the frequency domain
  - Definition of the *Smith* chart, mapping the complex impedance / admittance plane with the complex reflection coefficient
  - Basic facts and important points on the *Smith* chart
  - Examples for a *RL* and *RC* series circuit, and for a transmission-line terminated with a *RL* series circuit.
  - Operation of a  $\lambda/4$  transformer based on a transmission-line as a (normalized) impedance inverter
- ***Smith* chart exercise (if time permits...)**

Please note the references to the JUAS proceedings!

- **TEM: coaxial cable, PCB stripline, micro-stripline, co-planar waveguide, etc.**
  - but also, **TE / TM: waveguides** (rectangular, circular, elliptical)
- **Transport RF energy (EM waves) from a RF source to a load.**
- **Physical length  $\ell$  becomes relevant for**

$$\ell \gtrsim \frac{\lambda_g}{10}, \quad \text{with guide wavelength: } \lambda_g = \frac{v_p}{f}$$


$f$ : operating frequency (max.)


$$v_p = \frac{1}{\sqrt{L'C'}} = \frac{c}{\sqrt{\epsilon_r}} \text{ propagation velocity}$$

- **Reflections occur if the load impedance  $Z_L$  is not matched to the characteristic impedance  $Z_0$  of the TL**



$$Z_L = Z_0 \Rightarrow \Gamma = 0: \text{no reflections} \text{ 😊}$$
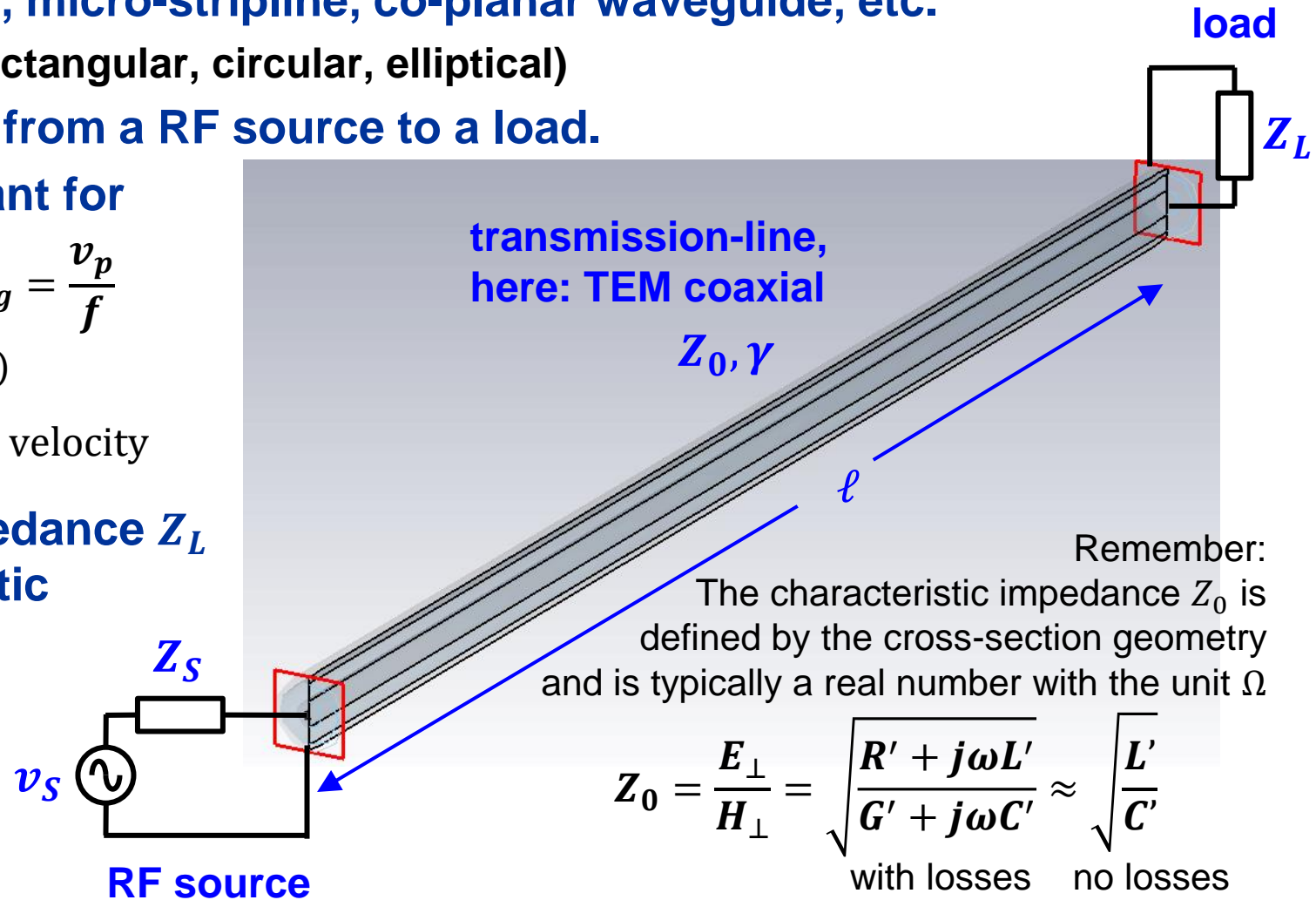
$$Z_L \neq Z_0 \Rightarrow \Gamma \neq 0: \text{reflections!} \text{ 😞}$$



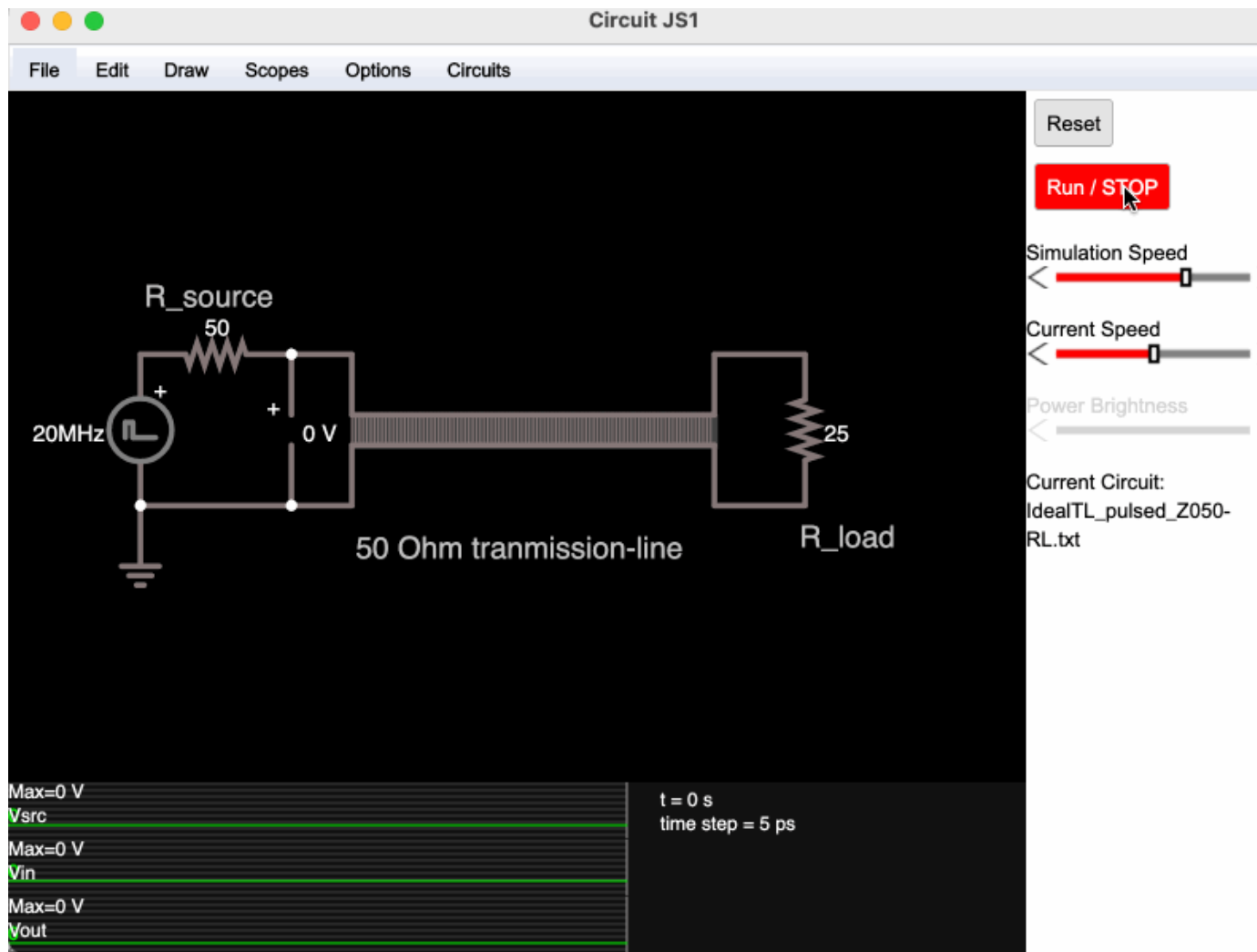

- **Circuit simulator applet:**  
<https://www.falstad.com/circuit/>
  - **Load file:**  
*IdealTL\_DCswitched\_Z050-RL.txt*
    - Change the load resistor value:  
 $R_L = 50, 100, 25 \Omega$
    - Operate the switch and observe the signals at the beginning, and at the end of the transmission-line.
  - **Load file:**  
*IdealTL\_pulsed\_Z050-RL.txt*
    - Change the load resistor value:  
 $R_L = 50, 100, 25 \Omega$
    - Observe the signal waveforms!  
Can you predict the values?!
      - (Press *Run/STOP* and hover with the mouse over the waveform)

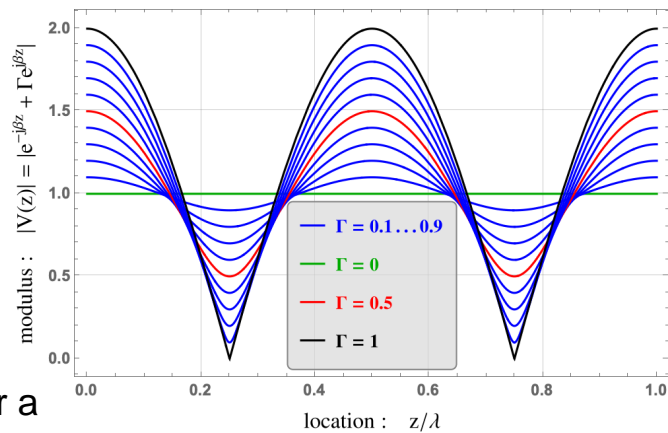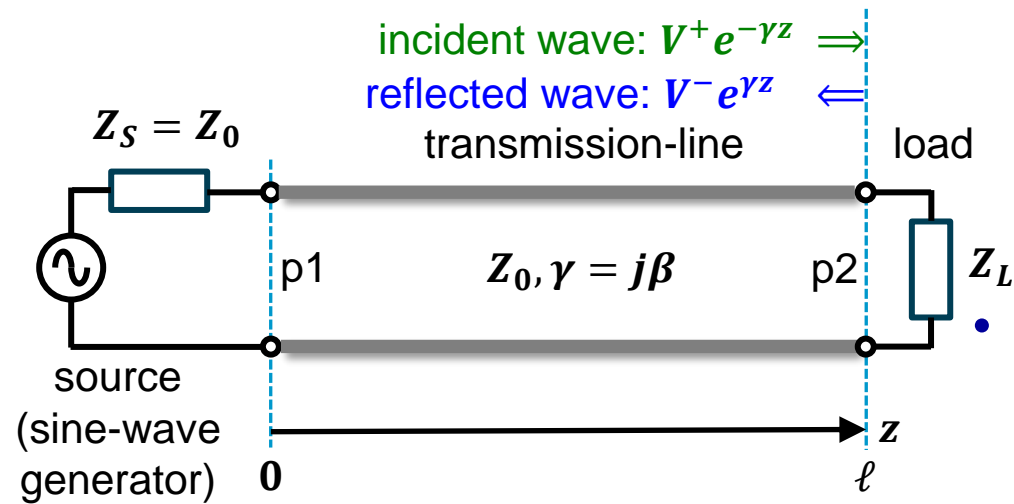

here:  
 $|V(z)|$  for a  
lossless TL  
( $\gamma = j\beta$ )

- For a single frequency, continuous wave (CW) signal on a transmission-line




- Superposition of forward  $a, E^{inc}, V^+$  and backward  $b, E^{refl}, V^-$  traveling waves
- $\Rightarrow$  **standing waves**

## Reflection coefficient $\Gamma$

$$\Gamma = \frac{b}{a} = \frac{E^{refl}}{E^{inc}} = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

waves E-fields voltages impedances

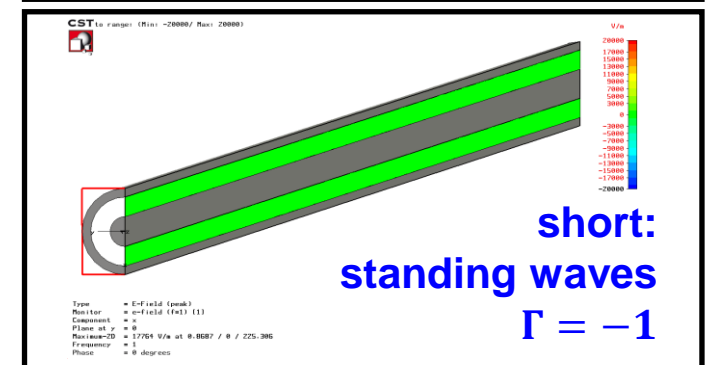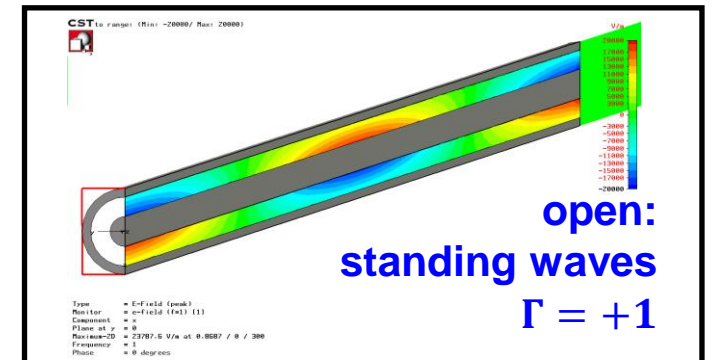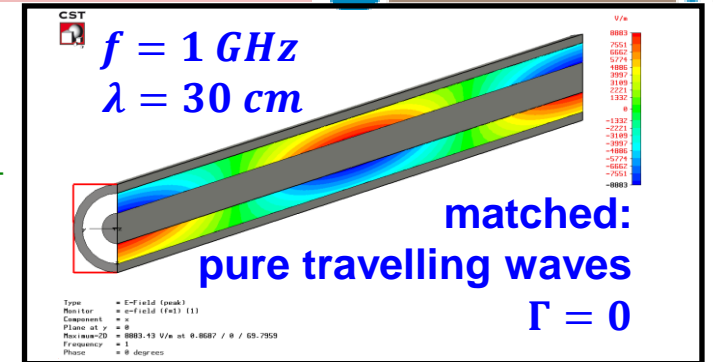- $\Gamma$  is related to the impedance ratio:  $Z_L/Z_0$ 
  - The load impedance  $Z_L$  can be complex
- $\Gamma$  is a complex number
- Reflections also originate due to discontinuities of the TL along  $z$ 
  - Same  $Z_0$  does not prevent reflections! EM-field effect!



- The voltage standing wave ratio (VSWR) expresses the ratio between the maximum and minimum voltage of a standing wave along a transmission-line

$$VSWR = \frac{|V_{max}|}{|V_{min}|} = \frac{|a| + |b|}{|a| - |b|} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \left| \frac{Z_L}{Z_0} \right|$$

with:  $\begin{cases} |V_{max}| = |V^+| + |V^-| \\ |V_{min}| = |V^+| - |V^-| \end{cases}$

symbols: incident (forward) wave:  $a, X^+$   
reflected (backward) wave:  $b, X^-$

- The VSWR is a function of the frequency.

- The return loss (RL) is another way to express reflection effects

$$RL [dB] = 10 \log_{10} \frac{P^+}{P^-} = -20 \log_{10} |\Gamma|$$

$\Gamma$	$VSWR = Z_L/Z_0$	Return Loss [dB]	Refl. Power $ \Gamma ^2$	Inc. Power $1 -  \Gamma ^2$
0.0	1.00	$\infty$	0.00	1.00
0.1	1.22	20.0	0.01	0.99
0.2	1.50	14.0	0.04	0.96
0.3	1.87	10.5	0.09	0.91
0.4	2.33	8.0	0.16	0.84
<b>0.5</b>	<b>3.00</b>	<b>6.0</b>	<b>0.25</b>	<b>0.75</b>
0.6	4.00	4.4	0.36	0.64
0.7	5.67	3.1	0.49	0.51
0.8	9.00	1.9	0.64	0.36
0.9	19.00	0.9	0.81	0.19
1.0	$\infty$	0	1.00	0.00

# Reminder: Circuit Vocabulary

conductor, with:  
**conductance  $G$  [S]**




resistor, with:  
**resistance  $R$  [ $\Omega$ ]**



inductor, with:  
**inductance  $L$  [H]**  
**reactance  $X_L = \omega L$  [ $\Omega$ ]**

**susceptance  $B_L = 1/\omega L$  [S]**

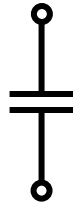

capacitor, with:  
**capacitance  $C$  [F]**  
**susceptance  $B_C = \omega C$  [S]**

**reactance  $X_C = -1/\omega C$  [ $\Omega$ ]**

- Resistance, impedance, reactance are inverse proportional to conductance, susceptance, admittance**


$$R = \frac{1}{G}$$

$$Z = \frac{1}{Y}$$


$$X = -\frac{1}{B}$$




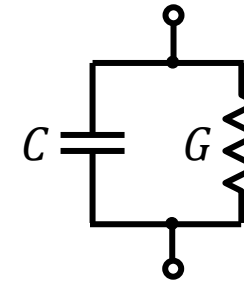
**complex impedance example:**  
 **$Z = R + j\omega L$  [ $\Omega$ ]**



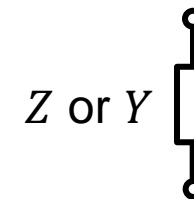**complex admittance example:**  
 **$Y = G + j\omega C$  [S]**






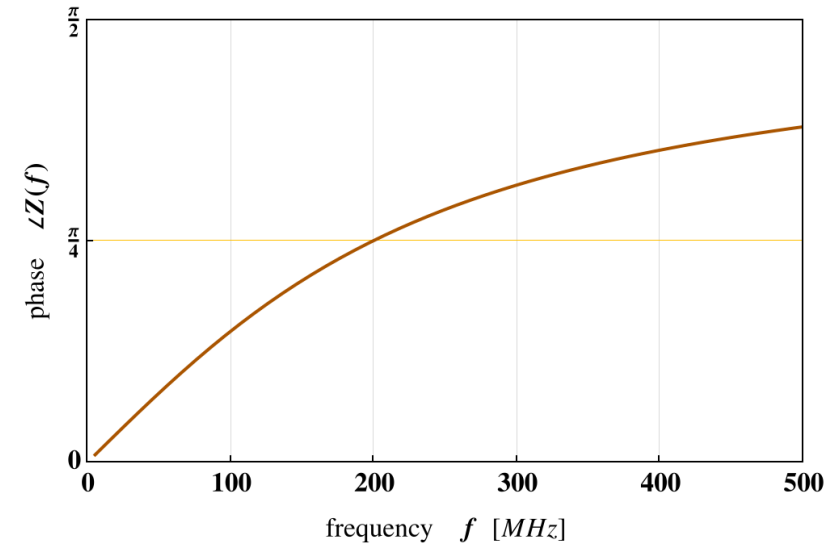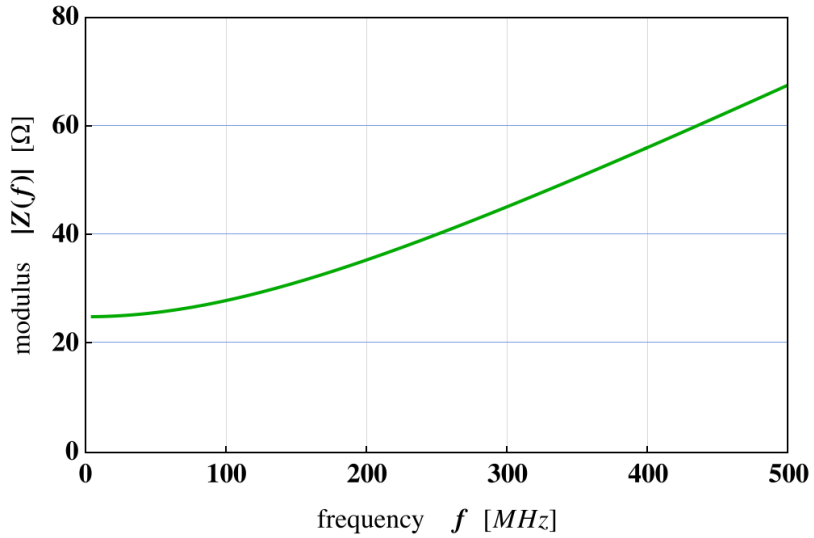complex impedance  $Z$   
or  
complex admittance  $Y$



- Different ways to visualize  $Z(f)$

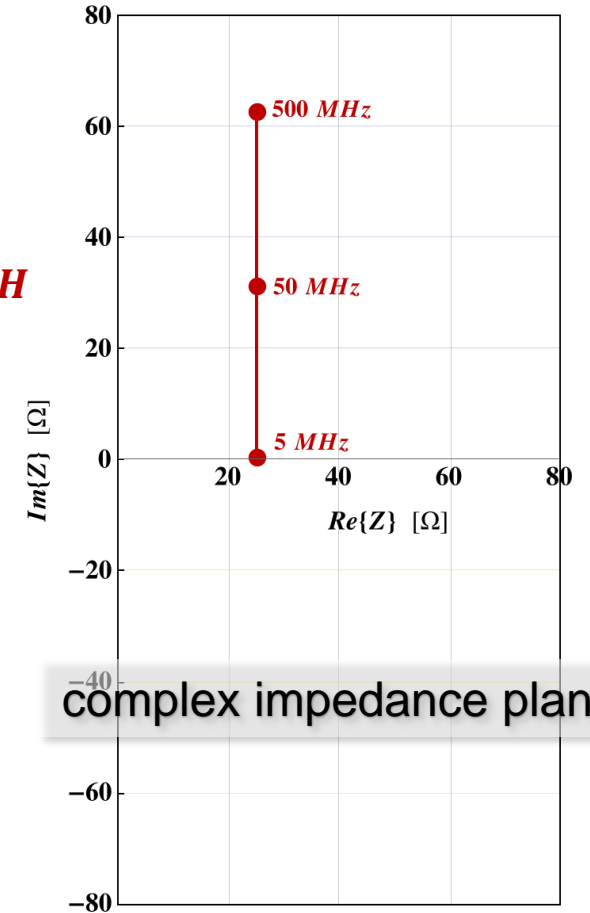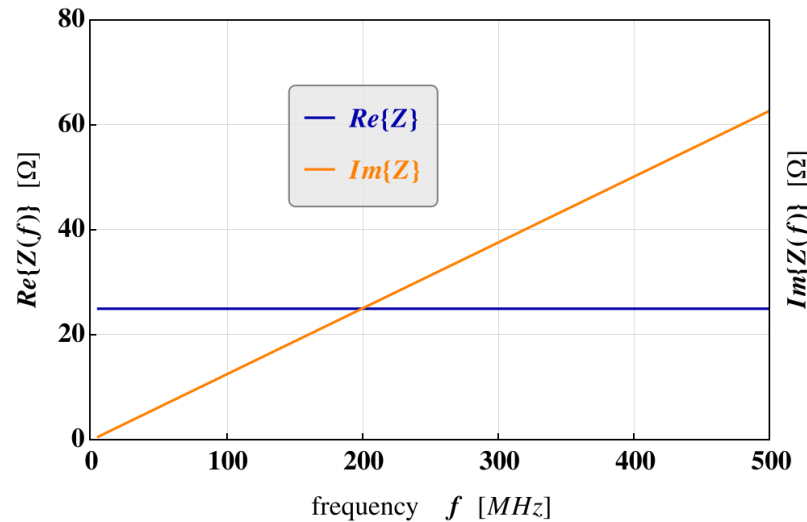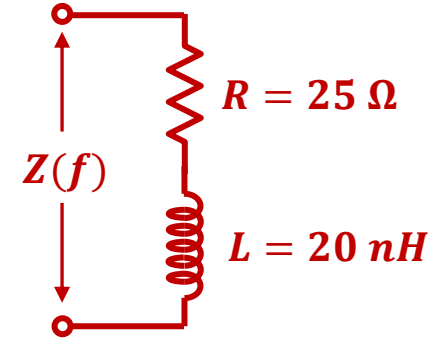- magnitude / phase
- real / imaginary
- complex Z-plane
  - Plot in the complex plane with  $f$  as parameter





complex impedance plane



NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

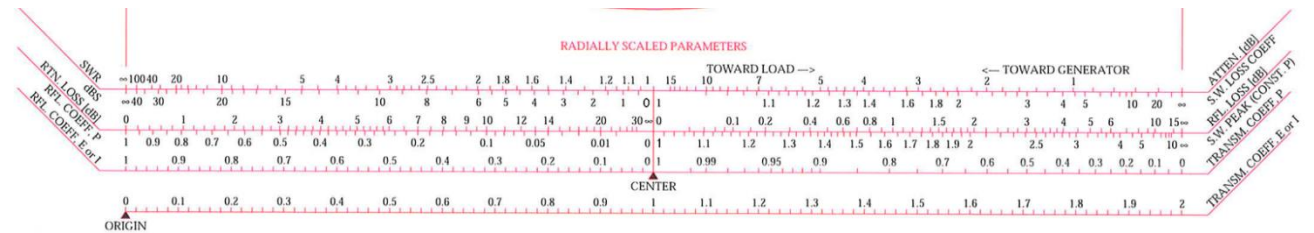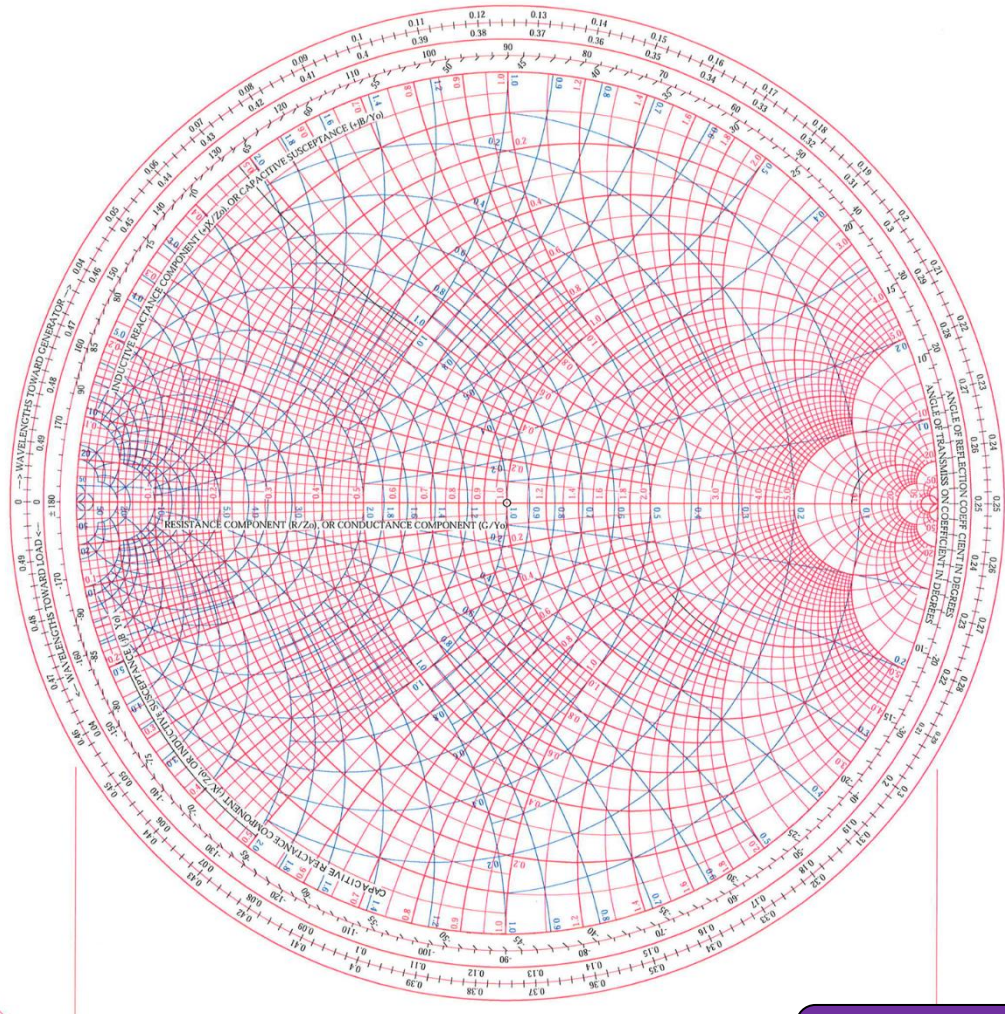
- The *Smith* chart is a calculation tool, divided in 2 parts:
  - A transformation of the complex, normalized **impedance  $z$**  and **admittance  $y$**  planes on a circle.
  - A set of “rulers” below, for additional computations
    - VSWR, return and reflection loss, etc.



- At a 1<sup>st</sup> look the *Smith* chart is quite overwhelming
  - In this introduction the focus is on the **complex  $z$ -plane**
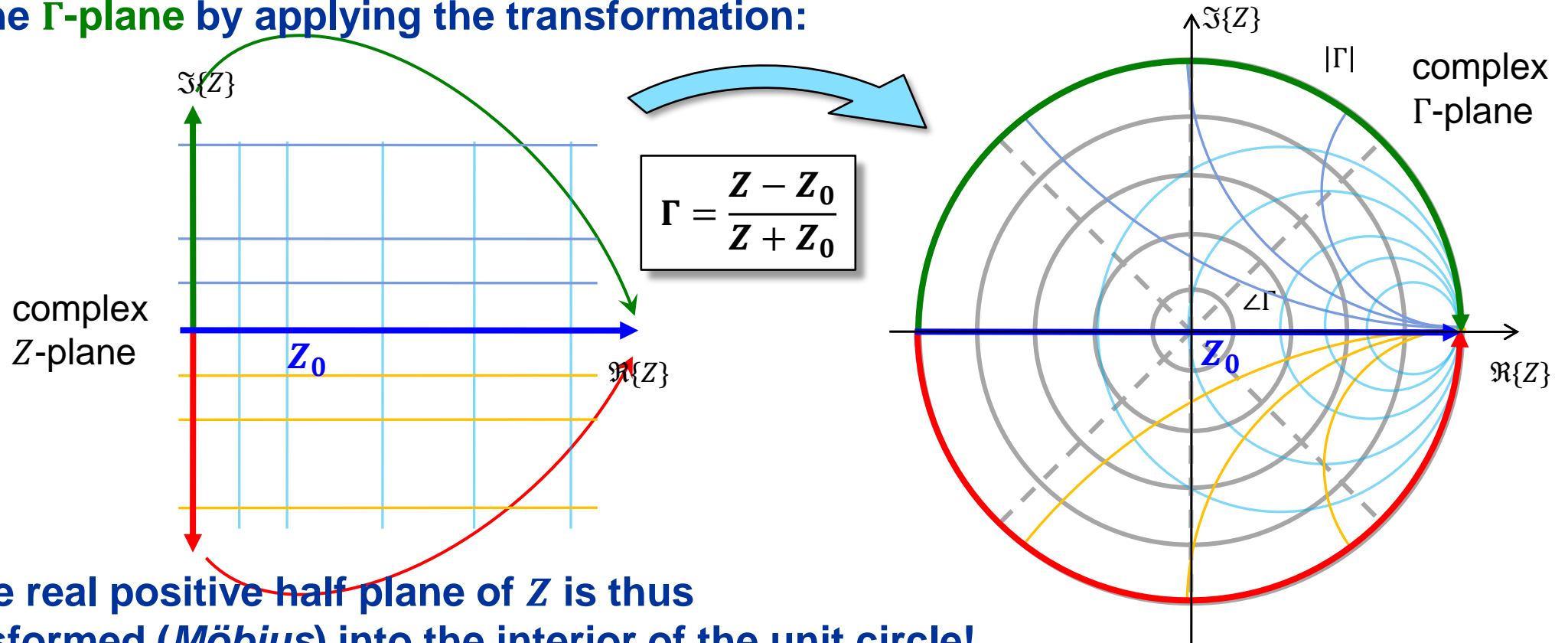
# The Smith Chart (2)

- The **Smith chart** (in impedance / admittance coordinates) represents the **complex  $\Gamma$ -plane** (in polar coordinates) within the unit circle.
- It is a conformal mapping of the **complex  $Z$ -plane** on the  **$\Gamma$ -plane** by applying the transformation:



- $\Rightarrow$  the real positive half plane of  $Z$  is thus transformed (**Möbius**) into the interior of the unit circle!

- In the classic **paper *Smith chart*** the impedance  $Z$  is **normalized**:

$$z = \frac{Z}{Z_0}$$


to a **reference impedance  $Z_0$** ,

typically, to the characteristic impedance of the coaxial cable transmission-lines used in RF / microwave engineering:  $Z_0 = 50 \Omega$ .

- The normalized form of the transformation follows then as:

$$\Gamma = \frac{z - 1}{z + 1} \Rightarrow \frac{Z}{Z_0} = z = \frac{1 + \Gamma}{1 - \Gamma}$$

- The **Smith chart** is a **parametric graph**
  - with the **frequency  $f$**  as parameter
  - and the **normalized, complex impedance  $z$**  and **complex reflection coefficient  $\Gamma$**  as variables
    - also, the normalized, complex admittance  $y = 1/z$  is mapped and can be used as variable.
- **In the past**
  - The ***Smith chart*** was used as a calculation tool for impedance matching, e.g., antennas to transmitters or receivers, amplifier input / output stages, couplers of accelerating cavities, etc.
- **At presence, the *Smith chart* is still popular**
  - for visualization purposes, e.g., vector network analyzer (VNA) measurement of input / output impedances (display of the *Sii* scattering parameters), in software tools, etc., usually using the **un-normalized impedance  $Z$**
  - for the optimization of the coupling between RF source and a cavity resonator.

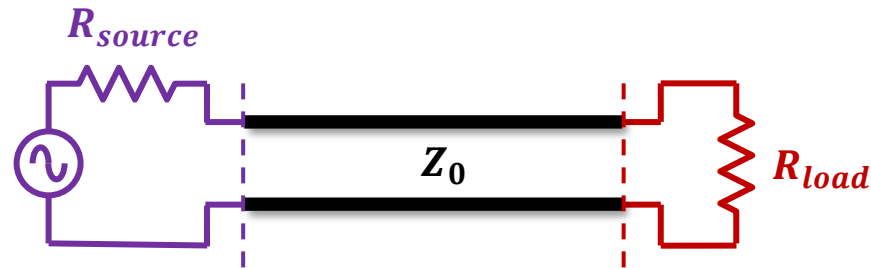


1. No signal reflections are observed at the end of a transmission-line, this means:

- $R_{source} = R_{load}$
- $R_{source} = Z_0$
- $Z_0 = R_{load}$
- $R_{source} = Z_0 = R_{load}$

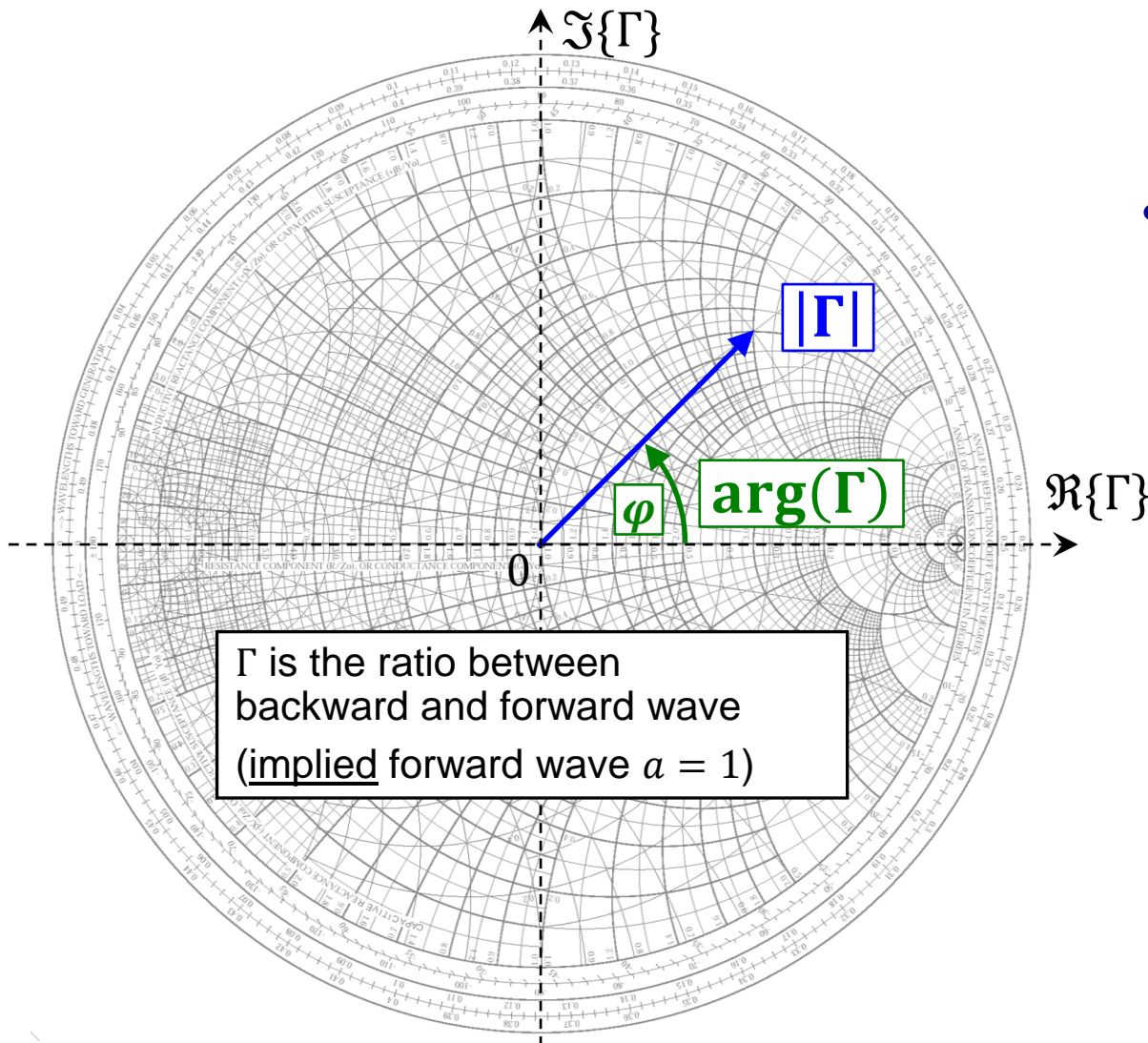2. The Smith chart transforms the  onto the complex Gamma (reflection coefficient) plane within the unit circle.





- In the *Smith* chart, the **complex reflection factor**


$$\Gamma = |\Gamma| e^{j\varphi} = \frac{b}{a}$$

is expressed in linear **polar coordinates**, representing the ratio of backward  $b$  vs. forward  $a$  traveling waves.

- The distance from the center of the diagram is directly proportional to the **magnitude of the reflection factor  $|\Gamma|$**  and permits an easy visualization of the **matching performance**.
  - In particular, the perimeter of the diagram represents total reflection:  $|\Gamma| = 1$ .
  - (power dissipated in the load) = (forward power) – (reflected power)

$$\begin{aligned}
 P &= |a|^2 - |b|^2 \\
 &= |a|^2 (1 - |\Gamma|^2)
 \end{aligned}$$

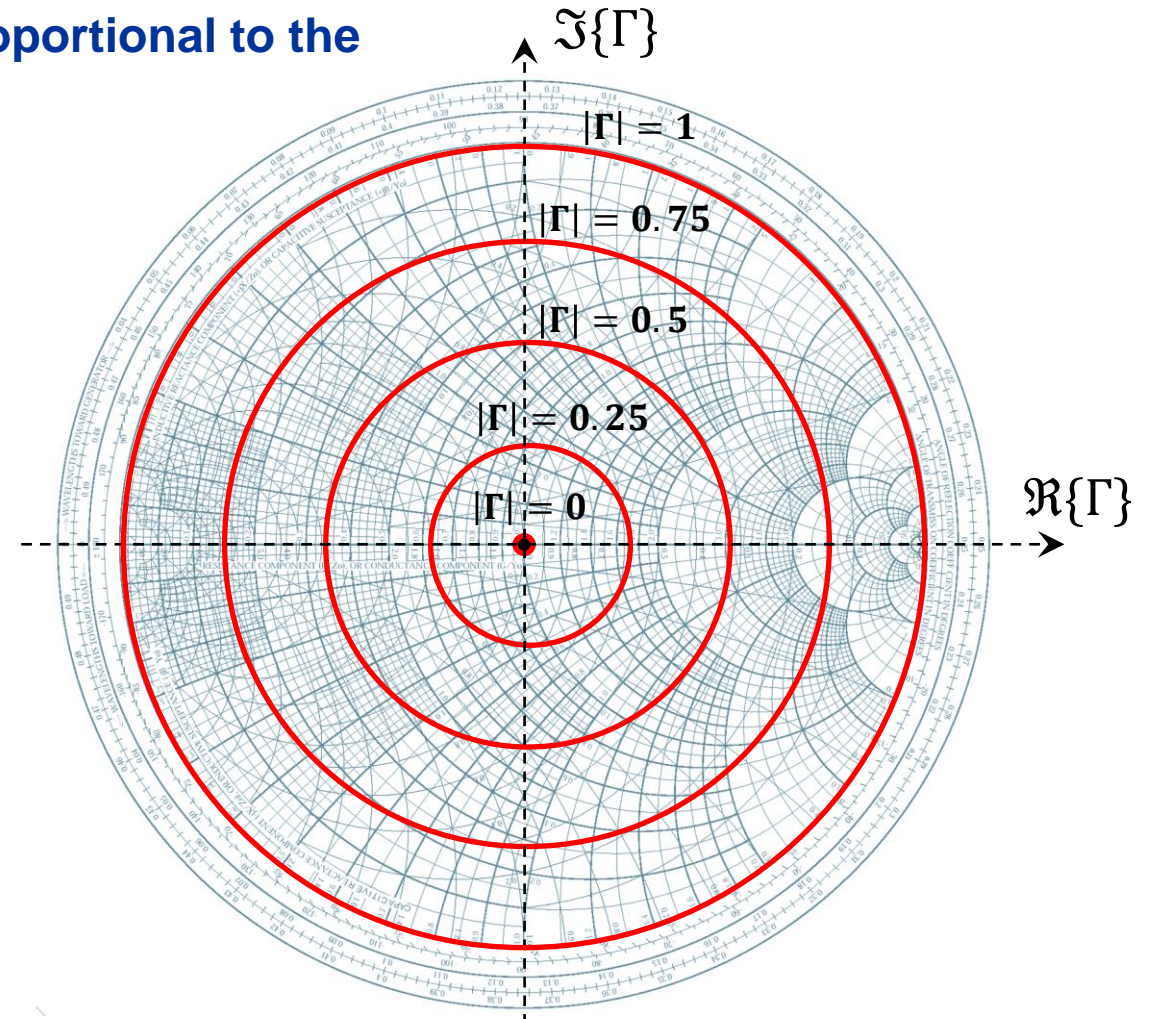
↑ available source power      ↑ mismatch losses






## Important Points:


- **Short Circuit**  
 $\Gamma = -1, z = 0$
- **Open Circuit**  
 $\Gamma = +1, z \rightarrow \infty$
- **Matched Load**  
 $\Gamma = 0, z = 1$
- **On the circle  $|\Gamma| = 1$ :  
lossless element**
- **Upper half:**  
”inductive” =  
**positive imaginary part of  $Z$**
- **Lower half:**  
”capacitive” =  
**negative imaginary part of  $Z$** 
  - **Outside the circle,  $\Gamma > 1$ :**  
active element, e.g., tunnel diode reflection amplifier

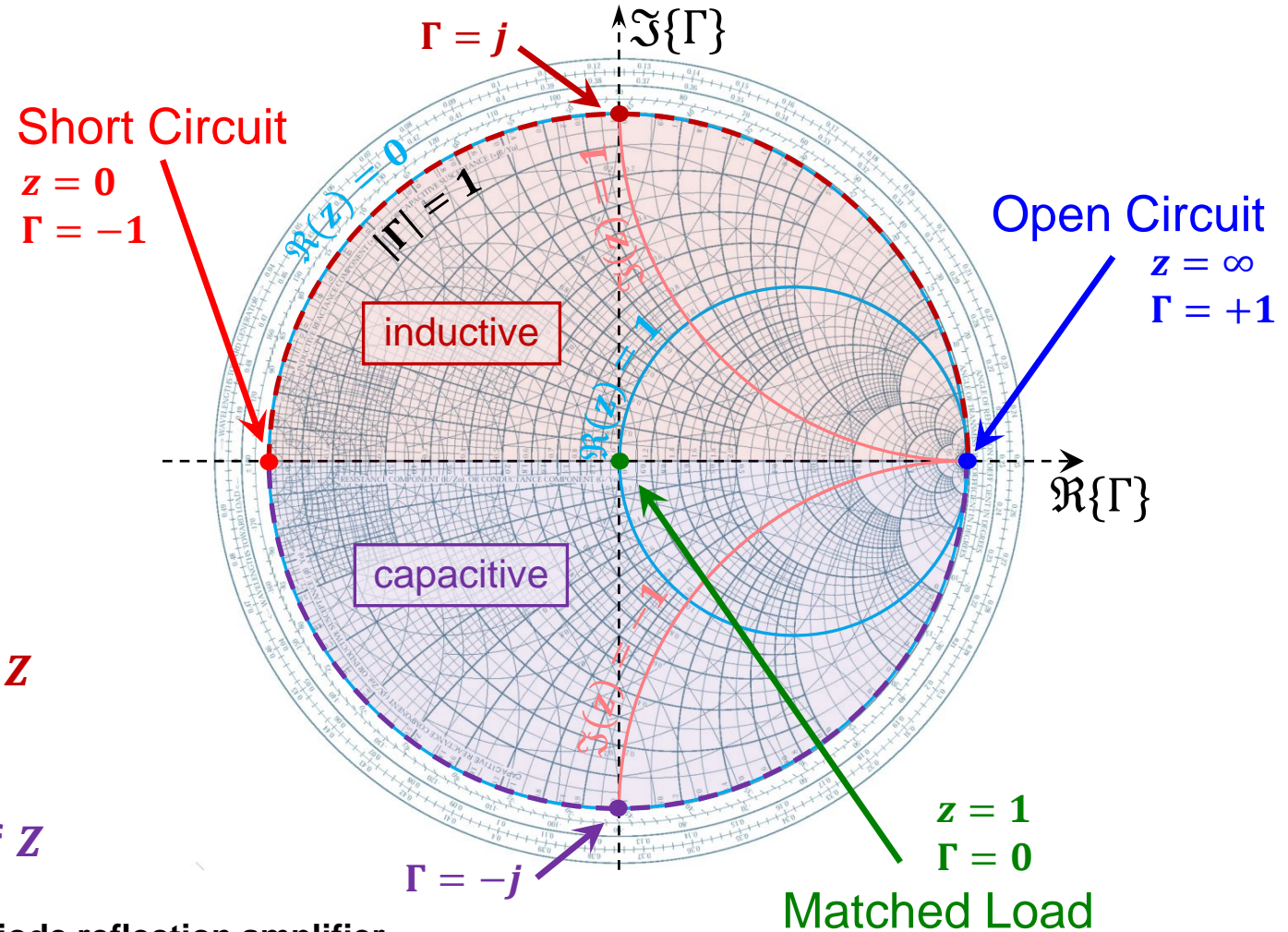

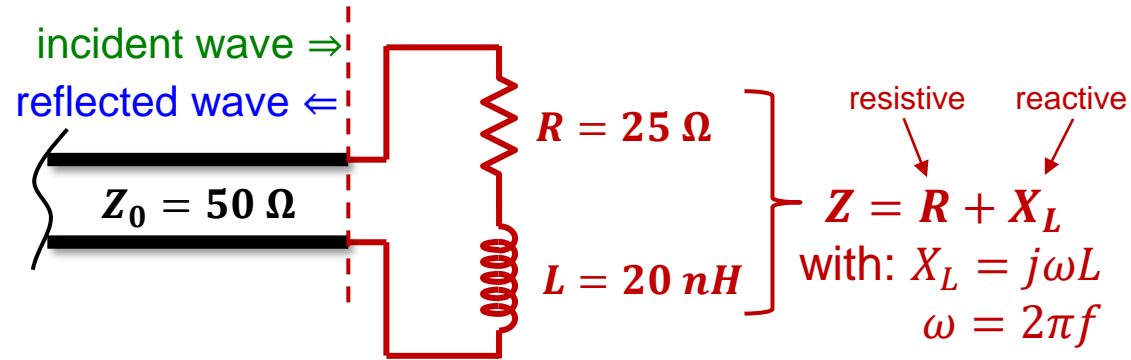

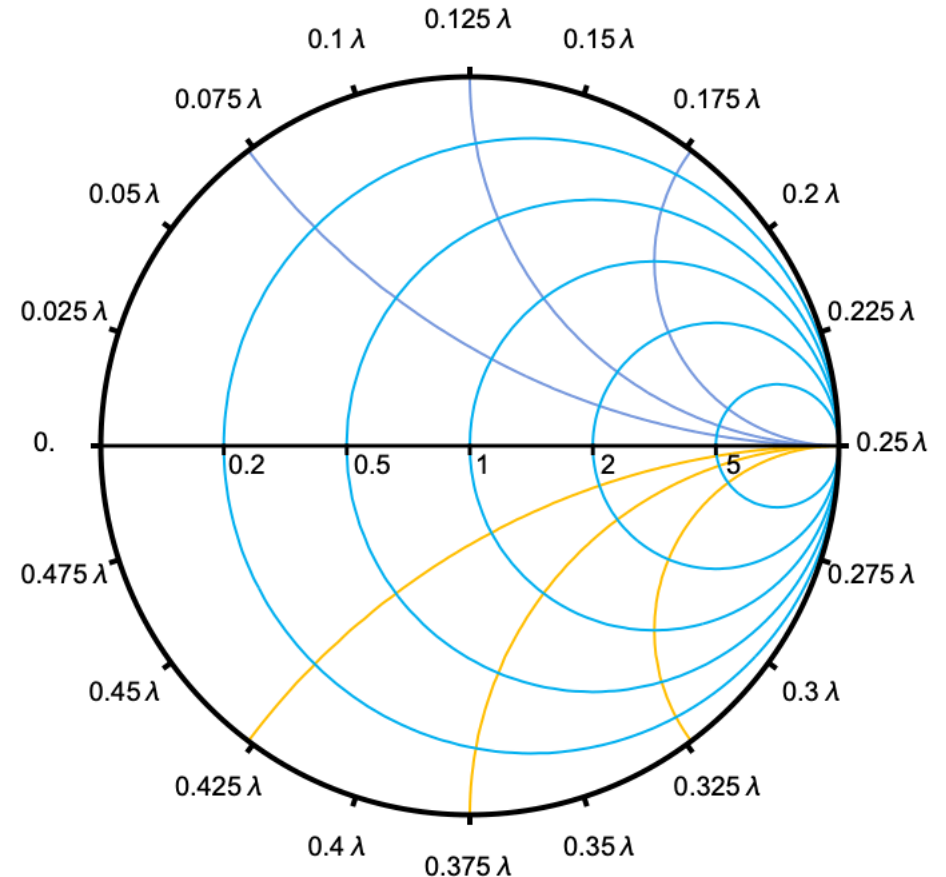
## Complex impedance based on lumped element components



- Calculate  $Z$  for a given frequency, e.g.,  
 $f = 50 \text{ MHz}$ :  $Z = (25 + j6.28) \Omega$
- Calculate the normalized impedance  
 $z = Z/Z_0 = 0.5 + j0.126$ 
  - Locate  $z$  in the Smith chart
  - Retrieve  $\Gamma = 0.34 \angle 161^\circ = 0.34e^{j2.81}$
- Repeat for other frequencies...





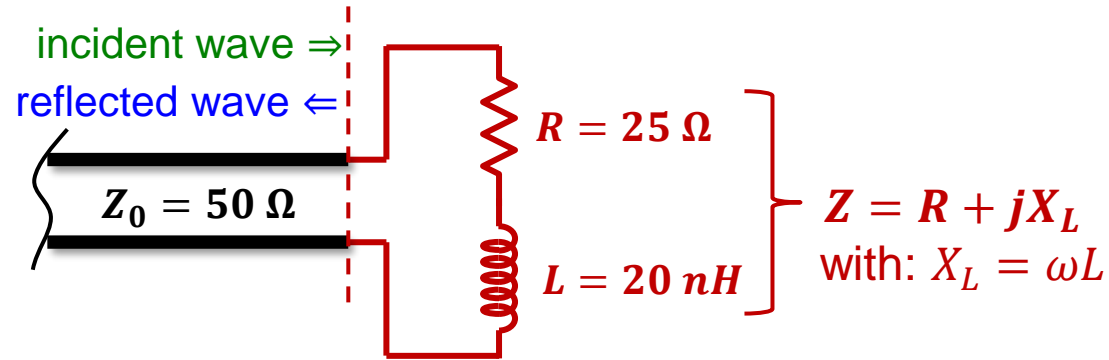


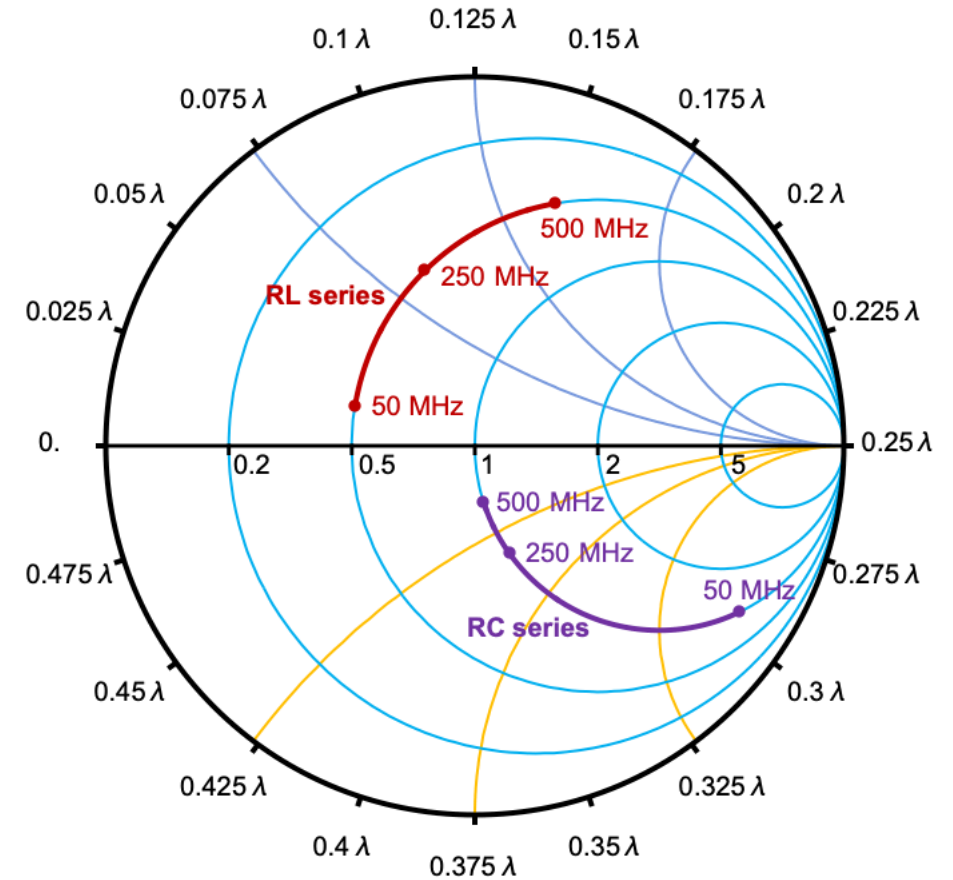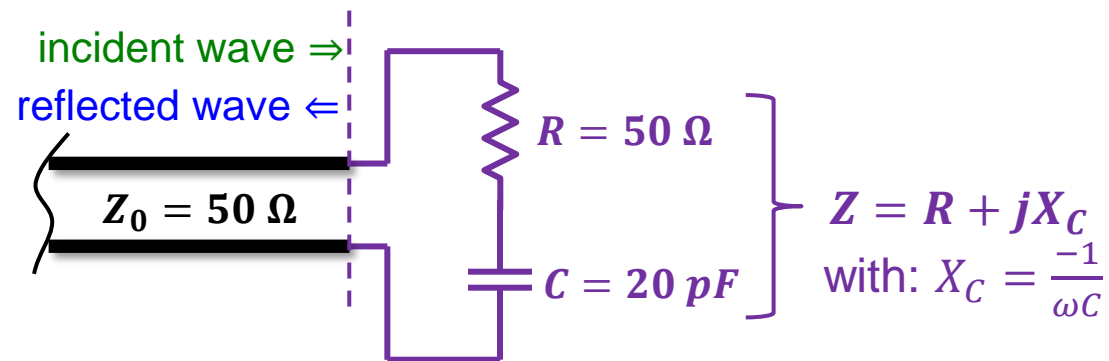- ...and for different component values and circuit combinations



# Quiz (2)


Prompts	Possible Answers
A. Point A	1. $\Gamma = +1, z \rightarrow \infty$
B. Point B	2. $\Gamma = -j$
C. Point C	3. $\Gamma = 0, z = 1$ , match
D. Point D	4. Point in the capacitive half plane
E. Point E	5. $\Gamma = +j$
	6. $\Gamma = -1, z = 0$
	7. Point in the inductive half plane

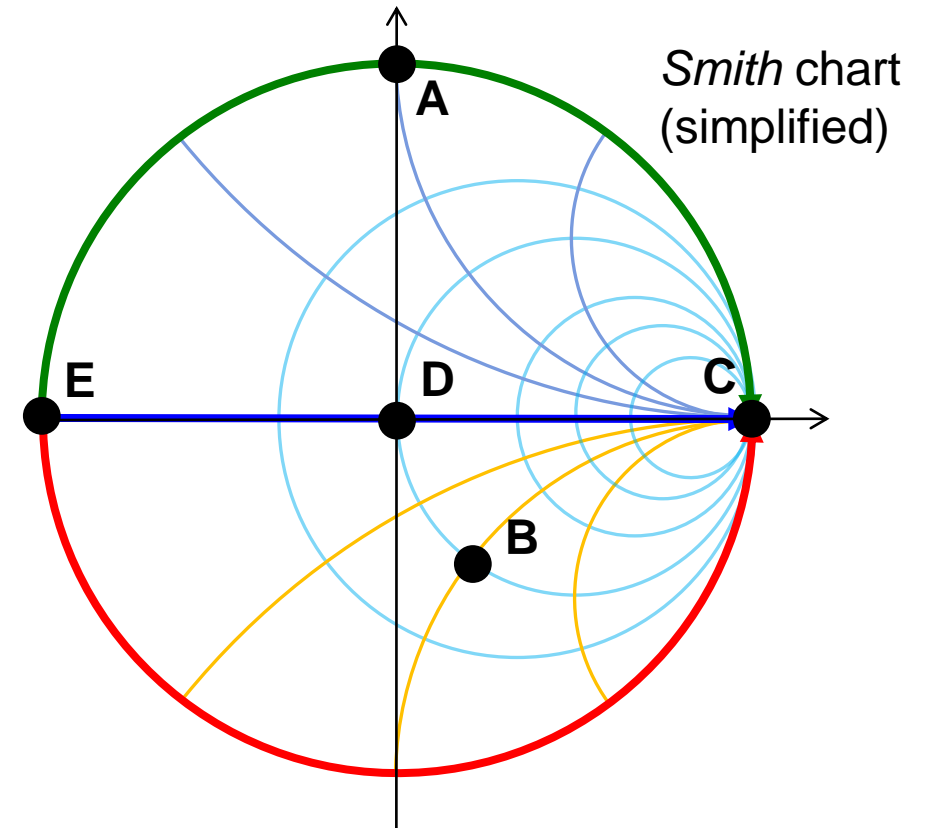

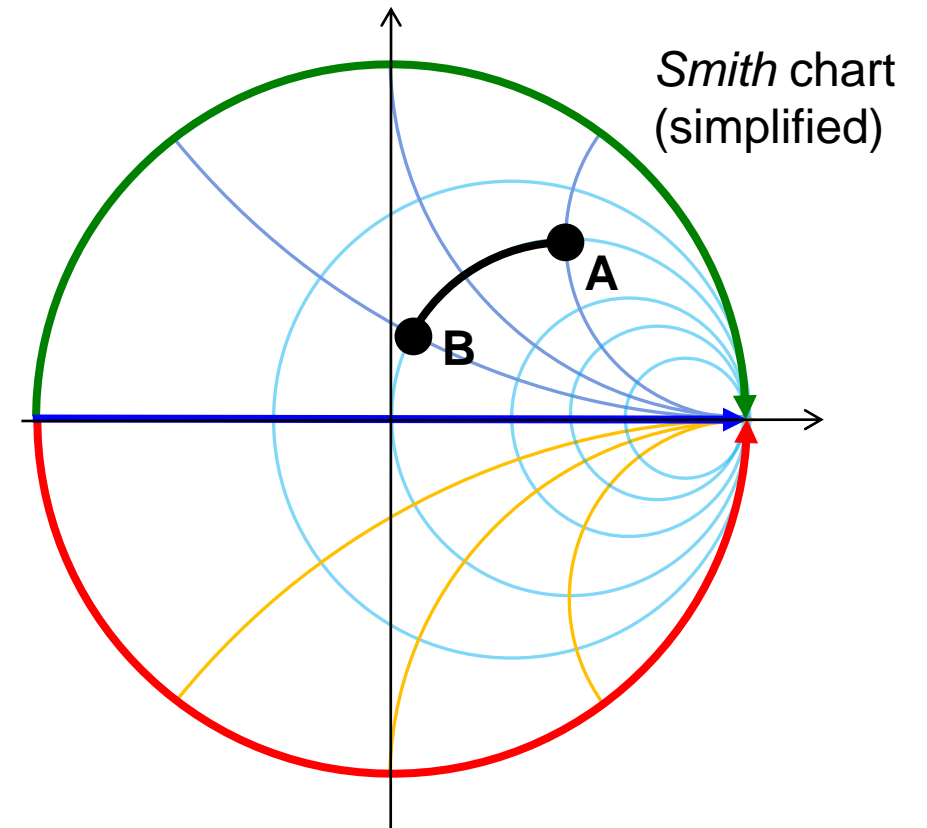
#### 4. Trace with marker points in the simplified *Smith chart* for an RL series impedance

- $f_B > f_A$
- $f_B < f_A$
- There is no frequency  $f$  related to points A and B
- $f_A = f_B$

Please try to complete  
Exercise II.2.6.2  
JUAS Proc. 2024  
II.2.6.3, p. 820



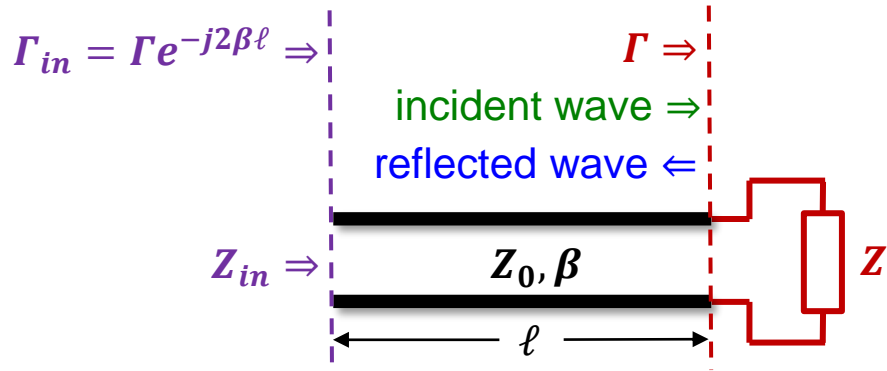

- **S-parameter of a lossless transmission-line:**

$$S = \begin{bmatrix} 0 & e^{-j\beta\ell} \\ e^{-j\beta\ell} & 0 \end{bmatrix}$$

forward transmission coefficient S21

backward transmission coefficient S12

– Phase delay (electrical length) of

$$\beta\ell = \theta$$


with:  $\beta = \frac{2\pi}{\lambda_g} = k$  (wave number)

- The lossless transmission-line adds a phase delay of  $2\beta\ell$ , seen at its input,  $\Gamma_{in}$ , to the reflection coefficient  $\Gamma$  at its output:

$$\Gamma_{in} = \Gamma e^{-j2\beta\ell}$$


- This results in a transformation of the impedance  $Z$  at the end of the line to a different impedance  $Z_{in}$  at the input of the line

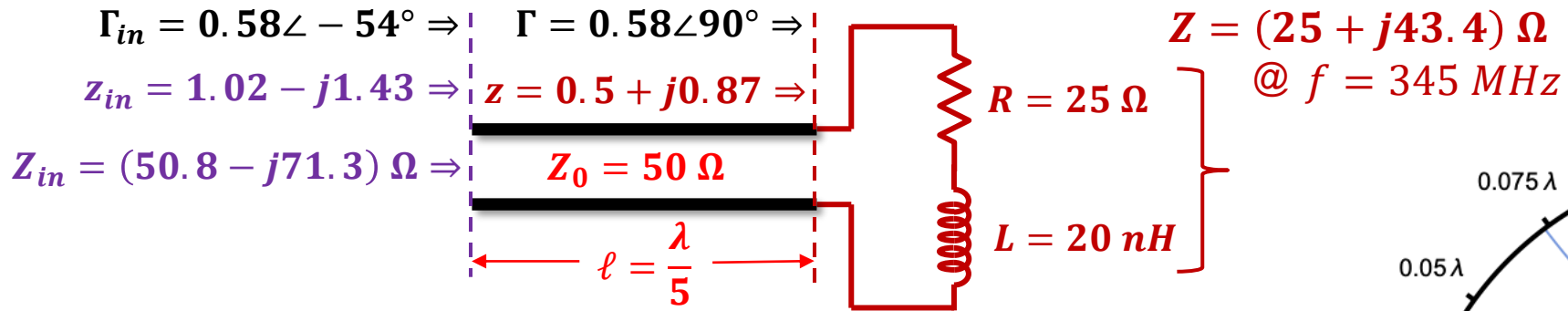
- The *Smith* chart offers an effective, simple graphical way to calculate this transmission-line based impedance transformation



Based on the previous example

- Calculate the normalized impedance  $z$  for  $f = 345 \text{ MHz}$  and locate the point in the Smith chart.
  - Notice the corresponding value of  $\Gamma$ , and read the  $\lambda$ -length value on the rim
- Add  $\ell = \lambda/5$  by rotating  $\Gamma$  by  $2\beta\ell = 4\pi/5 \equiv 144^\circ$ 
  - From  $0.125 \lambda$  to  $0.325 \lambda$ 
    - The phase is subtracted, therefore clockwise rotation!
- Notice the value of  $\Gamma_{in}$  and read the corresponding value of the normalized impedance  $z_{in}$ 
  - Calculate the transformed impedance  $Z_{in}@f = 345 \text{ MHz}$
  - What is the equivalent circuit, and what are the component values?
    - ...and what is the physical length  $\ell$  of the transmission-line?
      - assuming a coaxial cable as transmission-line with a dielectric constant of  $\epsilon_r = 2.1$

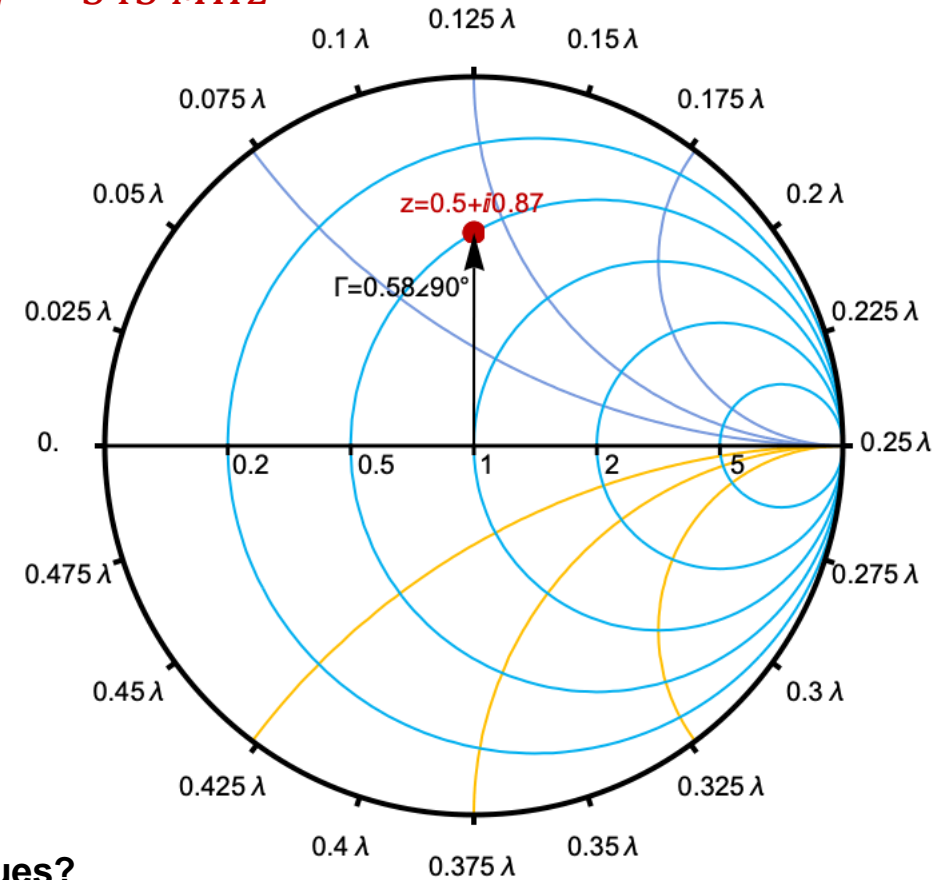

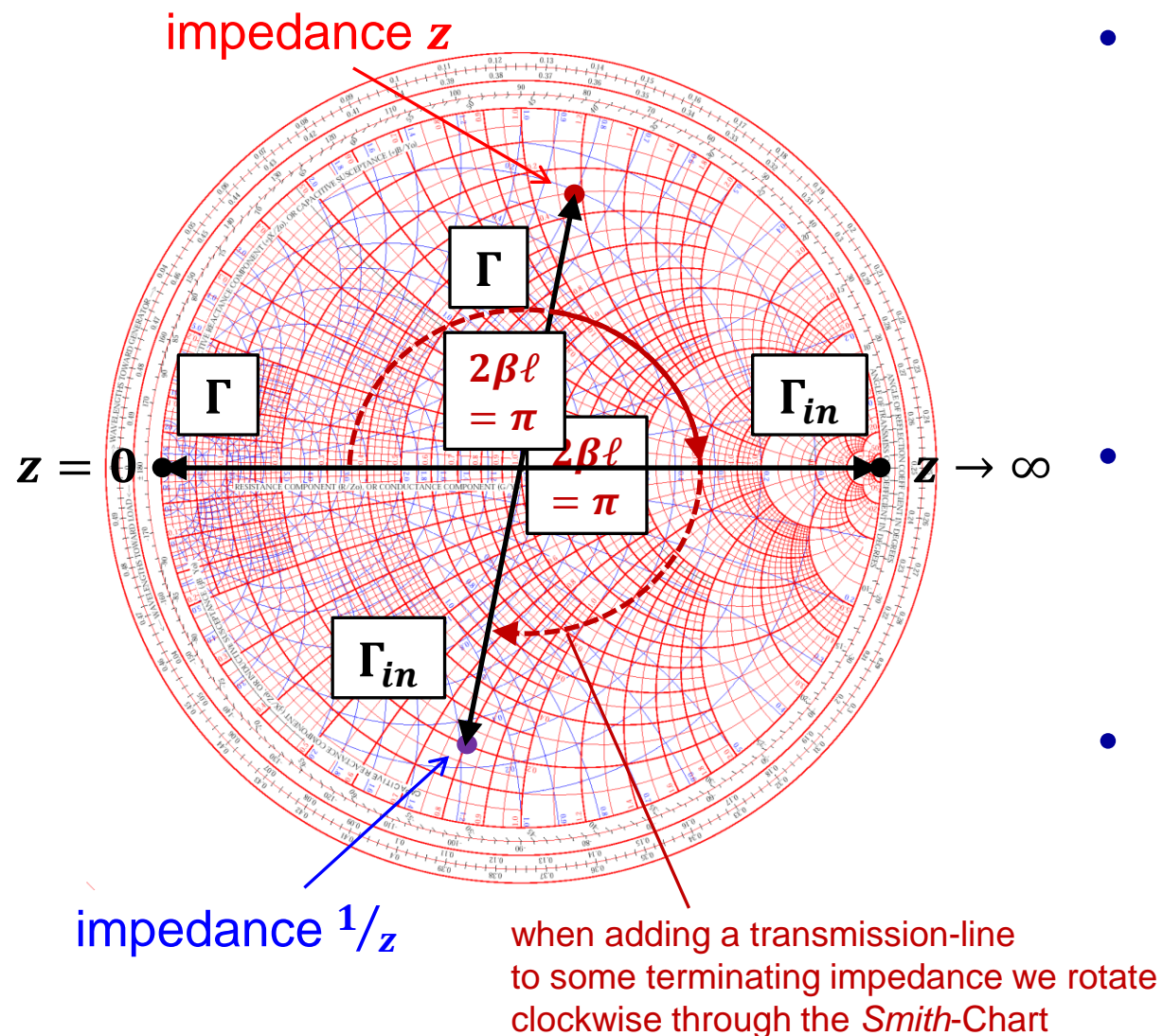

- A transmission-line of length

$$\ell = \lambda/4 \equiv \beta\ell = \frac{\pi}{2}$$

transforms a reflection  $\Gamma$  at the end of the line to its input as

$$\Gamma_{in} = \Gamma e^{-j2\beta\ell} = \Gamma e^{-j\pi} = -\Gamma$$

- This results the unitless, normalized impedance  $z$  at the end of the line to be transformed into:

$$z_{in} = 1/z$$

at the beginning of the line

- A short circuit at the end of the  **$\lambda/4$ -transformer** is transformed to an open, and vice versa
  - This is the principle of the  $\lambda/4$ -resonator.



- A network analyzer measurement of a RF amplifier, operated at  $f = 500 \text{ MHz}$  shows a reflection coefficient of  $\Gamma = 0.242e^{-j76^\circ}$ 
  - Locate  $\Gamma$  in the paper Smith chart
  - What is the un-normalized impedance  $Z$  ?
  - What is the lumped-element series equivalent circuit and what are the element values the make up  $Z$  ?
  - What circuit element , and its value, is required to match the impedance to  $Z_0 = 50 \Omega$  ?
    - Please use the paper Smith chart and find the value of the normalized matching impedance
    - Then de-normalize the value and calculate the value of the lumped element.



$$\Gamma = 0.242e^{-j76^\circ}$$

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES


- Locate  $\angle \cong -76^\circ$  on the circle  
ANGLE OF REFLECTION COEFFICIENT IN DEGREES
  - Mark with a **line**
- Locate  $|\Gamma| \cong 0.242$  on the ruler  
RFL. COEFF, E or I
  - Mark the point crossing the  $\angle$ -line

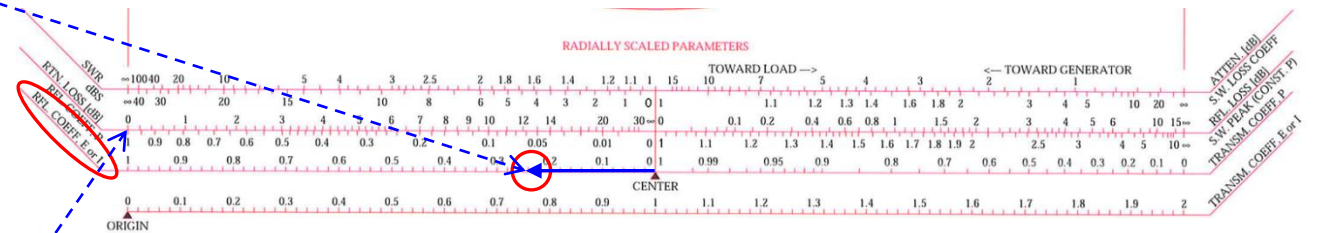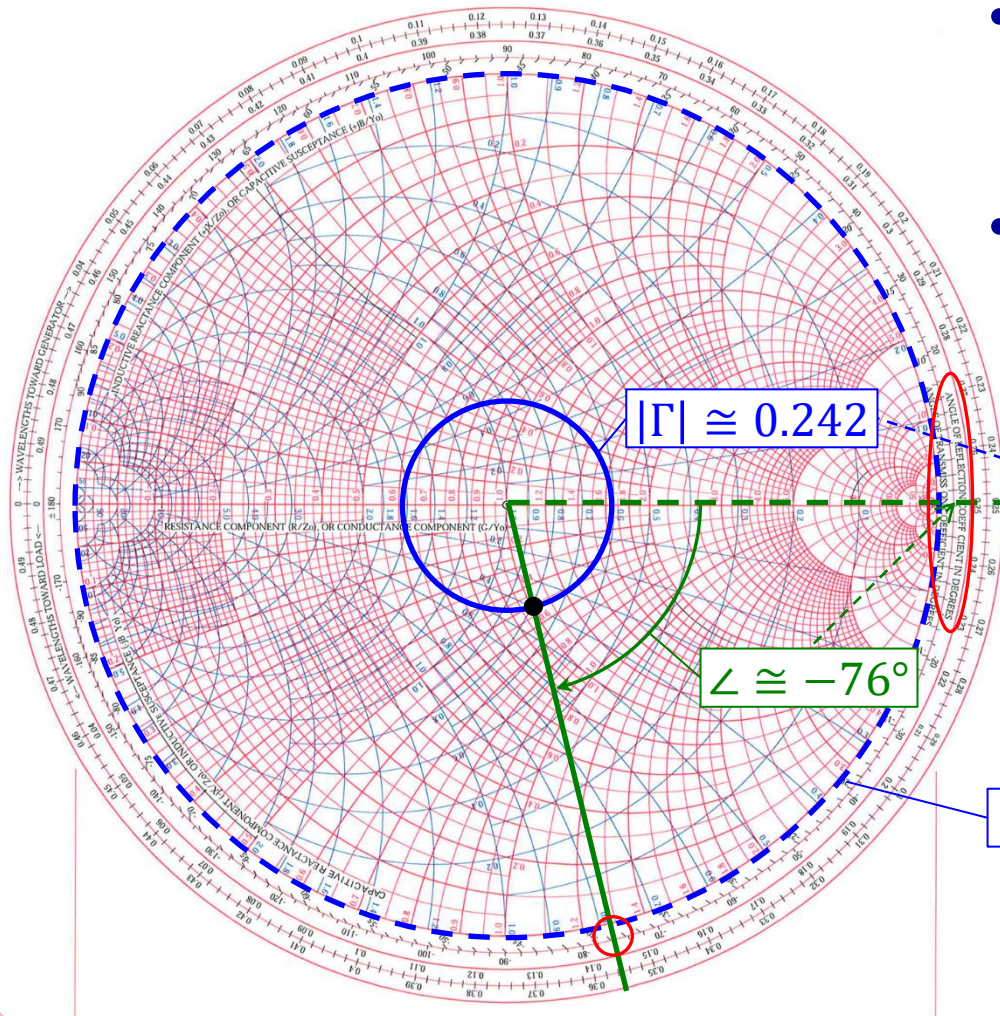



$$z = 1 - j0.5$$

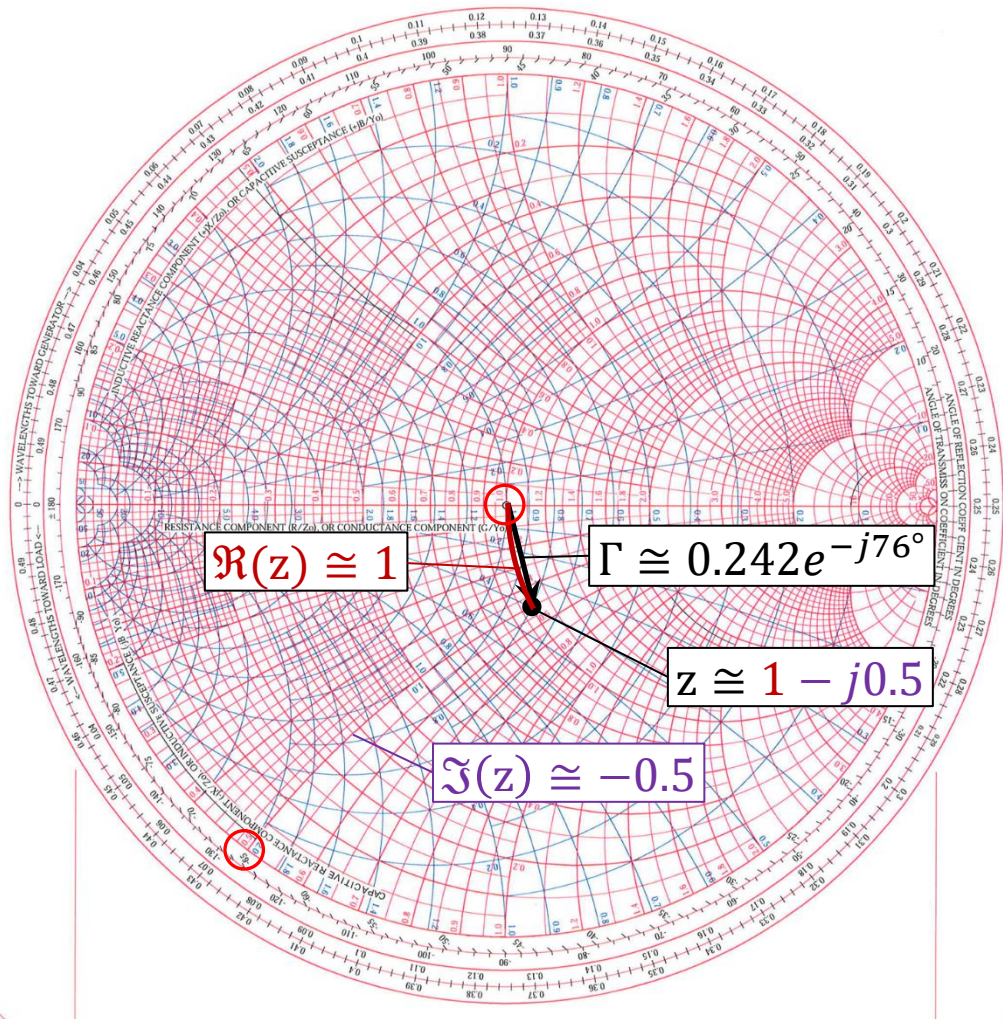NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



- Follow the real part circle to  $\mathcal{R} \cong 1$  on the real axis  
RESISTANCE COMPONENT ( $R/Z_0$ )
  - $\mathcal{R}(z) \cong 1$
- Follow the imaginary part to  $\mathcal{S} \cong -0.5$  to the positive imaginary axis  
CAPACITIVE REACTANCE COMPONENT ( $-jX/Z_0$ )
  - $\mathcal{S}(z) = -0.5$
- De-normalize the impedance for  $Z_0 = 50 \Omega$ 

$$Z = z Z_0 = (1 - j0.5)50 \Omega = (50 - j25)\Omega$$
  - $\mathcal{S}(Z) < 0 \Rightarrow$  capacitive

- As the imaginary part of the impedance is negative, the lumped-element equivalent series-impedance circuit is a RC series circuit

- We are in the lower, capacitive half plane of the Smith chart

$$Z = R + jX = R + \frac{1}{j\omega C} = (50 - j25)\Omega$$


$$\Rightarrow R = 50 \Omega,$$

$$\frac{1}{2\pi f C} = 25 \Omega \Rightarrow C = \frac{1}{2\pi \cdot 500 \cdot 10^6 \text{ s}^{-1} \cdot 25 \text{ V/A}} \cong 12.7 \text{ pF}$$

- We need to compensate the capacitive element by an inductive series element to get  $Z(f = 500 \text{ MHz}) = Z_0 = 50 \Omega$

- This is called a “dual” network:  $\omega L = \frac{1}{\omega C} \Rightarrow L = \frac{1}{\omega^2 C}$

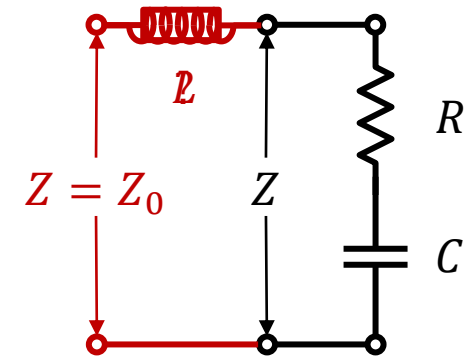- This is equivalent with the Smith chart operation:  $X_L = 2\pi f L = 25 \Omega$   
 $\Rightarrow L = \frac{25 \text{ V/A}}{2\pi \cdot 500 \cdot 10^6 \text{ s}^{-1}} = 7.96 \text{ nH}$




- The *Smith* chart is a special type of a parametric plot for the complex impedance or admittance, mapped to the complex reflection coefficient.
- The use of the *Smith* chart can be viewed in two ways:
  - As a calculation and impedance matching tool as originally envisioned.
    - However, today this will happen rather rarely!
    - Please notice: All the examples presented are based on the paper-style *Smith* chart, which is always based on an unitless, normalized impedance  $z = Z/Z_0$
  - As a visualization tool for the complex impedance, along with the reflection coefficient
    - Still very popular and useful for displaying and analyzing  $S_{ii}$  on a vector network analyzer, also used in data-sheets, and RF simulation and education software.
    - Here the *Smith* chart utilizes the actual complex impedance  $Z$  in units of  $\Omega$ ! Markers on the parametric trace give all relevant information, including the element values of a selected equivalent circuit.
- Old, but excellent information on transmission-lines and standing waves:
  - <https://www.youtube.com/watch?v=l9m2w4DgeVk>
  - <https://www.youtube.com/watch?v=DovunOxIY1k&t=38s>
- *Smith* chart education software (only for MS-Windows):
  - <https://www.fritz.dellsperger.net/smith.html>

# Backup Slides


This is a “bilinear” transformation with the following properties:

- **Generalized circles are transformed into generalized circles**
  - **circle** → **circle**
  - **straight line** → **circle**
  - **circle** → **straight line**
  - **straight line** → **straight line**
- **Angles are preserved locally**

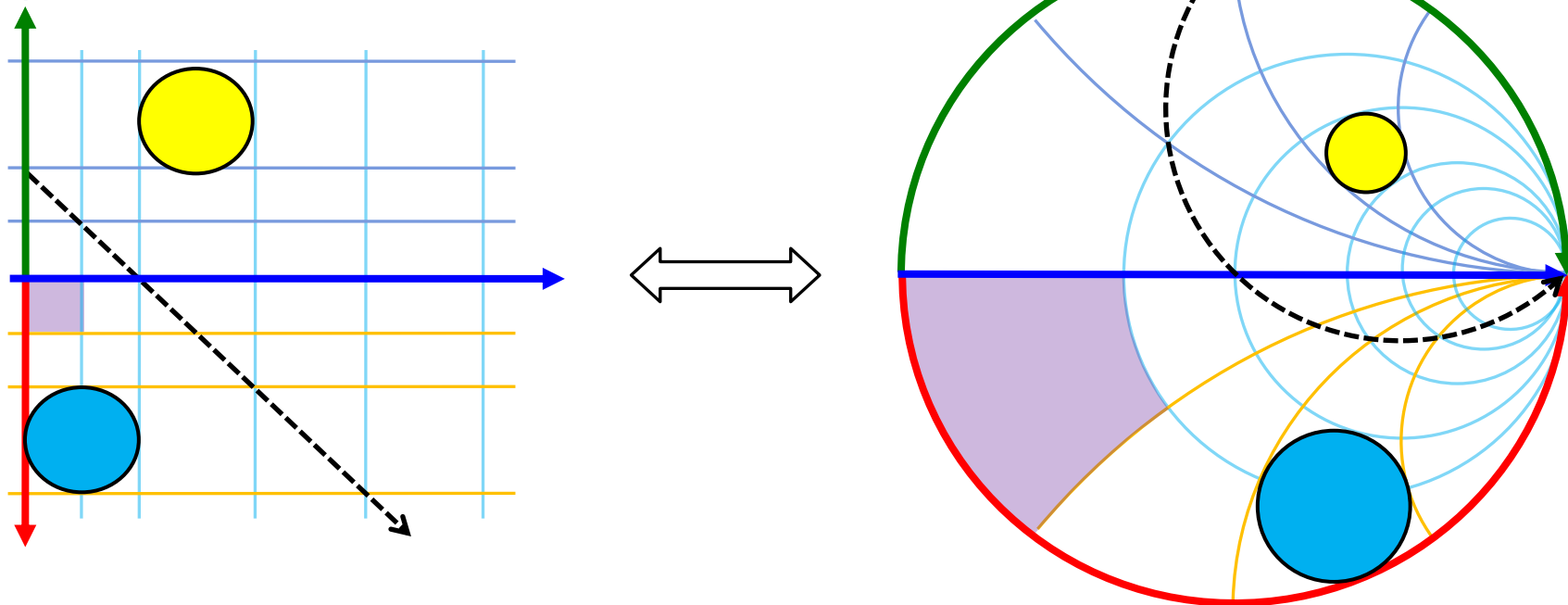- a straight line is equivalent to a circle with infinite radius
- a circle is defined by 3 points
- a straight line is defined by 2 points



# Navigation in the *Smith Chart* (2)

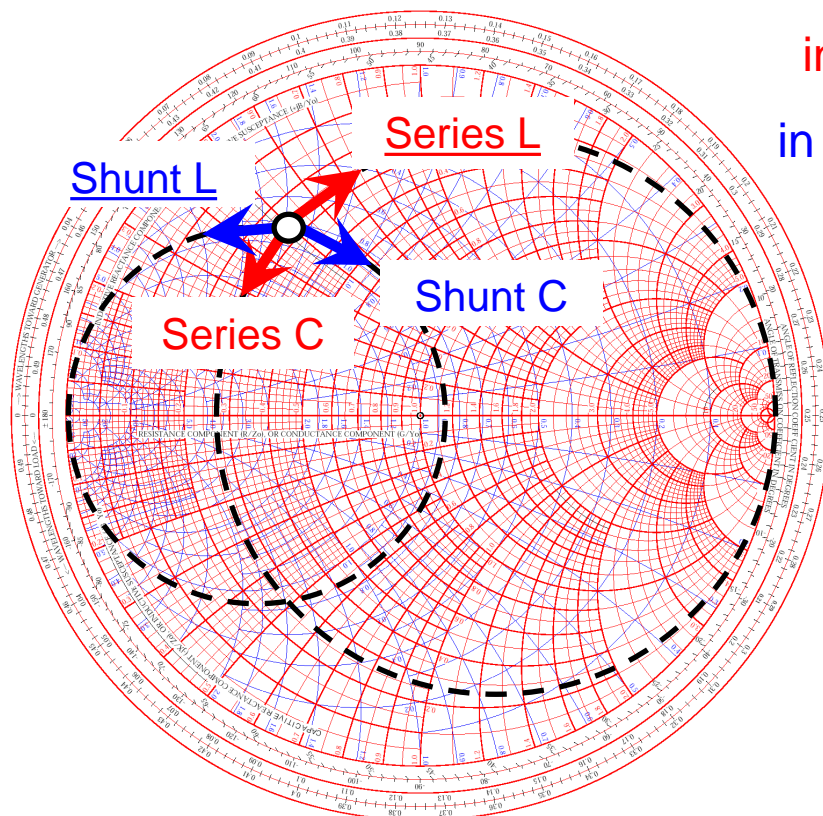


in red: impedance plane ( $= z$ )

in blue: admittance plane ( $= y$ )

	<u>Up</u>	Down
Red circles	<u>Series L</u>	Series C
Blue circles	<u>Shunt L</u>	Shunt C



# Navigation in the *Smith Chart* (3)

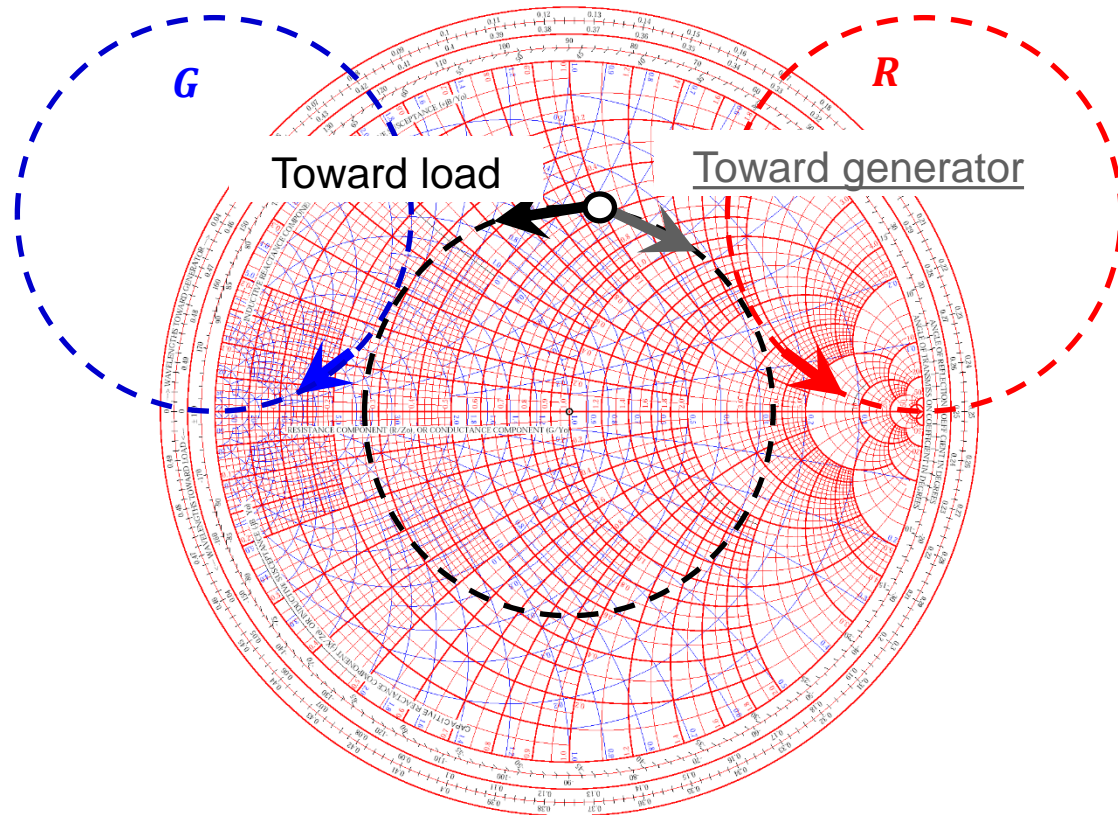

<b>Red arcs</b>	<b>Resistance <math>R</math></b>
<b>Blue arcs</b>	<b>Conductance <math>G</math></b>
<b>Con-centric circle</b>	<b>Transmission line going Toward load <u>Toward generator</u></b>