

# **RF Engineering**

## **A very brief Introduction into *QucsStudio***

***Christine Völlinger & Manfred Wendt – CERN***

- **Three ways to analyze a RF subsystem or component**
  1. Applying Maxwell's equations, analytical (if possible), but usually numerically
  2. Approximation by an equivalent circuit, to be analyzed analytically or numerically
  3. Building the RF subsystem or component, and characterize it by measurements
- **In an ideal world all three methods will agree**
- **Even simple equivalent circuit problems quickly become too complicated to be solved analytically**
  - Industry offers a large variety of numerical circuit and system simulation tools, e.g., Advance Design System (ADS), Microwave Office, many SPICE variants, etc.
    - Some include EM *Maxwell* solvers, linear, transient and harmonic balance solvers, and digital signal processing and system design including FPGAs
  - Freeware tools, e.g., Qucs, Qucs-S, **QucsStudio**, LTSpice, Ngspice, SPICE, etc., have many limitations, but are educationally valuable!

# Example: Pillbox TM010 Mode

- A cylindrical resonator was analyzed numerically and by measurement characterization:

Method	Q <sub>0</sub> value	R/Q	R <sub>shunt</sub> (MΩ)
Frequency shift	6180.3	15.54	9.6
Phase shift		16.55	10.2
CST	6408.4	13.21	10.1
From CST electric field		14.61	9.5


- We can extract the values of an equivalent *RLC* parallel circuit for critical coupling ( $R_g = 50 \Omega$ ):

$$R = \frac{R}{Q} \cdot Q$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{R}{\omega_0 L} = R \cdot \omega_0 C$$


$$n = \sqrt{R/R_g}$$

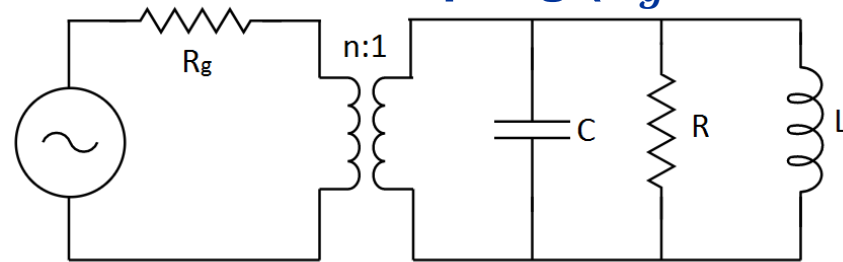

Element	Value
R	84.655 kΩ
L	2.6883 nH
C	15.405 pF
n	41.14

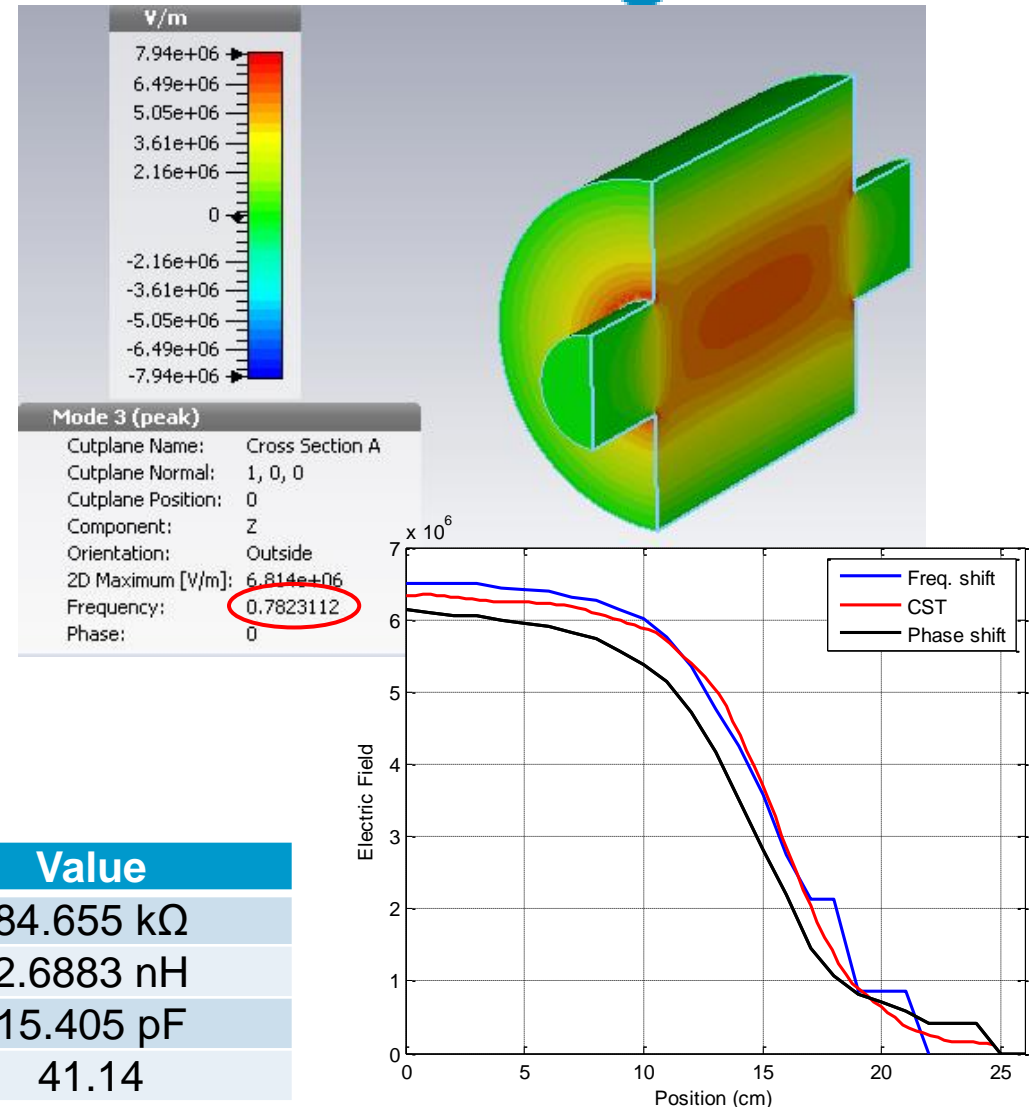


# Q-factor from $S_{11}$ Measurement

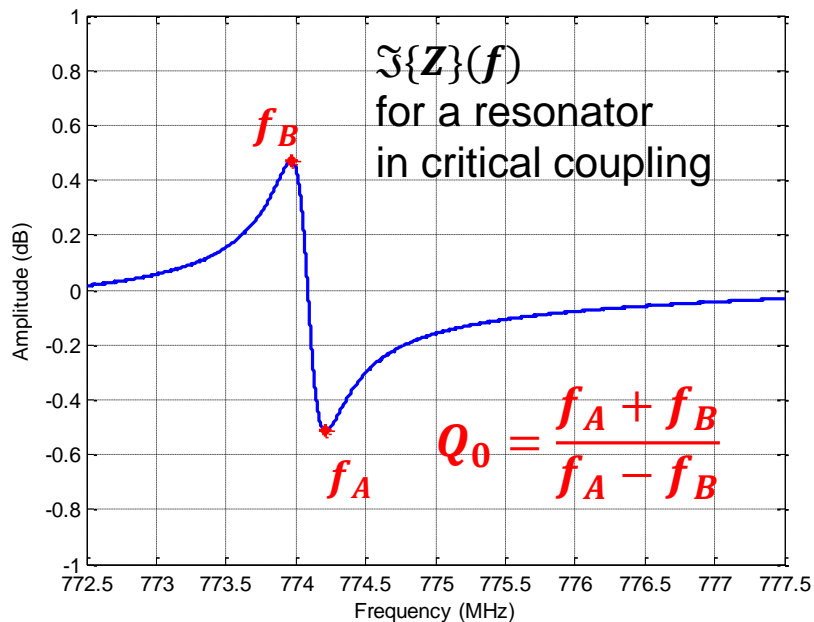

--- arbitrary coupling (here: over-critical)

— critical coupling

detuned  
short  
position  
( $Z = 0$ )

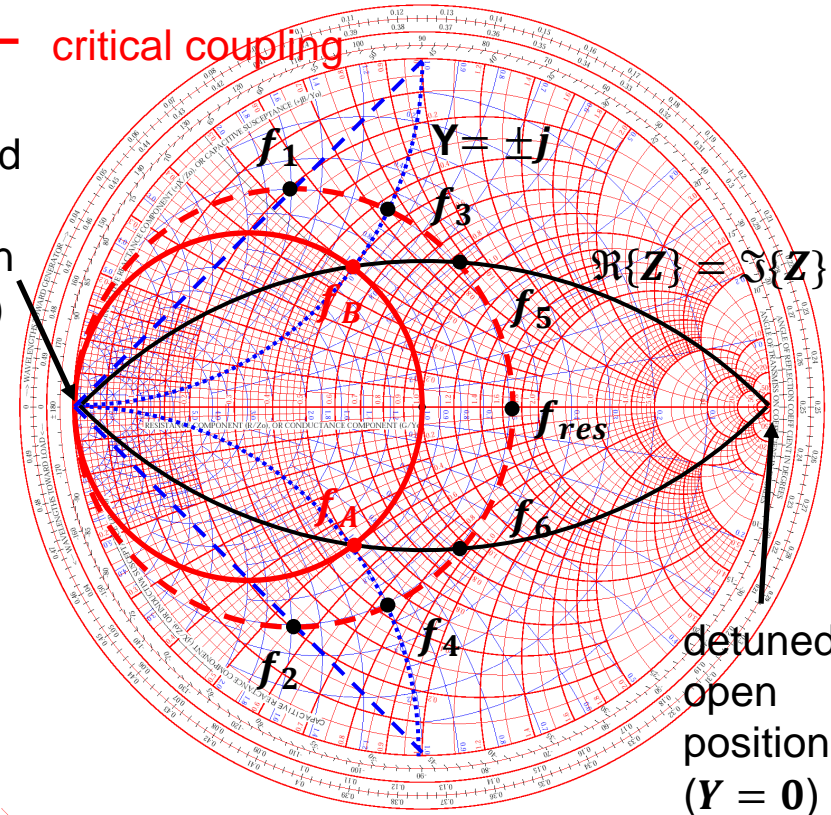

- **Correct for the uncompensated effects of the coupling loop**
  - Electrical length adjustment: "straight"  $\Im\{Z\}(f)$
- **Adjust the locus circle to the detuned short location**
  - Phase offset
- **Verify no evanescent fields penetrating outside the beam ports**
  - i.e., no frequency shifts if the boundaries at the beam ports are altered


Frequency marker points in the Smith chart:

$f_{1,2}$ :  $\Im\{S_{11}\} = \max.$  to calculate  $Q_L$

$f_{3,4}$ :  $Y = \Re \pm j$  to calculate  $Q_{ext}$


$f_{5,6}$ :  $\Re\{Z\} = \Im\{Z\}$  to calculate  $Q_0$

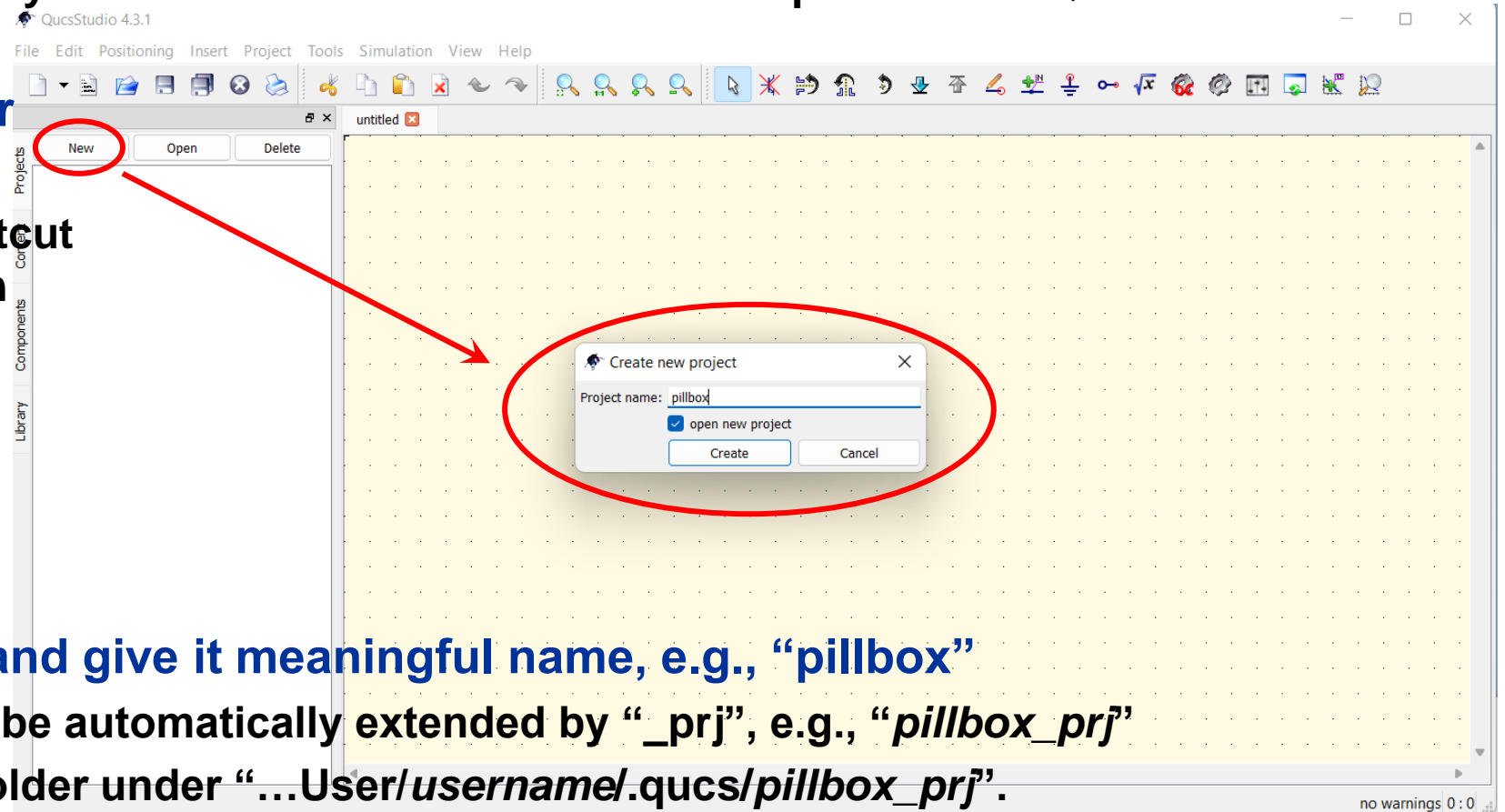- Is a better maintained derivate of Qucs
  - Runs unfortunately only under Windows and files are incompatible with Qucs
- Locate “start.bat” in the installation folder to start the program
  - Eventually link a shortcut on the desktop screen for convenience




- Open a “New project” and give it meaningful name, e.g., “pillbox”
  - The project name will be automatically extended by “\_prj”, e.g., “pillbox\_prj”
  - You find the project folder under “...User/username/.qucs/pillbox\_prj”.

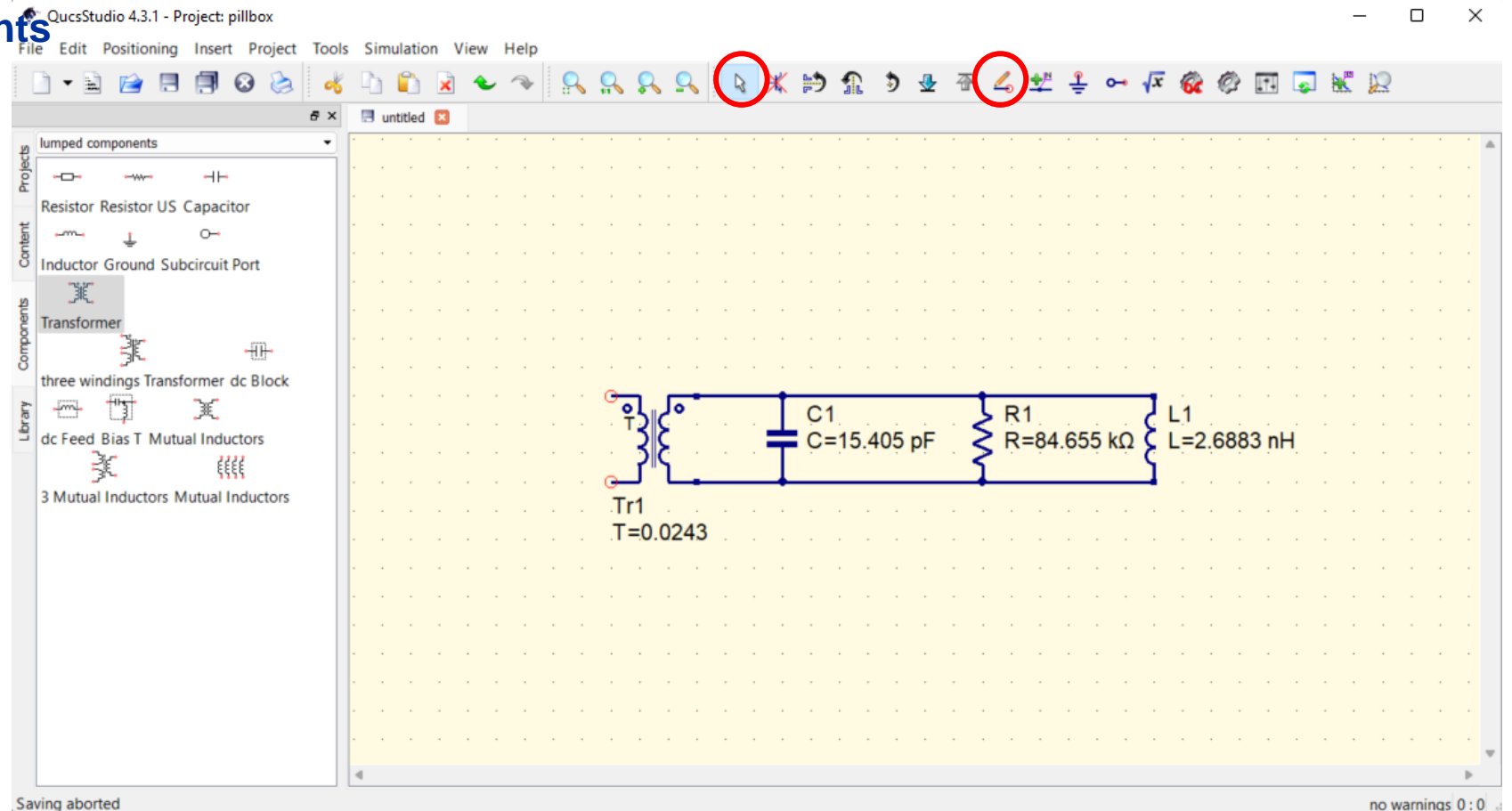- Locate the “Component” tap and select “lumped components” from the drop-down bar (default)
- Select your components on the schematics screen and edit the values
  - Use “esc” to unselect an action
- Wire up the components




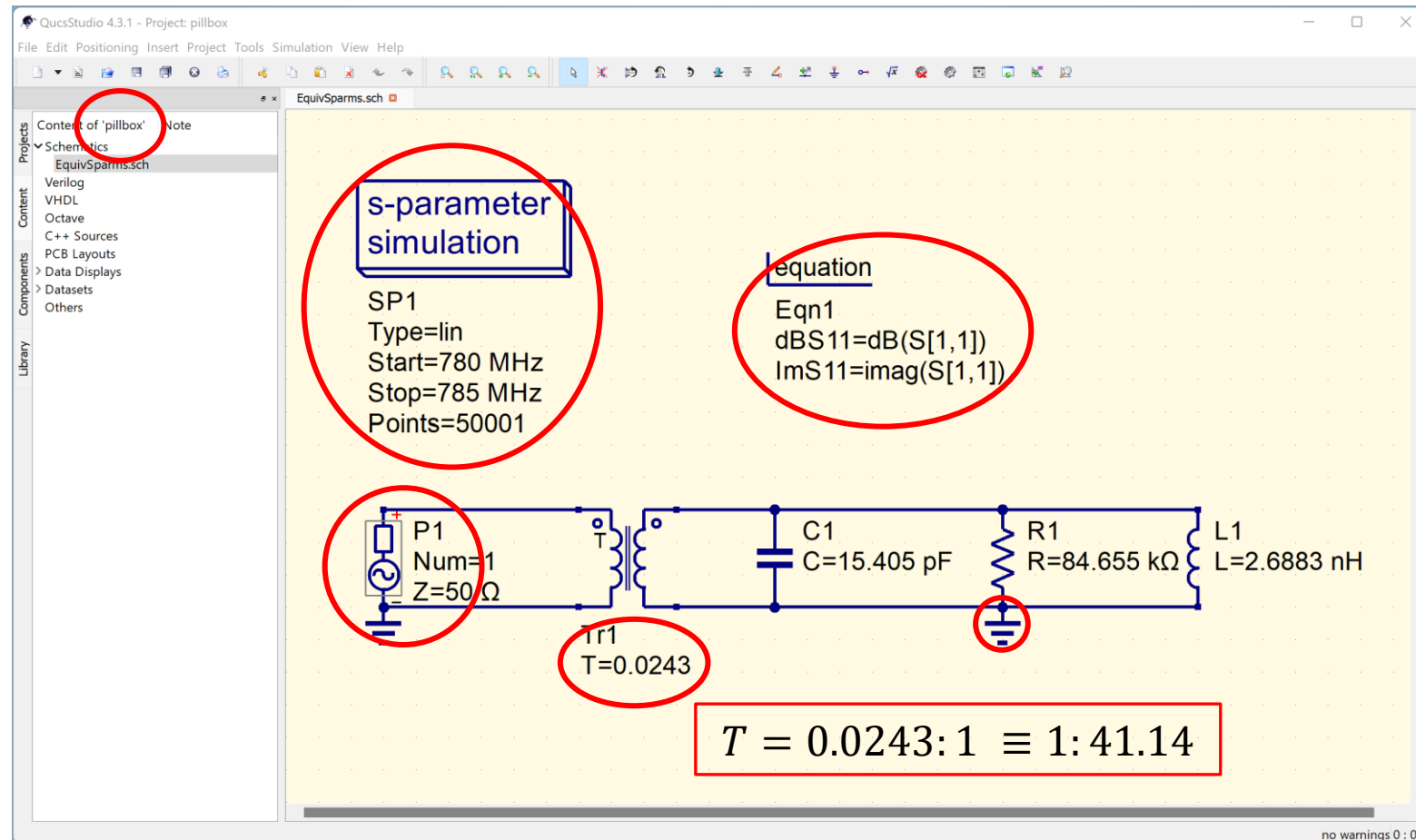- Finalize the schematics input by adding
  - “power source” and “s-parameter simulation”, grounding, “equation” for dBS11 and ImS11



- Save your schematic under a meaningful name

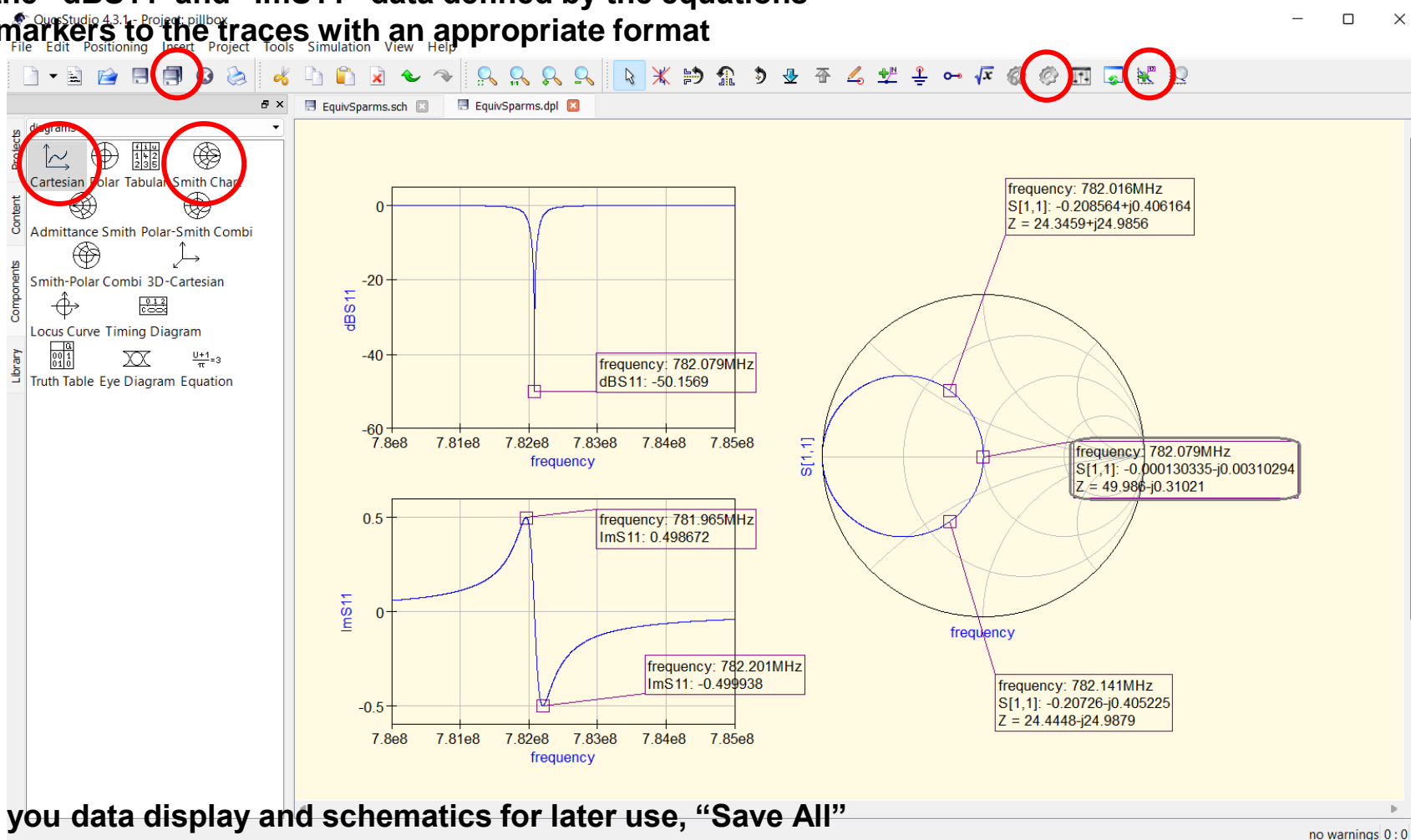- Execute the “simulation” and display the results using “Cartesian” and “Smith Charts” plots
  - Use the “dBS11” and “ImS11” data defined by the equations
  - Add markers to the traces with an appropriate format



- Save you data display and schematics for later use, “Save All”