

Design of an area-effective small digital cell library for pixel readout chip

WP3 sessions at the AIDA annual meeting , March 29th, DESY 2012

R.Szczygiel, P. Grybos, P.Otfinowski

Outline

- 1) Library design targets**
- 2) Library description**
- 3) Current status**

Library design targets

The library is optimized for area, for small logic block building

- 1) there are no well and substrate taps in the cells, separate „TAP” cell is used
- 2) PMOS/NMOS are not balanced
- 3) Cells not optimized for routing density - there is some routing in the MET2 layer in d-flop and latch cells
- 4) D-flops and latches have no buffered outputs, separate buffers available
- 5) set and reset signals of the D-flops are not connected internally (have to be connected externally)

Routing information – CMOS GF130nm

Metal	routing direction	pitch[μm]	offset [μm]
MET1	vertical	0.51	0.255
MET2	horizontal	0.48	0.0
MET3	vertical	0.51	0.255
MET4	horizontal	0.48	0.0

Row height: 2.4 μm

Placement x-pitch: 0.51 μm

Power net name: VDD


Ground net name: VSS

Substrate net name: VSSS, VDDD


Cell list

	<i>Cell name</i>	<i>description</i>	<i>status</i>	<i>layout size [$\mu\text{m} \times \mu\text{m}$]</i>
1.	AND21X1	2-input AND	DRC, LVS, QRC	2.04 x 2.4 = 4.896
2.	AOI21X1	AND-OR-INVERT with 2 input AND	DRC, LVS, QRC	2.04 x 2.4 = 4.896
3.	BUF1X1	Buffer	DRC, LVS, QRC	1.53 x 2.4 = 3.672
4.	DFFSBRBX1	D-flop with async set active low and reset active low; set has higher priority	DRC, LVS, QRC	10.2 x 2.4 = 24.48
5.	DFFSBX1	D-flop with async set active low	DRC, LVS, QRC	8.16 x 2.4 = 19.584
6.	DFFSX1	D-flop with async set active high	DRC, LVS, QRC	8.16 x 2.4 = 19.584
7.	DFFRX1	D-flop with async reset active high	DRC, LVS, QRC	8.16 x 2.4 = 19.584
8.	DFFRBX1	D-flop with async reset active low	DRC, LVS, QRC	8.16 x 2.4 = 19.584
9.	DFFX1	D-flop	DRC, LVS, QRC	6.63 x 2.4 = 15.912
10.	DLATCHX1	Transparent latch	DRC, LVS, QRC	3.57 x 2.4 = 8.568
11.	IMUX21X1	Inverting 2-input multiplexer	DRC, LVS, QRC	3.06 x 2.4 = 7.344
12.	INV1X1	Inverter	DRC, LVS, QRC	1.02 x 2.4 = 2.448
13.	INV1X2	Inverter 2x drive	DRC, LVS, QRC	1.53 x 2.4 = 3.672
14.	INV1X4	Inverter 4x drive	DRC, LVS, QRC	2.55 x 2.4 = 6.12
15.	MUX21X1	2-input multiplexer	DRC, LVS, QRC	3.57 x 2.4 = 8.568
16.	NAND21X1	2-input NAND	DRC, LVS, QRC	1.53 x 2.4 = 3.672
17.	NOR21X1	2-input NOR	DRC, LVS, QRC	1.53 x 2.4 = 3.672
18.	OAI21X1	OR-AND-INVERT with 2 input OR	DRC, LVS, QRC	2.04 x 2.4 = 4.896
19.	OR21X1	2-input OR	DRC, LVS, QRC	2.04 x 2.4 = 4.896
20.	TAP	Substrate and well contact	DRC	1.02 x 2.4 = 2.448


Cell - example

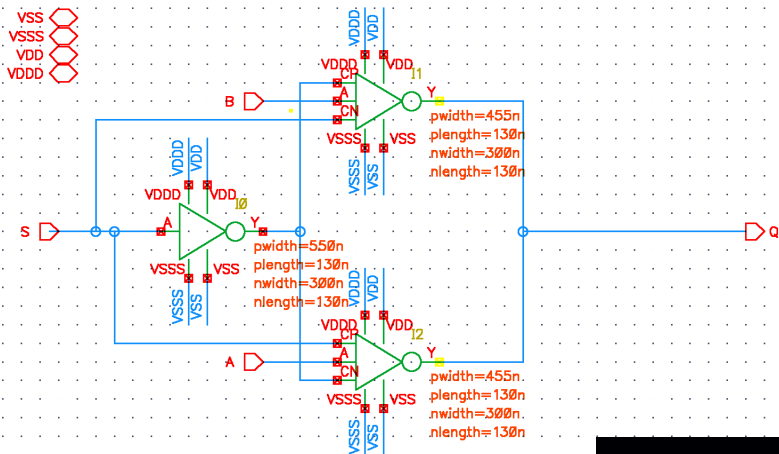


IMUX21X1
3,06 μm x 2,4 μm

 


Cell - example

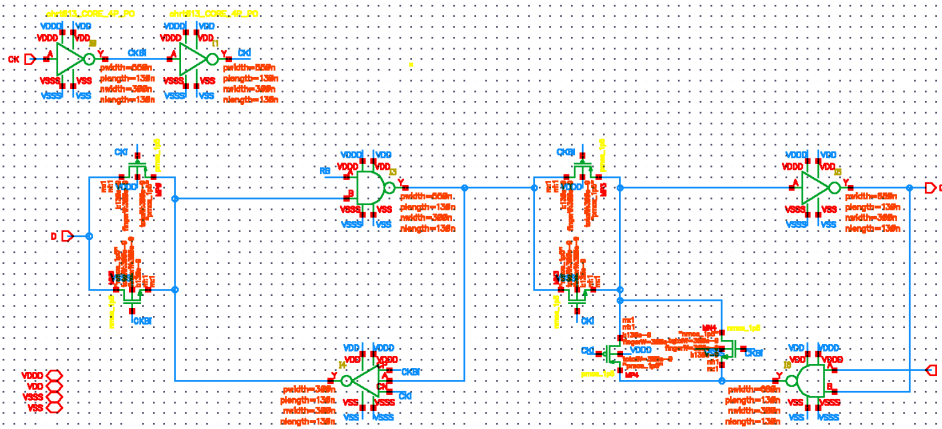


DFFRBX1
8,16 μm x 2,4 μm

 

Cell - example

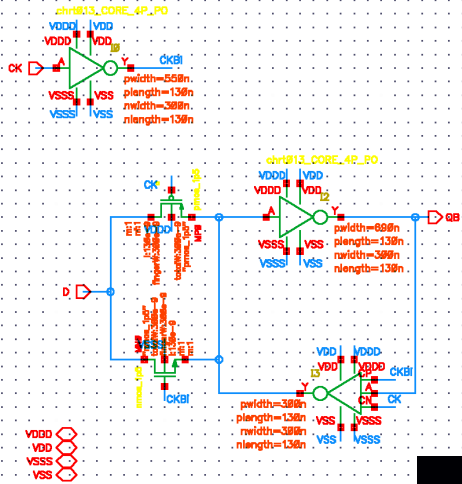

DLATCHX1
 3,57 μm x 2,4 μm

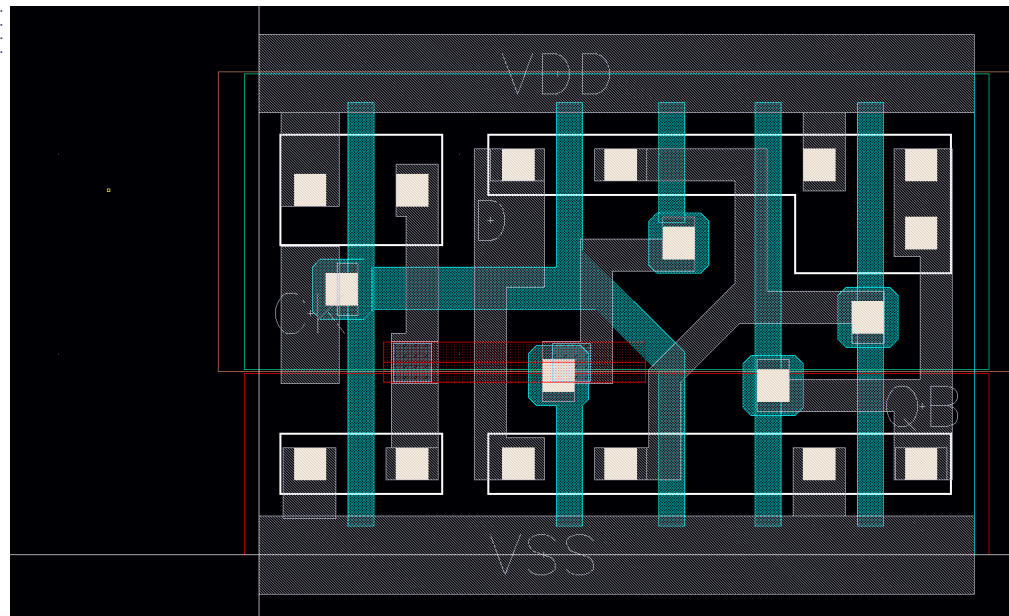

Layers

AV NV AS NS

MET3 drawing

All Valid Layers

Used Layers Only


Search

Layer	Purpose	V	S
MET3 drawing		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
MET3 dummy		<input type="checkbox"/>	<input type="checkbox"/>
MET3 label		<input type="checkbox"/>	<input type="checkbox"/>
VIA3 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET4 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET4 dummy		<input type="checkbox"/>	<input type="checkbox"/>
MET4 label		<input type="checkbox"/>	<input type="checkbox"/>
VIA4 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET5 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET5 dummy		<input type="checkbox"/>	<input type="checkbox"/>
MET5 label		<input type="checkbox"/>	<input type="checkbox"/>
VIA5 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET6 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET6 dummy		<input type="checkbox"/>	<input type="checkbox"/>
MET6 label		<input type="checkbox"/>	<input type="checkbox"/>
VIA6 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET7 drawing		<input type="checkbox"/>	<input type="checkbox"/>
MET7 dummy		<input type="checkbox"/>	<input type="checkbox"/>
MET7 label		<input type="checkbox"/>	<input type="checkbox"/>
VIA... drawing		<input type="checkbox"/>	<input type="checkbox"/>
ME... drawing		<input type="checkbox"/>	<input type="checkbox"/>
ME... dummy		<input type="checkbox"/>	<input type="checkbox"/>
ME... label		<input type="checkbox"/>	<input type="checkbox"/>
PAD drawing		<input type="checkbox"/>	<input type="checkbox"/>
NAT drawing		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
SAB drawing		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
DG drawing		<input type="checkbox"/>	<input type="checkbox"/>
TEXT drawing		<input type="checkbox"/>	<input type="checkbox"/>
FUS... drawing		<input type="checkbox"/>	<input type="checkbox"/>
ES... marking		<input type="checkbox"/>	<input type="checkbox"/>
LVT drawing		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>

Objects

Object	V	S
Shapes	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Circle/Elli...	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Donut	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Label	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Path	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
PathSeg	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Polygon	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Rectangle	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Other Sh...	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Instances	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Fluid Guardi...	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Mosaic	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
Pinc	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>

Objects Guides

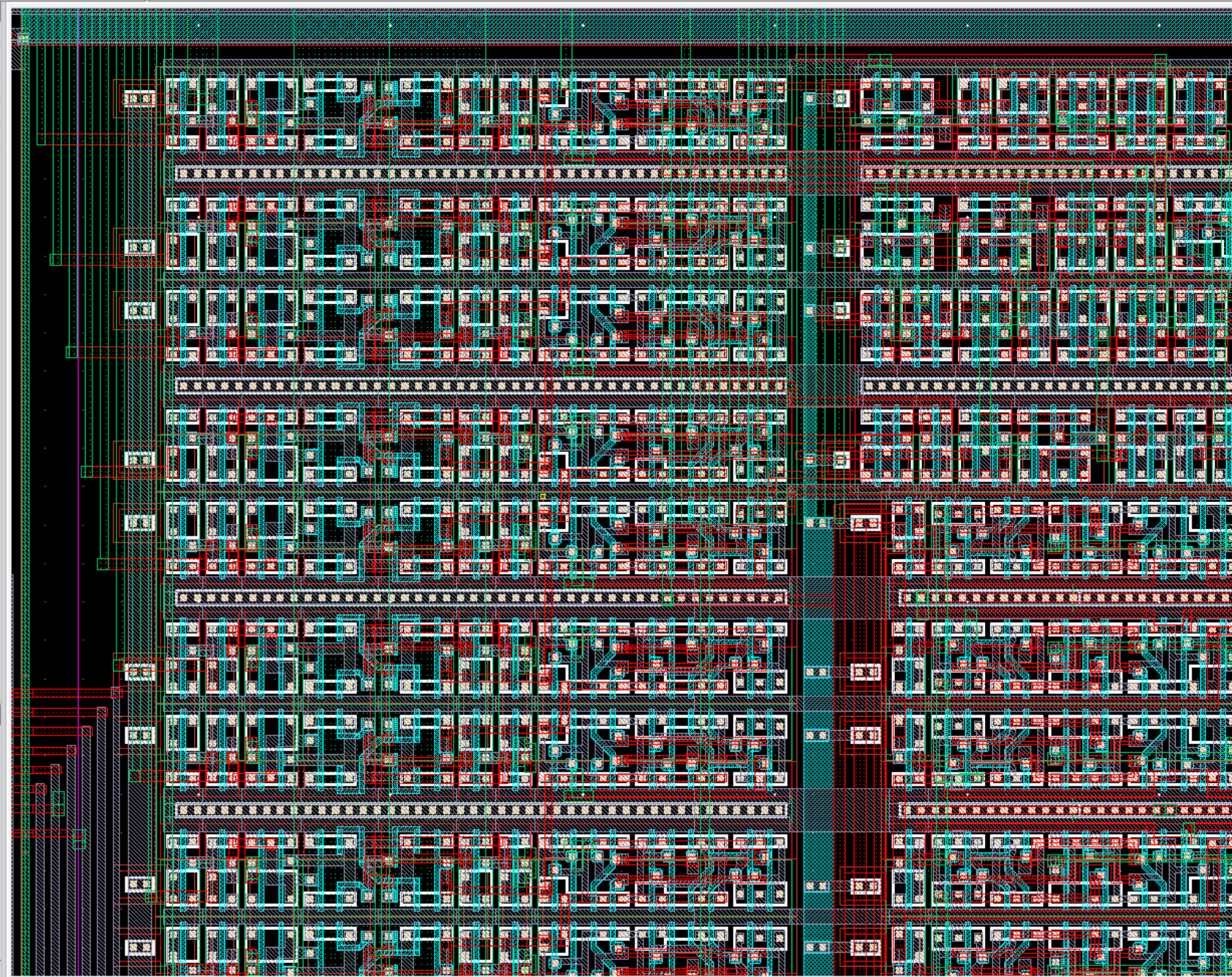

Current status

	Task	Status
1	Layout pre-study (define row height, metal pitch/offset, etc.)	Done
2	dfII technology file modifications	90%
3	Abstract generator configuration	90%
4	Cell schematics	100%
5	Cell layouts	100%
6	Verilog models	90%
7	Verilog models verification (vs analog simulations)	5%
8	Timing characterization setup (ETS 10.11)	Generated for ss, tt, ff corners and VDD=1.2, VDD=1.5
9	Synthesis tests	50%
10	Technology LEF files	20%
11	Place & route tests	0%
12	Import to Virtuoso tests	0%
13	Post-route DRC/LVS	0%
14	Post-layout verilog simulations	0%
15	Mixed-mode simulations	50%