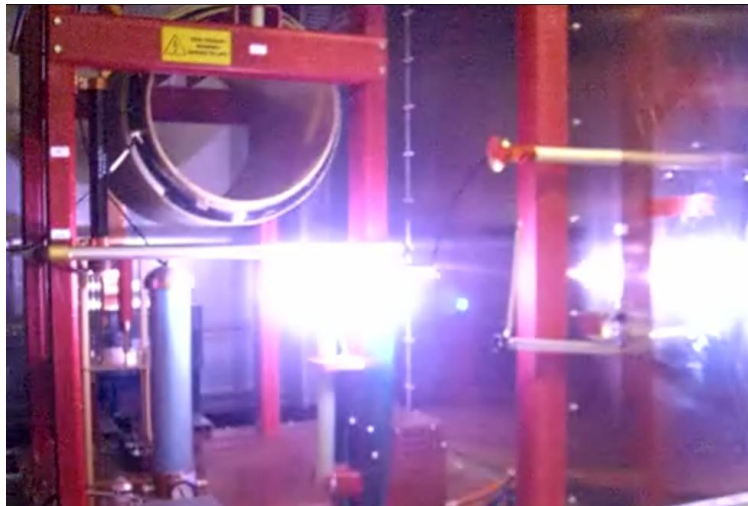


SHORT CIRCUIT ENERGY

CONSIDERATIONS USING THE EXAMPLE OF A PULSE STEP MODULATOR BASED HVPS



CWRF 8. – 11. May 2012

André Spichiger, Michael Bader, Marcel Frei

SHORT CIRCUIT ENERGY

► **Content**

- **Motivation: Why this topic?**
- **Tube Specifications**
- **How can the arc energy be measured or calculated**
- **HVPS Stored Energy**
- **Energy dissipation / arc energy**
- **Reduction of arc energy**
- **Inverse Voltage- System**
- **Summary**



► *Why this topic?*

- Questions during bids and acceptance tests
- Increasing filter / ripple requirements → what are the limitations?
- Frequently discussed issue: Cable length between the supply and the tube
- Important for a safe tube operation
- To give an idea / feeling about the figures


What is the energy dissipated in a load (tube) arc?

► ***Arc energy specifications***

- Usually in the region of 10..20 Joule
- 15 Joule corresponds to 15 bars of chocolate lifted 1m.



VERIFICATION

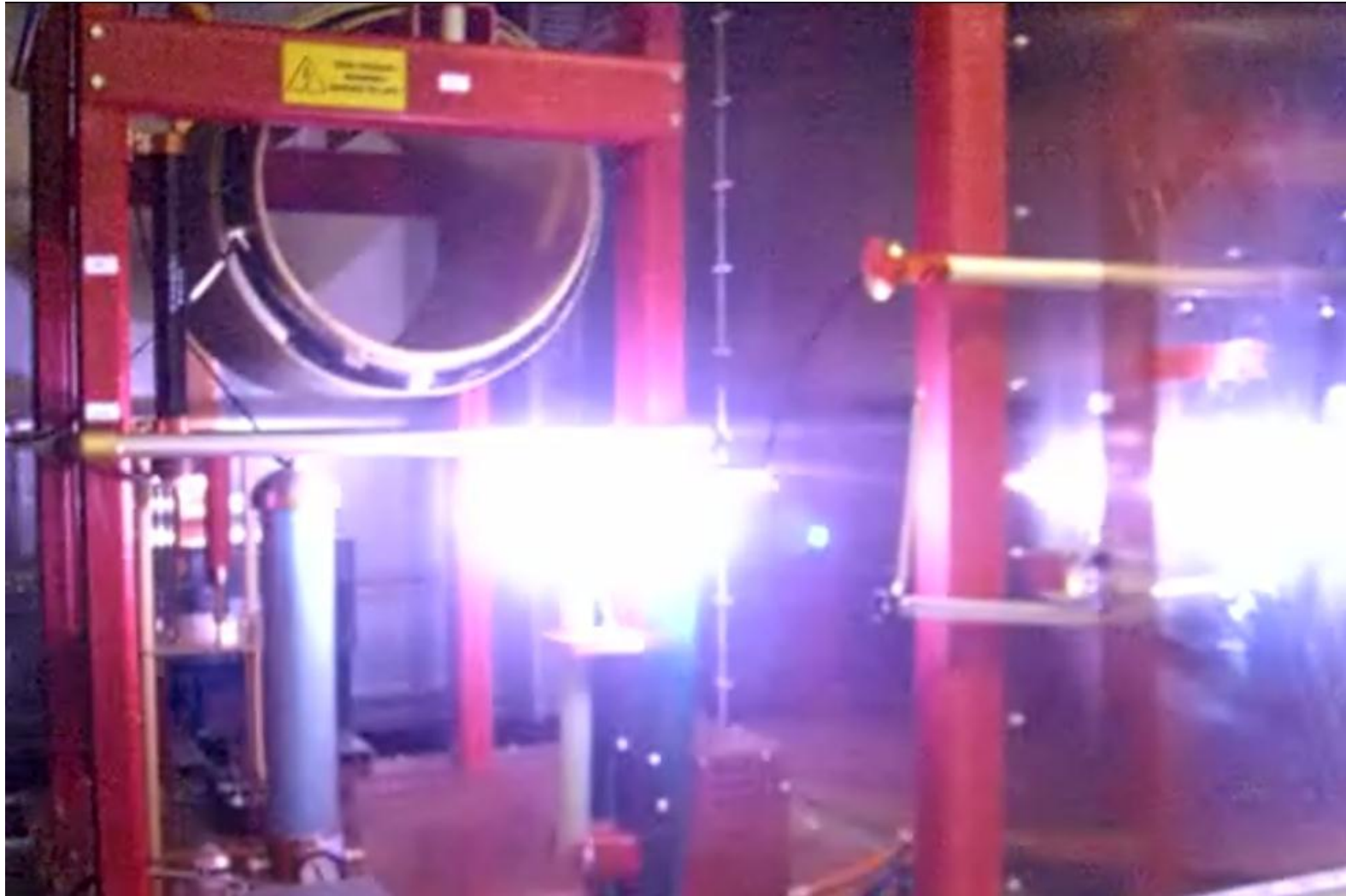


▶ **Measuring the arc energy**

- ▶ Simple test with a wire as proposed in tube Datasheets
- ▶ Using a real fuse I^2t value
- ▶ Accurate Current measurement is possible (e.g. pearson coil, coaxial shunt)
- ▶ Accurate Arc Voltage measurement is not easy to do
- ▶ We proposal: Measuring the current and post-calculating the energy dissipation with a defined arc Model

▶ **Calculating the arc energy**

- ▶ Arc Model Proposal for vacuum tubes: Series connection of DC Voltage source 100V and Resistor 200mOhm.
- ▶ Simulations provide good basis for later verification
- ▶ System optimization can be easily done in simulations

BASIC MODEL

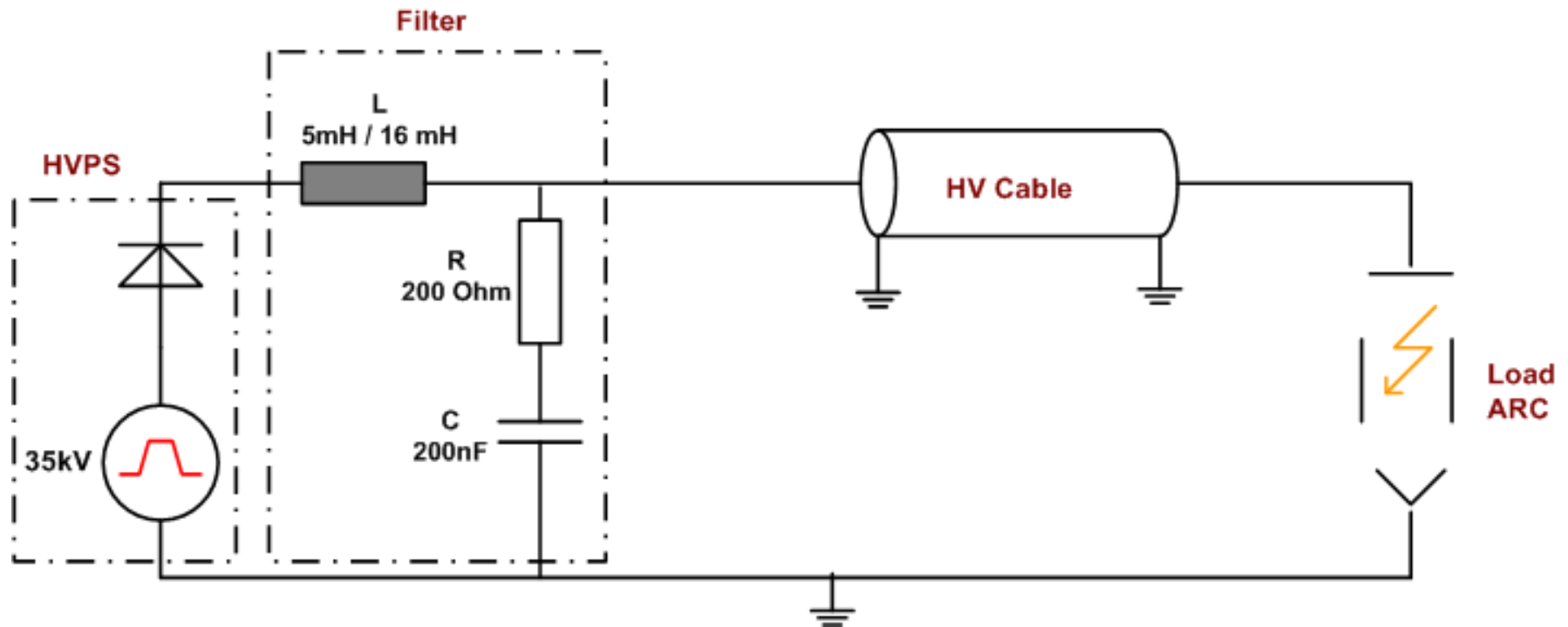

STORED ENERGY


- ▶ Basic model with a 2 – pole RLC filter network
- ▶ System parameter 35kV / 3.5A, a rather small system.
- ▶ ARC energy specifications **15 Joule**
- ▶ Stored energy is much higher

Parameter	Value	Stored Energy
Filter Inductor	16 mH 5 mH	0.1 Joule / 6 Joule 0.03 Joule / 15 Joule
Filter Capacitor	200nF	123 Joule
High Voltage Power Supply	60 modules 57 Joule / module	3420 Joule
Cable	100 pF / meter	0.06 Joule / meter


ENERGY DISSIPATION

► *Where is the energy dissipated in case of a short?*

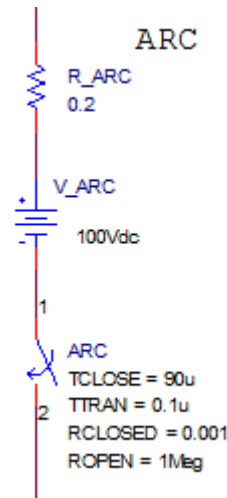
- What happens with the stored energy in the filter QL QC?
- Simulation model parameters:
 - Turn off delay 10 us
 - Voltage drop in the diodes: 2V / Diode
 - Short circuit model: 100V / 0.2 Ohm




SIMULATION MODEL

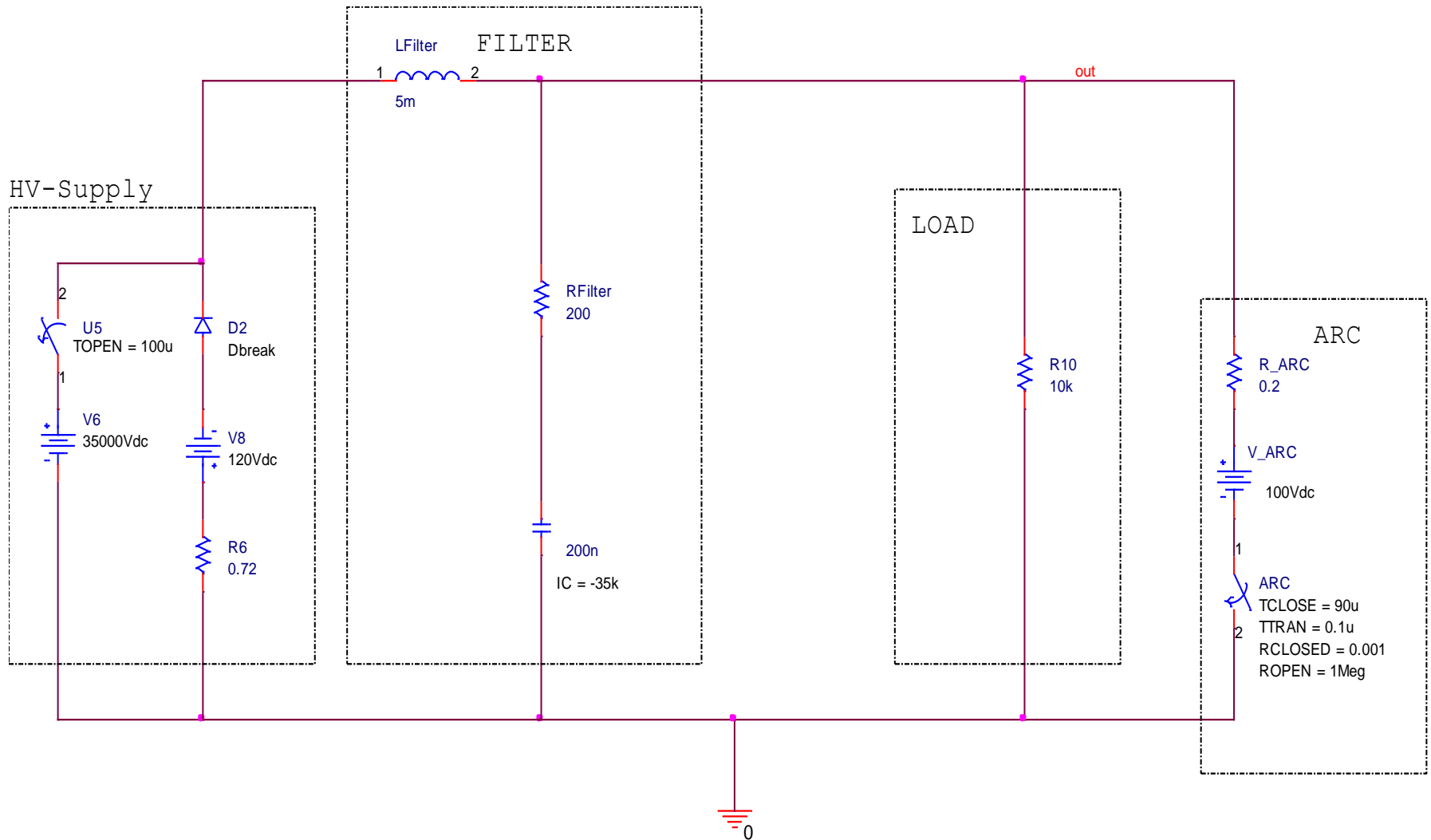


SIMULATION: 5 MH FILTER INDUCTANCE

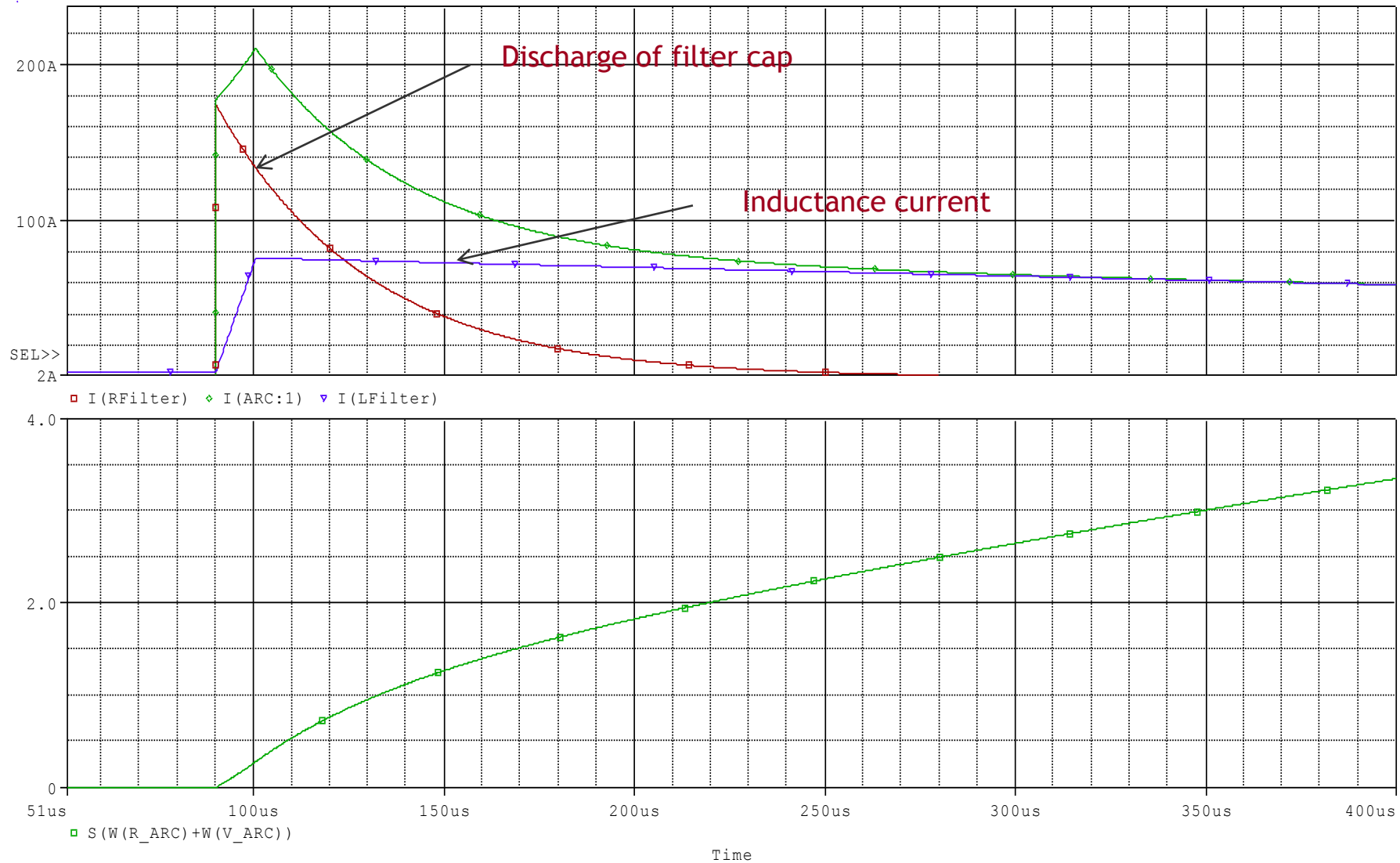


SIMULATION: 5 MH FILTER INDUCTANCE

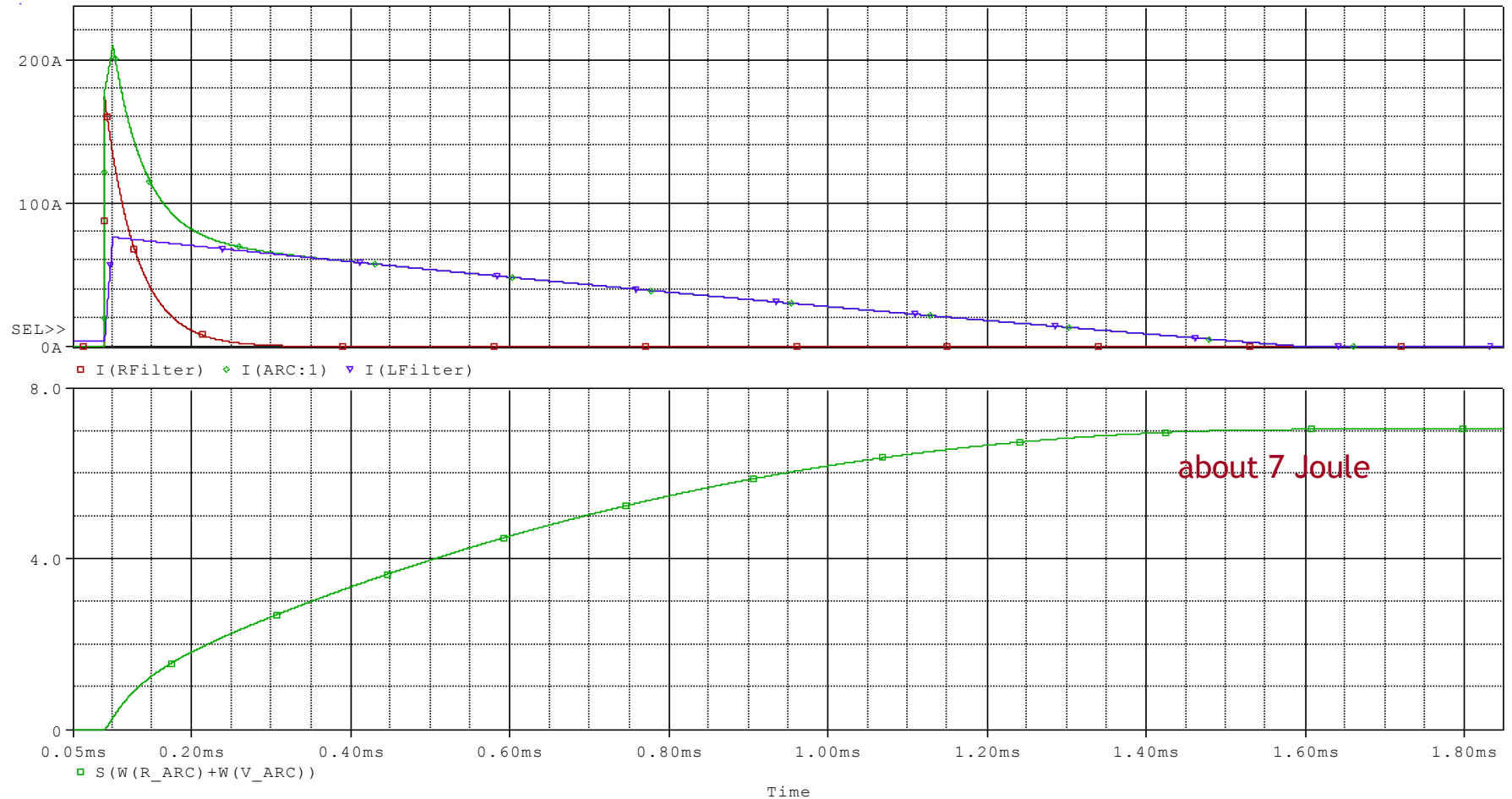

SIMULATION: 16 MH FILTER INDUCTANCE


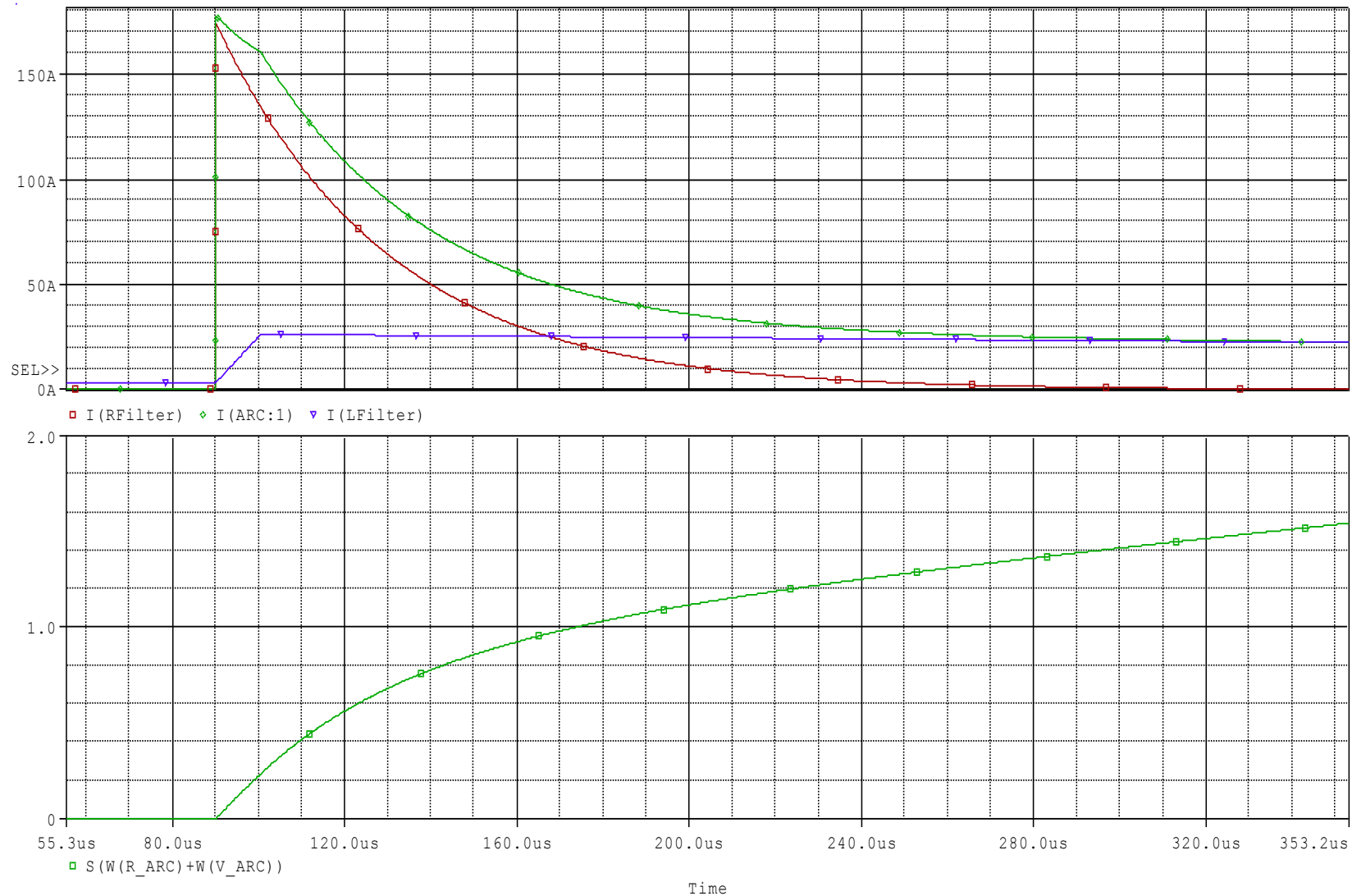


SIMULATION: 16 MH FILTER INDUCTANCE

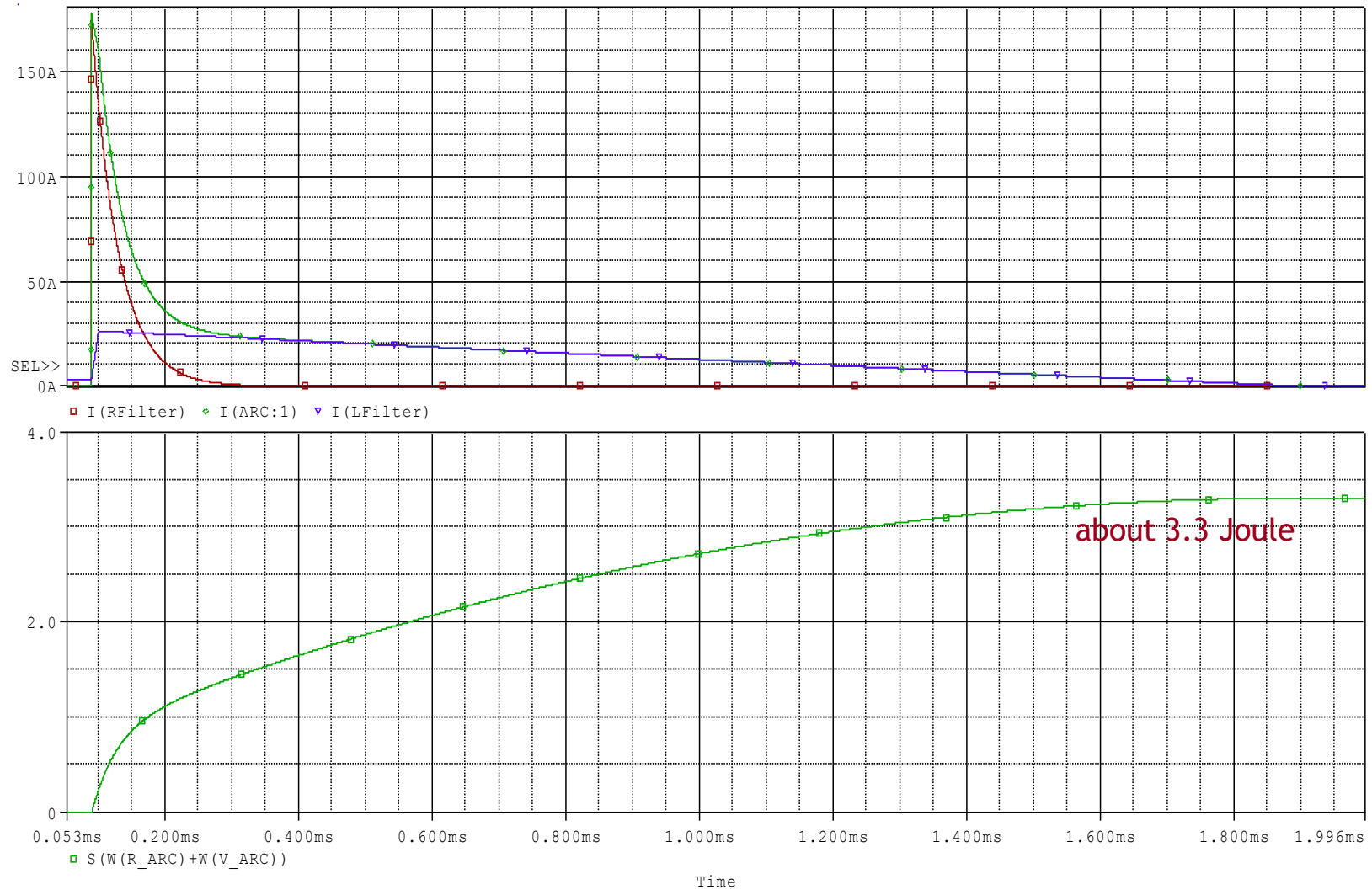


SIMULATION: WITH CABLE


100 METER CABLE ADDED TO THE SIMULATION

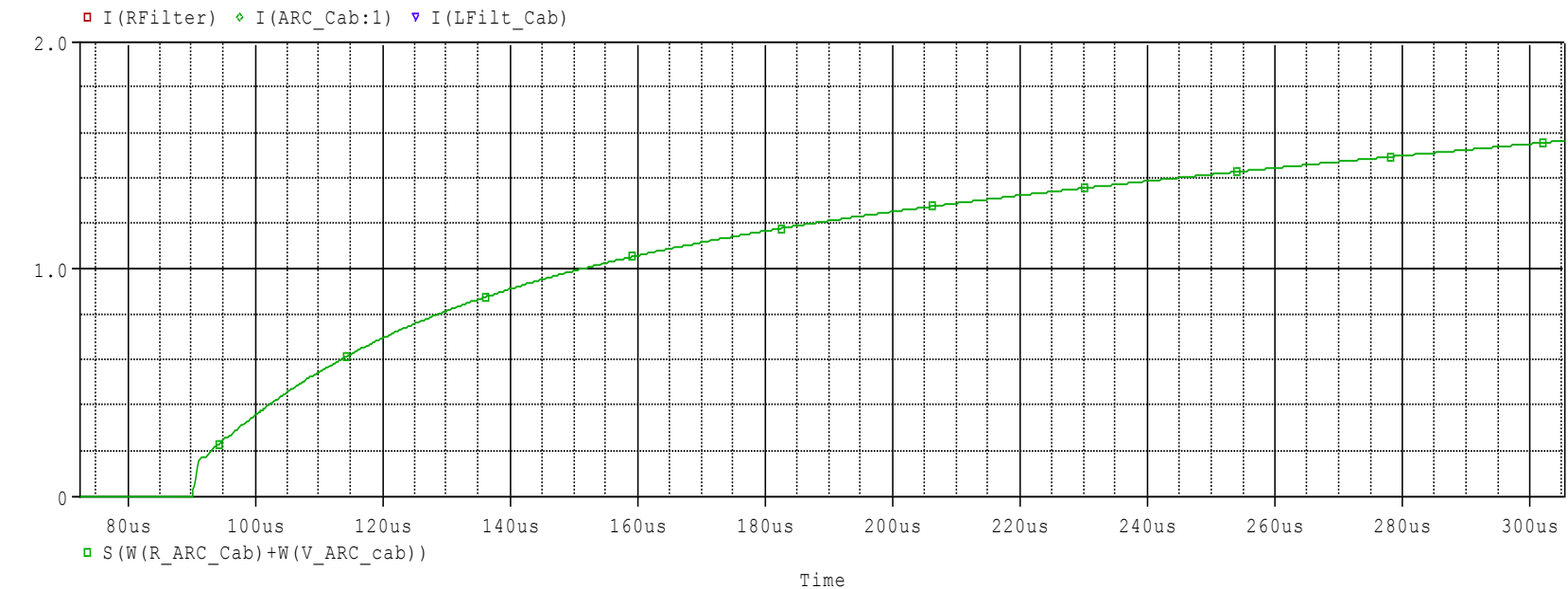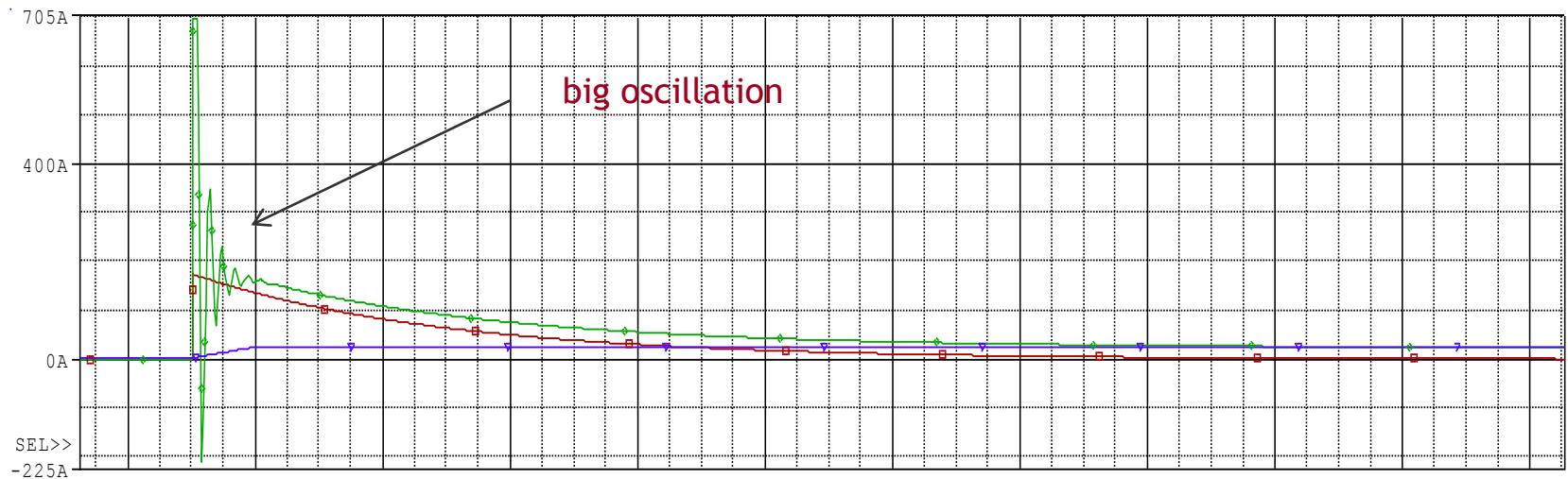

SIMULATION: WITH CABLE AND SNUBBER

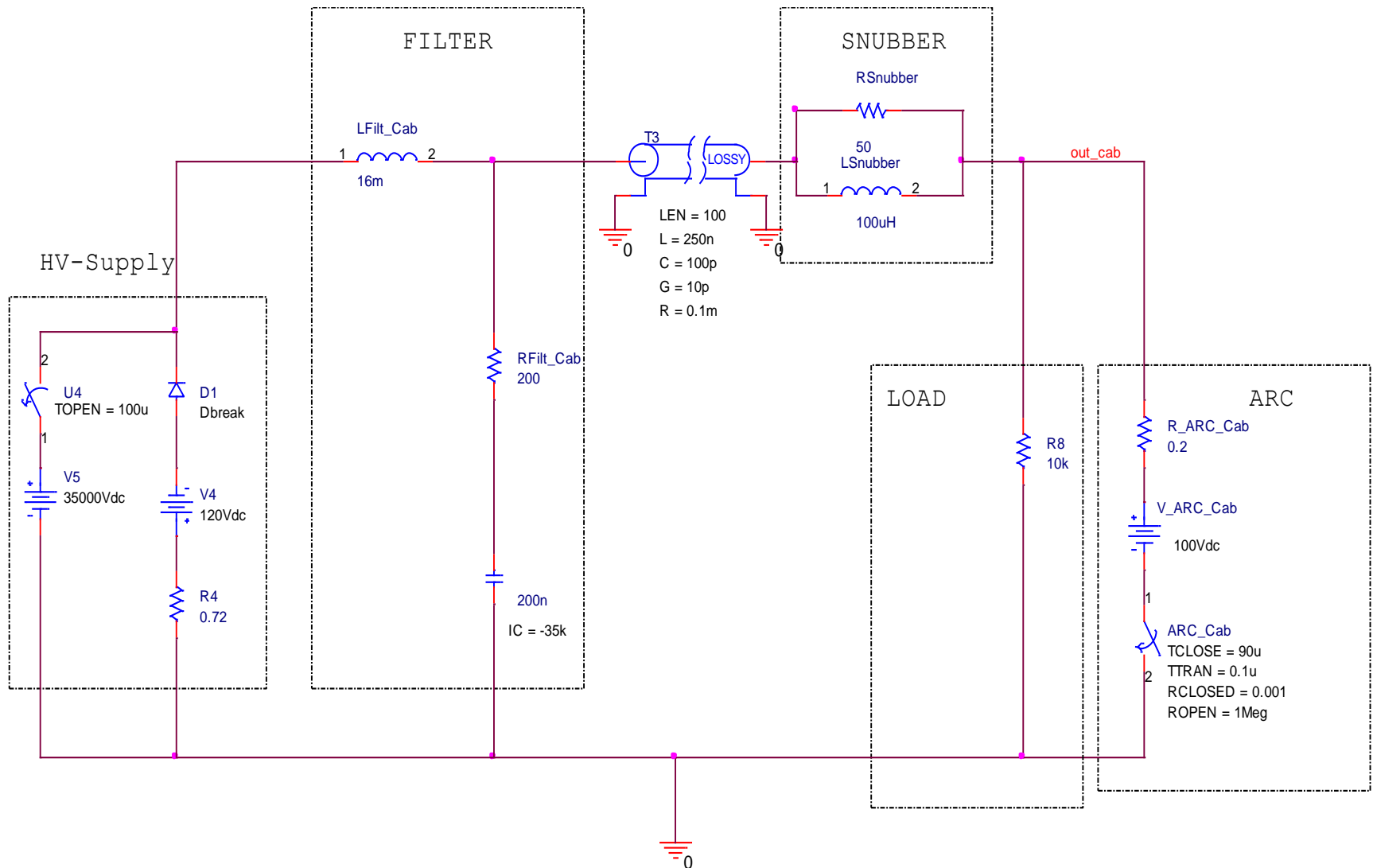

SIMULATION: WITH CABLE AND SNUBBER

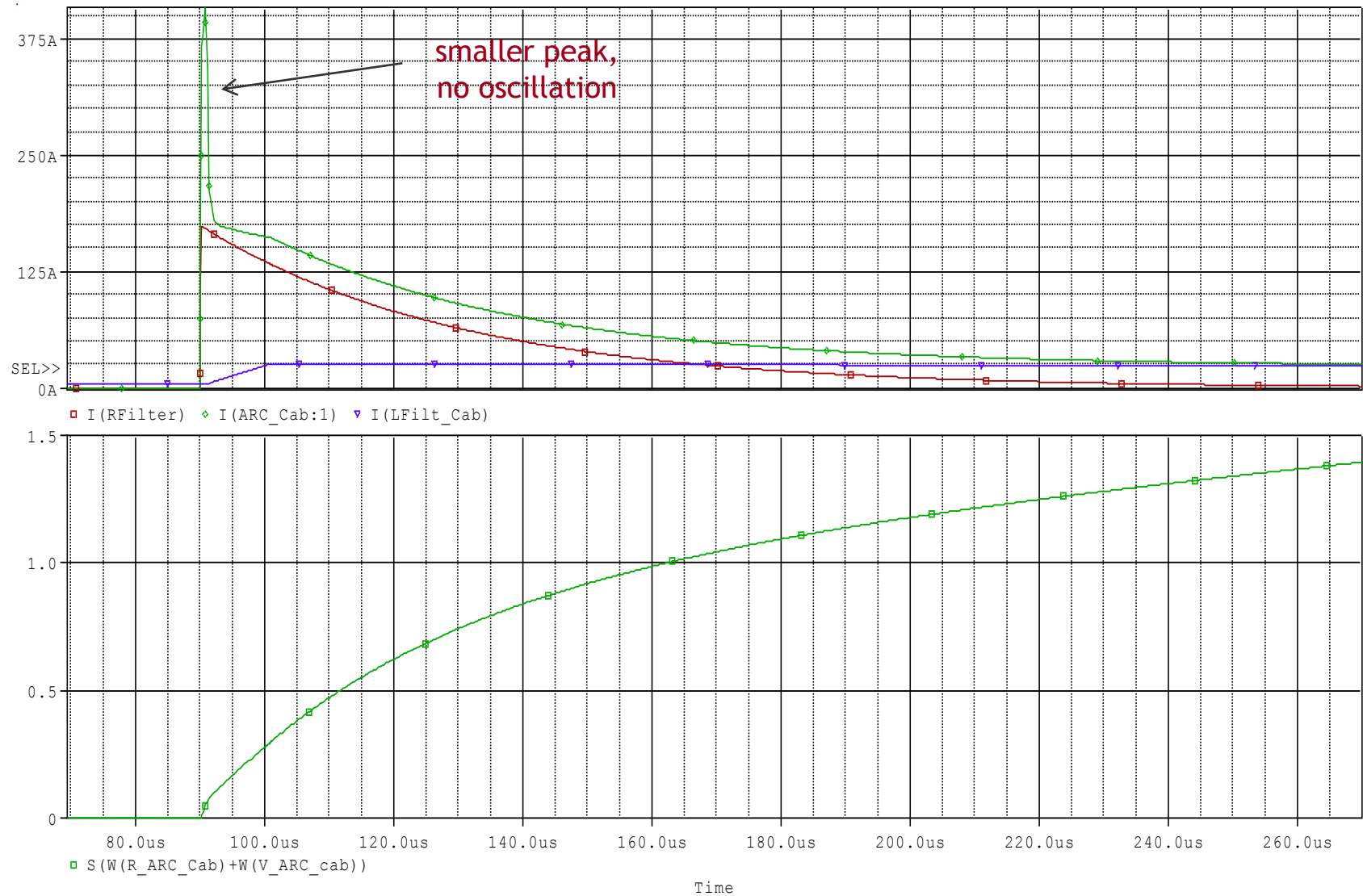

ENERGY DISSIPATION SUMMARY

► *Where is the energy dissipated in case of a short?*


► Filter Capacitor:

- Almost everything is dissipated in the filter resistor

► Filter Inductance:

- Before shutdown of the PSM the L is charged → Energy
- After PSM shutdown the energy is dissipated in the short and the diodes of the PSM

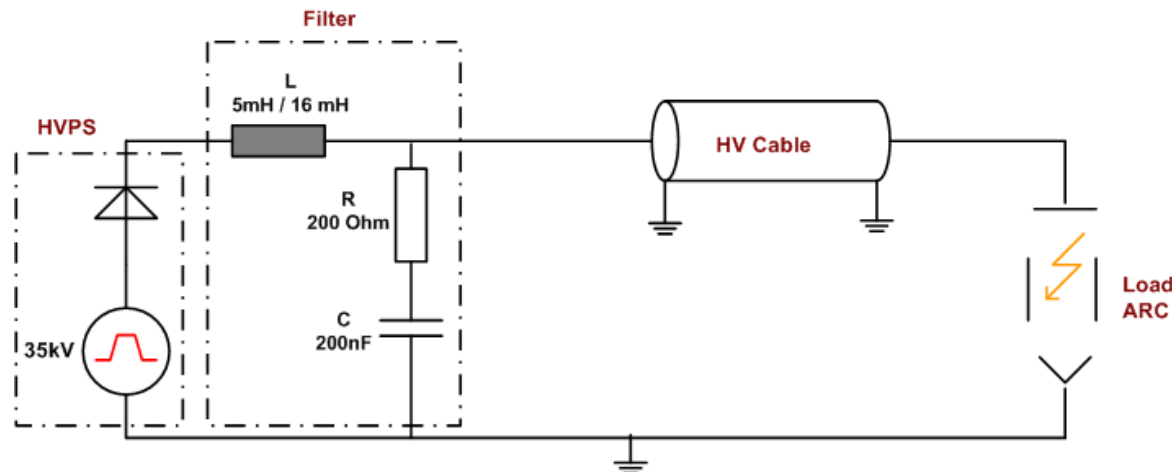► Cable snubber are reducing oscillations and Arc Energy



▶ ***How can the energy be reduced, measures?***

- ▶ Filter can be optimized according operating point.
- ▶ More complex filters instead a simple RLC network.
- ▶ Tradeoff: Filter vs. Energy
- ▶ Using Cable Snubbers for long cables
- ▶ Thomson patented Inverse voltage Operation Mode

KGP5: INVERSE VOLTAGE OPERATION


► *Application example: KGP5 Test stand for Tubes*

- 160 kV / 3.2 MW CW
- Higher power in pulsed mode
- 5 μ s Rise time
- Arc energy can be **set between 2 Joule and 20 Joule**
- This specifications required new solution:
 - **Inverse Voltage Operation Mode**



KGP5: INVERSE VOLTAGE OPERATION



► Principle

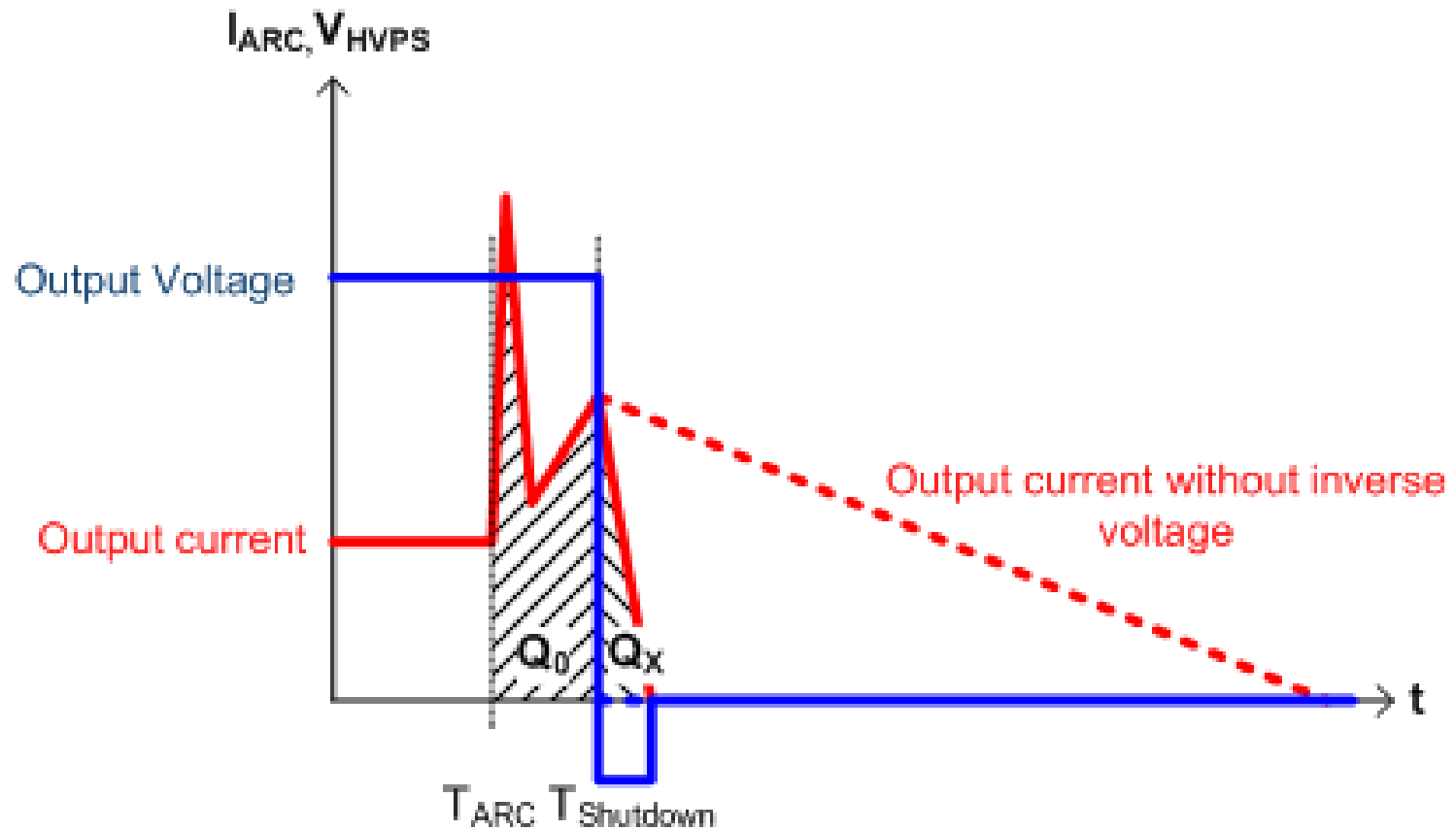

KGP5: INVERSE VOLTAGE OPERATION

► Short Circuit Current Simulations


- Green: output current without inverse voltage operation
- Red: output current with inverse voltage operation

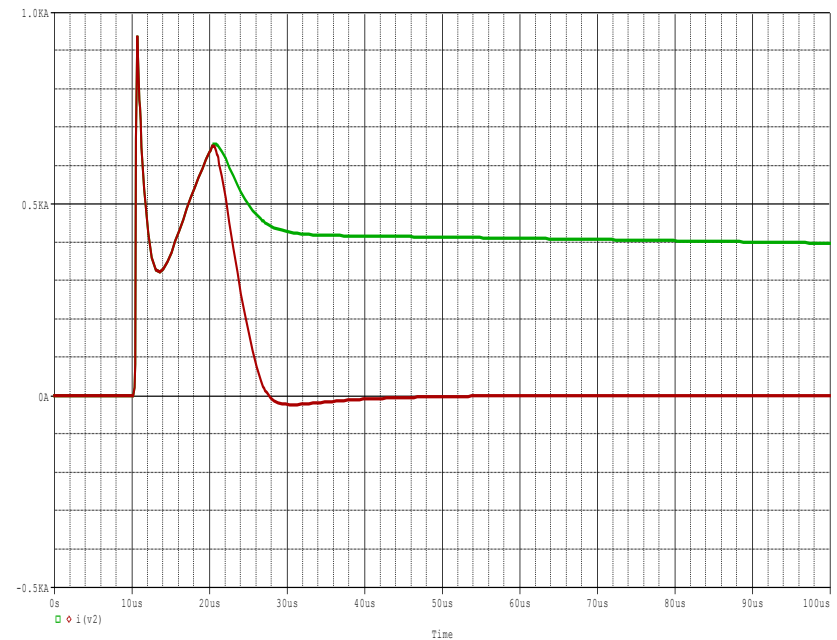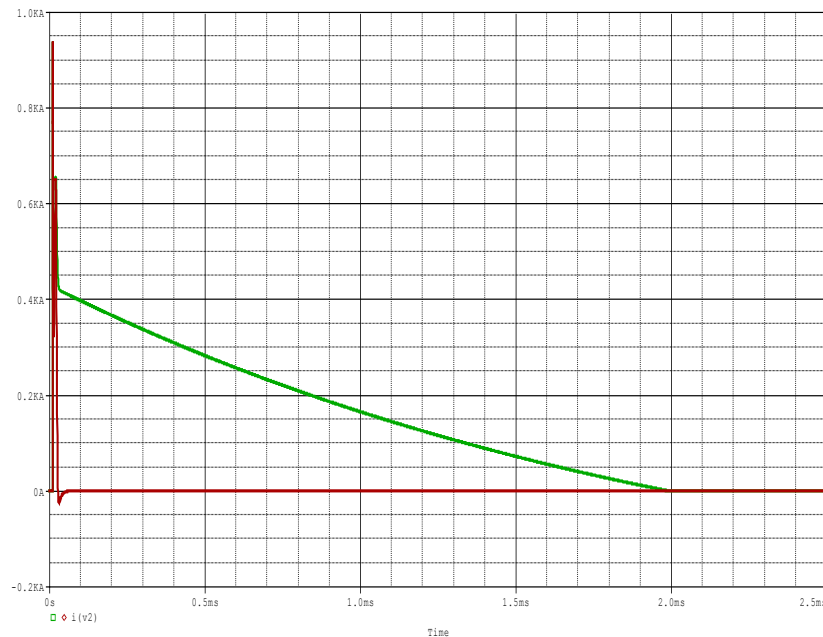

KGP5: INVERSE VOLTAGE OPERATION


► Short circuit Test on Tube teststand

- Adjustable arc energy 2 – 20J
- Main Issue with IVO was the 20J not the 2J → 2Point Regulation implemented
- Top Trace:
 - $V_{out} = 102\text{kV}$; Energy Setting = 2.5J
 - Charge Measured 29mAs (2.9J @100V)
- Bottom Trace:
 - Two point regulation until energy is reached

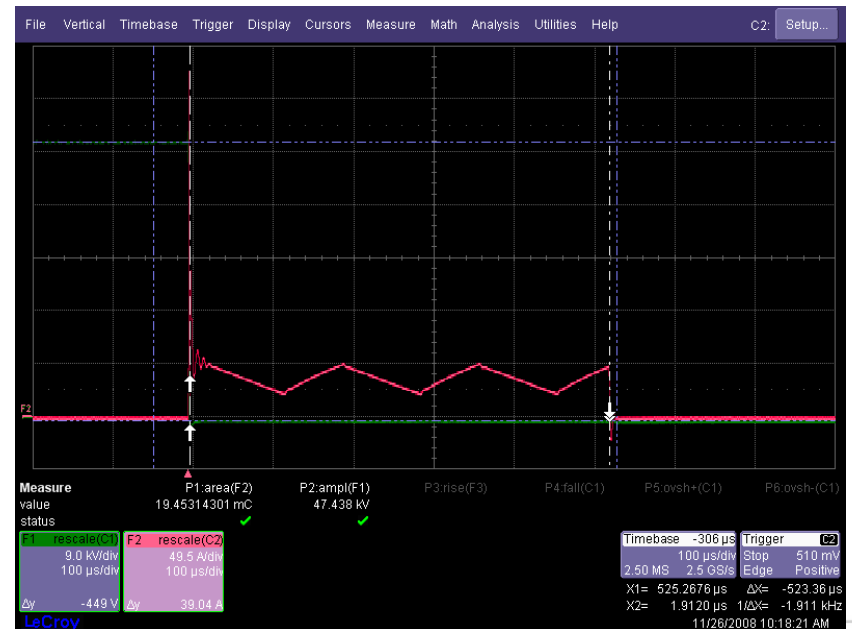

KGP5: INVERSE VOLTAGE OPERATION

► Two point regulation for a defined Q

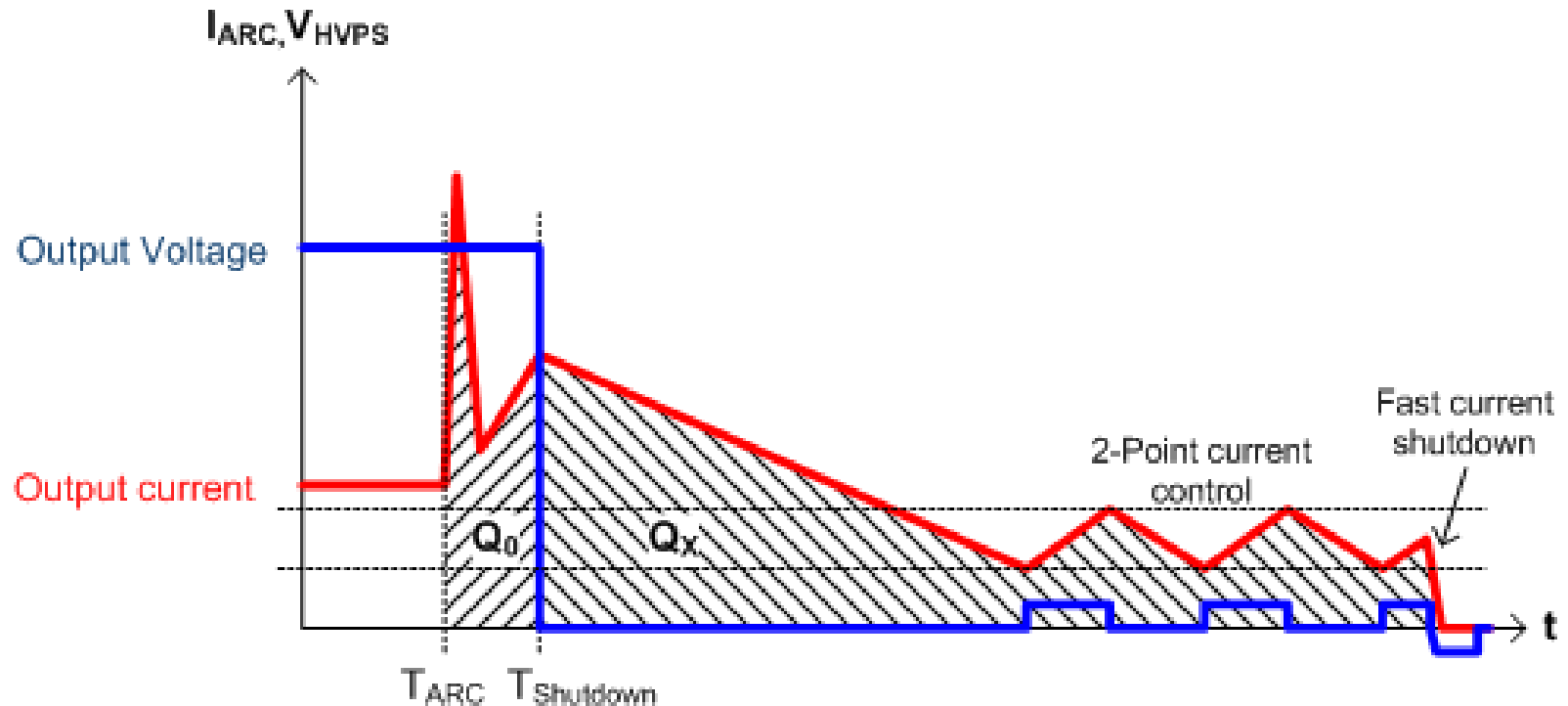

▶ **Summary**

- ▶ Bigger capacitors or inductors does not necessarily mean more energy in the arc.
- ▶ Considering the whole system is important!
- ▶ Degrees of freedom allow optimization → therefore it is important to know the real requirements.
- ▶ May be an iterative process together with the customer.
- ▶ Thomson's Inverse Voltage Supplies can reduce the energy to a minimum.

THANK YOU

