




CERN
European Organization for Nuclear Research
Organisation Européenne pour la Recherche Nucléaire

Power converters

Definitions and classifications
Converter topologies

Frédéric BORDRY
CERN

"Introduction to Accelerator Physics"
28 October - 9 November, 2012
GRANADA - SPAIN

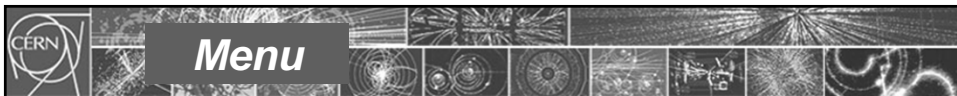Menu

- Power converter definition and classification
- Power converter topologies:
 - line commutated and switch mode based*
 - Sources, power switches (semiconductors), commutation rules,...
- Special case for magnet powering
(Voltage source - Current source)
- Pulsed power converters
- Control and precision

In 1 hour ????

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

2




High energy physics and power converters



The « Nobel prize » power converter :

[Cockroft & Walton] who in 1932 used this voltage multiplier to power their particle accelerator, performing the first artificial nuclear disintegration in history. They used this cascade circuit for most of their research, which in 1951 won them the Nobel Prize in Physics for "Transmutation of atomic nuclei by artificially accelerated atomic particles".

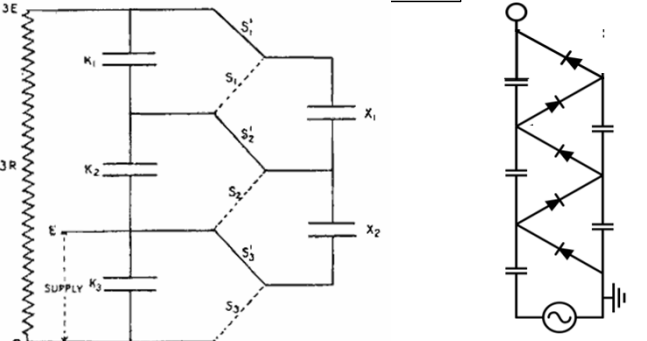Schematic of Cockcroft and Walton's voltage multiplier. Opening and closing the switches S_1, S_2 transfers charge from capacitor K_3 through the capacitors X up to K_1 .



Voltage multiplier : switches...

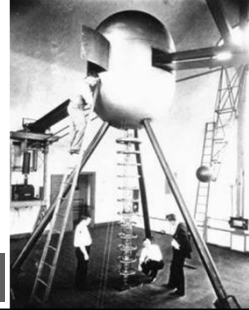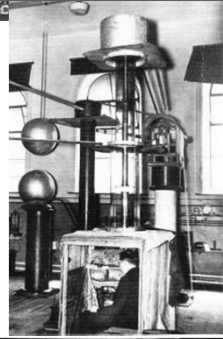

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



"On a new principle for the production of higher voltages."


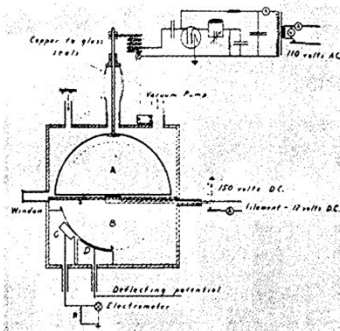


Diagram of the first successful cyclotron constructed by Lawrence and M. S. Livingston. The single dee is five inches in diameter.

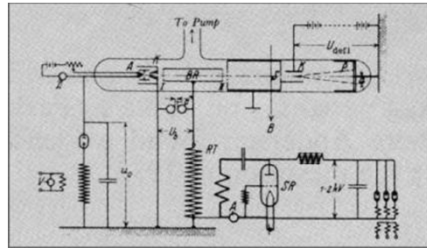

The difficulties of maintaining high voltages led several physicists to propose accelerating particles by using a lower voltage more than once. **Lawrence** learned of one such scheme in the spring of 1929, while browsing through an issue of *Archiv für Elektrotechnik*, a German journal for electrical engineers. Lawrence read German only with great difficulty, but he was rewarded for his diligence: he found an article by a Norwegian engineer, **Rolf Widerøe**, the title of which he could translate as "On a new principle for the production of higher voltages." The diagrams explained the principle and Lawrence skipped the text.

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



Power converters : Definitions

The source of the beam blow-up when we could not prove it was the RF (Control room operator)

A powerful (small) black box able to convert MAD files into currents (Accelerator Physics group member)

An equipment with three states, ON, OFF and FAULT (Another operator)

Is it the same thing as a power supply? (Person from another physics lab)

A big box with wires and pipes everywhere and blinking lamps. Occasionally it goes BANGG! (Former CERN Power Converter Group secretary view)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

5



Power converters : Definitions (cont'd)

That which feeds the magnets (a visitor)

A stupid installation taking a non-sinusoidal current at poor power factor (Power distribution engineer)

A standard piece of equipment available from industry off-the-shelf (a higher management person, not in in this room !)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

6



Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ? Precision is not important for time being. Don't worry it's not urgent. Next month is OK "
 (Email received 05.12.08)


Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

40A power converter:
 Size? Weight ? Cost?



[40A, 100 kV,] klystron power converter

DC Power: 4 MW

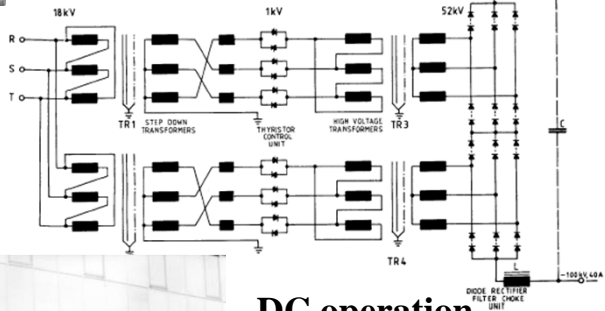

November 2012




DC operation





Pulsed klystron modulators for LINAC 4

Specification	symbol	Value	unit
Output voltage	V_{kn}	110	kV
Output current	I_{out}	50	A
Pulse length	$t_{rise}+t_{set}+t_{flat}+t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	%
Repetition rate	$1/T_{rep}$	2	Hz

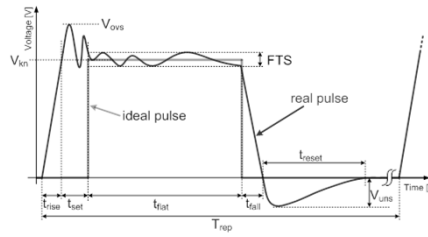

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

Peak power : 5.5MW
Average power: 20kW



LHC orbit corrector : [±60A,±8V]

Magnet : L=7 H ; R = 30 mΩ (60m of 35 mm²)
 $T = L/R = 300 \text{ s} \Rightarrow f^{CL}_B \cong 0.5 \text{ mHz}$
 $U_{static} = R \cdot I = 1.8 \text{ V}$



6 V for the di/dt with L= 7 H

(di/dtmax \cong 1A/s) OK

Small signal : $f^{CL}_B \cong 1 \text{ Hz}$: $\Delta I = 0.1 \text{ A} = 0.15 \% I_{max}$

“The power converters involved in feedback of the local orbit may need to deal with correction rates between 10 and 500 Hz”;
 $f^{CL}_B \cong 50 \text{ Hz}$ ($\Delta I = 1\%$: **Umax = 2400 V ??????..**)

(U_{max} = 8V => $\Delta I = 30 \text{ ppm } I_{max}$ at 50 Hz)



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

CERN **Power converters specifications**

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ? Precision is not important for time being. Don't worry it's not urgent. Next month is OK "
(Email received 05.12.08)

Need of more specification data:

- Output Voltage
- DC or Pulsed (pulse length and duty cycle)
- Output voltage and current reversibility
- Precision (short and long term)
- Ripple (load definition)

Environment conditions: grid, volume, water ,....

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

11

CEI **Energy source** **Applications**

Power converter

The task of a power converter is to process and control the flow of electric energy by supplying voltages and currents in a form that is optimally suited for user loads.

50 or 60 Hz ; AC

DC current

Control

Traction and auxiliary


Domestic Appliance

Medical applications

Industrial applications, Welding, Induction Heating,

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

12

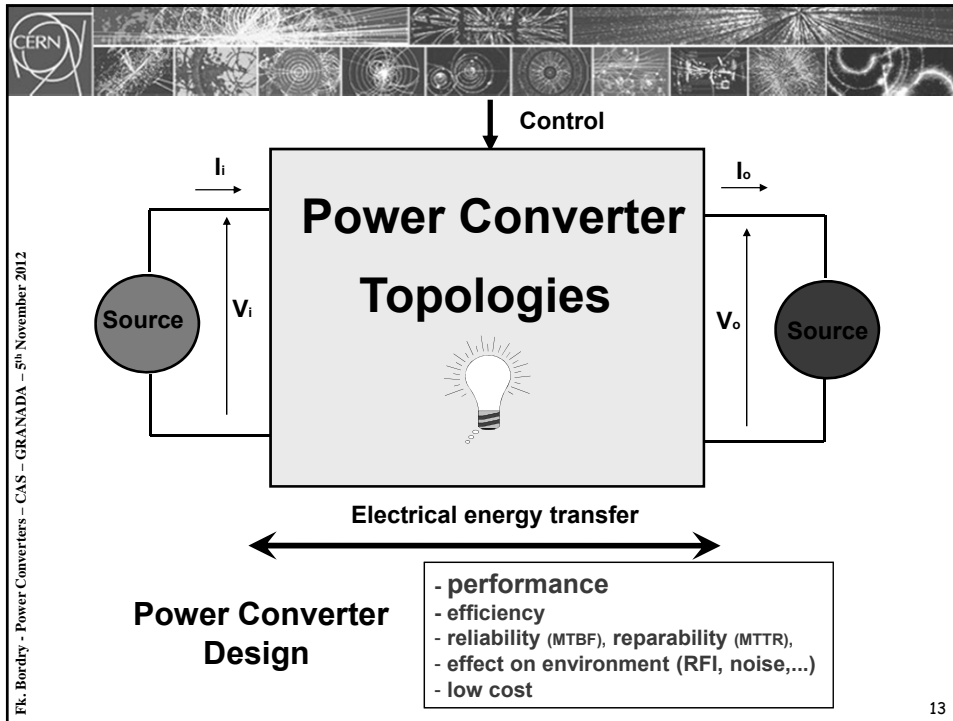

Source definition

Source definition: any element able to impose a voltage or a current, independently of, respectively, the current flowing through, or the voltage imposed at its terminals.

A source could be a generator or a receptor.

Two types of sources:

Voltage source
 which imposes a voltage independently of the current flowing through it. This implies that the series impedance of the source is zero (or negligible in comparison with the load impedance)

Current source
 which imposes a current independently of the voltage at its terminals. This implies that the series impedance of the source is infinite (or very large in comparison with the load impedance)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

14

CERN

Commutation

Direct Link Inverse Link Open Link

Active components used as switches to create a succession of link and no link between sources to assure an energy transfer between these sources with high efficiency.

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

15

CERN

Direct link configuration : Direct voltage-current converters

a b c

Connexion
(energy flow between sources)

Disconnexion
(current source short-circuited, voltage source open circuited)

U K1 I K4
K2 K3

- K1 and K3 closed => a
- K2 and K4 closed => b
- K1 and K4 (or K2 and K3) closed => c

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

16

CERN

Commutation rules

- *electronic switches modify the interconnection of impeding circuits*
- *any commutation leading instantaneous variations of a state variable is prohibited*

Turn On impossible

Turn Off impossible

Interconnection between two impeding networks can be modified only if :

- the two networks are sources of different natures (voltage and current)
- the commutation is achieved by **TWO** switches. The states of the two switches must be different.

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

17

CERN

Power Converter topology synthesis: the problem

the interconnection of sources by switches

Fundamental rules and source natures

Power converter topologies

switch characteristics

I_k

V_k

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

18




Switch characteristics

Switch : semiconductor device functioning in commutation

The losses in the switch have to be minimized


Z_{on} very low

Z_{off} very high

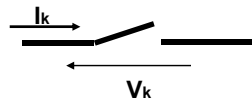

Switch : at least two orthogonal segments

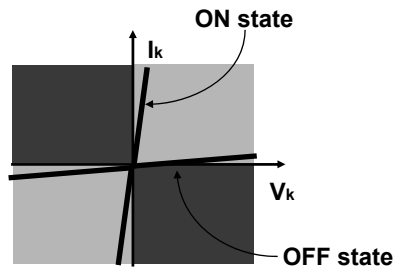(short and open circuit are not switches)



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



19



Once upon a time.... not so far





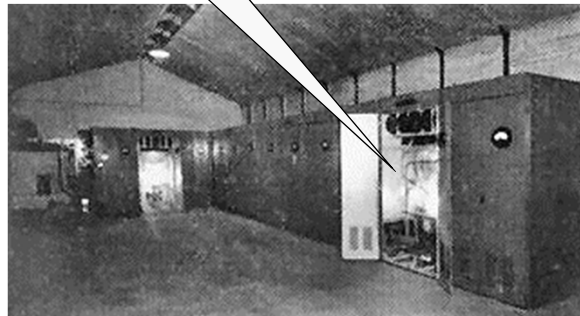
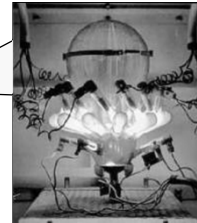
This is a 6-phase device, 150A rating with grid control. It measures 600mm high by 530mm diameter.



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

20

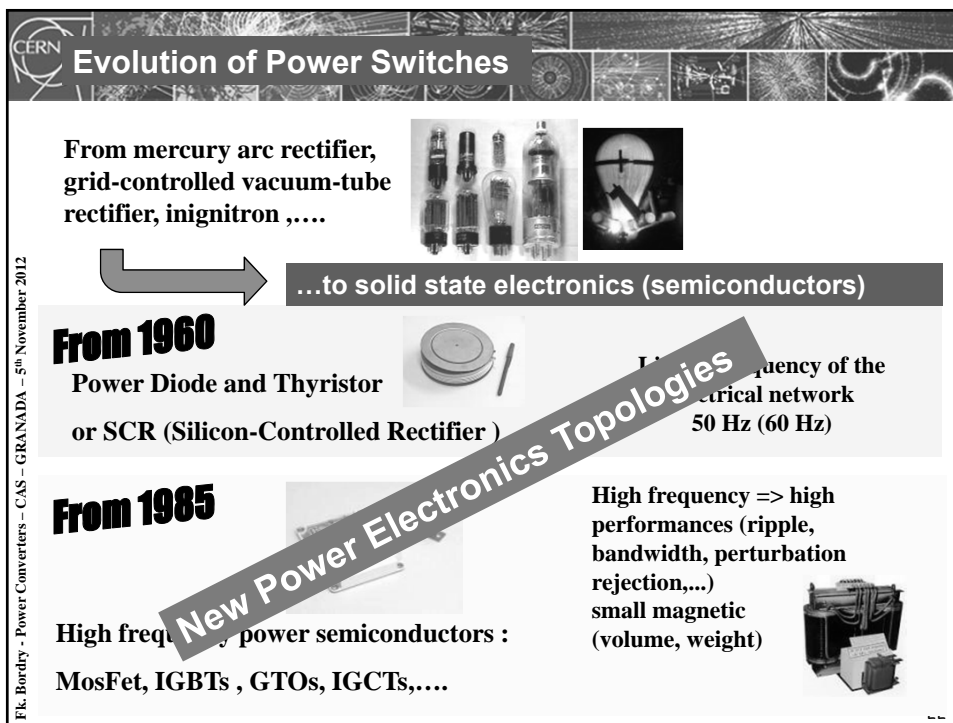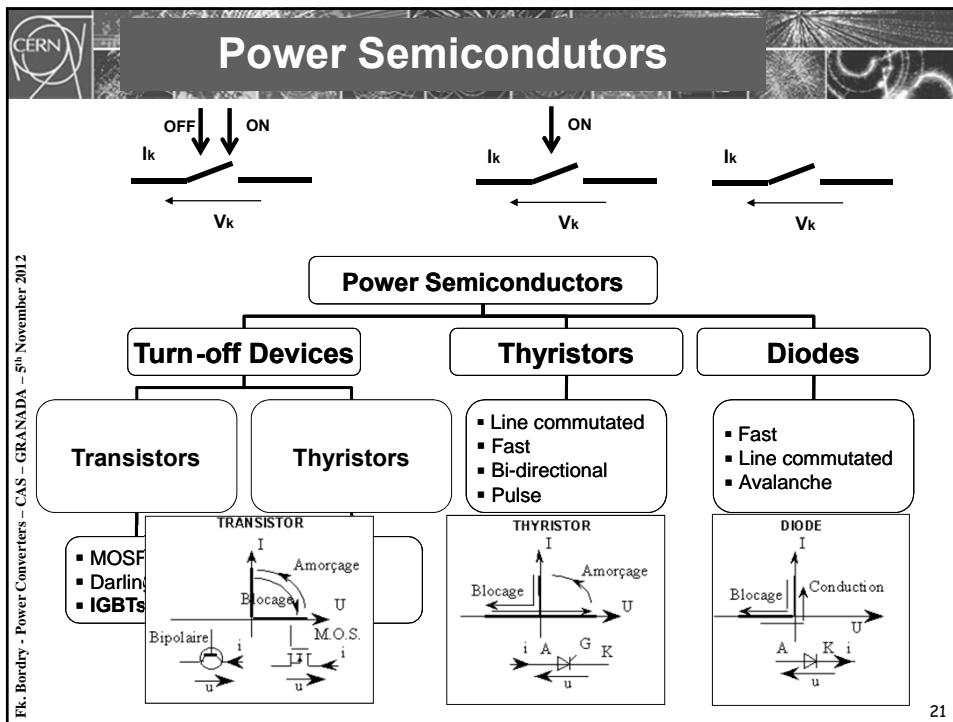

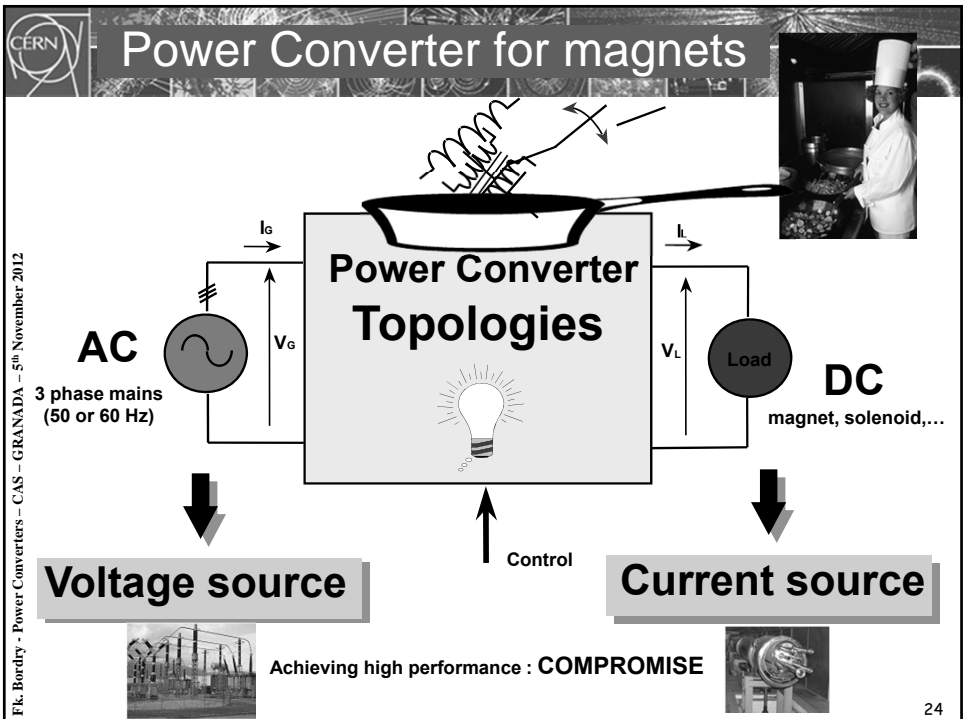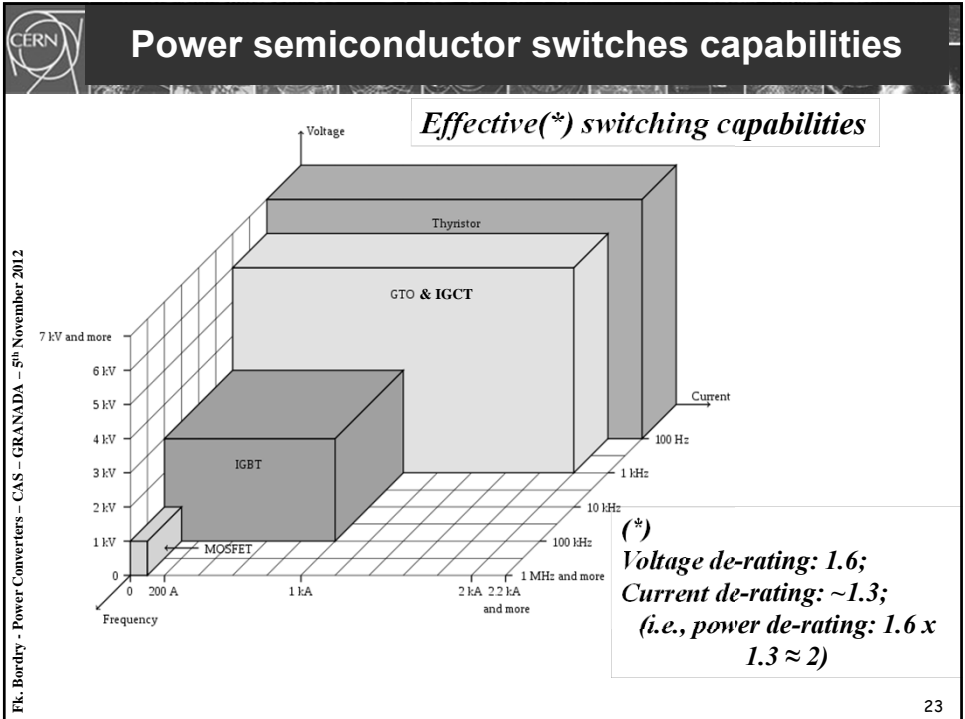

Operating Modes

Output Source

1 Quadrant mode

2 Quadrants mode

4 Quadrants mode

4	1
3	2

25

General power converter topologies

1



Rectifier

Filters

AC Voltage Source

DC Current Source

26

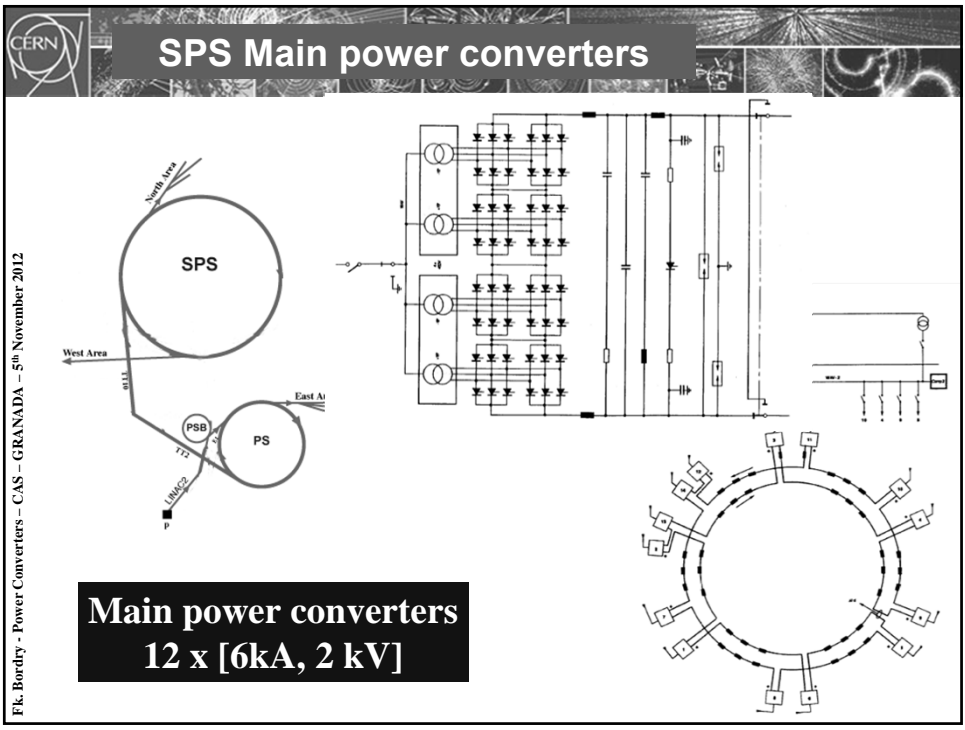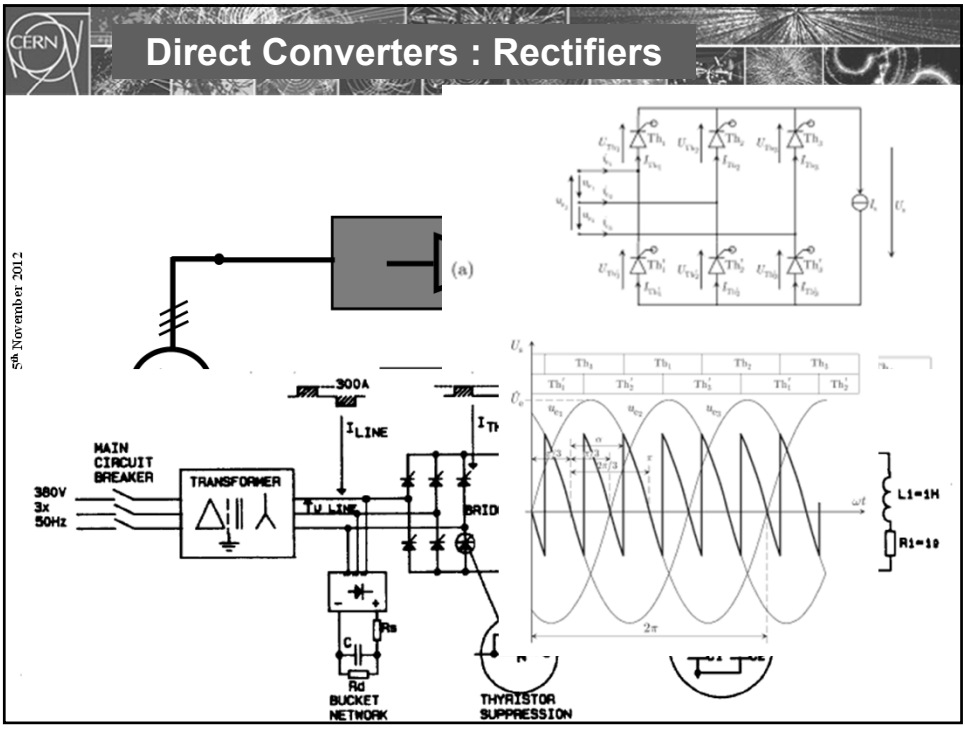

**Two Quadrant Phase Controlled Rectifiers
for high current SC magnets**

**3 Phase
50/60 Hz
Supply**

+15°


-15°

**LHC main bending power
converters
[13 kA, 190 V]**

Fig. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

29



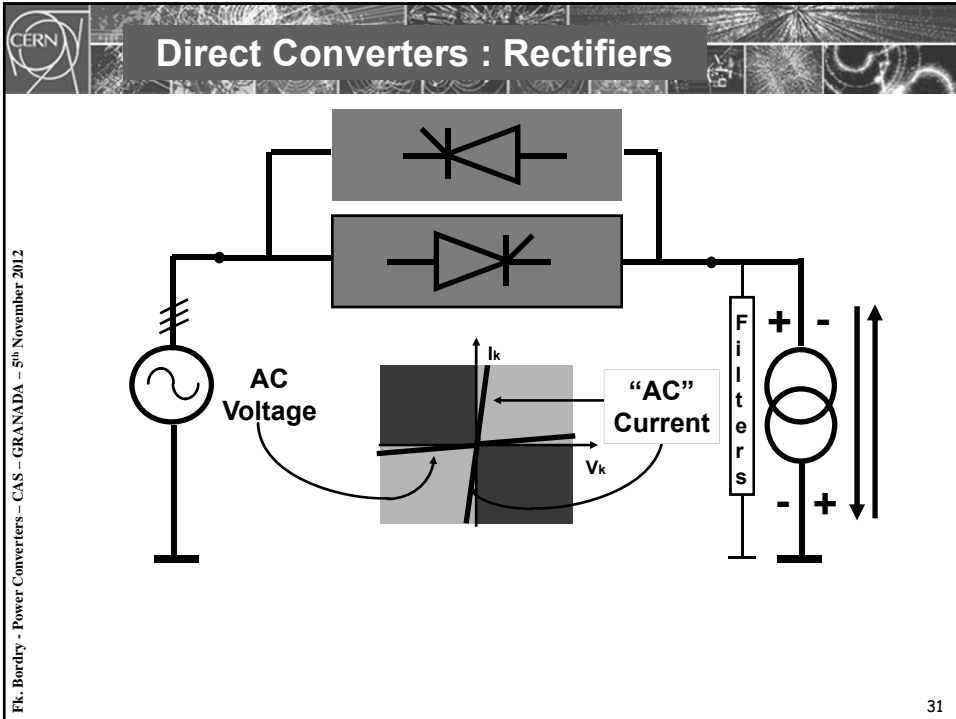

CERN

Direct Converters : Phase Controlled Rectifiers



- ☺ very high power capability
- ☺ moderate prices and competitive market
- ☺ simple structure, well understood (but care needed with high currents)
- ⊗ three phase transformer operates at low frequency (50 or 60 Hz)
- ⊗ variable power factor from 0 to 0.8
- ⊗ harmonic content on input current
- ⊗ response time is large (ms)
- ⊗ current ripple is large (passive or active filters)

passive (active) filters operating at low frequency

Increase of pulse number (3,6,12,24,48) but
complexity (cost, control,...)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

32

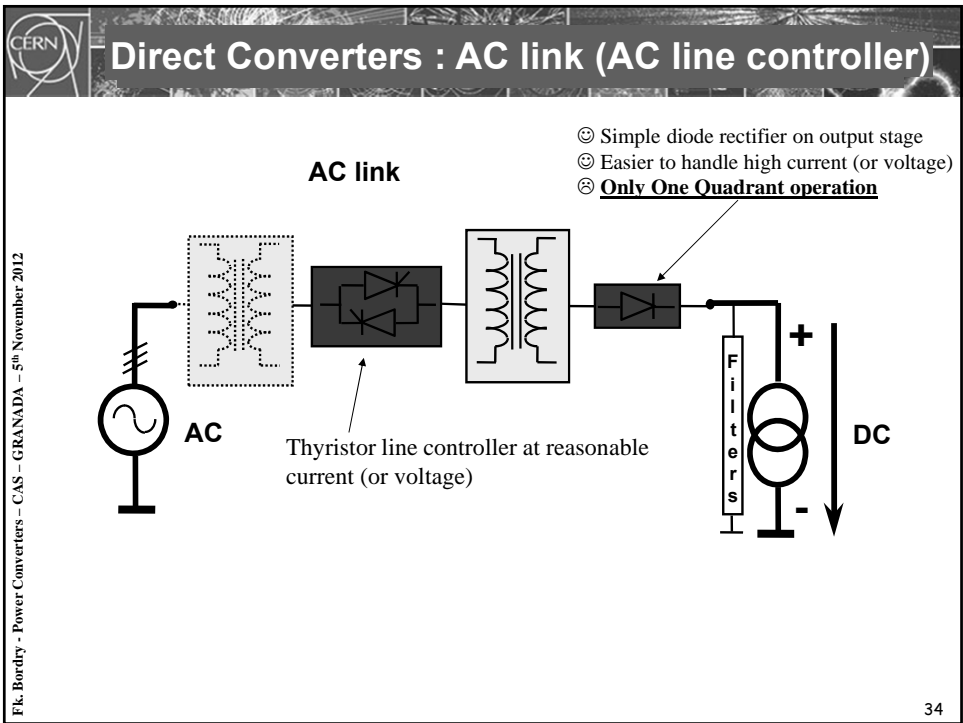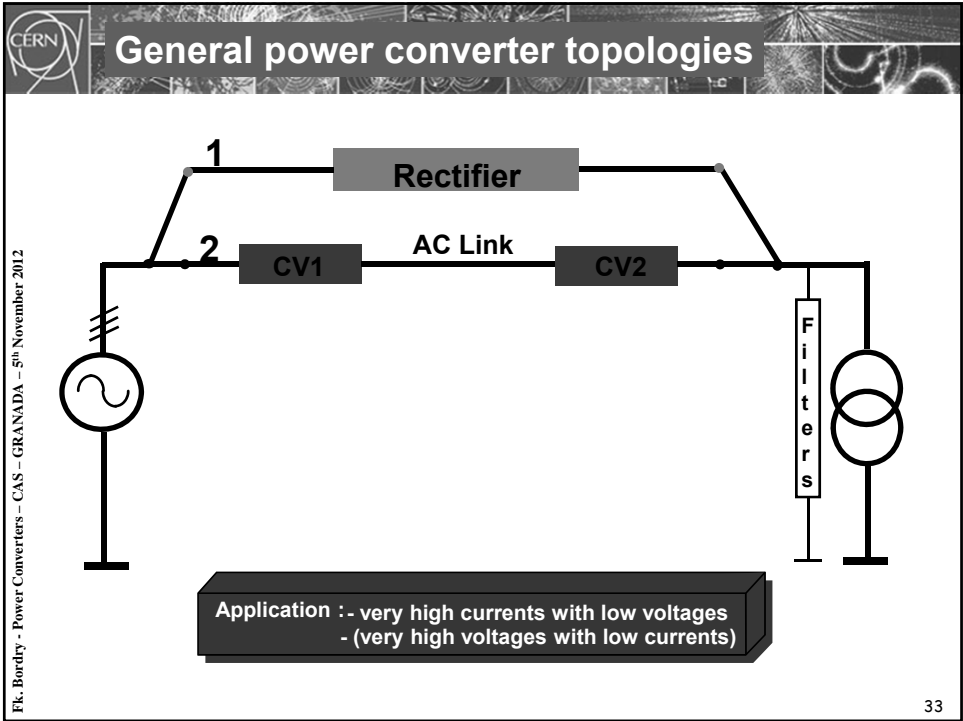

CERN [100 kV, 40A] klystron power converter

November 2012

DC operation

35

CERN General power converter topologies

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

1 Rectifier

2 CV1 AC Link CV2...

3 CV1 DC Link CV2

Rectifier

Filters

Voltage Source

Current Source

Voltage Source

Current Source

36

CERN Galvanic isolation at AC input source (50Hz transformer)

50 Hz transformer
Optimal voltage output
Galvanic isolation

CV1
Diode bridge
6 or 12 pulses

CV2
PWM Converter
Hard switching

Magnet

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

37

CERN New PS Auxiliary Power Converters

Peak Power: 405 kW
Voltage: $\pm 900V$
Max Current: $\pm 450A$

Multi-Turn Extraction: Current/Voltage waveforms

720V Peak
350 A Peak
14ms

Ch1 2.00 V 2.00 V 14.00ms A Ch1 3.84 V
27 Jun 2008 10:29:37
61.20 %

Current Loop Bandwidth $\approx 1kHz$

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

38


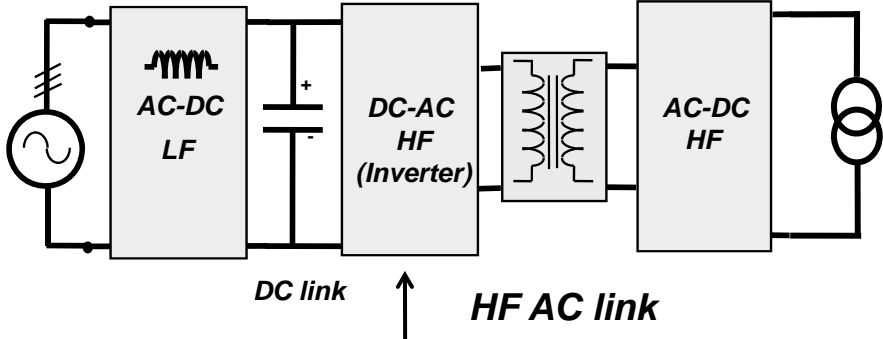
CERN

Indirect AC-DC-AC-DC converter

Three cascade power conversion stages:

- 1) Simple DC source (Diode (thyristor) rectifiers)
- 2) HF DC-AC converter (Inverter)
- 3) HF AC-DC converter (Rectifier) (often diode rectifier)

HF transformer to provide the galvanic isolation





Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

39

CERN

LHC Switch-Mode Power Converters

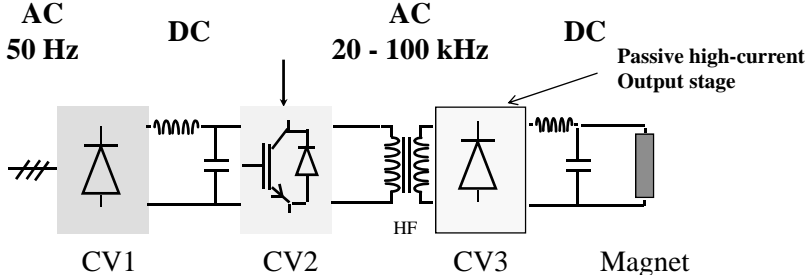

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

Voltage loop:
bandwidth few kHz

Fast power semiconductors (IGBT)

Semiconductor losses :
soft commutation


HF transformer and output filter : ferrite

- light weight, reduced volume (HF transformers and filters)
- good power factor (0.95)
- high bandwidth and good response time
- Soft commutation gives low losses and low electrical noise
- small residual current ripple at output
- More complex structure, less well understood, limited number of manufacturers

40



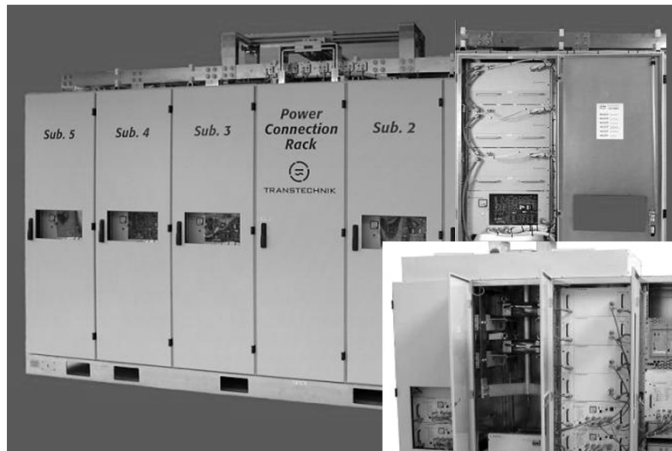LHC: 1-quadrant converter: modular approach



- 1-quadrant converters:**
- [13kA, 18V] : 5*[3.25kA, 18V]
 - [8kA, 8V] : 5*[2kA, 8V]
 - [6kA, 8V] : 4*[2kA, 8V]
 - [4kA, 8V] : 3*[2kA, 8V]

MTBF and MTTR optimization




Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

41



DC and slow pulsed converters

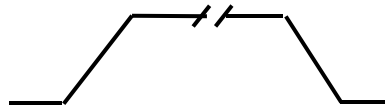

Rise and fall time < few ms

Control of the ramps

- High and medium power**
- Phase Controlled Rectifiers**
- Diodes and thyristors rectifiers
 - 50Hz transformers and magnetic component (filters)
 - 1-quadrant and 2-quadrants (but unipolar in current) : energy back to the mains
 - 4-quadrant: back-to-back converters

- Low and Medium power**
- Switch-mode power converters**
- Mosfets , IGBTs, IGCTs,... turn-off semiconductors
 - HF transformers and passive filters
 - excellent for 1-quadrant converter
 - 4-quadrant converters but with energy dissipation (very complex structure if energy has to be re-injected to mains)


Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

42

Pulsed converters


Synchrotrons

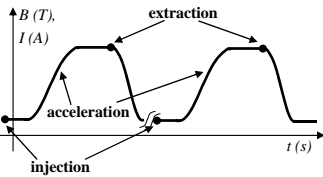- Beam is injected, accelerated and extracted in several turns;



Linac's and transfer lines

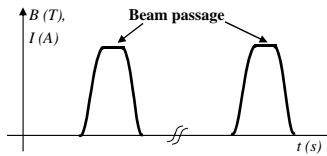- Beam is passing through in one shot, with a given time period;




Rise and fall time < few ms

Direct Energy transfer from mains is not possible:
Intermediate storage of energy
Peak power : could be > MW (average power kW)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

43

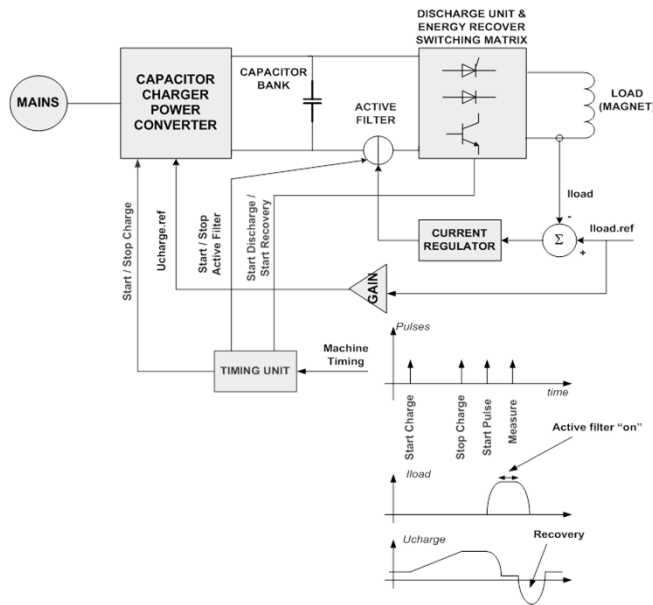Block schematic of a fast pulsed converter



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

44

High current, high voltage discharge capacitor power converters

Charging Unit
10kV - 20A

Thyristors Bridge
Diods Bridge
TR
Start Charging
Stop Charging

Discharge Circuit 1
Capa
Thyristors Discharge
Pulse 1
Delay 50ms
Pulse 2
Thyristors Discharge
Capa
Discharge Circuit 2

50 ms
6 ms

Polarity Changer
Earthing
Power Cables (~1000m)

Experimental Area
TR
HORN

150 kA for the horn
180 kA for the reflector

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

45

Pulsed klystron modulators for LINAC 4

Specification	symbol	Value	unit
Output voltage	V_{kn}	110	kV
Output current	I_{out}	50	A
Pulse length	$t_{rise} + t_{set} + t_{flat} + t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	5
Repetition rate	$1/T_{rep}$	2	Hz

Peak power : 5.5MW
Average power: 20kW

PS1, PS3, PS4 - Commercial
PS2 - CERN male
120kV High voltage cables
120kV High voltage connectors

Main solid state switches
Capacitor bank charger power converter, PS1
PULSE TRANSFORMER (OL TANK)
Anode power converter, PS3
Filament power converter, PS4
High Frequency ISOLATION TRANSFORMER
KLYSTRON (OL TANK)
A - Anode
C - Collector
K - Cathode
F - Filament

Drop compensation power converter or "bounce", PS2

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

46




Pulsed klystron modulators for LINAC 4


Specification	symbol	Value	unit
Output voltage	V_{kn}	110	kV
Output current	I_{out}	50	A
Pulse length	$t_{rise}+t_{set}+t_{flat}+t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	5
Repetition rate	$1/T_{rep}$	2	Hz



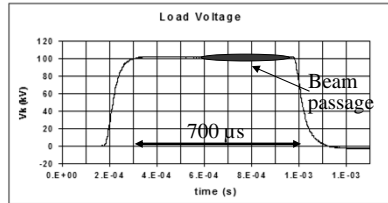Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



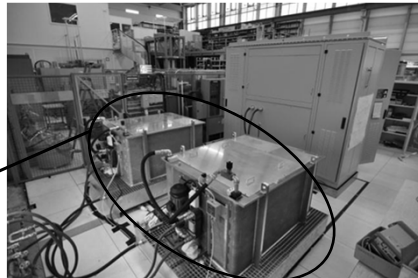
Test phase:
Water cooled
dummy loads
2.5T each!



47



Power Converter % Load


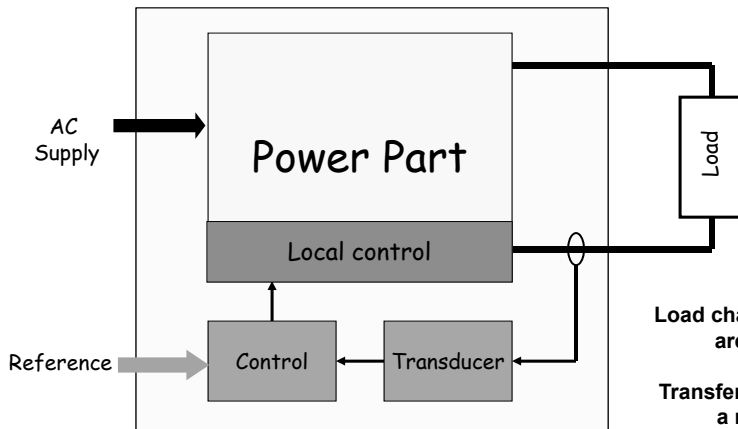


Load characteristics
are vital.

Transfer function is
a must !

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

48

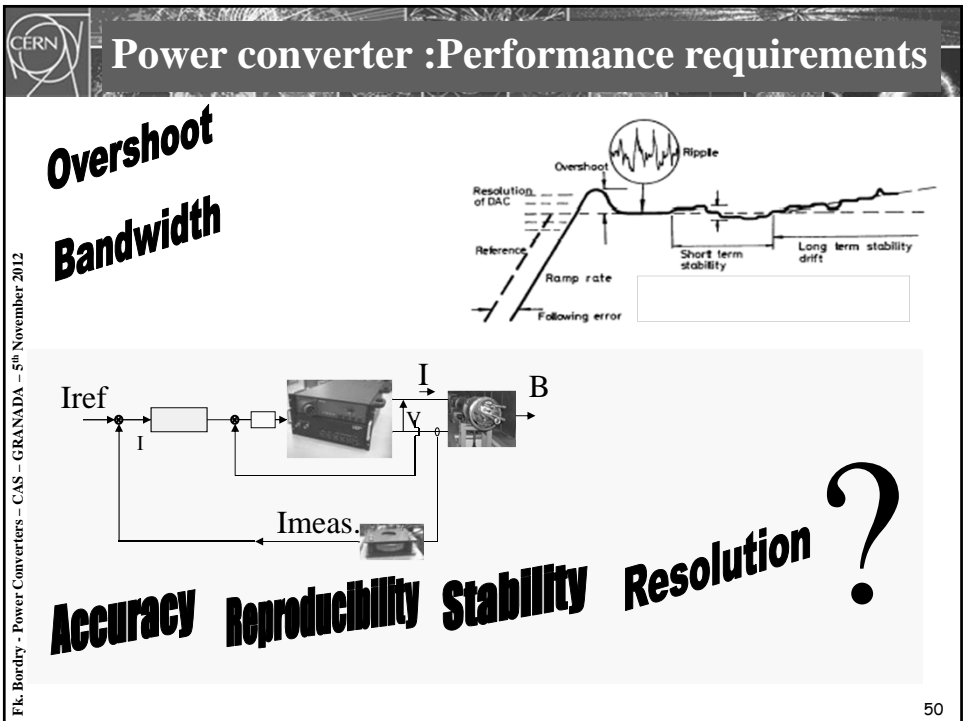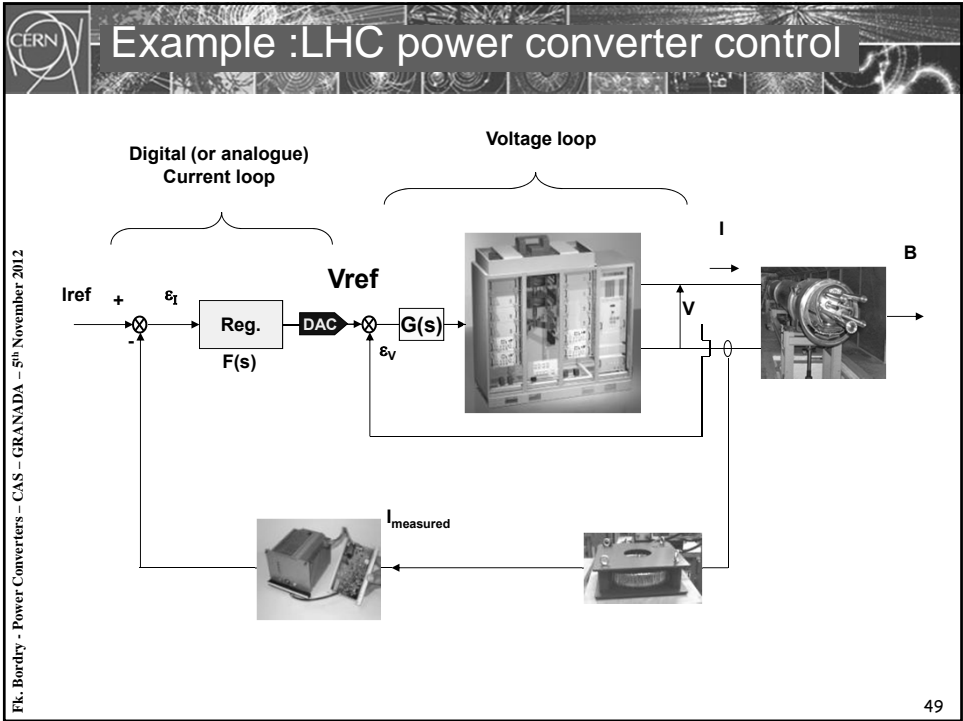




Glossary

Precision

- Accuracy


Long term setting or measuring uncertainty taking into consideration the full range of permissible changes* of operating and environmental conditions.

* requires definition

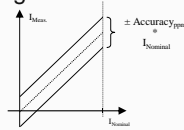


- Reproducibility

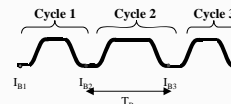Uncertainty in returning to a set of previous working values from cycle to cycle of the machine.



- Stability

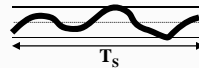Maximum deviation over a period with no changes in operating conditions.



Accuracy, reproducibility and stability are defined for a given period

Precision is qualitative . Accuracy, reproducibility, stability are quantitative.


Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012





Resolution

Smallest increment that can be induced or discerned.

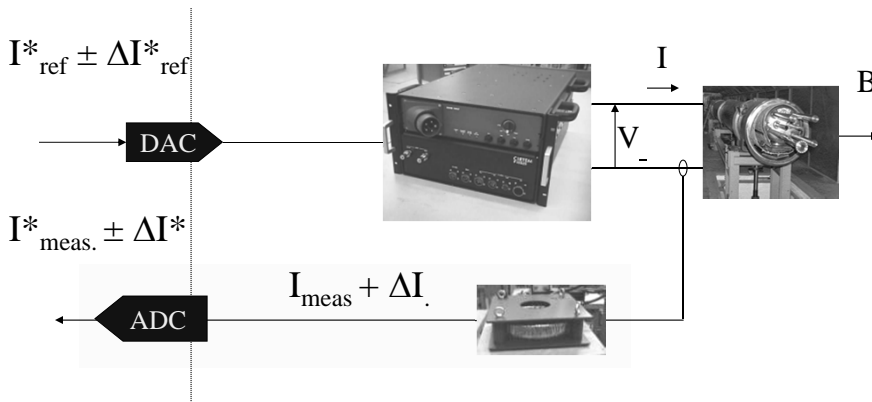The resolution is expressed in ppm of $I_{Nominal}$.
Resolution is directly linked to A/D system



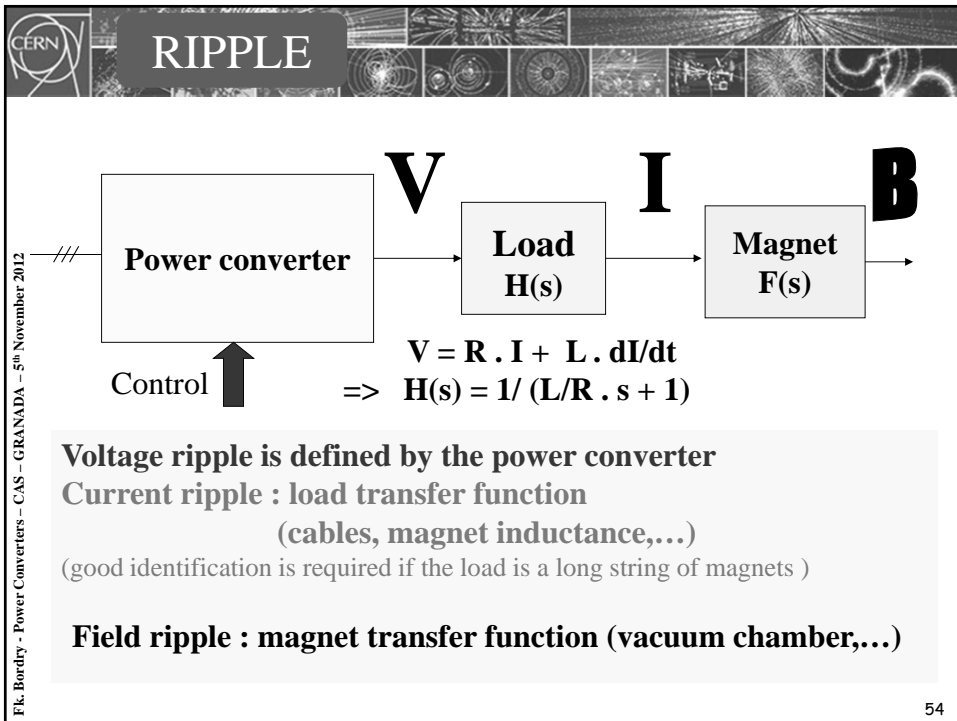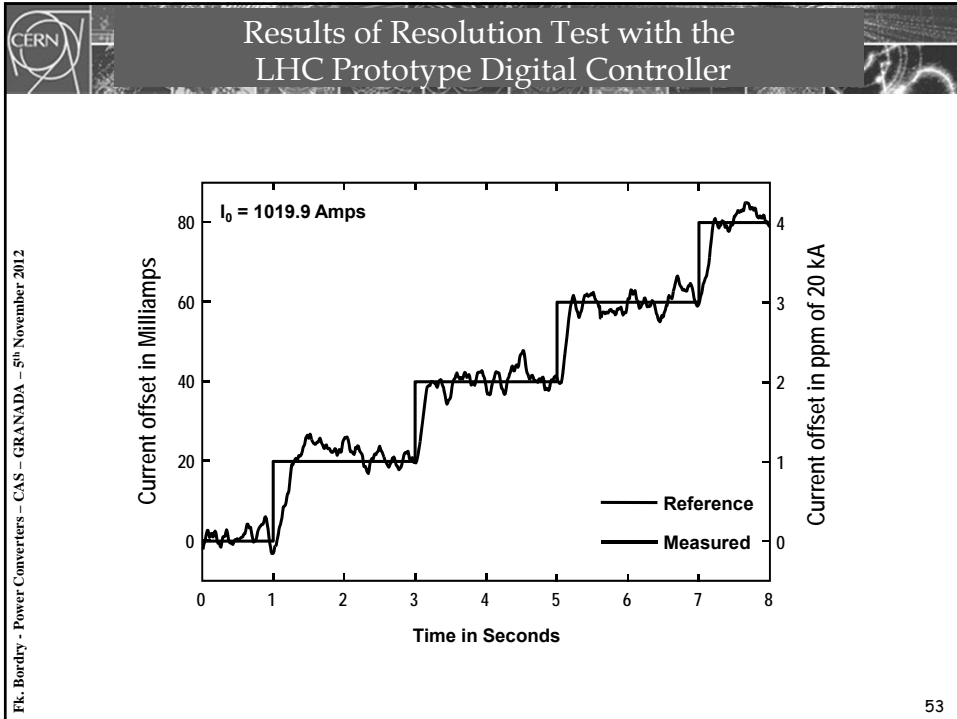Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



CERN

Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ? Precision is not important for time being. Don't worry it's not urgent. Next month is OK "
(Email received 05.12.08)

Load characteristics : I and V reversibility (1 , 2 or 4-quadrants ?) ;
 Transfer function (at least R, L, C) => will define V and then power

Range : I_{max} (and I_{min})

Rise and fall time (di/dt max; voltage constraint on the load); is the precision an issue during the ramps (beam or no beam) => Pulsed converters with intermediate storage ?
 => bandwidth (topology and control strategy)


Precision: accuracy, reproducibility, stability - Resolution


Ripple: $\Delta V(f)$ => passive (or active) filters ; control strategy (SMPC)

Is the volume a constraint ? Is water cooling possible ?
 Environment: temperature and humidity; EMI conditions, radiation, ...
 Hardware design and production take time.....

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

55

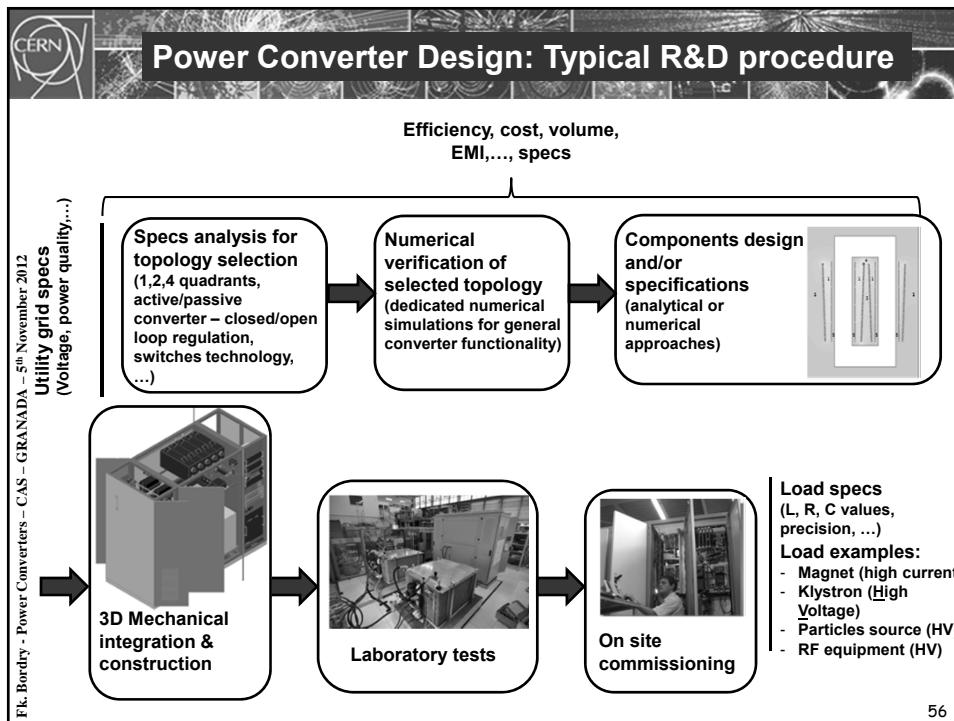

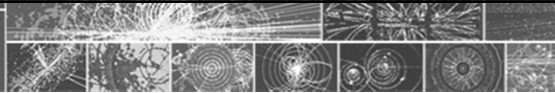

The end

**CAS - CERN Accelerator School :
Power converters for particle accelerators
26 - 30 Mar 1990, Switzerland**

**CAS - CERN Accelerator School :
Specialised CAS Course on
Power Converters for particle accelerators
12 - 18 May 2004 - Warrington, UK**

**2014: Next Specialised CAS Course on
Power Converters for particle accelerators**

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

CERN Accelerator School &
the University of Granada
will organise a course on


Introduction to Accelerator Physics

28 October - 9 November 2012
Granada, Spain

This basic introductory course will be of interest to young
staff from laboratories, universities and companies
manufacturing accelerator equipment.
The course will focus on the basics of Accelerator
Physics such as transverse and longitudinal dynamics,
beam measurements and an introduction
to multi-particle dynamics. A series of topical seminars
and tutorials will complete the programme.



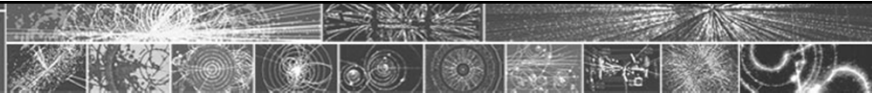Contact:
CERN Accelerator School
CH - 1211 Geneva 23
Tel: +41 22 767 94 80
www.cern.ch/cas/cas





Reserved slides

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



Energy conversion : transfer of energy between two sources

Introductory example

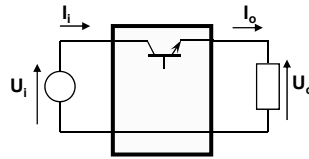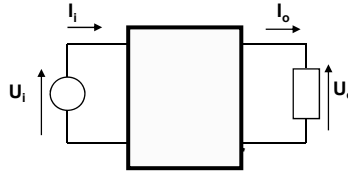

Linear solution

Transfer of energy between

- DC voltage source U_i
- DC source (nature is not defined) : U_o, I_o


Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

59



Linear solution
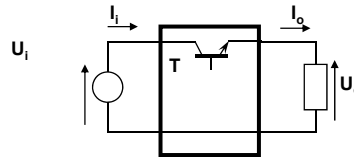
$$U_i = 24V ; U_o = 10V \text{ and } I_o = 600A$$



$$P_o = U_o \cdot I_o = 10 \cdot 600 = 6'000 \text{ W}$$

$$P_T \text{ (power dissipated by the switch)} = U_T \cdot I_T = (U_i - U_o) \cdot I_o = (24 - 10) \cdot 600 = 8'400 \text{ W}$$

$$\text{Converter efficiency} = P_o / (P_T + P_o) = 42 \% \text{ !!!!!}$$

Furthermore, it'll be difficult to find a component (semiconductor) able to dissipate 8'400 W .

Then impossible for medium and high power conversion

Commutation

$$\left. \begin{array}{l} - U_T \approx 0 \text{ if } I_T \neq 0 \\ - I_T = 0 \text{ if } U_T \neq 0 \end{array} \right\} P_T \approx 0 \text{ (if power switches are ideal)}$$

~~Linear mode~~



switch mode
(power switches either saturated or blocked)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

60



Reactive Components of Power Converters

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012



Inductors & Capacitors Functionalities in Power Converters

- Electrical Energy storage (POPS, SMES, indirect-link converters)
- Adaptation of converter I/O sources (DC or AC current & voltage filters, Bouncers ...)
- Phase control of power flow through HF resonant LC stage
- Implementation of non dissipative commutation (ZCS or ZVS snubbers)

Transformer Functionalities in Power Converters

- Galvanic Isolation
- High Voltage or Low Voltage converters (Klystrons or Magnets)



Reactive Components can degrade:

- Converter Efficiency
- Converter Power Density: W/m³ & W/kg
- Converter Control Bandwidth: Filter Time constants


61



Reactive Components of Power Converters

Fk. Bordry - Power Converters - CAS - GRANADA - 5th

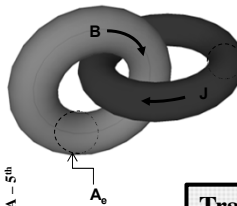Basic Dimensional Analysis of Reactive Components



Transformer Apparent Power (VA)

$$S = \sum VI = f \cdot K_u \cdot K_v \cdot B \cdot J \cdot A_e \cdot S_{Cu} \propto f \cdot B \cdot J \cdot [L]^4$$

Transformer Losses (W)

$$\text{MagLosses} \propto B^2 \cdot [L]^3$$

$$\text{CopperLosses} \propto J^2 \cdot [L]^3$$

Transformer Temperature Rise

$$\text{TempRise} = \frac{\text{Losses}}{h \cdot S_{ext}} \propto [L]$$

Transformer Apparent Power at Constant Temp Rise ($B \cdot J \propto [L]^{-1}$)

$$S(\text{VA}) \propto f \cdot [L]^3 \propto f \cdot \text{Volume}$$

Inductor Stored Magnetic Energy (J)

$$W_{mag} = \frac{1}{2} LI^2 = K_u \cdot B \cdot J \cdot A_e \cdot S_{Cu} \propto B \cdot J \cdot [L]^4$$


Inductor Stored Magnetic Energy at Constant Temp Rise ($B \cdot J \propto [L]^{-1}$)

$$W_{mag} (J) \propto [L]^3 \propto \text{Volume}$$

62

CERN **Reactive Components of Power Converters**

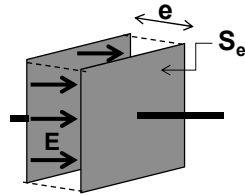Basic Dimensional Analysis of Reactive Components



Capacitor Stored Magnetic Energy (J)

$$W_{el} = \frac{1}{2} CV^2 = K \cdot \epsilon \cdot E^2 \cdot S_e \cdot e \propto \epsilon \cdot E^2 \cdot [L]^3$$

$$W_{el}(J) \propto [L]^3 \propto Volume$$



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012


Basic Dimensional Analysis of Converter I/O Filters

Inductor Current Filter L

$$V = L \cdot \frac{\Delta I}{\Delta t} \propto \frac{Volume}{I_o^2} \Delta I_{ppm} \cdot I_o \cdot f$$

$$\Delta I_{ppm} = \frac{\Delta I}{I_o} \quad \Delta t \propto \frac{1}{f}$$
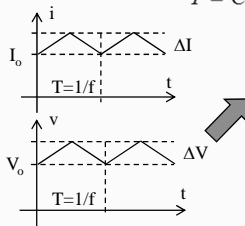
$$Volume \propto \frac{V \cdot I_o}{f \cdot \Delta I_{ppm}}$$



Capacitor Voltage Filter C

$$I = C \cdot \frac{\Delta V}{\Delta t} \propto \frac{Volume}{V_o^2} \Delta V_{ppm} \cdot V_o \cdot f$$

$$\Delta V_{ppm} = \frac{\Delta V}{V_o} \quad \Delta t \propto \frac{1}{f}$$

$$Volume \propto \frac{V_o \cdot I}{f \cdot \Delta V_{ppm}}$$

33

CERN **Reactive Components of Power Converters**

Trade-off on dynamic performance

Main Time Constant of LC Filter

$$\tau = \sqrt{L \cdot C} \propto \frac{1}{f \cdot \sqrt{V_{ppm} \cdot I_{ppm}}}$$

Main Design Trade off
Frequency

Volume
Mass

Ripple ppm

Dynamics τ (s)



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

64



EMC : ELECTROMAGNETIC COMPATIBILITY

COMPATIBILITY : Emission - Immunity IEC 61204 -3

Norms for the power converters :

Emission :

IEC 61204-3 (replaced IEC-60478-3)
(CISPR 11 ; EN 55011)


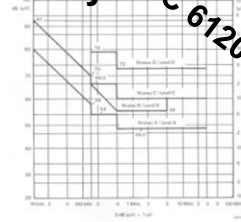


Figure 3 - Valeurs limites pour PEM par conduction
Limit values for conducted EMI

Immunity :

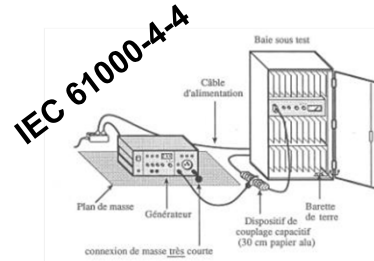IEC 61000 - 4 :
Burst 61000 - 4 - 4
Surge 61000- 4 - 5



65



Classification of switches

- According to the degree of controllability:
- Diodes: On and Off states controlled by the power circuit (uncontrolled).
- Thyristors: Turned On by a control signal but turned off by the power circuit (semi-controlled).
- Transistors: Controllable switches. Can be turned On and Off by a control signal.
- For analysis purposes power switches are usually considered ideal: Instantaneous, lossless, and infinite current and voltage handling capability.

66

Diodes

- 2 terminals device.
- An ideal diode turns On when forward biased and Off when its forward current goes to zero.

Figure 2-1 Diode: (a) symbol, (b) $i-v$ characteristic, (c) idealized characteristic.

press-pack case (high power)
ABB
 Ex: 6 kV_{pk}, 3 kA_{av}

modules case (medium power)
SEMIKRON
 innovation+service
 Ex: 1.8 kV_{pk}, 80A_{av}

Other cases (low power)
IXYS
SOT-227 Minibloc case 1000V_{pk}, 2x30A_{av}
DO-203 Stud case Ex: 800V_{pk}, 110A_{av}
TO-220 case Ex: 600V_{pk}, 30A_{av}

618-CAS - GRANADA - 5th November 2012

67

Thyristor (Silicon Controlled Rectifier - SCR)

- 3 terminals device.
- 3 main operating regions.
- Latches On by a gate current pulse when forward biased and turns Off as a diode.
- Requires low power gate drives and is very rugged.

Figure 2-3 Thyristor: (a) symbol, (b) $i-v$ characteristics, (c) idealized characteristics.

press-pack case (high power)
Infineon
 Infineon Technologies Bipolar Control & Co. etc.
 Ex: 4.8kV_{pk}, 3.2 kA_{av}

modules case (medium power)
OMEREX
 Power Semiconductor Solutions
 Ex: 1.8 kV_{pk}, 500A_{av}

Other cases (low power)
IXYS
TO-93 case Ex: 1200V_{pk}, 325A_{av}
TO-208 Stud case Ex: 800V_{pk}, 30A_{av}
TO-220 case Ex: 800V_{pk}, 20A_{av}

Fk. Bordery - Power Converters - CAS - GRANADA - 5th Nov 2012

68



Controllable switches

- Used in forced-commutated converters ($f_{sw} > 60 \text{ Hz}$)
- Different types: MOSFET, IGBT, GTO, IGCT.
- Gate requirements and performance are quite different.
- Generic switch: Current flows in the direction of the arrow when the device is On.



Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

69



MOSFET

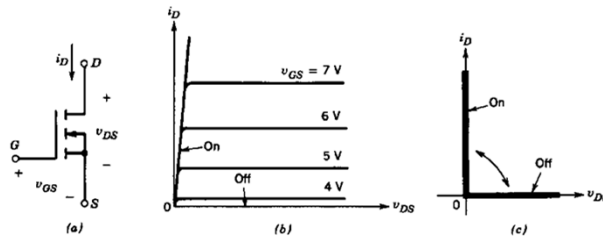


Figure 2-9 N-channel MOSFET: (a) symbol, (b) $i-v$ characteristics, (c) idealized characteristics.

- High input impedance on the gate (voltage controlled) device.
- Fast commutation times (tens to hundreds of ns). Low switching losses;
- Low On state resistance (R_{DS_on}).
- Easy paralleling
- Limited in voltage and power handling capabilities. Great for low voltage ($V_{DS} < 250V$) and low current ($I_{DS} < 150A$) applications.

International
IR Rectifier



SMD-220 case

Ex: 200V, 70A




TO-247 case

Ex: 200V, 130A

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

70

Insulated Gate Bipolar Transistor (IGBT)

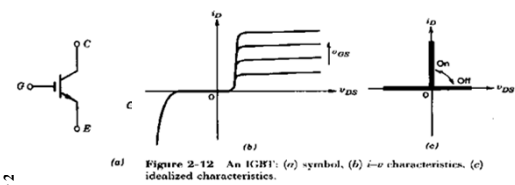

- High input impedance for controls (between gate (G) and emitter (E)) thanks to the use of a MOSFET.
- High voltage devices have low "on" state voltage drops, like a BJT
- High current (high power) switching capabilities;
- Fast switching (typ. < 500ns) -> Moderate switching losses

November 2

press-pack case (high power)

WESTCODE
AIGI LEXIS Company

Ex: 4.5kV, 2.4 kA

101A359

modules case (medium power)

Infineon

Ex: 1.7 kV, 3.6kA

Other cases (low power)

Semix
SEMIKRON innovation+service
Mini Skiiip

Ex: 1200V, 400A
(6 IGBT's)


Ex: 600V, 50A
(6 IGBT's)

Semitop

Ex: 600V, 100A
(6 IGBT's)

71

Gate-Turn-Off (GTO) thyristor

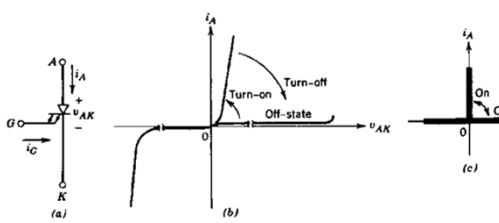

- Turns on and latches as an SCR but requires a large ($I_{AK}/3$) negative gate current to turn-off (elaborated gate control circuit);
- Blocks negative voltages but has low switching speeds;
- Still used in ultra high power applications.

Figure 2-10 A GTO: (a) symbol, (b) $i-v$ characteristics, (c) idealized characteristics.

press-pack case (ultra high power)

WESTCODE
AIGI LEXIS Company

Ex: 4.5kV, 4 kA

101A346

Fk. Boreddy - Power Converters - CAS - GRANADA - 5th November 2012

72

Comparison of controllable switches


Table 2-1 Relative Properties of Controllable Switches

		<i>Effective(*) switching</i>		
		<i>Device</i>	<i>Power Capability</i>	<i>Switching Speed</i>
obsolete	→	BJT/MD	Medium	Medium
Most popular (low power)	→	MOSFET	Low (< ~ 15 kW)	Fast (~0.1μs)
		GTO	High (< ~ 10 MW)	Slow (~ 5μs)
Most popular (high power)	→	IGBT	Medium (< ~ 3 MW)	Medium (~0.5μs)

(*)
Voltage de-rating: 1.6; Current de-rating: ~1.3
(i.e., power de-rating: 1.6 x 1.3 ≈ 2)

Fk. Bordry - Power Converters - CAS - GRANADA - 5th November 2012

73

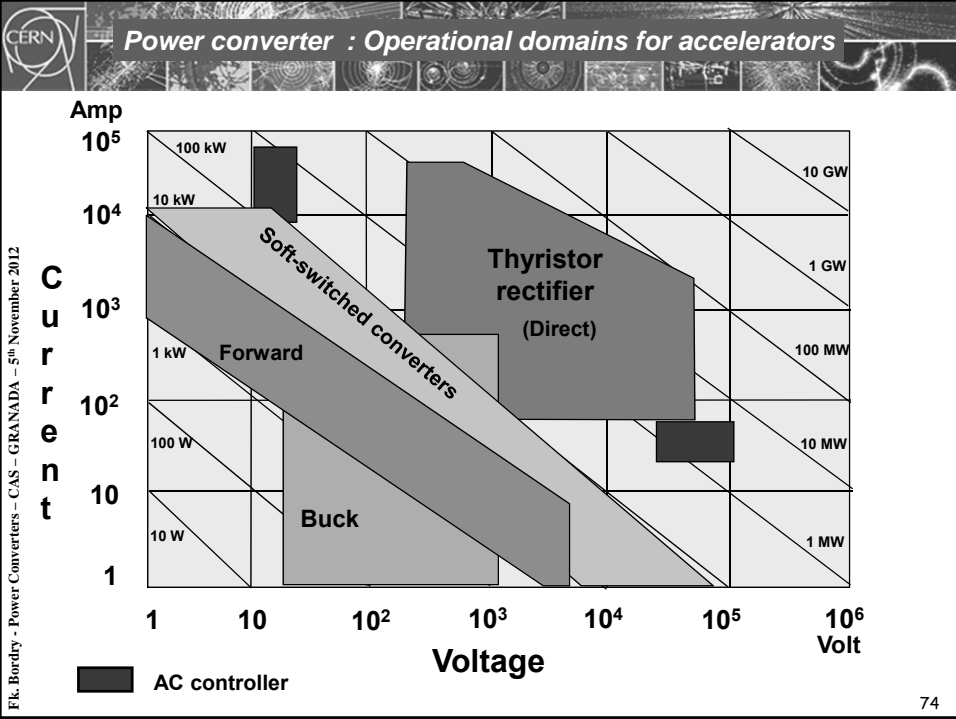



Interdisciplinary nature of power converters

