

HIGH POWER, WIDEBAND, SOLID-STATE AMPLIFIERS FOR LEIR AND J-PARC RF SYSTEMS.



Summary



- Overview
- Basic building block
- Hybrid coupler/splitter
- Delay compensated transformers
- An ultra wideband hybrid
- Directional coupler
- 1 kW amplifier
- Use at CERN
- Use at J-PARK

CERN LEIR machine and J-PARC RCS and Main Ring
required driver amplifiers for their grid tubes power stages:

- ✓ Frequency range : 0.5 – 6 MHz
- ✓ Power 1kW, 4kW and 9kW
- ✓ Duty cycle 50% to 100%
- ✓ High reliability
- ✓ Maintenance ease

Specs well suited for a solid-state modular solution!

- Since 1993 the CERN PSB accelerating cavities use solid-state drivers built around MRF151G RF mosfets.
- The operation experience (16 units) is very good as no amplifier failure happened in the past (except in case of tetrode ceramic breakdown!)
- The units are installed in a radioactive environment and the integrated dose over the last 14 years is $>10\text{k}$ gray.
- No performance degradation has been measured in the operational units.

This unit were the starting point of the new design!

- Class AB for good efficiency and linearity.
- Ability of operating on all load conditions.
- No circulators available for this frequency range so
 - ✓ Full reflected power must be dissipated on the active device.
 - ✓ Load mismatch directly affects the mosfet drain load.



- Single push-pull stage built around an over dimensioned MRF151G double mosfet.
- Device operated at 35V instead of nominal 50V
- Device operated at ~140W instead of nominal 300W

Similar or equivalent devices :

- ✓ D5029UK from Semelab
- ✓ BLF278 from Philips
- ✓ SD2932 from ST
- ✓ SR706 from Polyfet



- At high power, in class B, conduction angle is close to 180 degrees.
- One device provides the full power during half cycle.
- For 140W and 35V supply voltage the drain load and current are then:


$$R_D = \frac{(V_{DS} - V_{DSS(ON)})^2}{2 \cdot P} = \frac{(35 - 5)^2}{2 \cdot 140} \approx 3.125 \Omega$$

$$I_D = \frac{(V_{DS} - V_{DSS(ON)})^2}{R_D} \approx 10 A$$

- Matching achieved with a standard transformer made of coaxial cables wound on a ferrite core.
- When driven from one drain connection with a 50Ω load:


$$n = \frac{V_{OUT}}{V_D} = 4$$
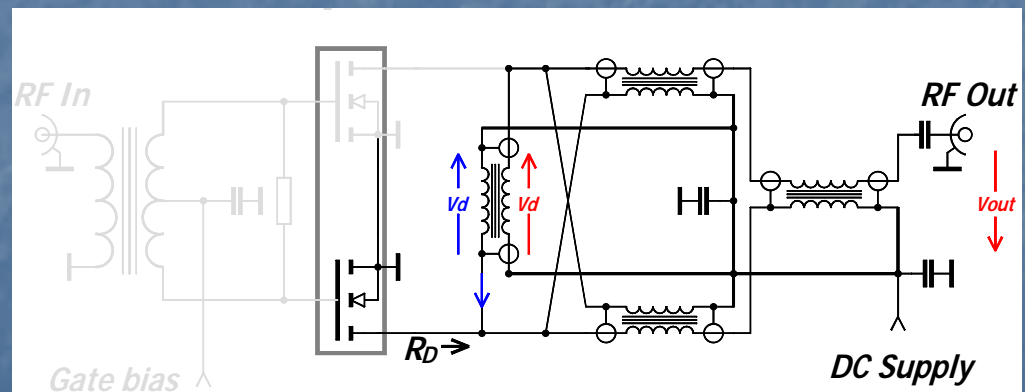
$$R_D = \frac{50 \Omega}{n^2} = 3.125 \Omega$$



Basic building block

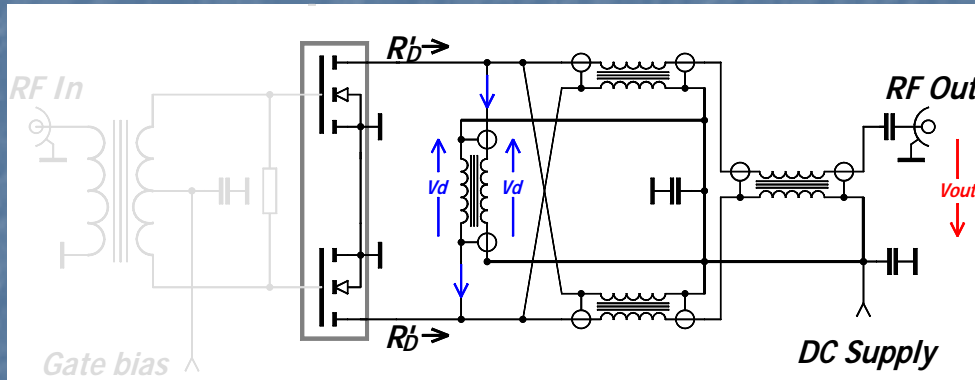- At low power, in class A, both devices provide power during the whole cycle and are driven in counter phase.



- In this case each drain is loaded by:


$$R'_D = \frac{50\Omega}{\left(\frac{n}{2}\right)^2} = 2 \cdot R_D = 6.25\Omega$$

- To equalize the mid-band gain at low and high power (class A and class B)

$$G_{VA} = g_{mA} \cdot R'_D \cdot n = g_{mA} \cdot 2 \cdot R_D \cdot n$$

$$G_{VB} = g_{mB} \cdot R_D \cdot n$$

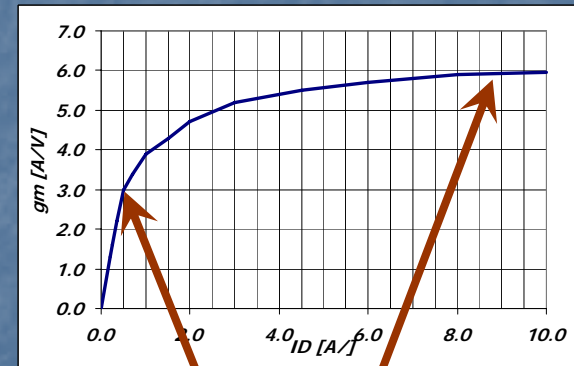
$$\frac{G_{VA}}{G_{VB}} = \frac{g_{mA} \cdot 2}{g_{mB}} = 1$$



$$g_{mA} = \frac{g_{mB}}{2}$$

- Assuming the transformer to be ideal and the mosfet output impedance purely capacitive the high frequency cutoff is:
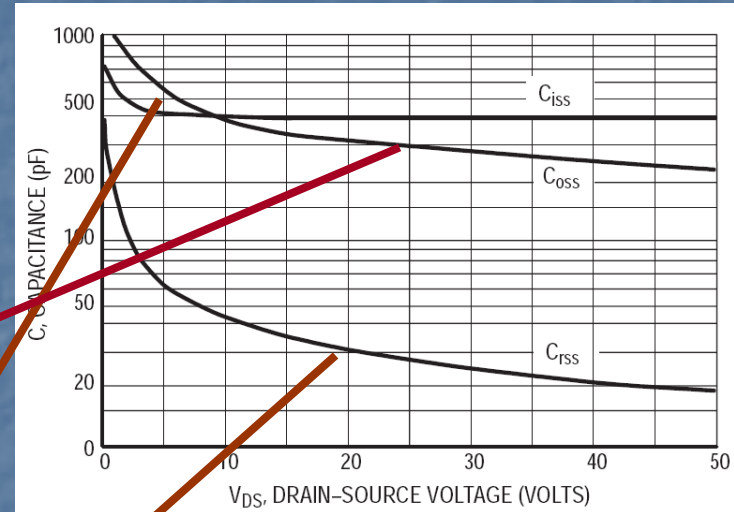
$$f_c = \frac{1}{2 \cdot \pi \cdot R'_D \cdot C_{OSS}} \approx 85 \text{ MHz}$$




- The gate capacitance is:

$$C_G \approx C_{ISS} + C_{RSS} \cdot (1 + g_{mB} \cdot R_D) \approx 400 \text{ pF} + 30 \text{ pF} \cdot (1 + 6 \cdot 3.125) \approx 990 \text{ pF}$$

- The input transformer is a balun with 1 to 9 impedance ratio (50Ω to 5.55Ω)
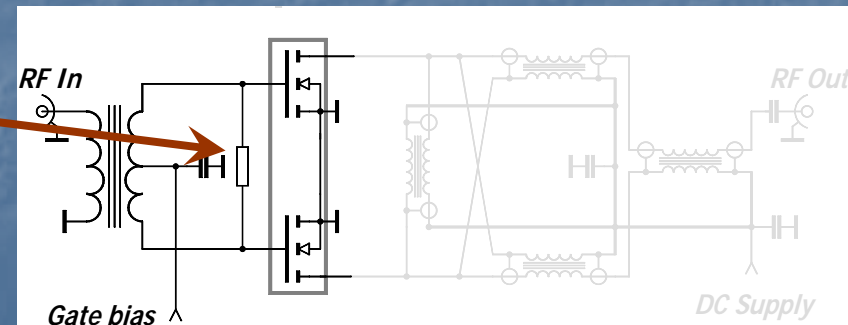
$$f_c = \frac{1}{2 \cdot \pi \cdot \frac{R_G}{4} \cdot C_G} \approx 115 \text{ MHz}$$




- The output transformer uses 1 tore type 4W620 (Wuerth)
 - ✓ $O_d=26\text{mm}$, $I_d=13\text{mm}$, $H=28.5\text{mm}$
 - ✓ $S=1.85 \cdot 10^{-4} \text{ m}^2$
 - ✓ $Al \sim 2.8\mu\text{H}/N^2$
- $N=4$ turns on the balun and $N=2$ turns for the transformer gives:
 - ✓ $B_{\text{MAX}}=26.5\text{mT}$ @ 0.5MHz and 140W
 - ✓ $f_L \sim 90\text{KHz}$


***Ferrite saturation typically $\sim 200\text{mT}$.
CW operation normally possible with $B \sim 20\text{-}30\text{mT}$***

- The input transformer uses 4 tores type 3E5 (Ferroxcube)
 - ✓ $Al \sim 5\mu\text{H}/N^2$
- $N=3$ turn on the high impedance side gives:
 - ✓ $f_L \sim 45\text{KHz}$

Basic building block


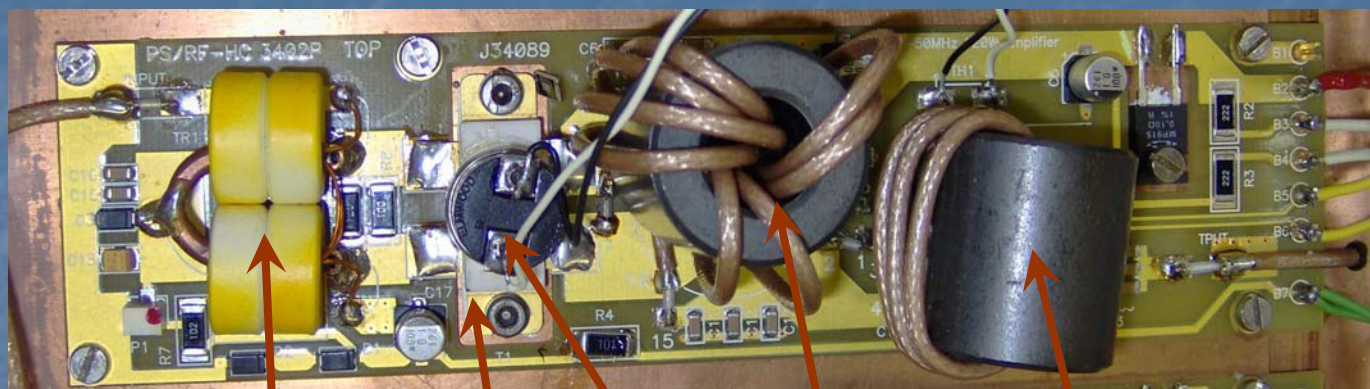


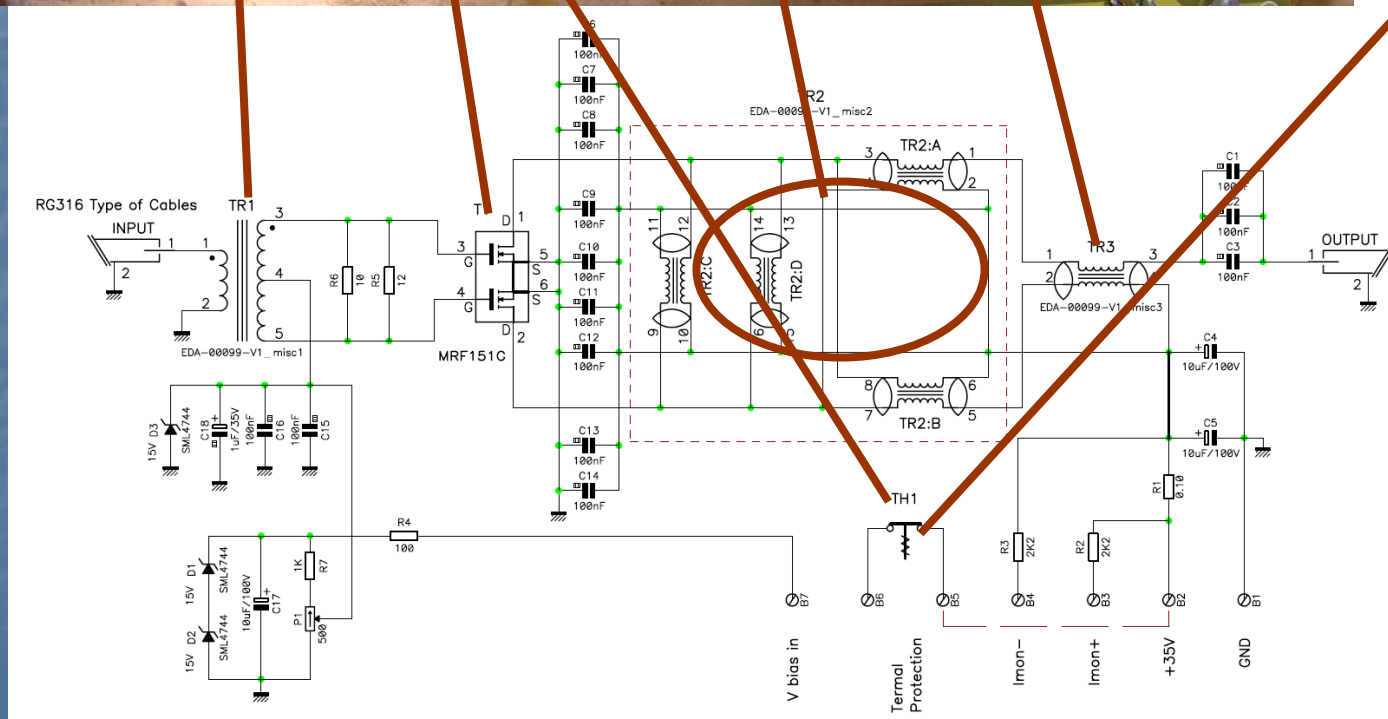- Thermal protection simply insured by thermal switch glued on the mosfet case.



Hybrid coupler/splitter

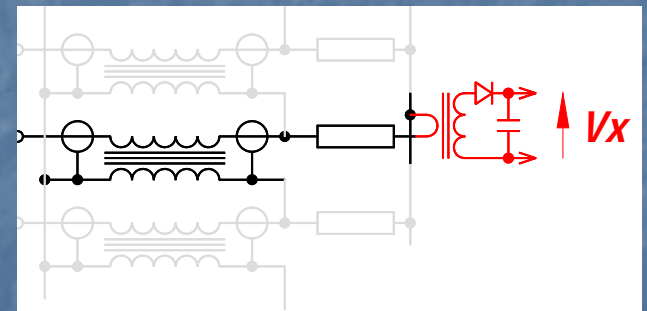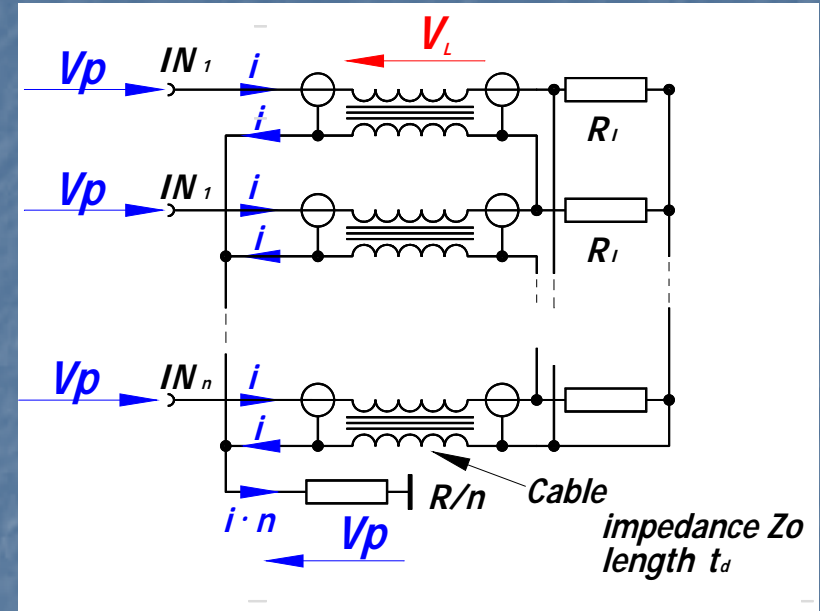- Classic hybrid combiner/splitter circuit
 - n-ways device
 - R_I provides isolation between ports.
 - If all ports driven with identical signals
 - ✓ no current through R_I .
 - ✓ $V_L \sim V_{IN} \sin(\omega t_d)$
 - Frequency response limited
 - ✓ notch at $f_n = 1/4t_d$
 - Simple detector provides indication of unbalanced drive (or broken module).
- Very useful for servicing!***



H. Granberg, *Broadband transformers and power combining techniques for RF*, Motorola AN-749

- In ferrite loaded hybrids and transformers $B_{MAX} < 20-30\text{mT}$ for CW operation.

$$B = \frac{V}{\omega \cdot S \cdot n}$$

Diagram illustrating the equation $B = \frac{V}{\omega \cdot S \cdot n}$ with arrows pointing to the variables:

- V : Voltage
- ω : Angular frequency
- S : Ferrite cross section
- n : Number of turns


- When combined power get high...
- When extending the low frequency response...

... B_{MAX} limited by increasing the number of turns or the ferrite cross section

- This increases the cable length that affects the high frequency response:

first notch placed at $f_n = 1/4t_d$

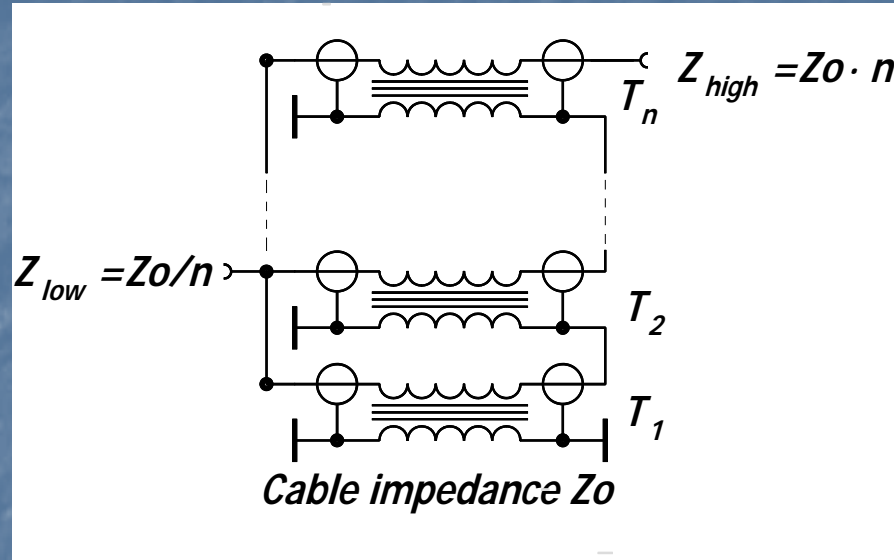... the solution is delay compensated devices!







- Cables paralleled on the low impedance side
- Cables in series on the high impedance side.

In theory no high frequency limit!


An ultra wideband hybrid



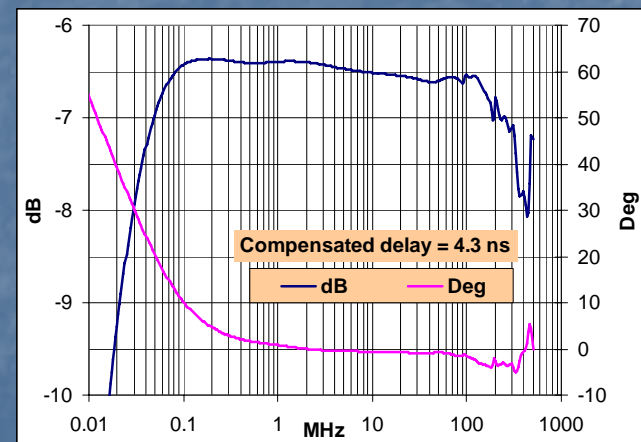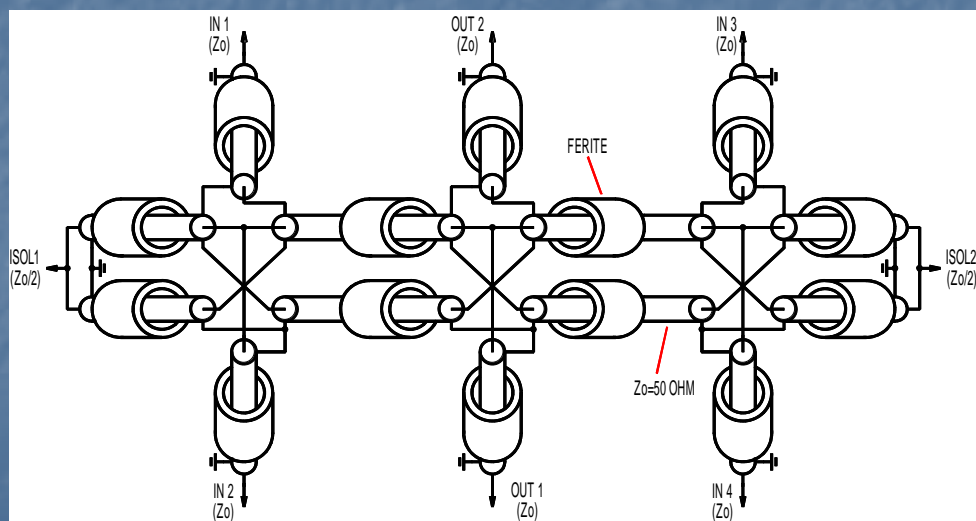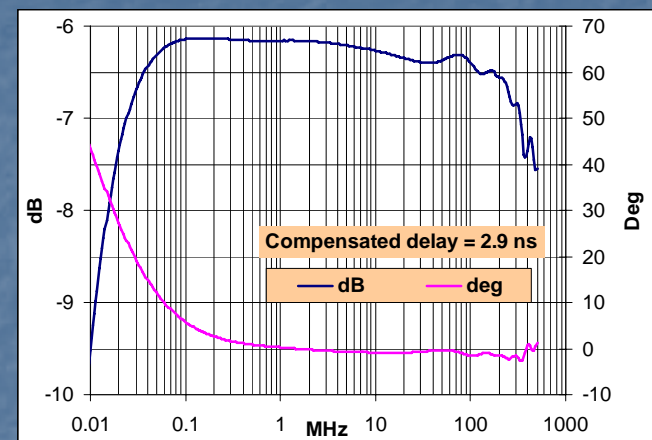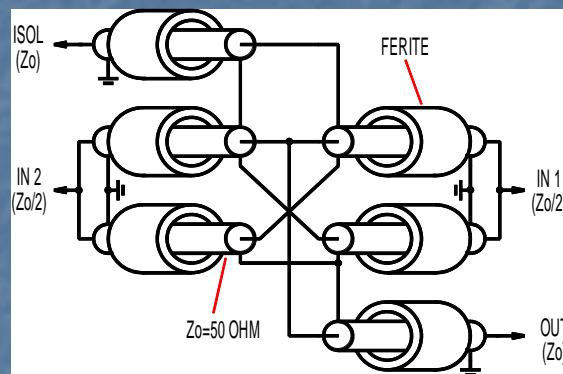Udo Barabas, "On an Ultrabroad-Band Hybrid Tee", IEEE Transactions on microwave theory and techniques, vol.MTT-27, no.1, January 1979




Directional coupler

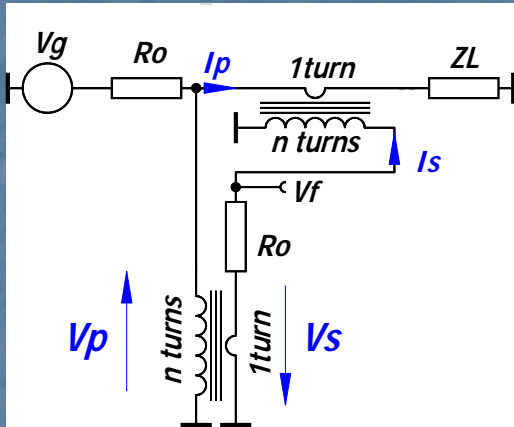

Assuming the impedance of the 1 turn winding $\ll R_o$ and the impedance of the n-turns winding $\gg R_o$ then, for any value of Z_L :

$$V_F \sim -\frac{V_g}{n}$$

simply proportional to the incident wave

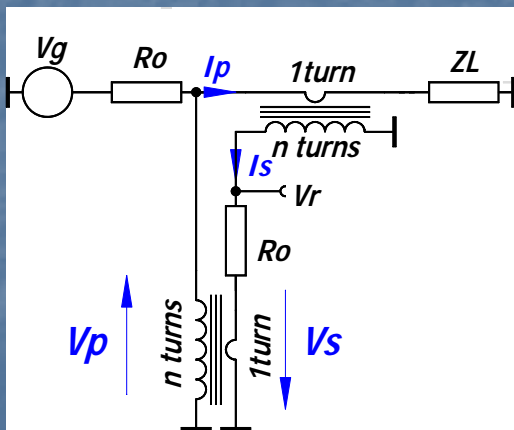


Inverting the current sample direction we get

$$V_R \sim V_F \cdot \left[\frac{Z_L - R_o}{Z_L + R_o} \right] \sim V_F \cdot \rho$$

thus proportional to the reflection coefficient.

1 kW amplifier

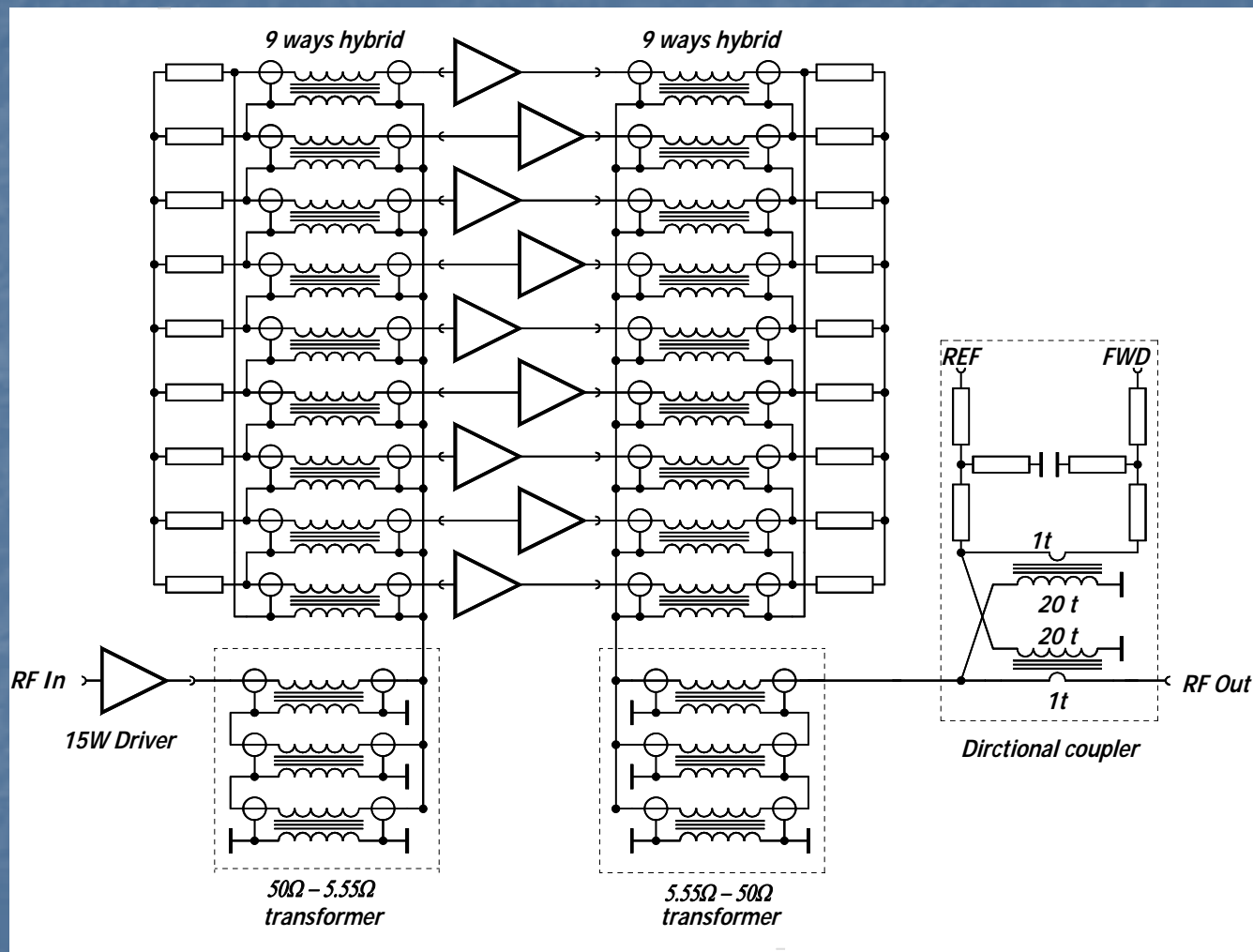


1 kW amplifier

*DC distribution
and filtering*

15W Driver

9 ways splitter


Survey electronics

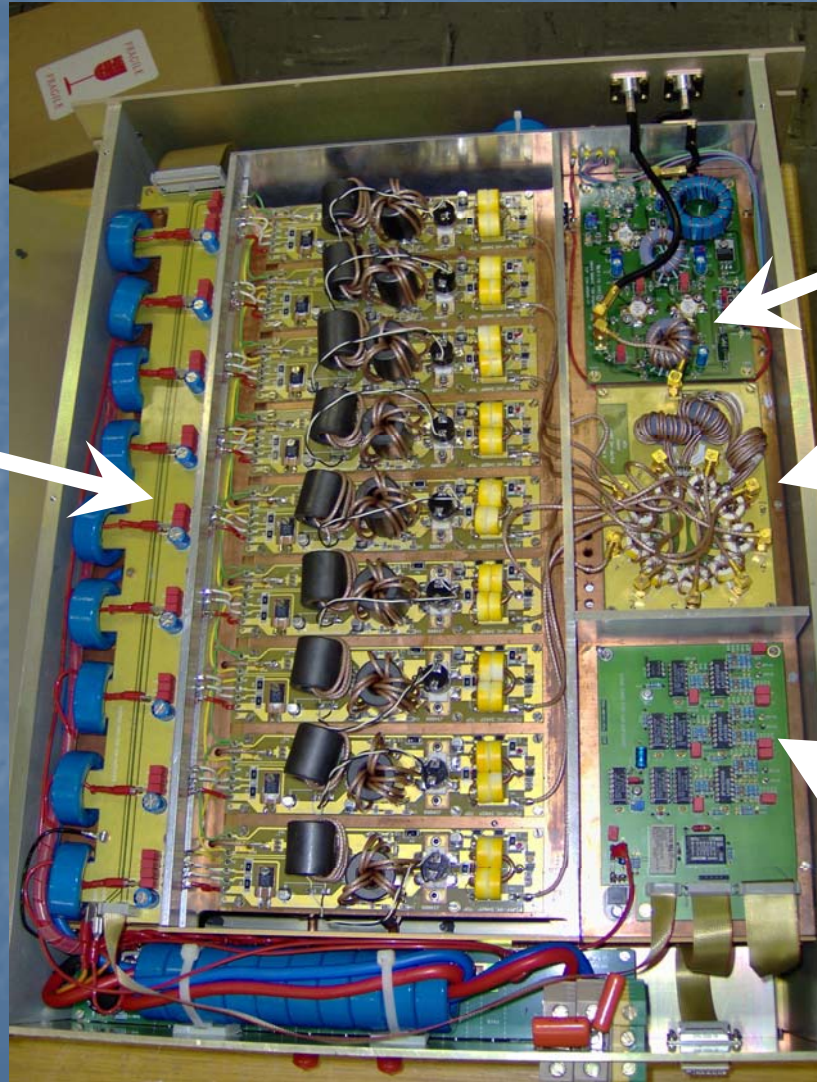

HIGH POWER, WIDEBAND, SOLID-STATE AMPLIFIERS FOR LEIR AND J-PARC RF SYSTEMS

M. Paoluzzi – 28th March 2008


1 kW amplifier

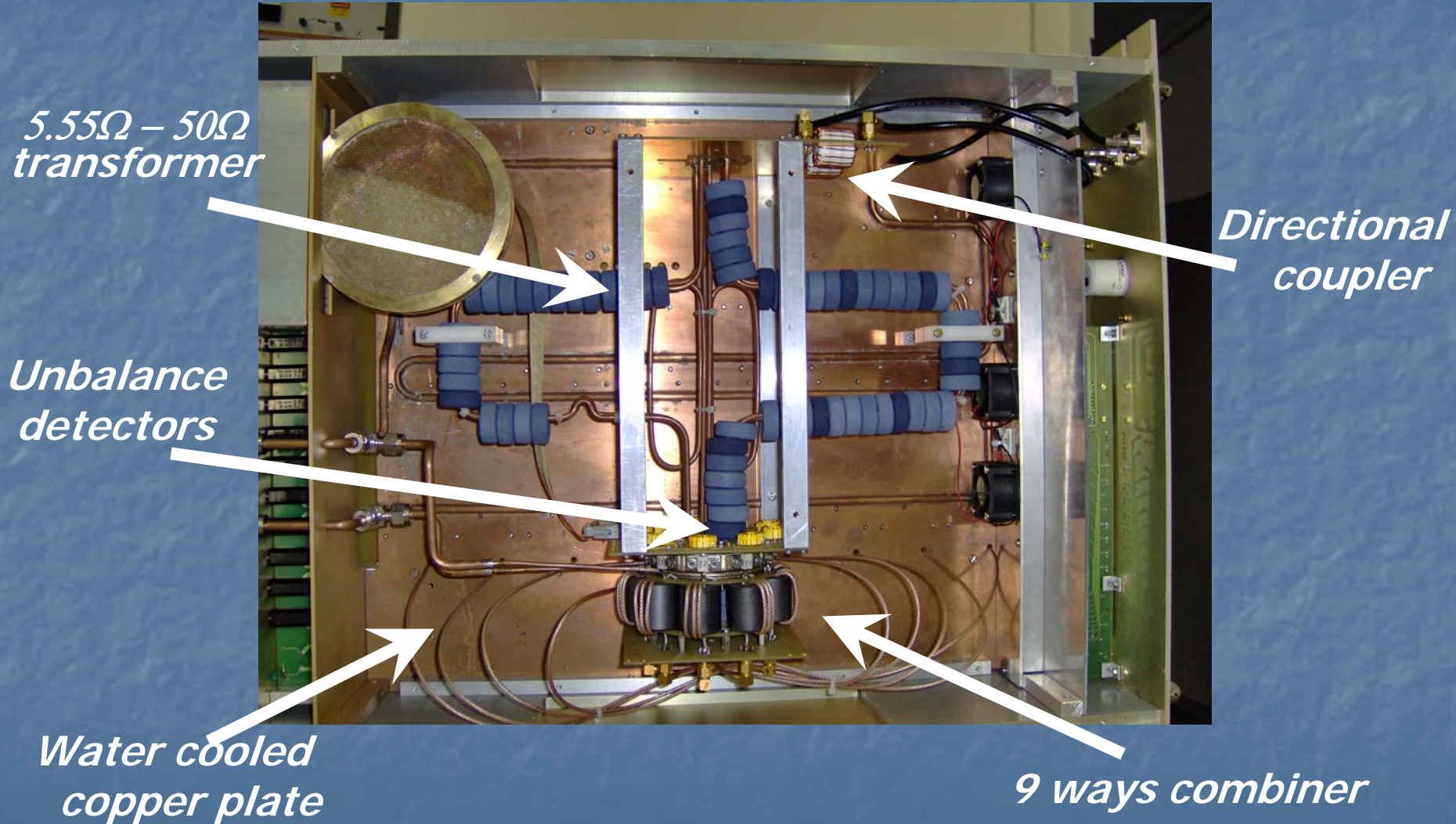


HIGH POWER, WIDEBAND, SOLID-STATE AMPLIFIERS FOR LEIR AND J-PARC RF SYSTEMS

M. Paoluzzi – 28th March 2008


1 kW amplifier

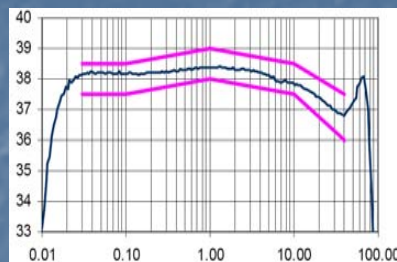


15W driver

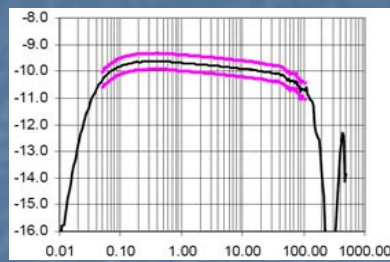

9 ways splitter

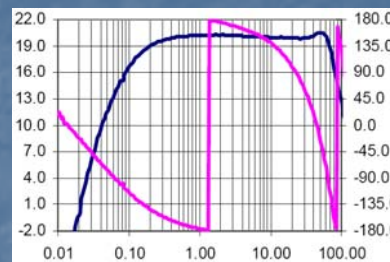


140W module

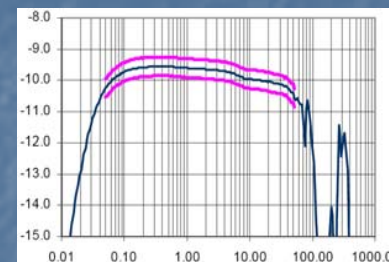

*9 ways combiner
(in splitting mode)*

-3dB Bandwidth	0.2 - 10 MHz
-1 dB Bandwidth	0.5 – 5 MHz
Gain	58 dB \pm 1.5 dB
Output power at 1 dB compression	> 1 kW
Harmonic distortion	< -15 dBc @ Pout 1 kW < -18 dBc @ Pout 500 W
Gain linearity	\pm 1 dB
Input impedance	50 Ω VSWR 1.1:1 max
Load impedance	50 Ω , no damage when operated with any load.
Protections	Overtemperature Overcurrent
Monitoring	RF Drive input (-26 dB) Output Forward Power (-46dB) Output Reflected Power (-46dB) Driver and final stages DC current 140W modules power balance
Power requirements	35 V 100 A DC
Cooling	Water

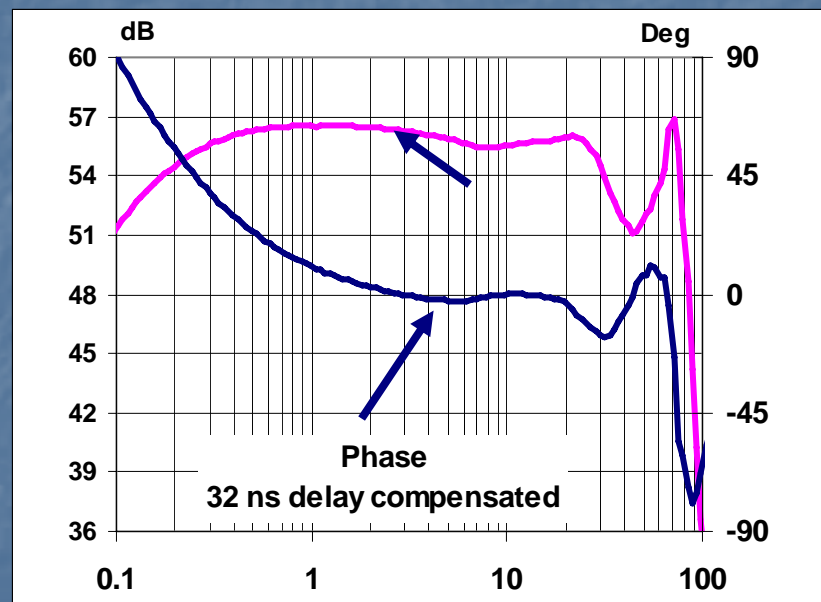

1 kW amplifier

- Six 1kW units have been produced for CERN use in LEIR machine



- 4 in use without troubles for 2 years (2 spares)

HIGH POWER, WIDEBAND, SOLID-STATE AMPLIFIERS FOR LEIR AND J-PARC RF SYSTEMS

M. Paoluzzi – 28th March 2008

- For J-PARC more than 100 1kW units have been manufactured.
- Units combined to get 4 kW and 8 kW.
- For 8 kW, nine units have been combined to achieve the required power also in case of failure of 1 unit.
- In 2007, 70 units have been operated for 3 months without troubles.
- This means a total of ~1000 MRF151G have been installed and tested.
- More than 600 MRF151G where operated.
- No failure occurred until now.
- Additional production of 40 more 1kW units planned.



Thanks to Dr. Chihiro Ohmori for the information and pictures!



Main Ring - 4 kW assemblies



***Rapid Cycling Synchrotron
8 kW assemblies***



1 kW unit #94