

# 65nm CMOS activities at LAL/LAPP

**Abdenour Lounis,  
LAL Orsay**

**Gisèle Martin, Damien Thienpont, Jeanne Tongbong  
OMEGA**

**Renaud Gaglione, Richard Hermel  
LAPP Annecy**

**Presented by Jean-Francois Genat  
LPNHE Paris**

**2d AIDA Annual Meeting**

April 10th 2013 LNF Frascati

# LAL/LAPP 65 nm projects

## IP blocks for WP3.3

LAL     -> Pixel (LAL/LPNHE)  
         -> OTA (Analog low noise Front-end)  
         -> PLLs

LAPP    -> LAL Omegapix  
         -> DAC 12b 80 MHz   -> 14b  
         -> Clusters centroid evaluation


# Pixels readout

Two options:


- 1 In-pixel circular buffer
- 2 Use in-pixel storage (FIFOs) instead of circular buffer to reduce power and Silicon area
  - Hit times are recorded for the L1 latency
  - At L1, hit times in FIFOs are compared to the current time and selected for L2 if **hit time** matches **L1 time**

# Pixels readout: on-pixel Circular buffer vs on-pixel FIFOs

## Circular buffer scheme

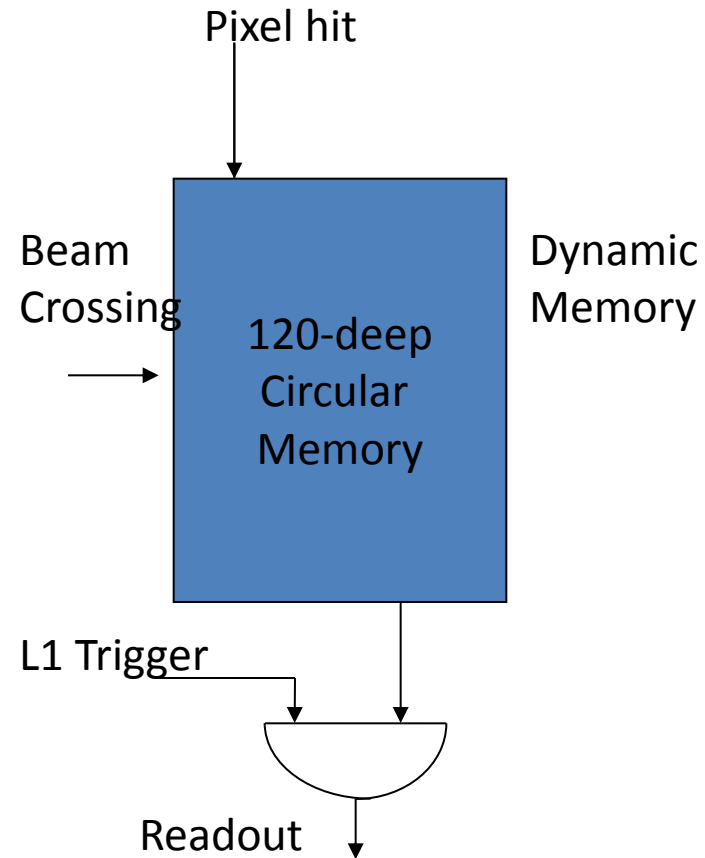


## Selective readout scheme

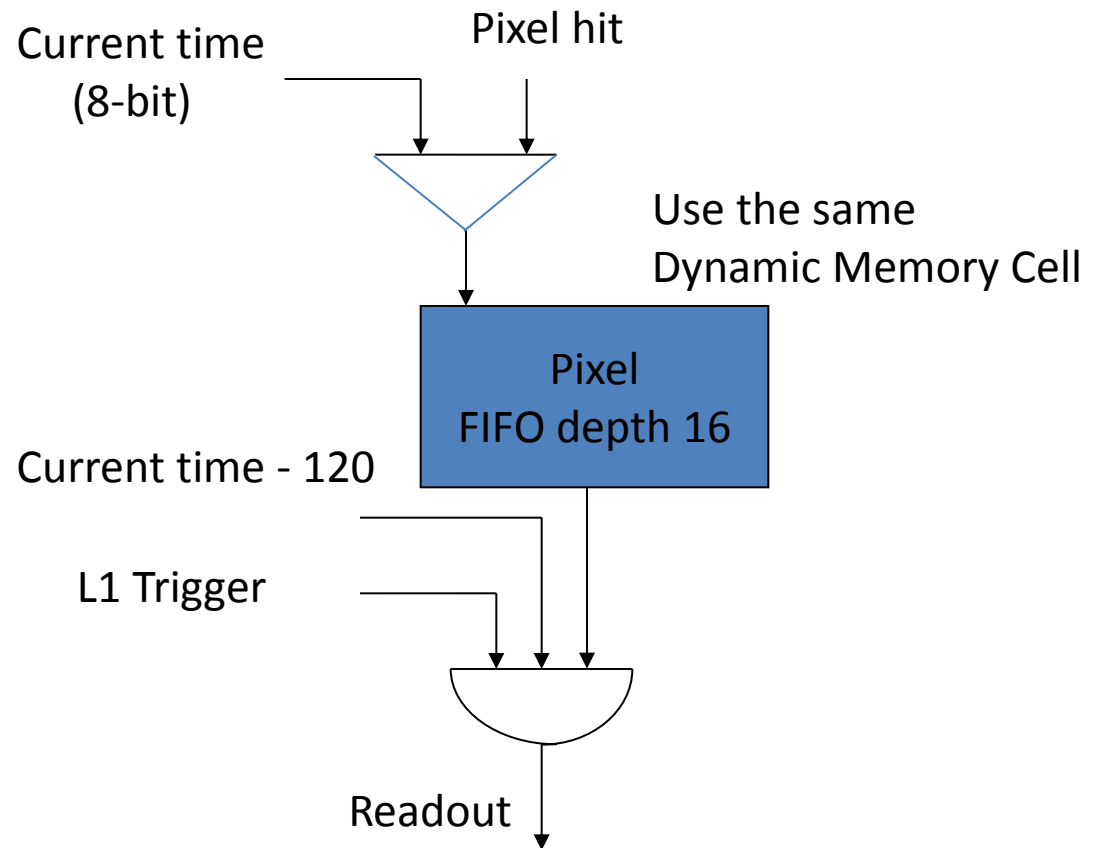

**Selective readout scheme: Save silicon area and power at the pixel level**
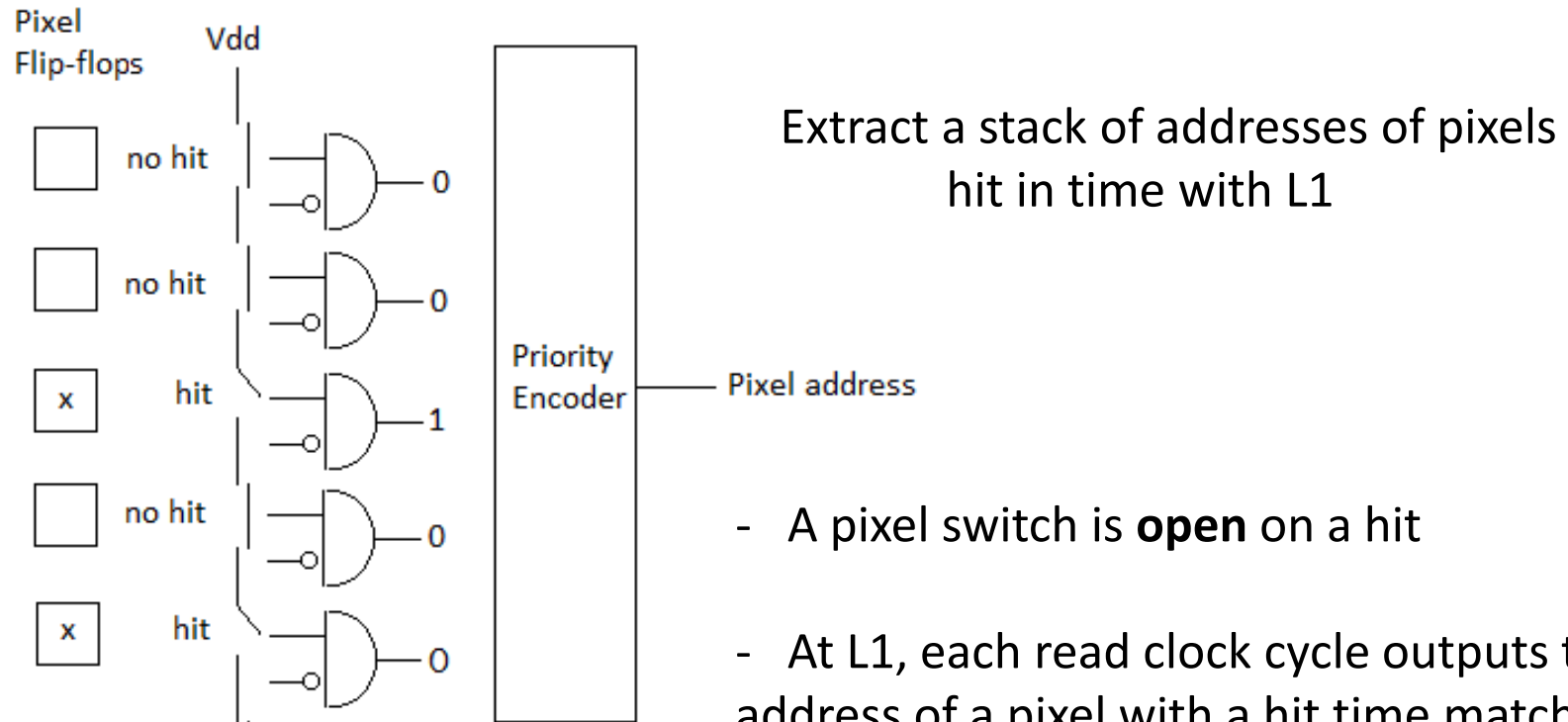
# Timing based pixels sparse scan readout




- A pixel switch is **open** on a hit
- At L1, each read clock cycle outputs the address of a pixel with a hit time matching this L1, from column top to bottom

Scan all columns in parallel to end of column FIFOs

- The read pixel switch is **closed** after read
- The next hit pixel (switch open) is read


# Building block

 

- VHDL model
- Cells library
- I/O locations file (x,y in microns)
- Dimensions (FIFO depth 16)

OK  
65nm TSMC  
text file  
35 x 70  $\mu\text{m}^2$


# Layout in TSMC 65nm

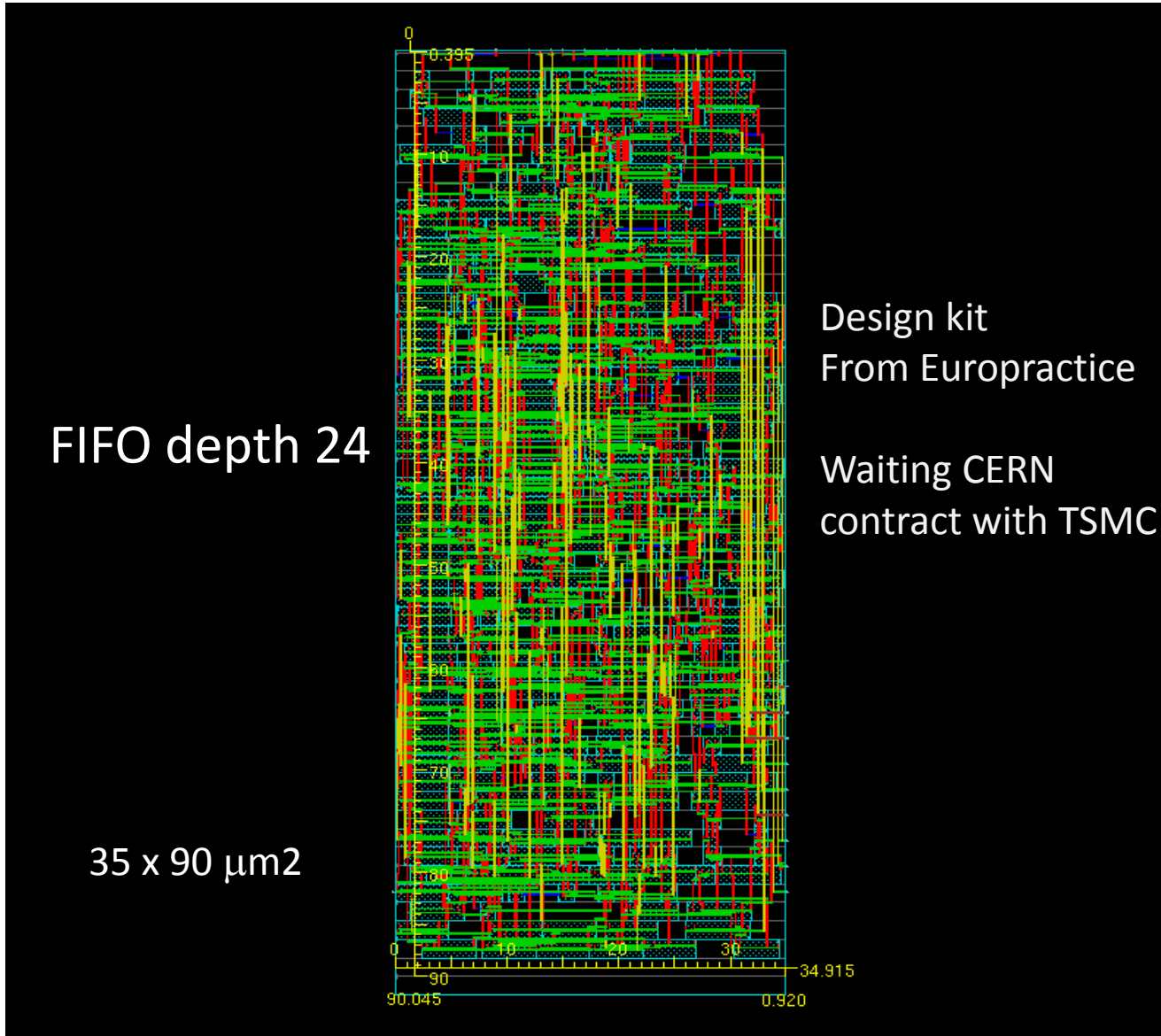

# PLLs (clock recovery)

Used as frequency synthesizers

Charge pump PLL (CP-PLL)

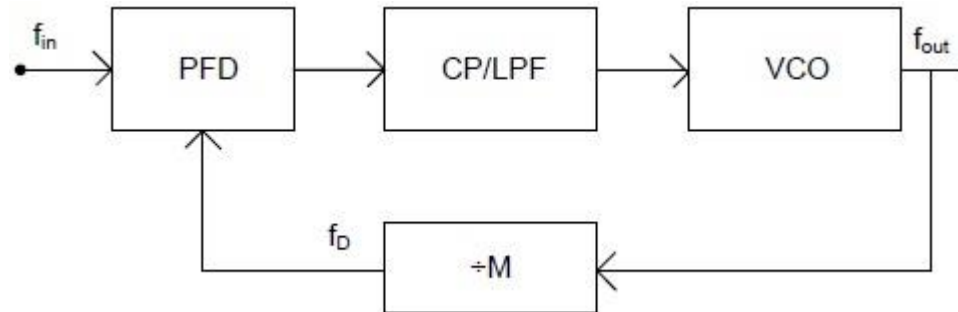

CP –PLL for frequency multiplication

Low power , low jitter , fully integrated


Typical Input frequency : 40 MHz

Output frequency range: 80 MHz-320 MHz

Slide from **Jeanne Tongbong (LAL Orsay)**




# PLLs (clock recovery)

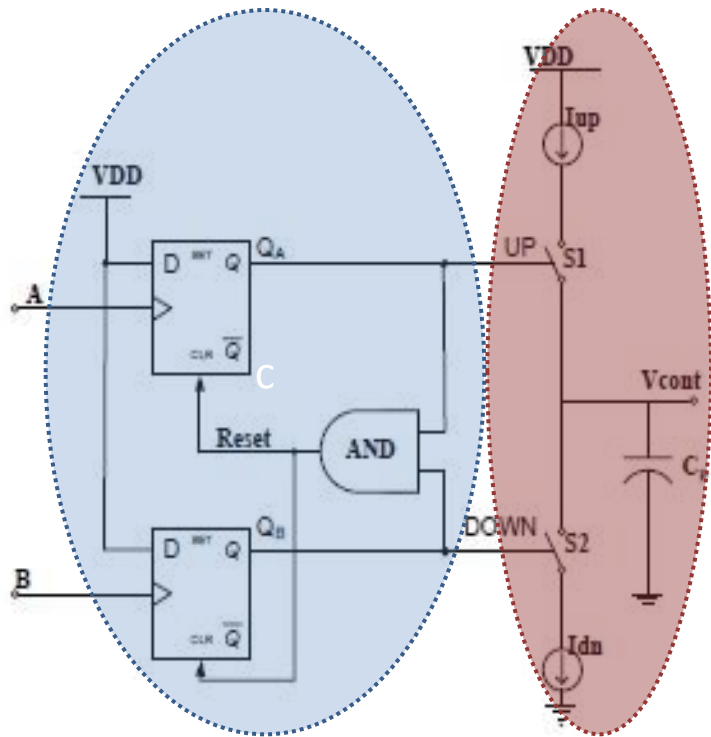

Phase Frequency  
Detector (PFD)

Charge Pump (CP) /  
Loop Filter (LP)

PFD-CP-LP basic implementation

 

Ring oscillator

**Status: OMEGA develops  
PLL block in 350nm as a  
debugging block**

**Simulations going on in 65nm  
Awaiting CERN design kit**

Slide from **Jeanne Tongbong (OMEGA)**

# LAPP involvement

- LAPP is strongly involved in the HL-LHC tracker upgrade (services, ALPINE design, cooling) and aims to be involved in tracker-related micro-electronics developments.
- support to OMEGA ;  
support to CPPM and FEi5 design.

→ LAPP team works on 65nm building blocks for future trackers which may be included in tracker readout chip.

Slide from **Renaud Gaglione LAPP**

# Developments


- **Present:** design of a capacitive 12 bits DAC for CPPM 12 bits SAR GADC. 1V, 1MHz, ~mW
- **Soon:** specs and design of comparator for CPPM SAR GADC and for LAL Wilkinson ADC;
- **Considered:** JTAG block.

Slide from **Renaud Gaglione LAPP**


The end...
 
# 65 nm OMEGAPIX2

- A new OMEGAPIX chip in 65 nm techno as an alternative to the 3D chip
  - Same pixel form factor: 35x200  $\mu\text{m}$
  - New analog front-end (LAL), new digital pixel (LPNHE)
  - TSMC 65 nm techno
    - 3x1z1u metal stack (RF, CRN65LP), 6 metal layers + RDL
    - tcbn65lp standard cells library
  - In waiting for the common PDK provided by CERN



# Sensor + Readout chip in 65nm

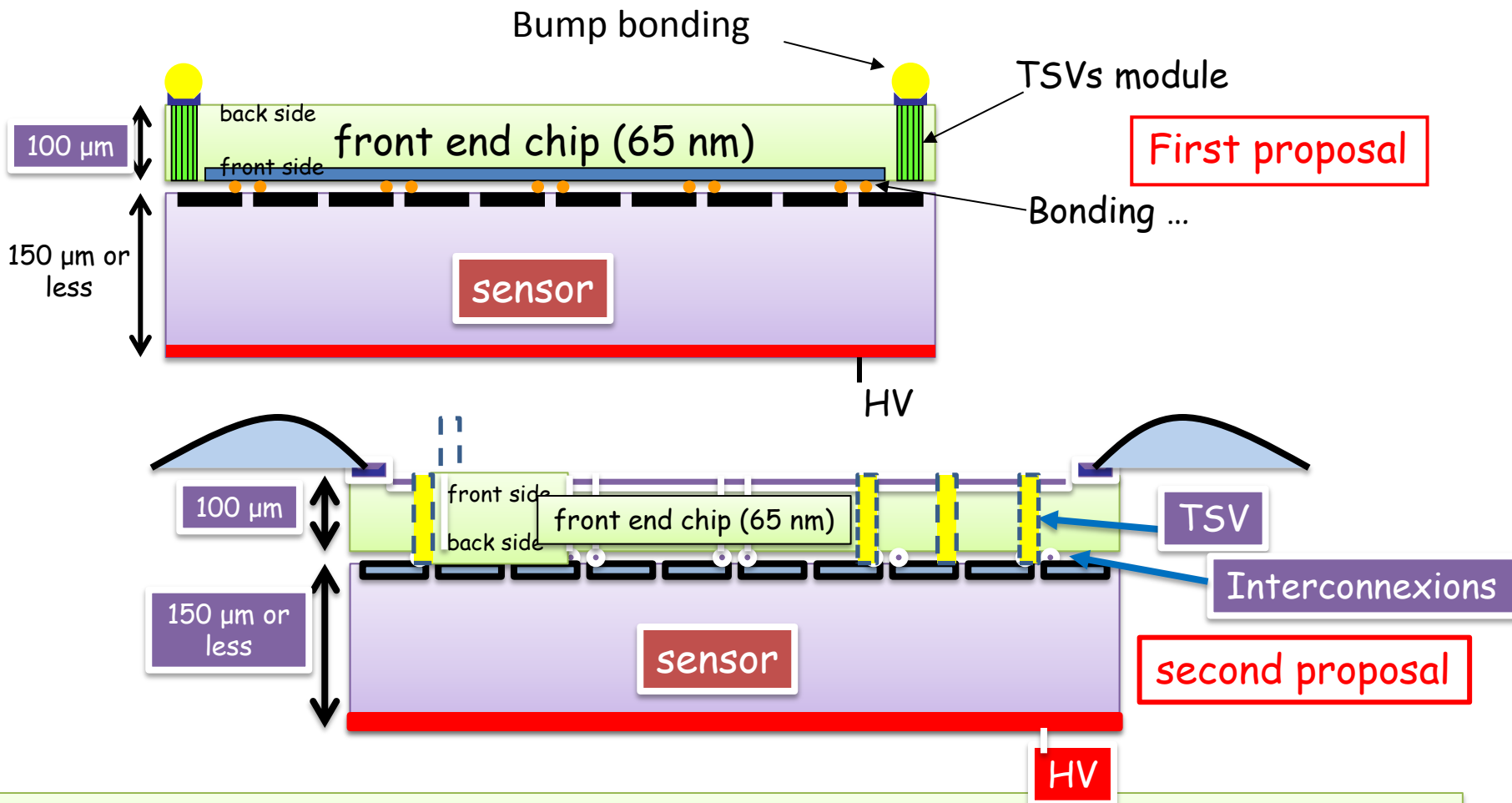

Via Last AIDA project: LAL + LPNHE+ LAPP