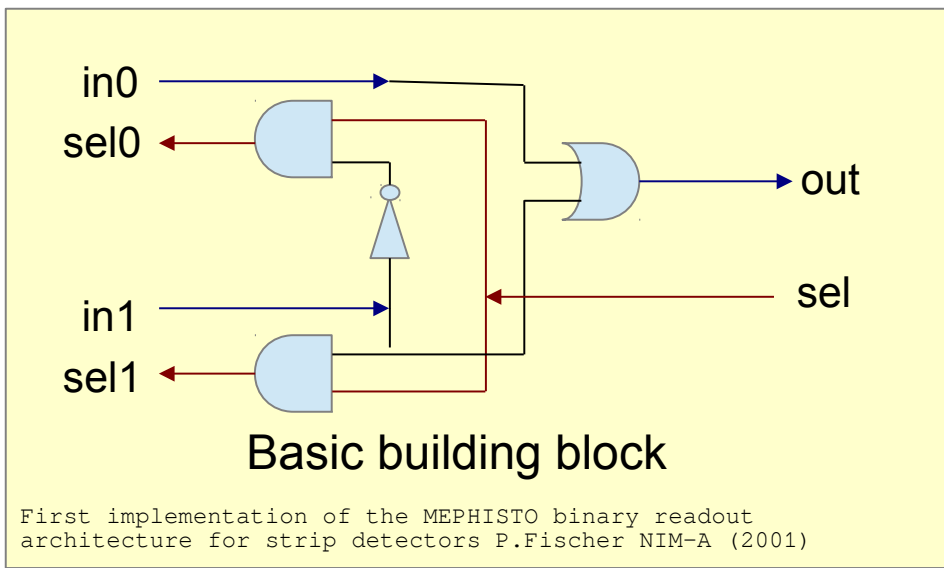


# 65 nm IP block: SET tolerant logic

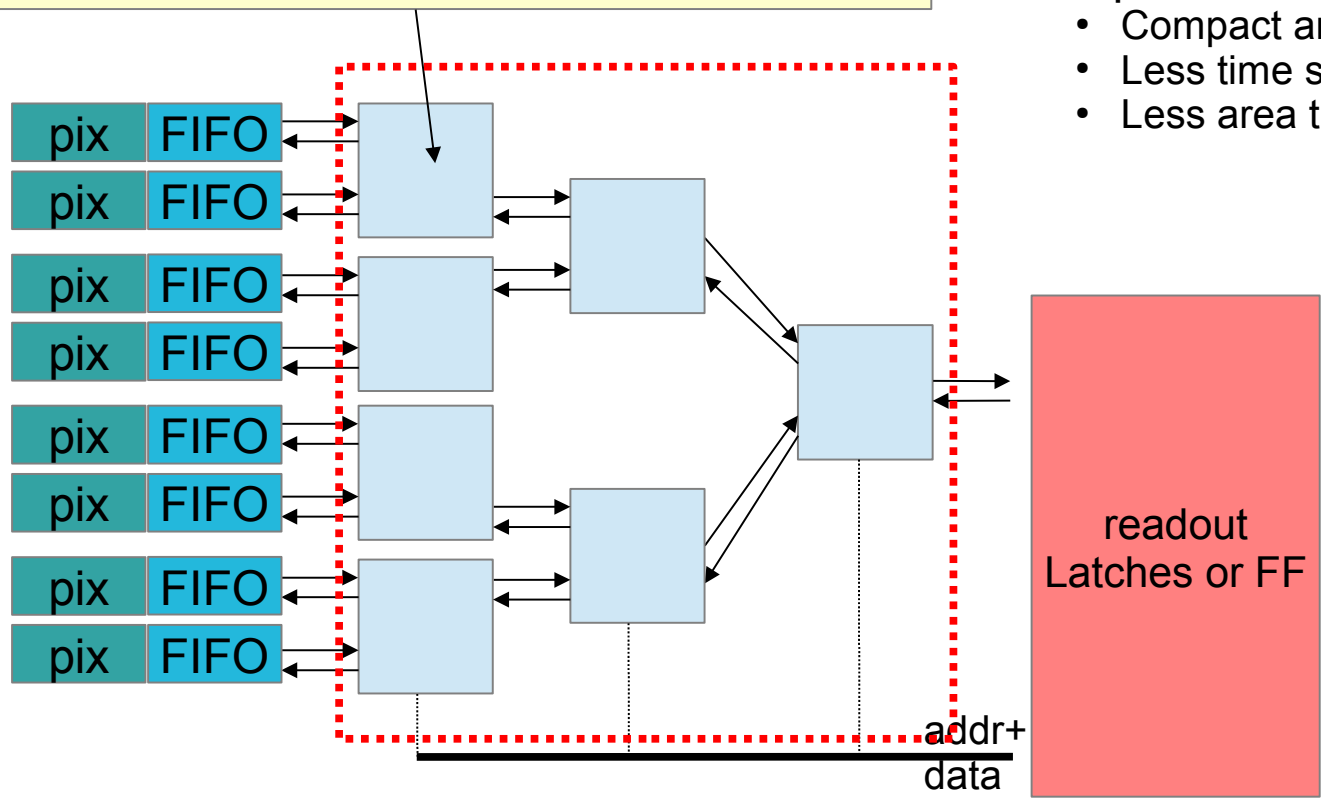
F. Crescioli, JF Genat – LPNHE Paris, IN2P3 CNRS  
A. Stabile, V. Liberali – INFN Milano





Build a library of logic blocks specialized for **SET-tolerant** combinatorial networks (ie. readout applications)


- Std cell kit compatible
  - Same size, same rules, abutable to other std cells in the kit
  - Usable by automatic place&route programs (ie. Cadence Encounter)
- Optimized
  - Compact and regular designs
  - Less time spent on routing
  - Less area than triplication with standard cells



Pixel address and additional data can be multiplexed using the sel signal


 
# Standard CMOS vs DCVSPG

DCVSPG → Differential Cascode Voltage Switch with the Pass Gate logic tree



- Logic function is implemented with **two complementary pass-gate trees** using nMOS (for complex logic they might also share transistors)
- Circuit **load is done by cross-coupled pMOS**
- **2-rail encoding**: provides always output and negated-output, needs always both inputs and negated-inputs
- Typically provides better performances wrt standard CMOS logic (**power, delay**)
- Well suited for radhard applications: **SET are always non-logic states** and propagate less in the combinatorial logic (Hatano, H., "Single Event Effects on Static and Clocked Cascade Voltage Switch Logic (CVSL) Circuits," Nuclear Science, IEEE Transactions on , vol.56, no.4, pp.1987,1991, Aug. 2009)
- **It's more difficult to handle with commercial synthesis and P&R tools**

# Standard DCVSPG → pMOS DCVSPG

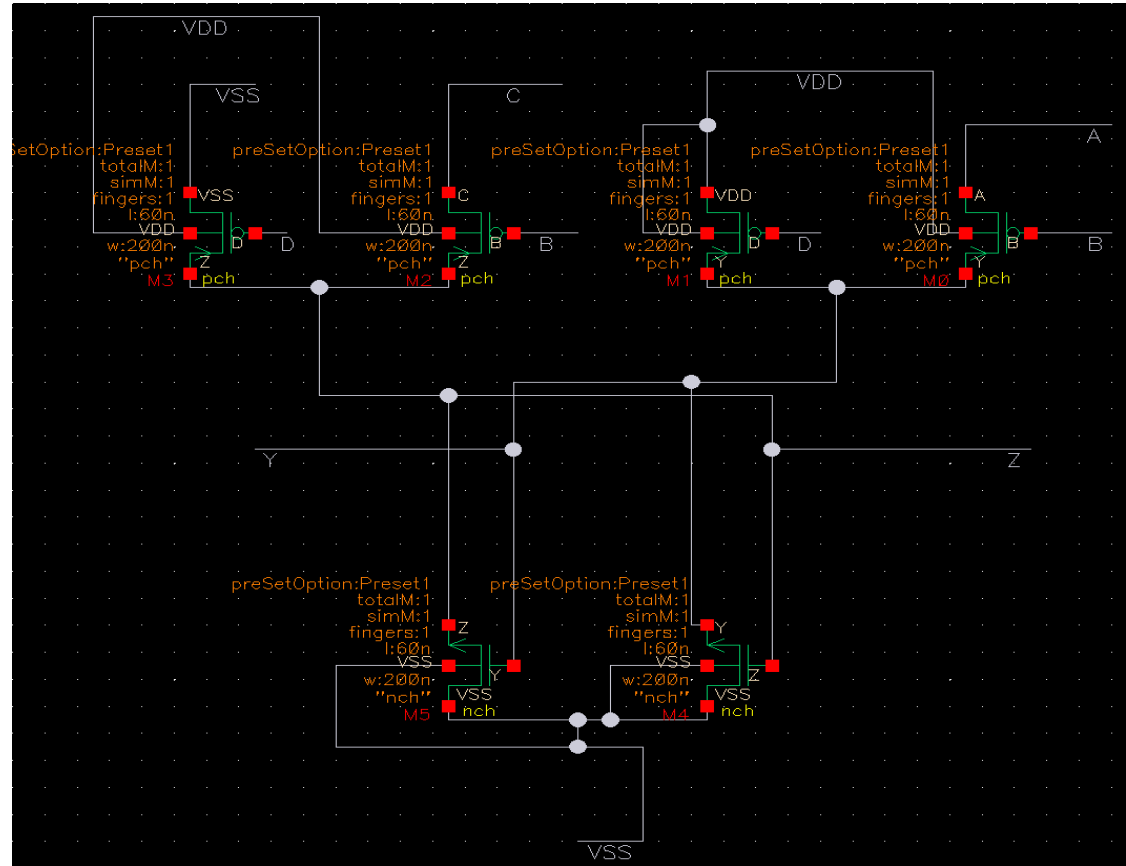 

- Pass Gate logic tree done with pMOS, cross-coupled load done with nMOS
- In radhard applications pMOS shows less increase of leakage current with dose
- Cell area is bigger and it's a bit more difficult to route

## Guard rings?


Protect from latch-up, But not really useful at 1.2-1V. Useful at higher Voltage.

## ELT for nMOS?

Not possible with current 65 nm rules

 
# 2 INPUT AND-like logic layout

About 3x the equivalent std cell from the kit. Without guard rings would be smaller


 
# 2 INPUT XOR-like logic layout


About 2x the equivalent std cell from the kit. Without guard rings would be smaller



~ 4  $\mu\text{m}$

# 2 INPUT AND-like timing

Transient Response

 

# Synthesis and P&R issues

- Software tools are **not very good** (yet) with differential/2-rail logic
- A possible flow to overcome software limitations is
  - Develop a 'fake' non-differential library with AND/NAND/OR/NOR/BUF/INV/LATCH/FF/etc
  - Convert with a script the netlist to the 'real' library with 2-rail inputs/outputs connected
    - Write a custom script is not difficult, however many **programs** to do that exists in the **async logic community**



# Readout tree synthesis test



Priority encoder + address generator + mux tree (8-bit): 1394 AND-like cells

Synthesis done with RTL Compiler + awk/sed/python scripts to add differential wires


# Status & conclusions


- Dual cascode switch logic with pass gate is an interesting candidate to build **SET-tolerant logic**
  - Few cells make a complete library → easier to maintain
- Schematics for AND-like, XOR-like, latch and master/slave ff **DONE**
- Layout with guard rings for AND-like and XOR-like **DONE**
  - **TODO**: layouts for latch and ff
  - **TODO**: layouts without guard rings
  - **TODO**: explore other layout techniques for dose resistance (are ELT really not possible?)
- Initial cell characterization in progress. The plan is to learn how to use Cadence automated tools for cell characterization in order to speedup comparison of different layouts
- A flow with custom scripts is possible and partially done.
  - **TODO**: explore tools for 2-rail async netlist conversion (similar to our case)
- **TODO**: this kind of logic opens interesting possibilities for low power. The cells might be used for **NULL convention logic (async)**

backup
 
# 2 INPUT AND-like logic ~ simulation


- A-C / B-D differential inputs
- Z-Y differential output
- Several logic functions with one layout:
  - $Z = A \text{ or } B$
  - $Y = A \text{ nor } B$
  - $Z = C \text{ and } D$
  - $Y = C \text{ nand } D$
  - ...




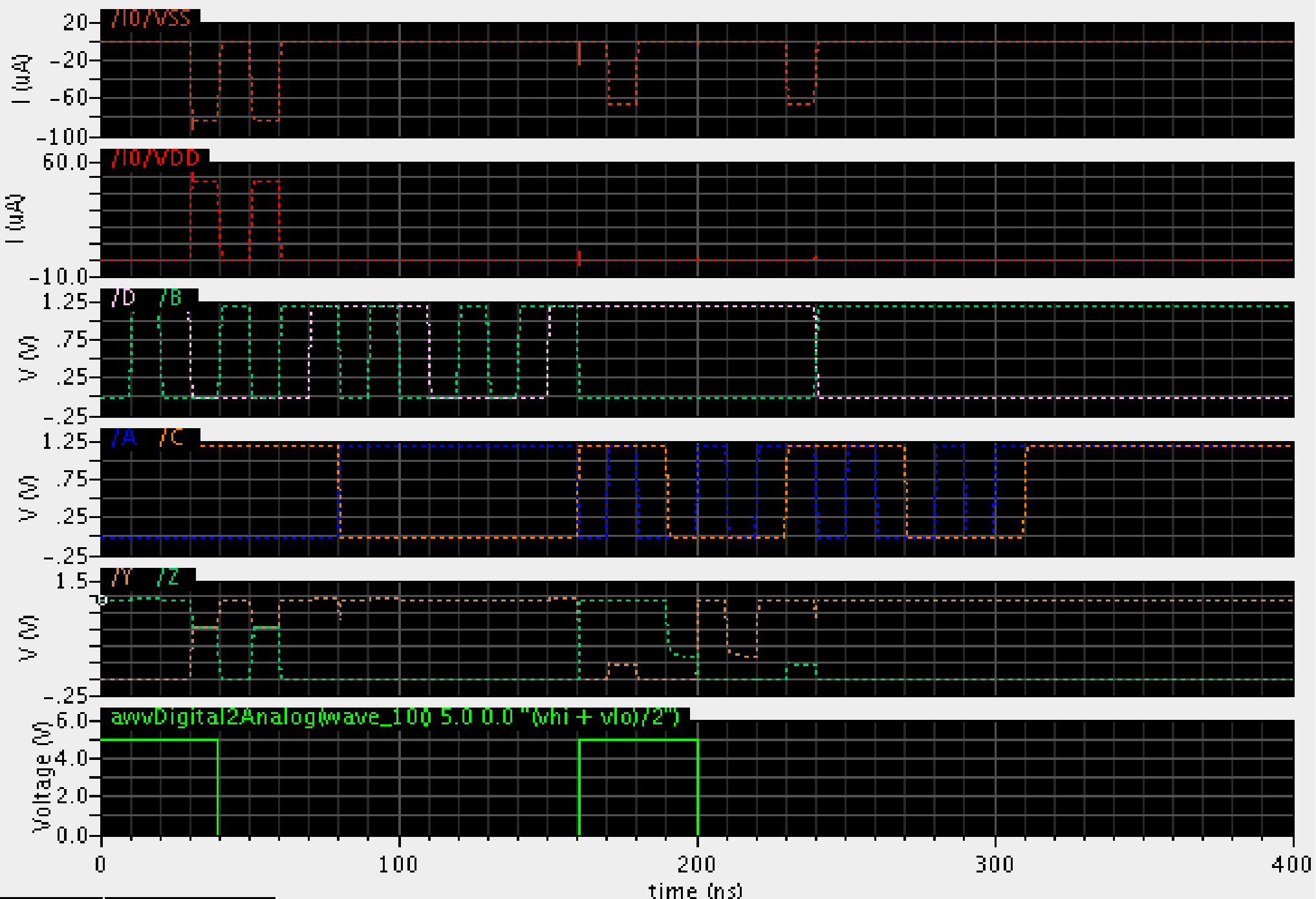

0.0s | 1.2V

time (ns)

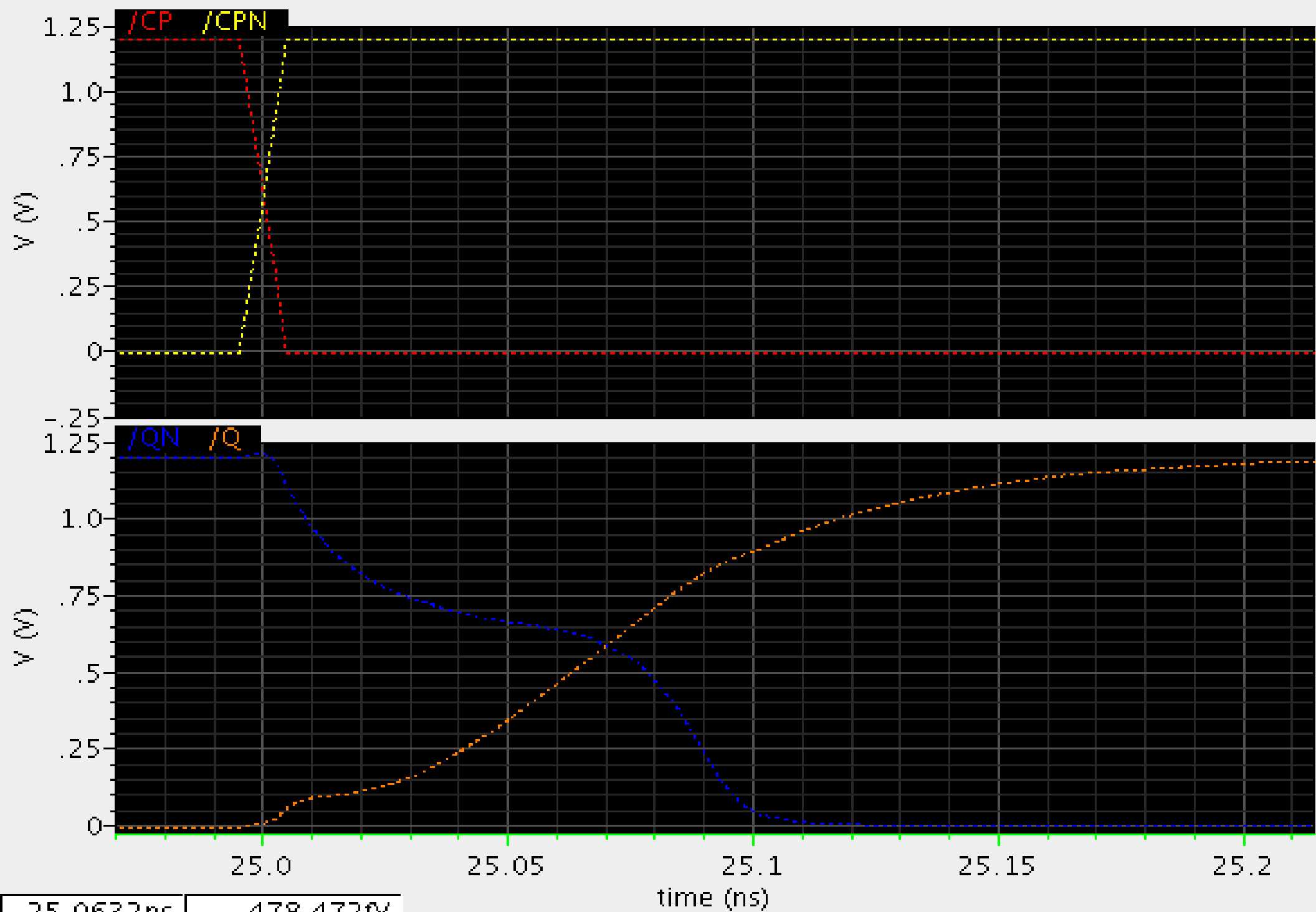

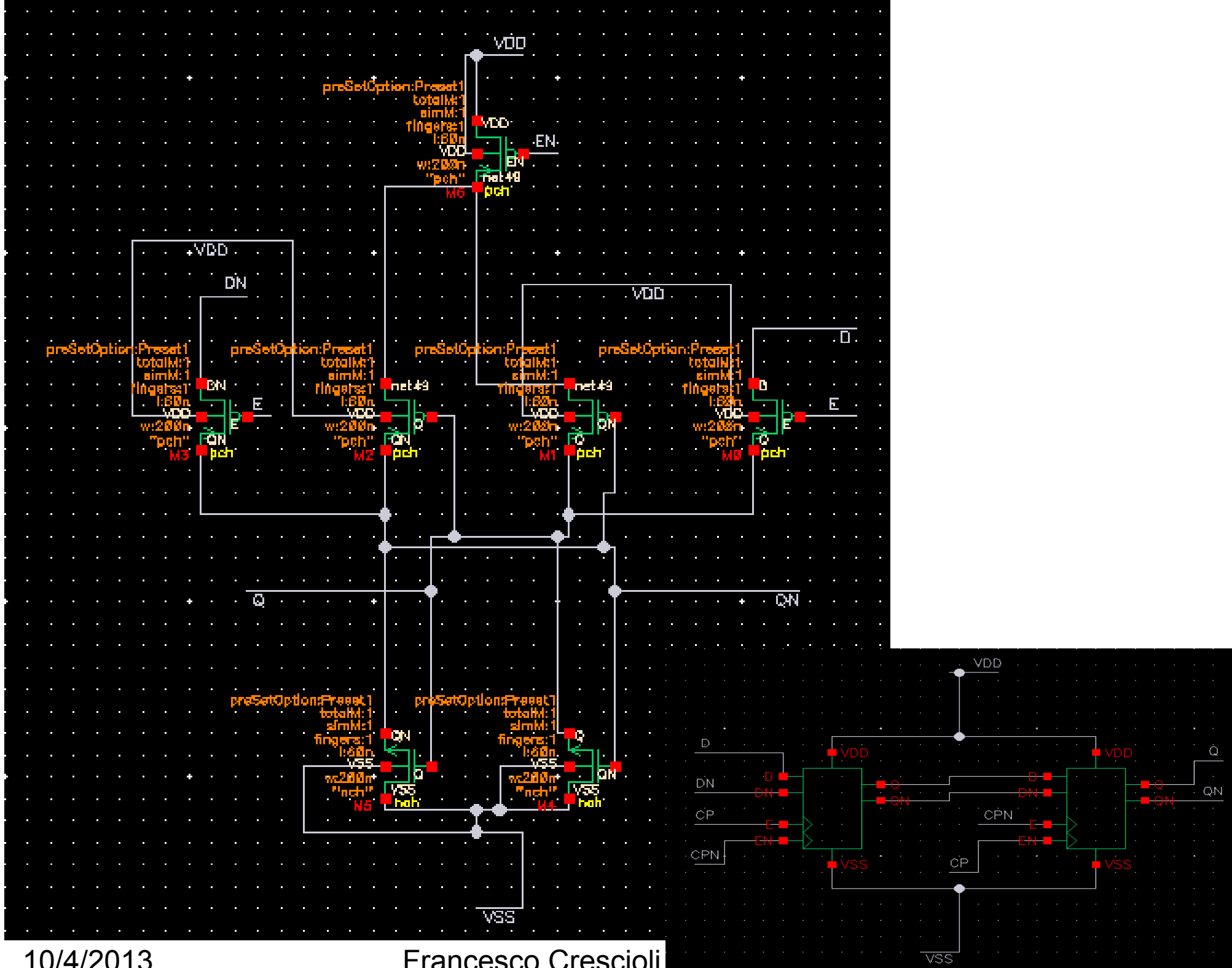

10/4/2013

Francesco Crescioli