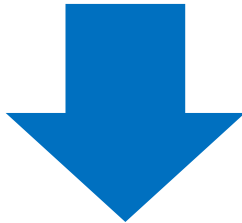




R & D on High Precision TDC for CMS MG-RPC

- Single Gap RPC timing resolution : < 1 ns
- Multi Gap RPC timing resolution ("LSB") : < 20 ps
- Counting rate : 10^4 Hz (100 μ s)



Goal




- TDC timing resolution : 10 ps
- Precision : < 3 ps RMS
- Dead Time : \ll 100 μ s

TDC for medical imaging based on DLL

- ✓ CMOS 0.35 μ m AMS process
- ✓ Clock : 160 MHz
- ✓ 32 cells delay
- ✓ LSB : 200 ps
- ✓ RMS resolution : 60 ps
- ✓ RMS jitter 15 ps
- ✓ Power supply : 5.6 mW

- Possible solution : Ring oscillators TDC
 - low area
 - low power

- Autocalibration
 - T_{slow}
 - Δt

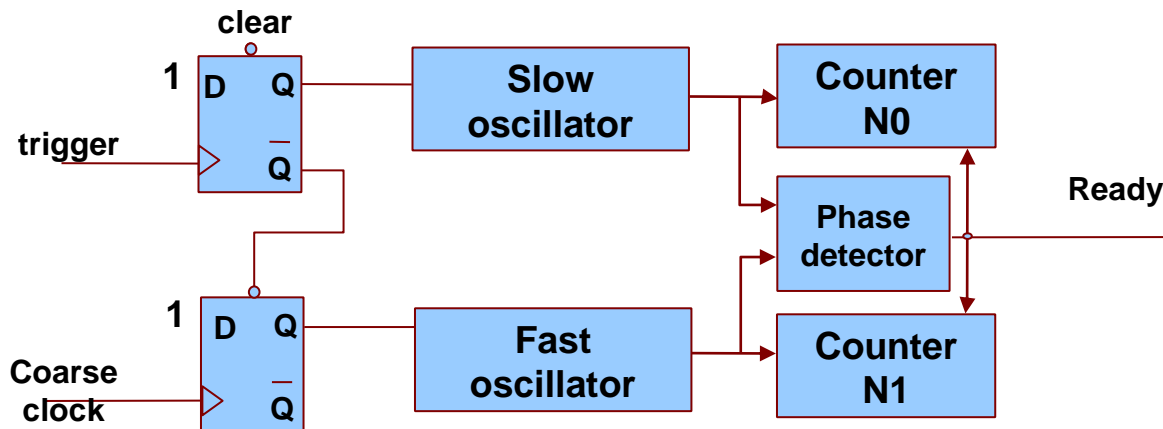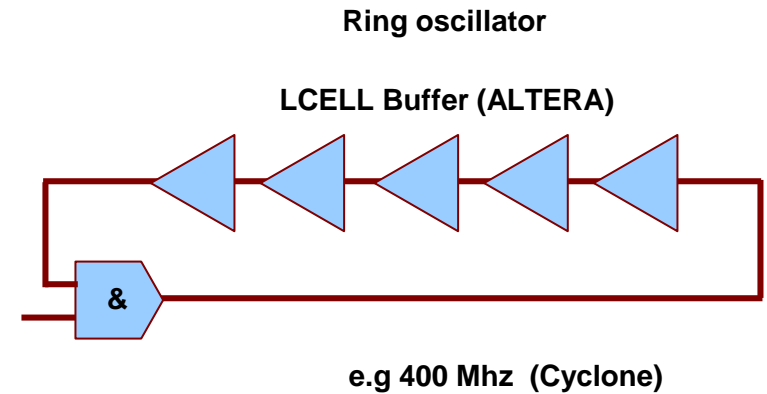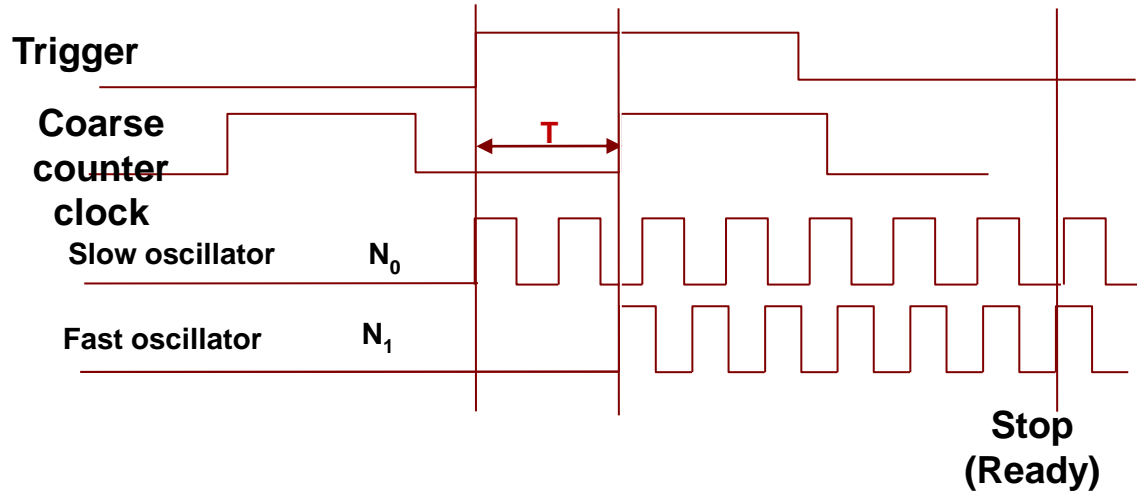

$$T = N_0 T_{slow} - N_1 T_{fast}$$

Some values

$$T - T' = (N_0 - N'_0) T_{\text{slow}} - (N_1 - N'_1) T_{\text{fast}}$$

$$\Delta t = T_{\text{slow}} - T_{\text{fast}}$$

$$T = (N_0 - N_1) \cdot T_{\text{slow}} + N_1 \cdot \Delta t$$



Timing Resolution = Δt

Dead Time = $T_m = T_{\text{coarse counter}} + (T_{\text{slow}}^2 / \Delta t)$

Counter Range N1 = $T_{\text{slow}} / \Delta t$

Counter Range N0 = $(T_{\text{slow}} / \Delta t) + (T_{\text{coarse counter}} / T_{\text{slow}})$



$F_{\text{coarse counter}}$ (Mhz)	F_{slow} (MHz)	Δt (ps)	T_m (ns)	DR N0	DR N1
40	400	10	625	260	250


Input

Design parameters

- Remote implementation on telescope : First tests are very positive
- Coarse counter clock period = 10 ns
- Trigger step 100 ps




TDC response (mean of 10 measurements)

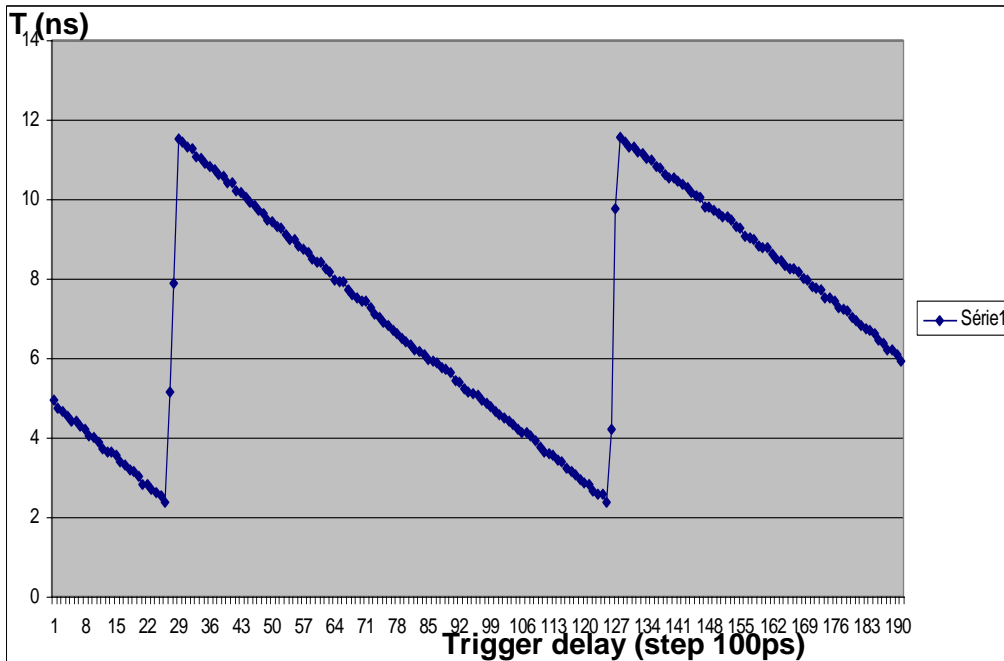

Good linearity and no missing code

T_{slow} response comparison on 6 FPGAs

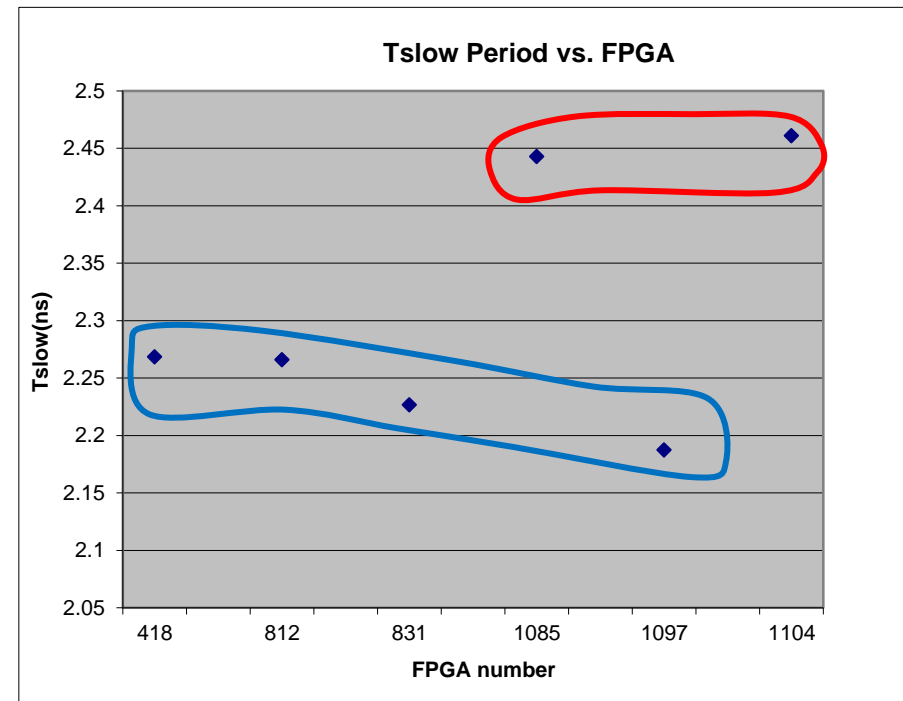

R & D in 2013 on this Architecture

- Implement this architecture in full a custom ASIC
- Based on ring oscillator :
 - $\Delta t = T_s - T_f = 10 \text{ ps}$?
 - Δt drift ?
 - Matched ring oscillators
 - T_s & T_f jitter
 - Process ?
 - Process Dispersion ?
 - Temperature effect ?
- Key issue is analog (ring oscillator)

Pro :

- Ring oscillator works on trigger event
- Power supply reduction
- Easy to calibrate with 2 specifics runs
- Mostly digital TDC (except ring oscillator)

Con:

- Dead Time
- Ring oscillator design



- Start by a design study on ring oscillator : process stability and Δt
- Run schedule by Q3 or Q4 2013
- Funds from IN2P3