



AGH UNIVERSITY OF SCIENCE
AND TECHNOLOGY

Multichannel ADC for physics applications

Marek Idzik AGH-UST

Presented works done by:

M. Firlej, T. Fiutowski, Sz. Kulis, J. Moroń, D. Przyborowski, K. Świentek

Faculty of Physics and Applied Computer Science
AGH University of Science and Technology

26 April 2013, CERN



Outline

- Introduction and motivation
- ADC testing issues
- Multichannel digitizer in AMS 0.35 μm
- Multichannel SAR ADC in IBM 130 nm
 - SAR architecture considerations
 - Design of 10(6)-bit SAR ADC
 - System level blocks (PLL, SLVS, ...)
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

ASIC group, infrastructure and activities at Faculty of Physics of AGH-UST

- People: staff 7, phd students 4, master students ~4
- Dedicated labs for microelectronics and detectors:
 - Clean-room class ISO6
 - Equipment: probe-stations (e.g. semi-automatic Cascade), bonder (F&K Delvotec 5330), semiconductor parameter analyzers (Agilent B1500A x 2, HP4145A), spectrum/signal analyzers (Agilent 4395A, N9030A), scopes up to 40GS/s (e.g. Agilent 90804A), generators (e.g. Agilent 81150A, 81160A), semiconductor lasers (Picoquant PDL 800-D with 660nm and 1060nm heads), radioactive sources, precise XYZ moving stages, High Voltage SMU (Keithley SMU237), RLC meters (e.g. Agilent E4980A)
 - Computer power for ASIC design: 2 servers DELL MD710HD (24 cores)+disc array MD3200i, 5 x very fast PCs for fast complex analyses, personal workstations
 - Software (>20 licenses): ASIC design (Cadence, Synopsis, Mentor Graphics), FPGA design (Xilinx), PCB design (Altium)
- Projects: ATLAS, **LHCb**, **ILC/CLIC**, PANDA, SOI, general microelectronics/detector R&D

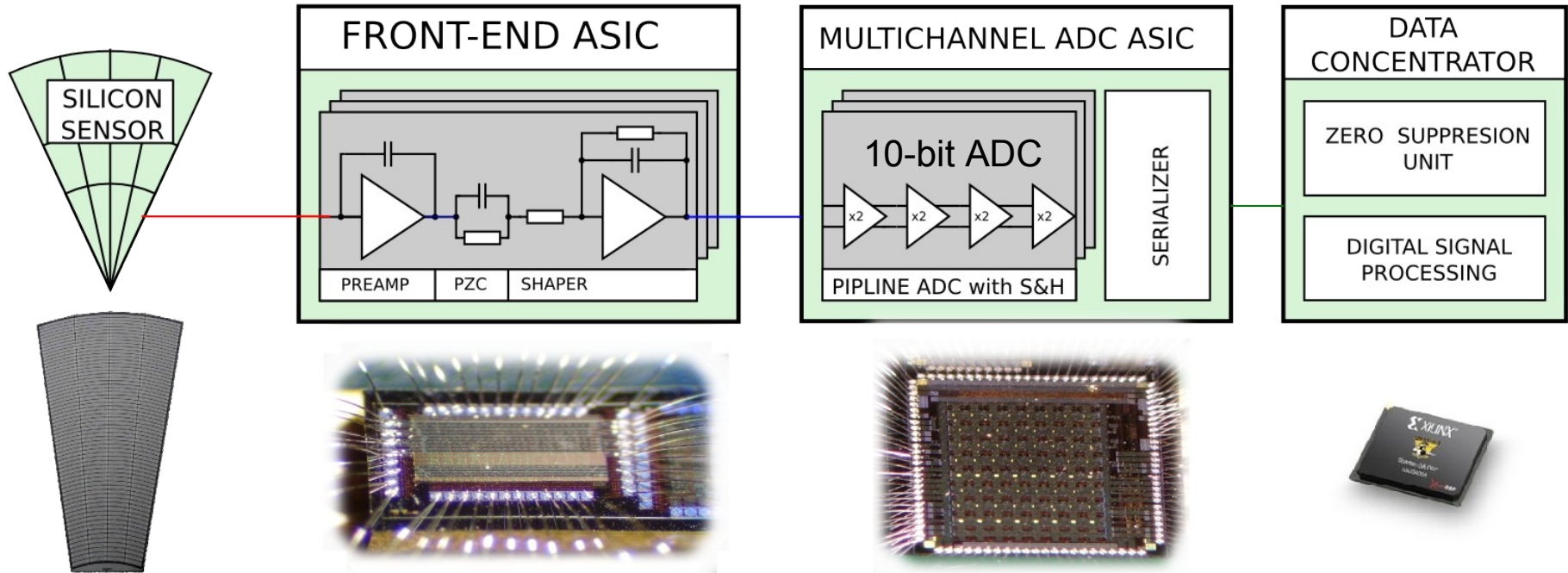 Motivation LumiCal detector readout electronics for ILC




- Present readout ASICs developed in CMOS AMS 0.35 μm
- Development of new readout in CMOS IBM 130 nm in progress...



AGH

Motivation...

 Multichannel readout ASIC for LHCb strip tracker



- Complex 128 channel ASIC
 - Preamplifier-shaper, 6-bit ADC, zero supp., serialization
 - Pitch $\sim 40\mu\text{m}$
- CMOS IBM 130 nm technology
- Application in various detectors
 - TT tracker, VELO strip, IT tracker ?

“Fast” Multichannel 10-bit ADC

Commercial and research solutions



Parameter	Our work	K. Kavani et al ESSCIRC 2002	AD9212 AnalogDevices	ADS5287 TexasInstruments	MAX1434 Maxim
Nr of channels	8	8	8	8	8
Architecture	10-bit pipeline	10-bit pipeline	10-bit pipeline	10-bit pipeline	10-bit pipeline
Serialization	Per channel & per chip	Per chip	Per channel	Per channel	Per channel
Technology	0.35 μm CMOS	0.25 μm CMOS	-	CMOS	BiCMOS
Supply	3.3 V	2.5 V	1.8 V	3.3/1.8 V (A/D)	1.8 V
Max. f_{sample}	25MS/s	20MS/s	65MS/s	65MS/s	50MS/s
Input range	2Vpp	-	2 Vpp	2 Vpp	1.4 Vpp
Power/channel	$\sim 1.2\text{mW/MS/s}$ plus I/O (<15%)	41mW@20MS/s	100mW@65MS/s 68mW@40MS/s	74mW@65MS/s 46mW@30MS/s	96mW@50MS/s
Area	8.2 mm ²	4mm ²	9x9mm ² (package)	9x9mm ² (package)	14x14mm ² (package)
INL	<0.68LSB	-	<0.5LSB	<1LSB	<1LSB
DNL	<0.62LSB	-	<0.4LSB	<0.55LSB	<0.5LSB
SINAD	$\sim 60.3\text{dB}$	54.3dB	$\geq 60\text{dB}$	$\geq 60.4\text{dB}$	$\geq 60\text{dB}$
$T_{\text{power_ON}}$	$\leq 10T_{\text{clk}}$ ($\sim \mu\text{s}$)	-	375 μs	-	100ms

M. Idzik, K. Swientek, T. Fiutowski, Sz. Kulis, D. Przyborowski “A 10-bit multichannel digitizer ASIC for detectors in particle physics experiments”, IEEE Trans. Nucl. Sci. v.59 p.294-302 2012

- Introduction and motivation
- **ADC testing issues**
- Multichannel digitizer in AMS 0.35 μm
- Multichannel SAR ADC in IBM 130 nm
 - SAR architecture considerations
 - Design of 10(6)-bit SAR ADC
 - System level blocks (PLL, SLVS, ...)
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

ADC testing

Static measurements

  


- **DNL** - Differential NonLinearity - the difference between an actual step width and the ideal step width
- **INL** - Integral NonLinearity - deviation of an actual transfer function from a straight line (integrated DNL)

ADC testing

Dynamic measurements

$$ENOB = \frac{SINAD [dB] - 1.76}{6.02}$$

 - Single tone, full scale sine wave applied to input of the ADC
- Fourier Transform computed from the collected digital samples



- **SINAD** – Signal to Noise And Distortions
- **THD** – Total Harmonic Distortions
- **SFDR** – Spurious Free Dynamic Range
- **SNHR** – Signal to Non Harmonic Ratio

ADC testing/design

Resolution vs sampling clock jitter

$$V_{IN}(t) = V_A \times \sin(2\pi \times f_{IN} \times t)$$


$$\frac{dV_{IN}(t)}{dt} = 2\pi \times f_{IN} \times V_A \times \cos(2\pi \times f_{IN} \times t)$$

$$\left. \frac{dV_{IN}(t)}{dt} \right|_{RMS} = \frac{2\pi \times f_{IN} \times V_A}{\sqrt{2}}$$

$$\frac{V_{ERROR_RMS}}{t_J} = \frac{2\pi \times f_{IN} \times V_A}{\sqrt{2}}$$


$$V_{ERROR_RMS} = \frac{2\pi \times f_{IN} \times V_A \times t_J}{\sqrt{2}}$$
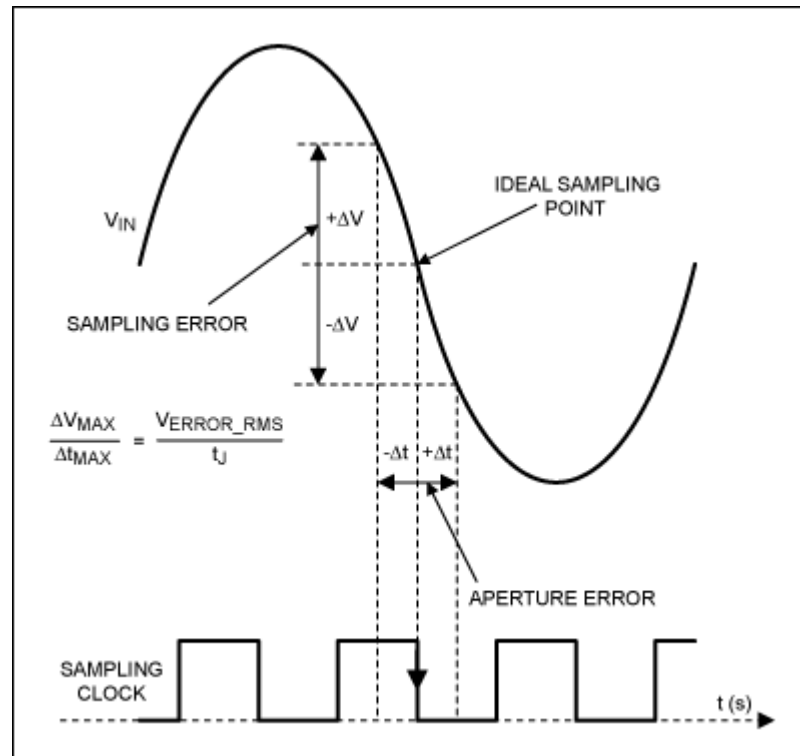
$$SNR = 20 \log_{10} \left[\frac{V_{IN_RMS}}{V_{ERROR_RMS}} \right] = 20 \log_{10} \left[\frac{V_A / \sqrt{2}}{2\pi \times f_{IN} \times V_A \times t_J / \sqrt{2}} \right]$$




ADC testing/design

Resolution vs sampling clock jitter...

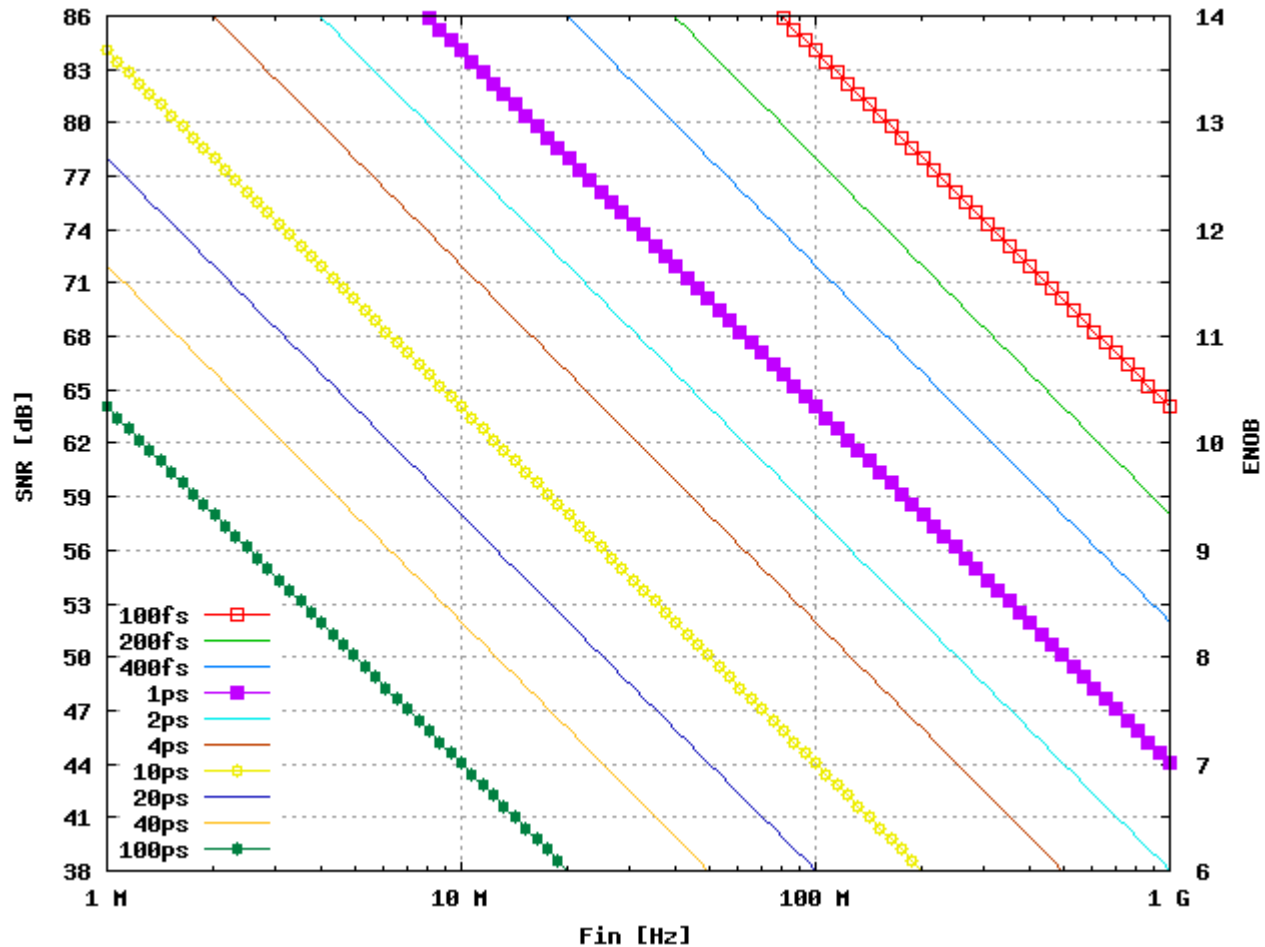

ADC testing FPGA based test setup

 

- Capturing data from ADC up to 300 MHz in LVDS standard
- AD9522 external PLL used to provide low jitter sampling clock (<10ps required !)

- Other instruments (power supplies-Agilent B1500A, signal generators-Agilent 81160A) controlled via GPIB/Ethernet by the supervising PC
- Fully automatic ASIC testing



Outline

- Introduction and motivation
- ADC testing issues
- **Multichannel digitizer in AMS 0.35 um**
- Multichannel SAR ADC in IBM 130 nm
 - SAR architecture considerations
 - Design of 10(6)-bit SAR ADC
 - System level blocks (PLL, SLVS, ...)
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

Multichannel digitizer Architecture

- Specs&impleentation issues:



- 8 channels of 10-bit pipeline ADC
- Technology AMS 0.35um
- Fully differential ADC
- Layout with 200um ADC pitch
- Multimode digital multiplexer/serializer:
 - Serial mode ($\sim 250\text{MHz}$): one data link per all channels (max $f_{\text{smp}} \sim 3 \text{ MSps}$)
 - Parallel mode ($\sim 250\text{MHz}$): one data link per channel (max $f_{\text{smp}} \sim 25 \text{ MSps}$)
 - Test mode: single channel output (max $f_{\text{smp}} \sim 50 \text{ MSps}$)
- High speed LVDS interface ($\sim 1\text{GHz}$)
- Bootstrapped S/H switches
- Power pulsing
- Low power DACs for internal settings
- BandGap reference source
- Temperature sensor

  

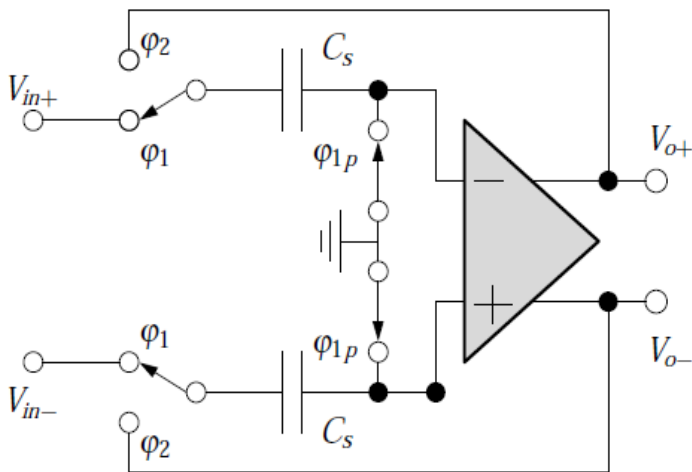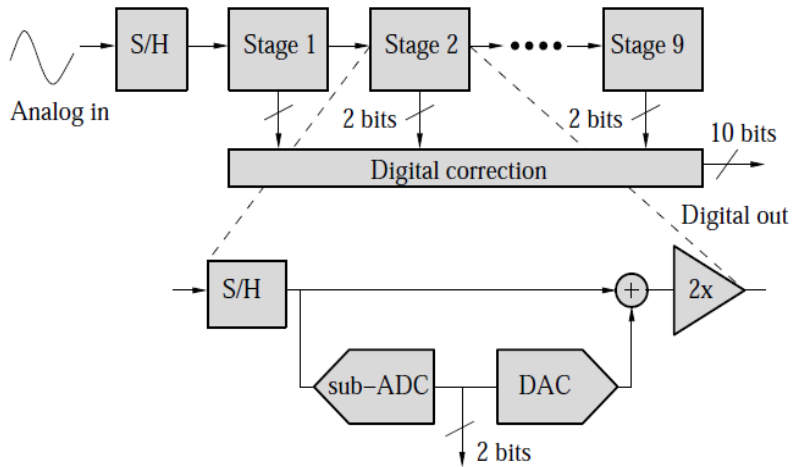2.6mm x 3.2mm


Three submissions were done (two to develop core ADC) to get final chip

Multichannel digitizer 10-bit pipeline ADC



S/H stage

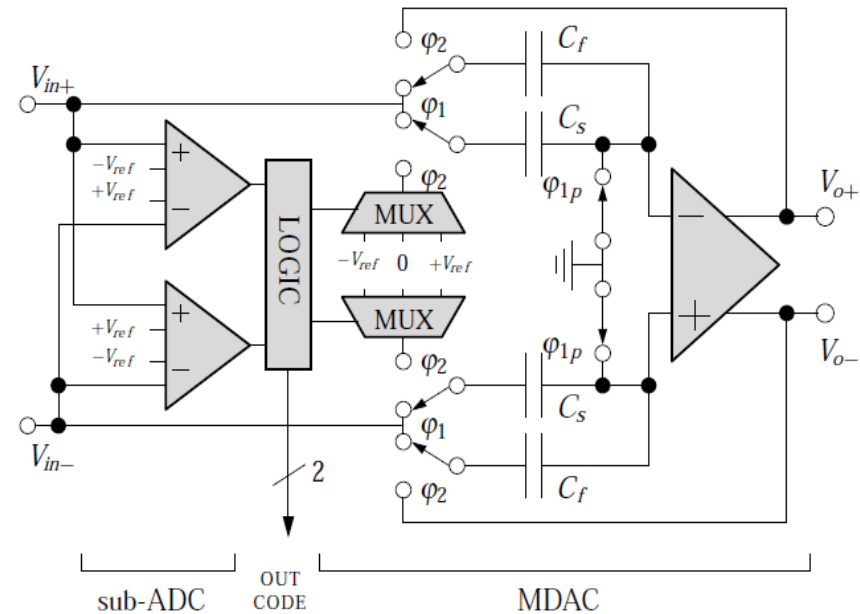- High throughput - conversion rate = clock rate
- 1.5 bit per stage - redundancy reduces comparator requirements
- Fully differential architecture



1.5 bit pipeline stage




Multichannel digitizer Performance



• Performance

- ENOB=9.7 up to 25 Ms/s (8 channels)
- INL<0.68, DNL<0.62
- Sampling rate up to ~25MS/s (multichannel) or up to ~50MS/s (single channel)
- Power scales linearly with sampling rate ~1.2mW/channel/MHz (without power pulsing)


Static measurements

 


Dynamic measurements

  

 Multichannel digitizer in LumiCal detector



4 pairs of Front-end + ADC

 

Sensor

- ❑ LumiCal detector module with 32 fully equipped channels (Front-end +ADC ASICs) plus FPGA data concentrator is regularly used during FCAL Collaboration test-beams


- Introduction and motivation
- ADC testing issues
- Multichannel digitizer in AMS 0.35 μm
- **Multichannel SAR ADC in IBM 130 nm**
 - **SAR architecture considerations**
 - Design of 10(6)-bit SAR ADC
 - System level blocks (PLL, SLVS, ...)
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

Design of SAR multichannel ADC

Specifications & implementation issues:

- 8 channels of 10-bit (6-bit) SAR ADC
- Technology IBM 130 nm
- Layout with 146um (40um) ADC pitch
- Multimode digital multiplexer/serializer:
 - Serial mode: one data link per all channels (external clk division or PLL clk generation)
 - Parallel mode: one data link per channel (external clk division or PLL clk generation)
 - Test mode: single channel output (max fsmp ~50 Msp/s)

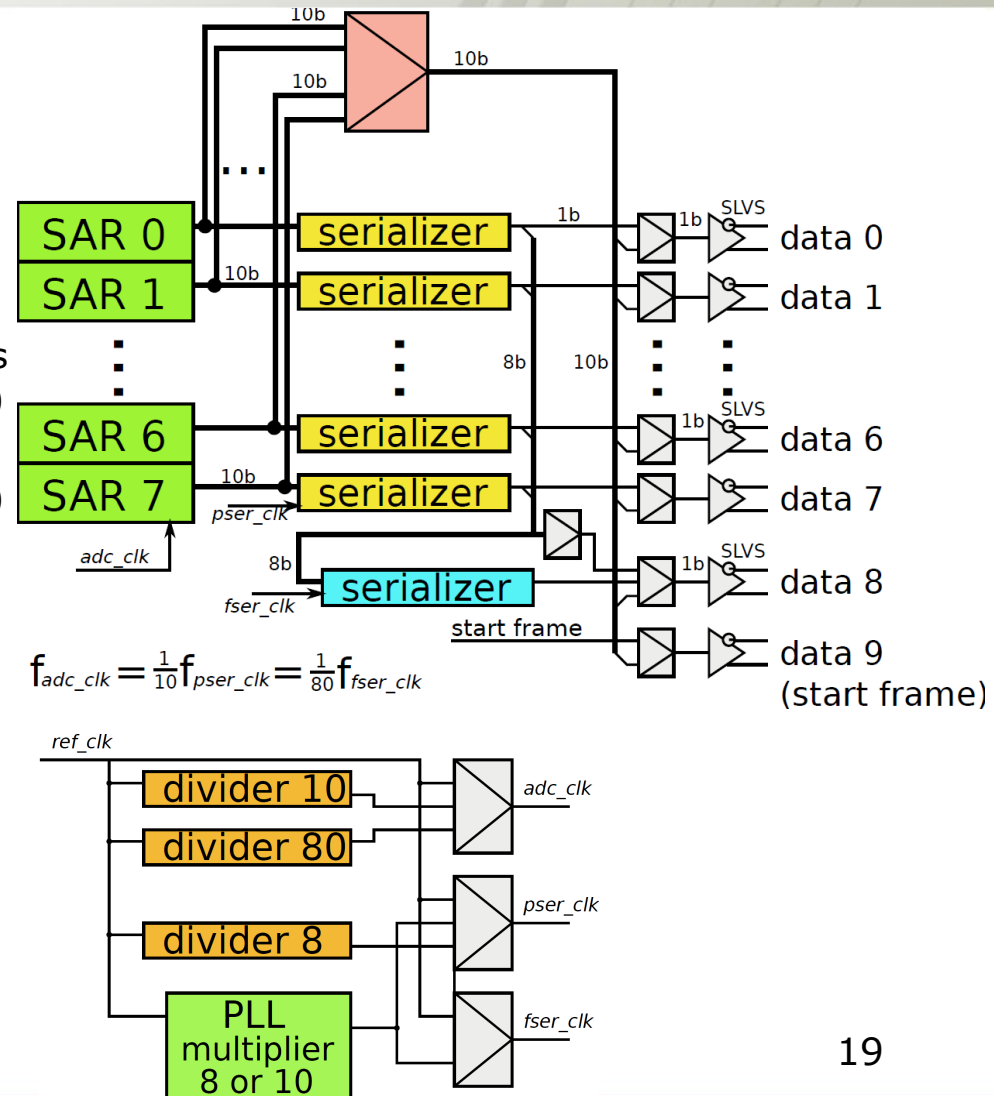
- PLL for data serialization
- High speed SLVS interface (~1GHz)
- Power pulsing
- Generation of short sampling pulse
- Bootstrapped S/H switches
- Voltage reference not yet addressed...
- SingleEnded-to-Differential converter ??



SAR ADC motivation

General features & design considerations

- Power and area-efficient architecture – the same circuitry is used N-times (for N-bit ADC) to approximate the input voltage
- Only one comparator, two DACs and SAR logic needed – fits well to modern digital CMOS
- Limited sampling rates - but with modern CMOS technology ($\sim 100\text{nm}$) up to $\sim 100\text{MSps}$ 10-bit ADCs were reported
 - next conversion cannot be started before completion of previous one
 - sampling time adds to conversion time (not like in pipeline)

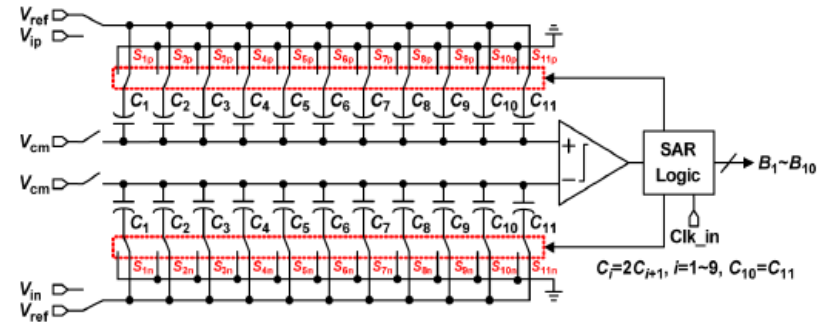


- Comparator – the only analog block
- DAC network serves as sampling capacitance
- Simple digital logic
- Fully differential implementation increases the resistance to disturbances

Why various SAR configurations ? Switching energy

- With CMOS technology scaling digital power consumption is decreasing rapidly - so minimizing analog power (DAC, comparator) is of main interest
- Huge progress has been obtained in the last ~10 years in optimizing capacitive DAC configurations and their switching schemes
- Various DAC switching configurations were proposed
 - Conventional (100% power consumption)
 - 2 step switching (~10% power saving)
 - Charge sharing (~24% power saving)
 - Split capacitor (~37% power saving)
 - Energy saving (~56% power saving)
 - Set and down (~81% power saving)
 - Vcm-based (~87% power saving)
 - Merge Capacitor Switching (MCS) (~93% power saving)
 - Last half year some new were proposed (up to ~98% power saving)

Switching energy – principle

2-bit capacitor array example

 


Energy drawn from Vref: $E = V_{ref} * \Delta Q$

“up” transitions – S_i short to V_{ref}


“down” transitions - S_i short to gnd

1. S_2 “up” transition: $E = C_0 V_{ref}^2$

 2. If $V_{in} > V_{ref}/2$ then S_1 goes “up”: $E = C_0 V_{ref}^2 / 4$, otherwise S_1 goes “down”:



 Conventional switching: $E = 5C_0 V_{ref}^2 / 4$




2 step switching: $E = 3C_0 V_{ref}^2 / 4$



“down” transitions consume much power...

Switching energy – principle 2-bit capacitor array example...

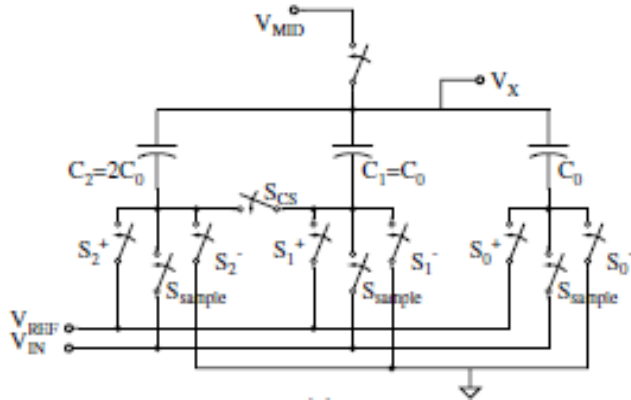
There are other ways to perform “down” transitions:



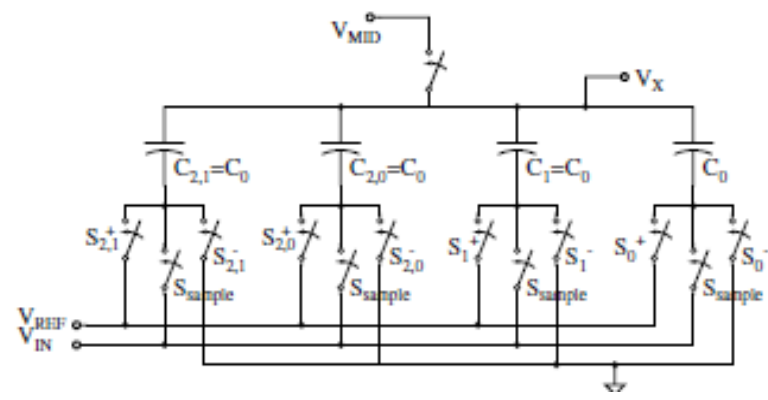 Charge sharing: $E = 7C_0 V_{ref}^2 / 12$




Split capacitor: $E = C_0 V_{ref}^2 / 4$

 

Switching scheme may be optimized to save power in “down” transitions!

Switching energy Comparison of simple schemes

Switching energy versus output code

 


only "up" transitions

Hspice points vs Matlab model (*from Ginsburg paper*)


Switching energy – more efficient configurations

Set and down vs conventional

Conventional 10-bit SAR

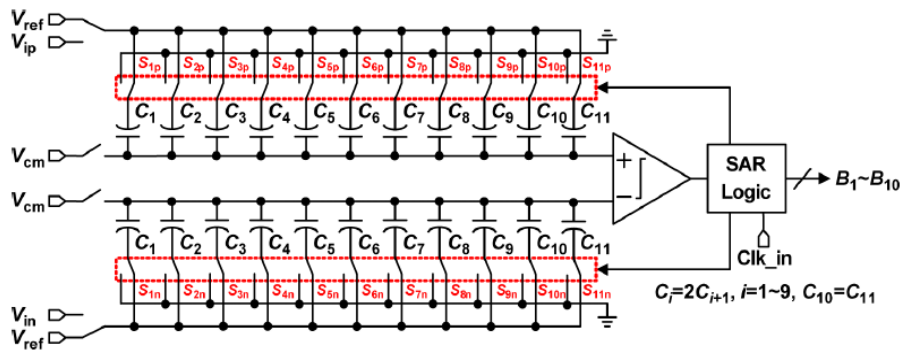


Set and down 10-bit SAR

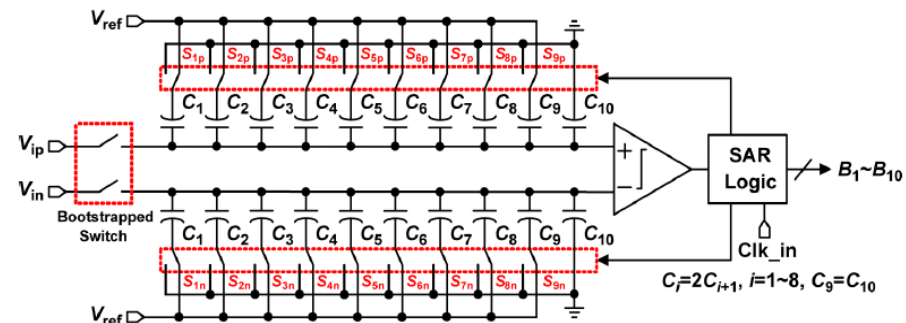

Set and down SAR ADC:

 
- pair of MSB capacitors less
- V_{in} sampled on top plate
- 1st comparison done before any switching



Variable common mode...

Switching energy – more efficient configurations


Set and down 3-bit SAR ADC example

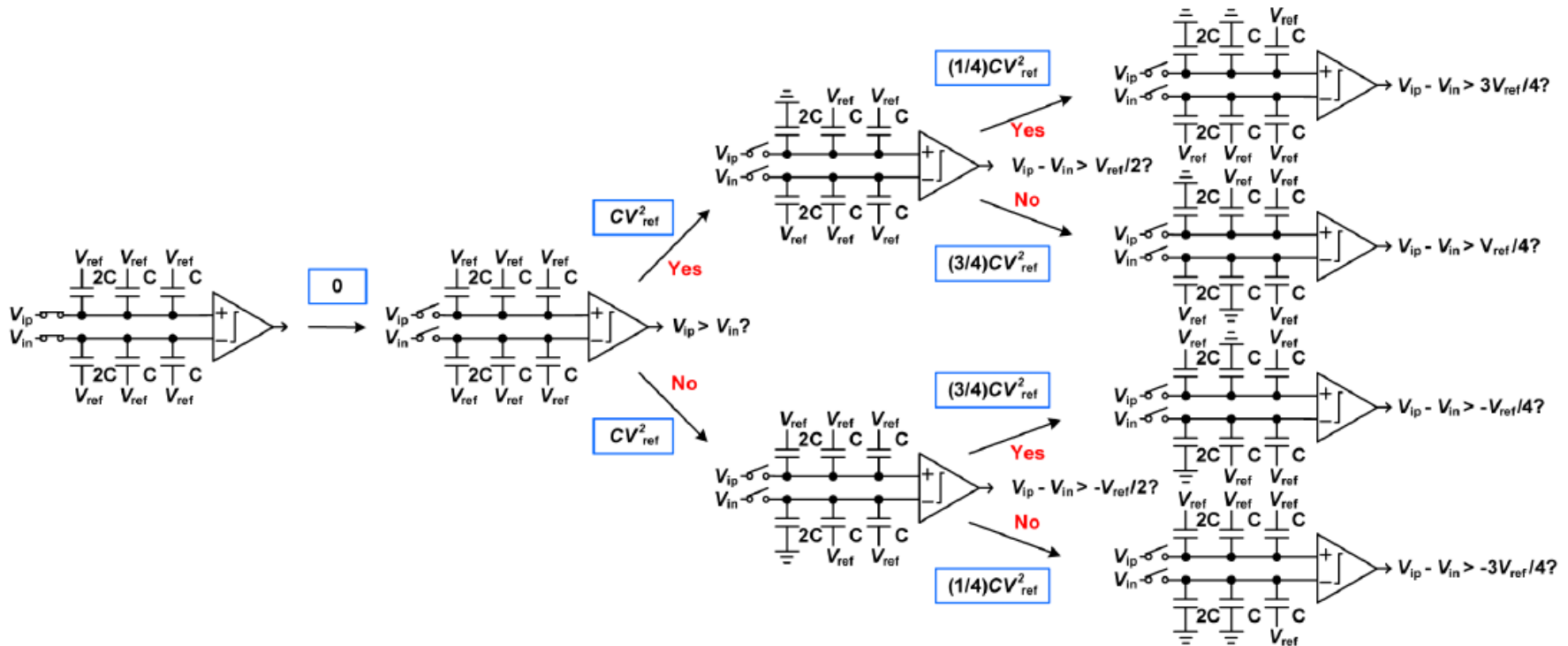

Switching energy $\sim 81\%$ less than conventional SAR ADC

Switching energy – more efficient configurations


Merge Capacitor Switching (MCS) SAR ADC

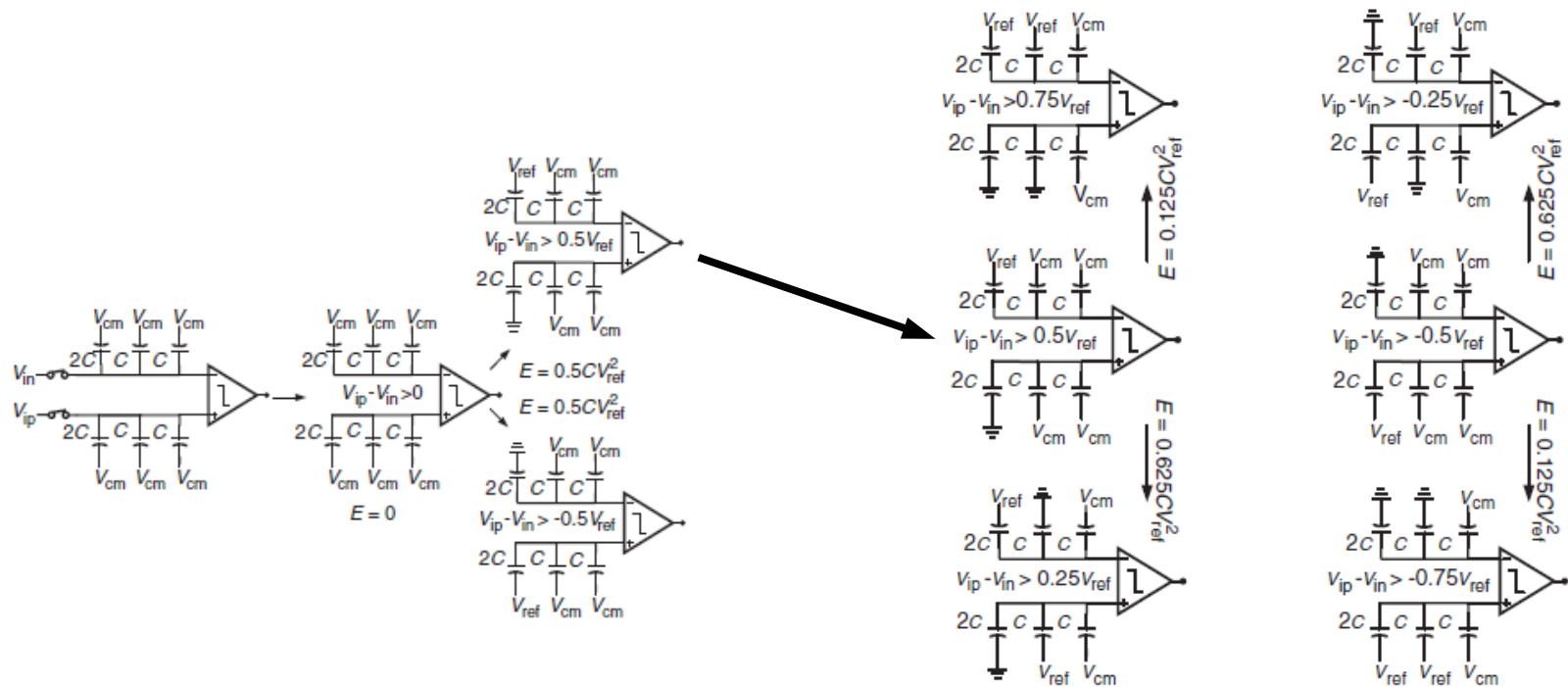

Switching energy ~93% less than conventional SAR ADC

Such switching scheme is used in our present design

 SAR switching energy Merge Capacitor Switching (MCS)...




Within last ~half year new papers with even more efficient schemes were published...

- Introduction and motivation
- ADC testing issues
- Multichannel digitizer in AMS 0.35 μm
- **Multichannel SAR ADC in IBM 130 nm**
 - SAR architecture considerations
 - **Design of 10(6)-bit SAR ADC**
 - System level blocks (PLL, SLVS, ...)
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

Design of SAR ADC Implementation issues


- Split DAC architecture
 - allows using higher unit capacitance for the given total DAC capacitance. It helps to bypass the problem of relatively high C_{min} available in CMOS technologies – allows to decrease the effective “LSB capacitance” and so power consumption
- Asynchronous logic
 - no fast clock needed for bit cycling
 - only sampling pulse needed for digital control
 - sampling pulse (trigger) does not need to be periodic
- Dynamic comparator
 - allows to obtain zero static power consumption and so “power pulsing” is given for free!
- Bootstrapped sampling switch
 - improves ADC linearity

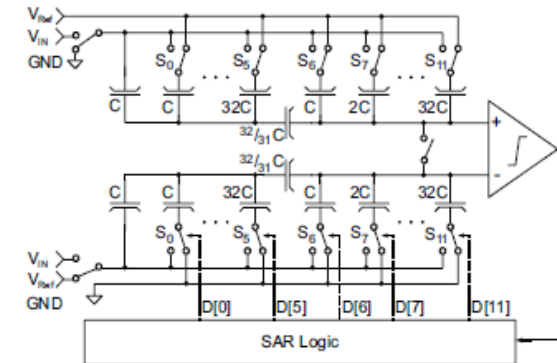


Design of SAR ADC

Bootstrapped S/H switch


Idea

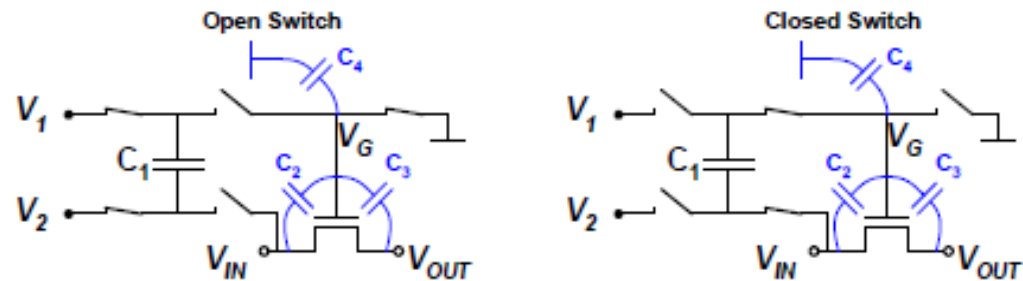

Implementation

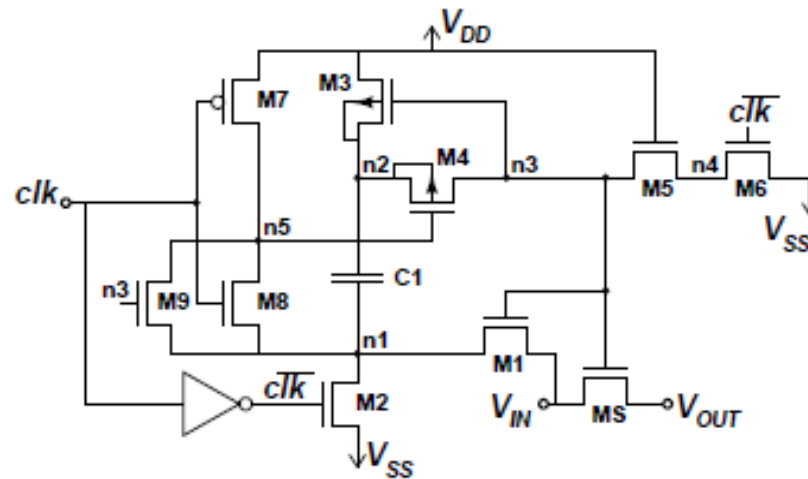

Design of SAR ADC Dynamic comparator

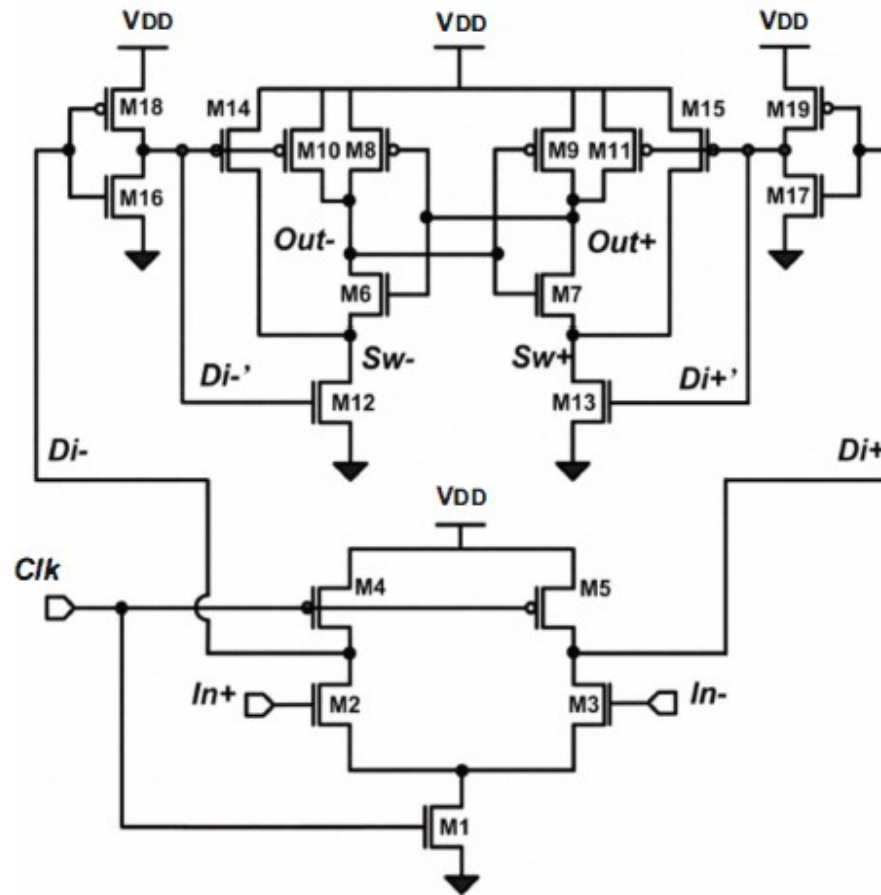

H.J. Jeon, Y-B. Kim, M. Choi "Offset voltage analysis of dynamic latched comparator", IEEE 54th Int. Midwest Symp. On Circuits and Systems, 2011

Design of SAR ADC – DAC capacitors

Noise and matching considerations

Noise

Thermal switch noise of sampling circuit – kT/C

$$kT/C < \sigma^2/12$$

$$kT/C < (V_{ref}/2^N)^2/12$$

$$C > 12 kT (2^N/V_{ref})^2$$

For $V_{ref} = 1$ V:

$$N=6 \text{ bits} \quad C > 0.2 \text{ fF}$$

$$N=8 \text{ bits} \quad C > 3.3 \text{ fF}$$

$$N=10 \text{ bits} \quad C > 52 \text{ fF}$$

$$N=12 \text{ bits} \quad C > 830 \text{ fF}$$

Switch noise is negligible

Matching

$$\text{VNCAP M1-M2} \sim 0.4 \text{ fF}/\mu\text{m}^2$$

$$\text{MIMCAP} \sim 2 \text{ fF}/\mu\text{m}^2$$

Mis-match % (3σ)


$$\text{VNCAP } 10 \times 20 \mu\text{m}^2 (\sim 80 \text{ fF}) \sim 5\%$$

$$\text{MIMCAP } 6 \times 7 \mu\text{m}^2 (\sim 80 \text{ fF}) \sim 0.7\%$$

MOM – no model exist, matching unknown...

MIMCAP has high density and good matching

Design of 10-bit SAR in IBM 130nm

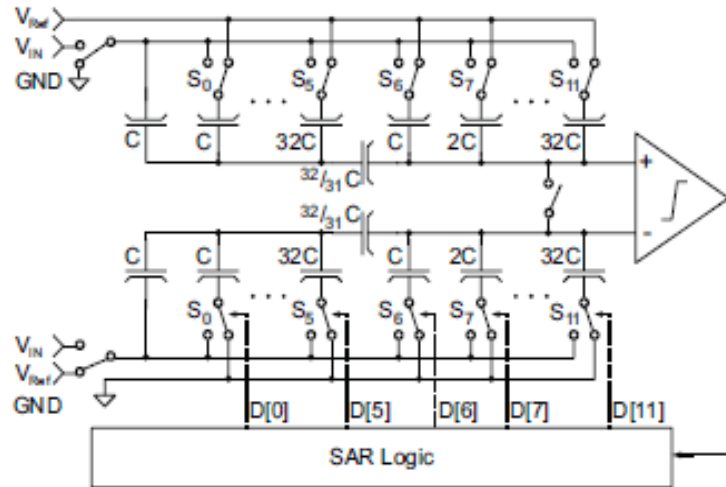


Designs of 10-bit ADC

- Architecture: SAR ADC with segmented/split DAC
- Asynchronous SAR logic – No-bit clk
- Scalable frequency (up to ~ 50 MS/s) and power consumption
- 1-2mW at 40MS/s
- 146um pitch
- Fabricated in 2012 (2 prototypes)

Design of 6-bit ADC

- Architecture: SAR ADC with segmented/split DAC
- Asynchronous SAR logic – No-bit clk
- Scalable frequency (up to ~ 100 MS/s) and power consumption
- $\sim 300\mu\text{W}$ at 40MS/s
- 40um pitch
- Fabricated in 2012

Design of 10-bit SAR in IBM 130nm


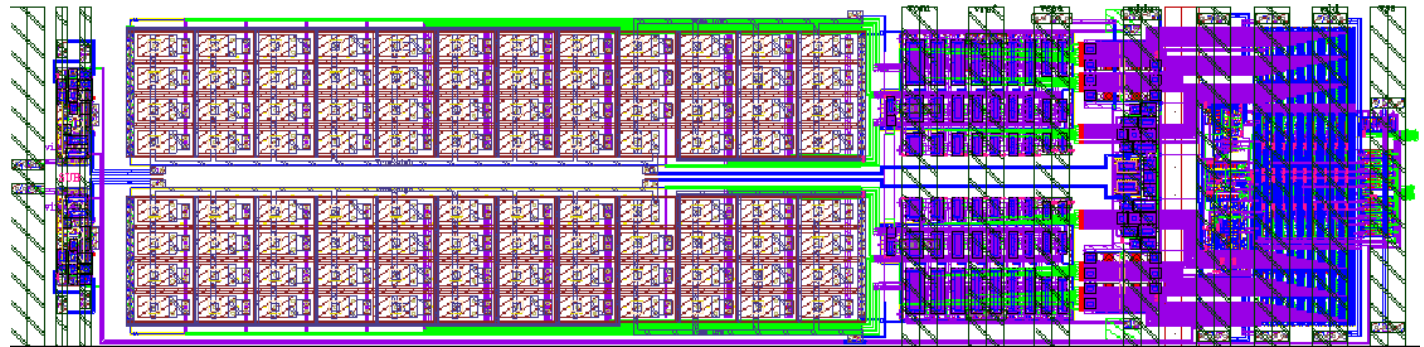


SAR DAC channel 600um x 146um

Two slightly different designs in IBM 130 nm submitted

- Simulated ENOB \approx 9.5-9.7 bits
- Maximum sampling rate \sim 50 MS/s
- Power consumption \approx 1-1.4mW @ 40 MS/s
- Slightly different DAC capacitance splitting in 2 prototypes
- No dummy capacitors in DAC network!

Design of 6-bit SAR ADC in IBM 130 nm

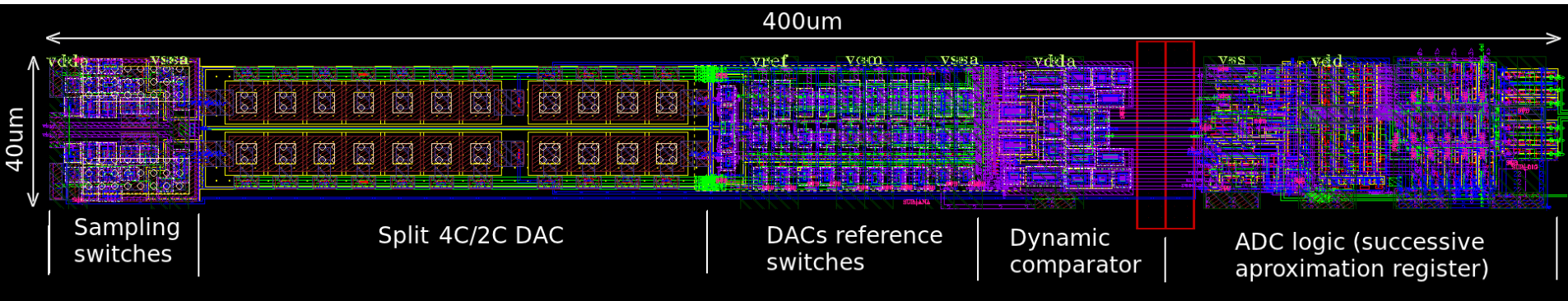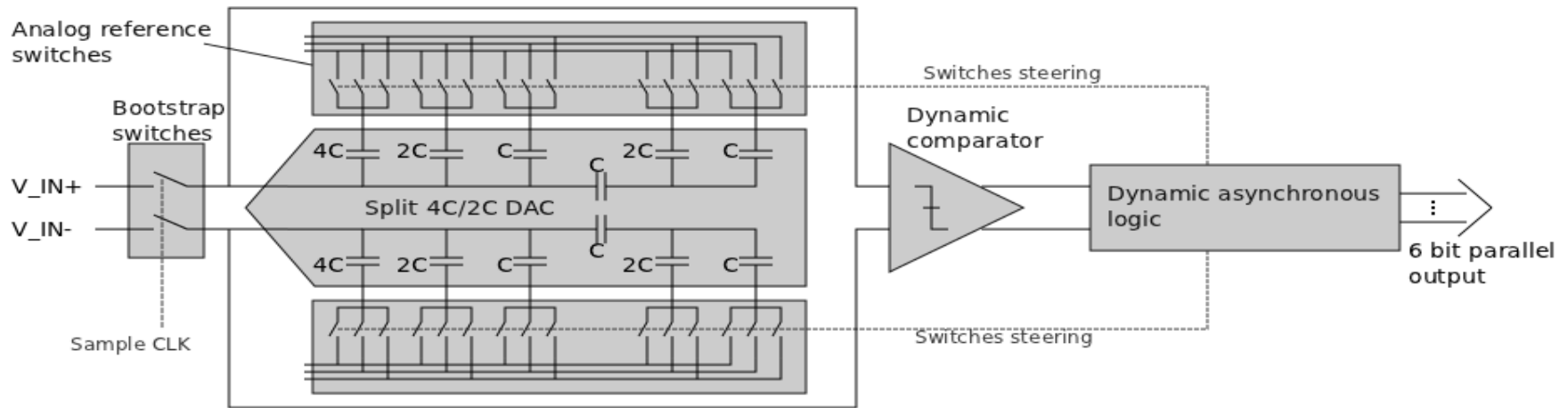


- Single channel: 40µm x 400µm (area 0.016 mm²)
- Custom capacitor p-cell layout done to obtain 40µm pitch

Simulation of 6-bit SAR ADC

 Example of dynamic performance

Dynamic parameters obtained from discrete Fourier analyses of 1024 samples of input sine wave.




Post-layout simulation results at 40MS/s:

- SINAD \approx 37.5 dB
- ENOB \approx 5.94 bits

Simulation of 6-bit SAR ADC

Example of Monte-Carlo mismatch analysis

 

Simulation performed
100 times


ENOB always above 5.8 bits, average 5.95 bits

Outline

- Introduction and motivation
- ADC testing issues
- Multichannel digitizer in AMS 0.35 μm
- **Multichannel SAR ADC in IBM 130 nm**
 - SAR architecture considerations
 - Design of 10(6)-bit SAR ADC
 - **System level blocks (PLL, SLVS, ...)**
- Preliminary tests of prototypes in IBM 130 nm
 - SAR ADC, PLL, SLVS
- Summary

Design of PLL for data serialization



Example of 6-bit ADC

 

PLL needed to multiply Sample CLK frequency by 6 (in this example)

- Flexible PLL needed for our applications
 - different division factors needed for 6(10)-bit ADCs and maybe also for different numbers of ADC channels
 - scalable frequency PLL needed for scalable sampling rate ADC
- Low power consumption is default requirement


Design of PLL for data serialization

 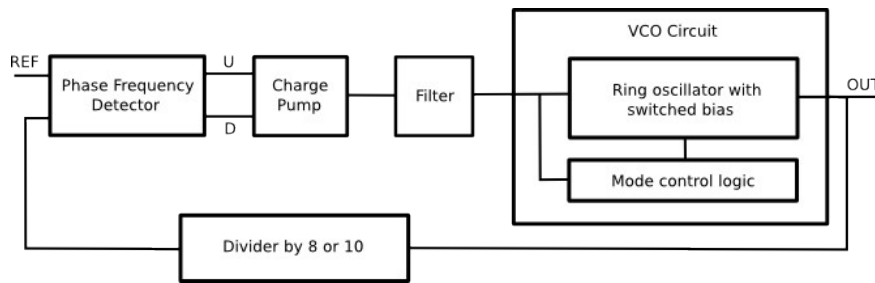

- Design specifications:

- Architecture – type II PLL with 2nd order filter
- Technology - IBM130 nm
- Scalable frequency and power consumption
- Automatically switched VCO range (narrow ranges for small jitter)
- Configurable division factors
- Very low power consumption

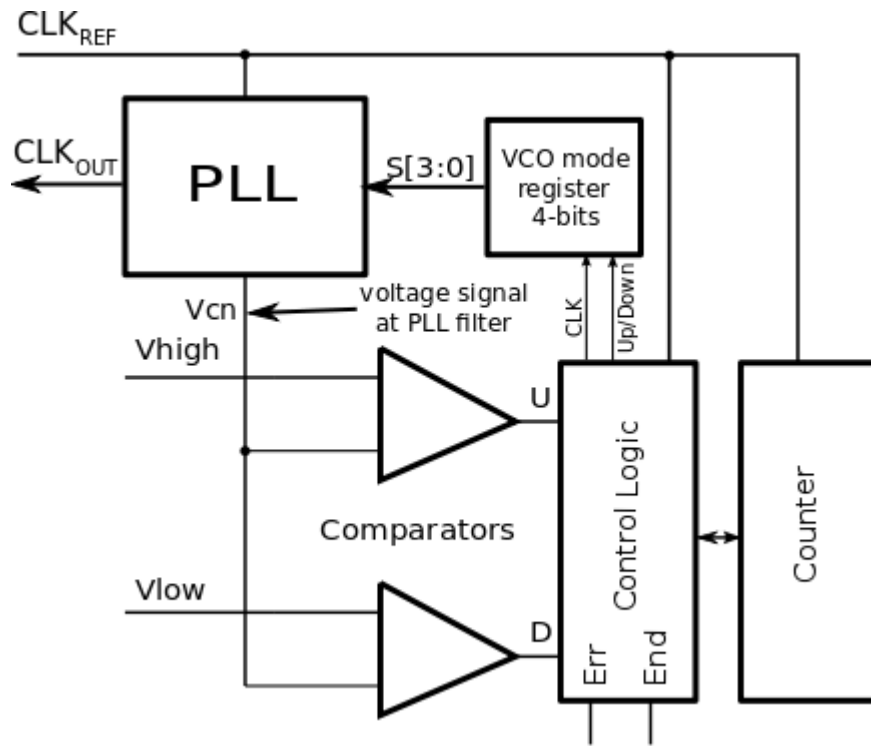
PLL - principle of automatic VCO mode change



- Comparators check whether a voltage signal at the PLL filter (V_{cn}) is greater than V_{high} or lower than V_{low} .
 - If $V_{cn} > V_{high}$ (VCO too slow) for certain period (measured by counter) control logic switches the mode register to faster mode (up).
 - If $V_{cn} < V_{low}$ (VCO too fast) VCO mode register is switched to slower mode (down).
 - When V_{cn} voltage stays between V_{high} and V_{low} the mode is not changed.

PLL prototypes in IBM 130nm


1st prototype

 

- Output frequency range 60 – 520MHz
- Simulated power $\sim 0.2\text{mW}$ @ 500MHz
- Low area 200x160 μm
- Automatically changed VCO modes
- PLL divider by 8 or 10
- Used for 10-bit ADC serialization

Fabricated in mid 2012

2nd prototype


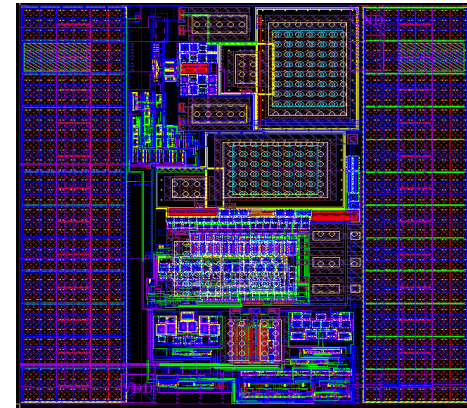


- Output frequency range 8MHz - 3GHz
- Simulated power $\sim 1\text{mW}$ @ 3GHz
- Low area 300x300 μm
- Automatically changed VCO modes
- PLL divider by 6, 8, 10 or 16
- Used for 6(10)-bit ADC serialization

Fabricated at the end of 2012

Design of SLVS interface

  
- Specifications:
 - Architecture
 - Driver – based on Boni paper
 - Receiver – based on self-biased amplifier (Bazes paper)
 - Technology – IBM 130 nm
 - Maximum frequency $\sim 1\text{GHz}$
 - Pitch matched to pads. Driver/receiver integrated with 2 pads (146 μm pitch)





A. Boni, A. Pierazzi, D. Vecchi, LVDS I/O Interface for Gb/s-per-Pin Operation in 0.35 μm CMOS, IEEE J. Solid-State Circuits, vol. 36, no. 4, pp. 706–711, April 2001

M. Bazes, Two Novel Fully Complementary Self-Biased CMOS Differential Amplifiers, IEEE J. Solid-State Circuits, vol. 26, no. 2, pp. 165–168, February 1991.

Design of sampling pulse generator

 


  Generator of sampling pulse converts 50% duty external sampling clock into internal variable width pulse (controlled by I_{bias})




Pulse generator design is based on MOS thyristor delay circuit.

 Layout of 8 channel 10-bit SAR ADC in IBM 130 nm



2200um x 2000um

 Layout of 8 channel prototype of 6-bit SAR ADC in IBM 130 nm



2340 μ m x 1380 μ m

- Introduction and motivation
- ADC testing issues
- Multichannel digitizer in AMS 0.35 μm
- Multichannel SAR ADC in IBM 130 nm
 - SAR architecture considerations
 - Design of 10(6)-bit SAR ADC
 - System level blocks (PLL, SLVS, ...)
- **Preliminary tests of prototypes in IBM 130 nm**
 - **SAR ADC, PLL, SLVS**
- Summary

Prototypes under tests...


10-bit ADC, PLL, SLVS

Prototype of 10-bit ADC

- SAR ADC with segmented DAC
- Scalable frequency (up to ~ 50 MS/s) and power consumption
- Simulated power consumption 1-2mW at 40MS/s
- 146um pitch

Prototype of PLL

 
- Type II PLL with 2nd order filter
- Scalable frequency&power
- Automatically switched VCO frequency range 8MHz – 3GHz
- VCO frequency division by 6, 8, 10 or 16
- Simulated power consumption ~ 1 mW at 3GHz




Preliminary measurements of 10-bit SAR ADC

Static measurements

Transfer function

 

INL/DNL measurements

 


- ADC is alive and works in the whole input signal range
- There are some codes with worse linearity (to be investigated...)

Preliminary measurements of 10-bit SAR ADC

Dynamic measurement at 40Ms/S



Sampling Rate = 40.0 MHz
Input Freq = 3.916 MHz
Harmonics = 10

 SINAD = 57.0 dB
THD = -69.6 dB
SNHR = 57.3 dB
SFDR = 74.6 dB



- First dynamic measurements show that ADC is fully functional and gives reasonable resolution results
- Quantitative measurements in progress...


 
 
Preliminary measurements of 10-bit SAR ADC Maximum sampling frequency



- It is suspected that measured ENOB is limited by the setup

Preliminary measurements of 10-bit SAR ADC


Dynamic measurements – f_{in} scan

   

- For low f_{in} ENOB of ≥ 9.2 was measured
- It is suspected that ENOB decrease with f_{in} is partially/mainly due to setup

Preliminary measurements of 10-bit SAR ADC

 Dynamic measurements – different channels




Results for different channels (only one channel ON during measurements) are similar

Preliminary measurements of 10-bit SAR ADC


Power consumption vs sampling frequency

 - Power measured for 8 ADC channels
- At 40MS/s power consumption is about 1 mW per channel – in agreement with simulations




Preliminary measurements of PLL CLK out vs CLK ref

Manual mode setting


 


Automatic mode setting

 


- PLL measurements have just started (~ 2 days) and are in progress...
- PLL output CLK in frequency range 15MHz-1.2GHz already observed
- There are some gaps between frequency ranges...
- Automatic mode detection looks promising
- SLVS driver works at least up to 1.2 GHz (used for PLL output)

Preliminary measurements of PLL Jitter

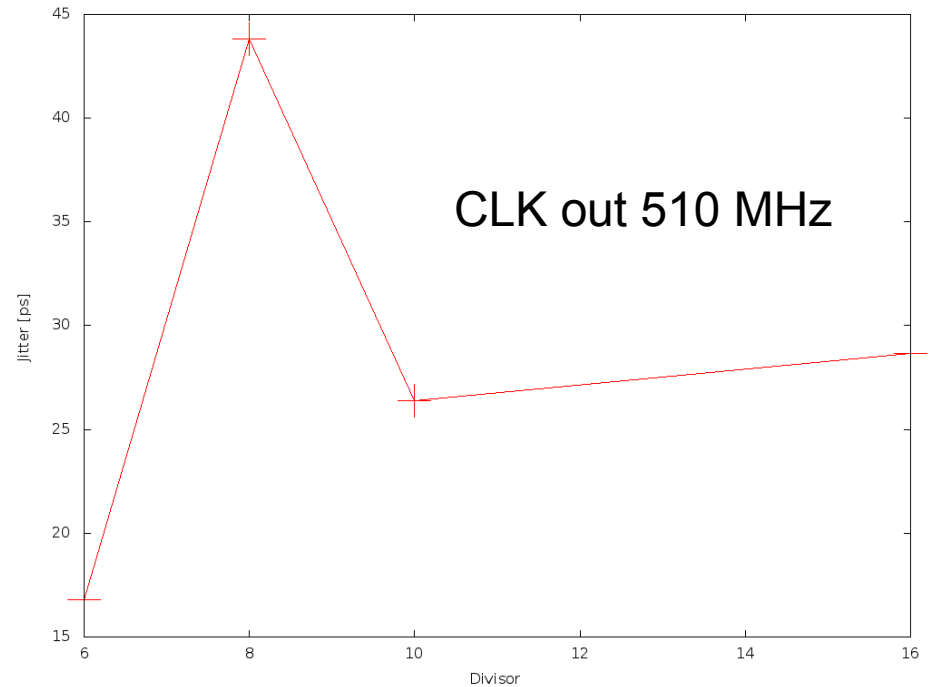 


- Measured jitter at least few times higher than simulated (to be verified...)

 Preliminary measurements of PLL Power consumption




- Power consumption seems to be higher than simulated (to be verified...) but anyway very low

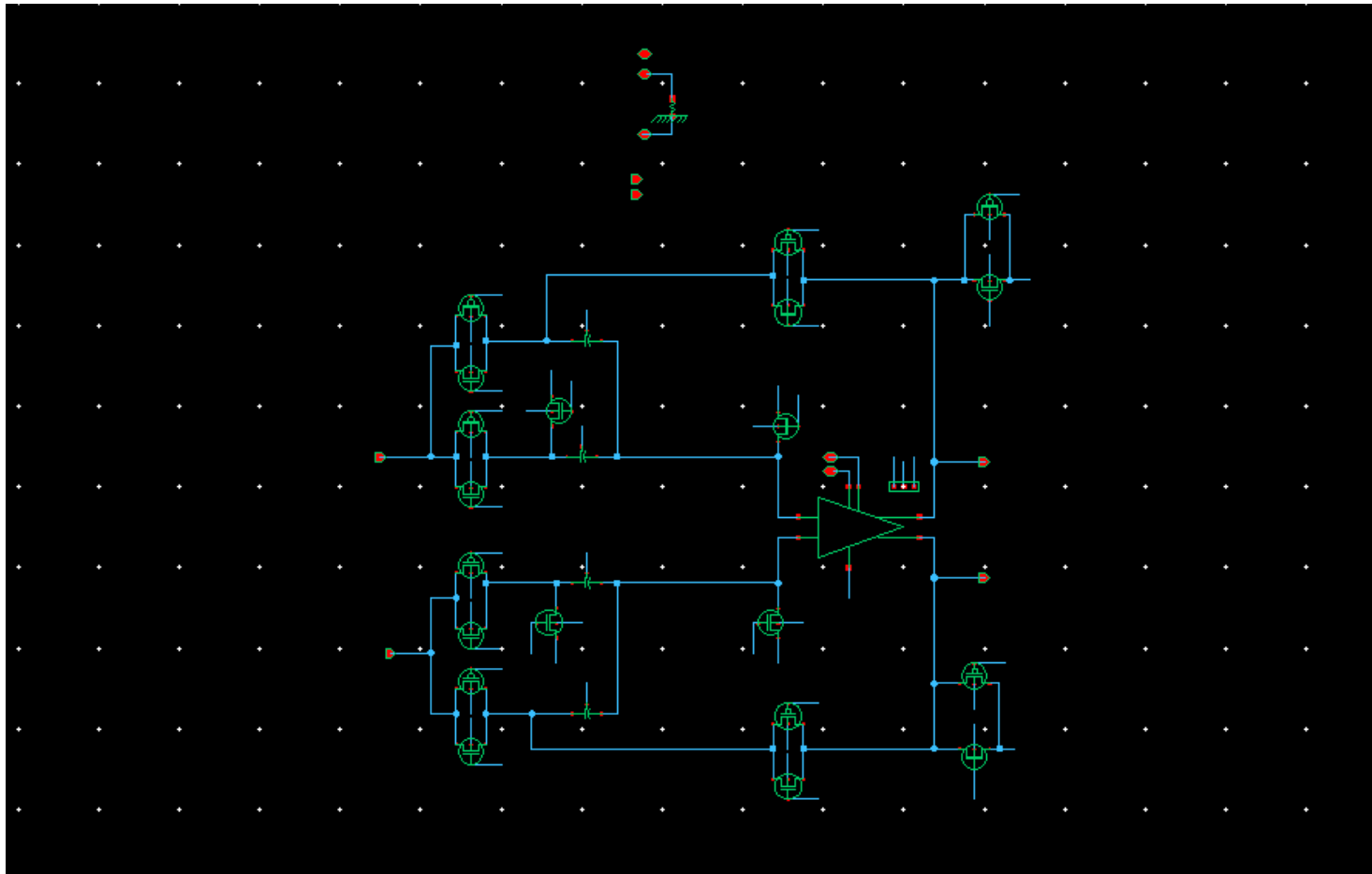Front-end architecture Single-to-Differential converter




Converter has gain of 2, 100-250 μA for 6-bit

Sampling amplifier issues

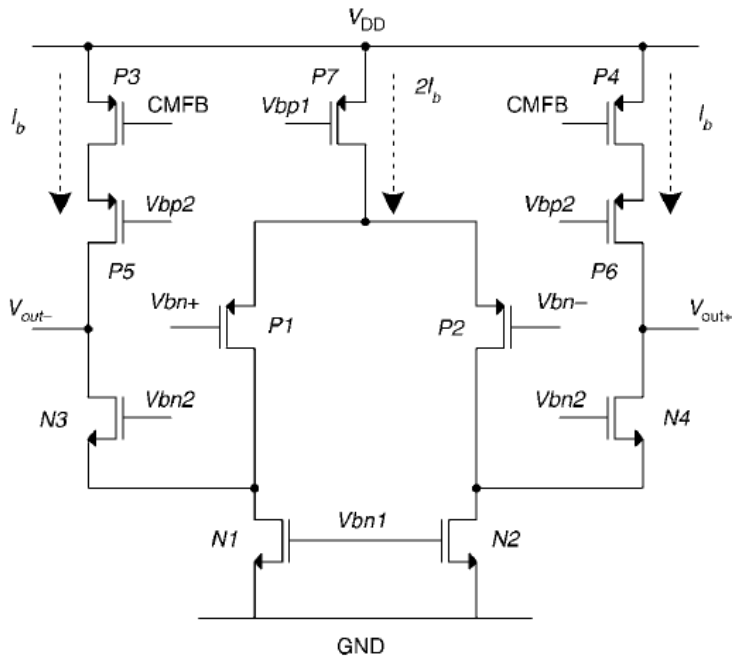

Conventional folded cascode (FC)
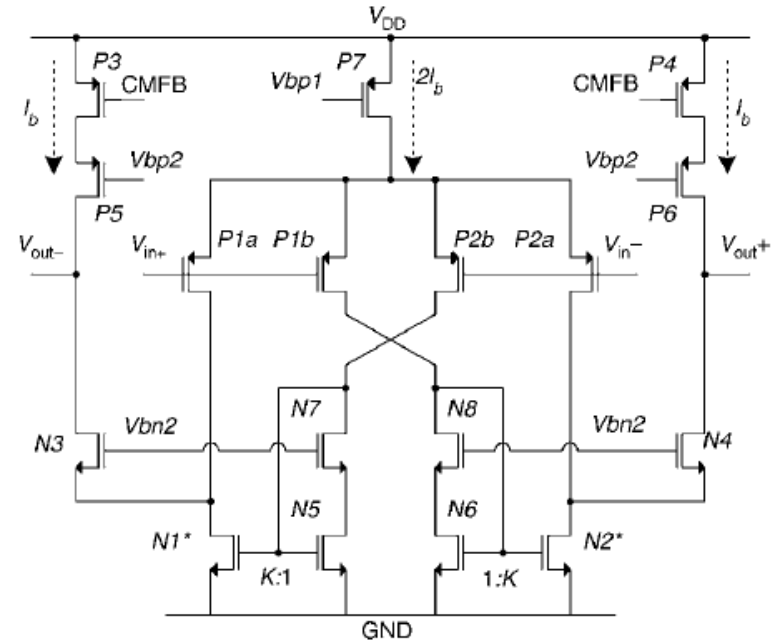
$$Gm_{FC} = gm_{P1}, \quad SR_{FC} = 2I_b / C_L$$



Recycling folded cascode (RFC)

$$Gm_{RFC} = gm_{P1} (1+K), \quad SR_{RFC} = 2KI_b / C_L$$


In 130nm a gain of few hundred may be achieved. For 10-bit accuracy a second stage or a gain boosting is needed

Summary

- Multichannel ADC in AMS 0.35um developed and working well in LumiCal detector module in test beams
- Two very low power multichannel SAR ADCs (10-bit, 6-bit) developed and fabricated in IBM 130 nm
- PLLs, SLVS, etc... developed as well
- First measurements of 10-bit SAR ADC showed that the blocks (ADC in particular) are functional
 - ENOB ~ 9 bits (preliminary and to be verified...)
 - Power consumption $\sim 1\text{mW}@40\text{MHz}$ in agreement with simulations
- Tests of 6-bit ADC should start in May...
- PLL works and looks promising
- SLVS works well up to above 1GHz
- Quantitative tests in progress...

Preliminary measurements of 10-bit ADC

Dynamic measurements – fin scan

 

- ENOB ~ 9.2 was measured

Sampling pulse width

