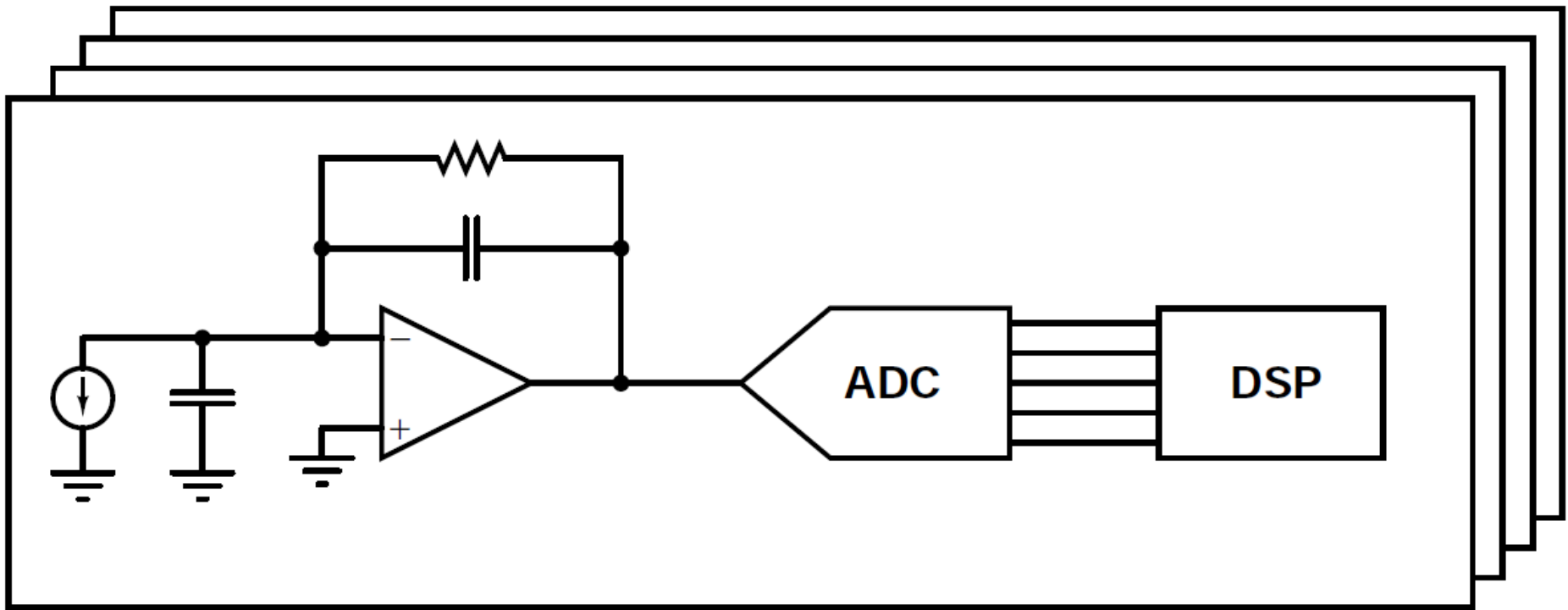




FAST FRONT-END ELECTRONICS FOR SEMICONDUCTOR TRACKING DETECTORS: Trends and Perspectives

Angelo Rivetti
INFN-Sezione di Torino, Italy

An interesting processing chain



- **Digital signal processing** naturally suited to **deep submicron CMOS technologies**.
- Possibility of applying **corrections** before event selection: very interesting to reject **common mode** noise.
- Accuracy of **feature extraction** does **not** depend on the accuracy of the **analog components**.



Super-Altro 16: A Front-End System on Chip for DSP Based Readout of Gaseous Detectors

P. Aspell, M. De Gaspari, E. França, E. García García, L. Musa
IEEE Trans. Nucl. Sci., vol. 60, No. 2, April 2013.

- **Prototype** chip developed for the read-out of the **Linear Collider TPC**.
- Based on the **present readout** of the **ALICE TPC** (PASA+ALTRO chip with DSP on two separate dies).
- **16 channels** with front-end, ADC and digital signal processor.
- Fully differential, 10 bit **pipeline** ADC
- **3 mm²** per channel (active area) in **CMOS 0.13 μm**.
- Key DSP functions: baseline subtraction, signal conditioning, baseline correction and zero-suppression

■ Noise 300 electrons: successful integration of preamp and DSP in the same ASIC

Key S-ALTRO features




S-ALTRO key performance

Gain	12, 15, 19, 27 mV/fC
Peaking time	30, 60, 90, 120 ns
Signal polarity	both
Detector capacitance	4-20 pF
Number of bits	10
Sampling Frequency	10-40 MHz
Power (active)	47 mW/ch
Power (sleep)	0.6 mW/ch

S-ALTRO power break down

PASA	10 mW/ch
ADC (analog)	31.28 mW/ch
ADC (digital)	1.7 mW/ch
DSP	4 mW/ch

 

Low power ADC: some examples




Ref	Technology	Architecture	N of bit	Sampling rate (MS/s)	ENOB	Power (mW)	FOM (Fj/step)
1	90 nm	SAR	9	40	8.23	0.82	68
2	130 nm	SAR	10	50	9.11	0.82	30
3	65 nm	SAR	10	100	9.01	1.13	22
4	90 nm	FLASH+SAR	9	100-200	8.44-8.31	0.75/1.33	34.7
5	90 nm	SAR	10	50	9.5	0.32	9

$$\text{FoM} = P / (2^{\text{ENOB}} F_s)$$

- ADC with 50 MS/s, 9-10 bit resolution and < 1mW of power are now common.
- The renaissance of the SAR ADC.

Traditional SAR ADC (1)

 

- In the **sampling** phase the **top plate** is connected to **VREF** and the bottom plate to **VIN**.
- After sampling the top plate is left **floating** and all the bottom plate are **switched to GND**. Voltage of the top plate is **$VREF - VIN$** .
- The capacitance of the **MSB (128C)** is switched to **VREF**. The voltage of the top plate is **$VREF - VIN + VREF/2$** . If the voltage is **$> VREF$** , the **MSB** is set to **zero** and the bottom plate of the **MSB** capacitors is switched **back to GND**.
- If **$VREF - VIN + VREF/2$** is **smaller** than **VREF**, the bottom plate of the **MSB** is **kept** at **VREF** and the corresponding bit is set to **1**.
- The procedure continues with the other bits.



Traditional SAR ADC (2)



- In conventional SAR ADC:
- Capacitors can be switched back and forth between **VREF** and **GND**: **unnecessary power** consumption in the DAC.
- DAC **capacitors** are usually **over-sized** with respect to the minimum required by noise **boundaries**.
- Logic is synchronous with a master clock: **40 MHz** clock leads to less than **4 MS/sec**.

Performance improvements stem from:

- Reduction of capacitor size
- Modified switching schemes
- Use of asynchronous logic


Modified switching algorithms





A 10-bit 50-MS/s SAR ADC With a Monotonic Capacitor Switching Procedure

Chun-Cheng Liu, *Student Member, IEEE*, Soon-Jyh Chang, *Member, IEEE*,
Guan-Ying Huang, *Student Member, IEEE*, and Ying-Zu Lin, *Student Member, IEEE*

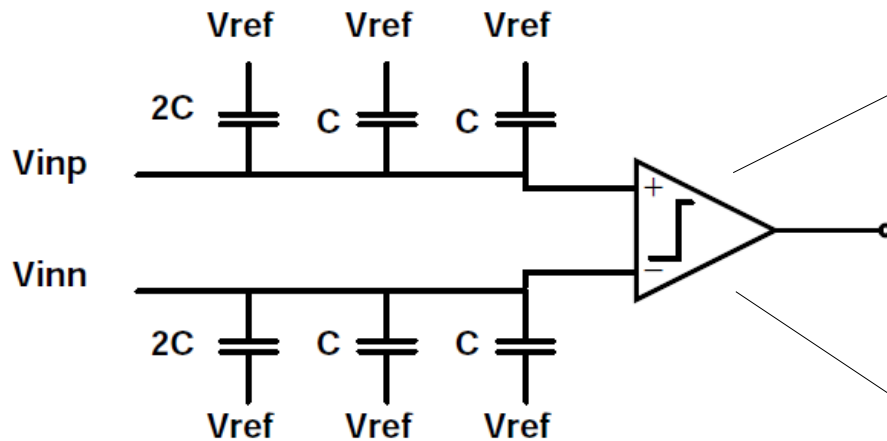Sampling & first comparison **If $V_{inp} > V_{inn}$**



If $V_{inp} < V_{inn}$

  

- Modern ADC are always **fully differential**.
- A **front-end** with fully differential outputs is necessary.
- Alternative switching schemes can save up to **98% of the DAC power**

Capacitor in SAR ADC




■ Noise limits:

$$V_{LSB} = \frac{V_{FS}}{2^N} \quad E_q = \frac{V_{LSB}}{\sqrt{12}} \quad \frac{kT}{C_{DAC}} = \frac{V_{FS}^2}{12 \cdot 2^{2N}}$$

Number of bits	Total DAC capacitance	LSB capacitance
5	$5.09 \cdot 10^{-17}$	$1.59 \cdot 10^{-18}$
6	$2.03 \cdot 10^{-16}$	$3.18 \cdot 10^{-18}$
7	$8.14 \cdot 10^{-16}$	$6.36 \cdot 10^{-18}$
8	$3.26 \cdot 10^{-15}$	$1.27 \cdot 10^{-17}$
9	$1.30 \cdot 10^{-14}$	$2.54 \cdot 10^{-17}$
10	$5.2 \cdot 10^{-14}$	$5.08 \cdot 10^{-17}$
11	$2.08 \cdot 10^{-13}$	$1.02 \cdot 10^{-16}$
12	$8.33 \cdot 10^{-13}$	$2.03 \cdot 10^{-16}$

- DAC capacitance can be very small
- Practical limit comes from matching rather than noise
- LSB capacitance as low as 1 fF already used.

Example of asynchronous logic

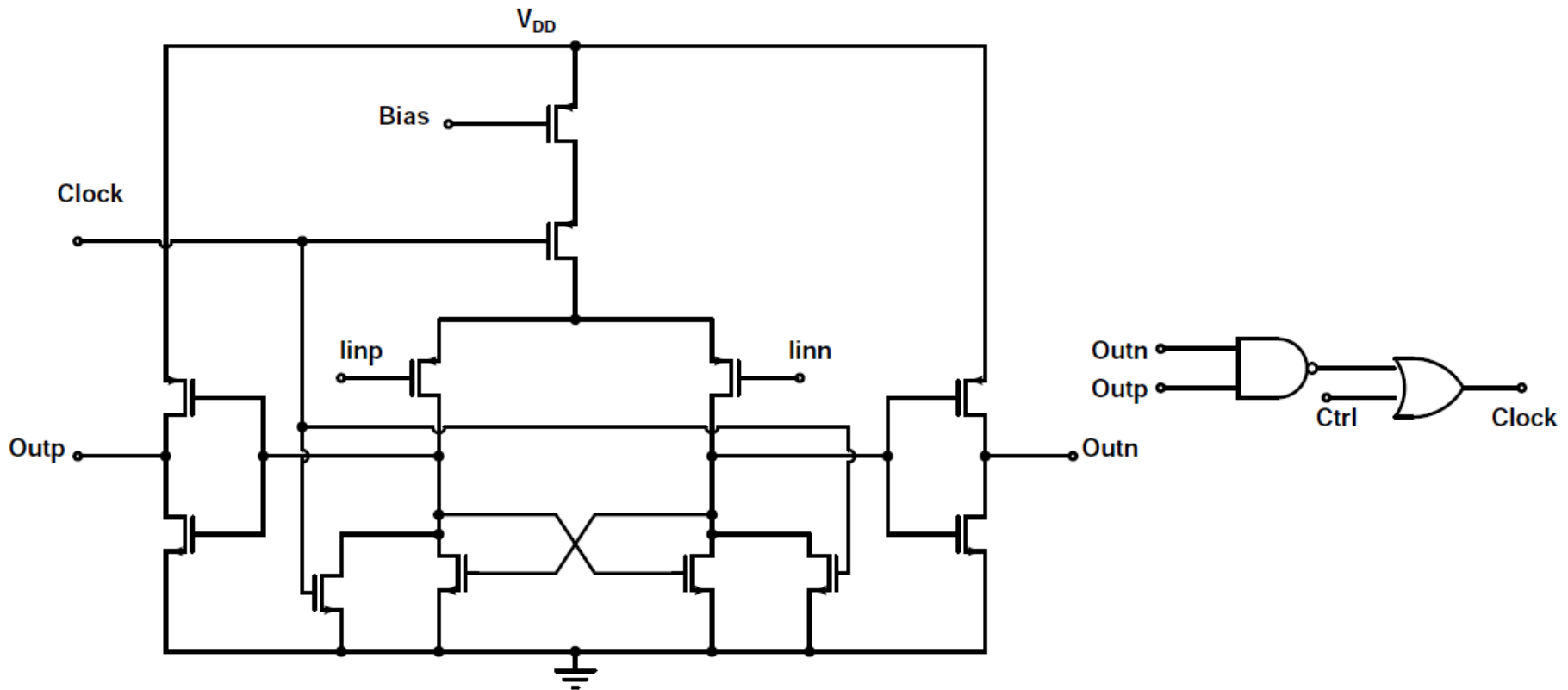



- Clock speed defined by the maximum **toggle frequency** of the **comparator**.
- Asynchronous logic design requires analog-grade simulations....
- In a **plain SAR**, clock frequency above **500 MHz** necessary to achieve **50 MS/s** of conversion speed.
- Higher speed achievable with **hybrid** architectures.

Recent developments in HEP (1)



From M. Idizik et al., **Multichannel ADC for physics applications**
<https://indico.cern.ch/conferenceDisplay.py?confId=225551>

Design of 6-bit SAR ADC in IBM 130 nm

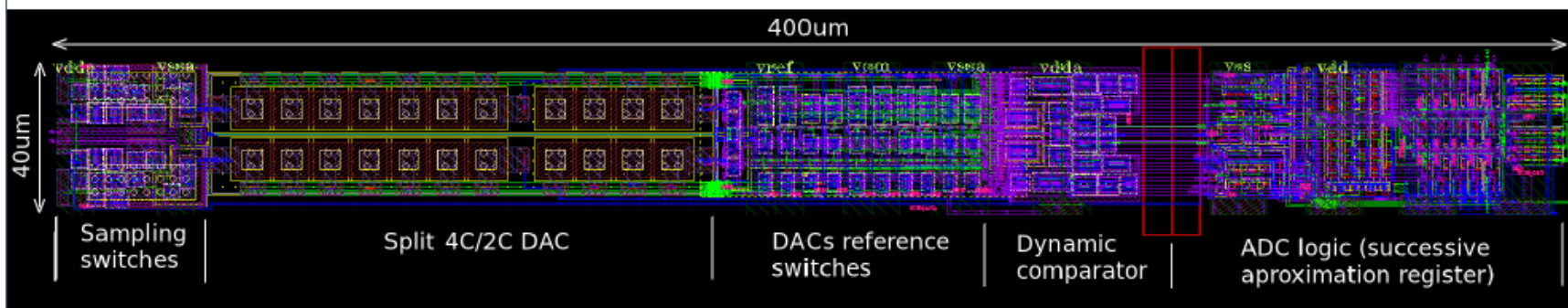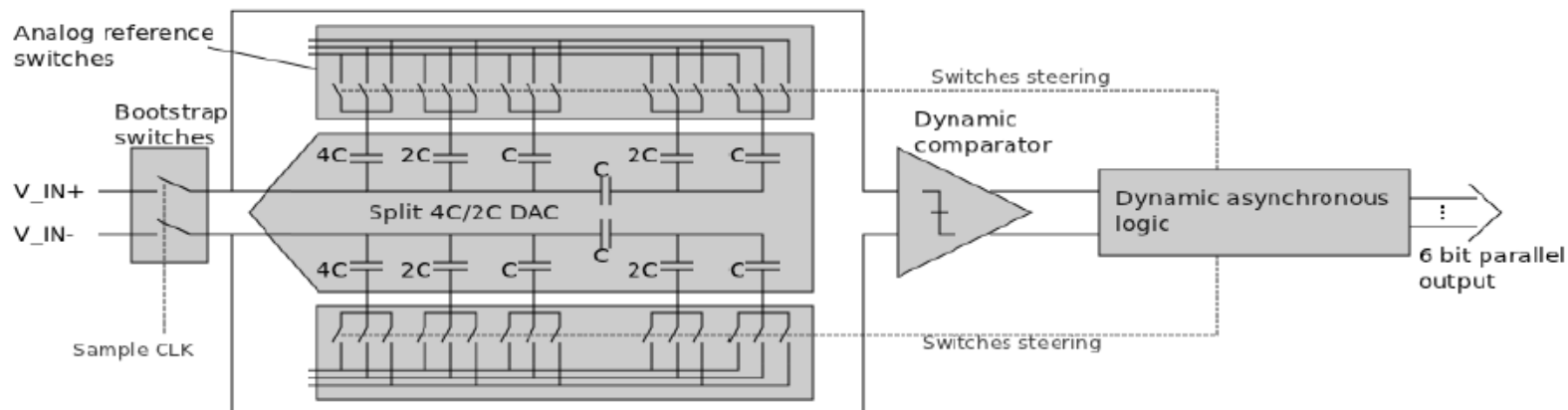

- Single channel: 40um x 400um (area 0.016 mm²)
- Custom capacitor p-cell layout done to obtain 40um pitch



Prototypes under tests... 10-bit ADC, PLL, SLVS

Tecnology: 0.13 μm CMOS
600 μm x 146 μm x 10 bit


Prototype of 10-bit ADC

- SAR ADC with segmented DAC
- Scalable frequency (up to ~ 50 MS/s) and power consumption
- Simulated power consumption 1-2mW at 40MS/s
- 146 μm pitch

Prototype of PLL

- Type II PLL with 2nd order filter
- Scalable frequency & power
- Automatically switched VCO frequency range 8MHz – 3GHz
- VCO frequency division by 6, 8, 10 or 16
- Simulated power consumption ~ 1 mW at 3GHz

 From M. Idizik et al., **Multichannel ADC for physics applications**
<https://indico.cern.ch/conferenceDisplay.py?confId=225551>



Recent developments in HEP (3)




Nuclear Instruments and Methods in Physics Research A ■ (■■■■) ■■■-■■■

A 10 MS/s 8-bit charge-redistribution ADC for hybrid pixel applications in 65 nm CMOS ☆

Tetsuichi Kishishita*, Tomasz Hemperek, Hans Krüger, Manuel Koch, Leonard Germic, Norbert Wermes

University of Bonn, Physikalisches Institut, Nussallee 12, 53115 Bonn, Germany

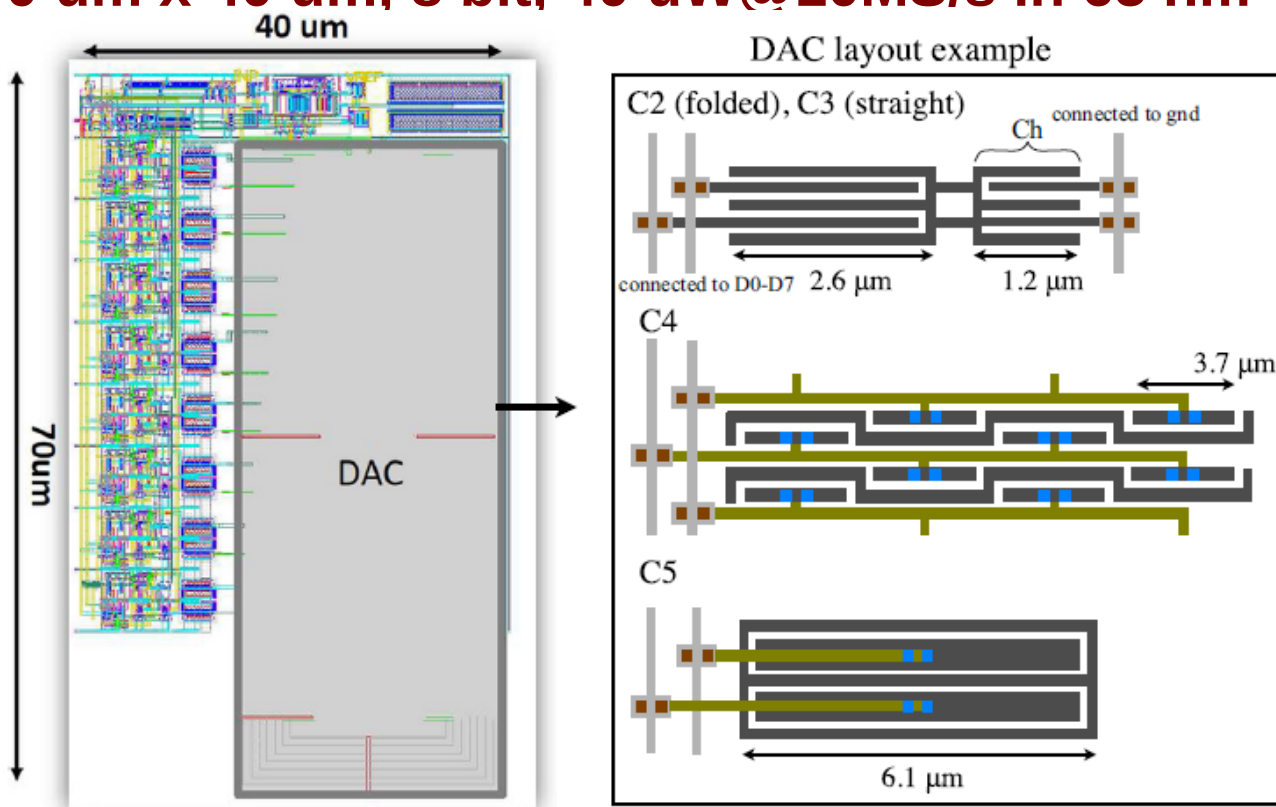70 μm x 40 μm , 8 bit, 40 μW @10MS/s in 65 nm





A first outlook




- Thanks to the spectacular progress in ADCs, in a 0.13 um technology, full sampling can be feasible at very low power
- For 10 bit resolution and 3 mW of power per channel (excluding the front-end).
- The most complex part of the DSP can be triggered only if there is a suspicion of an event, saving further power.
- Power could be cut further by going to more aggressive technologies
- In case of power cycling, average power consumption becomes very small
- More front-end chips are likely to be designed in the near future along this line.

What about timing?



Interest is growing around **tracking** detectors with improved **time-tagging** capabilities:


- **Free running** detectors with **data push** architectures or with high pile-up
 - Time resolution $O(\text{ns})$.
 - Can be derived from a **clock**: (20 ns clock provides 5.7 ns rms)
 - In case of analog readout with **waveform sampling**, can be improved with **interpolation**. Time resolution of 5-10% of the peaking time easily achievable.
- **Specialized** tracking detectors with very good time resolution (<100 ps)
 - Require **dedicated** high resolution **timing channels**.

 


TDC growth



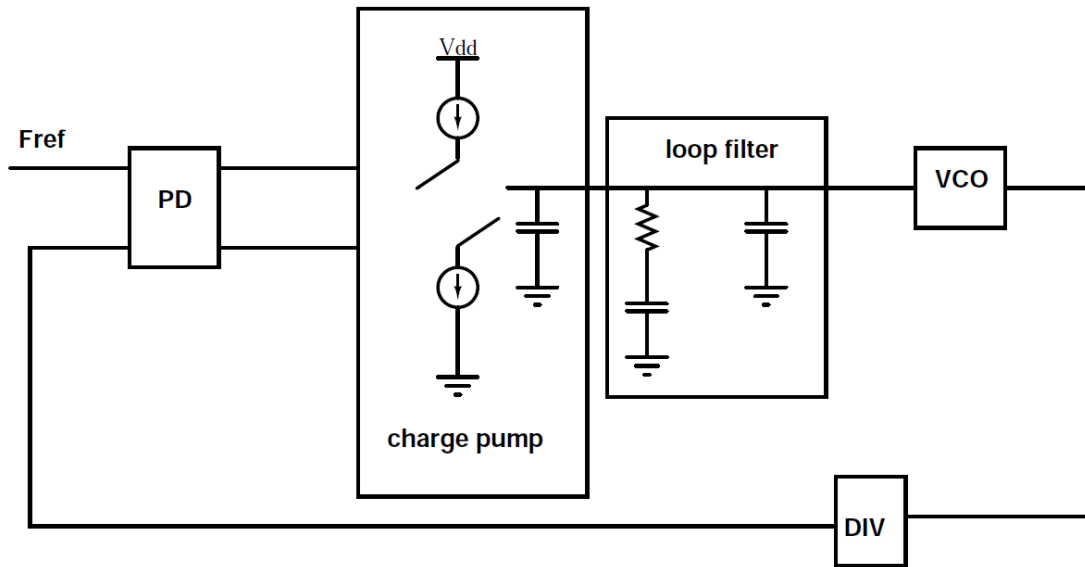Due to the interest in ALL Digital PLL (**ADPLL**), **TDC** left the niche market of instrumentation (HEP, range finding, testing) to become **more general purpose** components, with an significant increase on the number of published papers in the recent years.



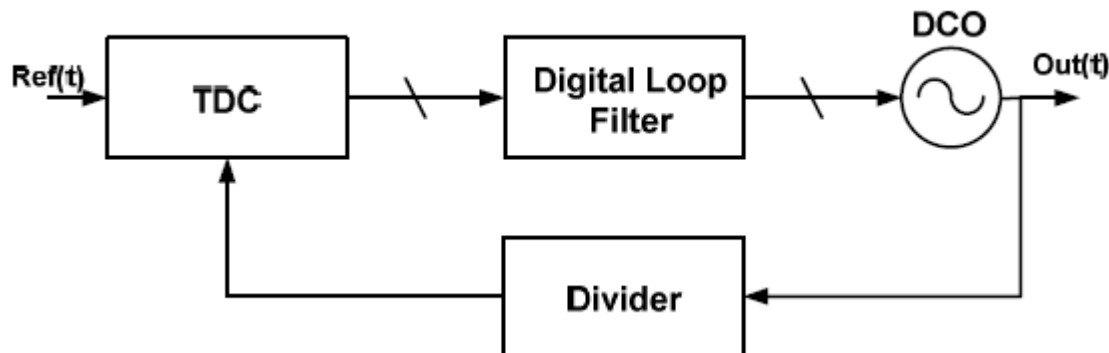Conventional analog PLL
Needs an **analog filter**



ALL Digital PLL
Phase difference measured
with a **TDC**



Some recent TDC designs




Ref	Technology	Architecture	Resolution (ps)	Sampling rate (MS/s)	Range (ns)	Power (mW)	Area
1	130 nm	GRO	1	50	12	2.2-21	0.04
2	130 nm	Vernier-ring	8	15	32	7.5	0.26
3	90 nm	Passive inter.	4.7	180	0.6	3.6	0.02
4	90 nm	Delay line	20	26	0.64	6.9	0.01
5	65 nm	2D delay line	4.8	50	< 0.6	1.7	0.02
6	90	Time Amp.	1.25	10	0.64	3	0.6
7	90	Vernier+GRO	3.2	25-100	40	3.6-4.5	0.027

- TDCs are now reaching the sub-ps resolution
- Many different architectures
- Dynamic range low in many high resolution TDC

Limits on timing: jitter



 
- For a total signal rise time of **2 ns**, a **10 ps** resolution can be reached with a noise of **200** electrons and a signal of **6 fC** or a signal of **2.5 fC** and a noise of **80** electrons.
- Peaking time should match **detector collection time**.






$$\sigma_t = \frac{\sigma_v}{\frac{dV}{dt}}$$

■ ENC=200
◆ ENC=80

Some time extraction methods

 


Leading edge timing

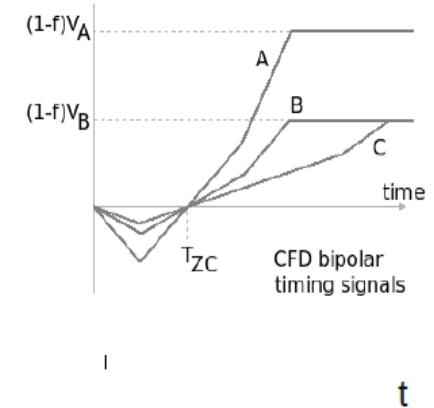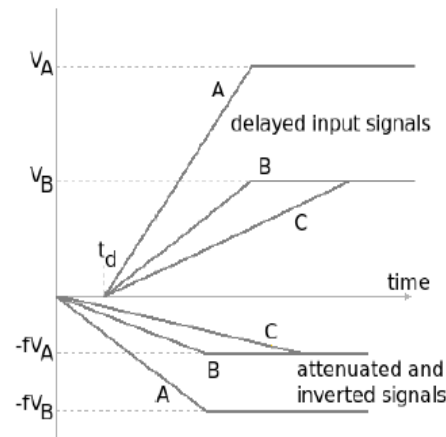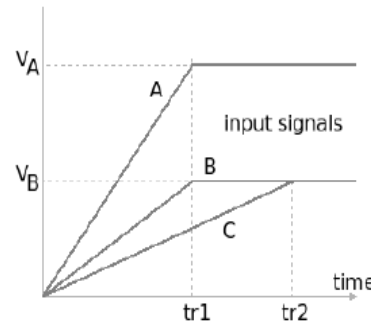

$t_d > t_r$, amplitude compensation only
 
$$fV_0 = \frac{t - t_d}{t_r} V_0 \quad t_{z_c} = ft_r + t_d$$



High speed waveform sampling (>GHz)

$t_d > t_r$, amplitude and rise time compensation

$$f \frac{t}{t_r} V_0 = \frac{t - t_d}{t_r} V_0 \quad t_{z_c} = \frac{t_d}{1 - f}$$



Constant fraction timing




The NA62 Giga-Tracker (GTK)



 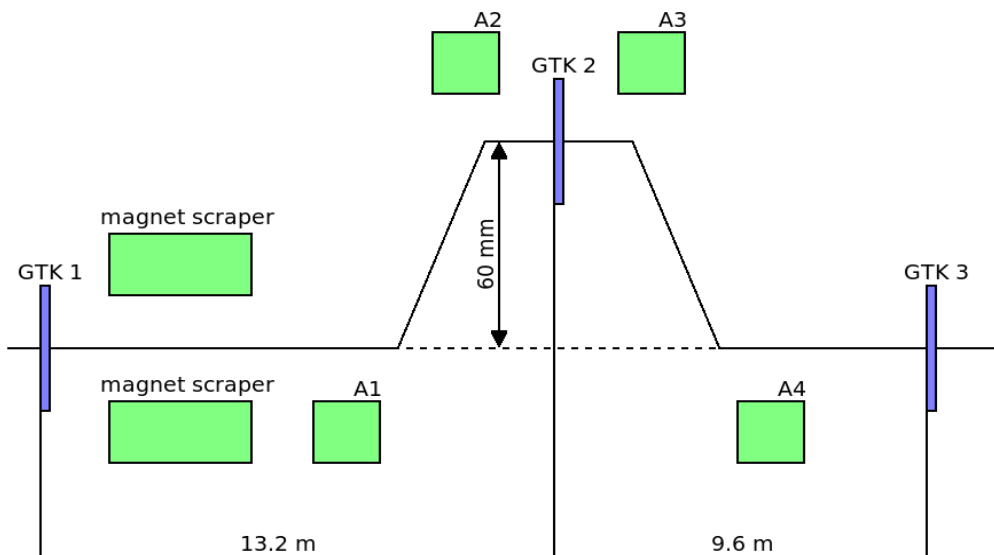- State of the art in **high granularity**, **high time resolution** trackers.
- Pixel size of **300 μm x 300 μm** targeting **100 ps rms** resolution.
- Sensor: standard hybrid pixels **200 μm thick**.
- **Leading edge** discriminator + **ToT correction** chosen as the timing extraction method.



12 mm

 

- 1800 pixels organized in a 45 x 40 matrix
- Equivalent of 720 independent TDC channels with 97 ps binning
- TDC based on DLL.
- 4 x 3.2 Gbit/sec serializer
- CMOS 0.13 μm

Design submitted to the foundry

A. Kluge et al, The TDCpix readout ASIC: A 75 ps resolution timing front-end for the NA62 Gigatracker hybrid pixel detector.


Nuclear Instr. Meth. A , available online 10 July 2013
<http://dx.doi.org/10.1016/j.nima.2013.06.089>

GTK prototype results




Jitter on the leading edge. Laser with 300 V sensor bias

 Resolution obtained in beam tests as a function of the sensor bias. ToT corrections applied.



 me resolution dependence on sensor V_{bias}



Charge injection with laser
300 V detector bias

Resolution worsening primarily due to distortion of the weighting field at the pixel edges, with an additional contribution from charge straggling.

Plots courtesy of NA62/GTK project

Same charge, but different signal shapes

Timing with constant fraction




- Time walk is a **deterministic effect** and in principle it can be corrected for.
- However, signal shape variations imply **change** in the threshold crossing point even for the **same charge**.
- A constant fraction discriminator is immune to rise time variation **only if** the signal has a **linear rising edge**.
- How much is a CFD resistant to shape variations in more realistic cases?


$$\frac{t - t_d}{\tau} e^{-\frac{t-t_d}{\tau}} - f \frac{t}{\tau} e^{-\frac{t}{\tau}}$$

$$t_{zc} = \frac{t_d e^{t_d/\tau}}{e^{t_d/\tau} - f}$$

Amplitude

 

Amplitude


 




CFD simulation studies



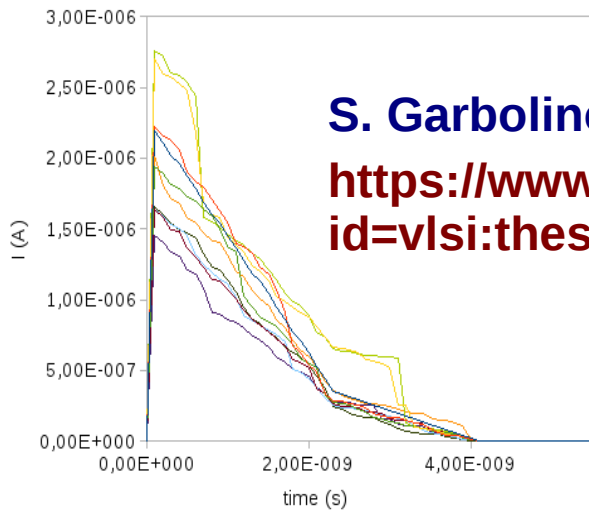 
Assume silicon sensor
200 um thick and minimum
ionizing particles.



S. Garbolino, PhD thesis

<https://www.to.infn.it/doku.php?id=vlsi:theses:archive>

Schematic results			
Process corner	RMS Jitter @ 1MIP (ps)	Error due to signal variations (ps RMS)	Time resolution (ps RMS)
Typical mean	40	20	53
+1.5 σ	45	27	48
+3 σ	52	23	59
-1.5 σ	38	23	52
-3 σ	38	21	67
Layout results			
Process corner	RMS Jitter @ 1MIP (ps)	Error due to signal variations (ps RMS)	Time resolution (ps RMS)
Typical mean	47	27	68
+1.5 σ	50	31	55
+3 σ	59	30	86
-1.5 σ	44	27	65
-3 σ	45	24	95

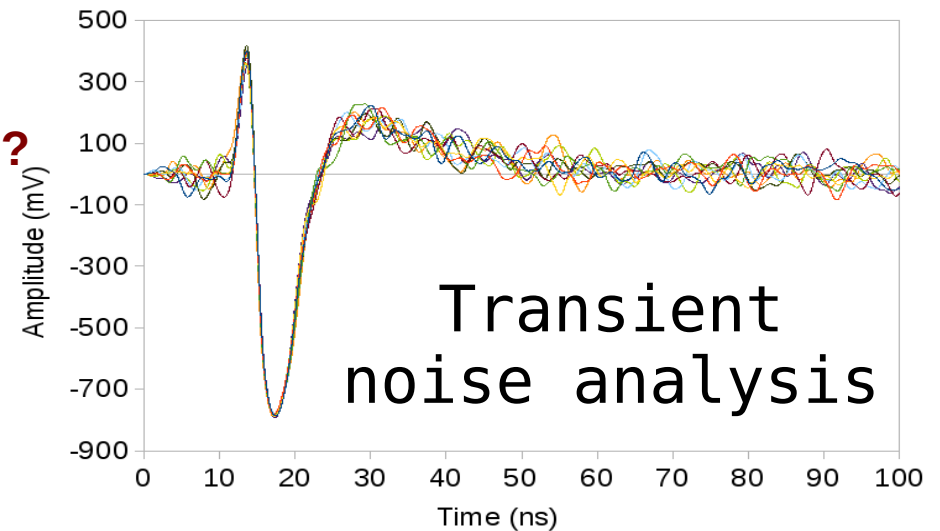

Some considerations on CFD

- Constant Fraction Discriminators can be effectively implemented in DSM technologies with moderate area and power.

S. Martoiu et al,
IEEE NSS-Mic 2008



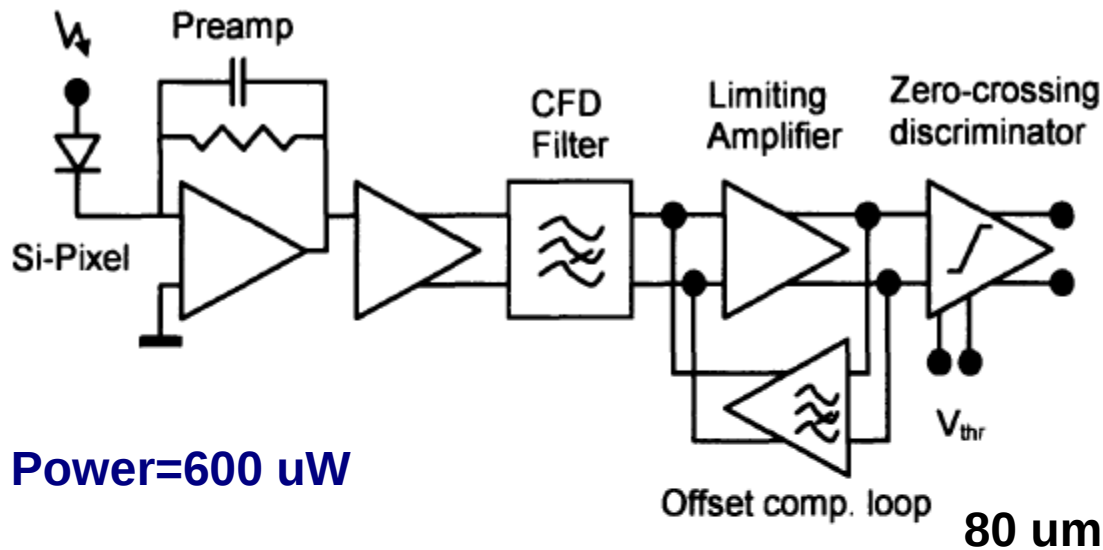




Fig. 1. Architecture of the front-end circuit.

 

 - CFD are effective in reducing effects relating to signal shape variations, but they are not the magic toolbox for perfect timing.
- CFD rely on linear filtering and performance can be easily corrupted if nominal pulse shape is distorted (layout, substrate noise, etc...)



Pixel with embedded TDC

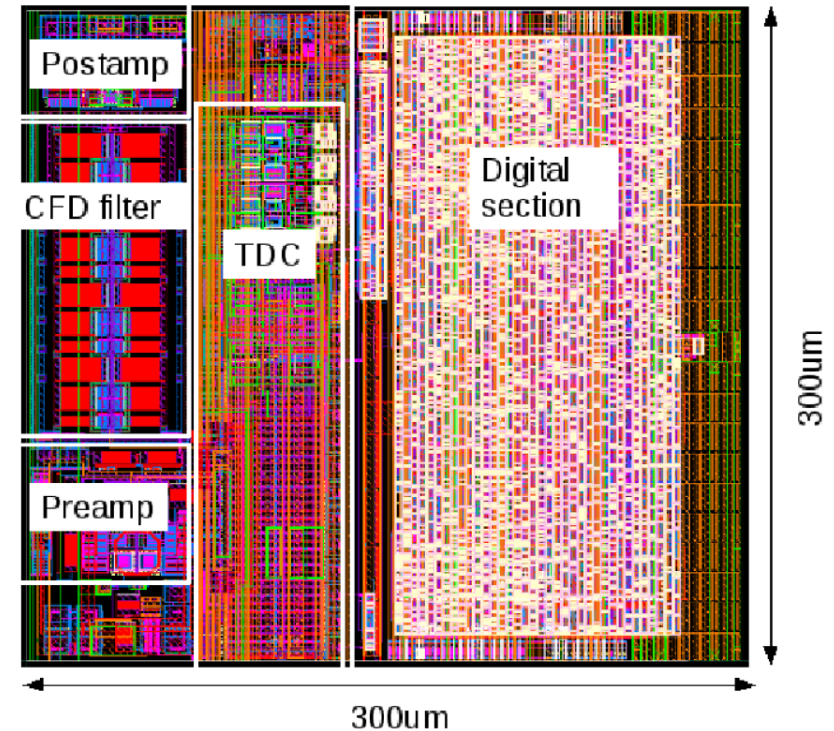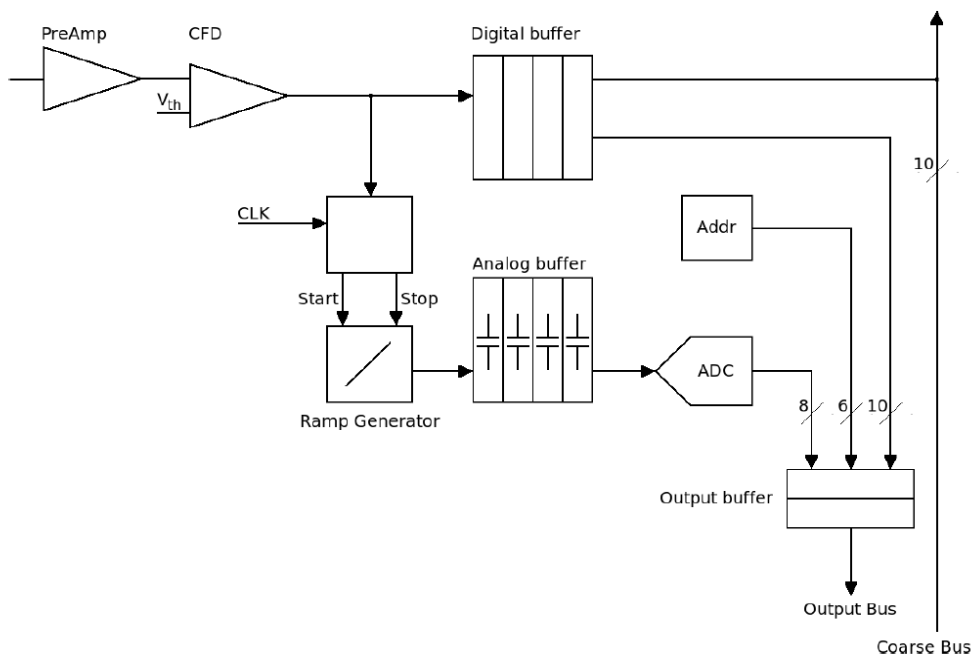

- Preamp. CFD, TDC incorporated on 300 um x 300 um
- Power 1mW/ch
- 250 kHz rate capability
- Major issue: preserve the CFD from digital noise aggression
- Development triggered by na62
- Did not reach maturity on time for an early use in the experiment, but very useful playground for other developments.

Example of time-based front-end



M. Rolo, Integrated Circuit Design for Time-of-Flight PET with Silicon Photomultiplier.

8th "Trento" Workshop on Advanced Silicon Radiation Detectors, Feb. 2013

<https://indico.cern.ch/contributionDisplay.py?sessionId=7&contribId=38&confId=226647>



Combined TOF-PET (200 ps time resolution), ultrasound imaging and endoscopic biopsy

PET components:

- dSiPM/crystal endoscopic probe
- aSiPM/crystal external plate

© DESY / Stuhmann



TOF-PET ASIC specifications




Parameter	Value
Number of channels	64
Clock frequency	80 – 160 MHz
Dynamic range of input charge	300 pC
SNR ($Q_{in} = 100$ fC)	> 20-25 dB
Amplifier noise (in total jitter)	< 25 ps (FWHM)
TDC time binning	50 ps
Coarse gain	$G_0, G_0/2, G_0/4$
Max. channel hit rate	100 kHz
Max. output data rate	320 Mb/s (640 w/ DDR)
Channel masking	programmable
SiPM fine gain adjustment	500 mV (5 bits)
SiPM	up to 320pF term. cap., 2MHz DCR
Calibration BIST	internal gen. pulse, 6-bit prog. amplitude
Power	< 10 mW per channel

How these specs impact the choice
of the readout chip architecture?






ASIC architecture

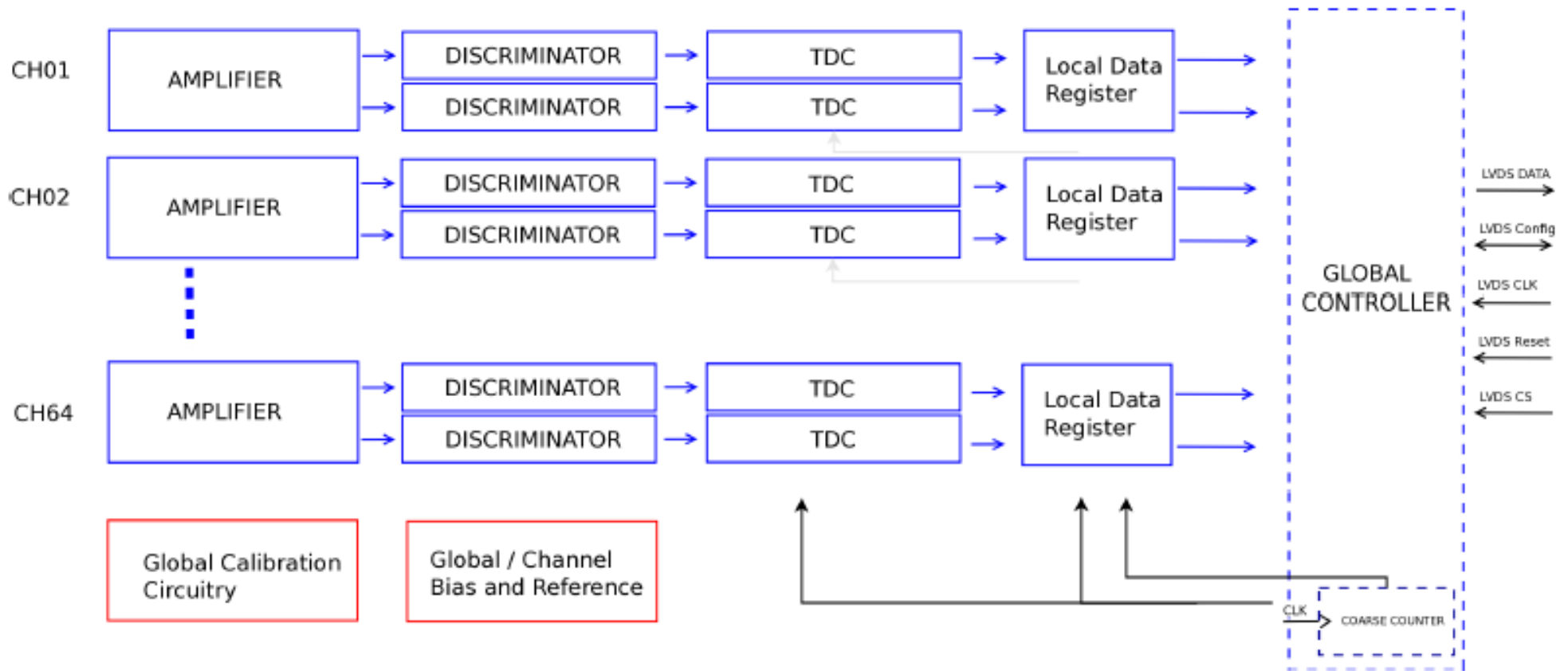




One of the test PCB

 

Other test PCBs developed at LIP (Lisbon) to accommodate packaged dies.



Some performance example

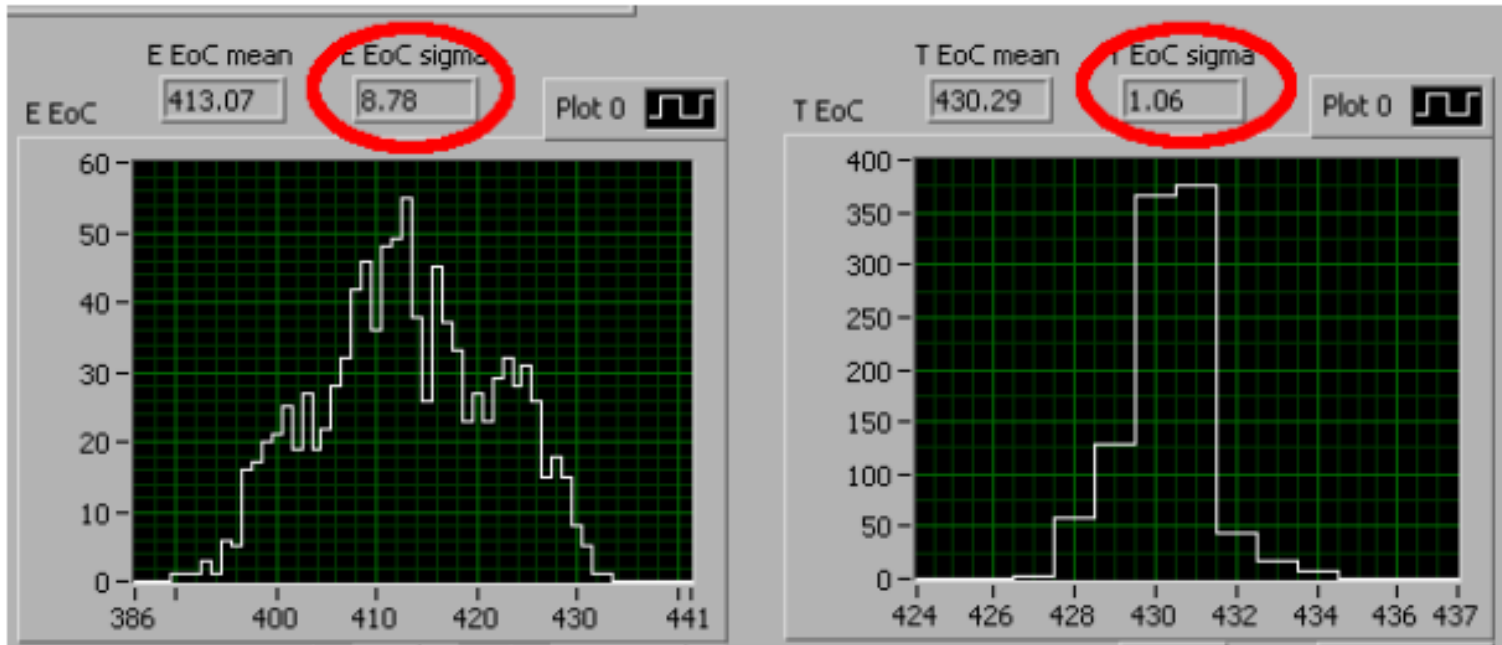

- TP jitter + FE jitter + TDC noise \approx 60 ps FWHM, using the id of the TDC buffer.



More on fast ADCs



26.4 A 3.1mW 8b 1.2GS/s Single-Channel Asynchronous SAR ADC with Alternate Comparators for Enhanced Speed in 32nm Digital SOI CMOS

Lukas Kull^{1,2}, Thomas Toifl¹, Martin Schmatz¹, Pier Andrea Francese¹, Christian Menolfi¹, Matthias Braendli¹, Marcel Kossel¹, Thomas Morf¹, Toke Meyer Andersen¹, Yusuf Leblebici²

¹IBM Research, Rüschlikon, Switzerland, ²EPFL, Lausanne, Switzerland

Specifications	[1]	[2]	[3]	[4]	[5]	This work		
Architecture	SAR	Ti-SAR	Ti-SAR	SAR	SAR	SAR		
CMOS Technology (nm)	65	65	65	28	40	32		
Resolution (bits)	8	6	8	8	6	8		
Supply Voltage (V)	1.2	1.2	1.0	1.0	1.0	1.0	1.1	0.9
SNDR near Nyquist (dB)	44.5	31.5	42.75	43.3	30.5	39.3	39.3	38.8
Sampling Speed (GHz)	0.4	1	1	0.75	1.25	1.2	1.3	1.0
Speed per Channel (GHz)	0.4	0.5	0.5	0.75	1.25	1.2	1.3	1.0
Power (mW)	4.0	6.7	3.8	4.5	6.08	3.1	4.2	2.0
FOM (fJ/conf step)	73	210	24	41	178	34	43	28
Area (mm ²)	0.024	0.11	0.013	0.004	0.013	0.0015		
Area for 64GS/s (mm ²)	3.8	7.0	8.3	0.26	0.67	0.080	0.074	0.096



A 9-bit 50MS/s Asynchronous SAR ADC in 28nm CMOS

Tuan-Vu Cao, Snorre Aunet, Trond Ytterdal

Circuits and Systems group, Department of Electronics and Telecommunications


Norwegian University of Science and Technology, Norway

Emails: {vu.tuan.cao, snorre.aunet, trond.ytterdal}@iet.ntnu.no

- Simulations indicate that 9 bit and 50 MS/s are achievable with 45 μ W of power!
- Digitization and basic DSP functions at 50 MS/s could be achieved with 150 μ W of power per channel (excluding the very front-end part).



Industry vs HEP

 

- MPW: 15 mm² in 28 nm: 156 000 (standard), 189 000 SOI
 - 1 mm²: 15 000 euros
- <http://cmp.imag.fr/products/ic/?p=prices>