



65nm activities in Turin (short status report)

Luca Pacher

INFN and University of Turin

Turin, 14/05/2013

pacher@to.infn.it


Design guidelines

- we want to design and test a complete front-end analog chain in 65 nm
- try to explore innovative options
 - fast and low threshold synchronous comparator (discrete time)
 - zero suppressed charge encoding using SAR-ADC
- make a comparison with more 'standard' approaches
 - asynchronous comparator (continuous time)
 - Time over Threshold (ToT) technique
- area
 - most recent CMS Phase-2 pixel size guess: **25 μm x 100 μm**
 - assume **25 μm x 50 μm** for the analog part
- power consumption
 - realistic constraints for the total analog power consumption becomes essential to fix DC bias currents
 - assume a total power consumption per unit area $< 0.4 \text{ W/cm}^2$
 - $< 10 \text{ } \mu\text{W}$ /pixel (50% analog + 50% digital... is this realistic?)
 - $< 5 \text{ } \mu\text{W}$ /pixel for the analog part \rightarrow $\sim 4 \text{ } \mu\text{A}$ total bias current (static current) !
 - $\sim 1 \text{ } \mu\text{A}$ per branch work fine (OK with weak and moderate inversion operating transistors)
 - the power contribution from a 5-bit SAR-ADC per pixel should not be a problem if a zero suppression scheme is adopted (= decide and digitize \rightarrow ~ 1 conversion cycle every 10 μs , 100 kHz)
- our goal: plan a submission before the end of 2013


Comparator designs

- we want to explore two different comparator designs
 - continuous time approach
 - discrete time (track-and-latch) @ 40 MHz clock (BX) → now optimizing the previous design
- both designs would employ self offset compensation techniques (autozeroing)
 - usage of input + output offset storage [1,2]
 - local trimming with DACs is no more required → no more configuration registers and SEU protections
 - we are considering to do the offset compensation for each bunch crossing
- try to exploit all transistor options available with the 65 nm PDK (high V_t , low V_t transistors etc.)

input + output offset storage

 

output offset storage

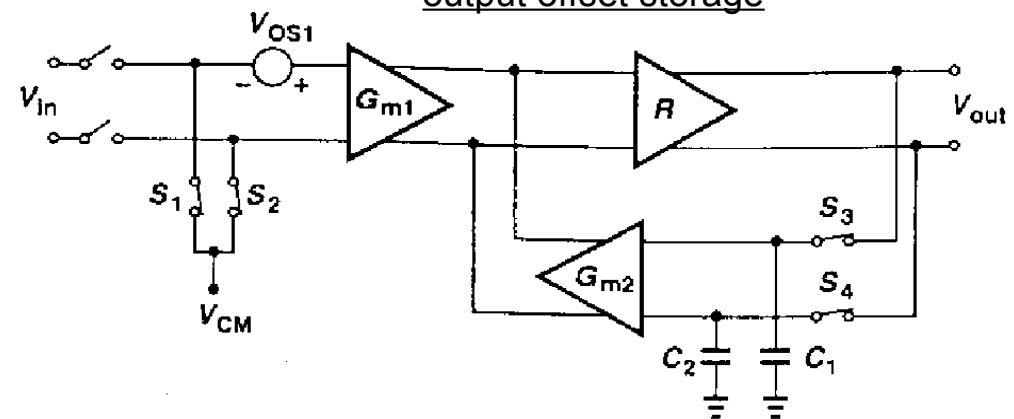


[1] F. Brianti, A. Manstretta, G. Torelli, *High Speed Autozeroed CMOS Comparator for Multistep A/D Conversion*

[2] A. Rivetti, G. Anelli, G. Mazza and F. Rotondo, *A Low-Power 10-bit ADC in a 0.25- μ m CMOS: Design Considerations and Test Results*

Very front-end preliminary studies

- preliminary studies on the very front-end stage are required to get a realistic estimation of the **total RMS noise** fed to the comparator
- getting started exercises with the **very front-end input stage** (E.Monteil – master thesis)
 - deep n-well nmos input device + cascode stage + ideal CR-RC2 shaper (12.5 ns peaking time)
 - optionally g_m enhancement using current splitting techniques
 - systematic studies on ENC by varying the input device aspect ratio (100 fF input capacitance)
 - compare simulation results with standard theoretical predictions [1,2]

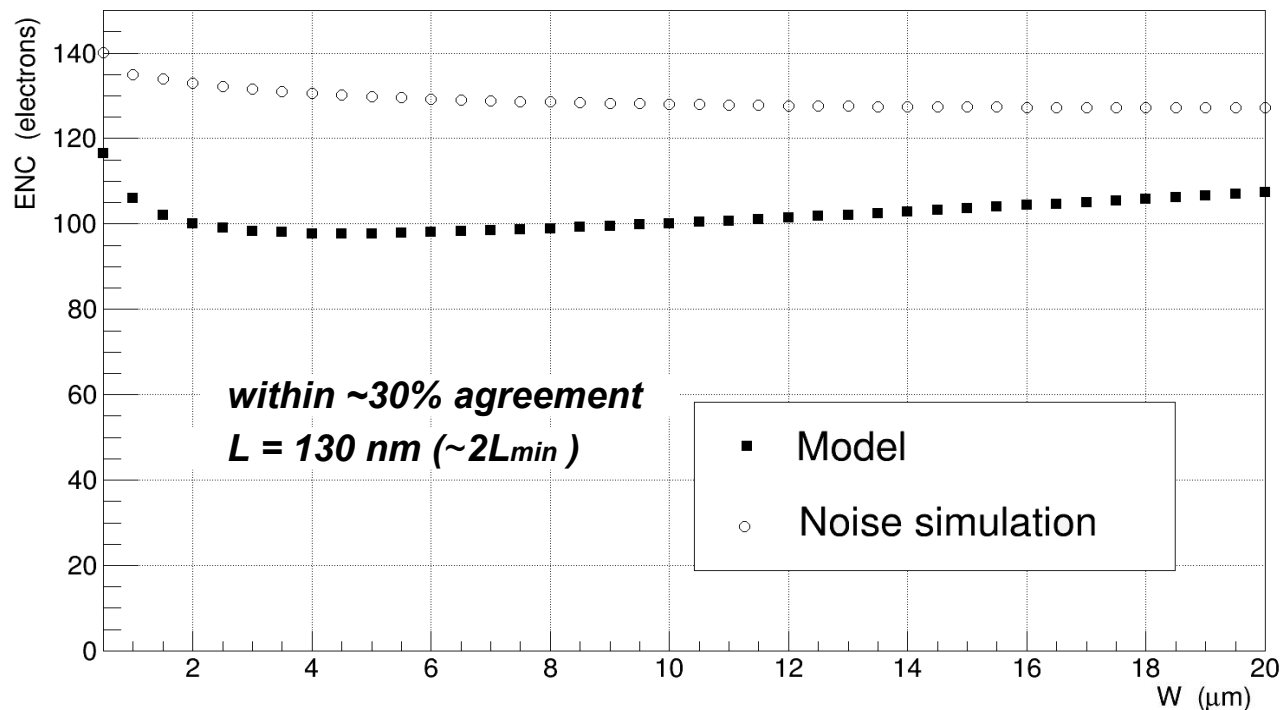

[1] C.C. Enz F. Krummenacher and E.A. Vittoz, *An Analytical MOS Transistor Model Valid in All Regions of Operation and Dedicated to Low-Voltage and Low-Current Applications*

[2] P.O'Connor, G. De Geronimo, *Prospects for Charge Sensitive Amplifiers in Scaled CMOS*

Next steps

- **continue on comparator architectures studies and optimizations**
- **exploring options for the very front-end stage**
- **getting ready as soon as possible with a complete schematic design (comparator + ADC)**
- **then move to layout**