



UNIVERSITAT DE BARCELONA



laSalle

Universitat Ramon Llull



# ***LHCb Calorimeter Upgrade Electronics Review***

**David Gascon, Guillermo Loustau, Juan Mauricio, Eduardo  
Picatoste**


***Universitat de Barcelona and La Salle***

Calorimeter Upgrade Review – 14<sup>th</sup> June 2013 – CERN

# Contents

- Introduction
- Integrated Implementation
- COTS
- Test Beam
- Delay line
- Slow control

# Current Analog Signal Processing

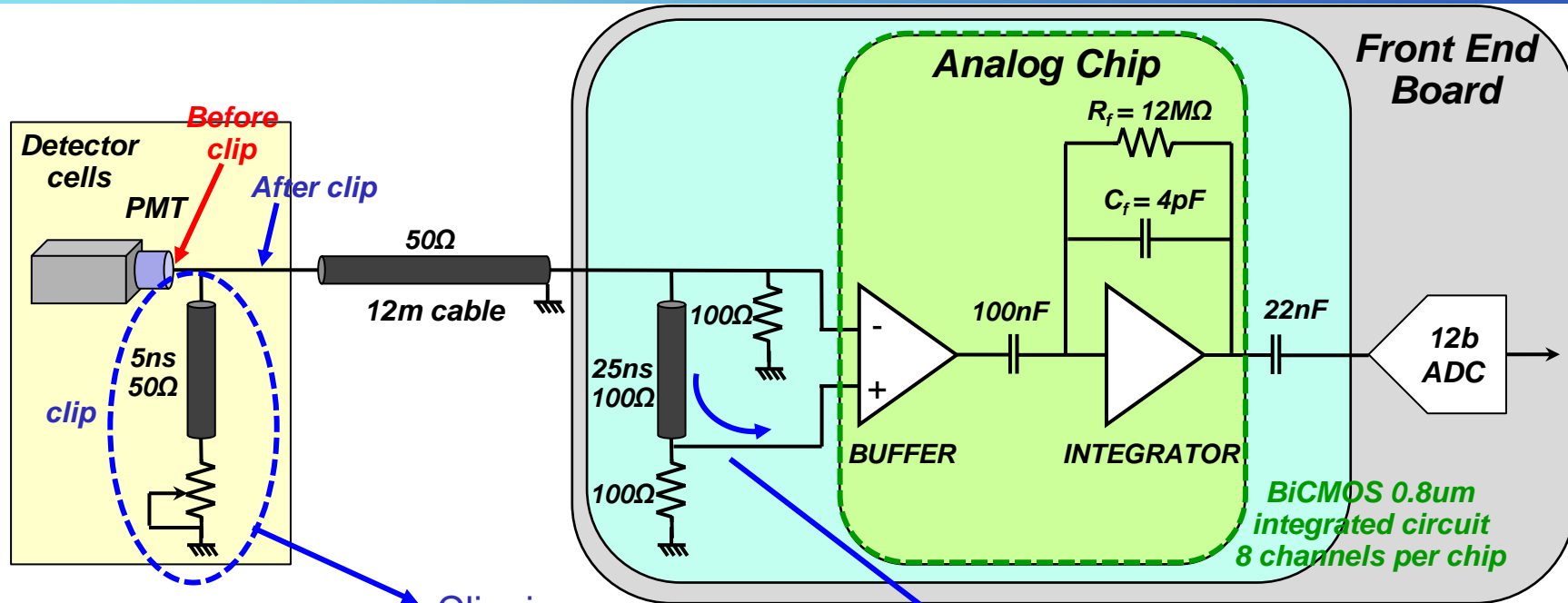


## Specifications:

- Pulse shaping in 25ns
- Spill over < 1% after 25ns
- Integrator plateau: 4ns
- Linearity < 1%
- Rise time ~ 5 ns

 
## Clipping:

- ⇒ Reduce signal tail
- ⇒ Reduce spill over



 
## Integrator discharge:

Clipped signal + delayed negative clipped signal



# Analog Electronics Upgrade Motivation

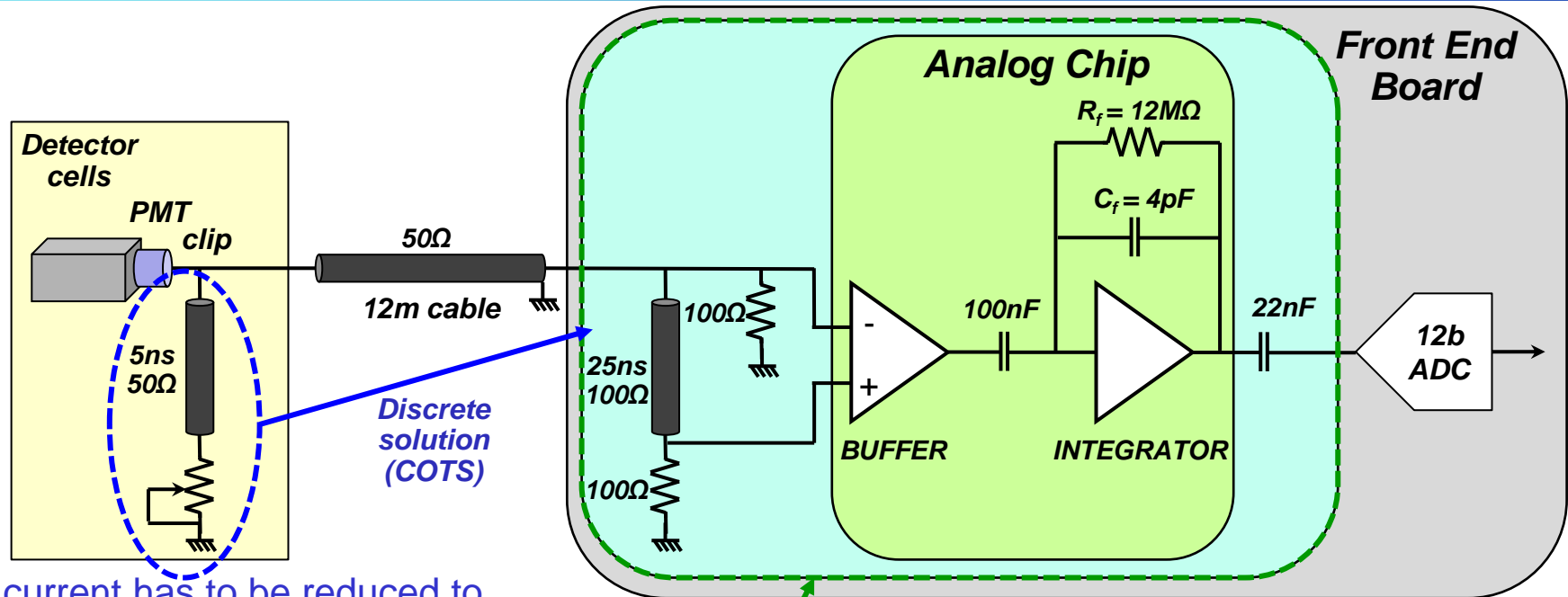

PMT current has to be reduced to increase lifetime

- ⇒ FE electronics gain has to be increased correspondingly
- BUT FE noise should not be increased in the operation!

Noise < 1 ADC Count

- For 12 bit DR, input referred noise < 1nV/sqrt(Hz)
- ⇒ Termination resistor at input generates too much noise

Solutions:

- New ASIC
  - ✓ Increased gain
  - ✓ Active cooled termination
- Discrete solution: Components Out-of-The-Shelf (COTS)
  - ✓ 2/3 of the signal are lost by clipping
  - ✓ Remove clipping at the PM base (detector)
  - ✓ Perform clipping after amplification in FE using delay lines

Radiation tolerance:


- Dose 15 krad per fb<sup>-1</sup>
- ✓ Radiation qualification tests
- ✓ Design techniques on ASIC
  - Enclosed transistors with guard rings

# Analog Signal Processing

Energy range	0-10 GeV/c (ECAL) Transverse energy
Calibration	4 fC / 2.5 MeV / LSB
Dynamic range	4096-256=3840 :12 bit
Noise	$\leq 1$ LSB or ENC $< 4$ fC
Termination	$50 \pm 5 \Omega$
Shaping	25 ns (99 % of the charge)
Spill-over noise	$< \text{LSB}$
AC coupling	5-20 $\mu\text{s}$
Baseline shift Prevention	Dynamic pedestal subtraction (CDS) Pedestal is the smallest of 2 prev. samples
Max. peak current	4-5 mA (clipped)
Spill-over correction	Clipping
Linearity	$< 1\%$
Crosstalk	$< 0.5\%$
Timing	Individual (per channel)


Noise PSD at different stages of the signal processing

 - **Signal processing elements (analog):**
  - Amplification
  - Integration / shaping
- **Dynamic pedestal subtraction (CDS):**
  - Needed to correct baseline shift
  - And to filter LF noise (pick-up)
    - Has proven to be crucial in LHCb
  - Noise Power Spectral Density (PSD) in signal increases by  $\sim \sqrt{2}$


 
# Analog Signal Processing

- Noise contributions of
- (1) Std high Zin amplifier




Referred to the clipped PMT current  $i_{nCLIP}$

$$i_{nCLIP}^2 = \frac{e_n^2}{|Z_0|^2} + i_n^2 \left| \frac{1}{2} \right|^2 + \frac{4KT}{R_T} \left| \frac{1}{2} \right|^2 + \frac{4KT}{R_C} \left| \frac{R_C}{Z_0 + R_C} \right|^2 + \frac{4KTR_S}{|R_S + Z_0|^2}$$

Typically dominant contributions

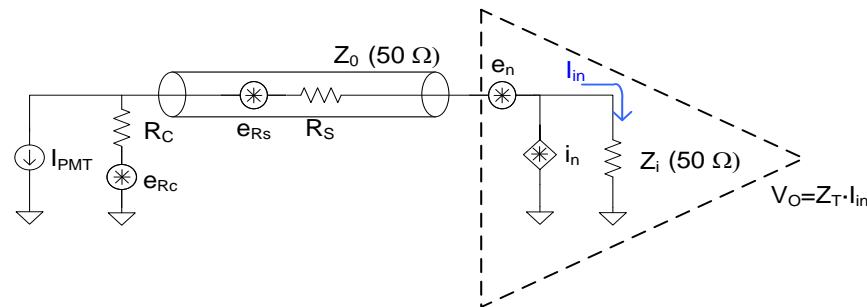- (2) Electronically cooled amplifier (OT)



$$i_{nCLIP}^2 = \frac{e_n^2}{|2Z_0|^2} + i_n^2 \left| \frac{1}{2} \right|^2 + \frac{4KT}{R_C} \left| \frac{R_C}{Z_0 + R_C} \right|^2 + \frac{4KTR_S}{|R_S + Z_0|^2}$$

# Analog Signal Processing


- ENC: amplifier + integrator (time T) + CDS:

- White noise  $ENC_{A+I}^2 \approx \frac{1}{2} i_{CLIP}^2 T$ 
  - Resistive source imp.
- Amp BW  $\gg 1/T$   $ENC_{A+I+CDS}^2 \approx i_{CLIP}^2 T$

- Assumptions:

- Cable modelled as lumped element\*
- Cable seen as  $Z_0$  at HF from amp. side\*
- $R_T = Z_0$  (V amp) and  $Z_i = Z_0$  (I amp)
- Uncorrelated noise for CDS

 Total input referred series noise requirement



- $R_C = 21 \Omega$
- $R_S = 18 \Omega$
- $i_n$  neglected

\* R.L. Chase, C. de La Taille et al., NIM A330, 1993

→ OT with  $e_n < 2$  nV/sqrt(Hz) fulfils requirements,

→ Whereas std amp should have  $e_n < 1$  nV/sqrt(Hz) !

# Integrated Solution

Very difficult to integrate  
inside an ASIC  
HQ analog delay lines





2 switched alternated  
paths (like in PS/SPD)



Switching noise!



Fully differential  
ASAP

 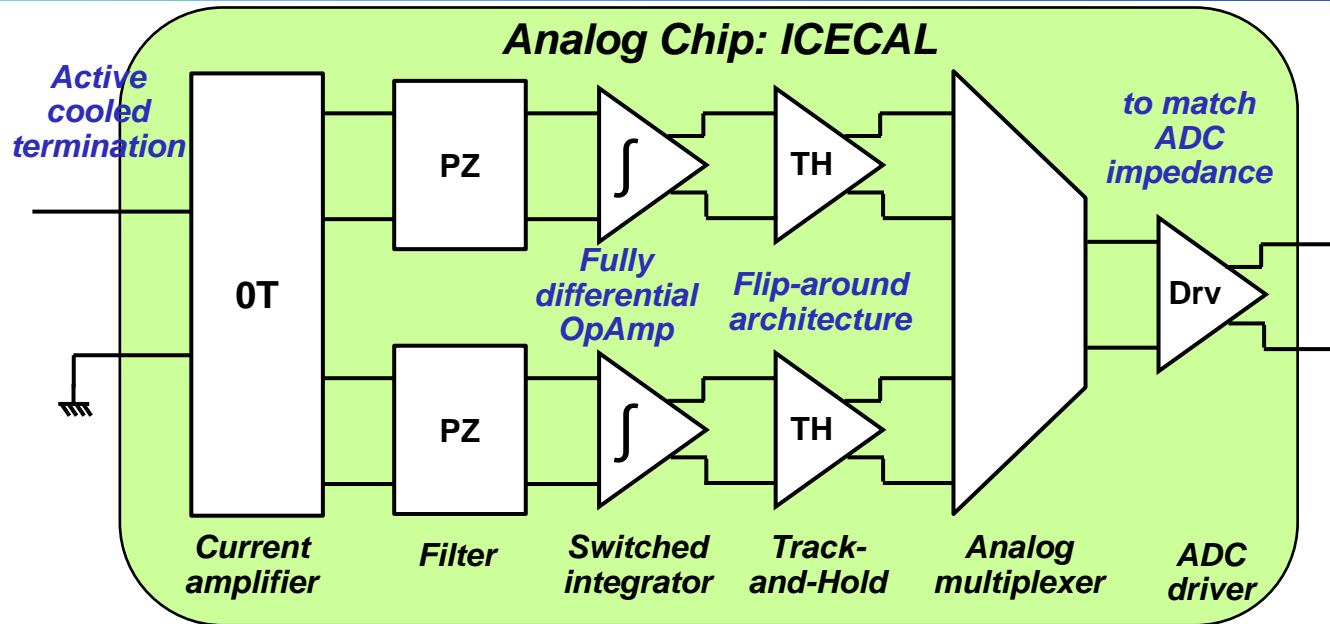

Two prototypes already  
designed and tested:

- Preamp + integrator
- Preamp + integrator + TH

Technology:

- SiGe BiCMOS 0.35um AMS



# Channel Architecture: Current Amplifier Input Stage

- Current mode feedback:

- Inner loop: lower  $Z_{in}$ 
  - Current feedback (gain): mirror: K
- Outer loop: control  $Z_{in}$ 
  - Current feedback: mirror: m
  - Current gain: m

- Electronically cooled input impedance

$$Z_i \approx \frac{1/g_{m1} + R_e}{1 + K} + \frac{K}{1 + K} m R_f$$

- Current mode feedback used


- Optical communications
- SiPM readout

- Low voltage

- Only 1 V<sub>be</sub> for the super common base input stage

- Better in terms of electrostatic discharge (ESD):

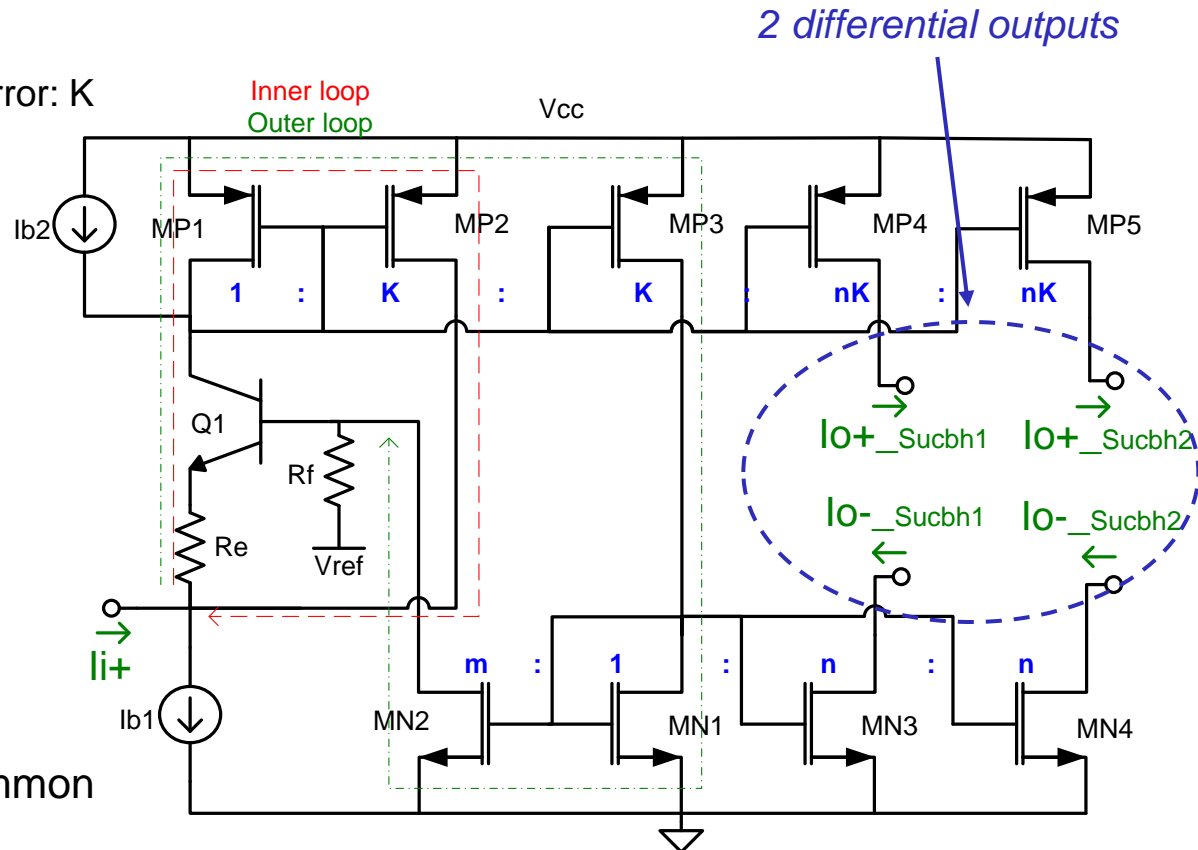- No input pad connected to any transistor gate or base



# Channel Architecture: Pole-Zero Filter

- **Problem :**

- Test beam signal is wider than expected

- **Solution: fast pole-zero filter**





- Pole at 250 MHz
- Zero at 125 MHz

- **To reduce signal LF component:**

- Better plateau
- Reduce spill over

- **Noise impact:**

  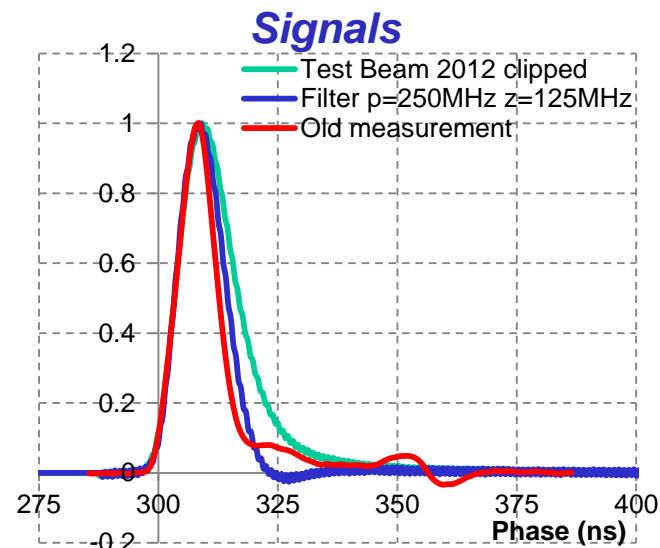 - Transient noise simulation
- 500 iterations
- 10% noise increase





# Channel Architecture: Switched Integrator / Track-and-Hold

- Switched integrator

- Integrator plateau : 4 ns
- Linearity < 1%
- Residue < 1% after 25 ns
- Reset time < 5 ns

Rf to improve  
the plateau

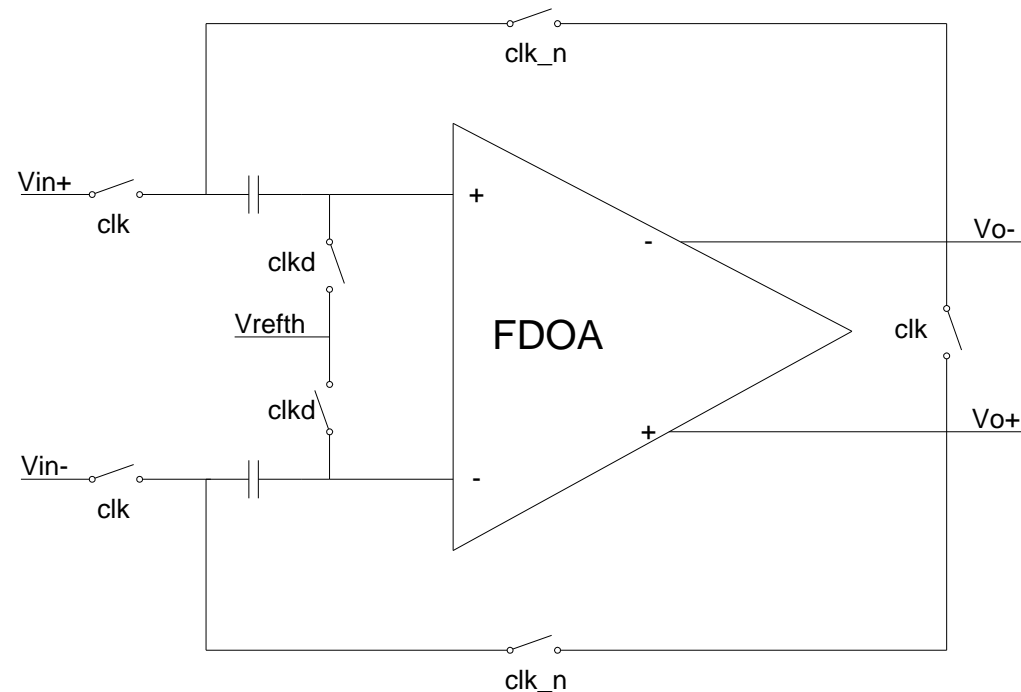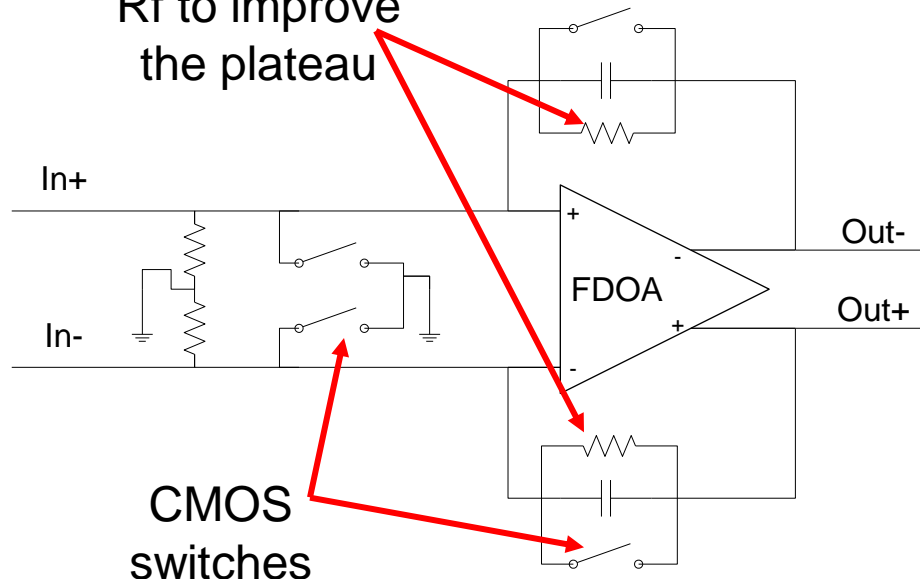


- Track-And-Hold:


- 12 bit: flip-around architecture

# Channel Architecture: Fully Differential Op Amp

- Fully differential Op Amp:
  - Folded cascode + Miller stage with CMFB


FDOA specifications	
Parameter	Value
Gain bandwidth	500 MHz
Phase margin	$> 65^\circ$
Slew rate	$> 2 \text{ V}/\mu\text{s}$
$V_{\text{CM}}$	1.65 V

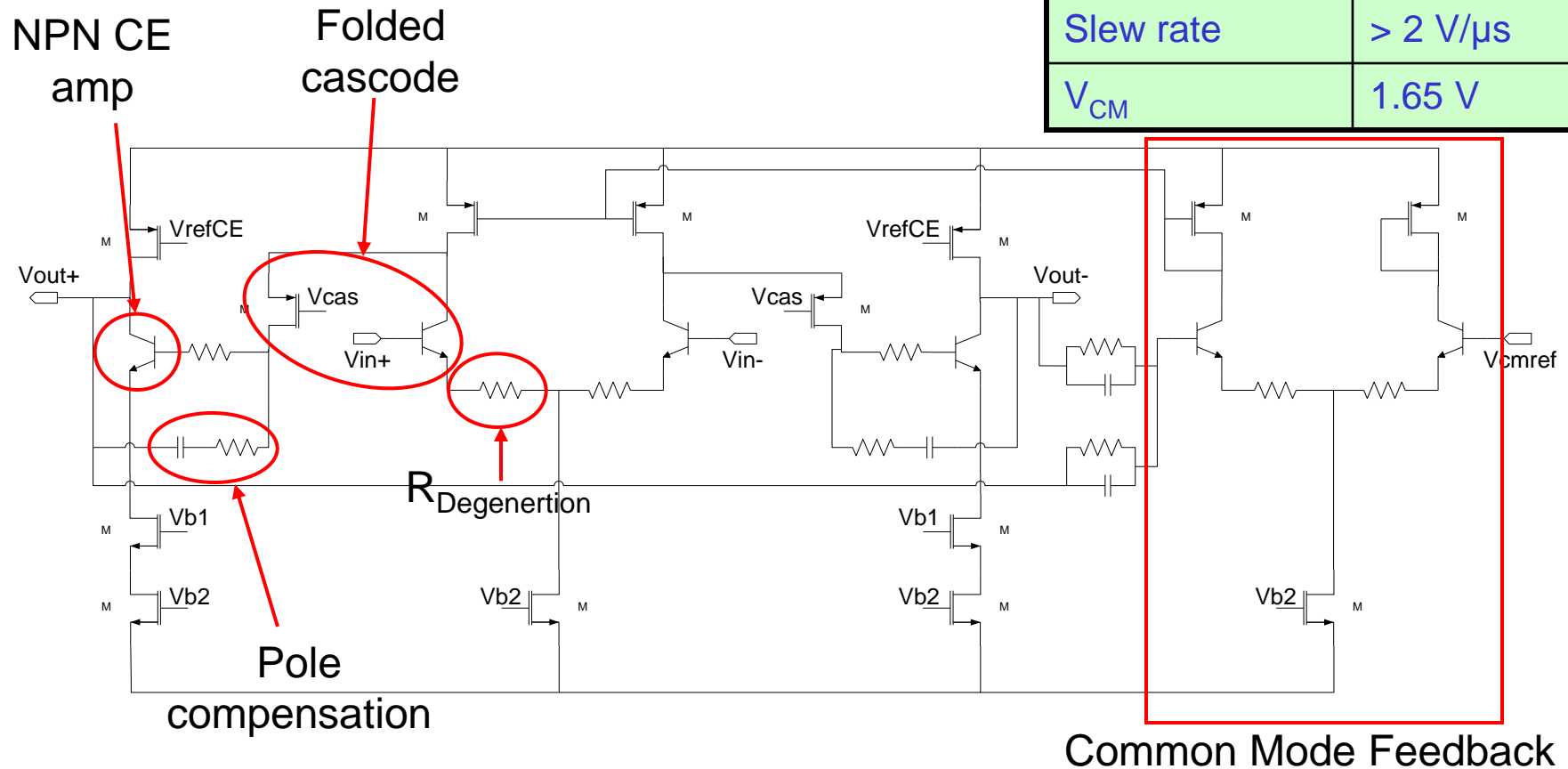

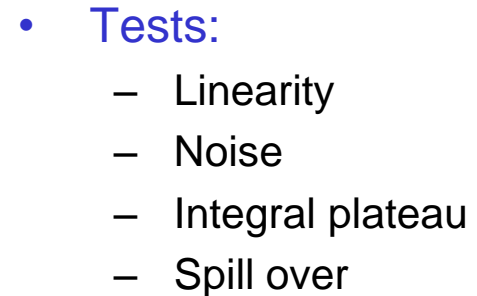

 
# ICECAL lab measurements

- $Z_{in}$ :
  - $Z_{in}$  fine tunable with R in parallel ( $\sim 390\Omega$ )
  - Study stability of  $Z_{in}$  as a function of frequency from reflections as seen at:
    - Input of the chip
    - Waveform generator output
  - Dynamic variation of input impedance  $\ll 1\%$  for full dynamic (50 pC)
  - Low Refl. Coef. dispersion  $< 0.5\%$



 
- Noise:
  - Spec: noise  $\sim < 1$  ADC count
  - Measurements with all setup:
    - $\sim 1,6$  ADC counts
    - $\sim 1,7$  ADC counts (dynamic pedestal subtraction)
  - Measurements without cable:
    - $\sim 1,0$  ADC counts
    - $\sim 1,25$  ADC counts (dynamic pedestal subtraction)


 
# ICECAL lab measurements


- **Linearity:**

- Simulations show that the linearity is lost at  $\sim 1.8V$
- Cause: single-ended limit to maximum  $V_{out}$  of FDOA at the NMOS stage
- Solution: apply different offset to each pos/neg signal to reduce overall signal excursion




- **Integrator output plateau:**

 - Spec:  $4ns < 1\%$  variation
- Cope with different particle time arrival
- Initially OK, but signal used was not correct; pulse width underestimated (due to cable and clipping effects)
- Solution: fast pole-zero filter to reduce low frequency components





# Analog Electronics Upgrade Motivation

 

PMT current has to be reduced to increase lifetime

- ⇒ FE electronics gain has to be increased correspondingly
- BUT FE noise should not be increased in the operation!

Noise < 1 ADC Count

- For 12 bit DR, input referred noise < 1nV/sqrt(Hz)
- ⇒ Termination resistor at input generates too much noise

**Solutions:**




- New ASIC
  - ✓ Increased gain
  - ✓ Active cooled termination
- Discrete solution: Components Out-of-The-Shelf (COTS)
  - ✓ 2/3 of the signal are lost by clipping
  - ✓ Remove clipping at the PM base (detector)
  - ✓ Perform clipping after amplification in FE using delay lines

**Radiation tolerance:**

- Dose 15 krad per fb<sup>-1</sup>
- ✓ Radiation qualification tests
- ✓ Design techniques on ASIC
  - Enclosed transistors with guard rings





# COTS Channel Architecture

  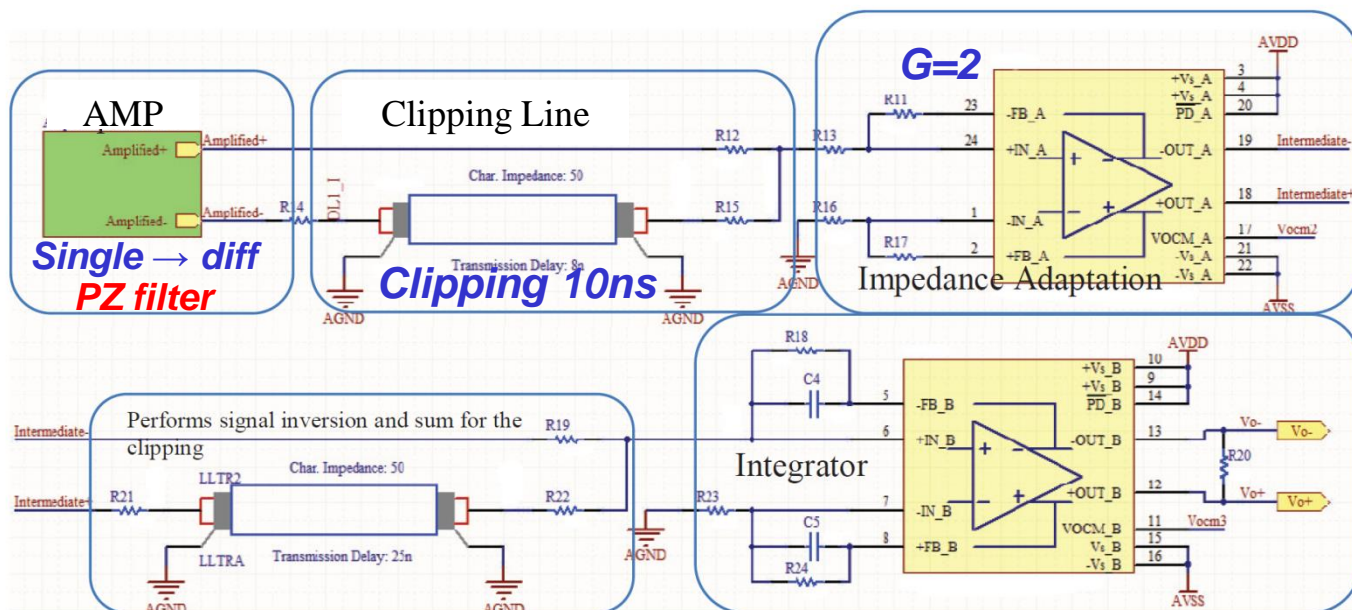

  
# COTS: clipping


- Clipping is done in the FEB, not in the PMT base:



 - 2/3 of the signal are lost by clipping
  - Remove clipping at the PM base (detector)
  - Perform clipping after amplification in FE using delay lines
- ⇒ Greater signal/noise ratio






## Clipping stage

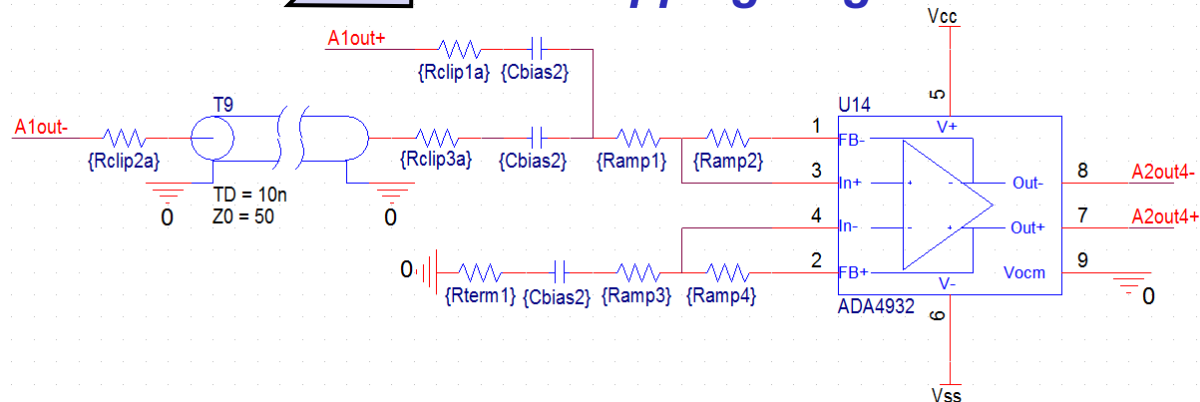

# COTS: integration


## Delayed lines integrator

  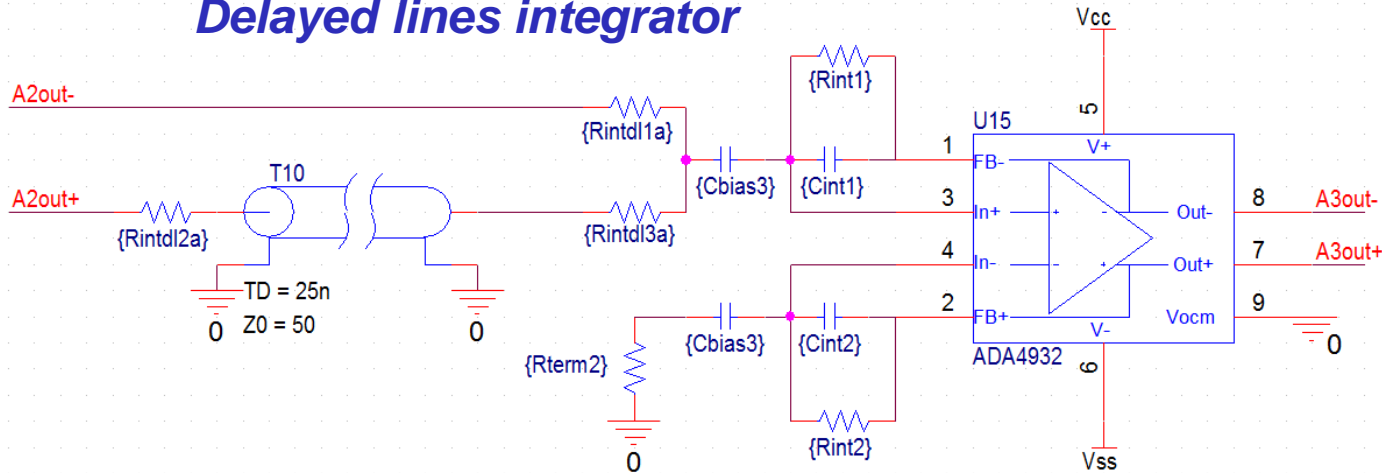
 
# COTS: lab measurements


- **Linearity:**

- Low voltage measurements present high relative errors
- Systematics due to the attenuator




- **Noise:**

 - Spec: noise  $\sim < 1$  ADC count
- Measurements with joint ground planes:
  - $\sim 4,23$  ADC counts
  - $\sim 2,31$  ADC counts (dynamic pedestal subtraction)
- Measurements with separated gnd planes:
  - $\sim 4,14$  ADC counts
  - $\sim 1,99$  ADC counts (dynamic pedestal subtraction)




- Integrator output plateau:

 - Spec: 4ns < 1% variation
- Cope with different particle time arrival
- Initially OK, but signal used was not correct; pulse width underestimated (due to cable and clipping effects)
- Solution: fast pole-zero filter to reduce low frequency components




- Spill over:

 - Spec: <1% in the following cycles respect to the signal
- Not met.
- Solution: fast pole-zero filter to reduce low frequency components


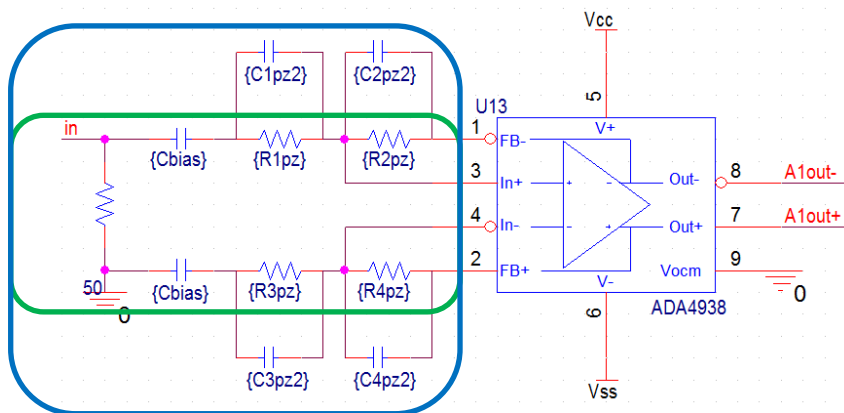
## COTS modifications after TB 2012


- Signal measured at Test Beam is more expanded than the one used for original design
- Need to equalize the cable effect
  - Pole-zero due (under study)
- Pole-zero on pre amplifier of the first stage proposed
  - Problems:
    - $G=10 \rightarrow BW \leq 100\text{MHz} \rightarrow$  pole & zero freq  $>$  AMP BW
    - Capacitor values  $< 1\text{p} \rightarrow$  values comparable to parasitic capacities
    - $Z_{in} \neq \text{cte } 50$




**Pre Amp  $\rightarrow$  PZ modification**

14<sup>th</sup> June 2013

## Clipping Tuning

 

## Input Integrator Tuning

 


Calo Upgrade Review

22



# COTS mezz 5 simulations

 

- COTS TB input signal

- Without pole-zero filter

Plateau = 4.55793 ns

T(1% - 100%) = -29.35551 ns

T(100% - 1%) = 59.23128 ns

- COTS TB input signal

- With pole-zero filter

Plateau = 4.35421 ns



T(1% - 100%) = 24.84842 ns

T(100% - 1%) = 24.75773 ns

- Tuning:

- Circuit tuning done in both results to optimize results:
  - Spillover → minimize
  - Plateau → maximize
  - Undershoot → minimize


# Test Beam Measurements

  

- November 2012
- Beam line T4-H8 at CERN
- Used  $e^-$  of 50 to 125 GeV
- Setup:
  - ECAL channel
  - PMT
  - 12m cable
  - FEB prototype
  - Lecroy integrator
  - Time-to-Digital Converter (TDC)






# Test Beam Measurements

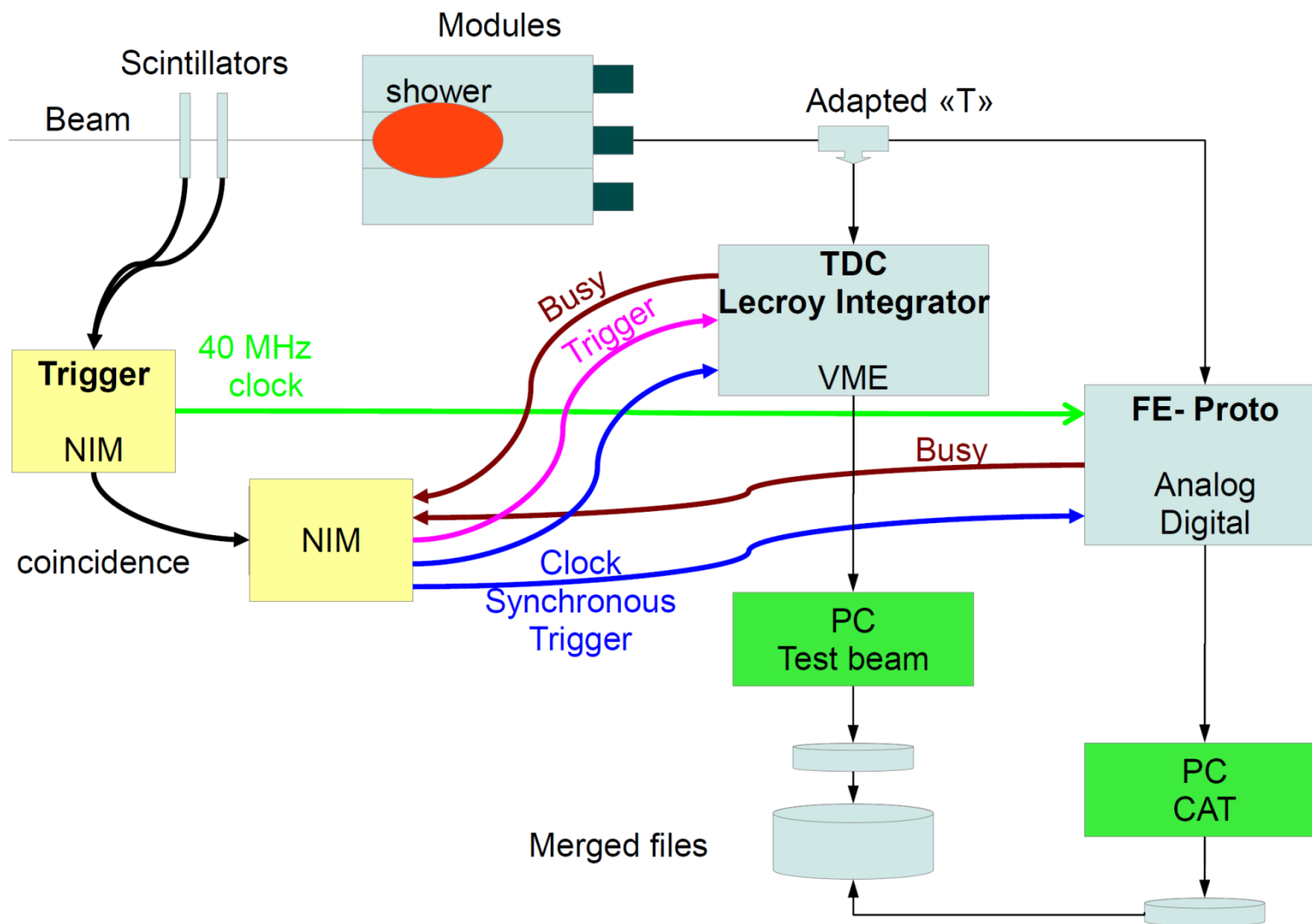

  
 
# Test Beam Measurements

- **Noise:**
  - Noise after pedestal subtraction:  
~1.6 ADC (ASIC)  
~2.6 ADC (COTS)
  - Contribution of 10-15% due to the use of a “T” to distribute the signal:  
~1.4 ADC (ASIC)  
~2.3 ADC (COTS)
- **Linearity:**
  - Linearity better than 1%


  
# Test Beam Measurements


- Plateau:
  - Integral plateau  $\sim 1.6\%$  at  $\pm 2\text{ns}$  (ASIC) and  $< 1\%$  (COTS)
- Spill over:
  - Spill over of  $\sim 8\%$  in following sample (ASIC)
- Pulse width underestimated (due to cable and clipping effects):
  - Affects plateau and spill over
  - $\Rightarrow$  Pole-zero filter proposed for final version of ASIC/COTS



Complete results can be found at the presentations by  
Olga Kochebina at Calorimeter Upgrade meetings  
[19/12/2012](#) and [12/04/2013](#)


- We need delay lines:
  - To synchronise ICECAL integrator, track & hold and the external ADC.
  - To adjust the ADC clock phase in COTS solution.
- Challenges:
  - Radiation hardness:
    - SEU → TMR (triple voting).
    - SET → glitch suppressors.
    - SEL → guard rings (full custom digital design).
  - Delay line variability:
    - Process variations → **external** adjust (coarse).
    - Environmental variations → **internal** locked loop adjust (vControl).
  - Noise:
    - Stringent noise requirements of the ASIC analog components (ICECALv3) → differential design, guard rings..

# Delay Line: design overview

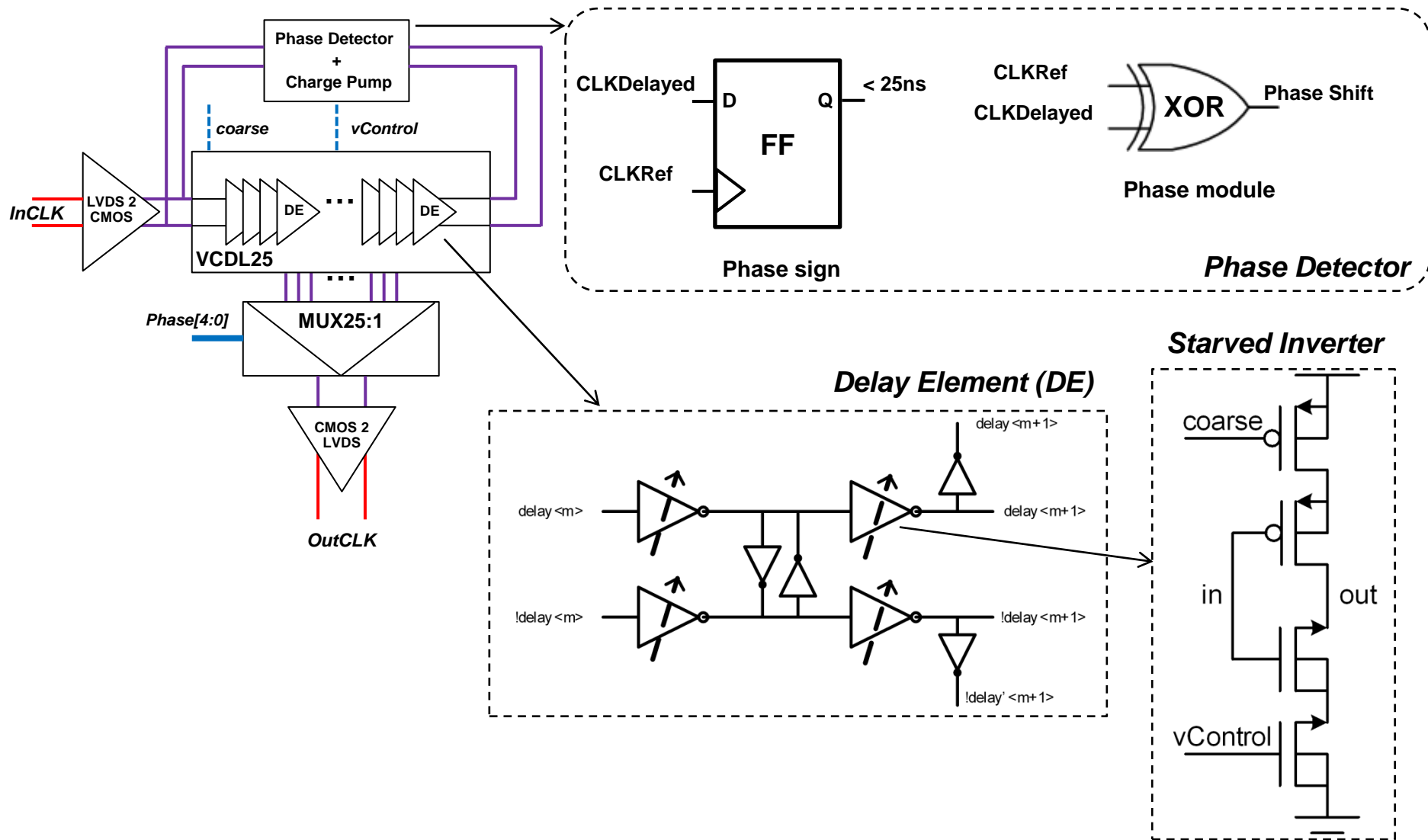
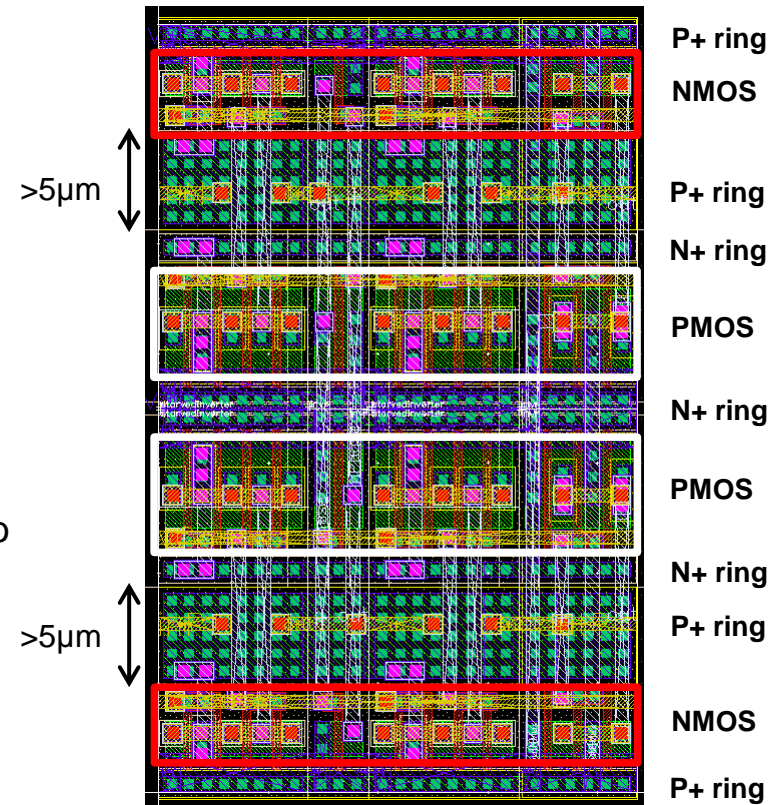
# Delay Line features


- 4 DLL Channels (4x3 = 12 independent sub-channels):
  - 25 configurable clock phases (1-ns step).
  - Peak-to-peak Jitter: 3 ps.
  - Differential Non Linearity (DNL): 18 ps.
  - Delay Range: 17.45 ~ 39.88 ns.
  - DLL Locking time: 2.5 ~ 10  $\mu$ s.
  - DLL peak-to-peak ripple voltage ~ 1 mV.
  - ~280 mW of power consumption.
  - Technology: AMS 0.35 CMOS.
- Reset:
  - Glitch supressor ( $\leq 8$ ns) ensures that SETs do not accidentally reset the chip.
- Reliability (SEL avoidance):
  - Extra design rules:
    - $\geq 5\mu$ m between N-DIFF layer and NWELL.
    - Guard rings between PMOS and NMOS.



**Example: Delay Element**

- We need slow control:
  - To configure and check the status of delay lines.
  - To configure ICECALv3 Analog blocks.
- Challenges:
  - Radiation hardness:
    - SEU → TMR (triple voting).
    - SEL → guard rings (full custom digital design).
- Features:
  - SPI slave:
    - Works fine @ 20 Mbps.
    - Up to 32 configuration registers and 32 status registers.
    - Also implements a software reset pulse (to reset DLL charge pumps).
  - Serial registers:
    - 16 bits R/W TMR registers (configuration).
    - 8 bits RO (status). No memory.


# Slow control: design overview

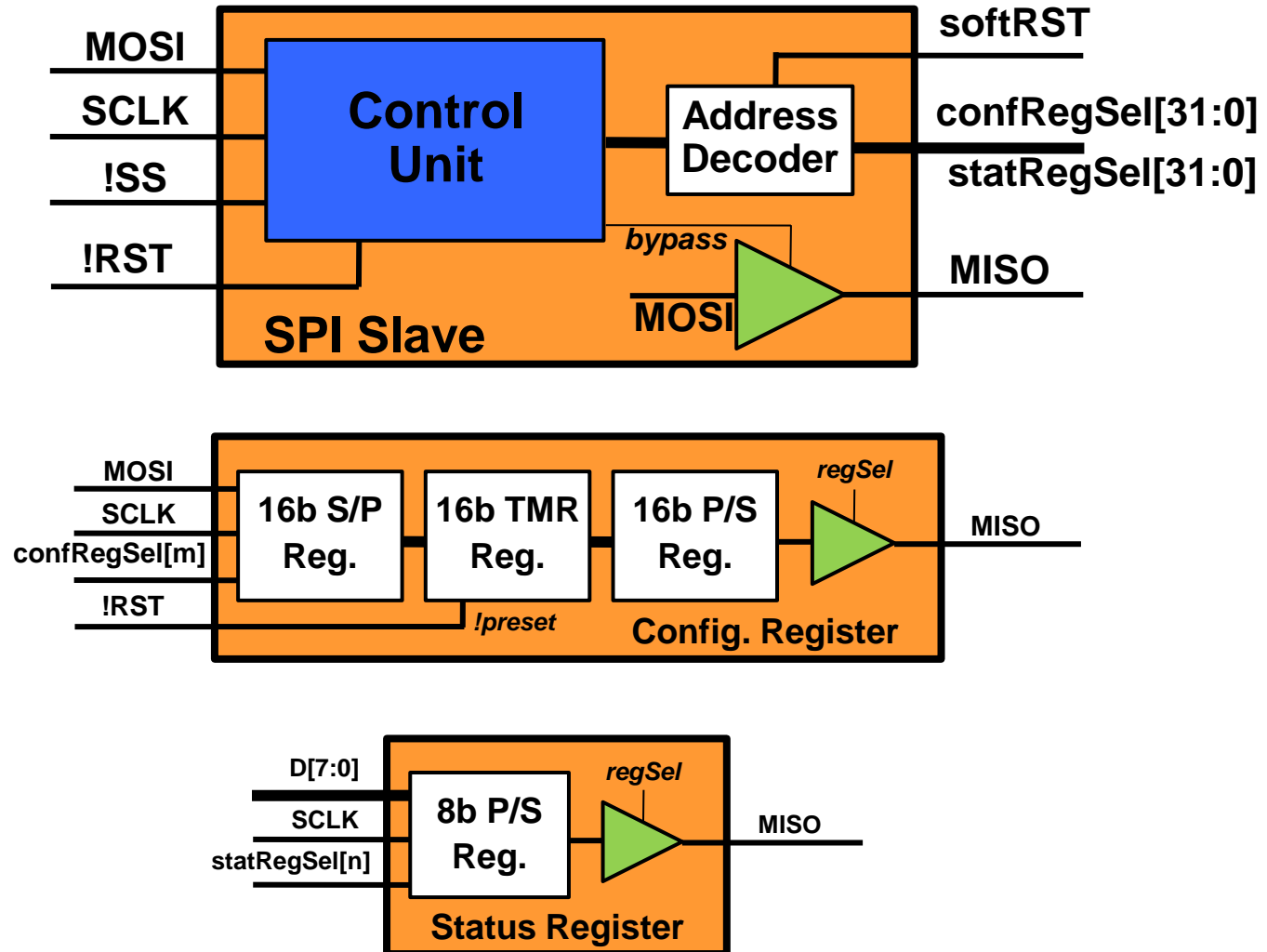



 
# Slow control implementation

- **SPI Slave control unit FSM:**
  - SEU tolerant.
    - Number of states = 4.
    - Necessary bits to encode the states: **2 bits**.
    - Used bits to encode the states: **3 bits**.
    - Hamming distance between idle state and critical states > 1:
      - If SEU occurs, the FSM is automatically recovered after the next clock rising edge.
      - **Problem: not corrected until the next frame arrives (slow control clock is inactive during idle periods).**
- **16 bits TMR register:**
  - Each bit is stored in 3 flip-flops.
  - A combinational block computes the majority.
  - If SEU occurs, the faulty bit is automatically corrected in the next clock rising edge.
    - **Problem: the register is protected as long as SC CLK is active.**


 
# Improved SPI slave (ICECALv3)

- Use the BXIDRst as auxiliary clock:
  - Only when SPI slave is idle (white).
  - This capability can be enabled/disabled via SPI (purple).
  - TMR registers and SPI FSM will be refreshed every 3564 BXs (red).



- Analog shaping electronics: two solutions
  - ASIC:
    - cooled input termination for reduced noise
    - 2 interleaved channels and switched integrators: no deadtime
    - Full 4 channel ASIC to be sent in November 2013
  - Discrete elements (COTS):
    - Clipping removed from PMT base and installed in the FEB: increase in signal
    - Definitive version scheduled for the end of 2013
  - Final decision beginning 2014
  - Prototypes tested both at lab and at a test beam:
    - Specifications met except for integrator plateau and spill over
    - Simulations show a pole-zero filter would fix it.
- A delay chip has been designed for the clock distribution
  - It will be integrated in the ASIC (Nov 2013)
  - Can be used standalone for COTS
  - Standalone prototype tests ongoing
- The slow control of the ASIC(s) is based on SPI protocol
- Radiation qualification tests foreseen

Backup...

# Choice of Technology

- SiGe BiCMOS is preferred:

- SiGe HBTs have higher  $gm/I_{bias}$  than MOS: less noise, less  $Z_i$  variation
- SiGe HBTs have higher  $f_t$  (>50 GHz): easier to design high GBW amplifiers

- Several technologies available:

- IBM
- IHP
- AMS BiCMOS 0.35  $\mu m$

	IBM	IHP	AMS
HBT $f_t$	> 100 GHz	190 GHz	60 GHz
CMOS	0.13 $\mu m$	0.13 $\mu m$	0.35 $\mu m$
Proto Cost [€ /mm <sup>2</sup> ]	> 3 K	> 3 K	1 K

- AMS is preferred

- Factor 2 or 3 cheaper
- Too deep submicron CMOS not required / not wanted:
  - Few channels per chip (4 ?)
  - Smaller supply voltage
  - Worst matching
- Radiation hardness seems to be high enough
  - 30 Krad seems to be OK (checked by other Upgrade projects)



# Choice of ADC

- In order to make the proper interface between the analogical part and the ADC it is necessary to have it previously selected.
- Our ADC needed 12 bits resolution, at least 40MHz conversion frequency and it was also desirable a small package due to space restrictions.
- The more suitable components for our application where:
  - Texas Instruments ADS6122
    - 1 ADC/Chip but 5x5mm only, LVDS, DDR!
  - Texas Instruments ADS6222
    - 2 ADC/Chip, LVDS, DDR!
  - Analog Devices AD9238
    - 2 ADC/Chip, LVTTTL.

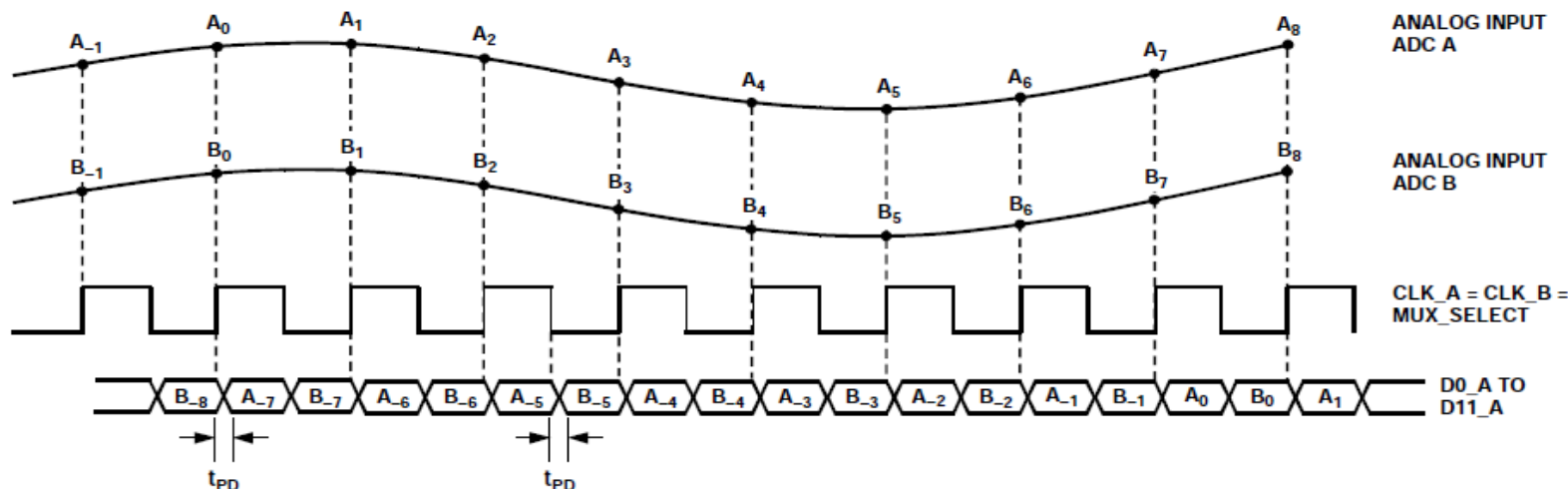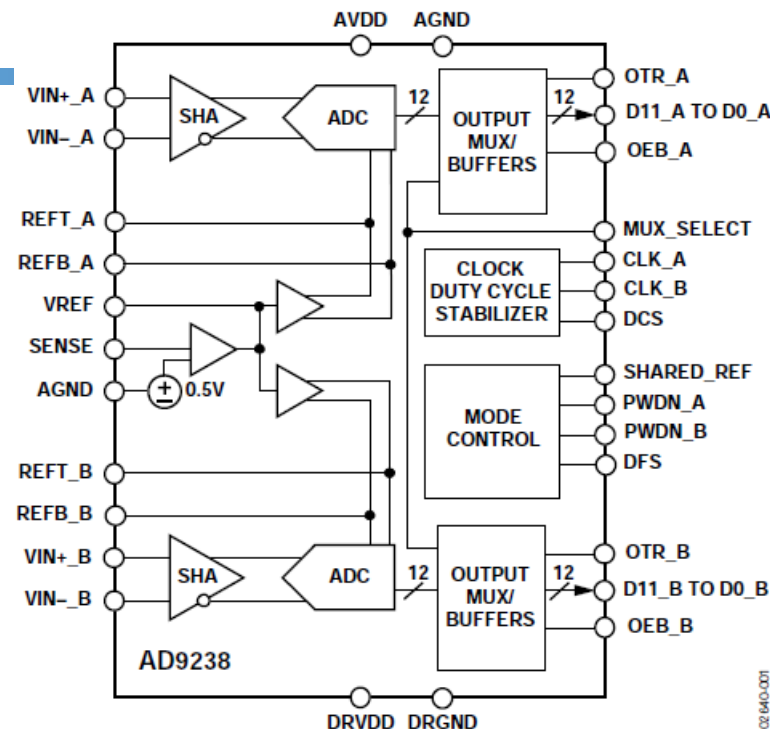
# Choice of ADC

- Analog Devices AD9238

- One sampling clock per channel
- Optional multiplexing
- No RAM configuration




# General Requirements

 

- 40 MHz frequency
- Front End Electronics Resolution must meet detector requirements
  - Precision
  - Noise
- Radiation tolerance conditions (SEU-SEL)
- ECAL : 6000 Channels
- HCAL : 1500 Channels
- Detector side
  - PMT + base
- Front End Electronics
  - Analog processing
  - Digital processing
  - Control Scheme




# The need for an upgrade

 

- 2018 : luminosity increase
  - Keep same detector
  - Lower PMT gain to protect against aging
  - Lower signal
  - Increase Electronics gain
  - Keep precision
- Change in the trigger structure
- Change in the control structure
  - Requires changes in digital FE part

# COTS: stage 1

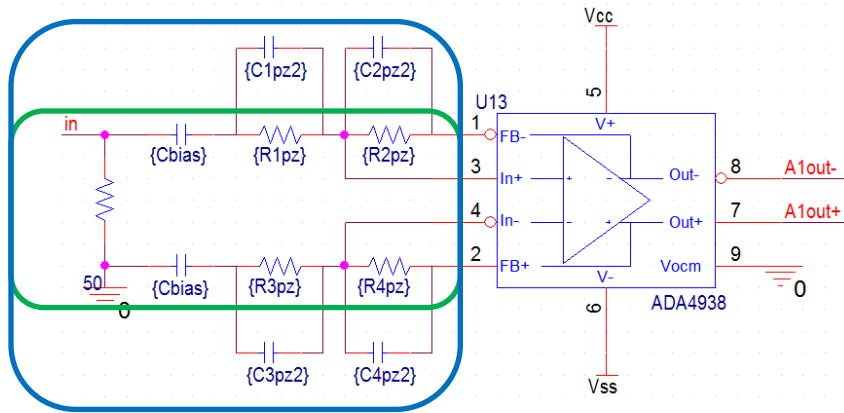

- Original COTS design


- Rin=50
- Amplifier ADA4938 G=10
- Single to differential

- COTS modifications after TB 2012

- Signal measured at Test Beam more expanded than the one used for design
- Added a filter to equalize the cable
  - Pole-zero (under study)


- Adjusting

 - Fixed values: BW
- Variables adjustable: Gain, pole, zero






# Delay Line: design overview

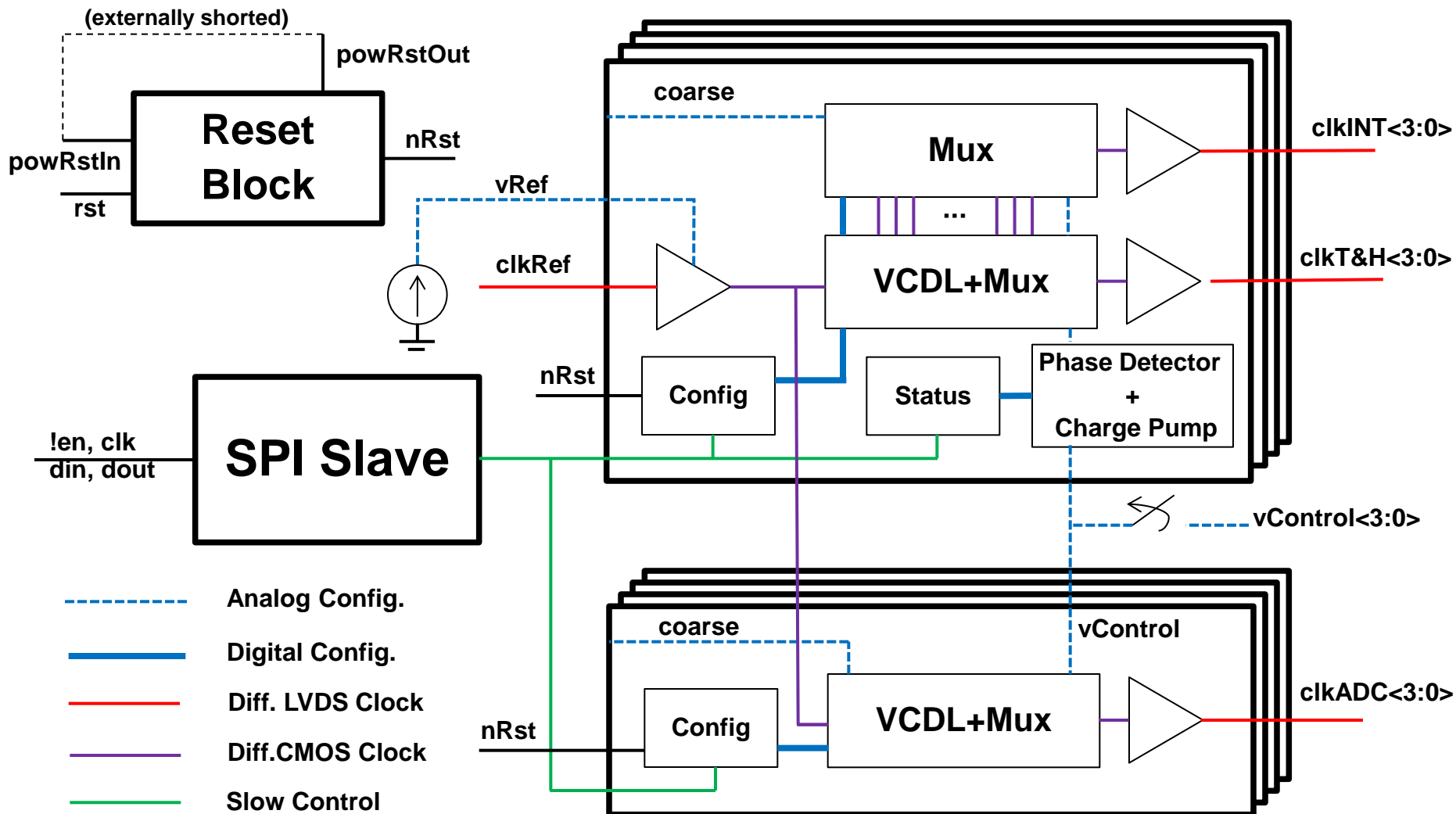


# Delay Line implementation

- Simulation results: Charge pump.

 
 
# Delay Line implementation



- Simulation results: Phase detector (locked).



# Delay Line implementation

Simulation results:

Power RST + glitch supressor

  

- Top: Power RST. 1-ms-wide.
- Mid: External RST.
- Bottom: glitch-free Internal !RST.



# SPI Slave Addressing Scheme

<b>b<sub>7</sub></b>	<b>b<sub>6</sub></b>	<b>b<sub>5</sub></b>	<b>b<sub>4</sub></b>	<b>b<sub>3</sub></b>	<b>b<sub>2</sub></b>	<b>b<sub>1</sub></b>	<b>b<sub>0</sub></b>
R/!W	Pump Rst	Status/!Conf	RSEL <sub>4</sub>	RSEL <sub>3</sub>	RSEL <sub>2</sub>	RSEL <sub>1</sub>	RSEL <sub>0</sub>

<b>ADDR</b>	<b>ICECAL Ch</b>	<b>Width (bits)</b>	<b>Description</b>
0x00	0	16	Integrator / Track&Hold Clock Configuration Register.
0x01	0	16	ADC Clock Configuration Register.
0x02	1	16	Integrator / Track&Hold Clock Configuration Register.
0x03	1	16	ADC Clock Configuration Register.
...			
0x10	2	16	Integrator / Track&Hold Clock Configuration Register.
0x11	2	16	ADC Clock Configuration Register.
0x12	3	16	Integrator / Track&Hold Clock Configuration Register.
0x13	3	16	ADC Clock Configuration Register.
...			
0x40	Any	-	Software Reset of the Charge Pumps.
...			
0xA0	0	8	Status Register.
0xA1	1	8	Status Register.
0xB0	2	8	Status Register.
0xB1	3	8	Status Register.
...			
0xFF	-	-	SDI / SDO Bypass. For testing purposes.