

Design Methods and Tools for Power Electronics

T. Meynard – G. Fontes

Laplace – N7 – CNRS

Toulouse




Outline of the presentation

- Simulation vs Design
- Semi Analytic Design
- Designing with objects and optimization


SIMULATION VS DESIGN

Standard simulation tools

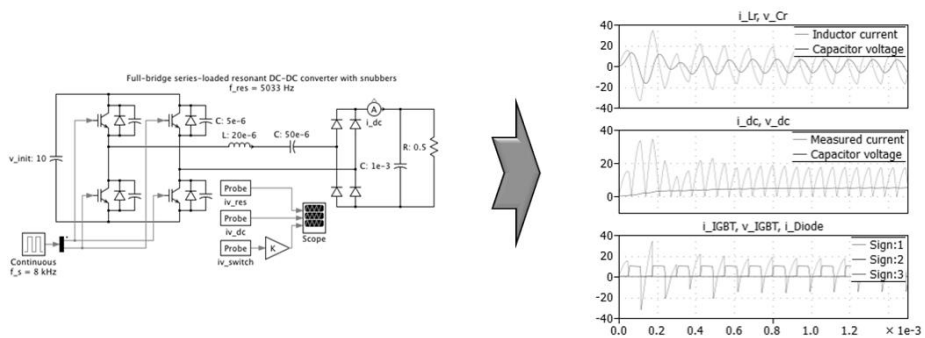


Simulation is an injection :
one circuit gives a single set of waveforms.

Design tools

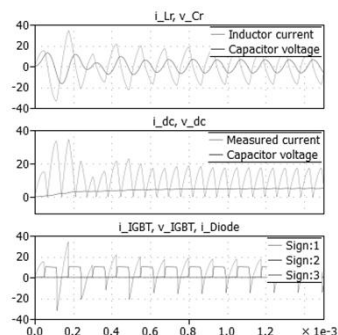


Design is NOT an injection :
there can be an infinity of solution for a given set of specifications
(and sometimes NO solution!...)

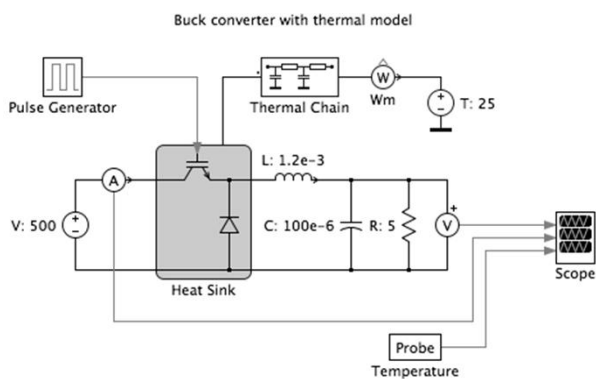Hidden quantities in standard simulation tools



Which of the components in this circuit is the biggest? => L? C? the heatsink?
Which of the components in this circuit is the most expensive?
If L is halved and C doubled to get the same voltage ripple, will the filter be smaller?
Or less expensive?

SEMI ANALYTIC DESIGN

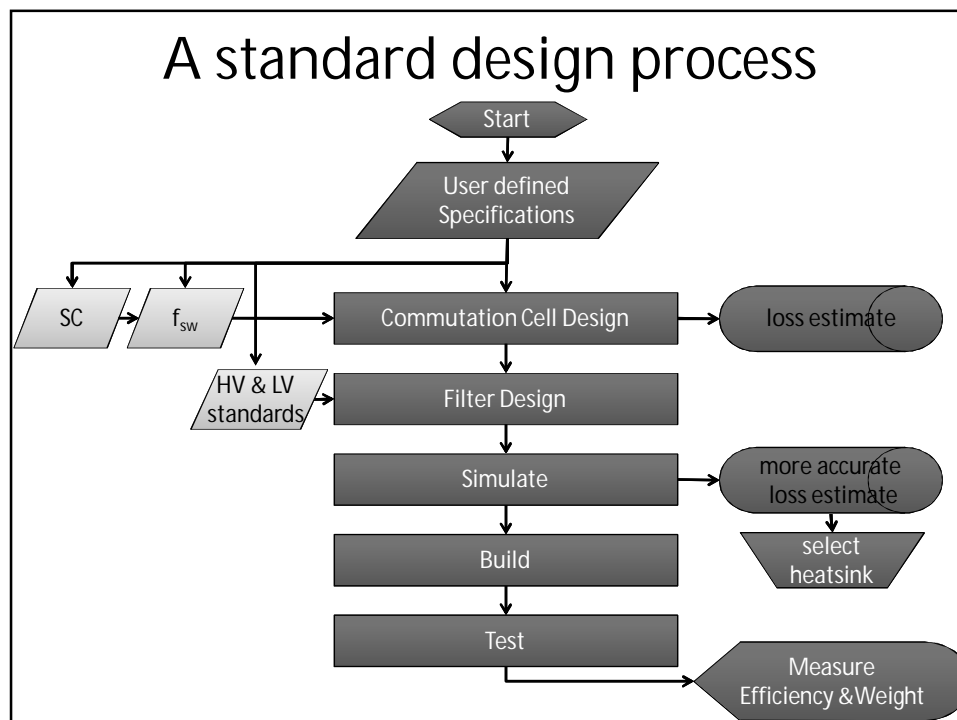

COMMUTATION CELL DESIGN

9

*Find the MacroSwitch
with the best efficiency*

Rules of the game

- a) Define a global switch requirement (Voltage current, Frequency, Duty Cycle, Case Temperature,..)
- b) Evaluate the limit of operation of a switch to determine how many must be connected in series and parallel to fulfill requirements
- c) Evaluate losses and other characteristics of the design
- d) Repeat a) to c) for each component and compare results and make a choice

10

1-Define MacroSwitch requirements

2-Find number of series connected switches

Voltage to be switched
+

Maximum collector-emitter voltage in switching mode

↓

Number of series connected switches

$$n_{Series} = \text{int}\left(\frac{V_{sw}}{V_{margin} J_{CE\ max}}\right) + 1$$

3-Find Maximum Current per switch for this profile : evaluate variation of losses as a function of the current

output characteristic IGBT-inverter (typical)
 $I_c = f(V_{CE})$
 $V_{GE} = 15\text{ V}$

$\Rightarrow P_{cond} = V_{CE} I = (V_T + R_T I) I = V_T I + R_T I^2$

switching losses IGBT-inverter (typical)
 $E_{on} = f(I_c), E_{off} = f(I_c)$
 $V_{GE} = \pm 15\text{ V}, R_{Gon} = 2.7\ \Omega, R_{Goff} = 4.7\ \Omega, V_{CE} = 900\text{ V}$

$\Rightarrow P_{sw} = f_{sw} E_{on,off} = f_{sw} (A_{on,off} + B_{on,off} I + C_{on,off} I^2)$

3-Find Maximum Current per switch for this profile :
solve thermal equation

Conduction losses
+
switching losses



$I_{max}(f_{sw})$

Conduction losses + Switching losses = Maximum Power extracted

$$D \cdot (R_T \cdot I^2 + V_T \cdot I) + f_{dec} \frac{V_{sw}}{n_{Series} V_{def}} [(A_{on} + A_{off}) + (B_{on} + B_{off}) \cdot I + (C_{on} + C_{off}) \cdot I^2] = \frac{\Delta\theta}{R_{th}}$$


$$\Delta_{Discriminant} = \left[D \cdot V_T + \frac{V_{sw}}{n_{Series} V_{def}} (B_{on} + B_{off}) \cdot f_{dec} \right]^2 - 4 \left[D \cdot R_T + \frac{V_{sw}}{n_{Series} V_{def}} (C_{on} + C_{off}) \cdot f_{dec} \right] \cdot \left[\frac{V_{sw}}{n_{Series} V_{def}} (A_{on} + A_{off}) \cdot f_{dec} - \frac{\Delta\theta}{R_{th}} \right]$$

$$\left[D \cdot R_T + \frac{V_{sw}}{n_{Series} V_{def}} (C_{on} + C_{off}) \cdot f_{dec} \right] \cdot I^2 + \left[D \cdot V_T + \frac{V_{sw}}{n_{Series} V_{def}} (B_{on} + B_{off}) \cdot f_{dec} \right] \cdot I + \left[\frac{V_{sw}}{n_{Series} V_{def}} (A_{on} + A_{off}) \cdot f_{dec} - \frac{\Delta\theta}{R_{th}} \right] = 0$$

$$I_{Pmax}(f) = \frac{- \left[D \cdot V_T + \frac{V_{sw}}{n_{Series} V_{def}} (B_{on} + B_{off}) \cdot f_{dec} \right] \pm \sqrt{\Delta_{Discriminant}}}{2 \left[D \cdot R_T + \frac{V_{sw}}{n_{Series} V_{def}} (C_{on} + C_{off}) \cdot f_{dec} \right]}$$

13

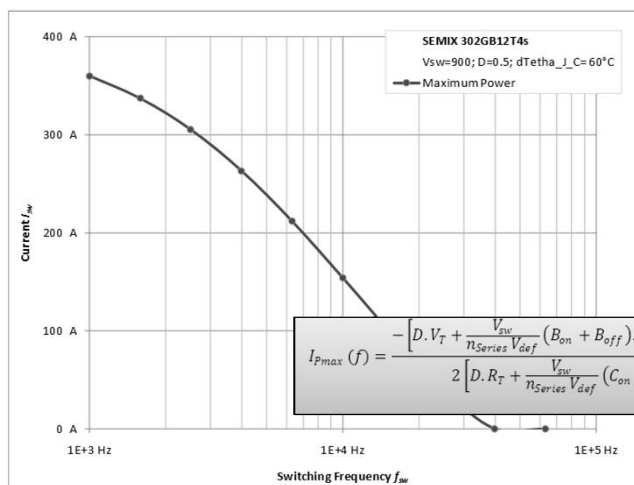
Current /frequency operating area of a switch
Maximum Power



14

4-Find number of parallel connected switches
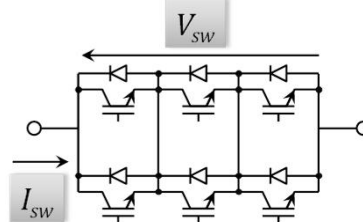
$$n_{Par} = \text{int} \left(\frac{I_{required}}{I_{max\ allowed}} \right) + 1$$




5-Find losses and efficiency

$$Pertes_{composant} = D \cdot \left(R_T \cdot \left(\frac{I}{n_{Par}} \right)^2 + V_T \cdot \frac{I}{n_{Par}} \right) + f_{dec} \cdot \frac{V_{SW}}{n_{Series} \cdot V_{def}} \left[(A_{on} + A_{off}) + (B_{on} + B_{off}) \cdot \frac{I}{n_{Par}} + (C_{on} + C_{off}) \cdot \left(\frac{I}{n_{Par}} \right)^2 \right]$$

$$Efficiency = 1 - \frac{n_{Series} \cdot n_{Par} \cdot Pertes_{composant}}{P_{out}}$$

18

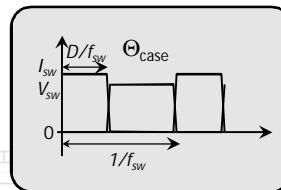6-Build a MacroSwitch with each component of the database





Explore IGBT database


Paramètres de la forme d'onde

Vsw	Isw	Dsw	fsw	Dtethasw
300 V	10 A	50 00%	0 Hz	50 °C


nSeries	Isw	nPar	Pertes	coeffPertes	(rappel)
7	10 A	10	396 W	0.54%	600 V
7	5 A	7	231 W	0.49%	600 V
7	5 A	7	231 W	0.49%	600 V
7	10 A	7	231 W	0.49%	600 V

19

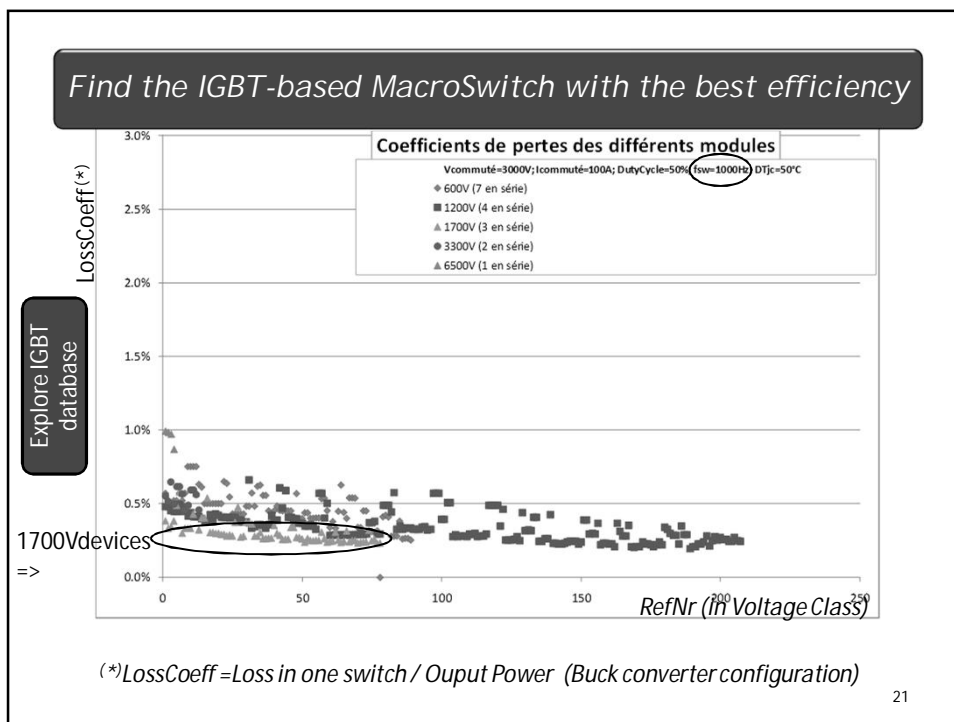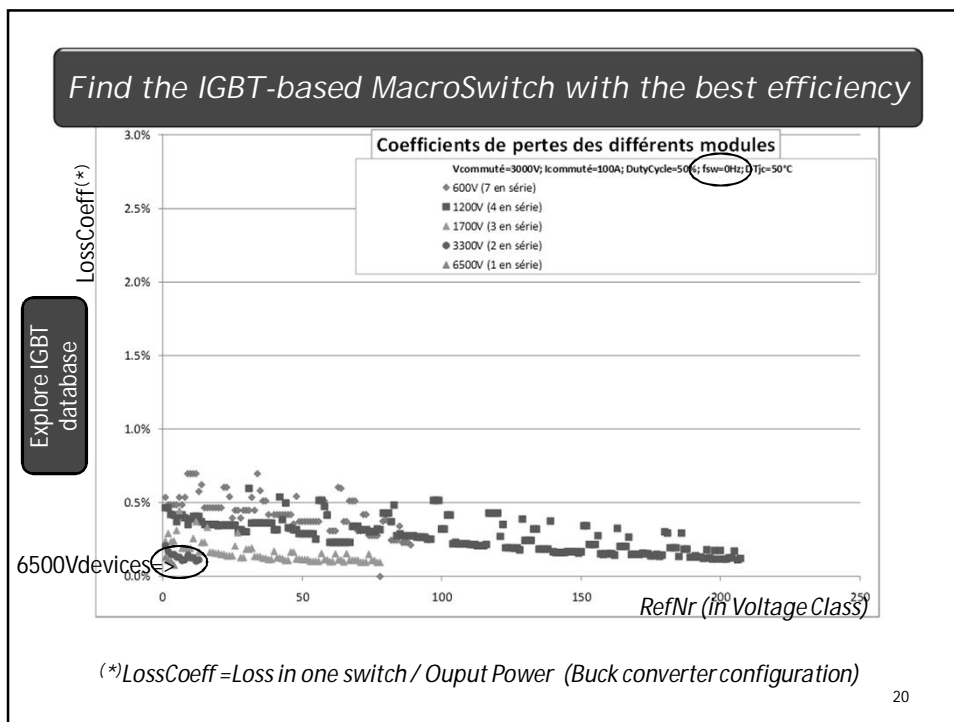

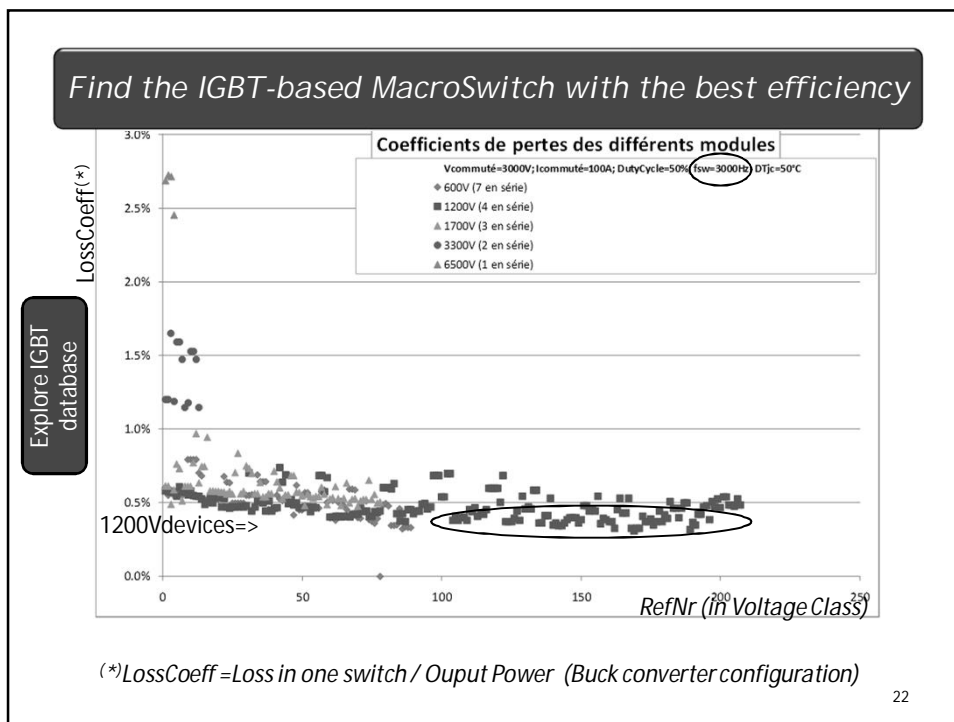

22

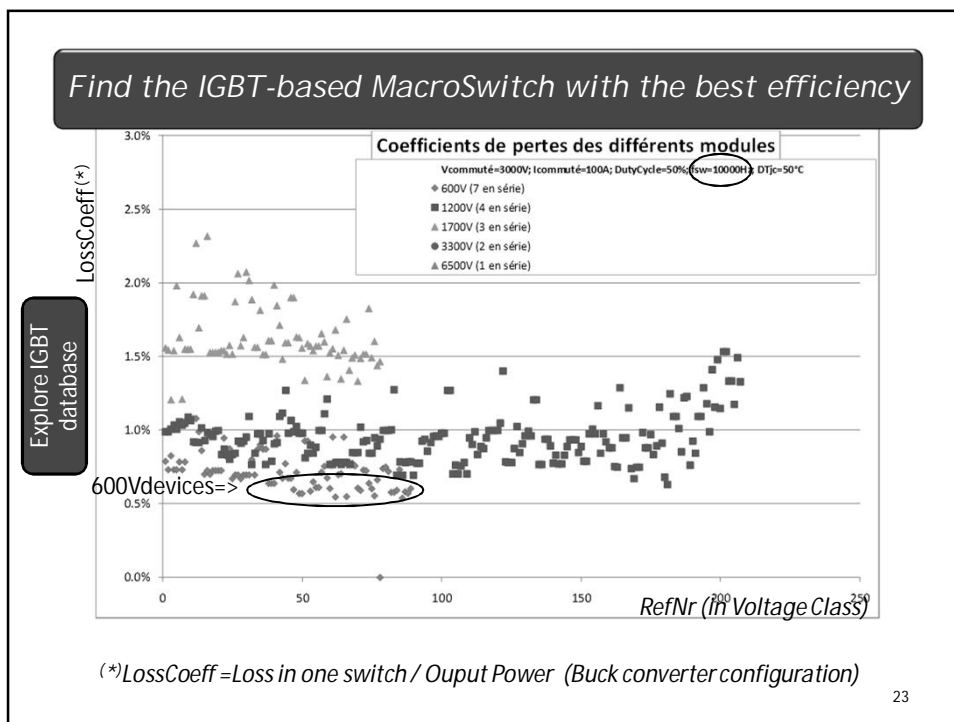

23

EXTENSION OF THE METHOD FOR VOLTAGE SOURCE INVERTERS WITH COMPLEX CONTROL PATTERNS

25

Rules of the game

Split the system in :

- a modulation/topology dependant subsystem,
- and a device specific subsystem.

$$P_{cond} = \frac{1}{T} \int_0^T v.i.dt = \frac{1}{T} \int_0^T (V_T + R_T i) i . dt = V_T \left(\frac{1}{T} \int_0^T i . dt \right) + R_T \left(\frac{1}{T} \int_0^T i^2 . dt \right) = V_T \cdot \bar{i}_{avg} + R_T \cdot \bar{i}_{RMS}^2$$

$$P_{switching} = f_{mod} \cdot \left(\sum_{OFF \rightarrow ON} \frac{V_{cell}}{V_{dof}} (A_{on} + B_{on} I_{cell} + C_{on} I_{cell}^2) + \sum_{ON \rightarrow OFF} \frac{V_{cell}}{V_{dof}} (A_{off} + B_{off} I_{cell} + C_{off} I_{cell}^2) \right)$$

$$P_{switching} = \frac{f_{mod}}{V_{dof}} \left(A_{on} \sum_{OFF \rightarrow ON} V_{cell\ on} + B_{on} \sum_{OFF \rightarrow ON} V_{cell\ on} I_{cell\ on} + C_{on} \sum_{OFF \rightarrow ON} V_{cell\ on} I_{cell\ on}^2 + A_{off} \sum_{ON \rightarrow OFF} V_{cell\ off} + B_{off} \sum_{ON \rightarrow OFF} V_{cell\ off} I_{cell\ off} + C_{off} \sum_{ON \rightarrow OFF} V_{cell\ off} I_{cell\ off}^2 \right)$$

26

PASSIVE COMPONENTS FOR MULTILEVEL CONVERTERS

31

Rules of the game


- Establish design criteria for filters and specific/internal components
- Apply them to all configuration
- Compare stored energy
- Evaluate converter size or cost based on a combined lost/stored energy criterion

32

FILTER DESIGN FOR MULTILEVEL CONVERTERS

33

Commutation Cell with Filters

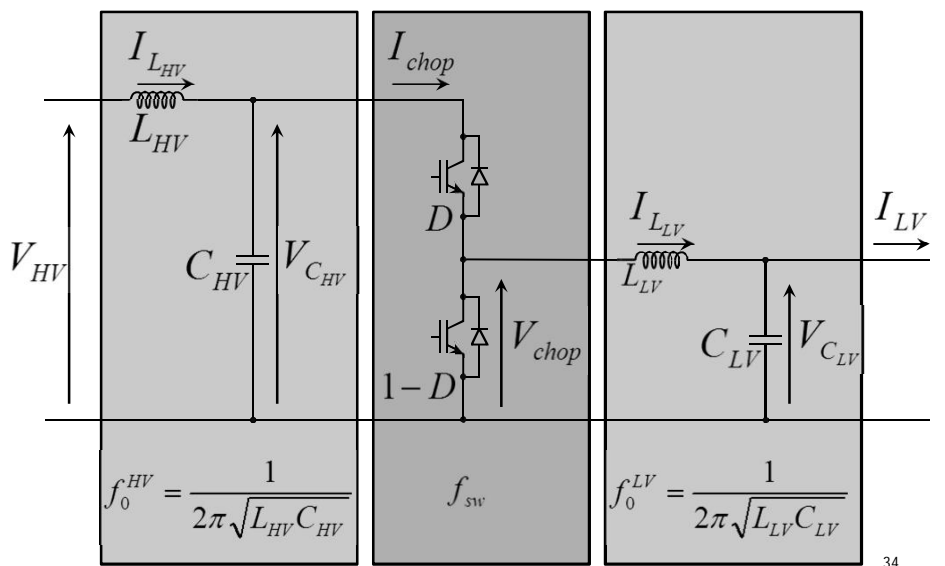


34

One (of the many) approach of filter design


Different functions of passive components

- Limit the impact of the converter on the external world :
=> limit the ripples of current on HV side and voltage on the LV side (Steady-state)
- Limit the impact of the external world on the converter :
=> limit HV and LV variations induced by load steps (Transient response)
- Limit the impact of the converter on itself :
=> limit the ripples of current ripple and HV voltage ripple (Steady-state)


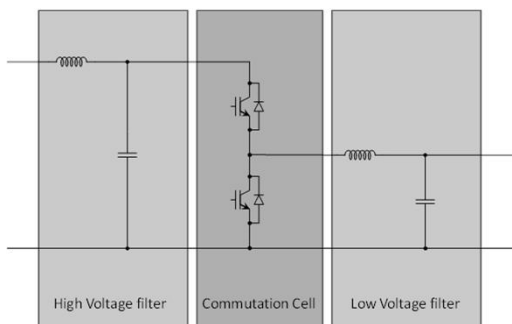


35

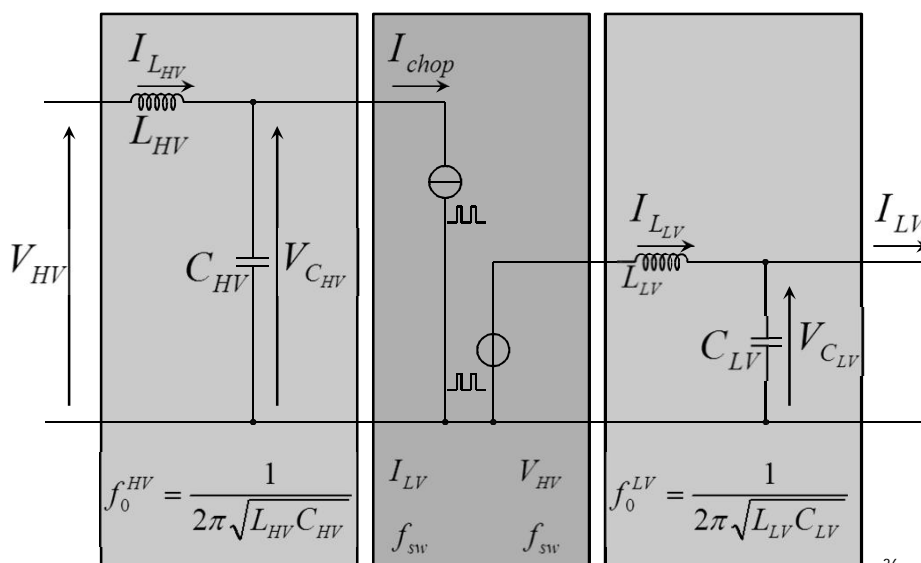AC Equivalent circuit of a Two-Level Cell



36

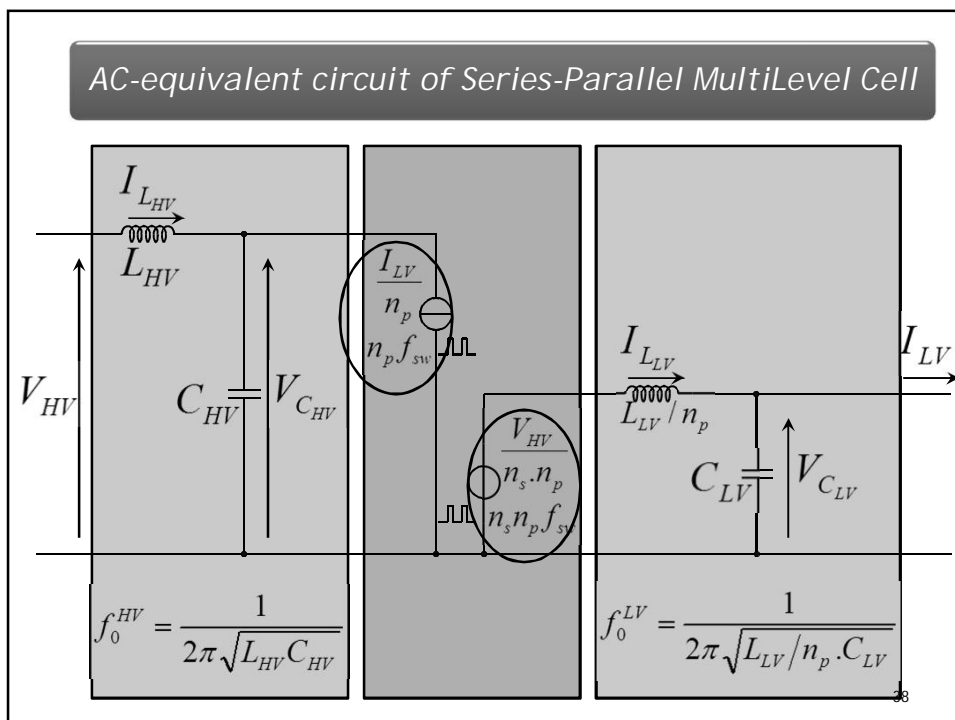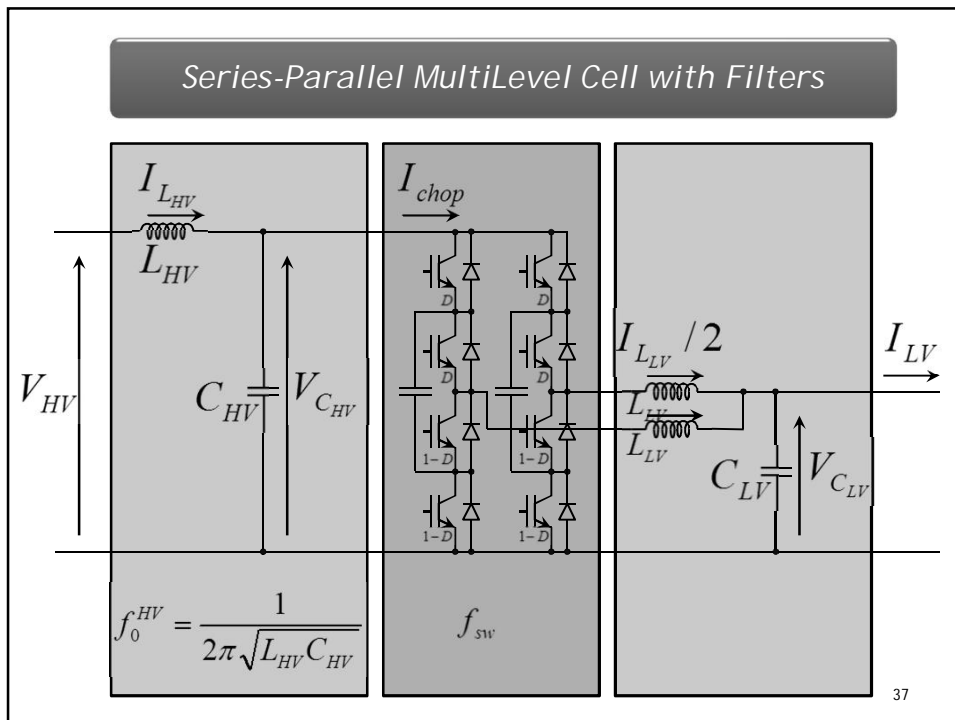

Req #1

Steady state, time domain : worst case ripples

Pulsation on the Low Voltage side (2nd order filter)

$$V_{ripple}^{LV} = \frac{V_{pk-ripple}^{LV}}{V_{HV}} = \frac{2}{\pi} \frac{1}{n_p n_s} \left(\frac{f_0^{LV}}{n_p n_s f_{sw}} \right)^2$$

$$f_0^{LV} = \frac{1}{2\pi \sqrt{L_{LV}/n_p \cdot C_{LV}}}$$

$$\Rightarrow \sqrt{L_{LV}/n_p \cdot C_{LV}} = \frac{1}{2\pi (n_p n_s)^{1.5} f_{sw} \sqrt{\frac{\pi}{2} V_{ripple}^{LV}}}$$

Pulsation on the High Voltage side (2nd order filter)

$$I_{ripple}^{HV} = \frac{I_{pk-ripple}^{HV}}{I_{LV,max}} = \frac{2}{\pi} \frac{1}{n_p} \left(\frac{f_0^{HV}}{n_p f_{sw}} \right)^2$$

$$f_0^{HV} = \frac{1}{2\pi \sqrt{L_{HV} \cdot C_{HV}}}$$

$$\Rightarrow \sqrt{L_{HV} \cdot C_{HV}} = \frac{1}{2\pi \cdot n_p^{1.5} f_{sw} \sqrt{\frac{\pi}{2} I_{ripple}^{HV}}}$$

39

Req #1



Ripples : from time domain to frequency domain



$$A_n = \frac{2V_{HV}}{n\pi} \sin(n\pi \cdot D) \quad \text{---} \quad B_n = \left(\frac{f_0}{f_{sw}} \right)^2 \frac{2V_{HV}}{n^3\pi} \sin(n\pi \cdot D)$$



-20dB/dcd + -40dB/dcd = -60dB/dcd



\Rightarrow Conclusion : the ripple requirement allows increasing f_0 when increasing $f_{switching}$

41

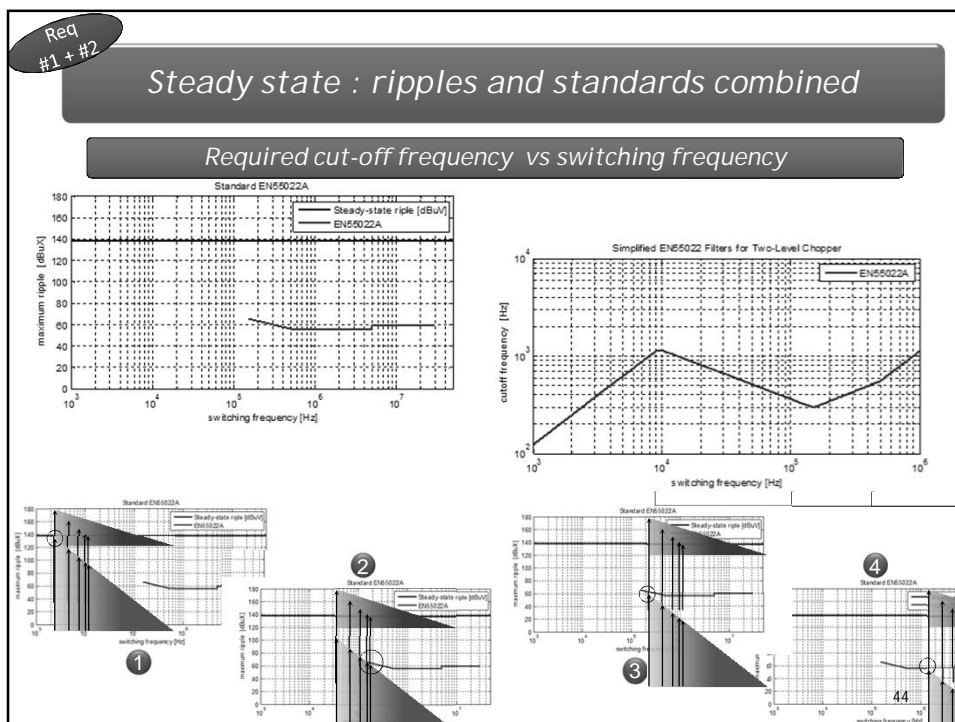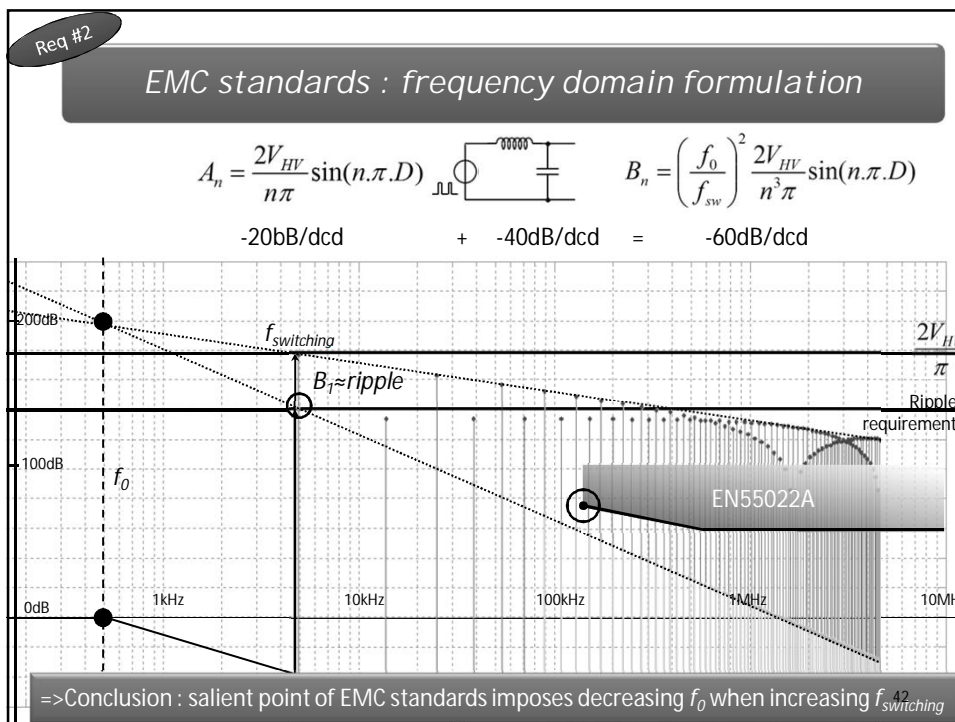

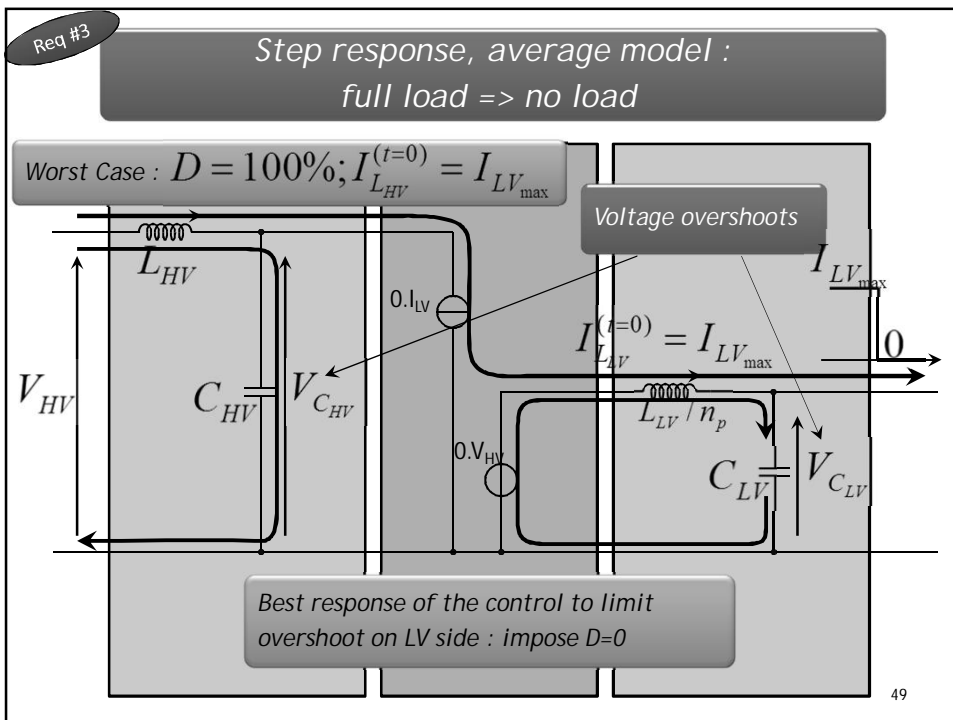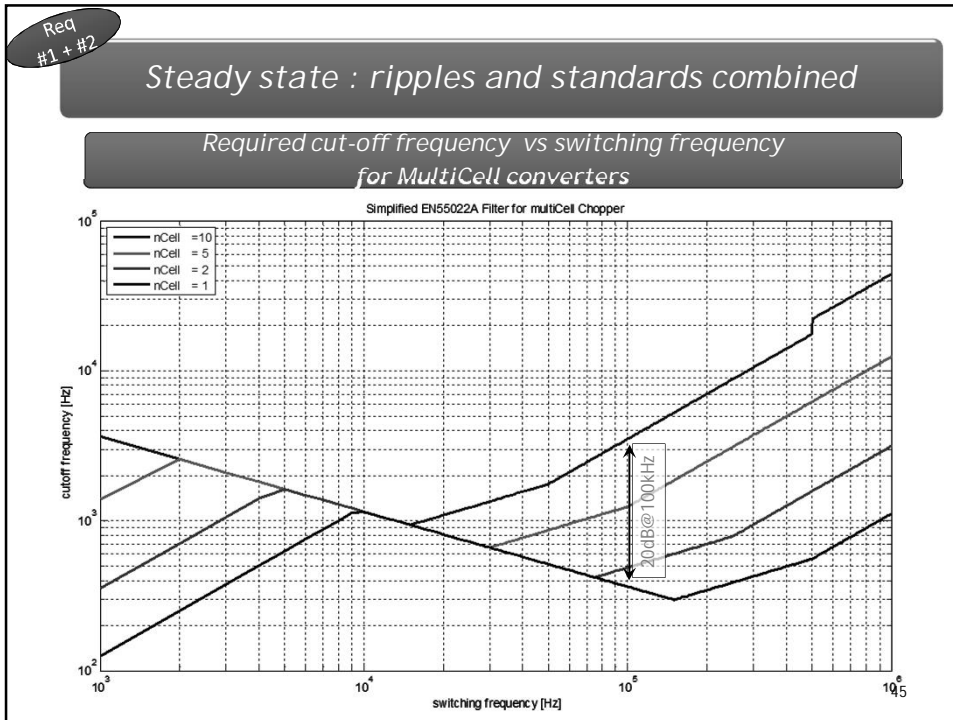

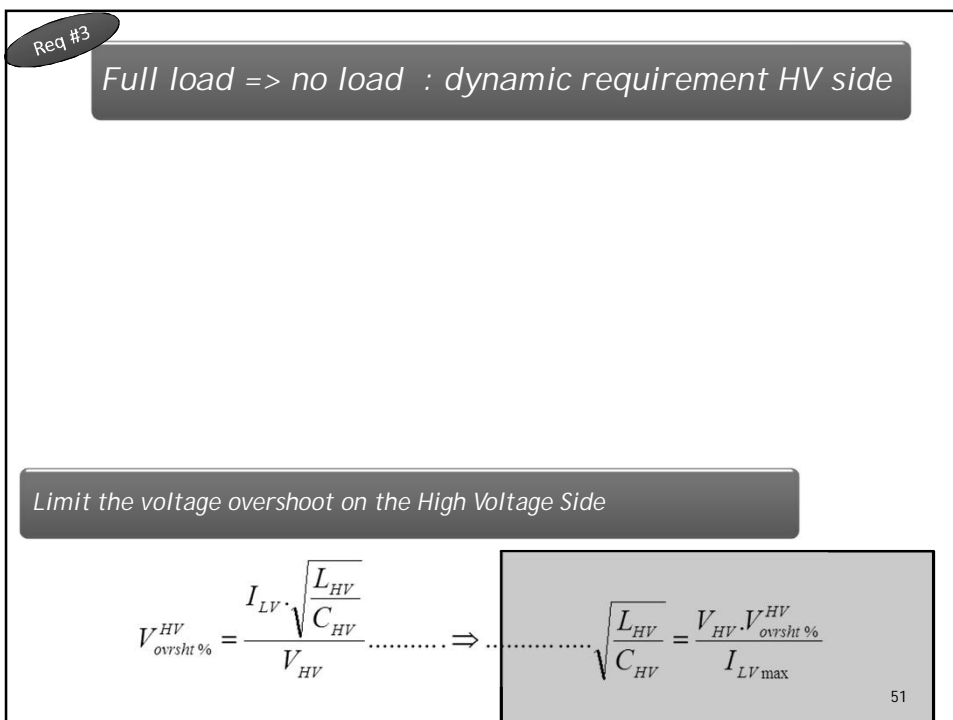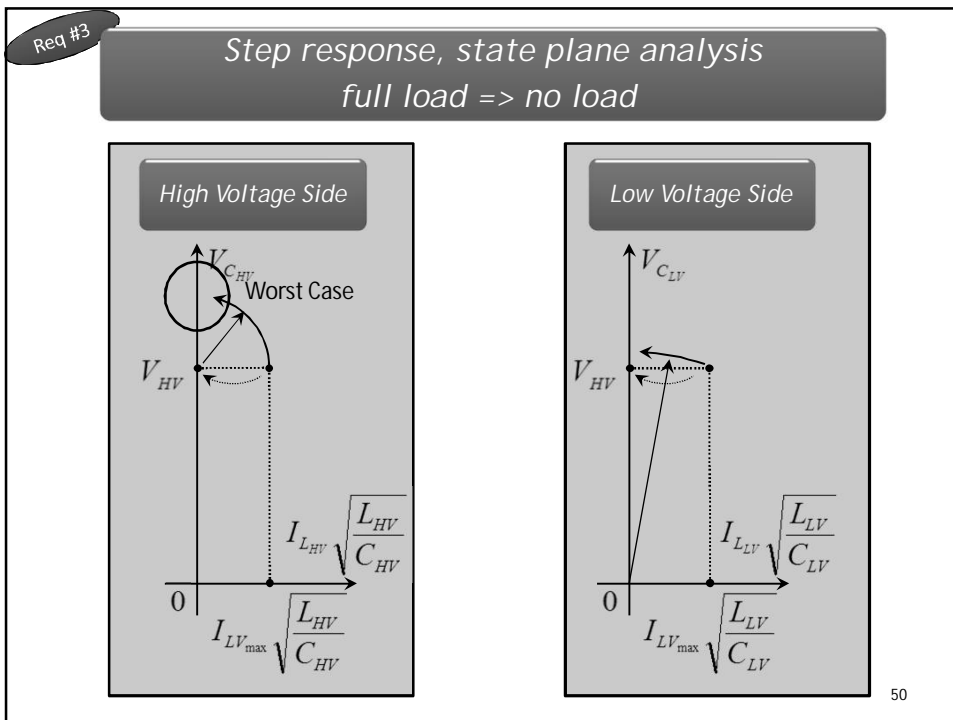

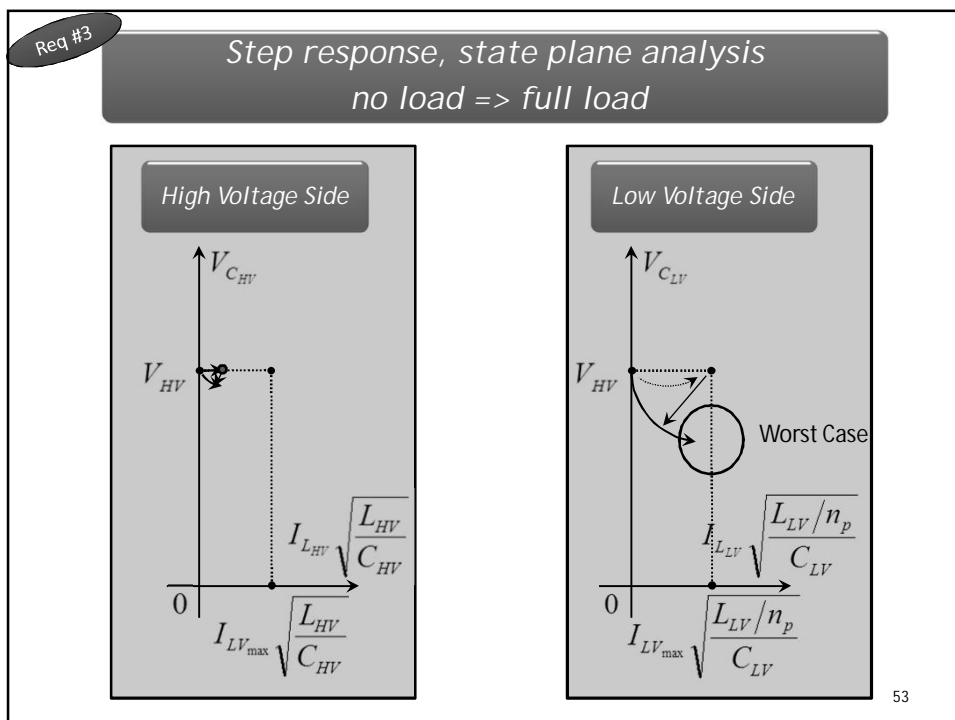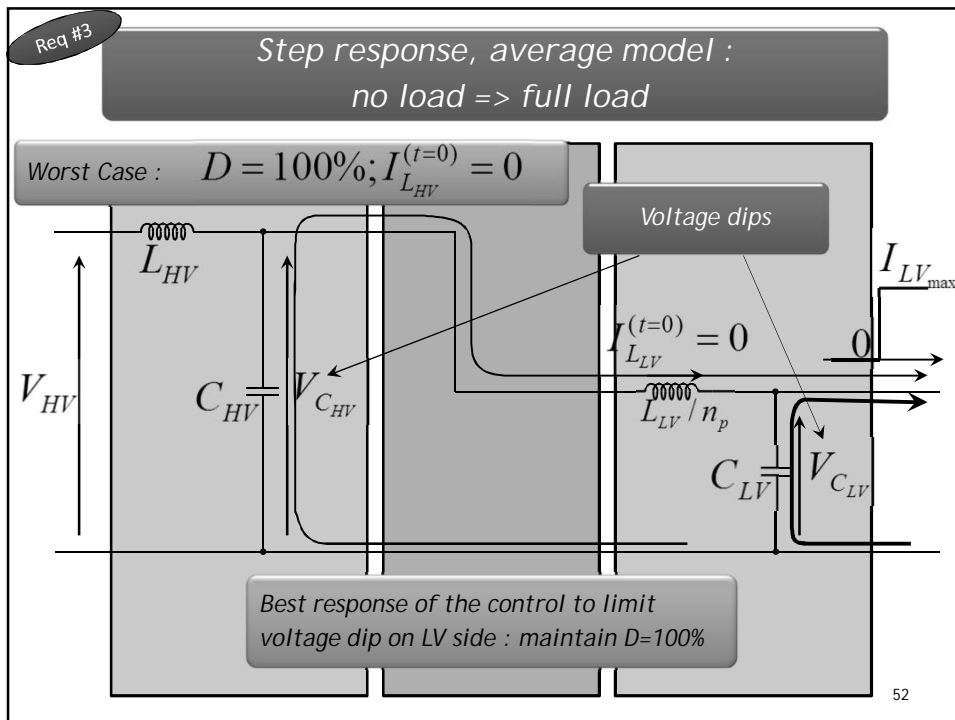

Req #3

No load => Full load : dynamic requirement LV side

Limit the voltage dip on the Low Voltage Side

$$V_{dip}^{LV} = \frac{I_{LV} \cdot \sqrt{\frac{L_{LV}}{n_p C_{LV}}}}{V_{HV}} \Rightarrow \sqrt{\frac{L_{LV}/n_p}{C_{LV}}} = \frac{V_{HV} \cdot V_{dip}^{LV}}{I_{LV_{max}}}$$

54

Req #1 + #2 + #3

Calculation of the components

High Voltage side

$$\left\{ \begin{aligned} n_{Cell} &= n_p \\ Rip_{\%} &= I_{ripple}^{HV} = \frac{I_{pk-ripple}^{HV}}{I_{LV_{max}}} \\ f_0 &= \frac{1}{2\pi \sqrt{L_{HV} \cdot C_{HV}}} \end{aligned} \right.$$

Low Voltage side

$$\left\{ \begin{aligned} n_{Cell} &= n_p \cdot n_s \\ Rip_{\%} &= V_{ripple}^{LV} = \frac{V_{pk-ripple}^{LV}}{V_{HV}} \\ f_0 &= \frac{1}{2\pi \sqrt{L_{LV}/n_p \cdot C_{LV}}} \end{aligned} \right.$$

$$f_0 = \min \left(n_{Cell}^{1.5} f_{sw} \sqrt{\frac{\pi}{2} Rip_{\%}} ; \sqrt{gab(\max(f_{salient}, n_{Cell} \cdot f_{sw})) \frac{\pi \cdot \max(f_{salient}, n_{Cell} \cdot f_{sw})^3}{2V_{HV} \cdot f_{sw}}} \right)$$

Valid for uncoupled AND coupled magnetic components

55

Req #1 + #2 + #3

Calculation of the components

High Voltage side

$$\begin{cases} \sqrt{\frac{L_{HV}}{C_{HV}}} = \frac{V_{HV} \cdot V_{ovrsh\%}^{HV}}{I_{LV\max}} \\ \sqrt{L_{HV} \cdot C_{HV}} = \frac{1}{2\pi \cdot f_0^{HV}} \end{cases}$$

$$\Rightarrow \begin{cases} L_{HV} = \frac{V_{HV} \cdot V_{ovrsh\%}^{HV}}{2\pi \cdot f_0^{HV} \cdot I_{LV\max}} \\ C_{HV} = \frac{I_{LV\max}}{2\pi \cdot f_0^{HV} \cdot V_{HV} \cdot V_{ovrsh\%}^{HV}} \end{cases}$$

Low Voltage side

$$\begin{cases} \sqrt{\frac{L_{LV}/n_p}{C_{LV}}} = \frac{V_{HV} \cdot V_{dip\%}^{LV}}{I_{LV\max}} \\ \sqrt{L_{LV}/n_p \cdot C_{LV}} = \frac{1}{2\pi \cdot f_0^{LV}} \end{cases}$$

$$\Rightarrow \begin{cases} L_{LV}/n_p = \frac{V_{HV} \cdot V_{dip\%}^{LV}}{2\pi \cdot f_0^{LV} \cdot I_{LV\max}} \\ C_{LV} = \frac{I_{LV\max}}{2\pi \cdot f_0^{LV} \cdot V_{HV} \cdot V_{dip\%}^{LV}} \end{cases}$$

Valid for uncoupled AND coupled magnetic components

56



Req #1 + #2 + #3



Calculation of the components


Example #1 : 2-level converter
 => from 10 to 150kHz, the tendency is an *increase* of passive components

MultiCell Chopper with: nS=1; VHV=800; ILVmax=250; IHVmax=125; relativeOutRipple=0.01; VHVovershoot=0.1; VLVdip=0.05; standardHV=HV/DCA; standardLV=EN65022A

57

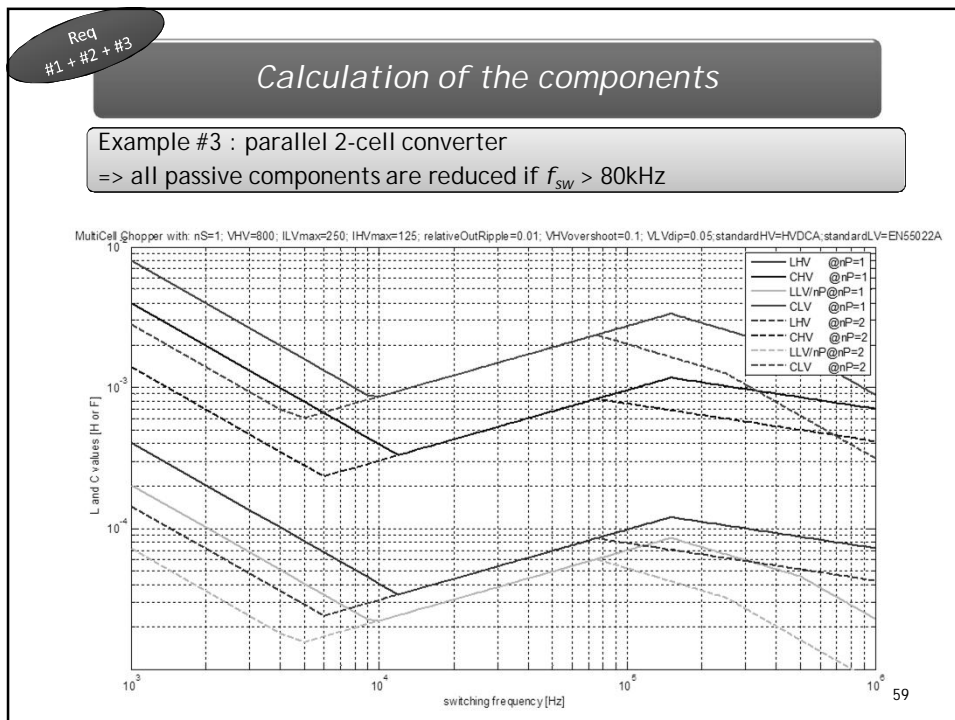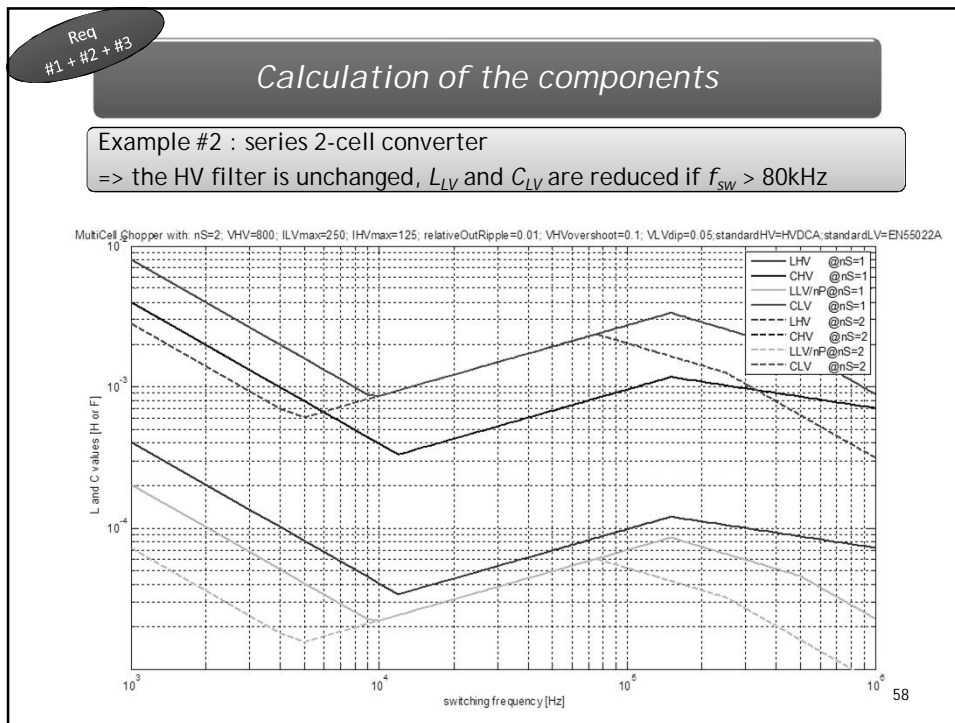

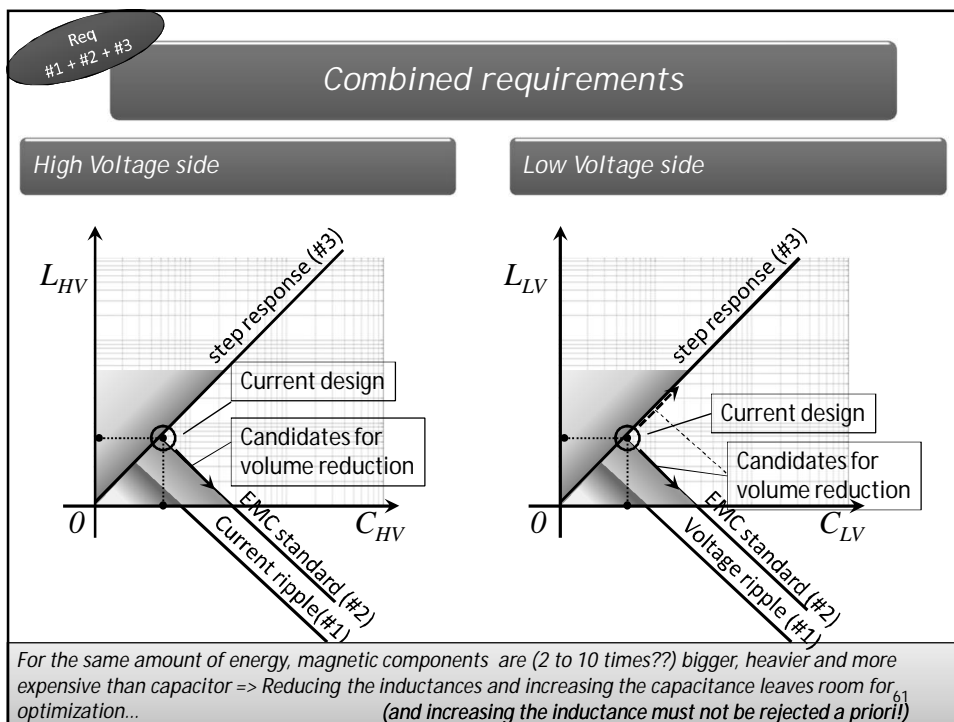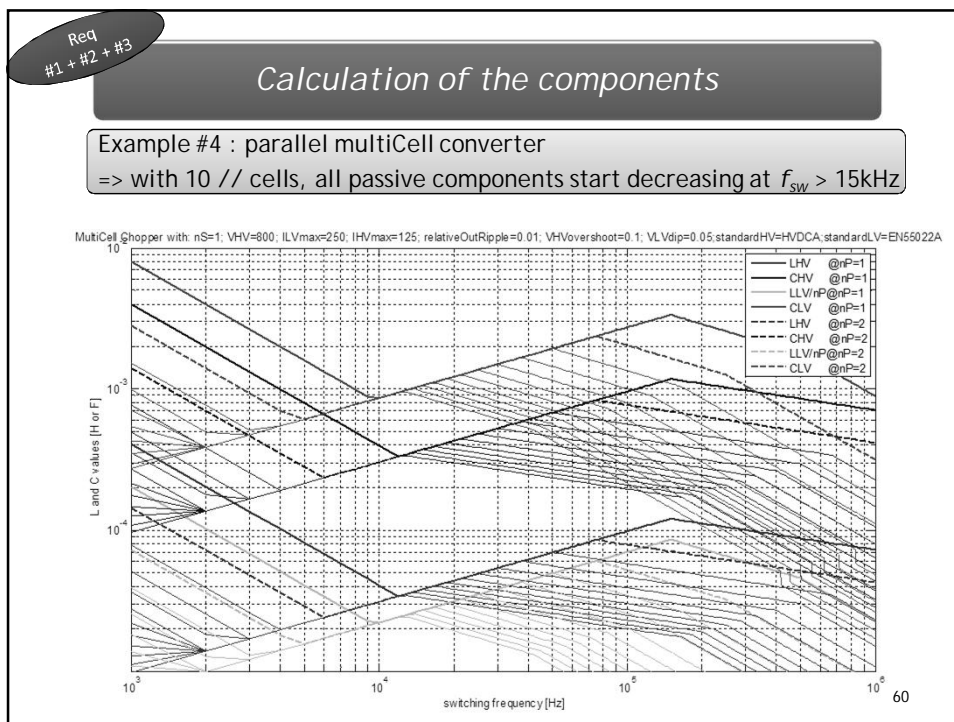

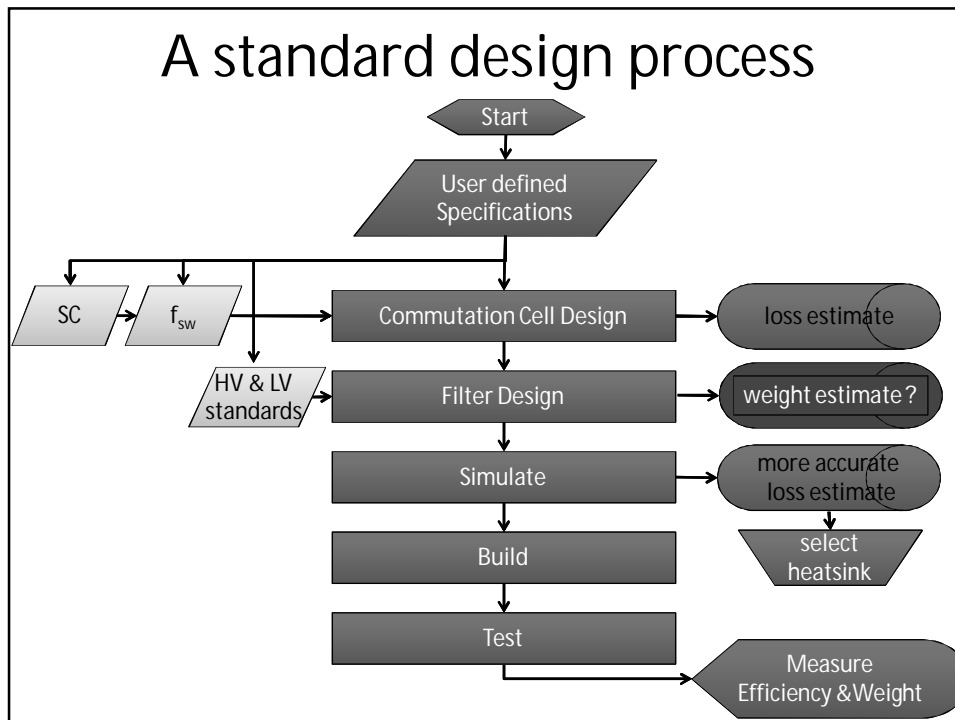


VOLUME OF PASSIVE COMPONENTS AND
FILTERS FOR MULTILEVEL CONVERTERS

Area Product of Magnetic Components : Inductors

Basic formulation

$$\hat{B} = \frac{L \cdot \hat{I}}{n_t \cdot A_c}$$
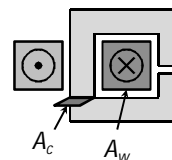
$$j_{eff} = \frac{n_t \cdot I_{eff}}{k_w \cdot A_w}$$



$$A_w \cdot A_c = L \cdot \hat{I} \cdot \frac{I_{eff}}{\hat{B} \cdot k_w \cdot j_{eff}}$$


Advantage : allows selecting the core

Drawback : L , I^{\wedge} and I_{eff} are not independent variables so the influence of L for example is not obvious

Taking into account : $L = \frac{V}{4\Delta I \cdot f}$; $\hat{I} = I_{DC} \cdot \left(1 + \frac{\Delta I}{2I_{DC}}\right)$ and $I_{eff} = I_{DC} \sqrt{1 + \frac{1}{12} \left(\frac{\Delta I}{I_{DC}}\right)^2}$

we get :
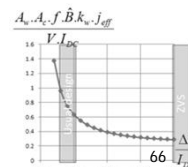
$$A_w \cdot A_c = \frac{V \cdot I_{DC} \cdot \left(1 + \frac{\Delta I}{2I_{DC}}\right) \cdot \sqrt{1 + \frac{1}{12} \left(\frac{\Delta I}{I_{DC}}\right)^2}}{4 \left(\frac{\Delta I}{I_{DC}}\right) \cdot f \cdot \hat{B} \cdot k_w \cdot j_{eff}}$$



Area Product of Magnetic Components : Inductors

Improved

Improved formulation #3 : combining copper losses and core losses


Limits on Core Loss Density and Copper Loss Density can be combined to form an Improved Normalized Area Product :

$$NAP_{core}^{copper} = \frac{A_c \cdot A_w \cdot B_{sat} \cdot f \cdot k_w \cdot j_{eff}}{V \cdot I_{DC}} = \frac{1}{8} \max \left(1 + \frac{2}{\Delta I / I_{DC}} ; \frac{B_{sat}}{B_{ACmax}} \right) \cdot \sqrt{1 + \frac{R_{AC}}{R_{DC}} \frac{1}{12} \left(\frac{\Delta I}{I_{DC}} \right)^2}$$

Though elegant, this formulation could be misleading :

B_{ACmax} and R_{AC}/R_{DC} are very difficult to determine a priori :

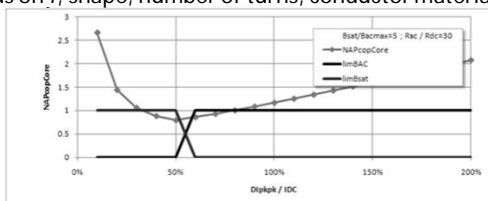- B_{ACmax} should be chosen to limit core temperature rise which in practice depends on f and core material (loss), size (volume/surface ratio), shape, cooling conditions...
- R_{AC}/R_{DC} depends on f , shape, number of turns, conductor material...




Area Product of Magnetic Components : Inductors

Basic formulation

Interleaved converters with uncoupled inductors

NVol

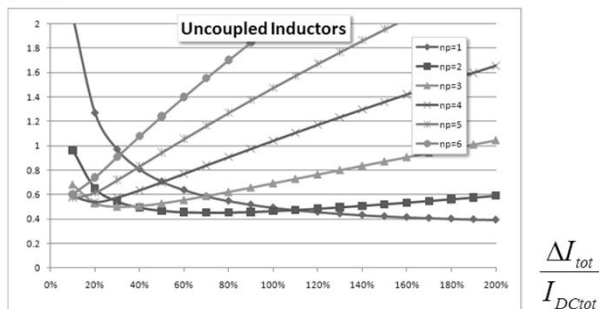


$$NVol = \frac{Vol_{tot}}{K_{shape}} \cdot \left(\frac{\hat{B} \cdot f \cdot k_w \cdot j_{eff}}{V \cdot I_{DCtot}} \right)^{3/4} = n_p \cdot \left(\frac{1}{8n_p} \left(1 + \frac{2I_{DCtot}}{n_p^2 \cdot \Delta I_{tot}} \right) \sqrt{1 + \frac{1}{12} \left(\frac{n_p^2 \cdot \Delta I_{tot}}{I_{DCtot}} \right)^2} \right)^{3/4}$$

Area Product of Magnetic Components : Inductors

Improved formulation

Interleaved converters with uncoupled inductors

NVol

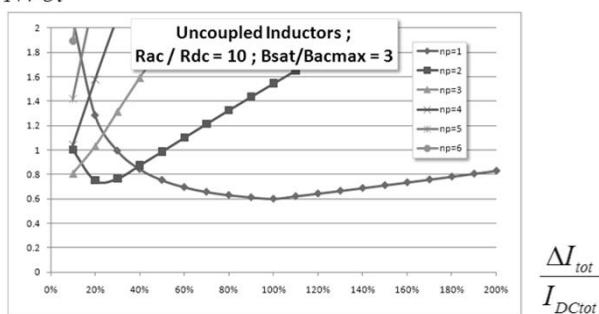

$$NVol = \frac{Vol_{tot}}{K_{shape}} \cdot \left(\frac{B_{sat} \cdot f \cdot k_w \cdot j_{eff}}{V \cdot I_{DC}} \right)^{3/4} = n_p \cdot \left(\frac{1}{8n_p} \max \left(1, \frac{2}{n_p^2 \cdot \Delta I_{tot} / I_{DCtot}} \cdot \frac{B_{sat}}{B_{ACmax}} \right) \sqrt{1 + \frac{R_{AC}}{R_{DC}} \frac{1}{12} \left(\frac{n_p^2 \cdot \Delta I_{tot}}{I_{DCtot}} \right)^2} \right)^{3/4}$$


Area Product of Magnetic Components : ICTs

Basic formulation

Interleaved converters with coupled inductors (or InterCell Transformers = ICTs)

Compared with uncoupled inductors:

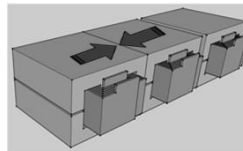- Fluxes unchanged ,
- Current ripples reduced



$$\left. \begin{aligned} \Delta I_{tot} &= \frac{\Delta I_{ind} \cdot n_p}{n_p} \\ I_{DCtot} &= n_p \cdot I_{DCind} \end{aligned} \right\} \Rightarrow \frac{\Delta I_{ind}}{I_{DCind}} = \frac{n_p \Delta I_{tot} / n_p}{I_{DCtot} / n_p} \cdot n_p^2 \frac{\Delta I_{tot}}{I_{DCtot}}$$

=> Total volume of the n_p coupled inductors :

$$Vol_{tot} = n_p \cdot K_{shape} \left(\frac{V \cdot I_{DCtot} \cdot \left(1 + \frac{2I_{DCtot}}{n_p^2 \cdot \Delta I_{tot}} \right) \sqrt{1 + \frac{1}{12} \left(\frac{n_p^2 \cdot \Delta I_{tot}}{I_{DCtot}} \right)^2}}{8 \hat{B} \cdot f \cdot k_w \cdot j_{eff}} \right)^{3/4}$$


77

Area Product of Magnetic Components : ICTs

Basic formulation

Interleaved converters with coupled inductors (or InterCell Transformers = ICTs)

NVol

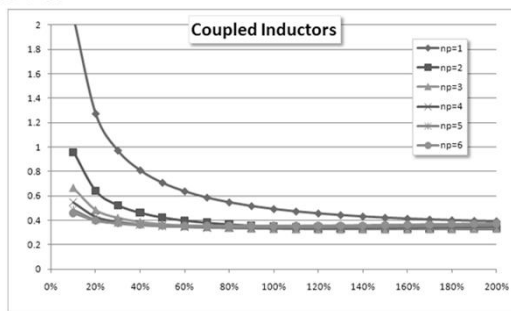

$$NVol = \frac{Vol_{tot}}{K_{shape}} \cdot \left(\frac{\hat{B} \cdot f \cdot k_w \cdot j_{eff}}{V \cdot I_{DC}} \right)^{3/4} = n_p \cdot \left(\frac{1}{8n_p} \left(1 + \frac{2I_{DCtot}}{n_p^2 \cdot \Delta I_{tot}} \right) \sqrt{1 + \frac{1}{12} \left(\frac{\Delta I_{tot}}{I_{DCtot}} \right)^2} \right)^{3/4}$$


78

Area Product of Magnetic Components : ICTs

Improved formulation

Interleaved converters with coupled inductors (or InterCell Transformers = ICTs)

NVol

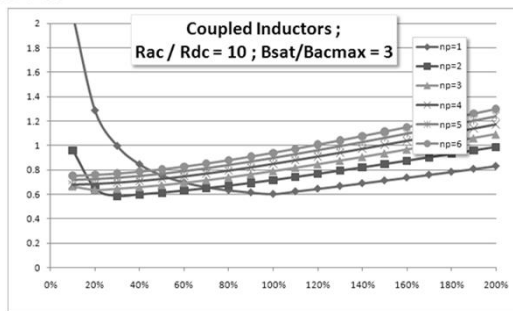

Excel Link

$\frac{\Delta I_{tot}}{I_{DCtot}}$

$$NVol = \frac{Vol_{tot}}{K_{shape}} \cdot \left(\frac{B_{sat} \cdot f \cdot k_w \cdot j_{eff}}{V \cdot I_{DC}} \right)^{3/4} = n_p \cdot \left(\frac{1}{8n_p} \max \left(1 + \frac{2}{n_p^2} \frac{\Delta I_{tot} / I_{DCtot}}{B_{ACmax}} ; \frac{B_{sat}}{B_{ACmax}} \right) \sqrt{1 + \frac{R_{AC}}{R_{DC}} \frac{1}{12} \left(\frac{\Delta I_{tot}}{I_{DCtot}} \right)^2} \right)^3$$

79

Minimum volume of LV-side uncoupled inductors and InterCell Transformers

Crossing($f_1=f_2$)

$$1 + \frac{2}{n_p^2 \Delta I_{tot} / I_{DCtot}} = \frac{B_{sat}}{B_{ACmax}} \Leftrightarrow \Delta I_{tot} / I_{DCtot} = \frac{2}{n_p^2} \frac{\frac{B_{ACmax}}{B_{sat}}}{1 - \frac{B_{ACmax}}{B_{sat}}}$$

⇒ Ripple giving the minimum volume of Magnetic Component :

uncoupled

$$\chi = \min \left(\frac{1}{n_p^2} \sqrt[3]{\frac{24}{R_{AC}/R_{DC}}} ; \frac{2}{n_p^2} \frac{\frac{B_{ACmax}}{B_{sat}}}{1 - \frac{B_{ACmax}}{B_{sat}}} \right)$$


coupled

$$\chi = \min \left(\frac{1}{n_p^2} \sqrt[3]{\frac{24}{R_{AC}/R_{DC}}} ; \frac{2}{n_p^2} \frac{\frac{B_{ACmax}}{B_{sat}}}{1 - \frac{B_{ACmax}}{B_{sat}}} \right)$$

85

Minimum volume of LV-side uncoupled inductors and InterCell Transformers

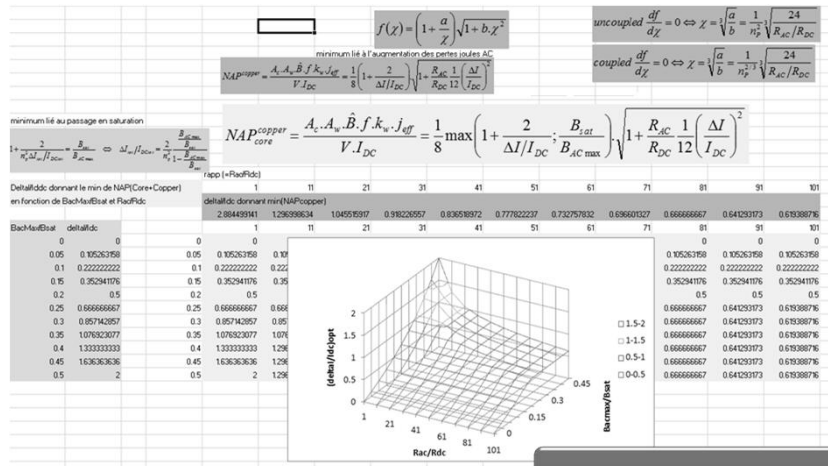
Ripple giving the minimum volume (as a function of B_{ACmax}/B_{sat} and $\Delta I/I_{DC}$)







Cf ProduitAire Selfs&ICTs.xls



Minimum volume of LV-side uncoupled inductors and InterCell Transformers


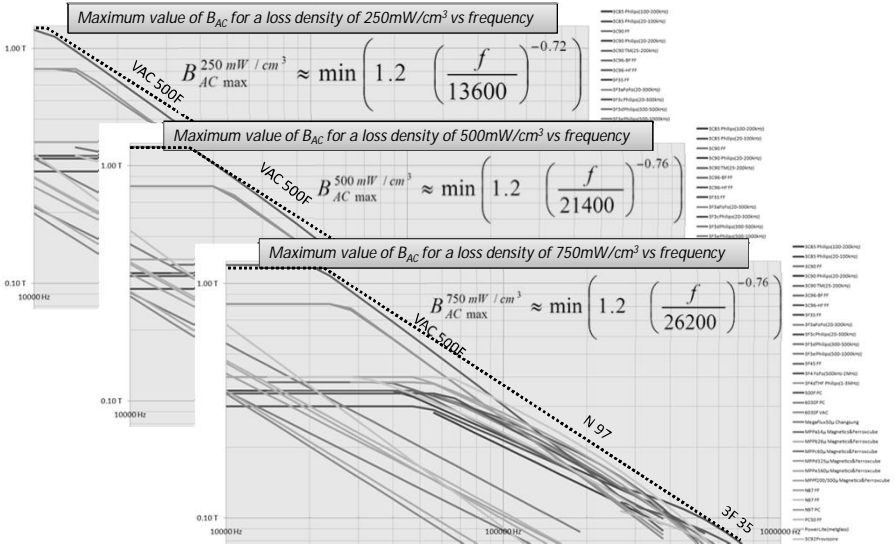
Technology-related data : Core loss limitation



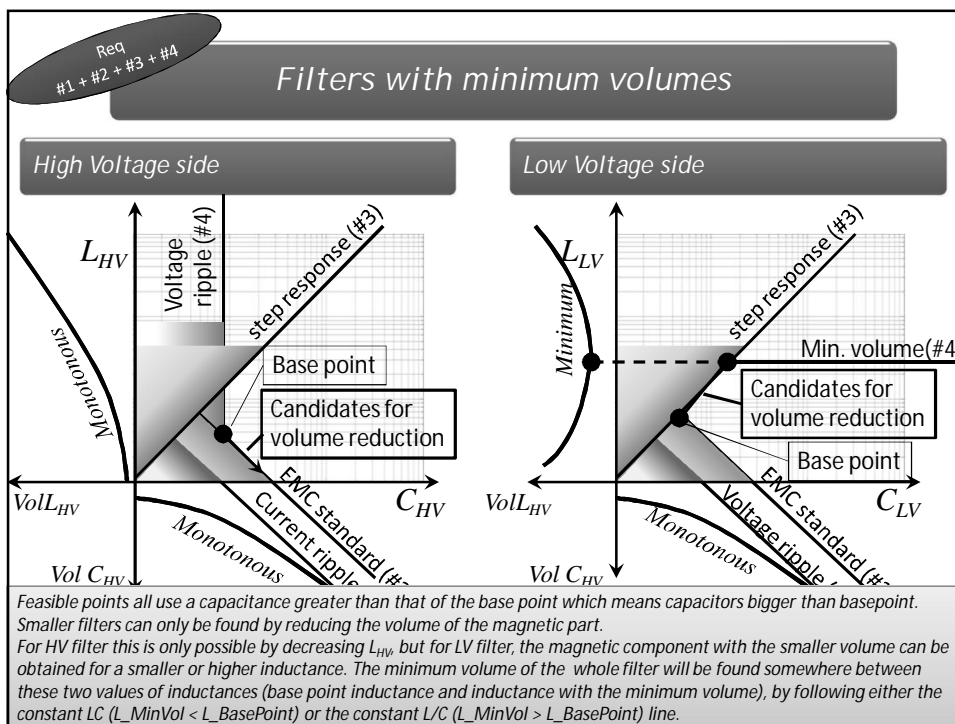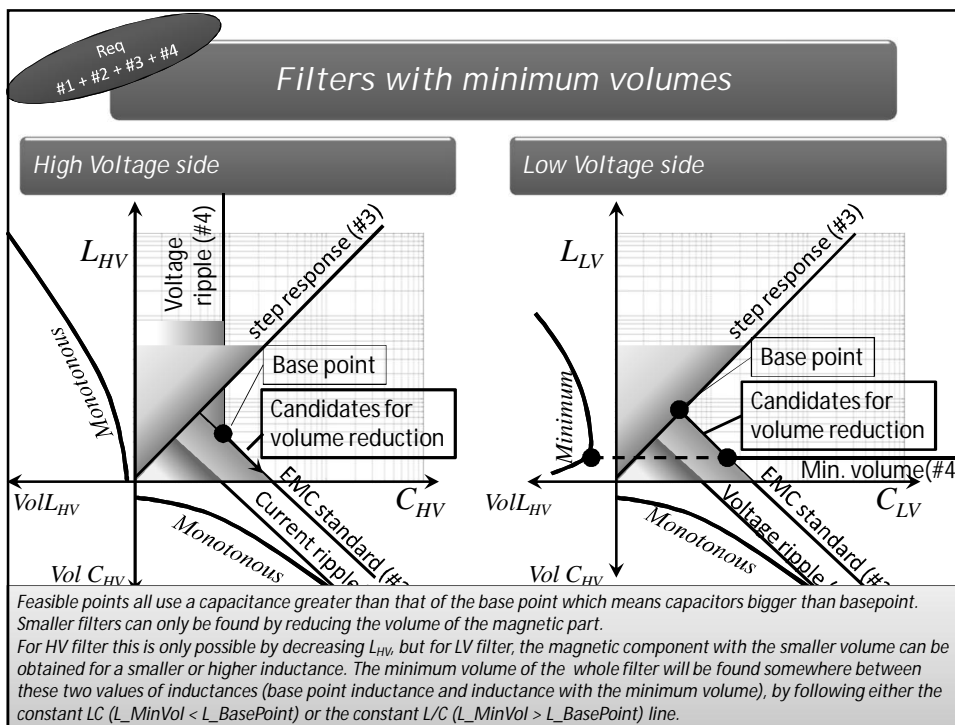


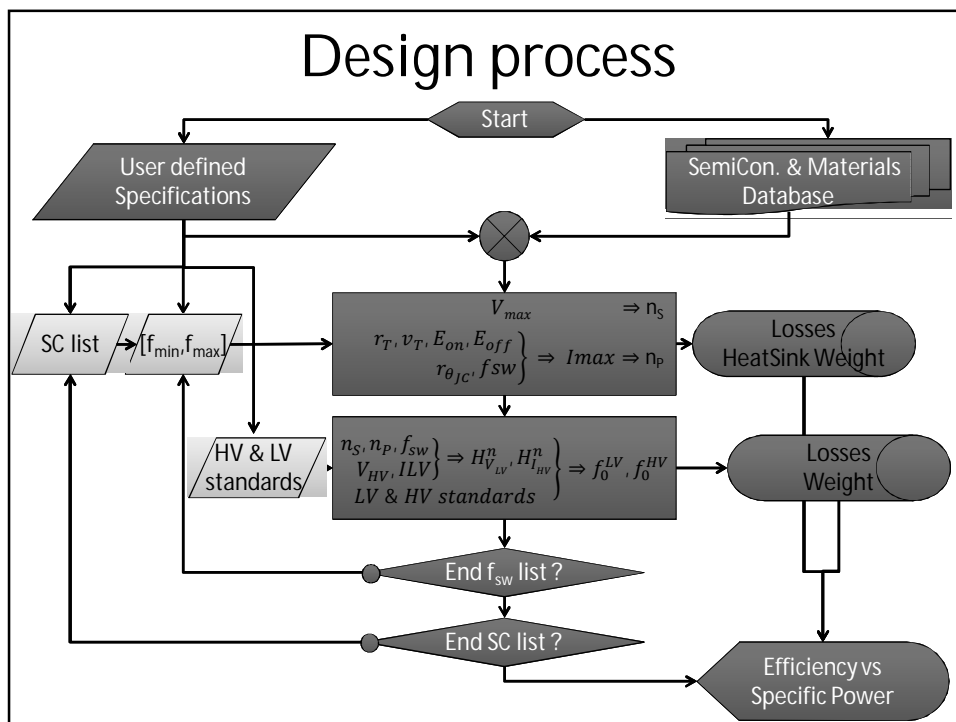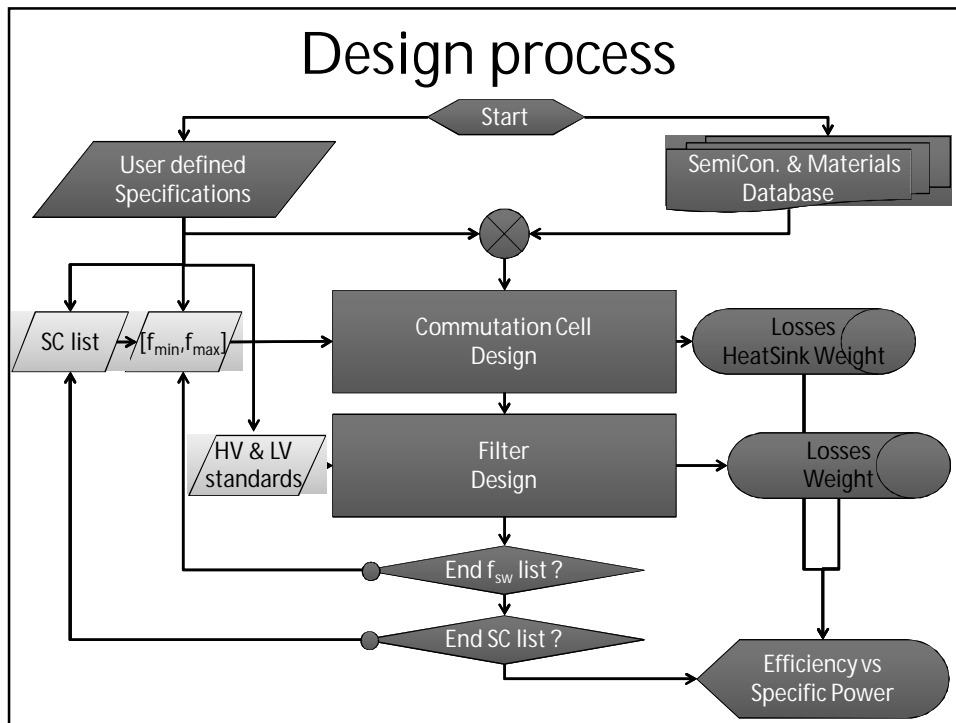

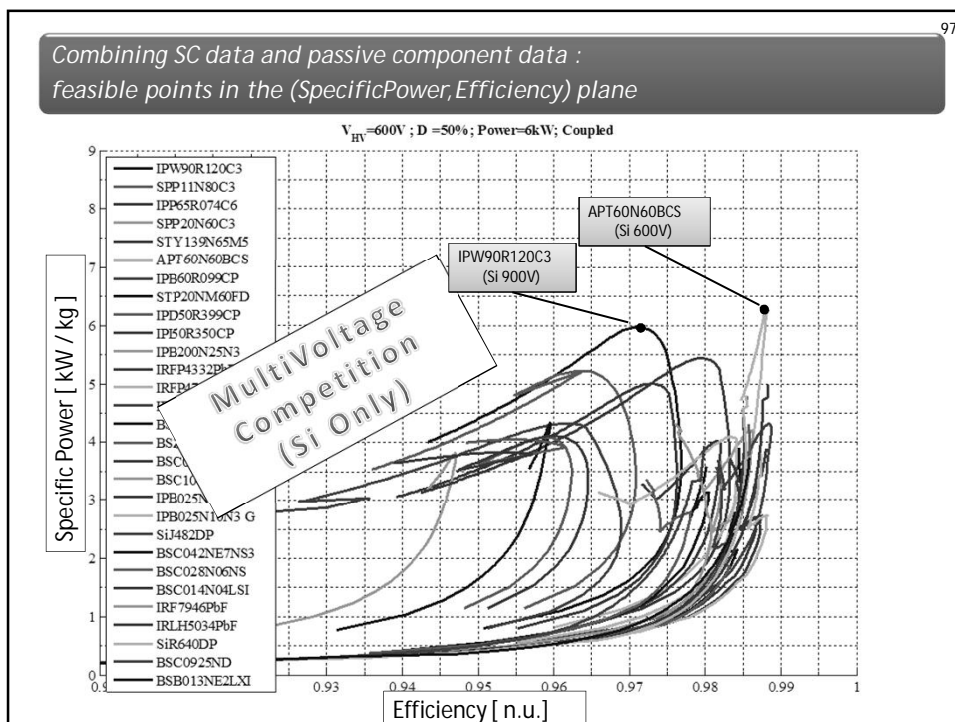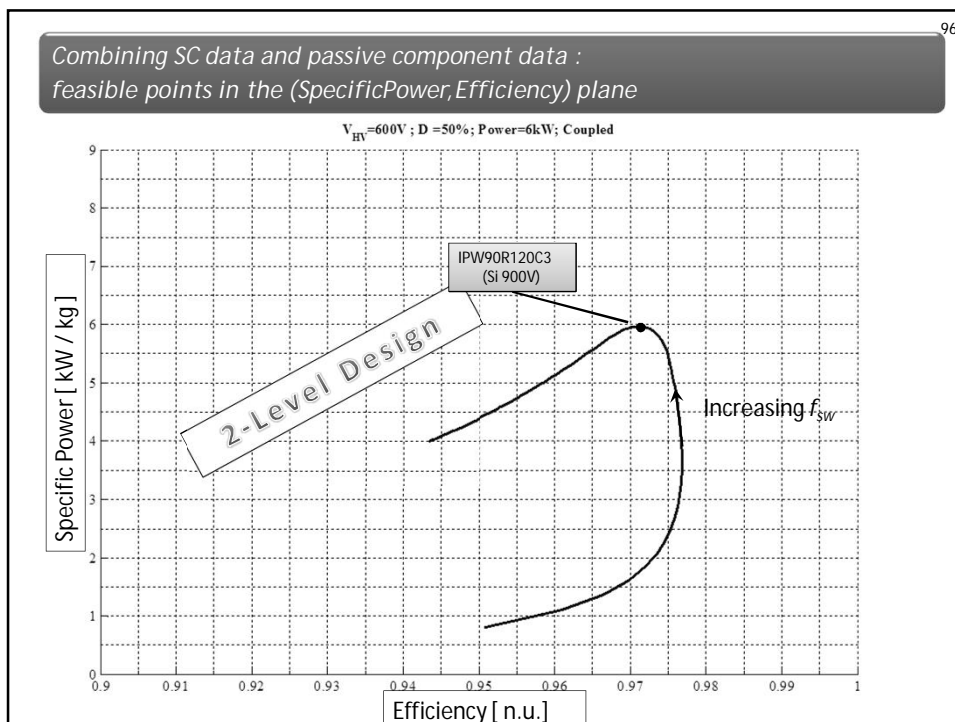


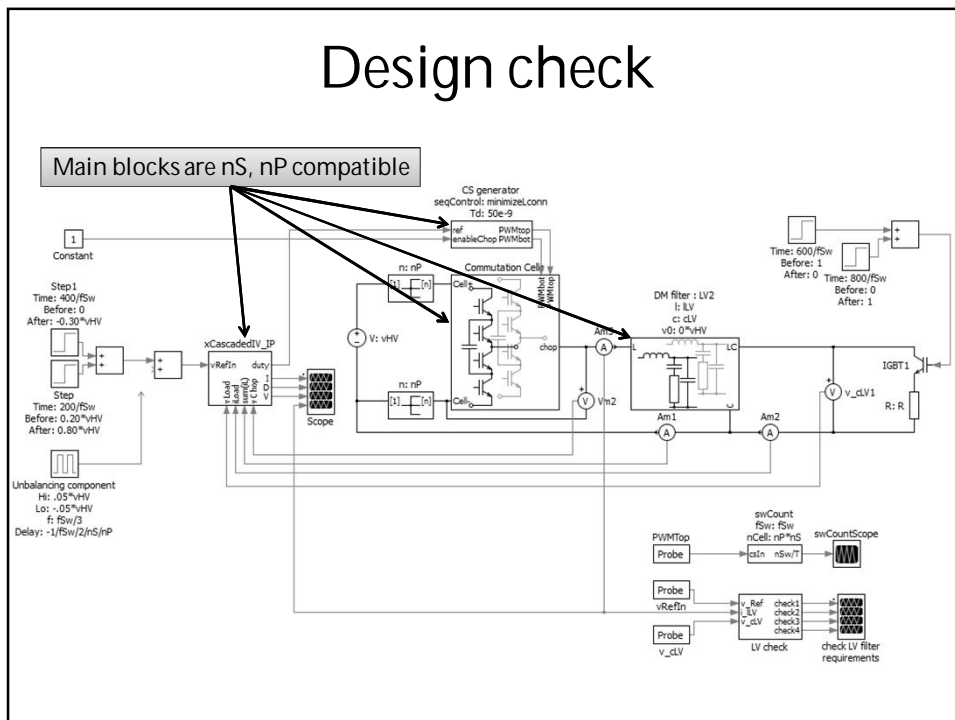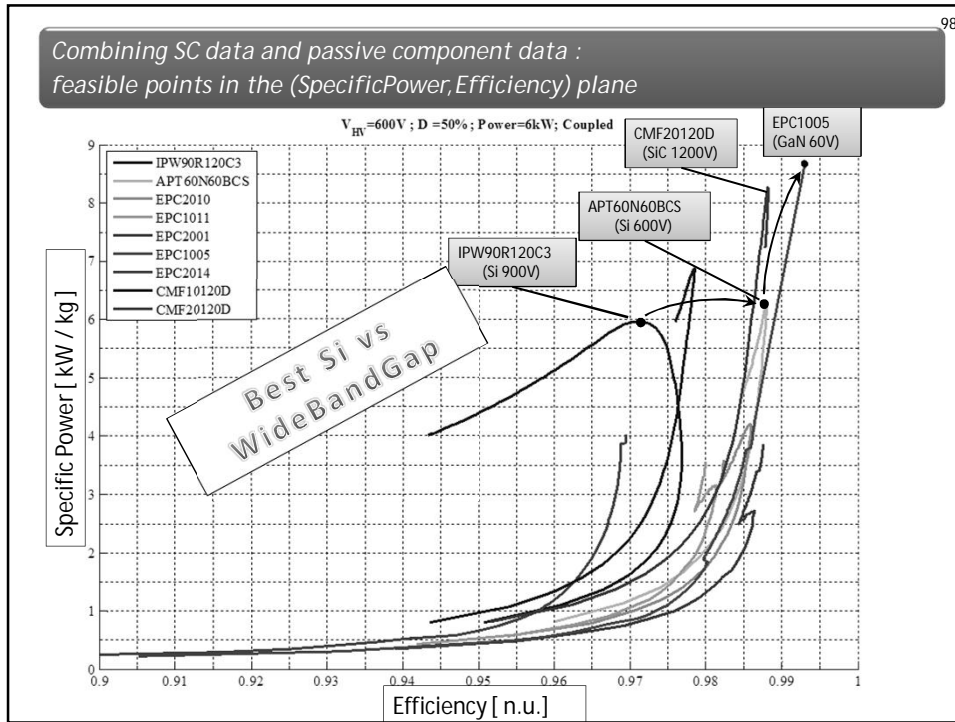


Graphic Vectorization in PLECS

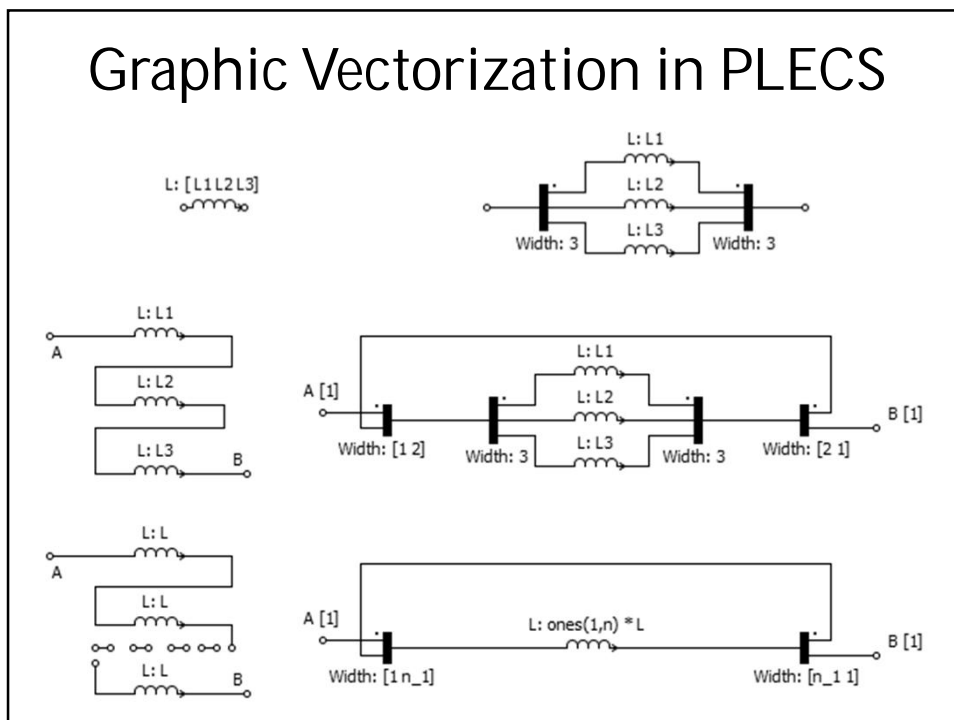

Dedicated blocks to help vectorization

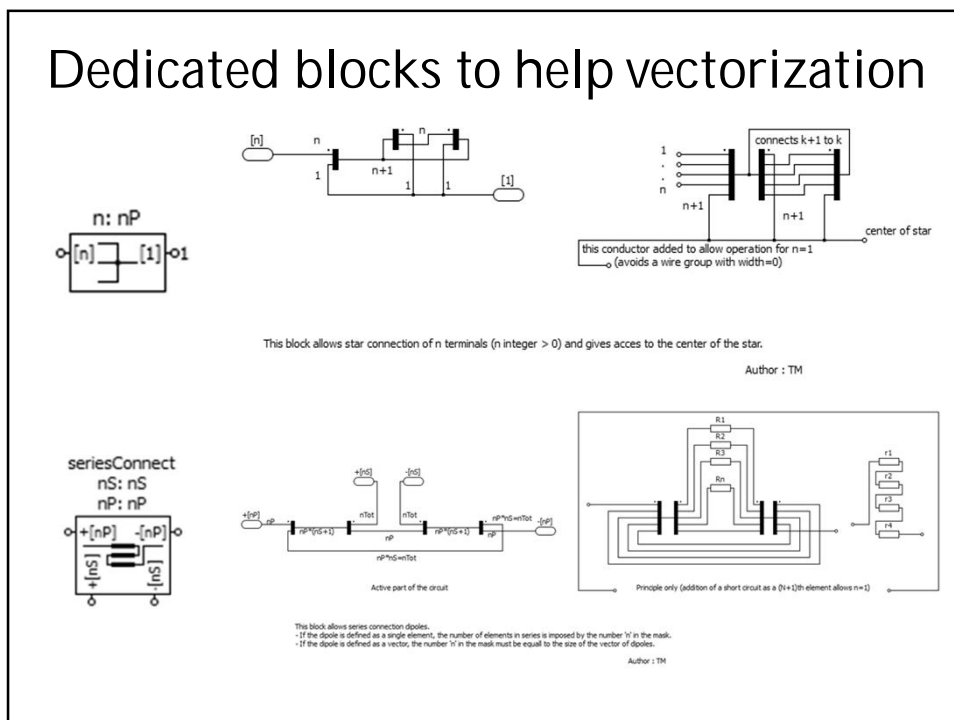

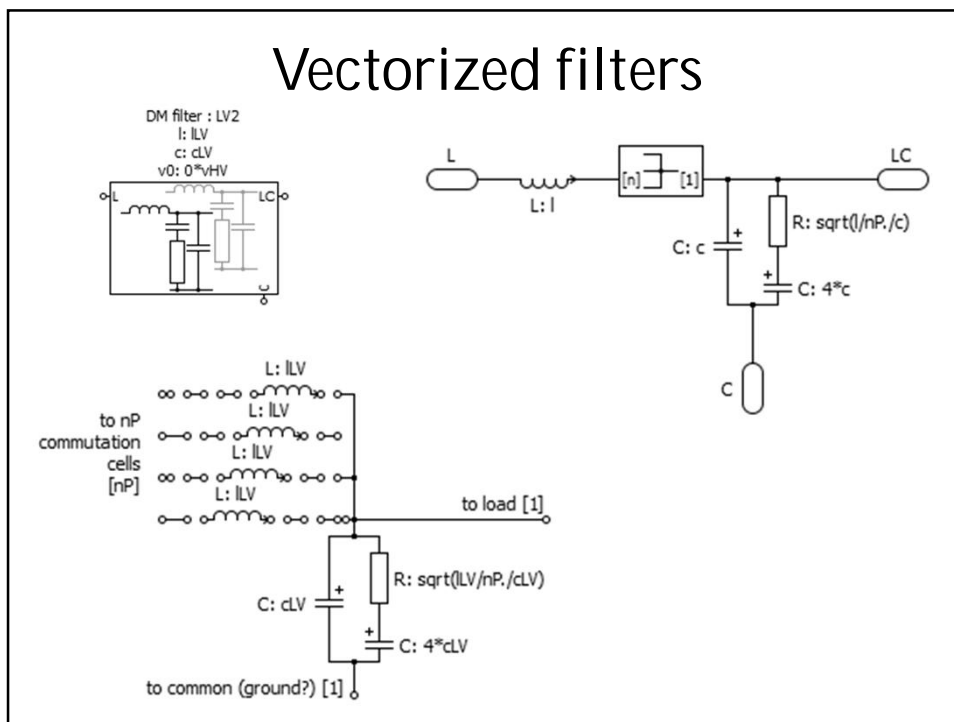


Vectorized filters with pre-design

Standard implantation is:

Parameters

Voltage on HV side:	Normalized current ripple on LV side:
vA	2.00
Initial voltage on filter capacitors:	Normalized voltage ripple on LV side:
D*vA	0.05
Max Current on LV side:	Standard:
vA/rLoad	EN55022A
Switching frequency:	Normalized voltage dip (LV side):
fSw	0.05
Number of cells in series:	Minimize Inductance Value:
nS	True
Number of cells in parallel:	Display calculation details in Octave Console:
nP	on




Vectorized commutation cell

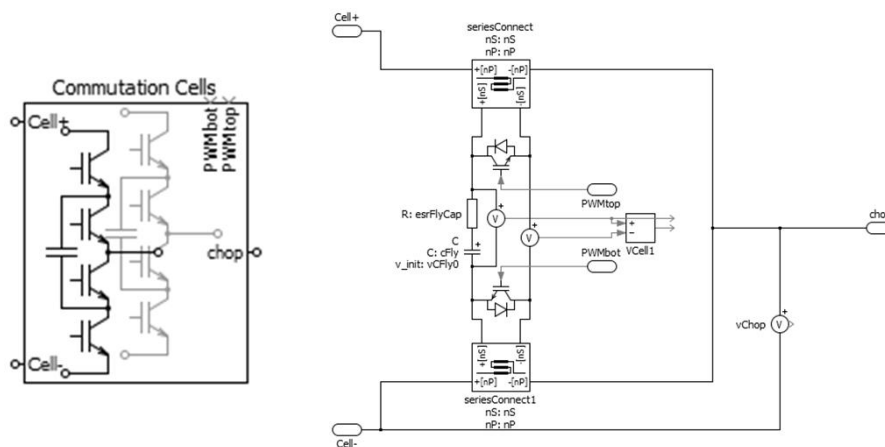





MacroCell is composed of Flying Cap Legs (nS commutation cells in series) that can typically be used in parallel connection (nP legs in parallel). Ideally, all commutation cells should all be controlled with the same duty cycle, but those in series with a phase-shift of $2\pi/nS$, and those in parallel with a phase-shift of $2\pi/nP$. When nP and nS are coprime, the input and output ripples are periodic at $nP.nS.fsw$.

Author : TM

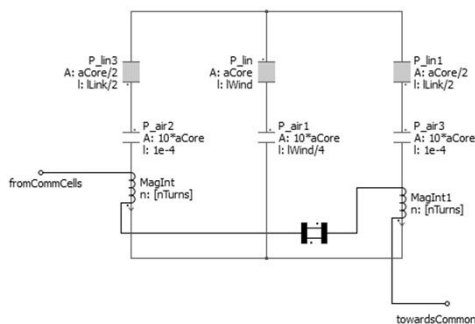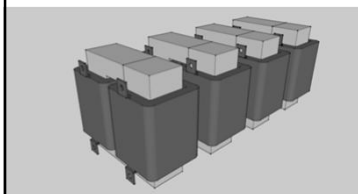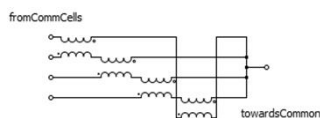
Vectorized Cyclic Cascade InterCell Transformer



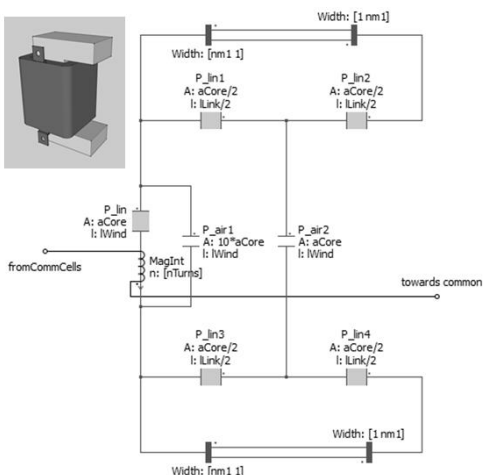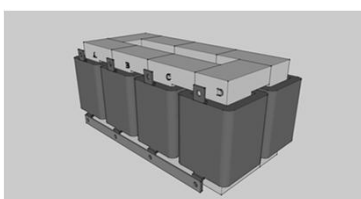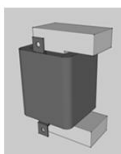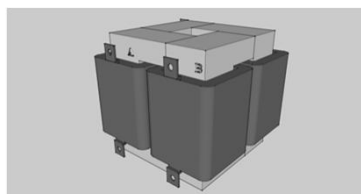
Vectorized Monolithic InterCell Transformer



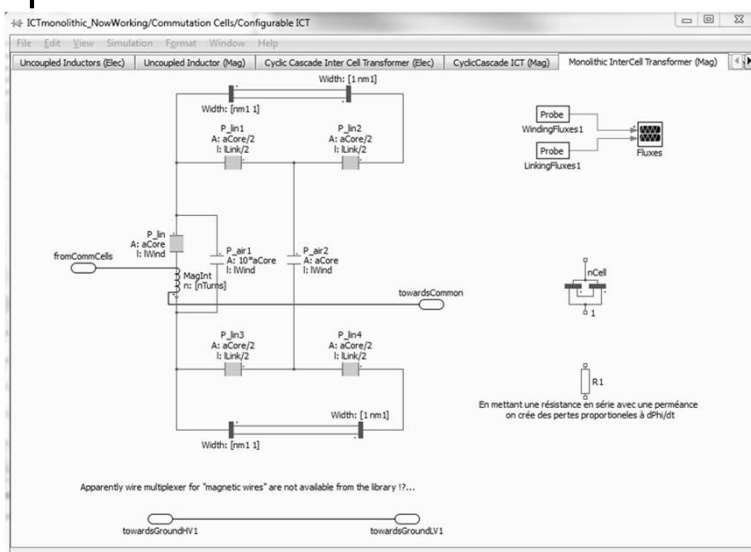
Vectorized and configurable magnetic components for interleaved converters



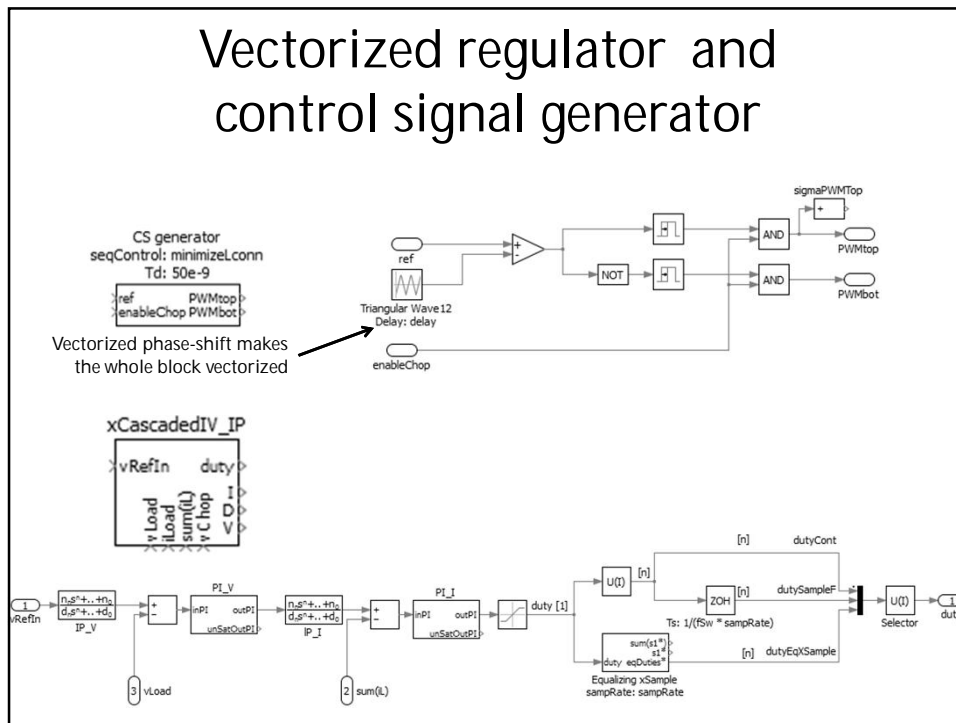Vectorized regulator and control signal generator



Vectorized equalizing sampler

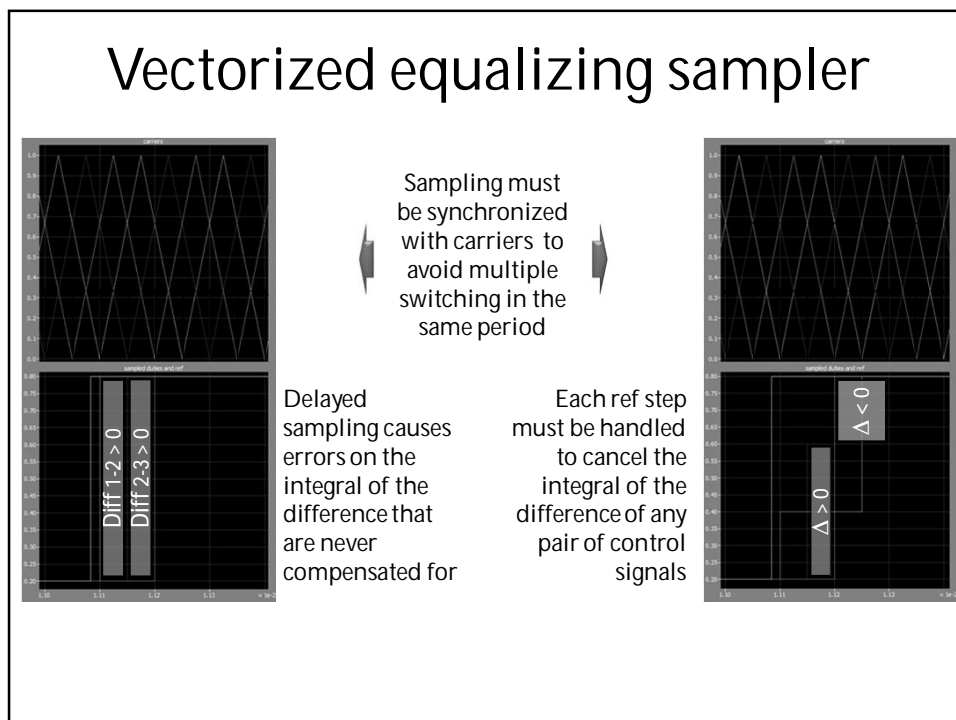

Vectorized equalizing sampler

The slide illustrates a vectorized equalizing sampler circuit. It includes two plots showing the 'integral of the differences' (scaled by $\times 10^{-5}$) and 'sampled duties and ref'. A central block diagram shows the circuit with components like ZOH, gain blocks (K), and delay blocks (phaseDelay). A code snippet for 'Equalizing xSampler' is provided:

```

Equalizing xSampler
sampRate: sampRate
> duty eqDuties*
  s1*
  sum(s1*)
    
```

Text on the slide states: "A simple circuit allows open-loop compensation of these unbalances without increasing the number of switchings".

Design check


The screenshot shows the 'MacroCellRegulatedVFilter' software interface. It displays several plots for 'Duty Cycles (continuous, sampled)', 'Voltage (Ref, AvgChopped, Load)', and 'Currents (Ref, Inductor, Load)'. A table of parameters is visible:

Name	Value
Time	0.0217017
Gain	40
Gain	55
Gain	45.3132
Constant1	0.00891251
Constant2	0.00892251
Constant3	0.00209675
Constant4	2
Constant5	-2
Constant6	0.0275926
Constant7	10
Constant8	20
Constant9	20
Constant10	0.20594
Constant11	0.242098
Constant12	-0.42091
Constant13	0.32087


A 'Link to MacroCellRegulatedVFilter' is also present in the bottom right corner.

DESIGNING WITH OBJECTS AND OPTIMIZATION

A real-world object

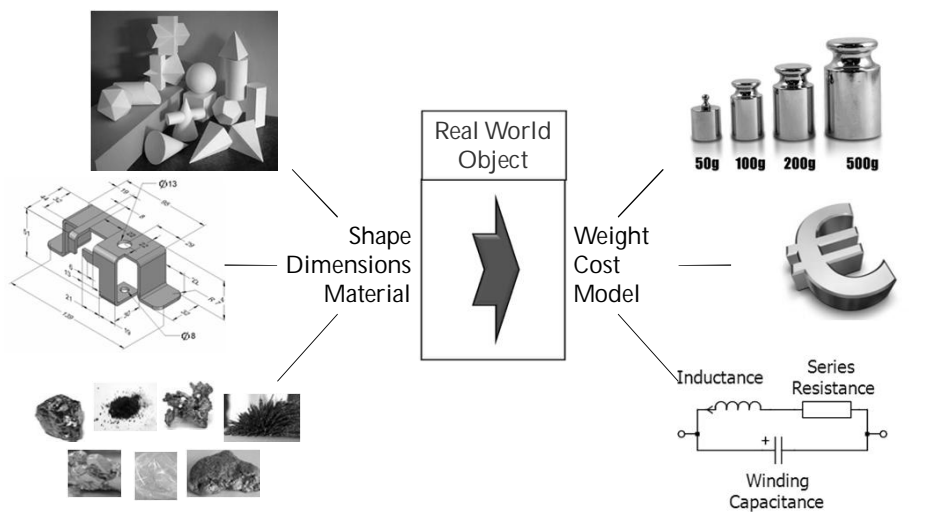



A real-world object

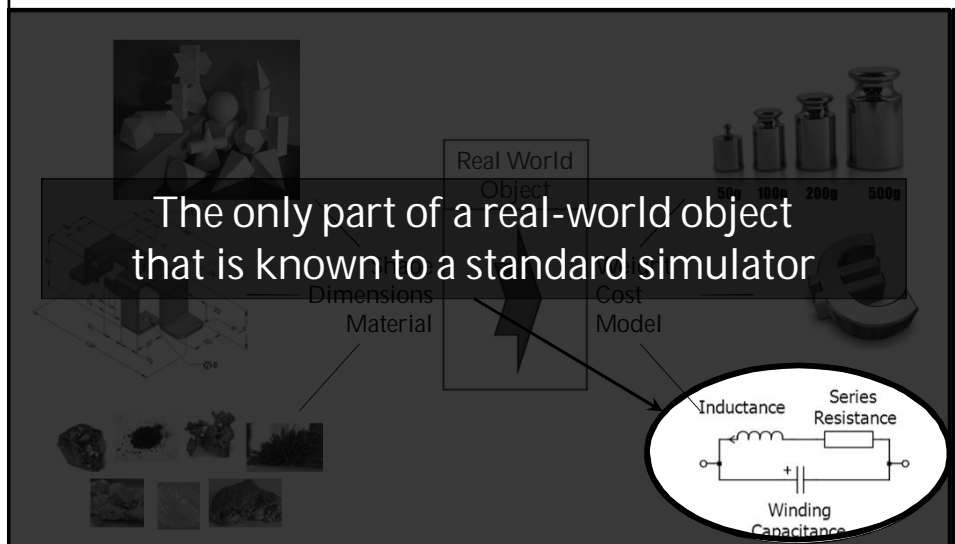

Designing a real-world object


Apply stimuli according to specifications:

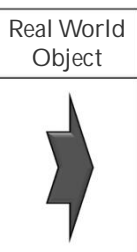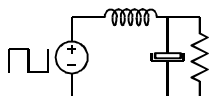- Voltage,
- Current,
- Switching Pattern,
- Ambient temperature
- ...



Check compatibility with maximum ratings:

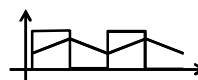- Peak voltage
- Peak & RMS current
- Peak induction
- Losses => Temperature
- ...



Example : InterCell Transformer

The screenshot displays the 'Figures - GUI ICT_Ncells' software interface. The left panel contains input and constraint values. The top center shows project settings. The middle section features a 3D model of the transformer core with various annotations. The right panel displays optimized values and main characteristics.

Category	Parameter	Value	
Initial Values	Conductor Width (ic)	0.361153 mm	
	Conductor Height (hc)	69.0241 mm	
	InterWinding Distance (dew)	1 mm	
	Vertical Core Leg Width (vl)	30 mm	
	Horizontal Core Leg Height (alh)	10.6733 mm	
	Core Depth (d)	29 mm	
	Number of Turns (N)	15	
	Switching Frequency (f)	20 kHz	
	Constant Values	Core Width (bmax)	300 mm
		Core Height (hmax)	300 mm
Max Output Current Ripple (b0tmax)		150 App	
Saturation Rate (k0atmax)		0.9	
Maximum Losses (l0max)		500 W	
Maximum Volume (v0max)		10000 cm3	
Maximum Mass (m0max)		25 kg	
Maximum Price (p0max)		0 Euros	
Maximum Current Density (d0max)		0 A/mm²	
Maximum Temperature Rise (t0max)		45 °C	

Category	Parameter	Value	
Optimized Values	Conductor Width (ic)	0.361153 mm	
	Conductor Height (hc)	69.0241 mm	
	InterWinding Distance (dew)	1 mm	
	Vertical Core Leg Width (vl)	30 mm	
	Horizontal Core Leg Height (alh)	10.6733 mm	
	Core Depth (d)	29 mm	
	Number of Turns (N)	15	
	Switching Frequency (f)	20 kHz	
	Main Characteristics	Core Width (b)	99.5346 mm
		Core Height (h)	91.3077 mm
Max Output Current Ripple (b0tapp)		6.20073 App	
Saturation Rate (k0at)		0.92056	
Total Losses (l0total)		30.899 W	
Total Volume (v0total)		1433.39 cm3	
Total Mass (m0total)		5.62556 kg	
Total Price (p0total)		0 Euros	
Total Current Density (d0ttotal)		3.62837 A/mm²	
Temperature Rise (t0at)		46 °C	


Example : InterCell Transformer

The screenshot displays the 'Figures - GUI ICT_Ncells' software interface after the first optimization step. The layout is similar to the first image, but with annotations indicating the optimization process and results.


Category	Parameter	Value	
Initial Values	Conductor Width (ic)	0.361153 mm	
	Conductor Height (hc)	69.0241 mm	
	InterWinding Distance (dew)	1 mm	
	Vertical Core Leg Width (vl)	30 mm	
	Horizontal Core Leg Height (alh)	10.6733 mm	
	Core Depth (d)	29 mm	
	Number of Turns (N)	15	
	Switching Frequency (f)	20 kHz	
	Constant Values	Core Width (bmax)	300 mm
		Core Height (hmax)	300 mm
Max Output Current Ripple (b0tmax)		150 App	
Saturation Rate (k0atmax)		0.9	
Maximum Losses (l0max)		500 W	
Maximum Volume (v0max)		10000 cm3	
Maximum Mass (m0max)		25 kg	
Maximum Price (p0max)		0 Euros	
Maximum Current Density (d0max)		0 A/mm²	
Maximum Temperature Rise (t0max)		45 °C	

Category	Parameter	Value	
Optimized Values	Conductor Width (ic)	0.361153 mm	
	Conductor Height (hc)	69.0241 mm	
	InterWinding Distance (dew)	1 mm	
	Vertical Core Leg Width (vl)	30 mm	
	Horizontal Core Leg Height (alh)	10.6733 mm	
	Core Depth (d)	29 mm	
	Number of Turns (N)	15	
	Switching Frequency (f)	20 kHz	
	Main Characteristics	Core Width (b)	99.5346 mm
		Core Height (h)	91.3077 mm
Max Output Current Ripple (b0tapp)		6.20073 App	
Saturation Rate (k0at)		0.92056	
Total Losses (l0total)		30.899 W	
Total Volume (v0total)		1433.39 cm3	
Total Mass (m0total)		5.62556 kg	
Total Price (p0total)		0 Euros	
Total Current Density (d0ttotal)		3.62837 A/mm²	
Temperature Rise (t0at)		46 °C	


Designing a full system

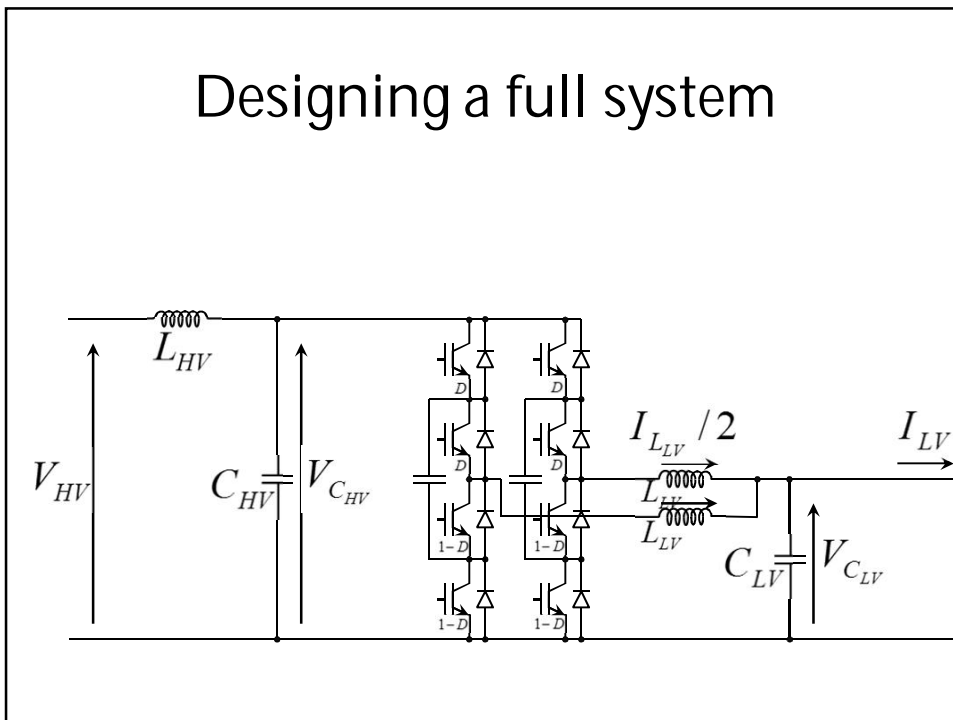


Collect objects

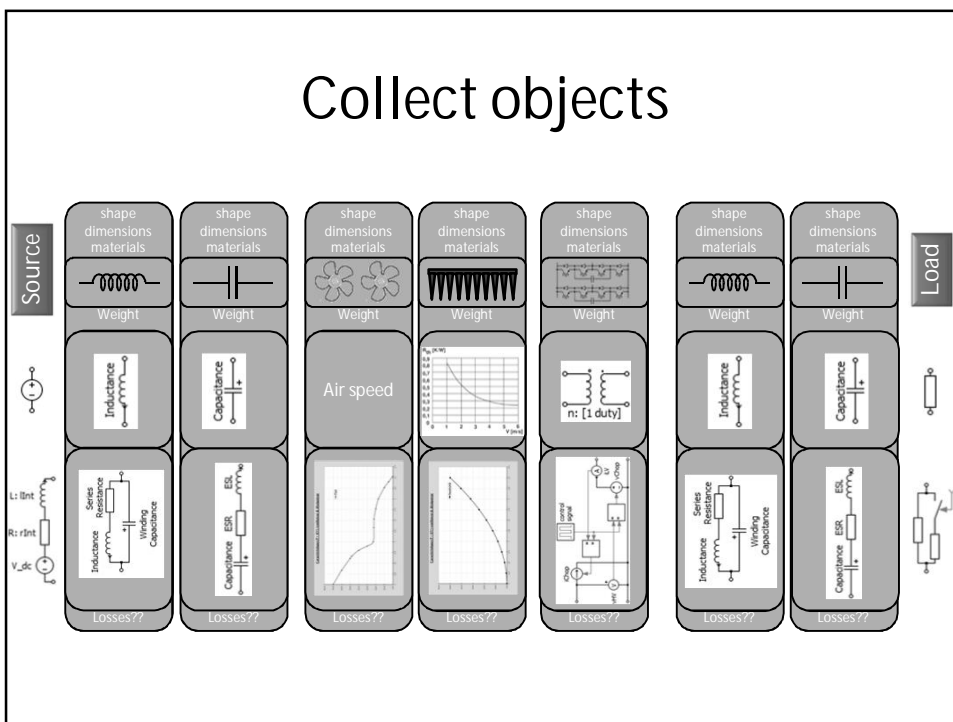

Compose objects

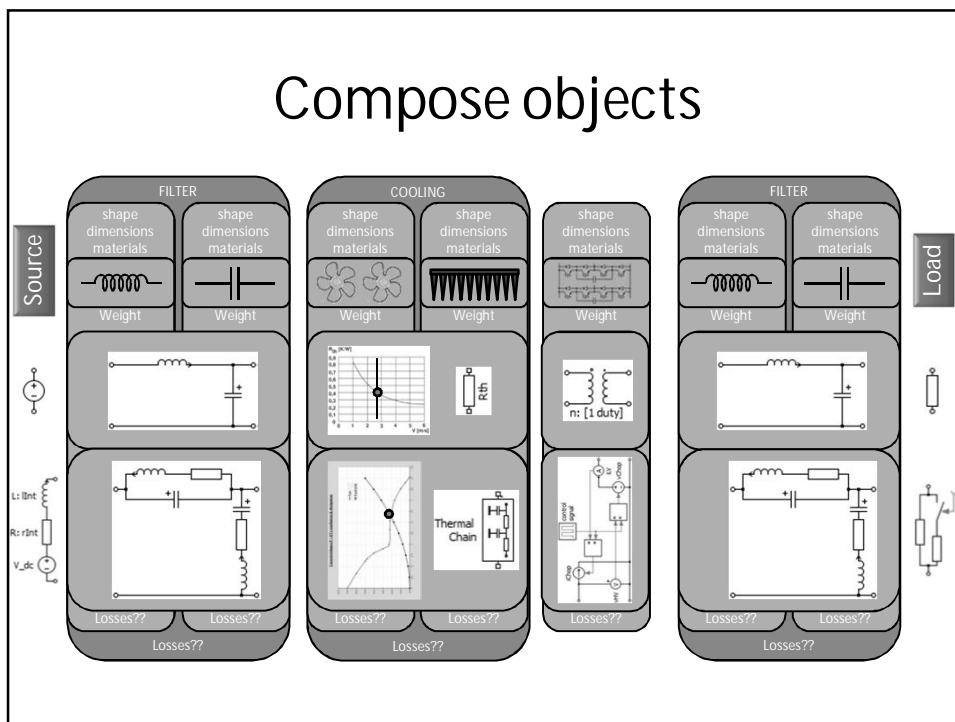

Build full system model and solve

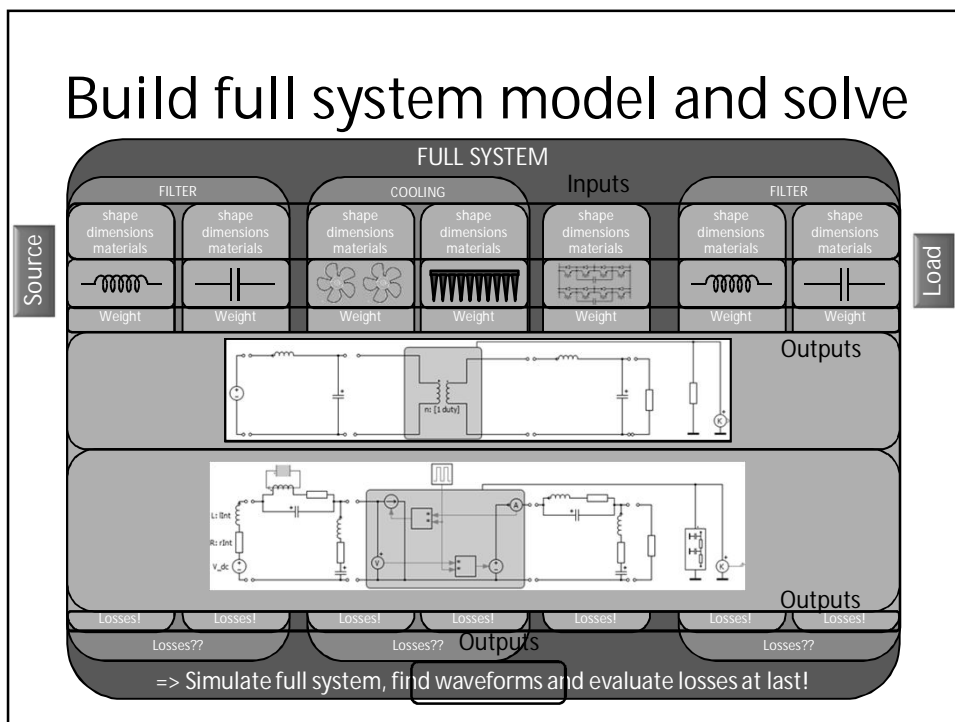

Need for a fast solver


Steady-state waveforms are needed

- Accelerated determination of steady-state waveforms with a standard (time-domain) simulator is not the best choice.
- In most cases simplifications can be made to allow frequency domain analysis which inherently is a direct determination of steady state waveforms.

Main assumptions to allow standard frequency analysis (linear system) :

- Intrinsic non-linearities of components (saturation of permeability of magnetic materials, exponential $V(I)$ characteristics of diodes, etc) can be neglected :
- Voltage/current ripple applied to commutation cells can be neglected to decouple the HV and LV sides,
- Influence of spontaneous commutations can be neglected,

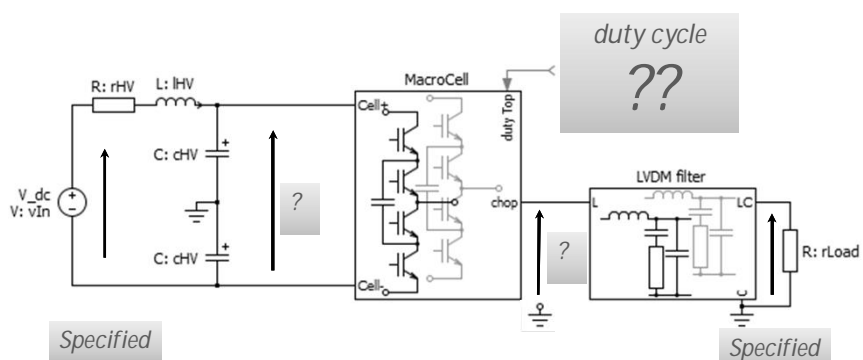Direct determination of the operating point




Principle used for approximate determination of the operating point

Assumptions:
=> linear systems, lossless commutation cell, v_{HV} is constant

Apply 1V@fRef to the LV side and solve LV circuit
Find amplitude v_{load} per Volt and delay
Scale v_{AC} and select phase to match v_{load} specifications
Find power delivered by v_{AC} and scale for specs ($P_{LV} \neq v_{AC}^2$)

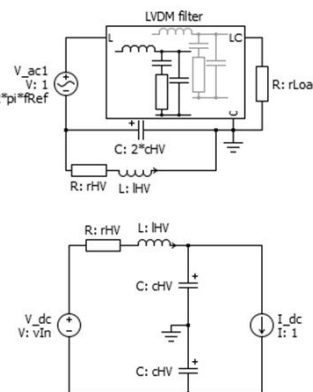Lossless commutation cell => $P_{HV} = P_{LV}$
Constant v_{HV} => only i_{HV}^{DC} gives P_{HV}
Solve HV circuit with $I_{dc} = 1A$ and find internal resistance
Find i_{HV}^{DC} and v_{HV} such that $P_{HV} = P_{LV}$
Find duty cycle so that $v_{AC} = D(t) \cdot v_{HV}$



Equations used for approximate determination of the operating point

Assumptions:
=> linear systems, lossless commutation cell, v_{HV} is constant


$$v_{AC}^{opPoint} = \frac{|v_{load}^{opPoint}|}{|v_{load}^N|} \angle(\varphi_{ref}^{opPoint} - \varphi_{load}^N)$$

$$P_{AC}^{opPoint} = P_{AC}^N \left(\frac{|v_{load}^{opPoint}|}{|v_{load}^N|} \right)^2$$


$$r_{int} = v_{in} - v_{HV}^N$$

$$v_{HV}^{opPoint} = \frac{v_{in}}{2} + \frac{\sqrt{v_{in}^2 - 4 \cdot r_{int} \cdot P_{AC}^{opPoint}}}{2}$$

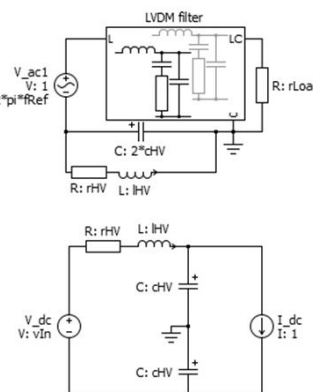
$$\Rightarrow duty(t) = \frac{v_{AC}^{opPoint}}{v_{HV}^{opPoint}}$$



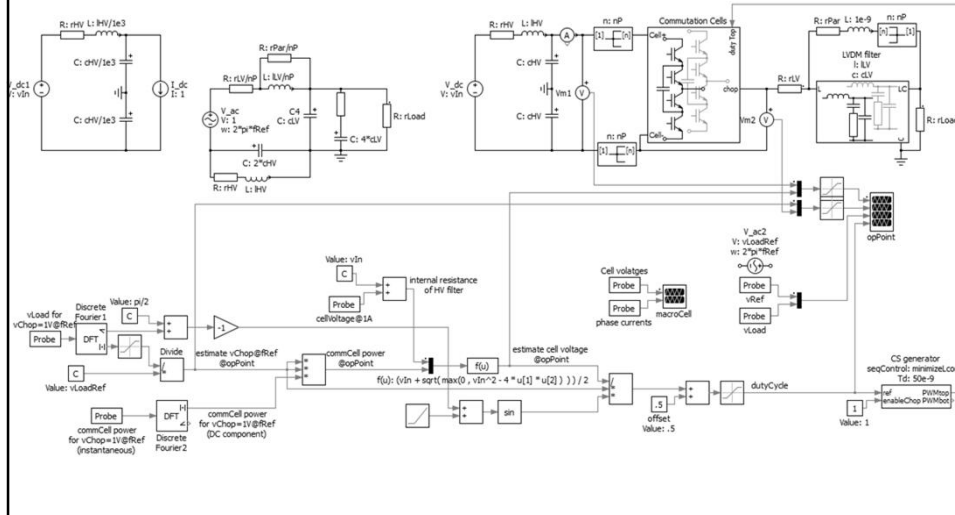
Approximate time domain determination of the operating point



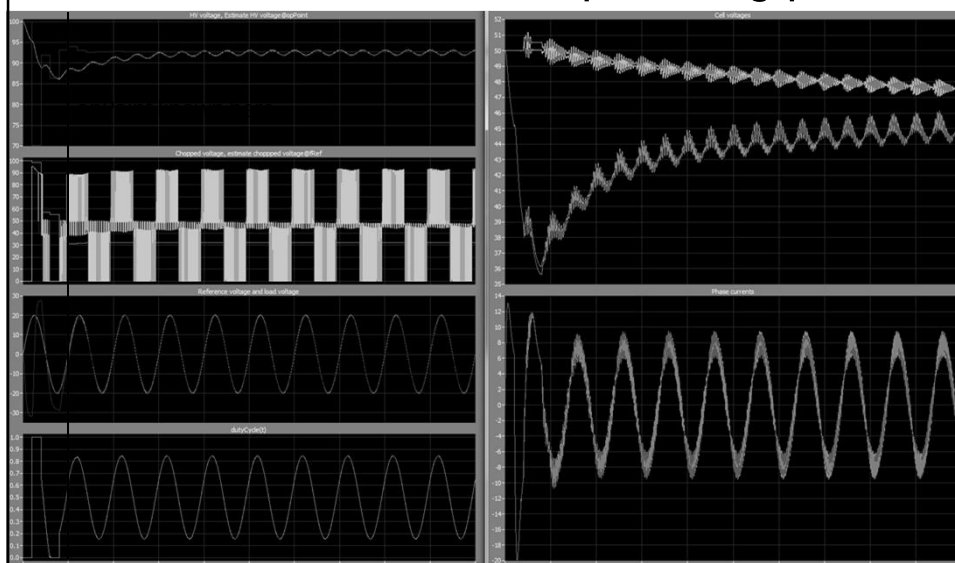Approximate time domain determination of the operating point





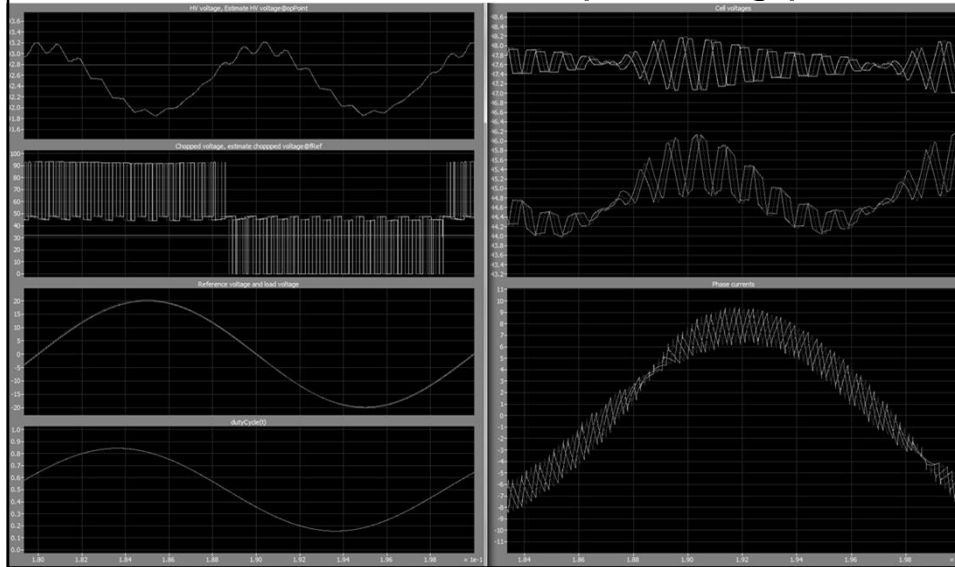Approximate time domain determination of the operating point



Approximate frequency domain determination of the operating point

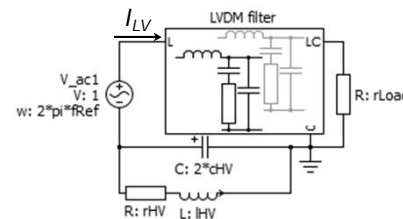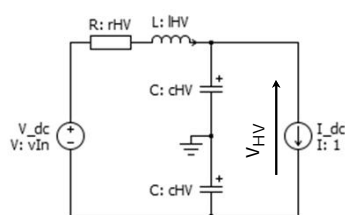Solve separate 'normalized' circuit ($I_{DC}=1A$; $V_{AC}=1V \angle 0^\circ$) using a single frequency! (DC and



$$\begin{cases} r_{int} = v_{in} - v_{HV}^N \\ v_{HV}^{opPoint} = \frac{v_{in}}{2} + \frac{\sqrt{v_{in}^2 - 4 \cdot r_{int} \cdot P_{AC}^{opPoint}}}{2} \end{cases}$$


$$\begin{cases} v_{AC}^{opPoint} = \frac{|v_{load}^{opPoint}|}{|v_{load}^N|} \angle (\varphi_{ref}^{opPoint} - \varphi_{load}^N) \\ P_{AC}^{opPoint} = P_{AC}^N \left(\frac{|v_{load}^{opPoint}|}{|v_{load}^N|} \right)^2 \end{cases}$$

$$\Rightarrow duty(t) = \frac{v_{AC}^{opPoint}}{v_{HV}^{opPoint}}$$

Full frequency domain analysis using the operating point

The control pattern $duty(t)$ determined previously allows direct calculation of the steady state waveforms at a point that is very close to the specified point:

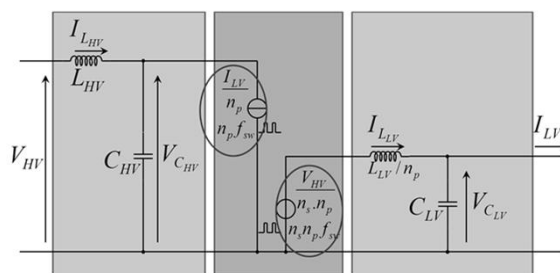- The circuit is split in independent linear subcircuits
- The spectra of the sources are derived from $duty(t)$, $v_{HVDC}^{opPoint}$ and $i_{LVf_{Mod}}^{opPoint}$ (time domain multiplication by $duty(t)$ followed by FFT, or direct convolution of spectra)



- The circuit is solved in the frequency domain
- If necessary time waveforms regenerated using iFFT.

139

Optimize at last...

