

Wir schaffen Wissen – heute für morgen

Paul Scherrer Institut





René Künzi

Filter Design - Passive Power Filters





CERN Accelerator School 2014, Baden, Switzerland

10.05.2014

Suitable Filter Structures

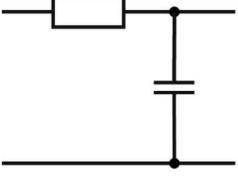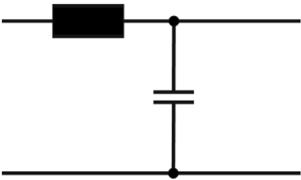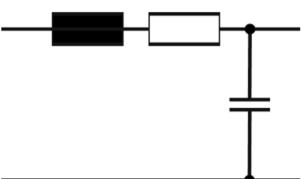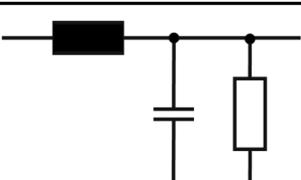		<p>For signal filters simple RC are commonly used</p> <p>Attenuation only 20dB/decade</p> <p>Full current through R → Losses !</p>
		<p>With a LC structure we get 40dB/decade</p> <p>There is a high resonance</p>
		<p>Series damping in order to overcome the resonance problem</p> <p>Full current through R → Losses!</p>
		<p>Parallel damping in order to overcome the resonance problem</p> <p>Full voltage across R → Losses!</p>


Suitable Filter Structures

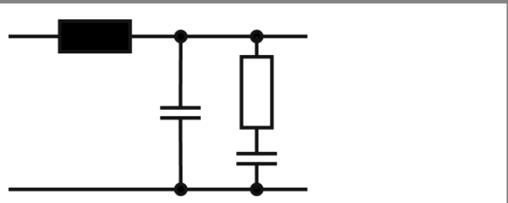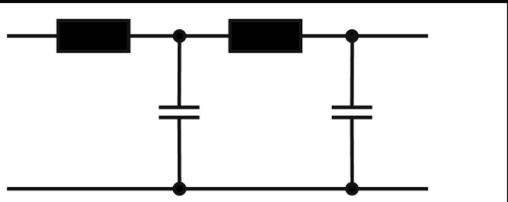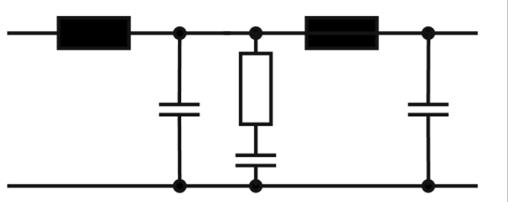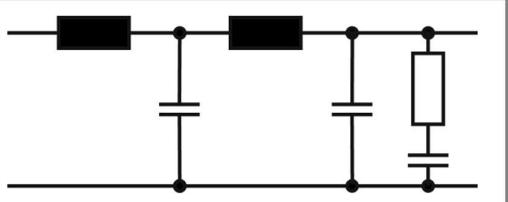		<p>2nd order <u>lowpass</u> filter with parallel RC-damping</p> <p>Resonance can be damped Reasonable losses</p>
		<p>For better attenuation 2 LC stages are necessary</p> <p>Again high resonance</p>
		<p>RC damping after first stage</p> <p>Resonance ok High losses in RC damping due to high ripple currents</p>
		<p>4th order <u>lowpass</u> filter with parallel RC-damping after second stage</p> <p>Resonance can be damped Reasonable losses</p>


R. Künzi Power Filter Design CAS 2014 10.05.2014

3

H-Bridge

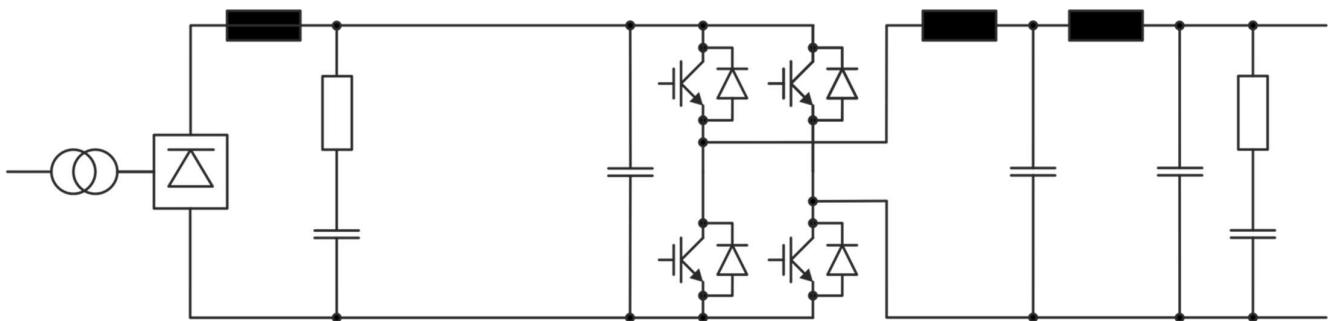


H-Bridge with CM filter

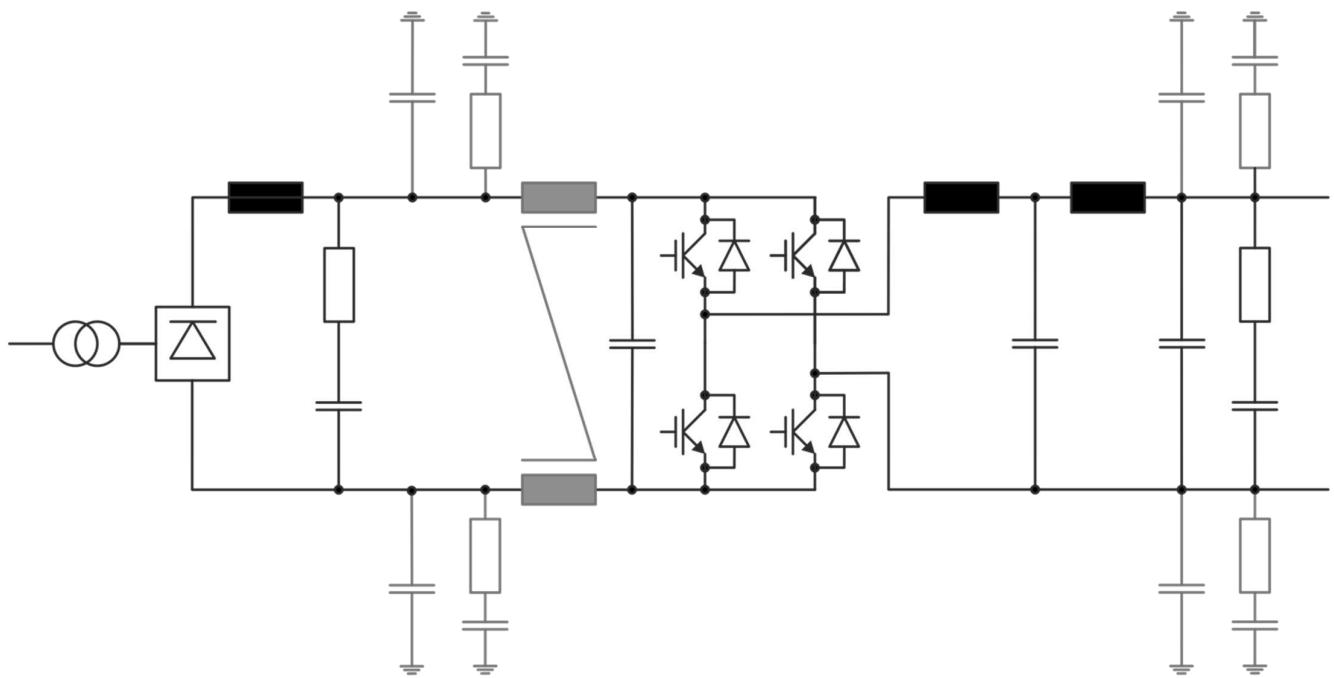

R. Künzi Power Filter Design CAS 2014 10.05.2014

5

2nd order filter - Transferfunction

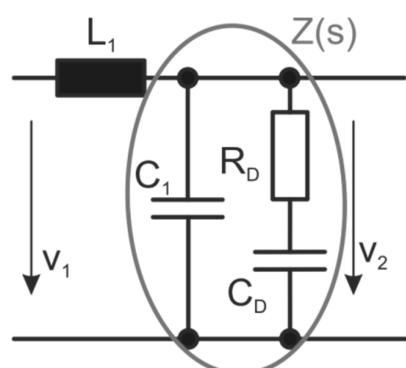

$$Z(s) = \frac{1}{C_1 s + \frac{1}{R_D + \frac{1}{C_D s}}} = \frac{R_D C_D s + 1}{C_1 R_D C_D s^2 + (C_1 + C_D)s}$$

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{Z(s)}{L_1 s + Z(s)} = \frac{R_D C_D s + 1}{L_1 C_1 R_D C_D s^3 + L_1(C_1 + C_D)s^2 + R_D C_D s + 1} \quad (1)$$

$$G(s) = \frac{k_1 s + 1}{k_3 s^3 + k_2 s^2 + k_1 s + 1}$$

1st order PD 3rd order PT

with $k_1 = R_D C_D$
 $k_2 = L_1(C_1 + C_D)$
 $k_3 = L_1 C_1 R_D C_D$

3rd order PT in its normalized form:

$$G_{PT}(s) = \frac{1}{(1 + a_1 \frac{s}{\omega_0}) \cdot (1 + a_2 \frac{s}{\omega_0} + b_2 \frac{s^2}{\omega_0^2})} \quad (2)$$

Method	a_1	a_2	b_2
Butterworth	1.0000	1.0000	1.0000
Bessel	0.7560	0.9996	0.4772
Critical damping	0.5098	1.0197	0.2599

By expanding (2) and comparing the coefficients with (1) we get:

$$G_{PT}(s) = \frac{1}{\frac{a_1 b_2}{\omega_0^3} s^3 + \frac{(a_1 a_2 + b_2)}{\omega_0^2} s^2 + \frac{(a_1 + a_2)}{\omega_0} s + 1}$$

$$k_1 = R_D C_D = \frac{a_1 + a_2}{\omega_0} \quad (3a)$$

$$k_2 = L_1 (C_1 + C_D) = \frac{a_1 a_2 + b_2}{\omega_0^2} \quad (3b)$$

$$k_3 = L_1 C_1 R_D C_D = \frac{a_1 b_2}{\omega_0^3} \quad (3c)$$

The 3 independent equations (3a....3c) contain 5 unknowns (L_1 , C_1 , R_D , C_D and ω_0). Therefore we have the choice to select 2 of them and the remaining 3 depend on that selection.

2nd order filter - Selection of ω_0

For a given frequency ω_B well in the blocking area ($\omega_B \gg \omega_0$) we can define the desired attenuation G_B . In the blocking area the highest order terms of both the numerator and denominator in equation (1) dominate, therefore (1) can be simplified to:


$$G_B = \frac{R_D C_D s}{L_1 C_1 R_D C_D s^3} = \frac{\frac{a_1 + a_2}{\omega_0} s}{\frac{a_1 b_2}{\omega_0^3} s^3} = \frac{a_1 + a_2}{a_1 b_2} \cdot \frac{\omega_0^2}{s^2} = -\frac{a_1 + a_2}{a_1 b_2} \cdot \frac{\omega_0^2}{\omega_B^2}$$

$$(j)^2 = -1$$

$$\omega_0 = \omega_B \cdot \sqrt{\frac{|G_B| \cdot a_1 b_2}{a_1 + a_2}} \quad (4)$$

2nd order filter - Definition of L_1

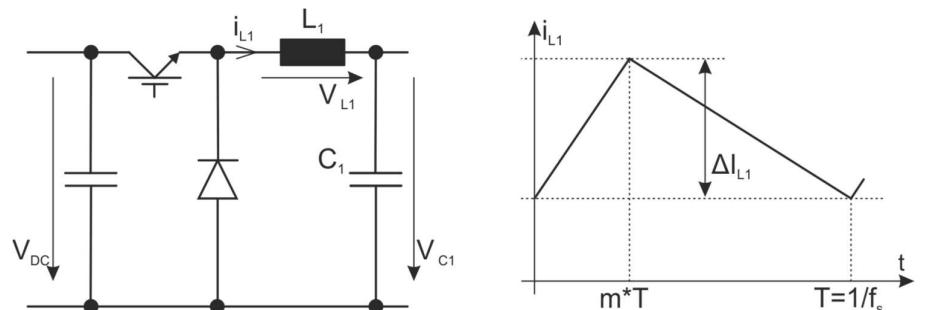For cost reasons L_1 should be as small as possible, but a too small inductance will result in an excessive ripple current!



The DC-voltage across C_1 is $m \cdot V_{DC}$. When the IGBT is on, the current in L_1 increases and the peak-peak ripple current ΔI_{L1} can be calculated:

$$V_{L1} = L_1 \cdot \frac{di_{L1}}{dt} = V_{DC} - V_{C1} = V_{DC} \cdot (1 - m)$$

$$\Delta I_{L1} = m \cdot T \cdot \frac{di_{L1}}{dt} = m \cdot \frac{1}{f_s} \cdot \frac{V_{DC} \cdot (1 - m)}{L_1} = \frac{V_{DC} \cdot (1 - m) \cdot m}{f_s \cdot L_1}$$

Maximum 0.25
for $m = 0.5$


$$L_1 = \frac{V_{DC} \cdot 0.25}{f_s \cdot \Delta I_{L1}} \quad (5)$$

2nd order filter - Definition of L₁

Alternative approach to determine L₁:

$$I_{L1_ripple_pp} = \frac{v_{1_ripple_pp}}{2 \cdot \pi \cdot f_{ripple} \cdot L_1}$$
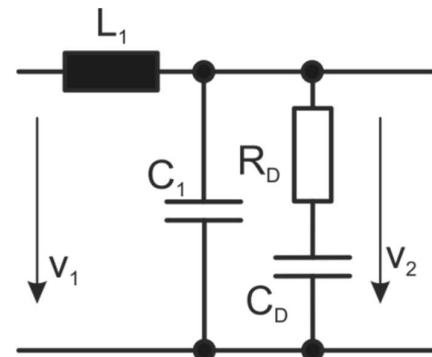
$$L_1 = \frac{v_{1_ripple_pp}}{2 \cdot \pi \cdot f_{ripple} \cdot I_{L1_ripple_pp}} \quad (6)$$



2nd order filter – Calculating filter elements

Substitute (3a) in (3c) and we receive:

Selection: L₁ and ω₀

Selection: C₁ and ω₀

Selection: L₁ and C₁

$$C_1 = \frac{a_1 b_2}{L_1 \omega_0^2 (a_1 + a_2)} \quad (7a)$$

$$L_1 = \frac{a_1 b_2}{C_1 \omega_0^2 (a_1 + a_2)} \quad (7b)$$


$$\omega_0 = \sqrt{\frac{a_1 b_2}{L_1 C_1 (a_1 + a_2)}} \quad (7c)$$

Solve (3b) for C_D:

$$C_D = \frac{a_1 a_2 + b_2}{L_1 \omega_0^2} - C_1 \quad (8)$$

Solve (3a) for R_D:

$$R_D = \frac{a_1 + a_2}{C_D \omega_0} \quad (9)$$

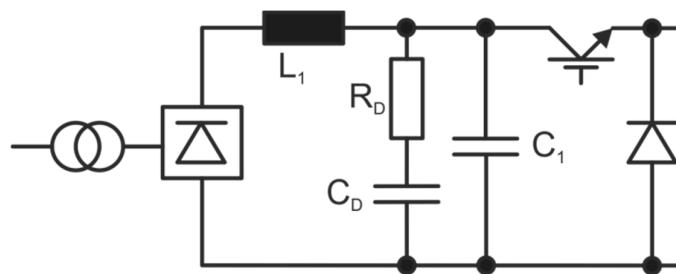2nd order filter – Example 1

- DC-link voltage: 200V
- DC-link current: 500A
- $\Delta I_{L1} \leq 50App$.
- C_1 must be $\geq 22mF$ (because of high ripple current)

Design a 2nd order filter for all three given optimization methods and compare the results.

2nd order filter – Example 1

Select L_1 to meet the ripple current requirement:

$$L_1 = \frac{v_{1_ripple_pp}}{2 \cdot \pi \cdot f_{ripple} \cdot I_{L1_ripple_pp}} \quad (6)$$

$$L_1 = \frac{(200 \cdot 0.13)Vpp}{2 \cdot \pi \cdot 300s^{-1} \cdot 50App} = 300\mu H$$

Select C_1 :

$$C_1 = 22mF$$

Calculate the remaining filter elements

(7c, 8, 9)

2nd order filter – Example 1

Results:


	Butterworth	Bessel	Critical damping
	$a_1 = 1.0000$ $a_2 = 1.0000$ $b_2 = 1.0000$	$a_1 = 0.7560$ $a_2 = 0.9996$ $b_2 = 0.4772$	$a_1 = 0.5098$ $a_2 = 1.0197$ $b_2 = 0.2599$
ω_0 (f_0)	275 s^{-1} (44 Hz)	177 s^{-1} (28 Hz)	115 s^{-1} (18 Hz)
L_1	$300 \mu\text{H}$	$300 \mu\text{H}$	$300 \mu\text{H}$
C_1	22 mF	22 mF	22 mF
C_D	66 mF ↘ x3	110 mF ↘ x5	176 mF ↘ x8
R_D	0.11Ω	0.09Ω	0.08Ω

2nd order filter – Example 1


Maximum amplitude of resonance:
 Butterworth 4.5 dB
 Bessel 3.1 dB
 Critical damping 2.3 dB

Frequency, for -3 dB attenuation:
 Butterworth 74 Hz
 Bessel 67 Hz
 Critical damping 59 Hz

Attenuation: -28dB @ 300Hz

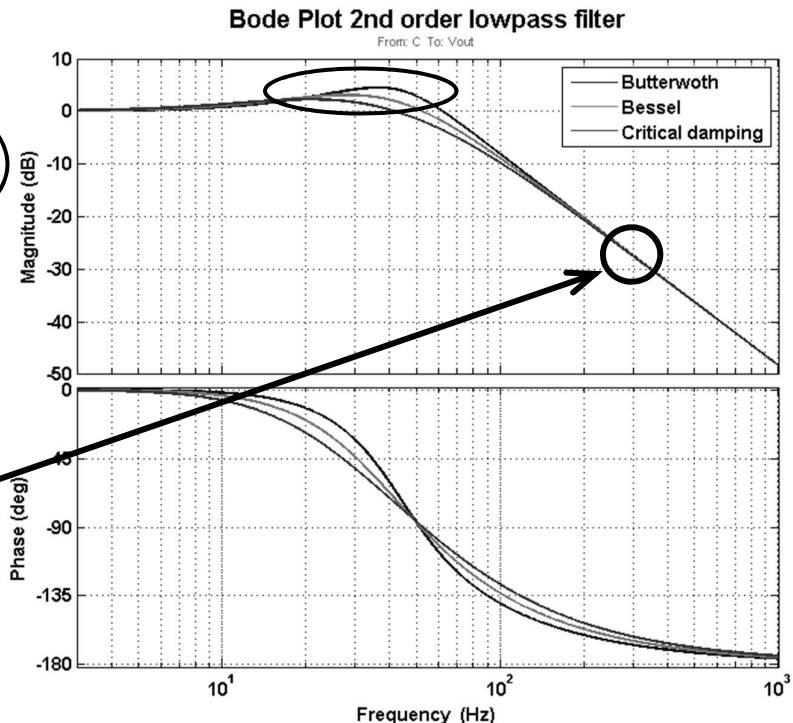

2nd order filter – Example 2

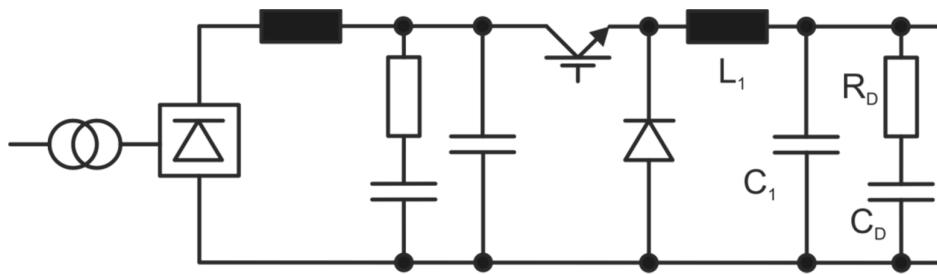

- DC-link voltage: 120V
- $f_s = 20\text{kHz}$
- $I_{\text{Out_max}} = 500\text{A}$
- $\Delta I_{L1} \leq 50\text{App.}$
- Attenuation: $G_B = 250$ @ $\omega_B = 2\pi \cdot 20\text{kHz}$

Same premises as
for example 3

Design a 2nd order filter for all three given optimization methods and compare the results.

2nd order filter – Example 2

Select L_1 to meet the ripple current requirement:

$$L_1 = \frac{V_{DC} \cdot 0.25}{f_s \cdot \Delta I_{L1}} = \frac{120V \cdot 0.25}{20\text{kHz} \cdot 50A} = 30\mu H \quad (5)$$

Select ω_0 to meet the attenuation requirement:

$$\omega_0 = \omega_B \cdot \sqrt{\frac{|G_B| \cdot a_1 b_2}{a_1 + a_2}} \quad (4)$$

Calculate the remaining filter elements

(7a, 8, 9)

2nd order filter – Example 2

Results:

	Butterworth	Bessel	Critical damping
	$a_1 = 1.0000$ $a_2 = 1.0000$ $b_2 = 1.0000$	$a_1 = 0.7560$ $a_2 = 0.9996$ $b_2 = 0.4772$	$a_1 = 0.5098$ $a_2 = 1.0197$ $b_2 = 0.2599$
ω_B	$1.26 \cdot 10^5 \text{ s}^{-1}$ (20kHz)		
G_B	0.004	(-48dB)	
ω_0	$5.62 \cdot 10^3 \text{ s}^{-1}$ (894 Hz)	$3.60 \cdot 10^3 \text{ s}^{-1}$ (573 Hz)	$2.34 \cdot 10^3 \text{ s}^{-1}$ (372 Hz)
L_1	30 μH	30 μH	30 μH
C_1	528 μF	528 μF	528 μF
C_D	1'580 μF	2'640 μF	4'220 μF
R_D	0.22 Ω	0.18 Ω	0.15 Ω

R. Künzi Power Filter Design CAS 2014 10.05.2014

19

2nd order filter – Example 2


Maximum amplitude of resonance:

- Butterworth 4.5 dB
- Bessel 3.1 dB
- Critical damping 2.3 dB


Frequency, for -3 dB attenuation:

- Butterworth 1.5 kHz
- Bessel 1.4 kHz
- Critical damping 1.2 kHz

Attenuation: -48dB @ 20kHz

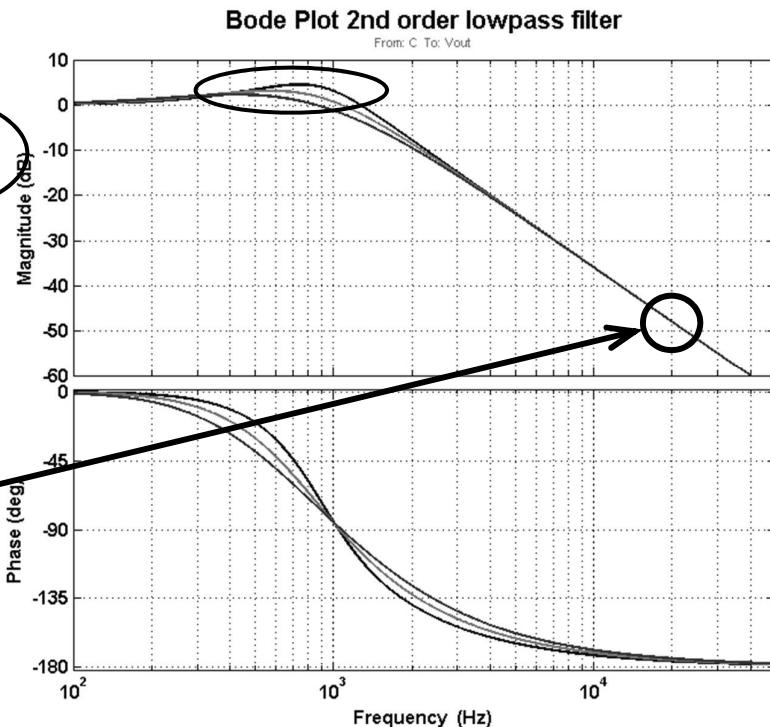

4th order filter - Transferfunction

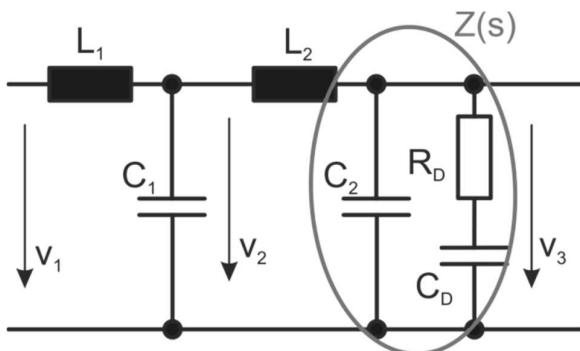

$$Z(s) = \frac{1}{C_2 s + \frac{1}{R_D + \frac{1}{C_D s}}} = \frac{R_D C_D s + 1}{C_2 R_D C_D s^2 + (C_2 + C_D)s}$$

$$G(s) = \frac{v_3(s)}{v_1(s)} = \frac{\frac{1}{C_1 s + \frac{1}{L_2 s + Z(s)}}}{\frac{1}{L_1 s + \frac{1}{C_1 s + \frac{1}{L_2 s + Z(s)}}}}.$$

$\frac{1}{C_1 s + \frac{1}{L_2 s + Z(s)}}$

$\frac{Z(s)}{L_2 s + Z(s)}$

$\rightarrow G_1(s) = \frac{v_2(s)}{v_1(s)}$

$\rightarrow G_2(s) = \frac{v_3(s)}{v_2(s)}$

4th order filter - Transferfunction

$$G(s) = \frac{R_D C_D s + 1}{L_1 L_2 C_1 C_2 R_D C_D s^5 + (C_2 + C_D)L_1 L_2 C_1 s^4 + [L_1 C_1 R_D C_D + (L_1 + L_2)C_2 R_D C_D]s^3 + \dots} \\ \dots + \frac{[L_1 C_1 + (L_1 + L_2)(C_2 + C_D)]s^2 + R_D C_D s + 1}{R_D C_D s + 1} \quad (10)$$

$$G(s) = \frac{k_1 s + 1}{k_5 s^5 + k_4 s^4 + k_3 s^3 + k_2 s^2 + k_1 s + 1} \quad \text{with} \quad k_1 = R_D C_D$$

1^{st} order PD

$k_1 s + 1$

5^{th} order PT

$k_5 s^5 + k_4 s^4 + k_3 s^3 + k_2 s^2 + k_1 s + 1$

$$k_2 = L_1(C_1 + C_2 + C_D) + L_2(C_2 + C_D)$$

$$k_3 = R_D C_D (L_1 C_1 + L_2 C_2 + L_1 C_2)$$

$$k_4 = L_1 L_2 C_1 (C_2 + C_D)$$

$$k_5 = L_1 L_2 C_1 C_2 C_D R_D$$

4th order filter - Transferfunction

5th order PT in its normalized form:

$$G_{PT}(s) = \frac{1}{(1 + a_1 \frac{s}{\omega_0}) \cdot (1 + a_2 \frac{s}{\omega_0} + b_2 \frac{s^2}{\omega_0^2}) \cdot (1 + a_3 \frac{s}{\omega_0} + b_3 \frac{s^2}{\omega_0^2})} \quad (11)$$

Optimisation methods:

	a_1	a_2	b_2	a_3	b_3
Butterworth	1.0000	1.6180	1.0000	0.6180	1.0000
Bessel	0.6656	1.1402	0.4128	0.6216	0.3245
Critical damping	0.3856	0.7712	0.1487	0.7712	0.1487

4th order filter - Transferfunction

By expanding (11) and comparing the coefficients with (10) we get:

$$G_{PT}(s) = \frac{1}{\frac{a_1 b_2 b_3}{\omega_0^5} s^5 + \frac{(b_2 b_3 + a_1 a_2 b_3 + a_1 a_3 b_2)}{\omega_0^4} s^4 + \frac{(a_2 b_3 + a_3 b_2 + a_1 b_3 + a_1 a_2 a_3 + a_1 b_2)}{\omega_0^3} s^3 \dots} \\ \dots \\ \dots + \frac{(b_3 + a_2 a_3 + b_2 + a_1 a_3 + a_1 a_2)}{\omega_0^2} s^2 + \frac{(a_1 + a_2 + a_3)}{\omega_0} s + 1$$

$$k_1 = R_D C_D = \frac{a_1 + a_2 + a_3}{\omega_0} \quad (12a)$$

$$k_2 = L_1(C_1 + C_2 + C_D) + L_2(C_2 + C_D) = \frac{b_3 + a_2 a_3 + b_2 + a_1 a_3 + a_1 a_2}{\omega_0^2} \quad (12b)$$

$$k_3 = R_D C_D (L_1 C_1 + L_2 C_2 + L_1 C_2) = \frac{a_2 b_3 + a_3 b_2 + a_1 b_3 + a_1 a_2 a_3 + a_1 b_2}{\omega_0^3} \quad (12c)$$

$$k_4 = L_1 L_2 C_1 (C_2 + C_D) = \frac{b_2 b_3 + a_1 a_2 b_3 + a_1 a_3 b_2}{\omega_0^4} \quad (12d)$$

$$k_5 = L_1 L_2 C_1 C_2 C_D R_D = \frac{a_1 b_2 b_3}{\omega_0^5} \quad (12e)$$

4th order filter – selection of ω_0 and L_1

The 5 independent equations (12a....12e) contain 7 unknowns ($L_1, C_1, L_2, C_2, R_D, C_D$ and ω_0). Therefore we have the choice to select 2 of them (ω_0 and L_1) the remaining 5 depend on that selection.

For a given frequency ω_B well in the blocking area ($\omega_B \gg \omega_0$) we can define the desired attenuation G_B . In the blocking area the highest order terms of both the numerator and denominator in equation (10) dominate, therefore (10) can be simplified to:

$$G_B = \frac{R_D C_D s}{L_1 L_2 C_1 C_2 R_D C_D s^5} = \frac{\frac{a_1 + a_2 + a_3}{\omega_0} s}{\frac{a_1 b_2 b_3}{\omega_0^5} s^5} = \frac{a_1 + a_2 + a_3}{a_1 b_2 b_3} \cdot \frac{\omega_0^4}{s^4} = \frac{a_1 + a_2 + a_3}{a_1 b_2 b_3} \cdot \frac{\omega_0^4}{\omega_B^4}$$

\downarrow \uparrow
 $(j)^4 = +1$

$$\omega_0 = \omega_B \cdot \sqrt[4]{\frac{G_B \cdot a_1 b_2 b_3}{a_1 + a_2 + a_3}} \quad (13)$$

Select L_1 according to ripple current requirements with (5) or (6)

4th order filter – Calculating filter elements

By solving the equation system (12a.....12e) we get:

$$L_2 = \frac{L_1}{(k_3 k_4 - k_2 k_5)(k_1 k_2 - k_3)} - 1 \quad (14a)$$

$$C_2 = \frac{k_5(k_1 k_2 - k_3)}{k_1(k_1 k_4 - k_5)(L_1 + L_2)} \quad (14b)$$

$$C_1 = \frac{k_5}{k_1 L_1 L_2 C_2} \quad (14c)$$

$$R_D = \frac{k_1 k_5}{C_2(k_1 k_4 - k_5)} \quad (14d)$$

$$C_D = \frac{k_1}{R_D} \quad (14e)$$

with

$$k_1 = \frac{a_1 + a_2 + a_3}{\omega_0}$$


$$k_2 = \frac{b_3 + a_2 a_3 + b_2 + a_1 a_3 + a_1 a_2}{\omega_0^2}$$

$$k_3 = \frac{a_2 b_3 + a_3 b_2 + a_1 b_3 + a_1 a_2 a_3 + a_1 b_2}{\omega_0^3}$$

$$k_4 = \frac{b_2 b_3 + a_1 a_2 b_3 + a_1 a_3 b_2}{\omega_0^4}$$

$$k_5 = \frac{a_1 b_2 b_3}{\omega_0^5}$$

4th order filter – Example 3

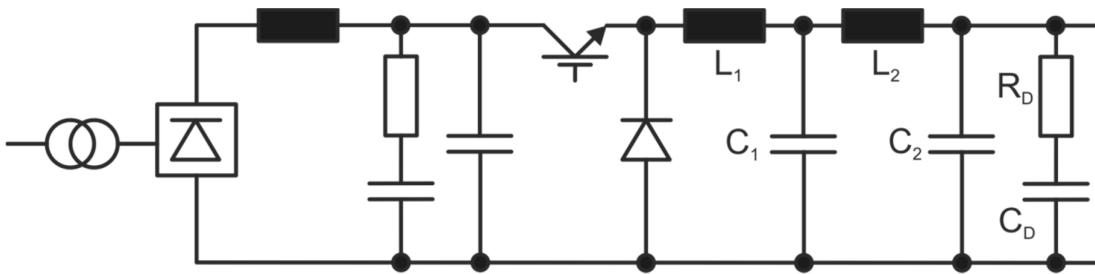

- DC-link voltage: 120V
- $f_s = 20\text{kHz}$
- $I_{\text{Out_max}} = 500\text{A}$
- $\Delta I_{L1} \leq 50\text{App.}$
- Attenuation: $G_B = 250$ @ $\omega_B = 2\pi \cdot 20\text{kHz}$

} Same premises as for example 2

Design a 4th order filter for all three given optimization methods and compare the results.

4th order filter – Example 3

Select L_1 to meet the ripple current requirement:

$$L_1 = \frac{V_{DC} \cdot 0.25}{f_s \cdot \Delta I_{L1}} = \frac{120V \cdot 0.25}{20\text{kHz} \cdot 50A} = 30\mu H \quad (5)$$

Select ω_0 to meet the attenuation requirement:

$$\omega_0 = \omega_B \cdot \sqrt[4]{\frac{G_B \cdot a_1 b_2 b_3}{a_1 + a_2 + a_3}} \quad (13)$$

Calculate the remaining filter elements

(14a....e)

4th order filter – Example 3

Results:

	Butterworth	Bessel	Critical damping
	$a_1 = 1.0000$ $a_2 = 1.6180$ $b_2 = 1.0000$ $a_3 = 0.6180$ $b_3 = 1.0000$	$a_1 = 0.6656$ $a_2 = 1.1402$ $b_2 = 0.4128$ $a_3 = 0.6216$ $b_3 = 0.3245$	$a_1 = 0.3856$ $a_2 = 0.7712$ $b_2 = 0.1487$ $a_3 = 0.7712$ $b_3 = 0.1487$
ω_B	$1.26 \cdot 10^5 \text{ s}^{-1}$ (20kHz)		
G_B	0.004 (-48dB)		
ω_0	$2.36 \cdot 10^4 \text{ s}^{-1}$ (3.8 kHz)	$1.38 \cdot 10^4 \text{ s}^{-1}$ (2.2 kHz)	$8.15 \cdot 10^3 \text{ s}^{-1}$ (1.3 kHz)
L_1	30 μH	30 μH	30 μH
L_2	57 μH	31 μH	17 μH
C_1	74 μF	90 μF	124 μF
C_2	7.9 μF	12 μF	16 μF
C_D	75 μF	168 μF	382 μF
R_D	1.83 Ω	1.04 Ω	0.62 Ω

4th order filter – Example 3


Maximum amplitude of resonance:

- Butterworth 8.6 dB
- Bessel 5.4 dB
- Critical damping 3.8 dB

Frequency, for -3 dB attenuation:

- Butterworth 5.5 kHz
- Bessel 5.0 kHz
- Critical damping 3.9 kHz

Attenuation: -48dB @ 20kHz

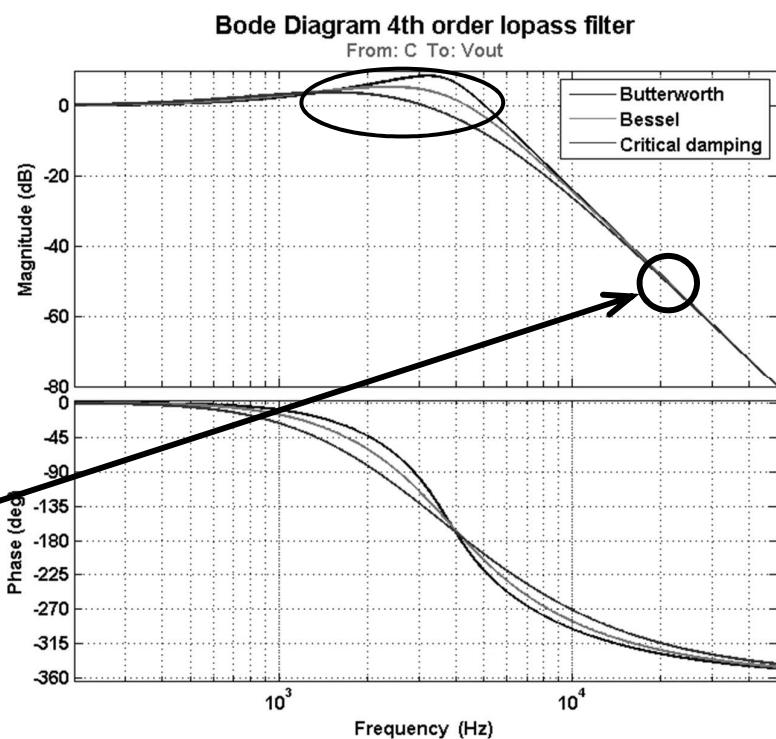

Comparison of different filter designs

Design 1
4th order

Acc. to example 3

Optimisation:
Bessel

$$L_1 = 30 \mu\text{H}$$

$$L_2 = 31 \mu\text{H}$$

$$C_1 = 90 \mu\text{F}$$

$$C_2 = 12 \mu\text{F}$$

$$C_D = 168 \mu\text{F}$$

$$R_D = 1.04 \Omega$$

$$f_0 = 2'200 \text{ Hz}$$

Design 2
2nd order

Acc. to example 2

Optimisation:
Bessel

$$L_1 = 30 \mu\text{H}$$

$$C_1 = 528 \mu\text{F}$$

$$C_D = 2'600 \mu\text{F}$$

$$R_D = 0.18 \Omega$$

$$f_0 = 573 \text{ Hz}$$

Design 3
2nd order

Acc. to example 2
but $L_1 = 100 \mu\text{H}$

Optimisation:
Bessel

$$L_1 = 100 \mu\text{H}$$

$$C_1 = 158 \mu\text{F}$$

$$C_D = 790 \mu\text{F}$$

$$R_D = 0.62 \Omega$$

$$f_0 = 573 \text{ Hz}$$

Design 4
2nd order

Acc. to example 2
but $L_1 = 100 \mu\text{H}$
and $G_B = 0.01$

Optimisation:
Bessel

$$L_1 = 100 \mu\text{H} \\ +64\%$$

$$C_1 = 63 \mu\text{F} \\ +42\%$$

$$C_D = 320 \mu\text{F}$$

$$R_D = 0.98 \Omega$$

$$f_0 = 907 \text{ Hz}$$


R. Künzi Power Filter Design CAS 2014 10.05.2014

31


Comparison of different filter designs

Bode Plots of different filter designs

From: C To: Vout

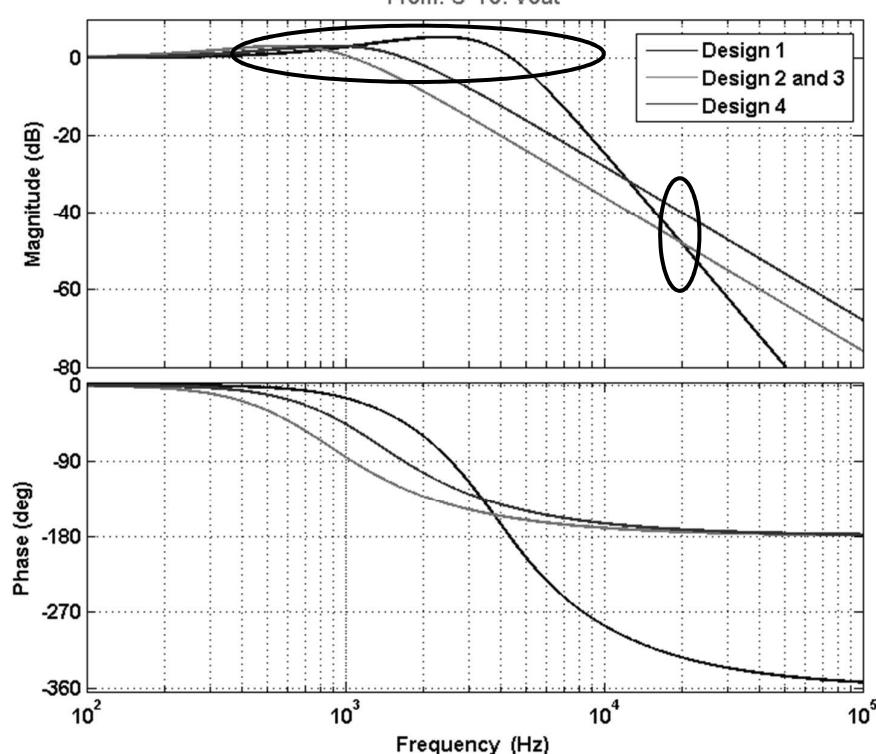

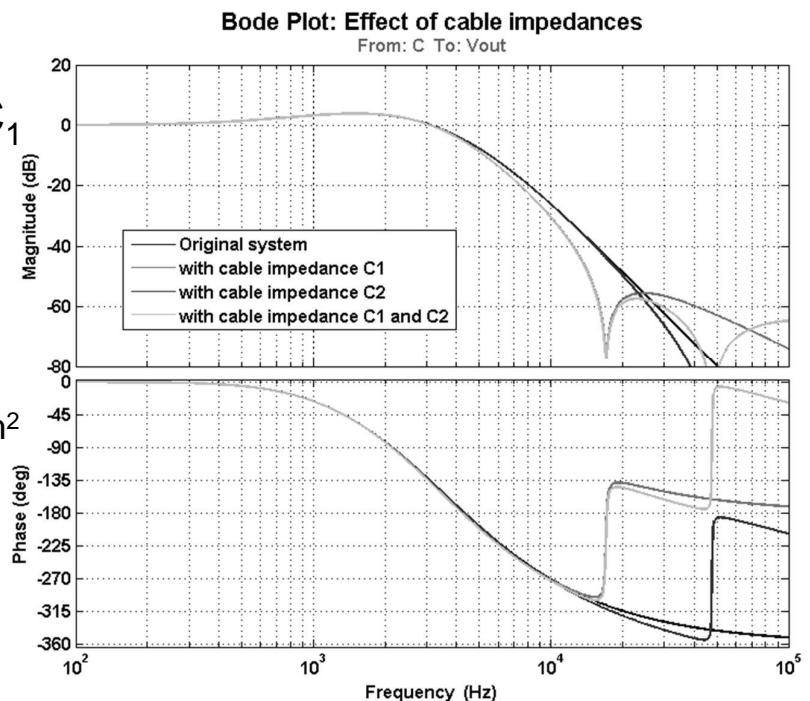- Effect of a 0.5m long wire 16mm^2 (wiring of C_1 and C_2)
 - Skin Effect
 - Skin depth in Cu @ 20kHz: 0.5mm
 - Reduces the effective cross section to 6.3 mm^2
 - Wire resistance @ 20kHz: $1.4\text{m}\Omega$
 - Wire inductance is approx. $0.5\mu\text{H}$



To be avoided !

Practical Aspects – low inductive setup



Life time of electrolytic capacitors


The useful life time of an electrolytic capacitor depends very much on the ripple current and the ambient temperature.

C_R 100 Hz 20 °C μF	Case dimensions $d \times l$ mm	ESR_{typ} 100 Hz 20 °C	Z_{\max} 10 kHz 20 °C	$I_{AC,\max}$ 100 Hz 40 °C	$I_{AC,R}$ 100 Hz 85 °C	$I_{AC,R}(B)$ 100 Hz 85 °C	Ordering code (composition see below)
$V_R = 200 \text{ V DC}$							
3300	51.6 × 80.7	40	48	21	7.9	15.3	B435*4E2338M0##
4700	51.6 × 105.7	29	35	27	10.1	17.6	B435*4E2478M0##
4700	64.3 × 80.7	29	35	27	10.0	18.6	B435*4F2478M0##
6800	64.3 × 105.7	21	25	34	12.6	22.0	B435*4E2688M0##
8200	76.9 × 105.7	17	20	41	15.2	26.8	B435*4E2828M0##
10000	76.9 × 105.7	14	17	47	17.4	32.8	B435*4E2109M0##
15000	76.9 × 143.2	8	10	57	25.6	43.6	B435*4E2159M0##
22000	91.0 × 144.5	5	6	80	35.9	63.6	B435*4E2229M0##

- Nominal ripple current at
 - nominal frequency (100Hz) and
 - nominal capacitor temperature (85°C).
 - *17.4A in our example*

Life time of electrolytic capacitors

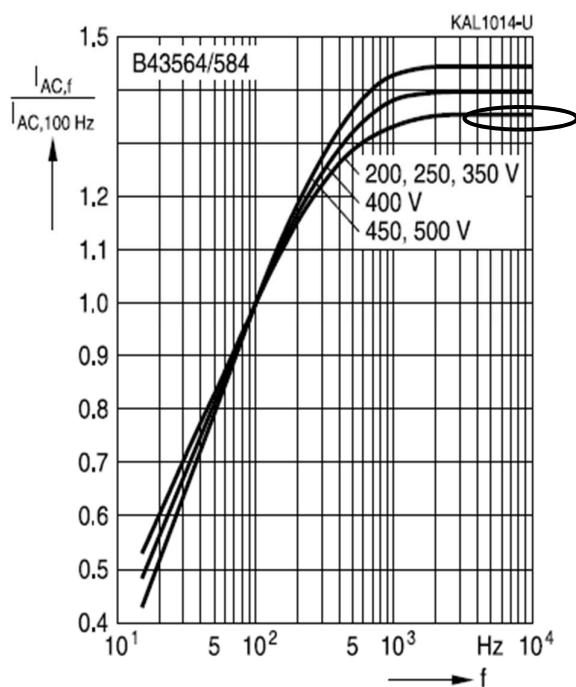Frequency factor of permissible ripple current I_{AC} versus frequency f



Apply frequency factor:


For 10kHz a current factor of 1.35 is applicable
→ 23.5A @ 10kHz

Life time of electrolytic capacitors

Determine the allowed ripple current for a desired useful life and T_a :

For 25'000h (3 years)
and $T_a = 50^\circ\text{C}$,
 $\rightarrow 2.6 * 23.5\text{A} = 61\text{A}$

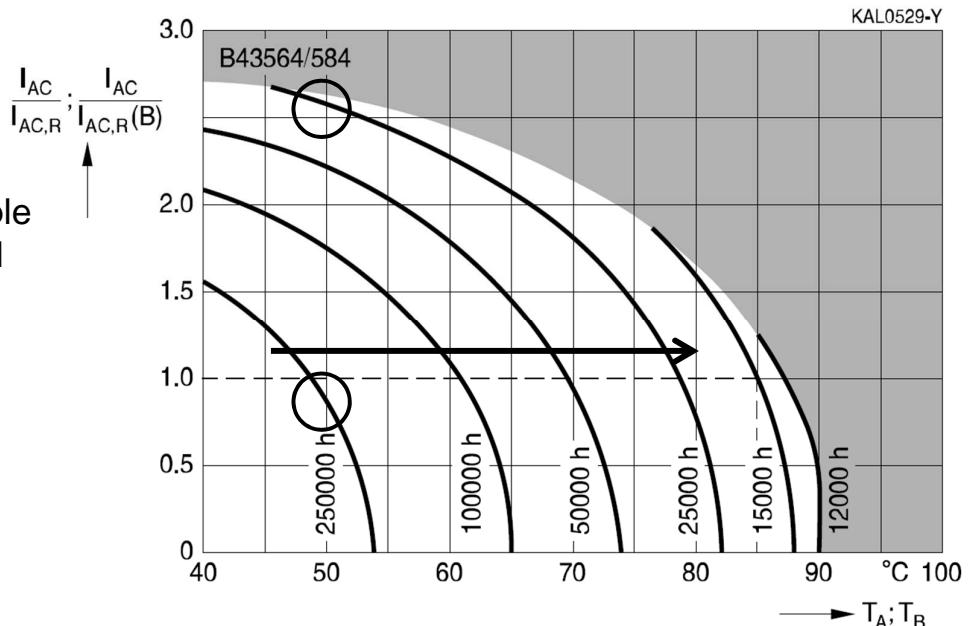For 250'000h (30 years)
and $T_a = 50^\circ\text{C}$
 $\rightarrow 0.85 * 23.5\text{A} = 20\text{A}$



The useful life time dramatically decreases at higher ambient temperatures!

Thank you for your attention

References

- U. Tietze, Ch. Schenk; Halbleiter-Schaltungs-Technik, 12. Auflage, Pages 815ff
- Epcos, Datasheet, Capacitors with screw terminals Type B43564, B43584, November 2012

Questions?

