

# Switched Mode One-Quadrant Power Converters

R. Petrocelli




## Summary


- Power Electronics. Basics definitions and rules
- Basic DC-DC Power Converters
- Control of DC-DC Power Converters
- Derived Topologies
- Other Issues




# Power converter Definition

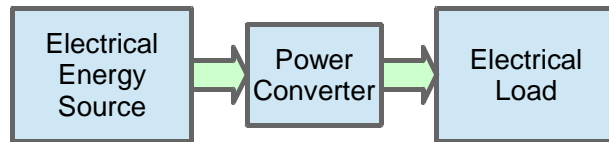



# Classification of Power converters

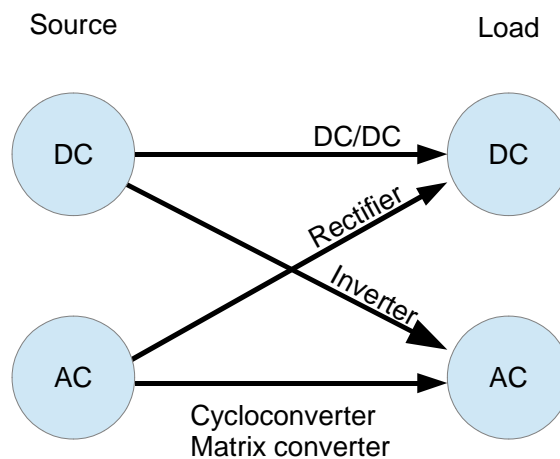


# One-Quadrant Definition

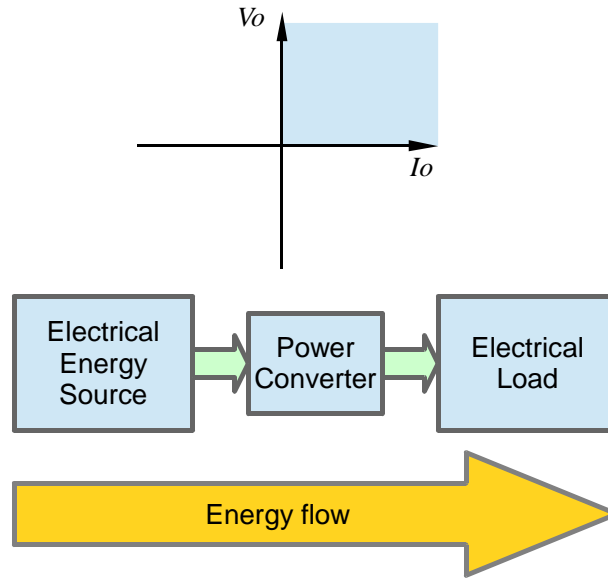
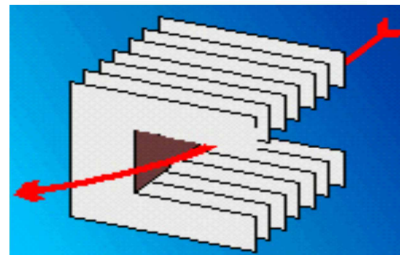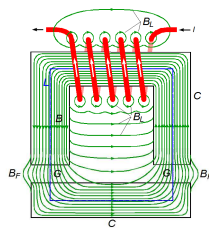
# One-Quadrant Power Converter in Particle Accelerators



## ■ 2n-pole:

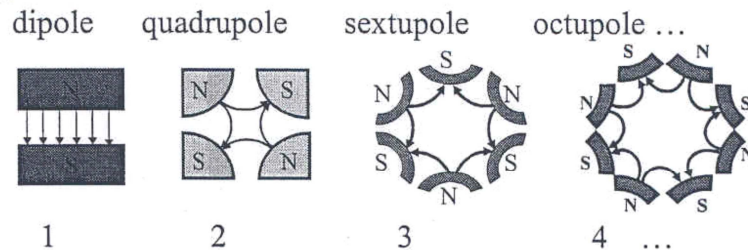

# Power Electronics



## Basic Definition and Rules

- Sources Definition
- Basic Rules
- Interconnection Rules

## Type of Sources
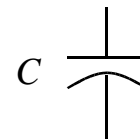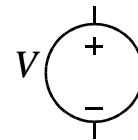
### Voltage Source


- A voltage source is able to impose a voltage regardless of the current flowing through it.
- In a more open sense, if the voltage across an element can not have discontinuities in time due to the current flowing through it



## Source Type
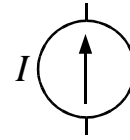
### Current Sources

A current are able to impose current regardless the voltage across its terminals.




Similar to the voltage sources this can be extended to elements which current can not have discontinuities.



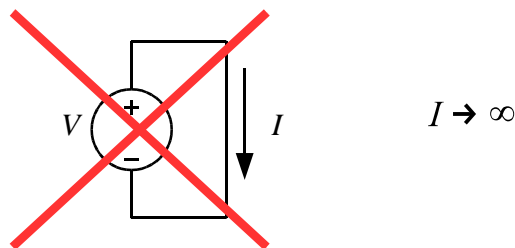
## Basic Rules

- Rule 1: A voltage source must never be short-circuited



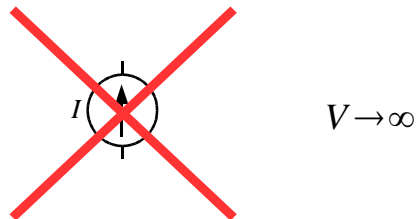
## Basic Rules

- Rule 2: A current source must never be open-circuited




## Basic Rules

- Interconnection Rules

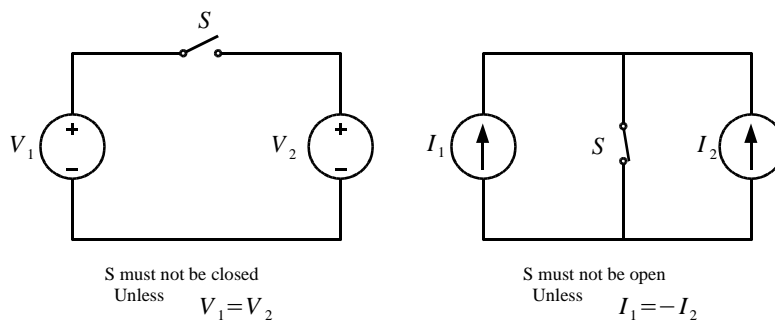

## Interconnection Rules

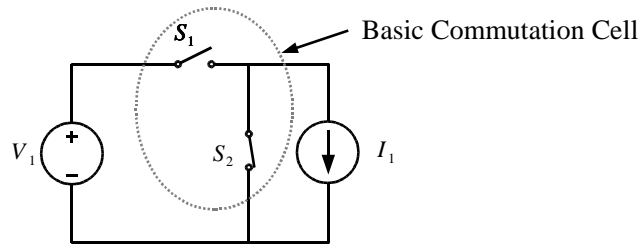


$S_1$	$S_2$	
<i>open</i>	<i>open</i>	Not allowed
<i>open</i>	<i>closed</i>	Allowed
<i>closed</i>	<i>open</i>	Allowed
<i>closed</i>	<i>closed</i>	Not allowed

## Basic DC-DC Converter

- Chopper
- Buck Converter
- Boost Converter
- Buck-Boost Converter


# DC Chopper

- Resistive Load

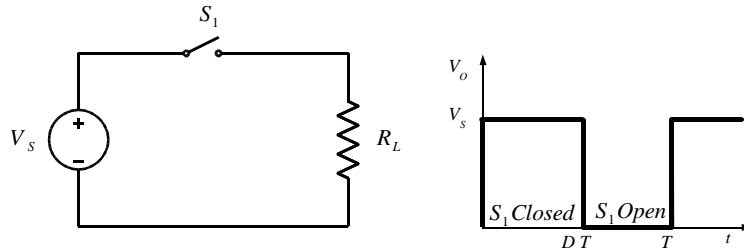

# DC Chopper



- Inductive Load

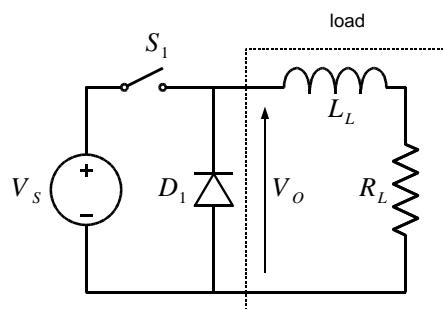

- Application: Motor control




# Chopper Waveforms

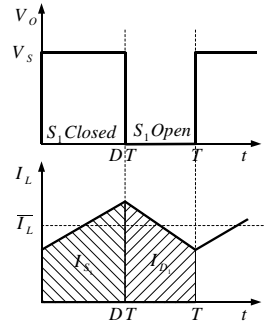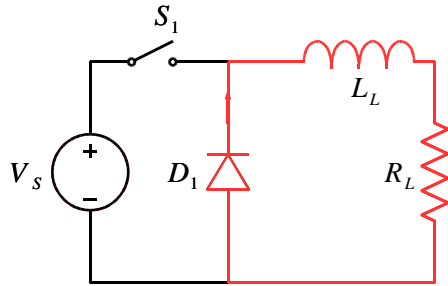


$$\bar{I}_L = \frac{V_S D}{R_L}$$

# Buck Converter

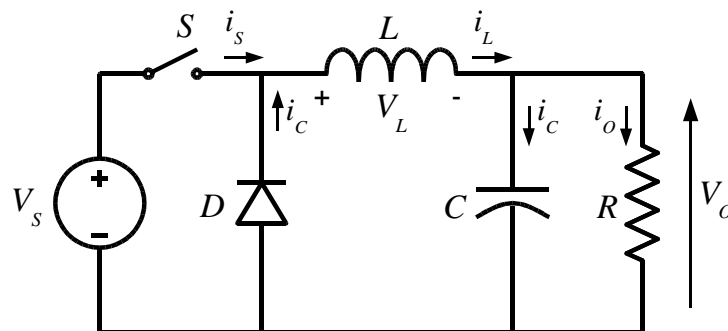


# Buck Converter

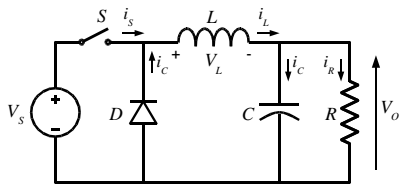


Faraday Law :  
volt-second product of the inductor  
voltage should be zero for steady-  
state operation

$$(V_s - V_o)DT = V_o(1 - D)T$$

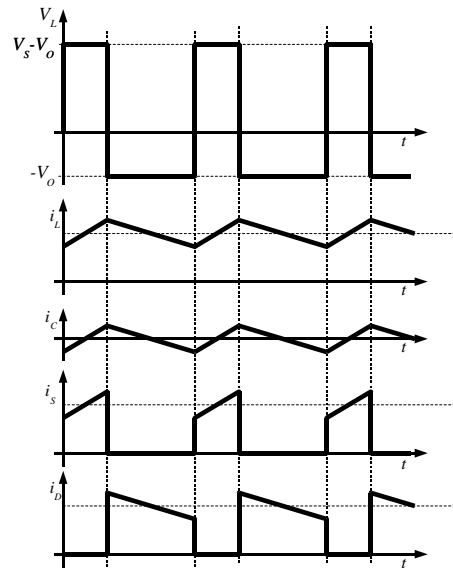

# Output-Input Voltage Ratio

$$M_v \equiv \frac{V_o}{V_s} = D$$

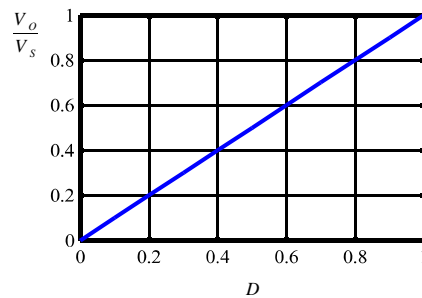

$$L_b = \frac{(1-D)R}{2f}$$



Inductance for boundary between CCM and DCM

$$C_{min} = \frac{(1-D)V_o}{8V_r L f^2}$$

Minimum capacitance for an output voltage ripple  $V_r$





## Continuous and Dis-Continuous Mode

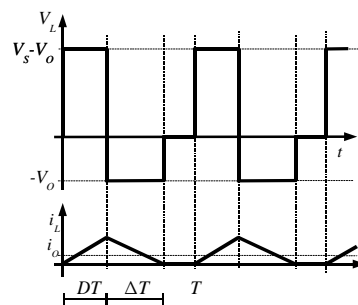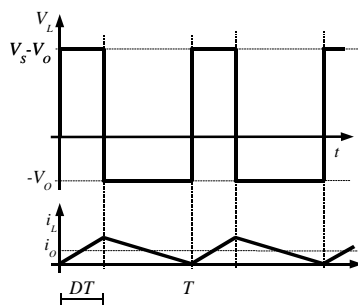

# CCM and DCM Boundary

$$i_{OB} = \frac{DT}{2L} (V_S - V_O) = \frac{TV_S}{2L} (D - D^2)$$

$$I_{OB_{MAX}} = \frac{TV_S}{8L}$$

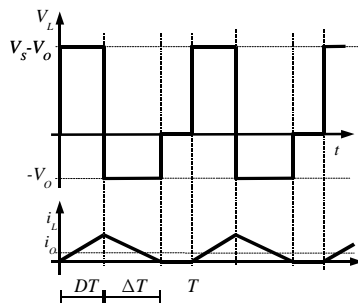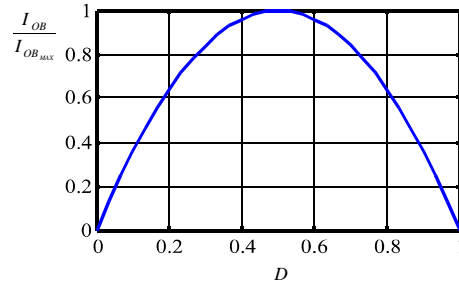

$$(V_S - V_O)DT = V_O \Delta T$$

$$\frac{V_O}{V_S} = \frac{D}{(D + \Delta)}$$


$$I_O = \frac{I_{L_{peak}} (D + \Delta) T}{2T}$$

$$I_{L_{peak}} = \frac{V_O \Delta T}{L}$$

$$I_O = 4 I_{OB_{MAX}} D \Delta$$
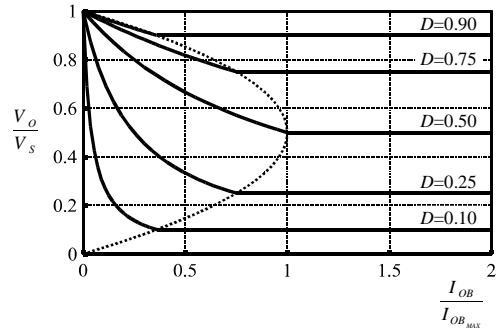
## Output-Input Voltage Ratio in DCM


$$\frac{V_o}{V_s} = \frac{D^2}{\left(D^2 + \frac{1}{4} \frac{I_o}{I_{OB\_MAX}}\right)}$$




## Buck Converter

- Widely used. Even for high power converters
- Advantages:
  - Simple
  - Linear output-input voltage ratio. It makes easier the control.
  - Smooth output current.
- Disadvantages:
  - Discontinuous input current
  - No isolation.

# Boost Converter

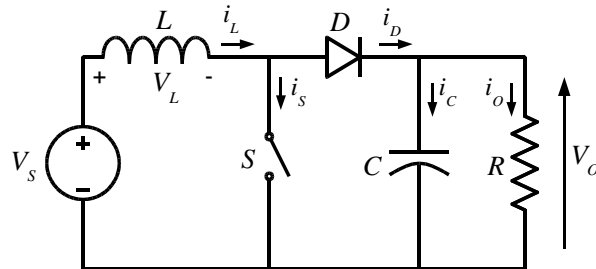

# Boost Converter

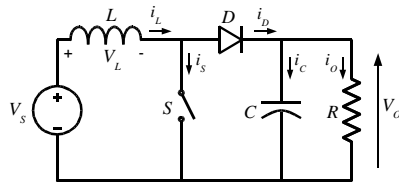


Faraday Law :

$$V_s DT = (V_o - V_s)(1 - D)T$$

$$M_v \equiv \frac{V_o}{V_s} = \frac{1}{1 - D}$$


$$L_b = \frac{(1 - D)^2 DR}{2f}$$

$$C_{min} = \frac{DV_o}{V_r R f}$$

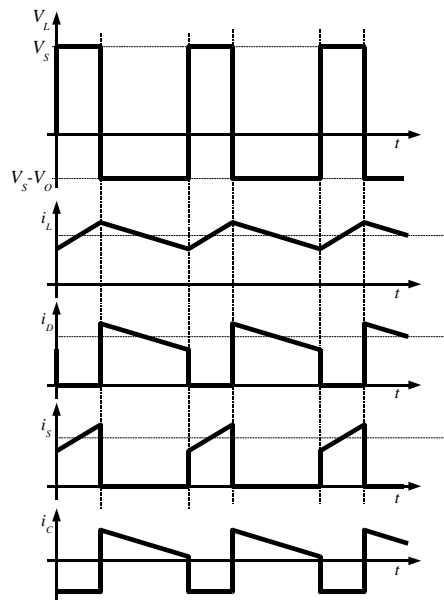
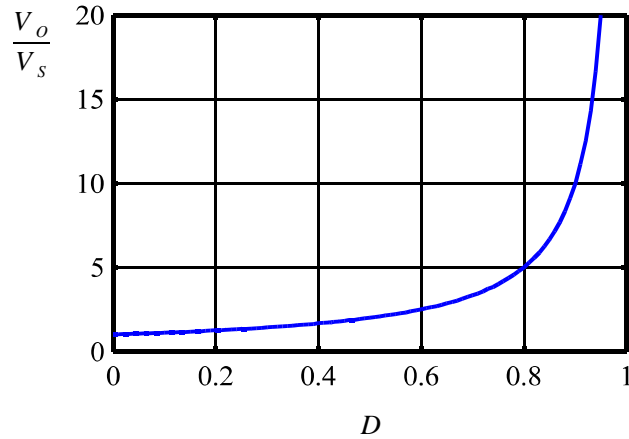
## Boost Converter: Output-Input Voltage Ratio



$$M_v \equiv \frac{V_o}{V_s} = \frac{1}{1-D}$$



## Boost Converter

- Output voltage higher than input voltage
  - Advantages:
    - Simple
    - Smooth input current.
  - Disadvantages:
    - Discontinuous output current. Stress the output capacitor
    - No isolation.
-


# Buck-Boost Power Converter

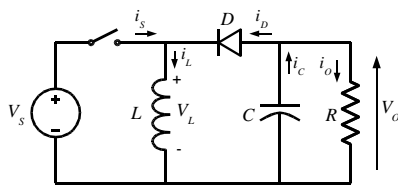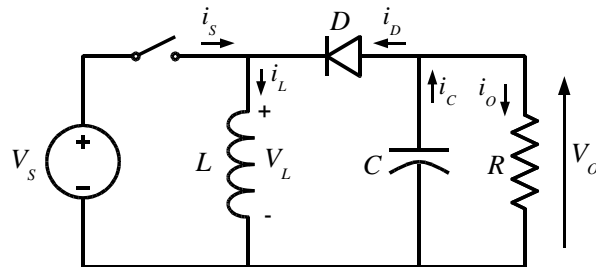

$$V_s T D = -V_o (1 - D) T$$

$$M_v \equiv \frac{V_o}{V_s} = -\frac{D}{(1 - D)}$$


$$L_b = \frac{(1 - D)^2 D R}{2 f}$$

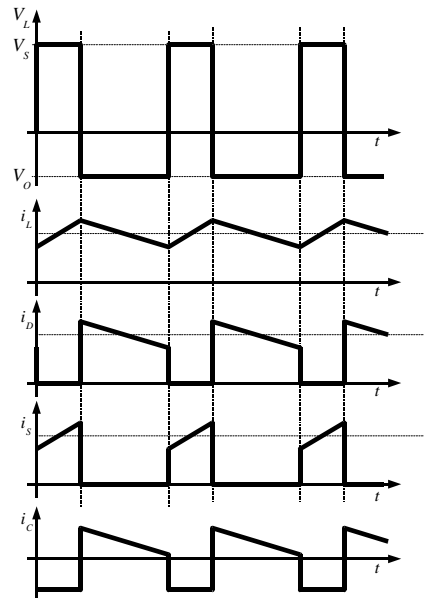


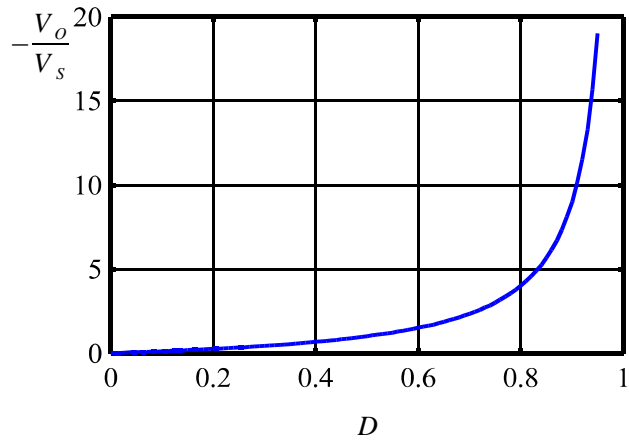
## Buck-Boost Converter: Output-Input Voltage Ratio

$$M_v \equiv \frac{V_o}{V_s} = -\frac{D}{(1-D)}$$



## Buck-Boost Converter

Reverse voltage polarity

- Advantages:
  - Simple
  - Step-down and step-up
- Disadvantages:
  - Discontinuous input and output current.
  - No isolation.

# Control of DC-DC Power Converters

- Regulation
- Pulse-Width Modulation. (PWM)
- Current Mode
- Variable Structure Control



# Control of Switched Mode DC-DC Power Converter

## Switching function.

Definition:


The switching function,  $S(t)$ , has a value of 1 when the corresponding physical switch is *on* and 0 when it is *off*.

Switching functions are discrete-valued functions of time, and control of switching devices can be represented with them.


$$s(t) = \begin{cases} 1 & \text{when the switch is on} \\ 0 & \text{when the switch is off} \end{cases}$$



# Power Converter Block Diagram

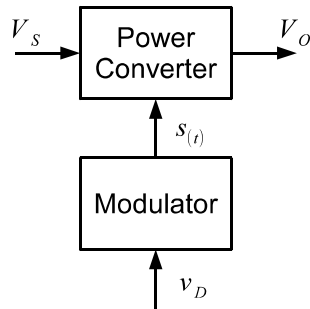


# Regulation – Feedback

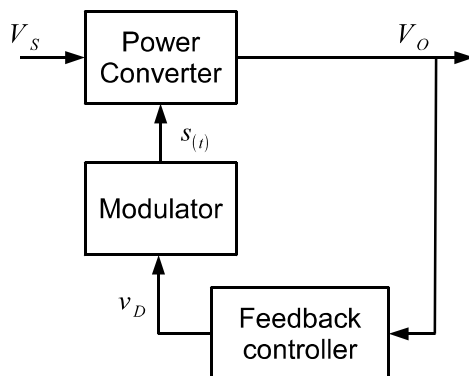


- Close loop, the output voltage is sensed and the feedback controller acts to get the wished value.
- Stability issues

## Regulation – Feed-Forward

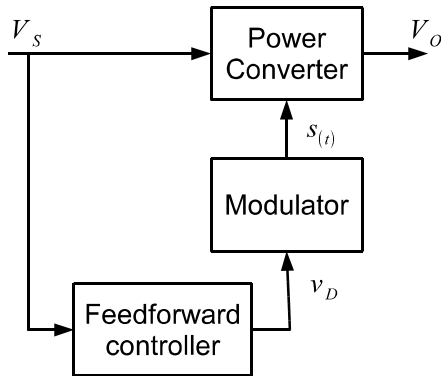


- It is very fast. Perturbations do not have to reach the output in order to be compensated.
- It need a good model of the converter in order to design the controller.
- Usually is used together with a feedback loop.

## Constant Frequency PWM

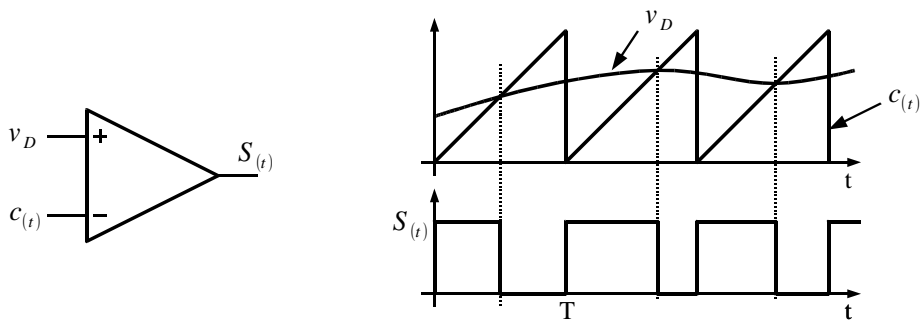

# Variable Frequency PWM



constant off-time, variable on-time

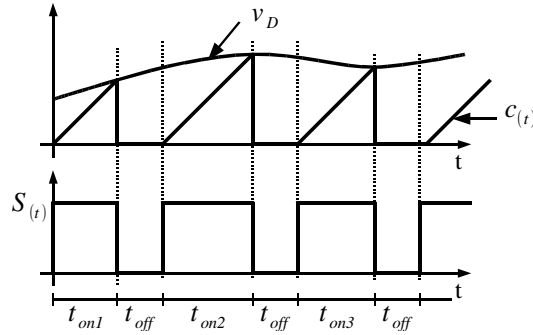

constant on-time, variable off-time



# Current Mode Control (CMC)

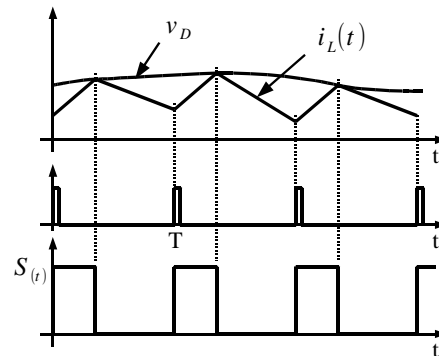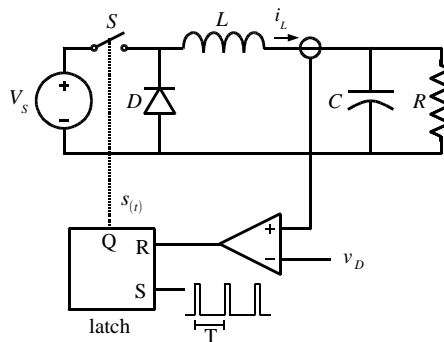

# Current Mode Control

The CMC controls the inductor current. An outer control loop is needed for output voltage regulation.

Advantages:

- Simple
- Low cost
- Easy input voltage feed-forward

Disadvantages

- Sub-harmonic oscillation for  $D > 0.5$ . An slope compensation solves this problem.



# Variable Structure Control

It is a nonlinear control which generates the switching function according to the state-space variables of the system.

Advantages:

- Low sensitivity to plant parameter uncertainty
- Robustness


Disadvantages

- Chattering
- Variable frequency



# Variable Structure Control


## Hysteresis control

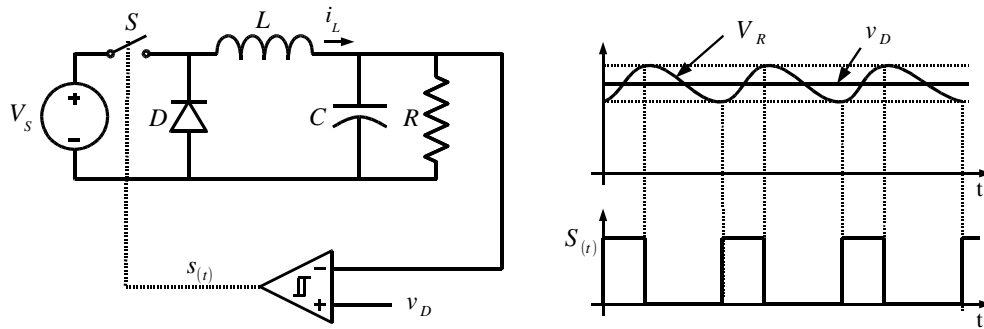


# Derived Topologies

- Half Bridge Converter
- Push-Pull Converter
- Full Bridge Converter
- Forward Converter
- Flyback Converter
- Ćuk Converter
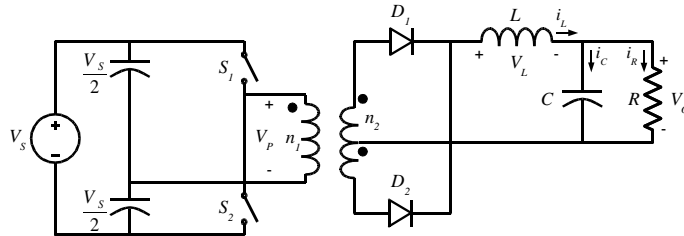
## Derived Topologies Half Bridge Converter



## Transformer Input Waveform

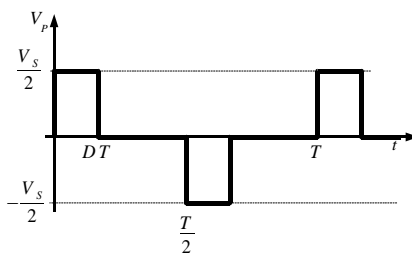


- Volt-second product over a period must be zero to avoid transformer saturation



## Derived Topologies


### Push-Pull Converter

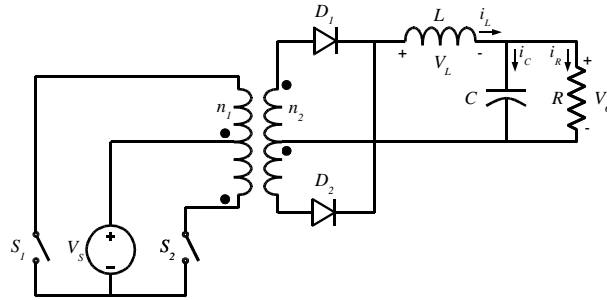

$$M_V \equiv \frac{V_o}{V_s} = 2D \frac{n_2}{n_1}$$

## Derived Topologies


### Full Bridge Converter

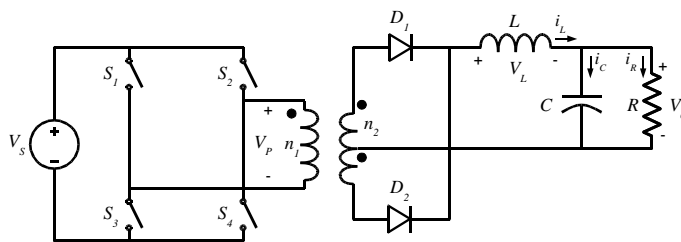

$$M_V \equiv \frac{V_o}{V_s} = 2D \frac{n_2}{n_1}$$

## Derived Topologies

### Forward Converter

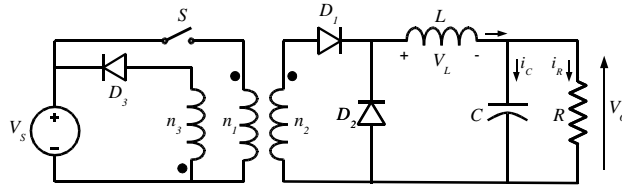


$$M_V \equiv \frac{V_o}{V_s} = D \frac{n_2}{n_1}$$

$$n_1 D \leq n_3 (1 - D)$$

## Derived Topologies


### Flyback Converter

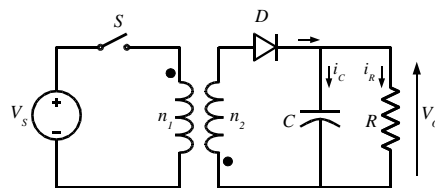

$$M_V \equiv \frac{V_o}{V_s} = \frac{n_2}{n_1} \frac{D}{1 - D}$$

## Derived Topologies

### Ćuk Converter

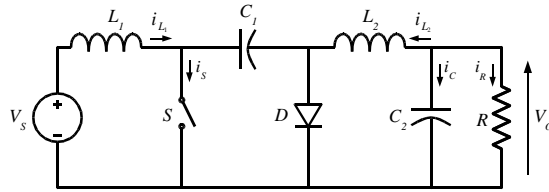

$$I_{L_2} D T = I_{L_1} (1 - D) T$$

$$P_{IN} = V_s I_{L_1} = -V_o I_{L_2} = P_{OUT}$$

$$M_V \equiv \frac{V_o}{V_s} = \frac{D}{(1 - D)}$$

## Derived Topologies

### Ćuk Converter

There is also an isolated version.

The inductors can be integrated using only one magnetic core

Advantage:

- Smooth input and output current

Disadvantage:

- More components

## Other Issues


- Synchronous Rectification
- Interleaved Converters
- Hard Switching, Snubbers and Soft Switching
- DC-DC Resonant Converters
- References and Further Readings

## Synchronous Rectification


Conduction losses  $P_D = V_F I_O (1 - D)$   $V_F =$  diode forward voltage drop

$$\eta = \frac{V_O I_O}{V_O I_O + V_F I_O (1 - D)} = \frac{V_O}{V_O + V_F (1 - D)}$$

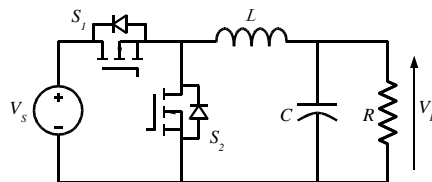
Efficiency is low for low output voltage power converters




# Power Losses in Diode and MOSFET

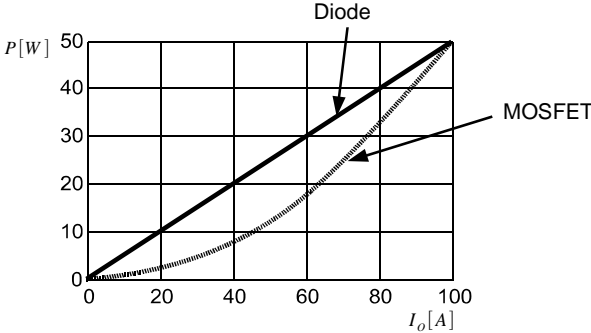


# Interleaved Converters

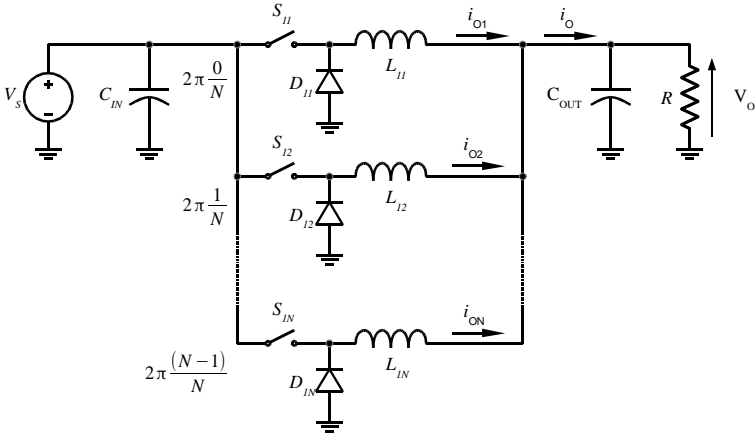

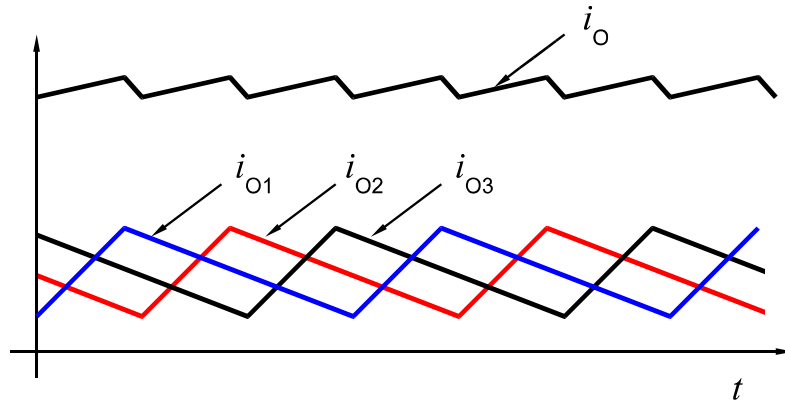
## Interleaved Converters: Output Current






## Normalized Output Current Ripple

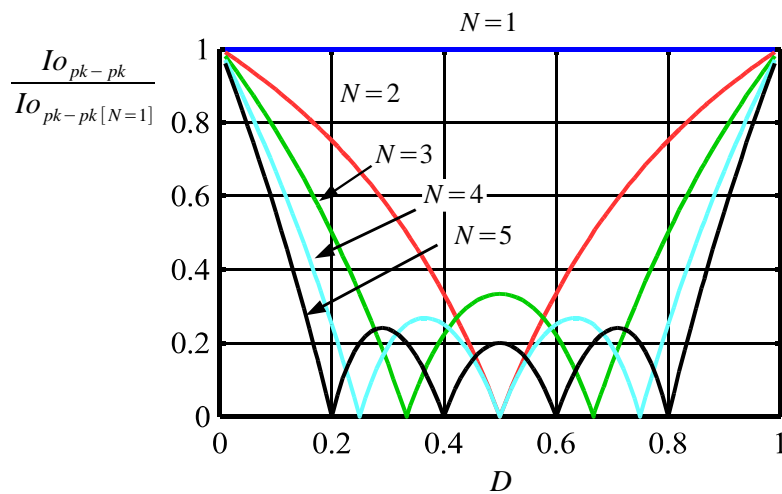




# Normalized Input Capacitor RMS Current

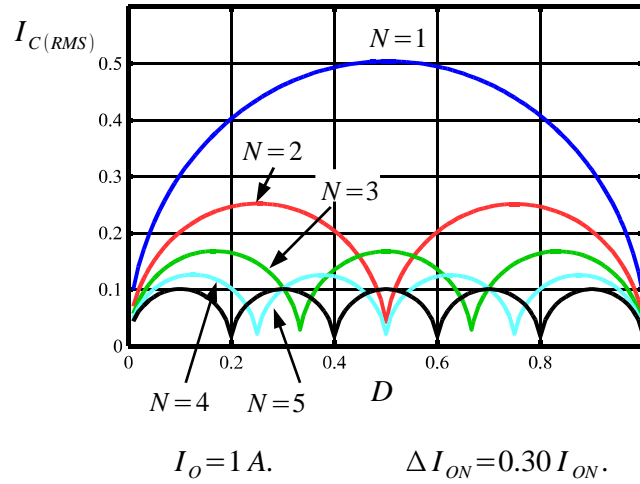



# Hard Switching

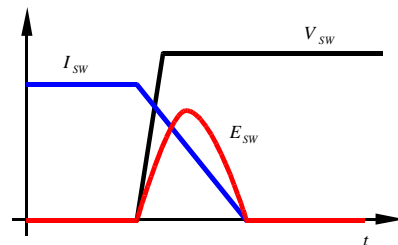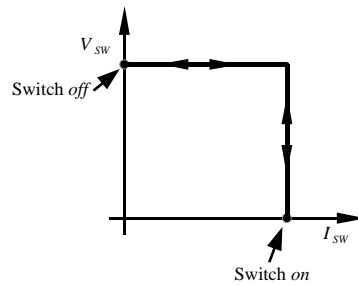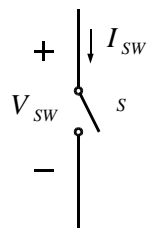

# Snubbers

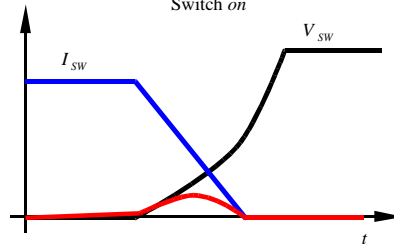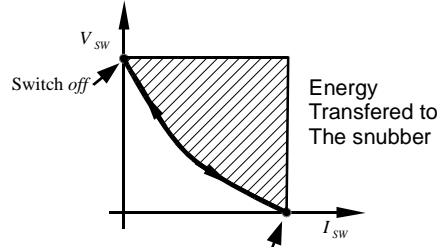
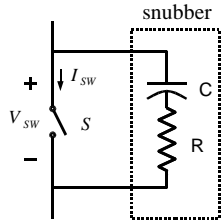


# Soft Switching

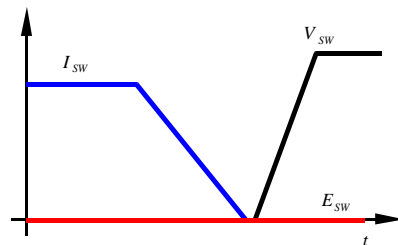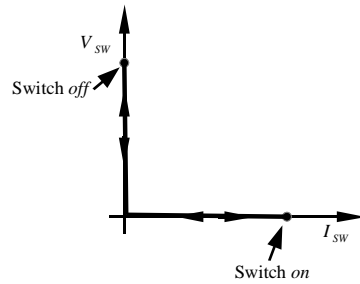




# Soft Switching

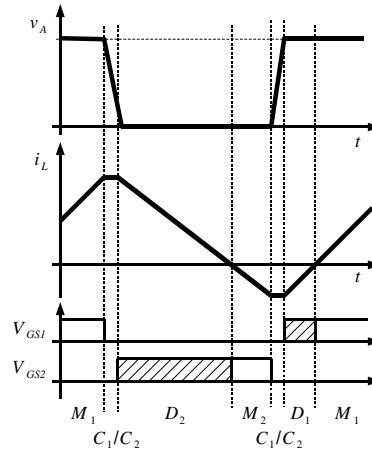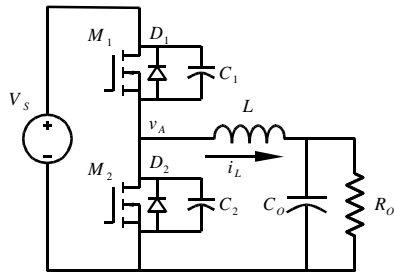


# DC-DC Resonant Converters

Resonant Converters operates by applying a square voltage or current generated by switches to a resonant circuit.

- Series resonant converter

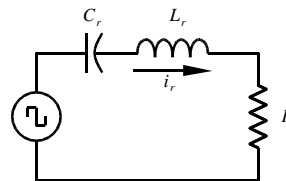

- Parallel resonant converter

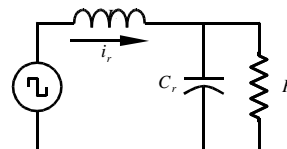


The converters operate at frequencies close to the resonant frequency.


The energy transferred to the load is controlled by changing the operating frequency.
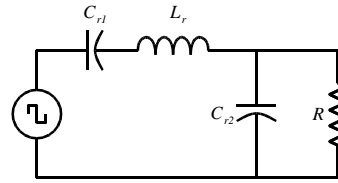
# LCC and LLC Resonant Converters


- LCC resonant converter
  - Disadvantages: two capacitors



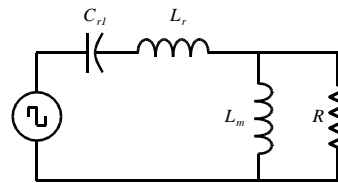
- LLC resonant converter
  - Advantage: the two inductances can be integrated into one magnetic component



# LLC Resonant Converters

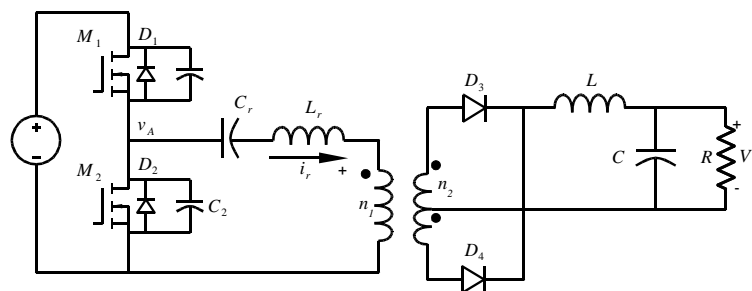

## LLC Converter Waveforms. ZVS

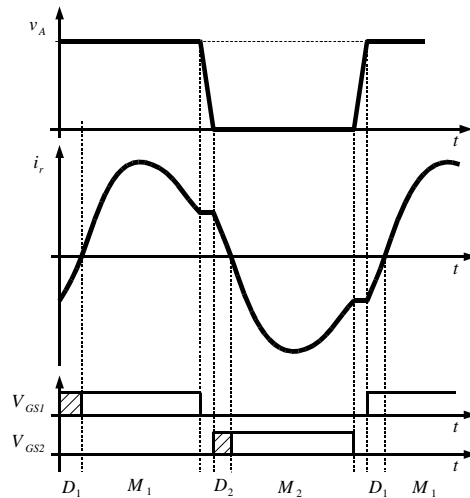

## DC-DC Resonant Converters

- High Efficiency – Soft switching operation
- High operating frequency – small reactive components
- High power density
  
- More complex control
- Stress in semiconductors (large voltages and currents)

# References and Further Reading

- MOHAN, Ned; UNDELAND, TORE M.; ROBBINS, W. P. Power electronics: converters, applications and design, 1995. 1997. ISBN: 978-0471226932
- RASHID, Muhammad H. (ed.). Power electronics handbook. Academic Pr, 2001.. ISBN: 978-0123820365
- BORDRY, F. Power converters: definitions, classification and converter topologies. CAS CERN Accelerator School and CLRC Daresbury Laboratory. 2004.
- SHEEHAN, Robert; ANATOLE, Hilton. Understanding and Applying Current-Mode Control Theory. En Power Electronics Technology Exhibition and Conference, Dallas. 2007. p. 1-26.
- HUNG, John Y.; GAO, Weibing; HUNG, James C. Variable structure control: a survey. Industrial Electronics, IEEE Transactions on, 1993, vol. 40, no 1, p. 2-22.
- MAPPUS, Steve. Synchronous rectification for Forward Converters. Fairchild Semiconductor Power Seminar 2010-2011.
- HEGARTY, T. Benefits of multi-phasing buck converters. EE Times-India, 2007, p. 1-4.
- HUANG, Hong. Designing an LLC resonant half-bridge power converter. En TI Power Supply Design Seminar SEM1900. 2010.



# Thank You !

